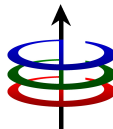



ECE 113: Communication Electronics

Meeting 7: Resonant Circuits II

February 12, 2019



Series RL Circuit

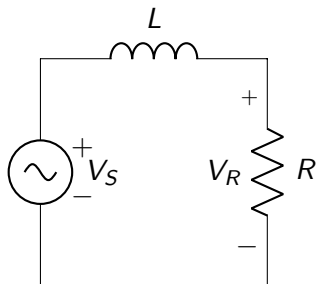


- Example of low pass filter
- Determine the cutoff frequency

- $|H(\omega)|_{dB} = -3dB$


$$\frac{R}{\sqrt{R^2 + \omega^2 L^2}} = \frac{1}{\sqrt{2}}$$

- $\omega_{cutoff} = \frac{R}{L}$

Low Pass Series RL Response

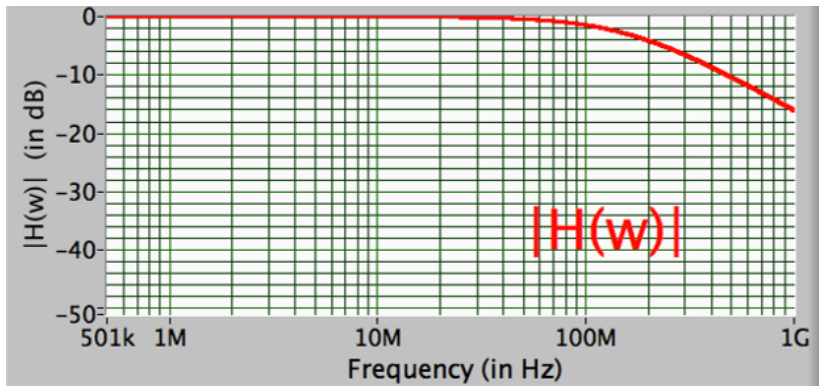

Series RC Circuit

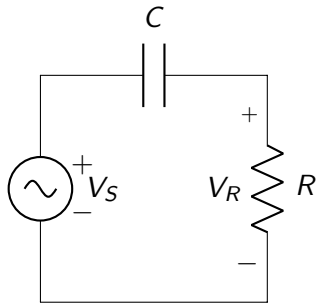


- Example of high pass filter
- Determine the cutoff frequency

- $|H(\omega)|_{dB} = -3dB$


$$\frac{\omega RC}{\sqrt{1 + \omega^2 R^2 C^2}} = \frac{1}{\sqrt{2}}$$

- $\omega_{cutoff} = \frac{1}{RC}$

High Pass Series RC Response

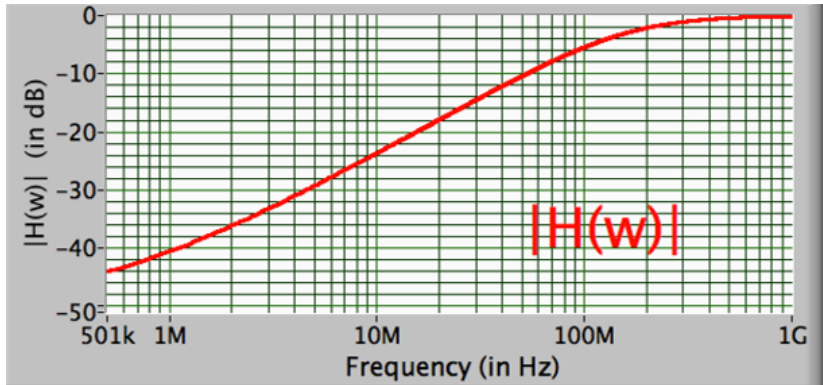

Series RLC Circuit

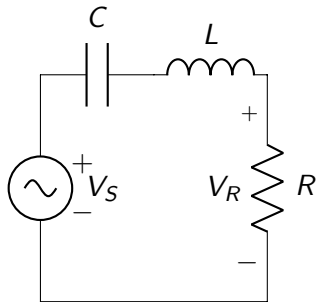

- Resonant frequency

$$\omega_o = \frac{1}{\sqrt{LC}}$$


- Example of band pass filter
- Determine the cutoff frequency

- $|H(\omega)|_{dB} = -3dB$

$$\frac{R}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} = \frac{1}{\sqrt{2}}$$

- $\omega_{Hcutoff} = \frac{R}{2L} + \sqrt{(\frac{R}{2L})^2 + \frac{1}{LC}}$
 - $\omega_{Lcutoff} = -\frac{R}{2L} + \sqrt{(\frac{R}{2L})^2 + \frac{1}{LC}}$

Band Pass Series RLC Response

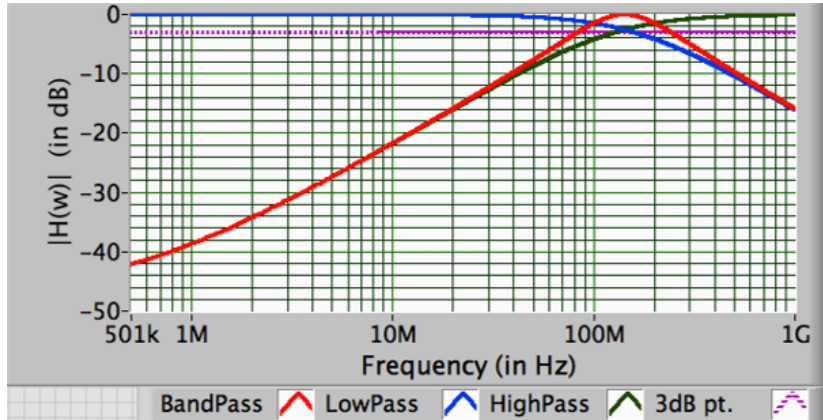


Loaded Q

- Assumptions in RLC resonant circuits
 - Ideal reactive elements (Lossless L & C)
 - Ideal resistive elements (R without parasitics)
 - Voltage source with zero source resistance
 - No load impedance
- Loaded Q takes into account actual "in-circuit" conditions


Loaded Q in Parallel LC Circuit

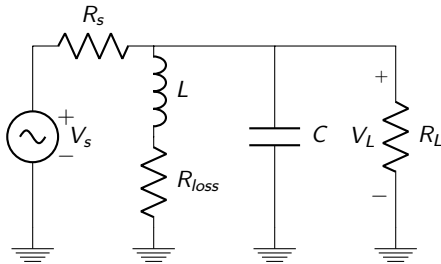- C - ideal (lossless) capacitor
- L - lossy inductor
- R_{loss} - DC resistance of L
- R_s - source resistance of V_s
- R_L - load resistance



Effects of Source Impedance on Circuit Q

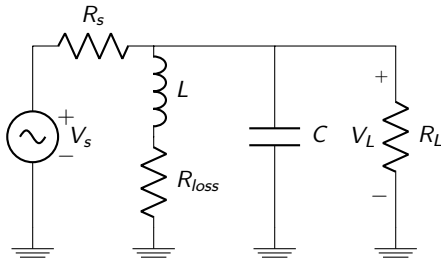- $C = 25\text{pF}$
- $L = 50\text{nH}$
- $R_{\text{loss}} = 0\Omega$ (lossless L)
- $R_s = 50\Omega$
- $R_L = \infty$ (no load)




- Resonant Frequency


$$f_o = \frac{1}{2\pi\sqrt{LC}} = 142.35\text{MHz}$$

- Circuit Q

$$Q = R_s \sqrt{\frac{C}{L}}$$

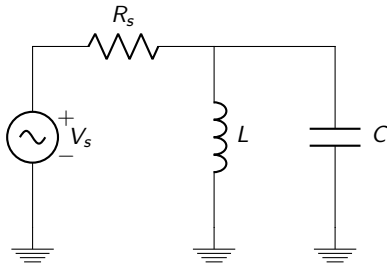


Effects of R_s on Circuit Q

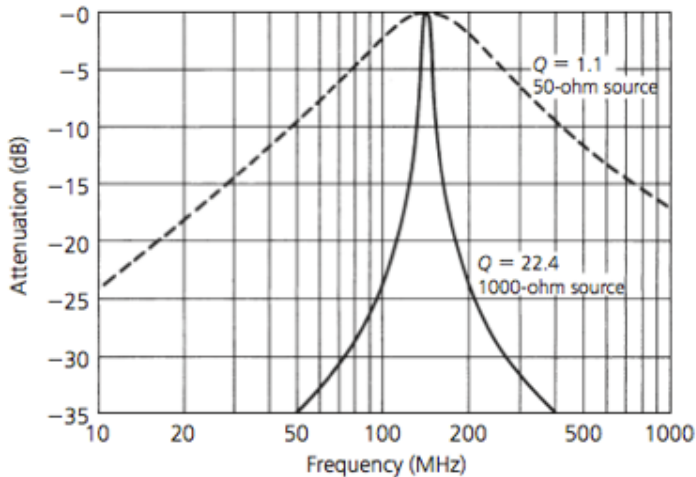


Equivalent Circuit Approach

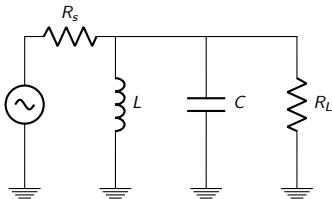- 1 Resonant Circuit with an external node



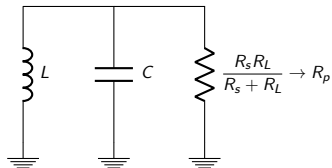- 2 Equivalent circuit for Q calculations



- At resonance

$$Q = \frac{R_p}{X_p}$$


R_p - equivalent load (parallel resistance of R_s and R_L)

X_p - inductive/capacitive reactance (they are equal at resonance)

Effects of R_s and R_L on Circuit Q


- In general, low values of source and load impedances load down ("de-Q") resonant circuits
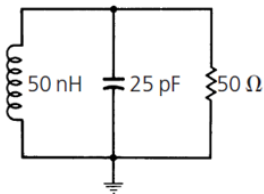
$$Q \approx 1.1, f = 142.35 \text{ MHz}$$



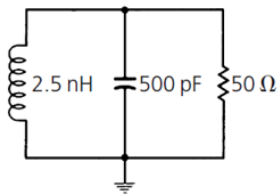(A) Large inductor,
small capacitor

$$Q \approx 22.4, f = 142.35 \text{ MHz}$$



(B) Small inductor,
large capacitor

- Becomes difficult to design high Q circuits with low source/load impedances
 - Theoretical design can be made, but component values might be impractical

Example

- Design a parallel LC circuit with the following specifications
 - Resonant frequency: $f_o = 1\text{GHz}$
 - Source Resistance: $R_s = 50\Omega$
 - Load Resistance: $R_L = 10\text{k}\Omega$

- List L and C for various Q

$$f_o = \frac{1}{2\pi\sqrt{LC}}, \quad Q_p = (R_s \parallel R_L)\sqrt{\frac{C}{L}}$$

Example

- Design a parallel LC circuit with the following specifications
 - Resonant frequency: $f_o = 1\text{GHz}$
 - Source Resistance: $R_s = 50\Omega$
 - Load Resistance: $R_L = 10\text{k}\Omega$

- List L and C for various Q

$$f_o = \frac{1}{2\pi\sqrt{LC}}, \quad Q_p = (R_s \parallel R_L) \sqrt{\frac{C}{L}}$$

Q	C	L
0.5	0.66pF	6.59nH
1	1.33pF	3.30nH
10	13.30pF	329.90pH


- Low R_s or R_L and High-Q requirements \rightarrow impractical values for L and/or C

Component Q Transformation

- To convert series equivalent component to its parallel equivalent and vice versa

$$Q_s = \frac{X_s}{R_s}, \quad Q_p = \frac{R_p}{X_p}$$

$$R_p = (Q^2 + 1)R_s$$

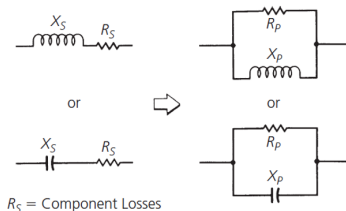


where: $Q_p = Q_s = Q(\text{component } Q)$

These transformations are valid at only one frequency

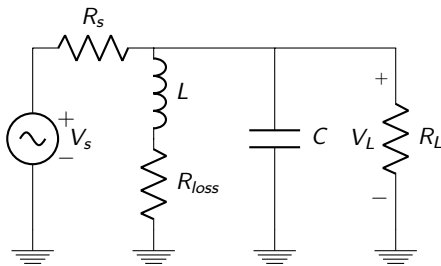Example

Suppose lossy $L = 50nH$ with
 $R_{loss} = 10\Omega$ at $100MHz$

- Solve for component Q
- Transform series R_{loss} into equivalent parallel RL circuit.



- The component Q of the inductor


$$Q = \frac{X_{L,s}}{R_{loss,s}} = \frac{2\pi(100 \times 10^6)(50 \times 10^{-9})}{10} = 3.14$$

- Equivalent parallel resistance

$$R_{loss,p} = (Q^2 + 1)R_{loss,s} = 108.7\Omega$$

- Equivalent parallel reactance
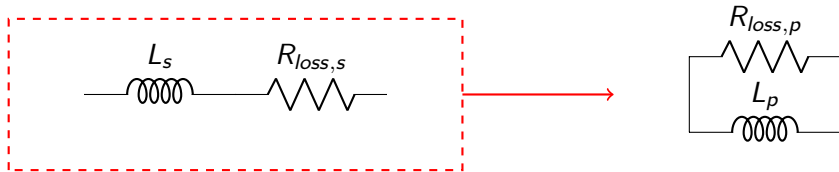
$$X_{L,p} = \frac{R_{loss,p}}{Q_p} = \frac{108.7}{3.14} = 34.62\Omega$$




- The parallel inductance

$$L_p = \frac{X_{L,p}}{\omega} = 55.1 nH$$


$$R_{loss,p} = 108.7 \Omega$$

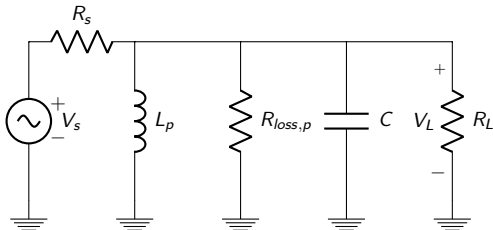- Equivalent circuit can be used to find loaded Q of circuit
- In general, lossy components tend to reduce loaded Q



Impedance Transformation

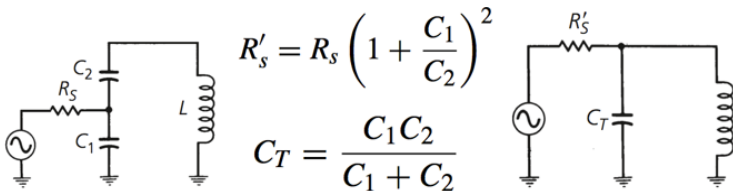
- We may use a tapped-C or tapped-L impedance transformer to make the small source or load impedance appear larger to the resonant circuit
- For a tapped-C circuit



- We always set $R'_s = R_L$ for maximum power transfer

Impedance Transformation

- For a tapped-L circuit

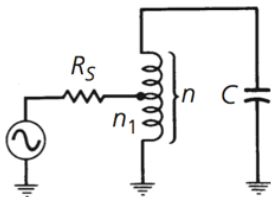

From C. Bowick, RF Circuit Design, Newnes 2008

$$R_S' = R_S \left(\frac{n}{n_1} \right)^2 \quad Q = \omega_0 R_S' C$$

$$Q_1 = \frac{R_S}{\omega_0 L_1}$$

$$R_S' = R_S \left(\frac{L}{L_1} \right)^2$$

$$L - L_1 = \frac{Q Q_1 - Q_1^2}{1 + Q_2^2} L_1$$

- Similarly, we set $R_S' = R_L$ for maximum power transfer

Example

Design a resonant circuit with a loaded Q of 20 at a center frequency of 100MHz that will operate between a source resistance of 50Ω and a load resistance of 2000Ω . The inductor has a Q of 100 at 100MHz.

- Loaded $Q = 20$
- $f_o = 100\text{MHz}$
- $R_s = 50\Omega$
- $R_L = 2000\Omega$

- Used a tapped-C transformer to match R_s with R_L

- Set $R'_s = R_L = 2000\Omega$

$$\frac{C_1}{C_2} = \sqrt{\frac{R'_s}{R_s}} - 1 = \sqrt{\frac{2000}{50}} - 1 = 5.3 \rightarrow C_1 = 5.3C_2$$

- Using the component Q of the inductor

$$R_{loss,p} = QX_p \rightarrow R_{loss,p} = 100X_p$$

- Using the loaded Q of the circuit

$$Q_{loaded} = 20 = \frac{R_{total}}{X_p} \qquad R_{total} = \frac{1000R_{loss,p}}{1000 + R_{loss,p}}$$

- Solving the equations simultaneously

$$X_p = 40\Omega \qquad R_{loss,p} = 4000\Omega$$


- Solving for the values of the components

$$L_p = \frac{X_p}{\omega} = 63.6nH \qquad C_T = \frac{1}{\omega X_p} = 39.78pF$$

- We can now solve for C_1 and C_2


$$C_T = \frac{C_1 C_2}{C_1 + C_2} = 39.78pF \qquad C_1 = 5.3C_2$$

$$C_1 = 250.6pF \qquad C_2 = 47.3pF$$

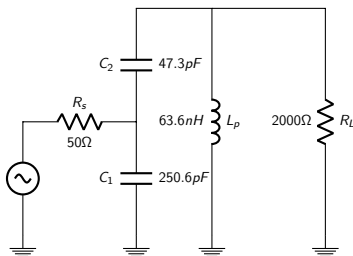

Insertion Loss

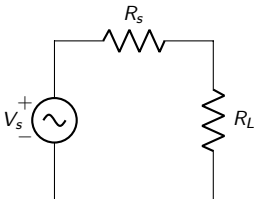
- Part of the power delivered by the source is dissipated by lossy resonant circuit placed in between source and load
- Consider the following circuit where $R_s = R_L$




- By voltage division,

$$\frac{V_L}{V_s} = \frac{R_L}{R_s + R_L} = \frac{1}{2}$$

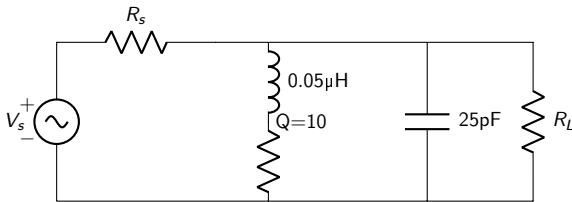- Inserting a parallel resonant circuit between source and load resistances



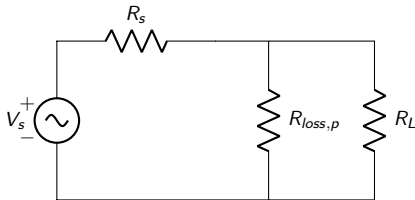- At resonance, the circuit is reduced to




$$\frac{V_L}{V_s} = \frac{(R_{loss,p} \parallel R_L)}{R_s + (R_{loss,p} \parallel R_L)} < \frac{1}{2}$$

$$IL_{dB} = 20 \log\left(\frac{V_L/V_s}{0.5}\right)$$



Coupling of Resonant Circuits

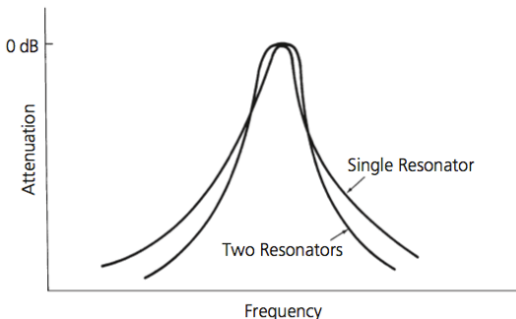- In some applications, one resonant circuit may not be enough to meet necessary requirements
 - "steep" passband skirts
 - Small shape factors
- Resonant circuits may be coupled together to produce more attenuation at certain frequencies



Capacitive Coupling

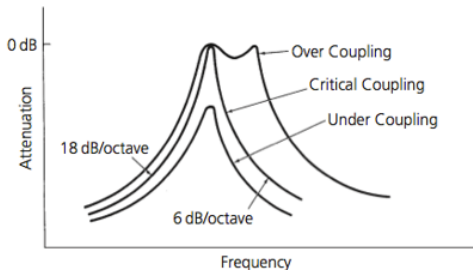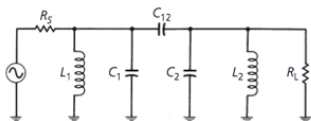- Most common due to simplicity and low cost




- Critical coupling
 - Reasonable bandwidth
 - Lowest insertion loss
 - Maximum power transfer


$$C_{12} = \frac{C}{Q}$$

- $Q = 0.707 Q_{circuit}$

Inductive Coupling

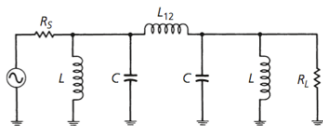

(A) Series inductor

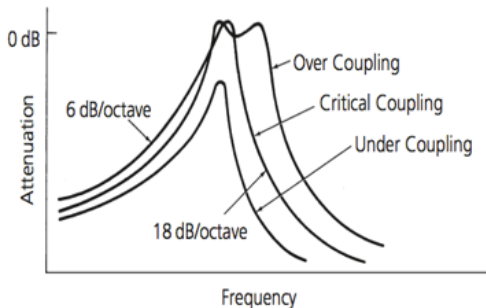

- For Critical Coupling

$$L_{12} = QL$$

- For same operating Q, $X_{L12} = X_{C12}$ at resonant frequency

$$\omega_o L_{12} = \frac{1}{\omega_o C_{12}}$$

Example

- Design a parallel resonant circuit to provide a 3dB bandwidth of 10 MHz at a center frequency of 100 MHz. The source and load impedances are 100Ω each. Assume the capacitor to be lossless, and the inductor have a Q of 85. What is the insertion loss of the network?

END