

EEE 51 Assignment 8

2nd Semester SY 2017-2018

Due: 5pm Tuesday, Apr. 24, 2018 (Rm. 220)

Instructions: Write legibly. Show all solutions and state all assumptions. Write your full name, student number, and section at the upper-right corner of each page. Start each problem on a new sheet of paper. Box or encircle your final answer.

Answer sheets should be color coded according to your lecture section. The color scheme is as follows:

THQ – yellow
THR – blue
THU – white
THX – green
WFX – pink

1. **CS amplifier with source degeneration frequency response.** For the given circuit below, assume that there is no body effect and channel length modulation is ignored.

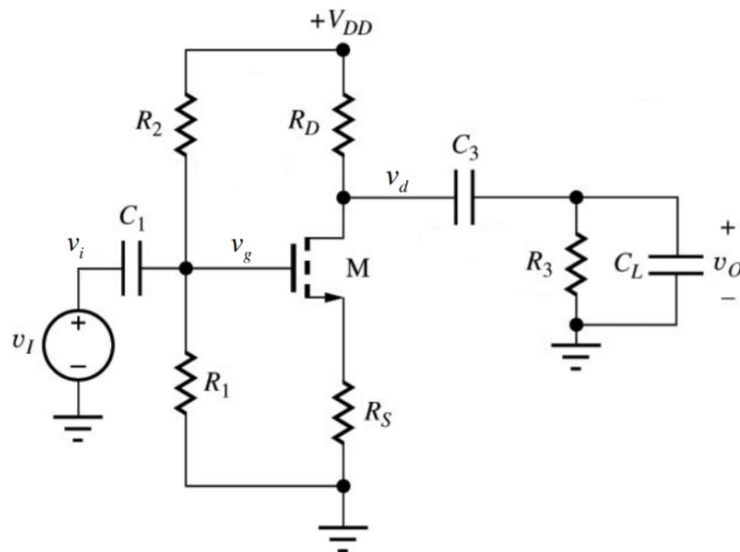


Figure 1: CS Amplifier with Source Degeneration

- (a) Draw the small-signal equivalent circuit including C_{GD} and C_{GS} . [2 pts]
- (b) Find the expression for the small-signal transfer function of the circuit. State *all* assumptions and show your *complete* solution. [5 pts]
- (c) Determine the expression(s) for the pole(s) and/or zero(s) of the circuit. [3 pts]
2. **Emitter-degenerated BJT Amplifier.** A BJT Q_1 with $\beta = 100$, $I_S = 10 \text{ fA}$, $V_{CE,sat} = 0.2 \text{ V}$ and $V_A = 200 \text{ V}$ is biased with resistors. Assume that the BJT has no parasitic capacitances. The resistors used are $R_C = 500 \Omega$, $R_B = 50 \text{ k}\Omega$, $R_E = 300 \Omega$. The supply voltage V_{CC} is 5 V . A DC-blocked input is connected to the base, as shown in Figure 2. The DC block is not ideal, with a finite capacitance $C_{in} = 1 \mu\text{F}$. A capacitor is placed in parallel to the emitter resistor, with $C_E = 1 \text{ fF}$. The amplifier drives a load capacitor, $C_L = 1 \text{ nF}$.

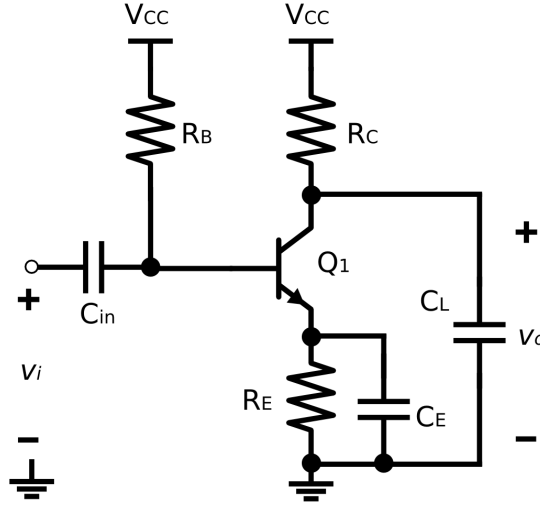


Figure 2: Emitter-degenerated amplifier with load capacitance

- Solve for the overall transfer function $H(s) = \frac{v_o(s)}{v_i(s)}$. Write this in terms of the small-signal parameters and component values. [7 pts]
- Compute for and list all the pole and zero frequencies in $H(s)$. If multiple poles or zeroes are on the same frequency, list them separately. [3 pts]

3. **Two-stage differential amplifier frequency response.** Given the circuit with the parameters below, solve for the following:

$$V_{DD} = 5V, I_{M8} = 50\mu A, k_{1,2,8} = 100 \frac{\mu A}{V^2}, k_{3,4} = 75 \frac{\mu A}{V^2}, k_{5,6,7,9} = 50 \frac{\mu A}{V^2}, \lambda = 0.02V^{-1}, \text{ and } |V_{TH_{n|p}}| = 1V$$

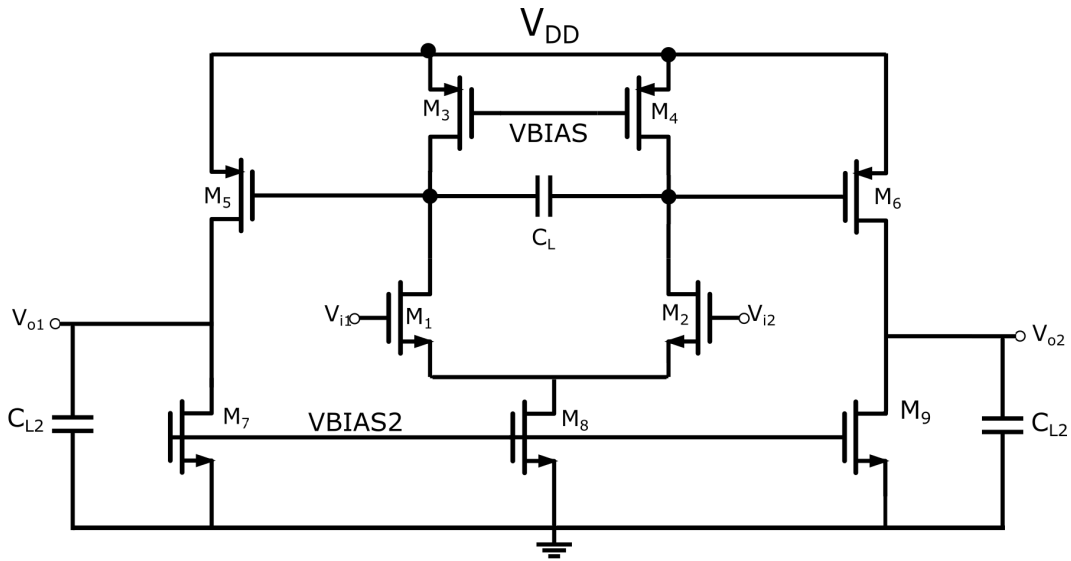


Figure 3

- Plot the magnitude and phase response of the amplifier. [2 pts]
- Determine ω_{p1} [2 pts], ω_{p2} [2 pts], $-3dB$ point [2 pts], and unity gain bandwidth [2 pts].

TOTAL: 30 points.