

# EEE 51 Assignment 6

2nd Semester SY 2017-2018

Due: 5pm Tuesday, Mar. 13, 2018 (Rm. 220)

*Instructions:* Write legibly. Show all solutions and state all assumptions. Write your full name, student number, and section at the upper-right corner of each page. Start each problem on a new sheet of paper. Box or encircle your final answer.

Answer sheets should be color coded according to your lecture section. The color scheme is as follows:

**THQ** – yellow  
**THR** – blue  
**THU** – white  
**THX** – green  
**WFX** – pink

## 1. MOSFET Differential CS Amplifier. Given the following:

$V_{DD} = 5V$ ,  $I_R = 50\mu A$ ,  $k_{1,2,7,8} = 2k_6 = 100 \frac{\mu A}{V^2}$ ,  $k_{3,4} = 2k_5 = 75 \frac{\mu A}{V^2}$ ,  $\lambda = 0.02V^{-1}$ , and  $V_{TH_{n|p}} = 1V$ :

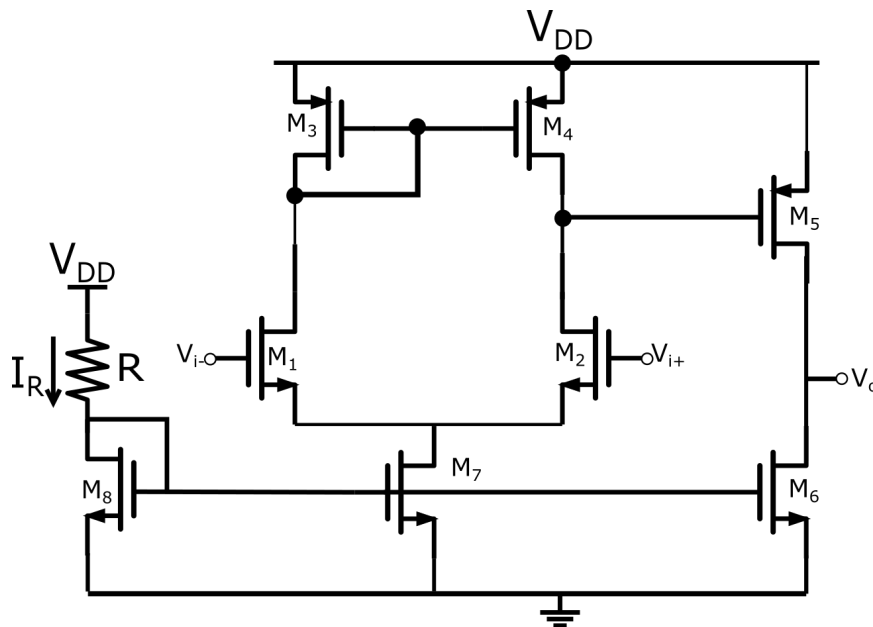


Figure 1: Differential-CS amplifier

- (a) Complete the table and ignore channel length modulation effect and assuming all transistors in saturation. [7 pts]

Parameter	M1	M2	M3	M4	M5	M6	M7	M8
ID								
Vgs								
gm								
ro								

Figure 2: Parameter table

- (b) Solve for the gain of the 1st and 2nd stage as well as the overall gain of the amplifier. [3 pts]

2. **BJT Cascode Amplifier with Cascode Load.** A Cascode amplifier is designed as shown in Figure 3. Bias voltages have been provided to it, and the input is fed through a DC block in order to maintain proper biasing. All transistors are confirmed to be biased properly to forward active. The load is a Cascode current mirror designed to provide an output resistance similar to the amplifier's.

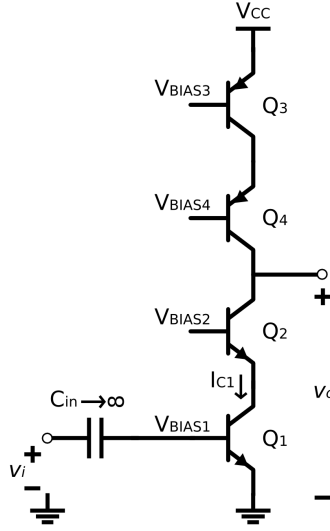


Figure 3: Cascode Amplifier

- Draw the small-signal equivalent circuit. Determine the total output resistance  $R_o$ , transconductance  $G_m$  and gain  $A_v$  of the whole amplifier as a function of the small-signal parameters ( $g_{m1}$ ,  $r_{o1}$ ,  $r_{\pi1}$ ,  $g_{m2}$ , etc.). [6 pts]
  - Convert the small-signal parameters such that  $G_m$ ,  $R_o$  and  $A_v$  are then a function of the quiescent collector current of  $Q_1$ ,  $I_{C1}$ . For both NPN and PNP transistors,  $V_A = 200\text{ V}$ ,  $\beta = 200$ , and let  $V_T = 26\text{ mV}$ . [3 pts]
  - Given that the gain and output characteristics of the amplifier have been shown in relationship to the bias current, as a design problem how would you determine what to set the bias current as, based on what possible and reasonable parameters or specifications? [1 pt]
3. **Multistage Amplifier.** For the given figure below, you are given the following assumptions:  $\beta \gg 1$  and  $|V_{BE}| = 0.7\text{ V}$ . The input and output DC quiescent voltages are set to 0.

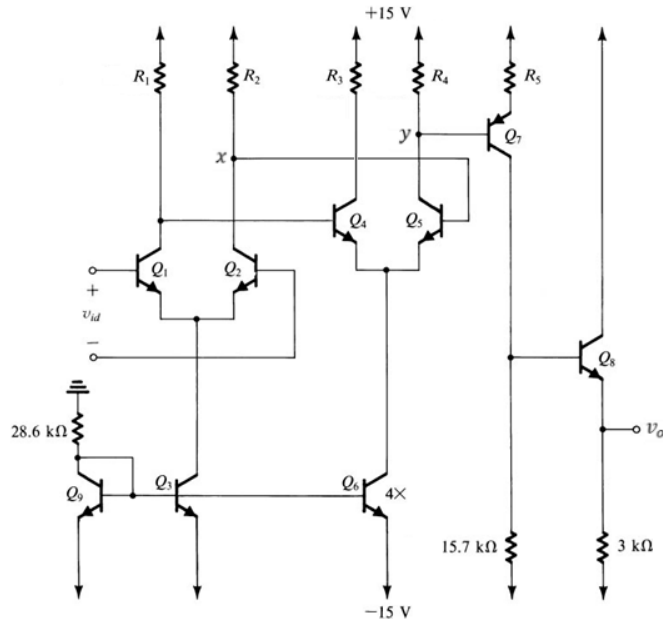


Figure 4: Multistage Amplifier

- Determine all the DC collector currents of each transistor. [2 pts]
- Given  $V_x = 6\text{ V}$  and  $V_y = 7.5\text{ V}$ , what are the values of resistors  $R_1$  to  $R_5$ ? [2 pts]
- Assuming ideal current sources, find the circuit gain  $A_v$  with loading in-between stages. Write your *complete* solution. [6 pts]

TOTAL: 30 points.