

EEE 51 Assignment 9 Solution

2nd Semester SY 2017-2018

Due: 5pm Tuesday, May 8, 2018 (Rm. 220)

Instructions: Write legibly. Show all solutions and state all assumptions. Write your full name, student number, and section at the upper-right corner of each page. Start each problem on a new sheet of paper. Box or encircle your final answer.

Answer sheets should be colored according to your lecture section. The color scheme is as follows:

THQ – yellow

THR – blue

THU – white

THX – green

WFX – pink

1. **What is Feedback?** Chaeyoung is an engineer who is building a communication system. She wants to reduce the effect of noise from unwanted nearby signals by using a negative feedback circuit, which is shown in Figure 1. Assume that the op amp is ideal, and $\beta \rightarrow \infty$ for the transistor.

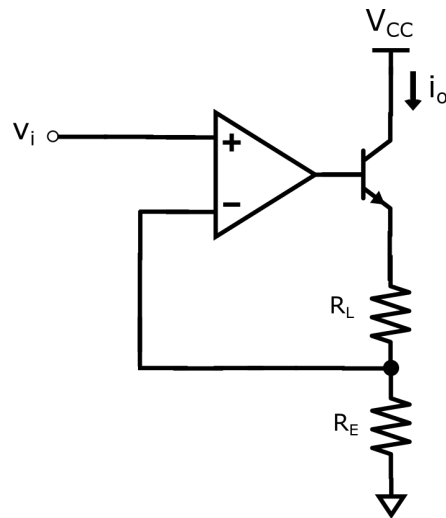


Figure 1: Tzuyu's negative feedback circuit

- (a) What is the quantity being sampled (i.e. what is the output quantity): voltage or current? [0.5 pt]

current [0.5 pt]

- (b) What is the quantity being mixed with the input: voltage or current? [0.5 pt]

voltage [0.5 pt]

- (c) From your answers in (a) and (b), what type of feedback topology is being used? [1 pt]

series-series [1 pt]

- (d) Recall that the forward gain, A , is the ratio of the output signal (s_o) to the error signal (s_e). Express A in terms of R_L and R_E . [2 pts]

Remember that the quantity being sampled is current, and the quantity being mixed is voltage. Therefore:

$$A = \frac{s_o}{s_e} = \frac{i_o}{v_e} \quad (1)$$

The feedback voltage, v_{fb} , is the voltage at the inverting input of the op amp. So the error voltage is:

$$v_e = v_i - v_{fb} \quad (2)$$

We can then express Eq. (1) as:

$$A = \frac{i_o}{v_i - v_{fb}} \quad (3)$$

But since the op amp is ideal,

$$v_i = v_{fb} \quad (4)$$

therefore the open loop gain is:

$A \rightarrow \infty$ [2 pts]

- (e) On the other hand, the feedback factor F is the ratio of the signal being fed back to the input (s_{fb}) to the output signal (s_o). Express F in terms of R_L and R_E . [2 pts]

$$F = \frac{s_{fb}}{s_o} = \frac{v_{fb}}{i_o} \quad (5)$$

v_{fb} can be expressed as the voltage across R_E :

$$v_{fb} = R_E i_o \quad (6)$$

F then becomes:

$$F = \frac{R_E i_o}{i_o} \quad (7)$$

$F = R_E$ [2 pts]

- (f) Given your answers in (d) and (e), what is the closed loop gain, A_{CL} ? [2 pts]

The general expression for A_{CL} is:

$$A_{CL} = \frac{A}{1 + AF} \quad (8)$$

But since $A \rightarrow \infty \gg 1$, A_{CL} simplifies to:

$$A_{CL} = \frac{1}{F} \quad (9)$$

$A_{CL} = \frac{1}{R_E}$ [2 pts]

2. **Frequency response of a common emitter amplifier with feedback.** A common emitter amplifier is shown in ???. Given that $V_{CC} = 12\text{ V}$, $V_{IN} = 5\text{ V}$, $V_A = 100\text{ V}$, $I_S = 1\text{ fA}$, $R_S = 10\text{ k}\Omega$, $R_C = 500\text{ }\Omega$, $R_f = 1\text{ k}\Omega$, and $\beta = 50$, answer the following questions.

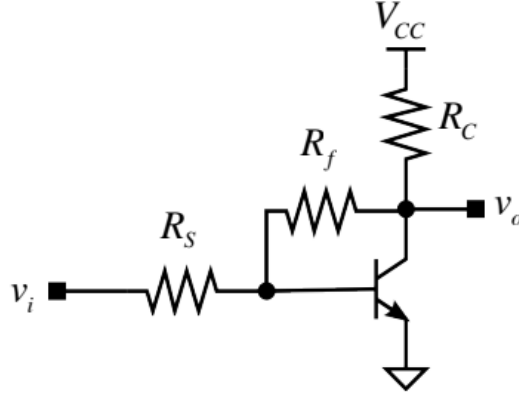


Figure 2: Common Emitter Amplifier with Resistive Feedback Network

- (a) Draw the equivalent small-signal circuit for both open-loop and closed-loop circuits. (Ignore parasitic capacitances.)

In order to find the bias current, the equations that we need are the following,

$$\beta I_B = I_C \quad (10)$$

$$I_B = \frac{1}{\beta + 1} I_S (e^{\frac{V_{BE}}{V_T}} - 1) \quad (11)$$

$$I_B = \frac{\beta}{\beta + 1} I_S (e^{\frac{V_{BE}}{V_T}} - 1) \quad (12)$$

$$\frac{V_o - V_{BE}}{R_f} = I_{R_f} \quad (13)$$

$$\frac{V_{CC} - V_o}{R_C} = I_{R_C} \quad (14)$$

KCL at the output node:

$$I_{R_C} = I_C + I_{R_f} \quad (15)$$

KCL at the base terminal node:

$$I_B = I_{R_f} + I_{R_s} \quad (16)$$

Combining equations, we get two simultaneous equation:

$$\frac{V_{CC} - V_o}{R_C} = \frac{\beta}{\beta + 1} I_S (e^{\frac{V_{BE}}{V_T}} - 1) + \frac{V_o - V_{BE}}{R_f} \quad (17)$$

$$\frac{1}{\beta + 1} I_S (e^{\frac{V_{BE}}{V_T}} - 1) = \frac{V_o - V_{BE}}{R_f} + \frac{V_{IN} - V_{BE}}{R_S} \quad (18)$$

Substituting actual values and the isolating V_o :

$$V_o = \frac{V_{BE}}{3} + \frac{24}{3} - \frac{50000}{153} (1\text{ fA}) (e^{\frac{V_{BE}}{0.026}} - 1) \quad (19)$$

$$V_o = \frac{1000}{51} (1\text{ fA}) (e^{\frac{V_{BE}}{0.026}} - 1) + \frac{11V_{BE}}{10} - \frac{1}{2} \quad (20)$$

Using these simultaneous equations, we can find V_{BE} :

$$V_{BE} = 0.827815 \text{ V} \quad (21)$$

Solving for I_C :

$$I_C = \frac{\beta}{\beta + 1} (1 \text{ fA}) (e^{\frac{0.827815}{0.026}} - 1) \quad (22)$$

$$\begin{aligned} g_m &= \frac{I_C}{V_T} = 2.53 \text{ S} \\ r_o &= \frac{V_A}{I_C} = 1517.3 \Omega \\ r_\pi &= \frac{\beta V_T}{I_C} = 19.7253 \Omega \end{aligned}$$

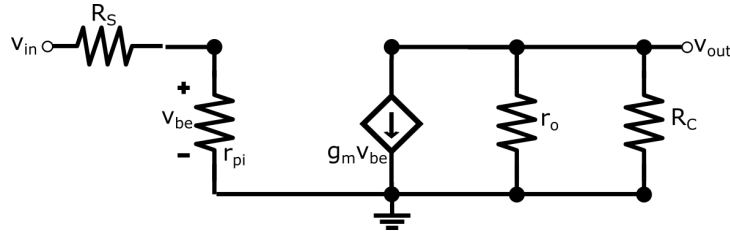


Figure 3: Common Emitter Amplifier with Resistive Feedback Network Open-Loop Small-Signal Circuit [1 pts]

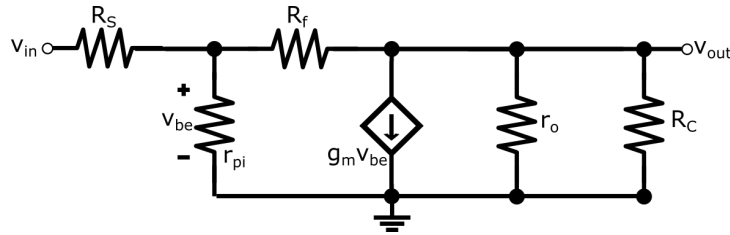


Figure 4: Common Emitter Amplifier with Resistive Feedback Network Closed-Loop Small-Signal Circuit [1 pts]

- (b) What is the small-signal open-loop gain of the amplifier?

The gain of a simple common-emitter is given by:

$$A_v = -g_m R_o = -g_m (r_o || R_L) \quad [2 \text{ pts}] \quad (23)$$

$$A_v = -g_m (R_C || r_o) = 951.46 \quad [1 \text{ pt}]$$

- (c) What is the small-signal closed-loop gain of the amplifier?

Solution 1: Assuming direct solution, the gain of the amplifier is given by (from the slides):

$$R_1 = R_S || R_f || r_\pi = 19.2068 \Omega \quad (24)$$

$$R_2 = R_C || R_f = 333.33 \Omega \quad (25)$$

$$\frac{v_o}{v_i} = -\frac{R_f}{R_S} \frac{\frac{R_1 R_2}{R_f} \left(g_m - \frac{1}{R_f} \right)}{1 + \frac{R_1 R_2}{R_f} \left(g_m - \frac{1}{R_f} \right)} \quad (26)$$

$$\frac{v_o}{v_i} = -0.0942 \quad [1 \text{ pt}]$$

Solution 2: Assuming feedback analysis, the gain of the amplifier is given by(again, from the slides):

$$\frac{v_o}{v_i} = -\frac{R_f}{R_s} \frac{\frac{g_m R_1 R_2}{R_f}}{1 + \frac{g_m R_1 R_2}{R_f}} \quad (27)$$

$$\frac{v_o}{v_i} = -0.0942 \text{ [1 pt]}$$

3. **Analysis of a feedback amplifier.** Consider the feedback amplifier shown in Fig. 5. Provided that all transistors have $\beta \rightarrow \infty$, $V_{be,on} = 0.7V$, $V_A \rightarrow \infty$, an input DC voltage of 1V and an output DC voltage of 1.5V,

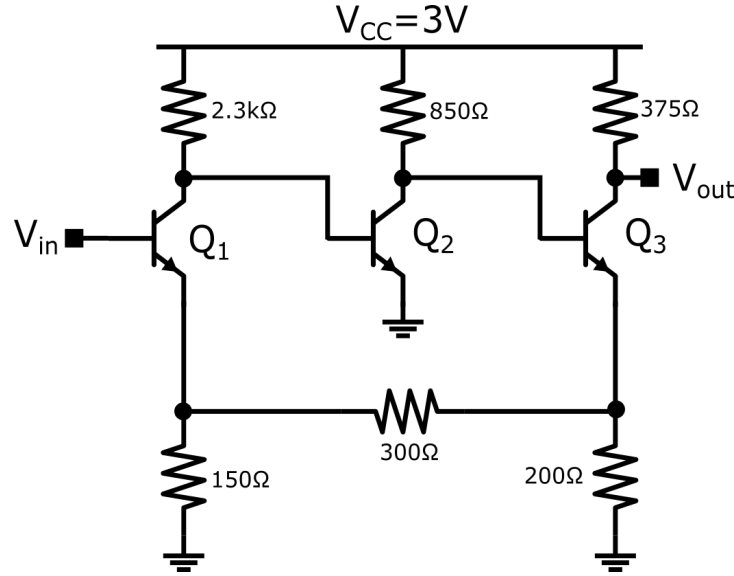


Figure 5: Basic feedback amplifier

- (a) Determine the collector currents and transconductances of Q_1 , Q_2 and Q_3 . [1 pt]

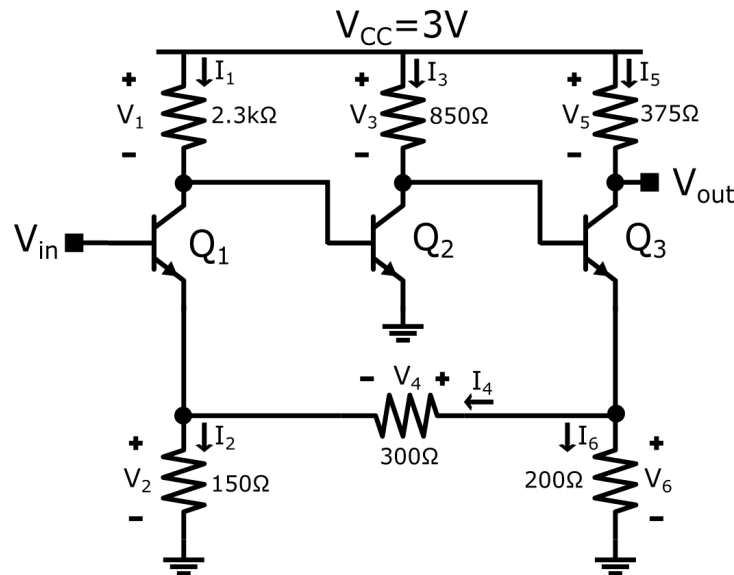


Figure 6: Basic feedback amplifier with voltage and current notations

Refer to Fig. 6 above. First, with $\beta \rightarrow \infty$, all of the base currents of Q_1 , Q_2 and Q_3 are zero ($I_{b1} = I_{b2} = I_{b3} = 0A$). Also from Fig. 6, we solve the indicated voltages and currents as follows:

$$V_1 = V_{CC} - V_{be,on_Q2} = 3 - 0.7 = 2.3V \rightarrow I_1 = I_{C_Q1} = \frac{2.3}{2.3k} = 1mA \quad (28)$$

$$V_2 = V_{in} - V_{be,on_Q1} = 1 - 0.7 = 0.3V \rightarrow I_2 = \frac{0.3}{150} = 2mA \quad (29)$$

$$I_4 = I_2 - I_1 = 2mA - 1mA = 1mA \rightarrow V_4 = 300 * I_4 = 0.3V \quad (30)$$

$$V_6 = V_4 + V_2 = 0.3 + 0.3 = 0.6V \rightarrow I_6 = \frac{0.6}{200} = 3mA \quad (31)$$

$$V_5 = V_{CC} - V_{out} = 3 - 1.5 = 1.5V \rightarrow I_5 = I_{C_Q3} = \frac{1.5}{375} = 4mA \quad (32)$$

$$V_3 = V_{CC} - V_{be,on_Q3} - V_6 = 3 - 0.7 - 0.6 = 1.7V \rightarrow I_3 = I_{C_Q2} = \frac{1.7}{850} = 2mA \quad (33)$$

$$\begin{aligned} I_{C_Q1} &= 1mA \\ I_{C_Q2} &= 2mA \\ I_{C_Q3} &= 4mA \\ [0.5pts \text{ all or nothing}] \end{aligned}$$

For the transconductances we use the following equation and considering room temperature ($T = 300K$),

$$g_m = \frac{I_C}{V_T} \quad (34)$$

$$\begin{aligned} g_{m_Q1} &= \frac{I_{C1}}{V_T} = \frac{1mA}{26mV} = 38.5mS \\ g_{m_Q2} &= \frac{I_{C2}}{V_T} = \frac{2mA}{26mV} = 76.9mS \\ g_{m_Q3} &= \frac{I_{C3}}{V_T} = \frac{4mA}{26mV} = 153.8mS \\ [0.5pts \text{ all or nothing}] \end{aligned}$$

- (b) What type of feedback topology is used in this circuit? Draw the feedback network. [2 pts]
The feedback network is shown below in Fig. 7

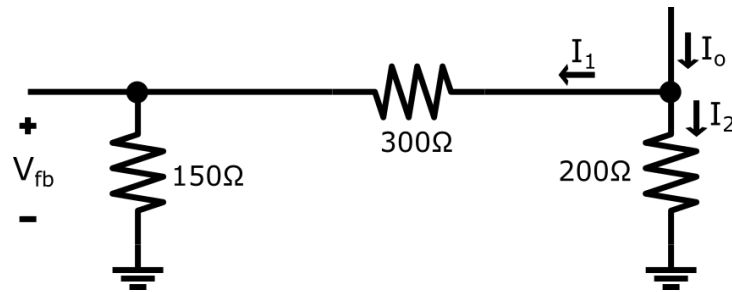


Figure 7: Feedback network

The sampled signal is a current signal and the feedback signal is a voltage signal, hence the feedback topology of this amplifier is **series-series**.

[1 pt] will be given for the drawing of the feedback network and [1 pt] will be given for the correct feedback topology.

- (c) Find the feedback factor, F , the input and output resistances of the feedback network. [3 pts]
From Fig. 7,

$$V_{fb} = 150 * I_1 \quad (35)$$

$$(300 + 150)I_1 = 200I_2 = 200(I_o - I_1) \quad (36)$$

$$I_1 = \frac{200}{200 + 300 + 150} I_0 \quad (37)$$

Substitute Eq. 37 to Eq. 35,

$$V_{fb} = 150 * \frac{200}{200 + 300 + 150} I_0 \rightarrow F = \frac{V_{fb}}{I_0} = \frac{600}{13} V/A = 46.15 V/A \quad (38)$$

For the input resistance,

$$R_{i,fb} = 200 // 450 = 138.46 \Omega \quad (39)$$

For the output resistance,

$$R_{o,fb} = 150 // 500 = 115.38 \Omega \quad (40)$$

$$\begin{aligned} F &= 46.15 V/A \text{ [1pt]} \\ R_{i,fb} &= 138.46 \Omega \text{ [1 pt]} \\ R_{o,fb} &= 115.38 \Omega \text{ [1 pt]} \end{aligned}$$

- (d) Draw the small signal model of the amplifier. [2 pts]

Since $\beta \rightarrow \infty$ and $V_A \rightarrow \infty$, $r_\pi = r_o = \infty$,

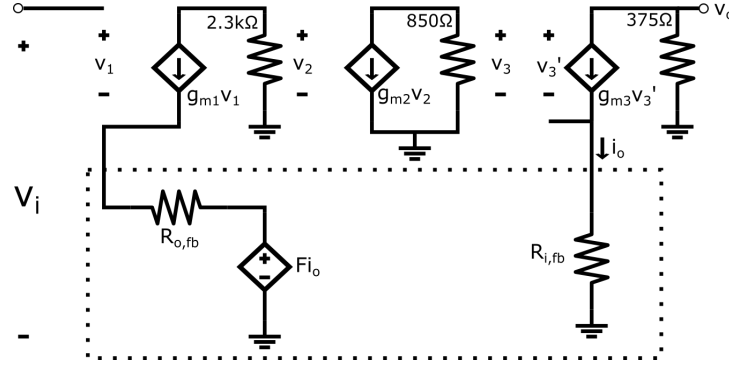


Figure 8: Small signal model

- (e) Determine the open-loop gain of the amplifier. [2 pts]

To determine the open-loop gain of the amplifier, we analyze the circuit shown in Fig. 9 below and get the expression for $\frac{i_o}{v_i}$,

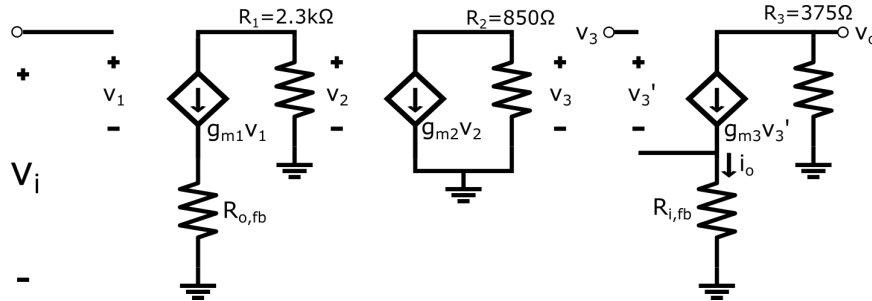


Figure 9: Open loop circuit

Thru basic circuit analysis techniques (KCL, KVL) we get the following expressions:

$$v_i = v_1 + g_{m1}v_1R_{o,fb} = v_1(1 + g_{m1}R_{o,fb}) \quad (41)$$

$$v_2 = -g_{m1}v_1R_1 \quad (42)$$

$$v_3 = -g_{m2}v_2R_2 \quad (43)$$

$$v_3 = v_{3'} + g_{m3}v_{3'}R_{i,fb} = v_{3'}(1 + g_{m3}R_{i,fb}) \quad (44)$$

$$i_o = g_{m3}v_{3'} \quad (45)$$

Combining Eqs. 41-45 together, we get the expression for the open-loop gain as,

$$A = \frac{i_o}{v_i} = \frac{g_{m1}R_1}{1 + g_{m1}R_{o,fb}} * g_{m2}R_2 * \frac{g_{m3}}{1 + g_{m3}R_{i,fb}} \quad (46)$$

Substitute the values for the resistances and transconductances, we get the following open-loop gain:

$$A = \frac{i_o}{v_i} = 7.337A/V \text{ [0.5 pts]}$$

[1.5 pts] will be given for the solution

- (f) What is the loop gain of the feedback network? [1 pt]

The loop gain of the amplifier is,

$$T = AF = 7.337A/V * 46.15V/A = 338.6 \text{ [1 pt]}$$

- (g) What is the closed-loop gain of the amplifier? [1 pt]

The closed-loop **transconductance** gain is,

$$G_{m,cl} = \frac{A}{1 + AF} = 0.0216A/V \quad (47)$$

However, this is not the closed-loop gain of the whole amplifier. Since

$$i_o = G_{m,cl}v_i \quad (48)$$

and

$$v_o = -i_o * 375 \quad (49)$$

$$\frac{v_o}{v_i} = -G_{m,cl} * 375 \quad (50)$$

$$A_v = \frac{v_o}{v_i} = -8.1 \text{ [1 pt]}$$

TOTAL: 30 points.