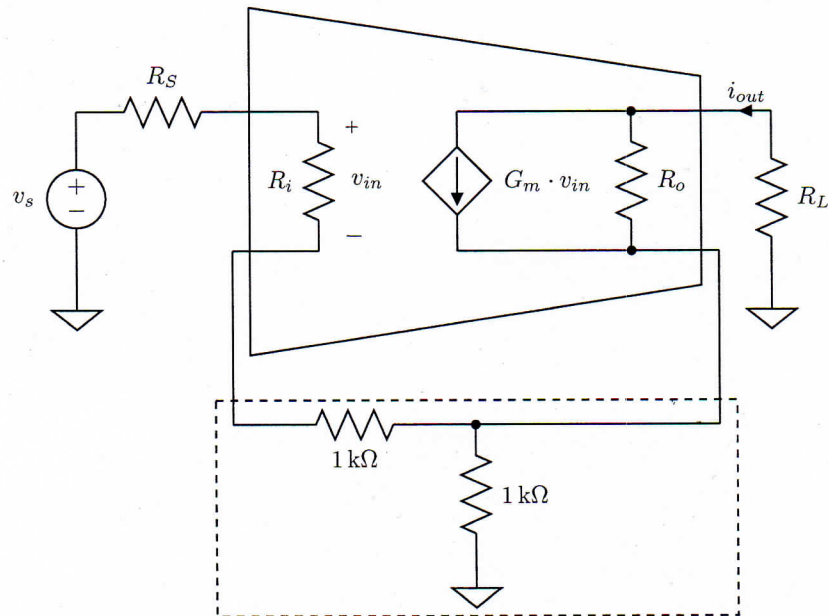


Part I:

(20 points) A feedback amplifier employing **series-series** feedback is shown in the figure below, where the feedback network is contained within the dashed box. For the open loop amplifier, $R_i = 7\text{ k}\Omega$, $G_m = 100\text{ mS}$, and $R_o = 3\text{ k}\Omega$. The other component values are $R_S = 7\text{ k}\Omega$ and $R_L = 6\text{ k}\Omega$.



1. What is the unloaded open loop amplifier small signal gain, i_{out}/v_{in} ? (1 point)

$i_{out}/v_{in} = 100\text{ mS}$

open-loop amp:

$$\frac{i_{out}}{v_{in}} = G_m = 100\text{ mS}$$

2. Draw the Thevenin two-port network representation of the feedback network. Label all components with their calculated values. (7 points)



\equiv

$$R_{if} = 1\text{ k}\Omega$$

$$R_{of} = 2\text{ k}\Omega$$

$$f = \frac{v_{fb}}{i_{out}} \Big|_{i_{fb}=0} = 1\text{ k}\Omega$$

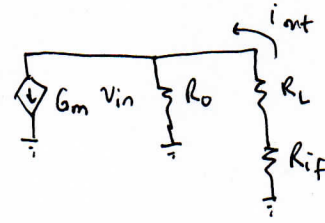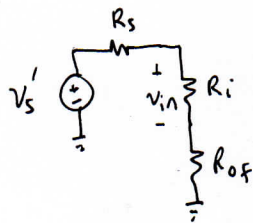3. Calculate the open-loop gain of the amplifier, i_{out}/v_s' , with the loading of the feedback network, source resistance, and load resistance. (4 points)



$$i_{out} = \frac{R_o}{R_o + R_L + R_{of}} \cdot G_m \cdot v_{in}$$

$$= \frac{3k}{3k + 6k + 1k} \cdot 100mS \cdot v_{in}$$

$$= 0.03 v_{in}$$

$$v_{in} = \frac{R_i}{R_s + R_i + R_{of}} \cdot v_s' = \frac{7k}{7k + 7k + 2k} \cdot v_s'$$

$$v_{in} = 0.4375 \cdot v_s'$$

$$i_{out}/v_s' = 13.125 \text{ mS}$$

$$i_{out} = 0.03(0.4375) v_s'$$

$$\frac{i_{out}}{v_s'} = 0.013125 \text{ A/V}$$

4. Calculate the closed-loop gain of the amplifier, $A_{CL} = i_{out}/v_s$, using feedback analysis. (2 points)

$$T = \frac{i_{out}}{v_s'} \cdot f = (0.013125)(1000) = 13.125$$

$$A_{CL} = \frac{\frac{i_{out}}{v_s'}}{1 + T} = \frac{0.013125}{1 + 13.125} = 929 \mu S$$

$$A_{CL} = 929 \mu S$$

5. Calculate the closed-loop input resistance of the amplifier, $R_{i,CL}$, using feedback analysis. (2 points)

$$R_{i, \text{open loop}} = R_s + R_i + R_{of} = 16 \text{ k}\Omega$$

$$R_{i,CL} = R_{i, \text{open loop}} (1 + T) = 226 \text{ k}\Omega$$

$$R_{i,CL} = 226 \text{ k}\Omega$$

6. Calculate the closed-loop output resistance of the amplifier, $R_{o,CL}$, using feedback analysis. (2 points)

$$R_{o, \text{open loop}} = R_o \parallel (R_L + R_{if}) = 3k \parallel (6k + 1k) = 2.1 k\Omega$$

$$R_{o, cl} = R_{o, \text{open loop}} (1 + T) = 29.7 k\Omega$$

$$R_{o,CL} = 29.7 k\Omega$$

7. If G_m increases by 5%, by approximately how much (as a percentage) does the closed-loop gain change? (2 points)

if G_m increases by 5%, $\frac{dA}{A} = 0.05$ where A is open-loop amplifier gain.

$$\text{hence, } \frac{dA_{cl}}{A_{cl}} \approx \frac{\frac{dA}{A}}{1 + T} = \frac{0.05}{1 + T} = 0.00354$$

$$\frac{dA_{CL}}{A_{CL}} = 0.354 \%$$