

# EEE 51 Assignment 9 Answer Key

2nd Semester SY 2018-2019

## 1. Positive-Negative.

You are to implement an amplifier with feedback. Given in Figure 1 are two possible designs.


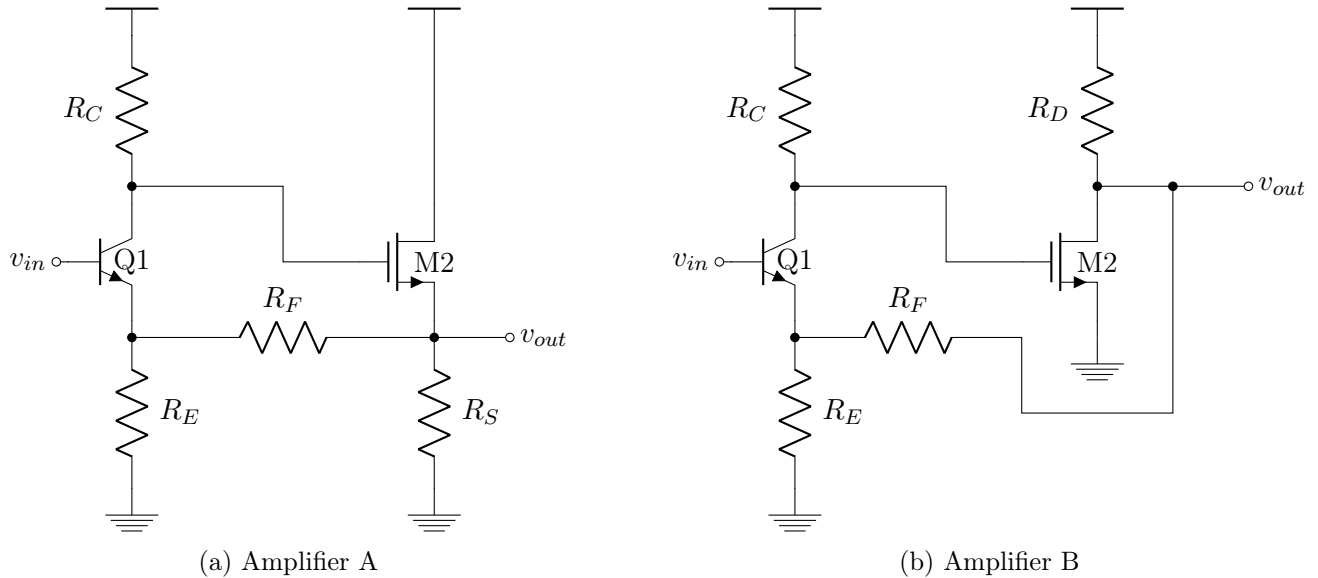


Figure 1: Feedback Amplifiers.


- (a) Both of the designs use the same type of feedback. Identify the type of feedback being used. (1 pt)
- Looking at the input side, the input to the amplifiers is both  $v_{be}$  which is the difference between the input voltage and the voltage across  $R_E$ . We can say that a voltage is sampled at the input, and the input side is therefore in **series**. (0.5 pt for this answer)
  - At the output, the feedback path is directly connected at the output node. We can say that the voltage is being sampled at the output and thus the output side is **shunt**. (0.5 pt for this answer)
  - The type of feedback used is **SERIES-SHUNT**.
- (b) Which of the two designs is valid (employs negative feedback and will not blow-up)? Be careful since your answers in the next item will be dependent here. Committing a mistake in this item will automatically void the answers for the next item. (2 pts)
- The output voltage at amplifier A is negative of the input. Feeding it back to the input, the error voltage will be  $v_{be} = v_{in} - (-|a_v f| v_{in})$ . A positive feedback. This might overload the transistors and blow them up at worse.
  - At amplifier B, the output is a positive voltage. Feeding the output back yields  $v_{be} = v_{in} - (|a_v f| v_{in})$ . A negative feedback.
  - **AMPLIFIER B** is the valid design.
  - 1 point will be given if you answered incorrectly in this item but still answered the rest of the problem.

- (c) Using your answer in (b), use the parameters  $\beta$ ,  $g_{mx}$ , and  $r_\pi$ ; and the resistors  $R_C$ ,  $R_D$ ,  $R_E$ ,  $R_F$ , and  $R_S$  to express your answers. Assume that  $r_o \rightarrow \infty$  for both transistors. For parallel resistors, just use  $(R_1 || R_2 || \dots || R_n)$  notation instead. Do not expand the expressions.

- We need to identify the open-loop circuit first.
  - i. For easier analysis, we assume that the feedback network is ideal such that it does not load the amplifier. The supposed load will be "moved" to the open-loop amplifier instead.
  - ii. To "move" the load at the INPUT side, we look first at the output. We will break the loop at the output side (cut the connection of  $R_F$  to the  $v_{out}$  node). Since we know that the output network is shunt, the loose end of  $R_F$  will be grounded (we leave it open/hanging for the case of a series network). We do this so the output has zero direct influence on the resistance that can be "seen" at the input.
  - iii. To "move" the load at the OUTPUT side, we look first at the input. Break the loop at the input side as well (separate emitter of  $Q_1$  to the node where  $R_E$  and  $R_F$  meet). Since we know that the input network is series, we leave the node of  $R_F$ - $R_E$  connection hanging (we short that node to ground for the case of a shunt network). We do this so the input has zero direct influence on the resistance that can be "seen" at the output.
  - iv. The open-loop circuit for amplifier B is:

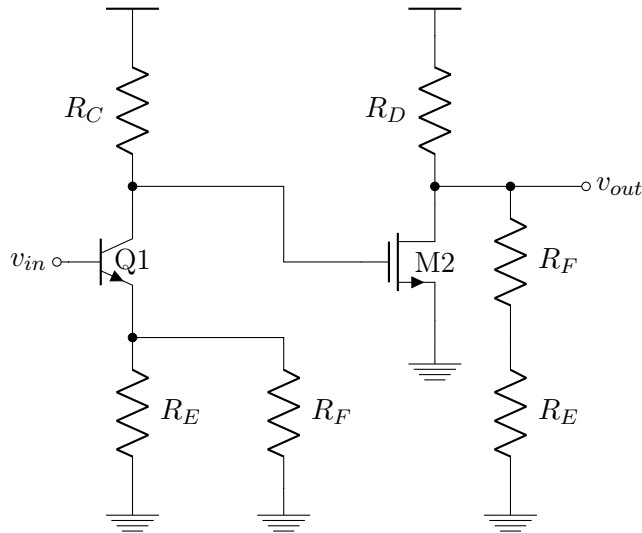

- The closed-loop small signal is:

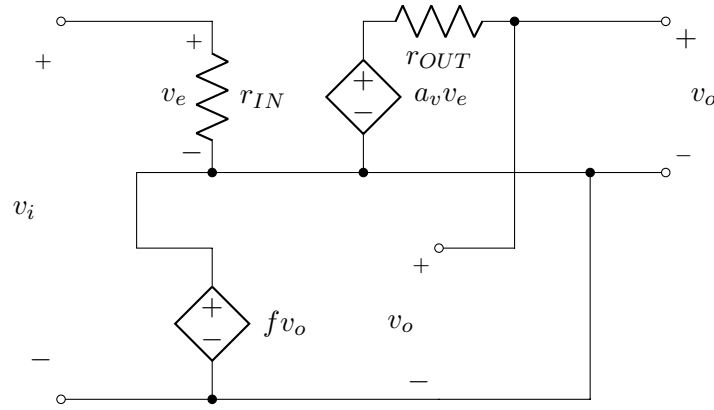

- Note that the open-loop circuit is just for simpler analysis. Any circuit connected to amplifier B will still "see" it in its closed-loop form.

i. Feedback gain  $f = \frac{v_{fb}}{v_o}$ . (1 pt)

- The feedback voltage is just the voltage across  $R_E$  in series with  $R_F$  (output side of the open-loop circuit). Note that we need to sample  $v_{out}$  so we solve for  $f$  with respect to  $v_{out}$ .

$$v_{fb} = v_{out} \frac{R_E}{R_E + R_F}$$

$$f = \frac{v_{fb}}{v_{out}} = \boxed{\frac{R_E}{R_E + R_F}}$$

ii. Open-loop gain (with feedback loading)  $a_v = \frac{v_{out}}{v_{in}}$ . (1 pt)

- Gain at first stage (common-emitter with degeneration resistance) (0.5 pt. for correct expression):

$$a_{v1} = \frac{-g_{m1} R_C}{1 + g_{m1} (R_E || R_F)}$$

- Gain at second stage (common source) (0.5 pt. for correct expression):

$$a_{v2} = -g_{m2} [R_D || (R_E + R_F)]$$

- Open-loop gain:

$$a_v = \boxed{\frac{g_{m1} g_{m2} R_C [R_D || (R_E + R_F)]}{1 + g_{m1} (R_E || R_F)}}$$

iii. Closed-loop gain  $A_V = \frac{v_{out}}{v_{in}}$ . (1 pt)

$$A_V = \frac{a_v}{1 + a_v f}$$

$$= \frac{\frac{g_{m1} g_{m2} R_C [R_D || (R_E + R_F)]}{1 + g_{m1} (R_E || R_F)}}{1 + \frac{g_{m1} g_{m2} R_C [R_D || (R_E + R_F)]}{1 + g_{m1} (R_E || R_F)} \frac{R_E}{R_E + R_F}} \quad \text{or}$$

$$= \boxed{\frac{g_{m1} g_{m2} R_C [R_D || (R_E + R_F)] (R_E + R_F)}{R_E + R_F + g_{m1} (R_E || R_F) (R_E + R_F) + g_{m1} g_{m2} R_C R_E [R_D || (R_E + R_F)]}}$$

iv. Closed-loop input resistance  $R_{IN} = \frac{v_{in}}{i_{in}}$ . (2 pts)

- Get the open-loop open resistance first. This input resistance is just the resistance seen at the base of  $Q_1$  (1 pt. for having this correct):

$$r_{IN} = r_{\pi} + (\beta + 1) (R_E || R_F)$$

- The closed-loop input resistance is:

$$R_{IN} = r_{IN} (1 + a_v f)$$

$$= [r_{\pi} + (\beta + 1) (R_E || R_F)] \left( 1 + \frac{g_{m1} g_{m2} R_C [R_D || (R_E + R_F)]}{1 + g_{m1} (R_E || R_F)} \frac{R_E}{R_E + R_F} \right)$$

- Since we sample a voltage at the input, it is reasonable that we have a large input resistance.
- Moreover,  $Q_1$  is in CE configuration which is a voltage amplifier. A large input resistance will "absorb" most of the input voltage.

v. Closed-loop output resistance  $R_{OUT} = \frac{v_{out}}{i_{out}}$ . (2 pts)

- Get the open-loop output resistance, which is the resistance at the output node (1 pt. for having this correct):

$$r_{OUT} = R_D || (R_E + R_F)$$

- The closed-loop output resistance is:

$$R_{OUT} = \frac{r_{OUT}}{1 + a_v f}$$

$$= \frac{R_D || (R_E + R_F)}{1 + \frac{g_{m1} g_{m2} R_C [R_D || (R_E + R_F)]}{1 + g_{m1} (R_E || R_F)} \frac{R_E}{R_E + R_F}} \text{ or}$$

$$= \frac{[R_D || (R_E + R_F)] [1 + g_{m1} (R_E || R_F)] (R_E + R_F)}{R_E + R_F + g_{m1} (R_E || R_F) (R_E + R_F) + g_{m1} g_{m2} R_C R_E [R_D || (R_E + R_F)]}$$

- For an amplifier that has voltage as an output ( $M_2$  is a buffer or a voltage follower), we want a small output resistance so we can deliver the output to any load of greater resistance.

- Sbeve

## 2. Feed me, feed me, feed me back!

The parameters for all transistors are the following:  $V_{be,on} = 0.7V$ ,  $\beta$  and  $V_A$  approaches infinity.  $v_{in,DC} = 0.9V$ ,  $v_{out,DC} = 2.5V$ ,  $V_{DD} = 5V$ . All transistors operate in the forward active region at  $T = 300$  K.

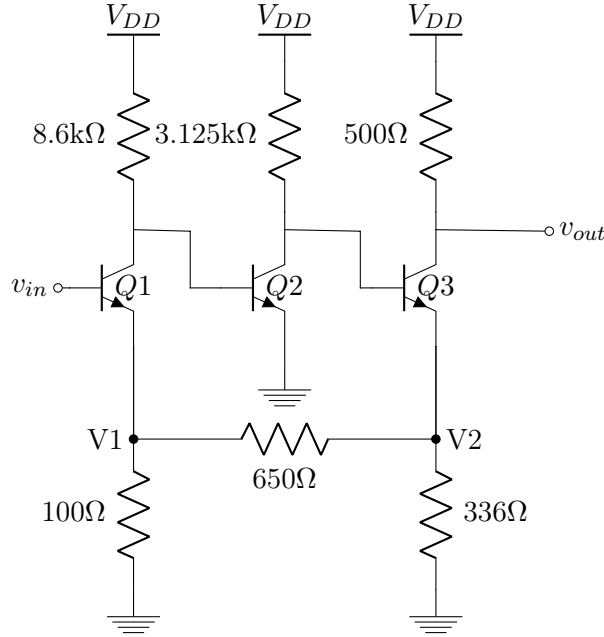


Figure 2: BJT Circuit

- (a) Solve for the collector currents,  $I_{C1}$ ,  $I_{C2}$ ,  $I_{C3}$ , and small signal  $g_{m1}$ ,  $g_{m2}$ ,  $g_{m3}$  for transistors Q1, Q2, and Q3 (3 pts)

- $I_{C1}$  and  $I_{C3}$  can be solved readily by nodal equations in the collector terminals of Q1 and Q3

$$I_{C1} = \frac{V_{DD} - V_{be2}}{8.6k\Omega} = \boxed{0.5mA}$$

$$I_{C3} = \frac{V_{DD} - V_{OUT,DC}}{500\Omega} = \boxed{5mA}$$

For  $I_{C2}$ , the value of V2 must be solved first. Note that  $V1 = v_{in,DC} - 0.7V = 0.2V$ . The nodal equation at node V2 is

$$I_{C3} = \frac{V2 - V1}{650\Omega} + \frac{V2}{336\Omega}$$

$$V2 = 1.175V$$

$$I_{C2} = \frac{V_{DD} - V_{be3} - V2}{3.125k\Omega} = \boxed{1mA}$$

The small signal gms are

$$g_{m1} = \frac{I_{C1}}{26mV} = \boxed{19.23mS}$$

$$g_{m2} = \frac{I_{C2}}{26mV} = \boxed{38.46mS}$$

$$g_{m3} = \frac{I_{C3}}{26mV} = \boxed{192.3mS}$$

- (b) Identify the feedback configuration (1 pt)

The feedback configuration is series-series

- (c) Draw the two-port network of the feedback circuit then solve for the feedback parameters  $R_{i,fb}$ ,  $R_{o,fb}$ , and feedback factor F (4 pts)

The two-port network of the feedback circuit is shown in Figure 3. Since this is a series-series feedback, the input is a current  $i_{in}$  and supplies a voltage  $V_{fb}$  to some load.

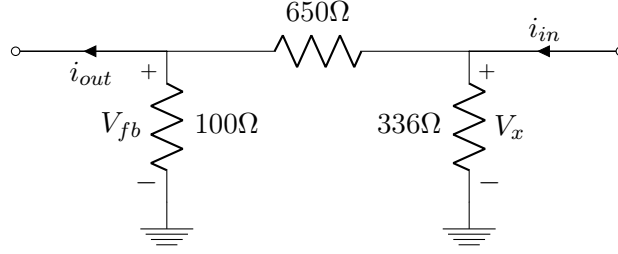


Figure 3: Feedback circuit

To get  $R_{i,fb}$ , set  $i_{out}$  to zero to satisfy a no-load condition then get equivalent resistance seen at  $i_{in}$ .

$$R_{i,fb} = 336 \parallel (650 + 100) = \boxed{232\Omega}$$

To get  $R_{o,fb}$ , set  $i_{in}$  to zero to satisfy a zero-input condition then get equivalent resistance seen at  $i_{out}$ .

$$R_{o,fb} = 100 \parallel (650 + 336) = \boxed{90.79\Omega}$$

The feedback factor F, is

$$\begin{aligned} F &= \frac{V_{fb}}{i_{in}} \\ &= \frac{336}{336 + 650 + 100} 100 \\ &= \boxed{30.94 \frac{V}{A}} \end{aligned}$$

- (d) Solve for the loaded open-loop "gain" (depends on your answer in (b) ) (2 pts)

Since the feedback configuration is series-series, an open-loop transconductance gain is expected. Moreover, the load resistance  $R_L$  is not part of the forward path for the open-loop transconductance. Figure 4 shows the small-signal equivalent circuit.

To solve for the open-loop forward transconductance gain, set the feedback factor F to zero and absorb the feedback resistances to the forward path. Moreover, since the  $\beta$ 's of the transistors approach infinity, the circuit can be divided into three stages with corresponding gains such that

$$\frac{i_{out}}{v_e} = \frac{v_{o1}}{v_e} \frac{v_{o2}}{v_{o1}} \frac{i_{out}}{v_{o2}}$$

where  $V_e$  is the voltage across  $V_{in}$  to node 1.

For the first stage, it can be noted that it is a degenerated common-emitter amplifier. Therefore the gain  $\frac{v_{o2}}{v_{o1}}$  can be written as

$$\begin{aligned} \frac{v_{o1}}{v_{in}} &= -\frac{g_{m1} R_{C1}}{1 + g_{m1} R_{o,fb}} \\ &= \boxed{-60.23V/V} \end{aligned}$$

For the second stage, it is a simple common-emitter amplifier. Therefore its voltage gain can be solved using

$$\begin{aligned}\frac{v_{o2}}{v_{o1}} &= -g_{m2}R_{C2} \\ &= \boxed{-120.23\text{V/V}}\end{aligned}$$

For the third stage, it is again an emitter-degenerated common-emitter amplifier. Therefore its transconductance can be solved using

$$\begin{aligned}\frac{i_{out}}{v_{o2}} &= \frac{g_{m3}}{1 + g_{m3}R_{i,fb}} \\ &= \boxed{4.216\text{mS}}\end{aligned}$$

Therefore, the open-loop transconductance gain is  $A_{f,OL} = (-60.23)(-120.23)(4.216\text{mS}) = \boxed{30.53 \text{ A/V}}$

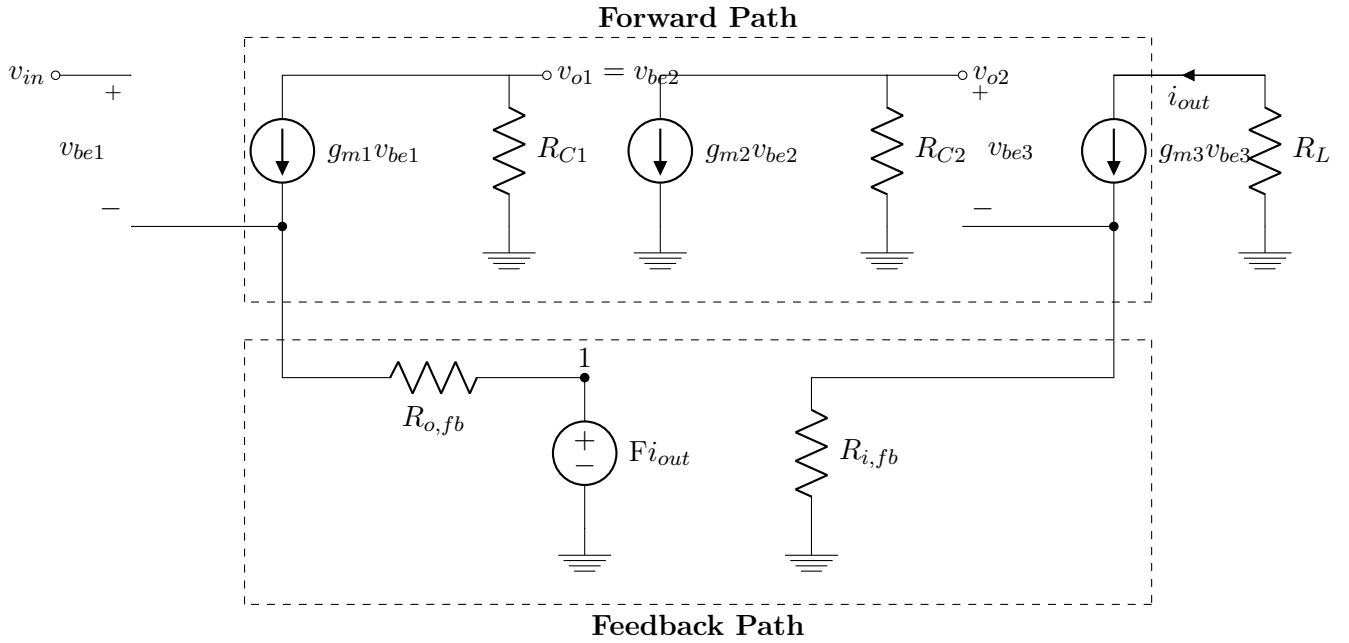


Figure 4: small signal circuit

- (e) Solve for the closed-loop voltage gain,  $\frac{v_{out}}{v_{in}}$  of the whole circuit (3 pts) First, solve for the closed loop transconductance gain of the whole circuit. From feedback analysis, the equation below can be written

$$\begin{aligned}A_{f,CL} &= \frac{i_{out}}{v_{in}} \\ &= \frac{A_{f,OL}}{1 + F A_{f,OL}} \\ &= \boxed{32.29\text{mS}}\end{aligned}$$

Note that  $v_{out} = -i_{out}R_L$ . Dividing both sides by  $v_{in}$ , the expression below can be obtained.

$$\begin{aligned}\frac{v_{out,CL}}{v_{in}} &= \frac{-i_{out}R_L}{v_{in}} \\ A_{v,CL} &= -A_{f,CL}R_L \\ &= \boxed{-16.14\text{V/V}}\end{aligned}$$

- (f) Suppose the open-loop "gain" increased by 10%, by how much is the approximate increase, in percentage, of the closed-loop voltage gain? (2 pts)

It has been established in (e) that  $A_{v,CL} = -A_{f,CL}R_L$ . Express  $A_{f,CL}$  in the form where the loaded open-loop gain and feedback factor  $F$  is involved such that

$$A_{v,CL} = -\frac{A_{f,OL}R_L}{1 + FA_{f,OL}}$$

Get the derivative of both side to get the change of the closed loop gain with respect to a change in the open loop gain.

$$\begin{aligned} dA_{v,CL} &= d\left(-\frac{A_{f,OL}R_L}{1 + FA_{f,OL}}\right) \\ dA_{v,CL} &= \frac{R_L}{(1 + FA_{f,OL})^2}dA_{f,OL} \end{aligned}$$

To get the percentage change, divide it by the original expression. Also note that 10% change in open loop gain means  $\frac{dA_{f,OL}}{A_{f,OL}} = 0.1$ .

$$\begin{aligned} \frac{dA_{v,CL}}{A_{v,CL}} &= \frac{R_L}{(1 + FA_{f,OL})^2}dA_{f,OL} \cdot \frac{1}{A_{v,CL}} \\ &= \frac{R_L}{(1 + FA_{f,OL})^2}dA_{f,OL} \cdot \frac{1 + FA_{f,OL}}{A_{f,OL}R_L} \\ &= \frac{dA_{f,OL}}{A_{f,OL}} \cdot \frac{1}{1 + FA_{f,OL}} \\ &= 0.1 \cdot \frac{1}{1 + 30.94(30.53)} \\ &= .000105753 = \boxed{.0105753\%} \end{aligned}$$



### 3. Give Me Some More Feedback

Referring to Figure 3a:

- (a) The sampled feedback signal going to the input is voltage. Also, the signal sampled at the output is voltage. Therefore the feedback configuration is **series-shunt**.
- (b) The feedback circuit is shown:

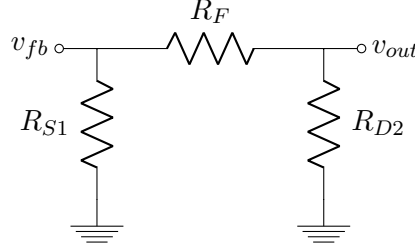


Figure 5: Feedback Circuit

From the feedback circuit above,  $R_{I,fb}$ ,  $R_{O,fb}$ , and  $F$  expressions can be extracted. To get  $R_{I,fb}$ , look at the resistance seen at  $v_{out}$  terminal while remaining  $v_{fb}$  terminal open(**series**).

$$R_{I,fb} = (R_{S1} + R_F) || R_{D2}$$

To get  $R_{O,fb}$ , look at the resistance seen at  $v_{fb}$  terminal while shorting(**shunt**) the  $v_{out}$  terminal.

$$R_{O,fb} = R_{S1} || R_F$$

The feedback factor  $F$  is:

$$F = \frac{v_{fb}}{v_{out}}$$

$$F = \frac{R_{S1}}{R_{S1} + R_F}$$

Next, the unilateral two-port equivalent circuit model of the feedback is shown in Figure 6.

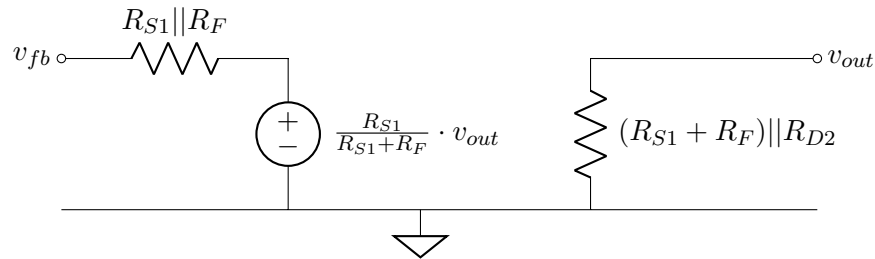


Figure 6: Unilateral Two-Port Model for Feedback Circuit

- (c) The small signal equivalent model for the amplifier+feedback is shown in Figure 7. Simply move the resistances ( $R_{I,fb}$ ,  $R_{O,fb}$ ) to the forward gain path to get the ideal feedback path.

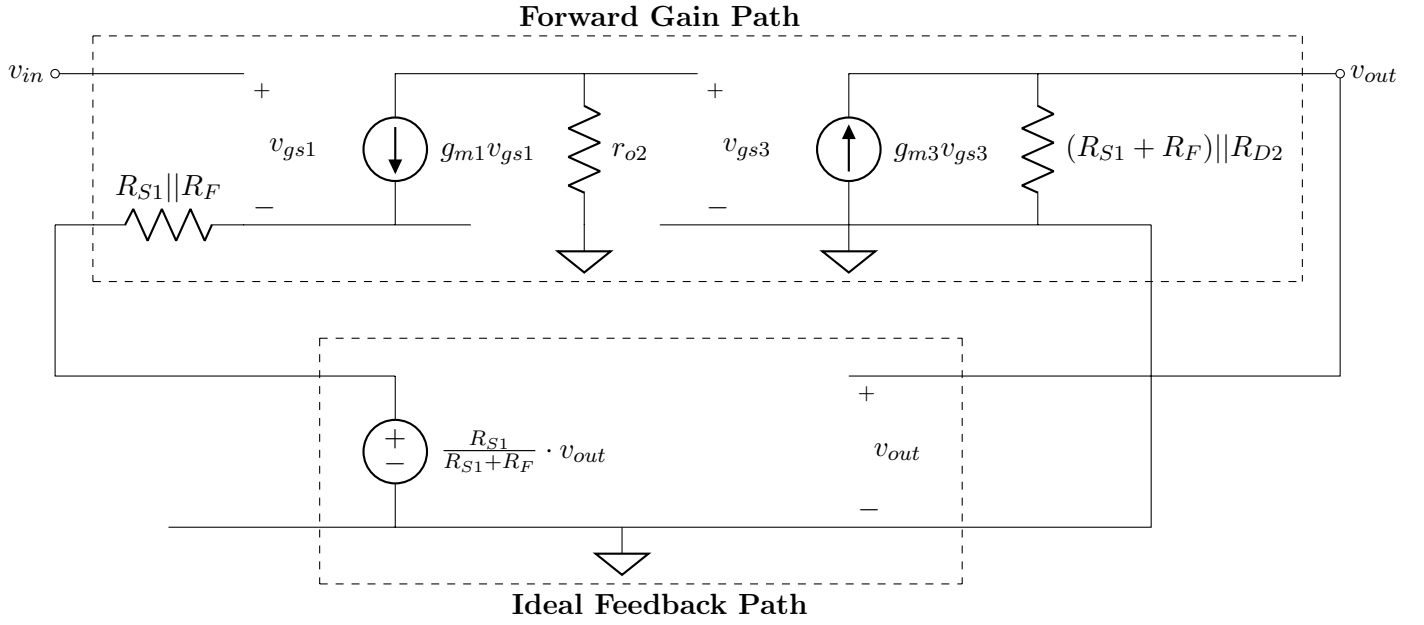


Figure 7: Small signal equivalent model for Amplifier+Feedback emphasizing **Forward Gain Path** and **Ideal Feedback Path**

- (d) The Amplifier is two stage both are Common Source configuration. To obtain the open loop gain/forward gain ( $A_{v,ol}$ ), set  $F = 0$  (shorting the dependent voltage source in the ideal feedback path). Now, the first stage is a common source with degenerated source resistance and the second stage is a simple common source.

$$A_{v,ol} = A_{v1} \cdot A_{v2}$$

$$= -\frac{g_{m1}r_{o2}}{1 + g_{m1}(R_{S1} || R_F)} \cdot -g_{m3}[(R_{S1} + R_F) || R_{D2}]$$

$$A_{v,ol} = \frac{g_{m1}g_{m3}r_{o2}[(R_{S1} + R_F) || R_{D2}]}{1 + g_{m1}(R_{S1} || R_F)}$$

$$A_{v,ol} = 32.695 \text{ V/V}$$

- (e) For Loop Gain ( $T$ ):

$$T = A_{v,ol} \cdot F$$

$$T = \frac{g_{m1}g_{m3}r_{o2}[(R_{S1} + R_F) || R_{D2}]}{1 + g_{m1}(R_{S1} || R_F)} \cdot \frac{R_{S1}}{R_{S1} + R_F}$$

$$T = 16.348$$

- (f) For closed-loop gain ( $A_{v,cl}$ ):

$$A_{v,cl} = \frac{A_{v,ol}}{1 + T}$$

$$A_{v,cl} = \frac{\frac{g_{m1}g_{m3}r_{o2}[(R_{S1} + R_F) || R_{D2}]}{1 + g_{m1}(R_{S1} || R_F)}}{1 + \left( \frac{g_{m1}g_{m3}r_{o2}[(R_{S1} + R_F) || R_{D2}]}{1 + g_{m1}(R_{S1} || R_F)} \cdot \frac{R_{S1}}{R_{S1} + R_F} \right)}$$

$$A_{v,cl} = 1.885 \text{ V/V}$$

- (g) To compute for the closed loop output resistance, must first find the expression for the open loop resistance  $R_{O,ol}$ .

$$R_{O,ol} = (R_{S1} + R_F) || R_{D2}$$

For closed loop output resistance:

$$R_{O,cl} = \frac{R_{O,ol}}{1 + T}$$

$$R_{O,cl} = \frac{(R_{S1} + R_F) || R_{D2}}{1 + \left( \frac{g_{m1}g_{m3}r_{o2}[(R_{S1}+R_F)||R_{D2}]}{1+g_{m1}(R_{S1}||R_F)} \cdot \frac{R_{S1}}{R_{S1}+R_F} \right)}$$

$$R_{O,cl} = 115.29\Omega$$

Referring to Figure 3b:

- (h) No, Feedback configuration (**series-shunt**) is still the same.  $M_4$  accepts the sampled voltage from the feedback and outputs a voltage that goes to the input of the main amplifier depending what type of amplifier configuration  $M_4$  is.
- (i) The feedback circuit is shown:

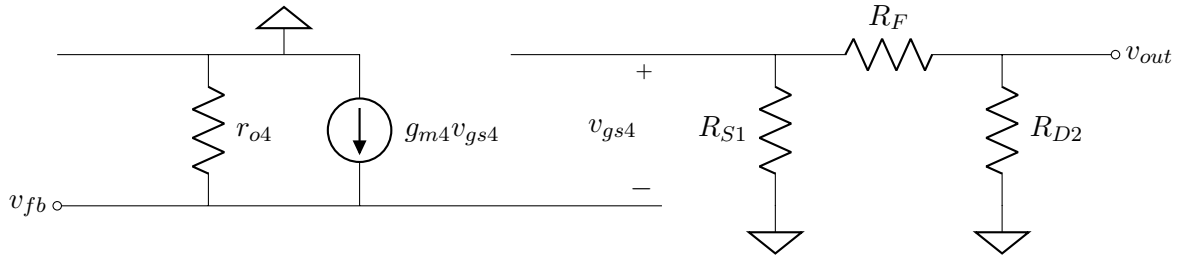


Figure 8: Feedback Circuit with  $M_4$

From the feedback circuit,  $R_{I,fb}$ ,  $R_{O,fb}$ , and  $F$  can be obtained:

$$R_{I,fb} = (R_{S1} + R_F) || R_{D2}$$

$$R_{O,fb} = r_{o4} || \frac{1}{g_{m4}}$$

$$F = \frac{g_{m4}r_{o4}}{1 + g_{m4}r_{o4}} \cdot \frac{R_{S1}}{R_{S1} + R_F}$$

Next, the unilateral two-port model of the feedback is shown in Figure 9.

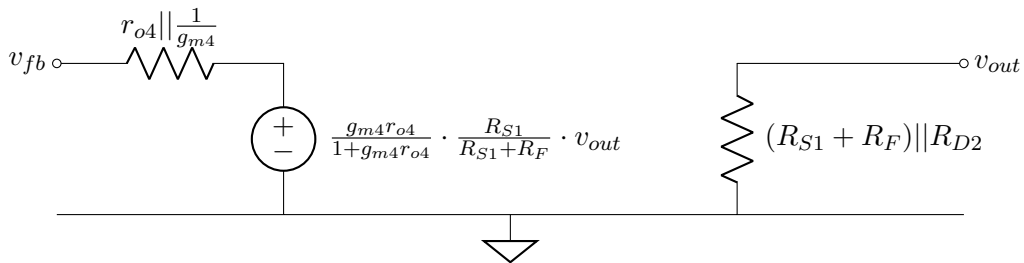


Figure 9: Unilateral Two-Port Model for Feedback Circuit with  $M_4$

The small signal equivalent for the amplifier+feedback is shown in Figure 10.

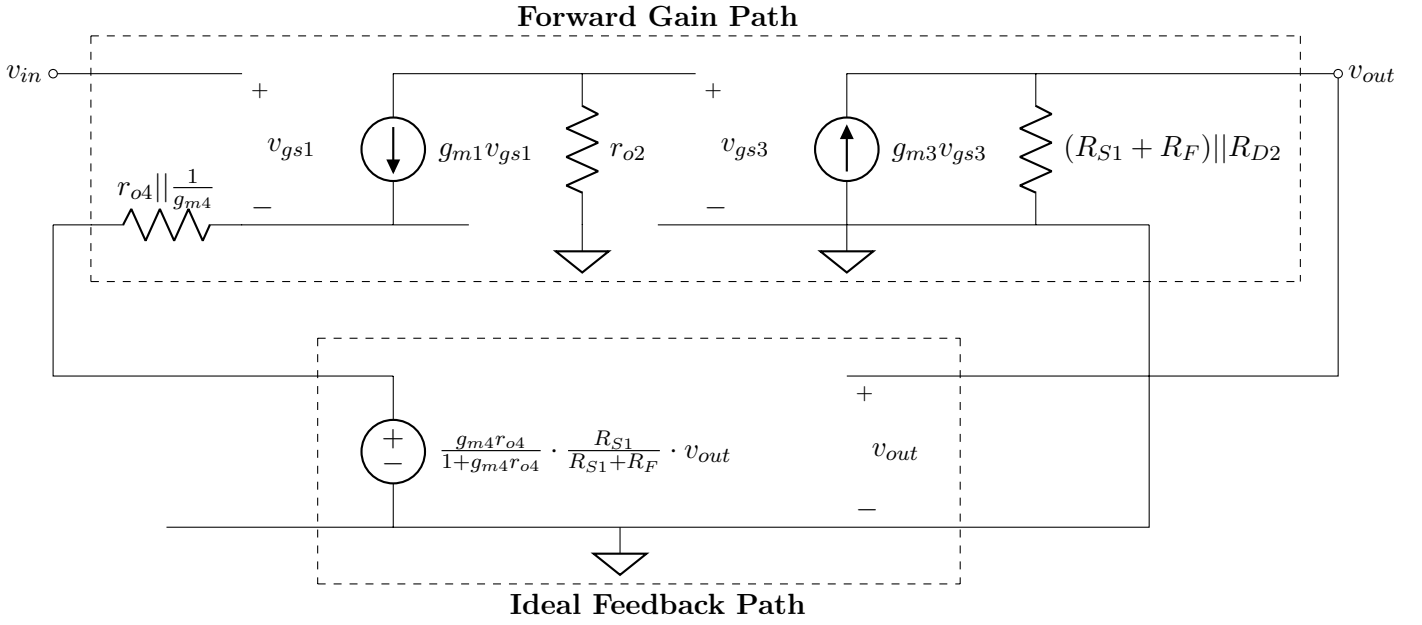


Figure 10: Small signal equivalent model for Amplifier+Feedback with  $M_4$  in Feedback emphasizing **Forward Gain Path** and **Ideal Feedback Path**

The open-loop gain/forward gain ( $A_{v,ol}$ ) is:

$$A_{v,ol} = -\frac{g_{m1}r_{o2}}{1 + g_{m1}\left(r_{o4} \parallel \frac{1}{g_{m4}}\right)} \cdot -g_{m3}[(R_{S1} + R_F) \parallel R_{D2}]$$

$$A_{v,ol} = \frac{g_{m1}g_{m3}r_{o2}[(R_{S1} + R_F) \parallel R_{D2}]}{1 + g_{m1}\left(r_{o4} \parallel \frac{1}{g_{m4}}\right)}$$

$$A_{v,ol} = 144.07 \text{ V/V}$$

The Loop Gain ( $T$ ) is:

$$T = \frac{g_{m1}g_{m3}r_{o2}[(R_{S1} + R_F) \parallel R_{D2}]}{1 + g_{m1}\left(r_{o4} \parallel \frac{1}{g_{m4}}\right)} \cdot \frac{g_{m4}r_{o4}R_{S1}}{(1 + g_{m4}r_{o4})(R_{S1} + R_F)}$$

$$T = 71.349$$

The closed-loop gain ( $A_{v,cl}$ ) is:

$$A_{v,cl} = \frac{\frac{g_{m1}g_{m3}r_{o2}[(R_{S1} + R_F) \parallel R_{D2}]}{1 + g_{m1}\left(r_{o4} \parallel \frac{1}{g_{m4}}\right)}}{1 + \left(\frac{g_{m1}g_{m3}r_{o2}[(R_{S1} + R_F) \parallel R_{D2}]}{1 + g_{m1}\left(r_{o4} \parallel \frac{1}{g_{m4}}\right)} \cdot \frac{g_{m4}r_{o4}R_{S1}}{(1 + g_{m4}r_{o4})(R_{S1} + R_F)}\right)}$$

$$A_{v,cl} = 1.991 \text{ V/V}$$

The closed loop output resistance ( $R_{O,cl}$ ) is:

$$R_{O,cl} = \frac{R_{O,ol}}{1 + T}$$

$$R_{O,cl} = \frac{(R_{S1} + R_F) || R_{D2}}{1 + \left( \frac{g_{m1}g_{m3}r_{o2}[(R_{S1} + R_F) || R_{D2}]}{1 + g_{m1} \left( r_{o4} || \frac{1}{g_{m4}} \right)} \cdot \frac{g_{m4}r_{o4}R_{S1}}{(1 + g_{m4}r_{o4})(R_{S1} + R_F)} \right)}$$

$$R_{O,cl} = 27.644\Omega$$

- (j) The closed-loop gain and output resistance for the resistive only feedback are  $A_{v,cl} = 1.885$  and  $R_{O,cl} = 115.29\Omega$  while the resistive feedback with transistor  $M_4$  are  $A_{v,cl} = 1.991$  and  $R_{O,cl} = 27.644\Omega$ . It shows that inserting the transistor  $M_4$  shows an improvement on both the  $A_{v,cl}$  and  $R_{O,cl}$ . This is because  $M_4$  is a source follower/common drain configuration which has the advantage of a very low output impedance that does not load or serves as a buffer of the sampled voltage from the resistive feedback going to the input of the main amplifier.

TOTAL: 45 points.