

Lecture 15

THREE PHASE TRANSFORMER ADVANCED TOPICS

Agenda

R.D. del Mundo
Ivan B.N.C. Cruz
Christian. A. Yap



cysales01@chuangy.com

www.chuangy.com

FROM SINGLE PHASE TO
THREE PHASE




Lecture Outcomes


at the end of the lecture, the student must be able to ...

- Understand how phase shifts manifests in three-phase transformers
- Derive the models for different types of three-phase transformers


Phase Shifts in Three-Phase Transformers

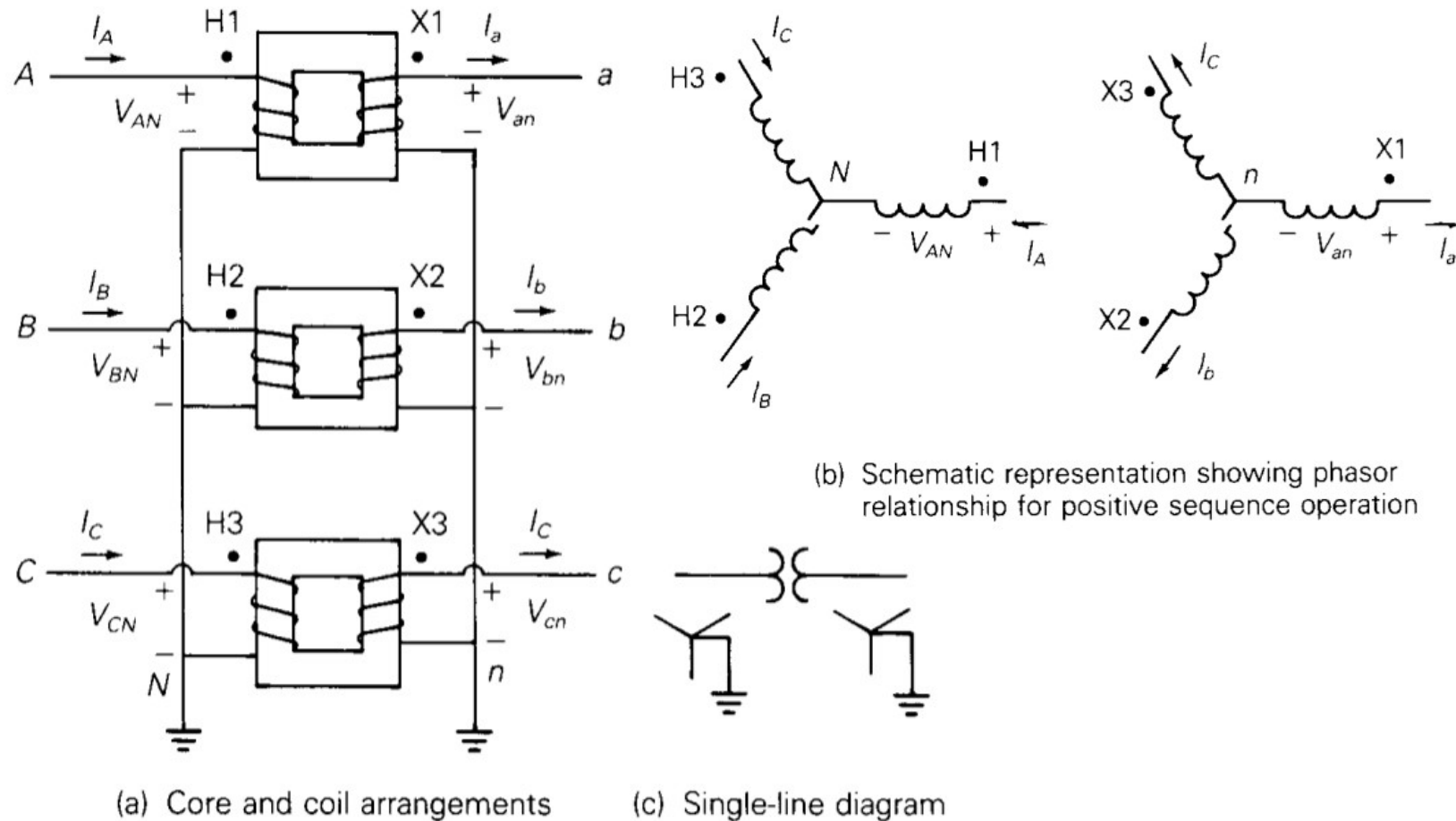


Phase Shifts in Three-Phase Transformers

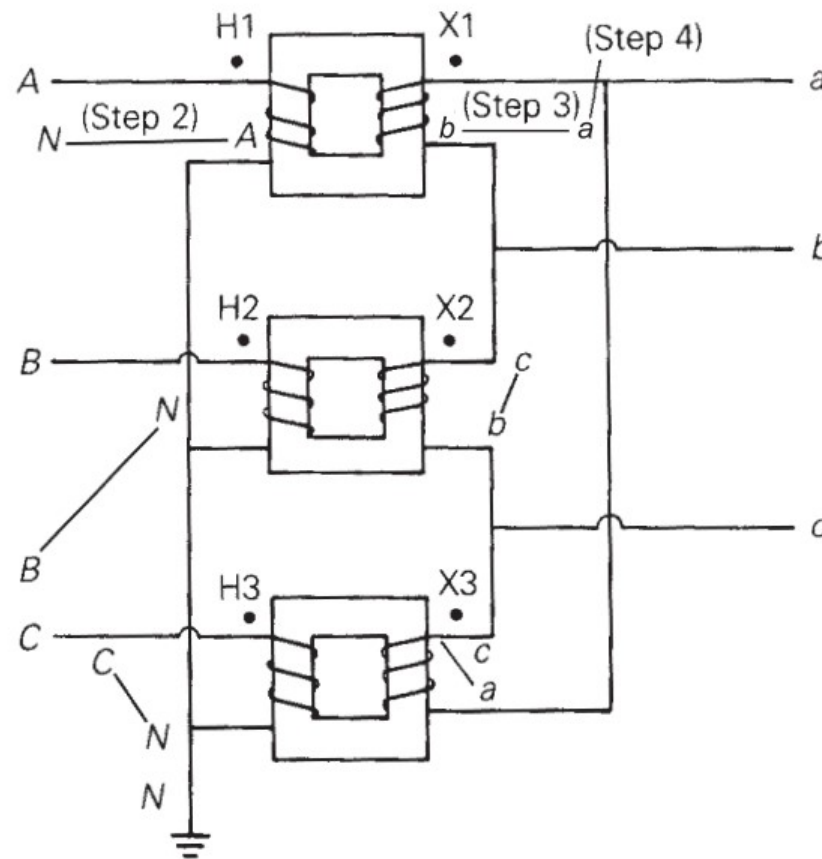

(a) Core and coil arrangement

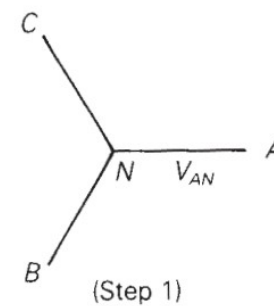


(b) Positive-sequence phasor diagram

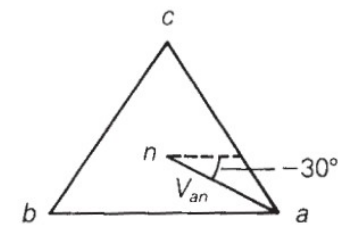


(Step 5)

Three-Phase Transformer


Transformer Core

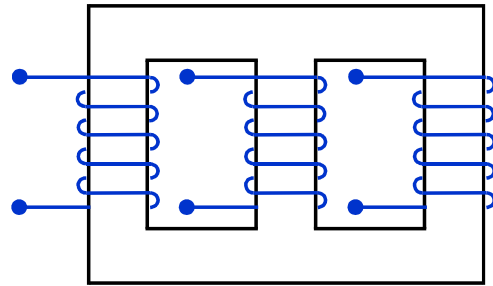

3-Legged Core Type

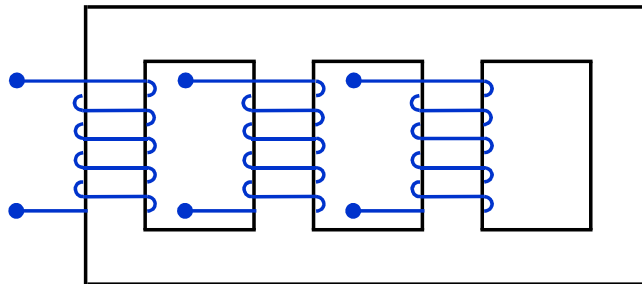

4-Legged Core Type

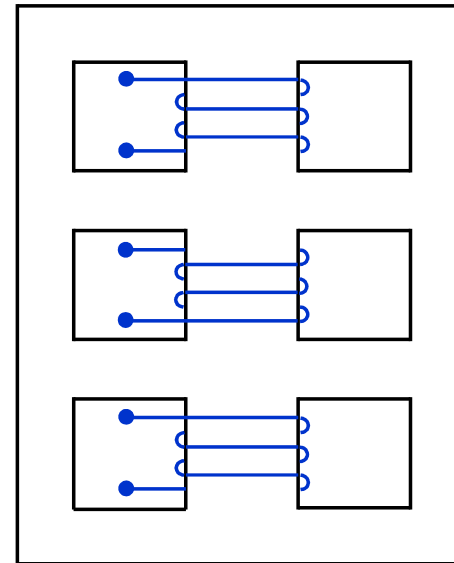


Shell Type

Note: Only the X windings are shown.

Three-Phase Transformer

Three-Legged Transformer Core

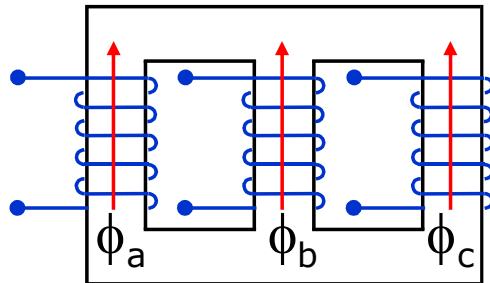The 3-legged core type three-phase transformer uses the minimum amount of core material. For balanced three-phase condition, the sum of the fluxes is zero.



Note: For positive- or negative-sequence flux,

$$\phi_a + \phi_b + \phi_c = 0$$

The 3-legged core type three-phase transformer does not provide a path for zero-sequence flux. On the other hand, a bank of single-phase units, the 4-legged core type and the shell-type three-phase transformer provide a path for zero-sequence flux.

Equivalent Circuit of Transformers

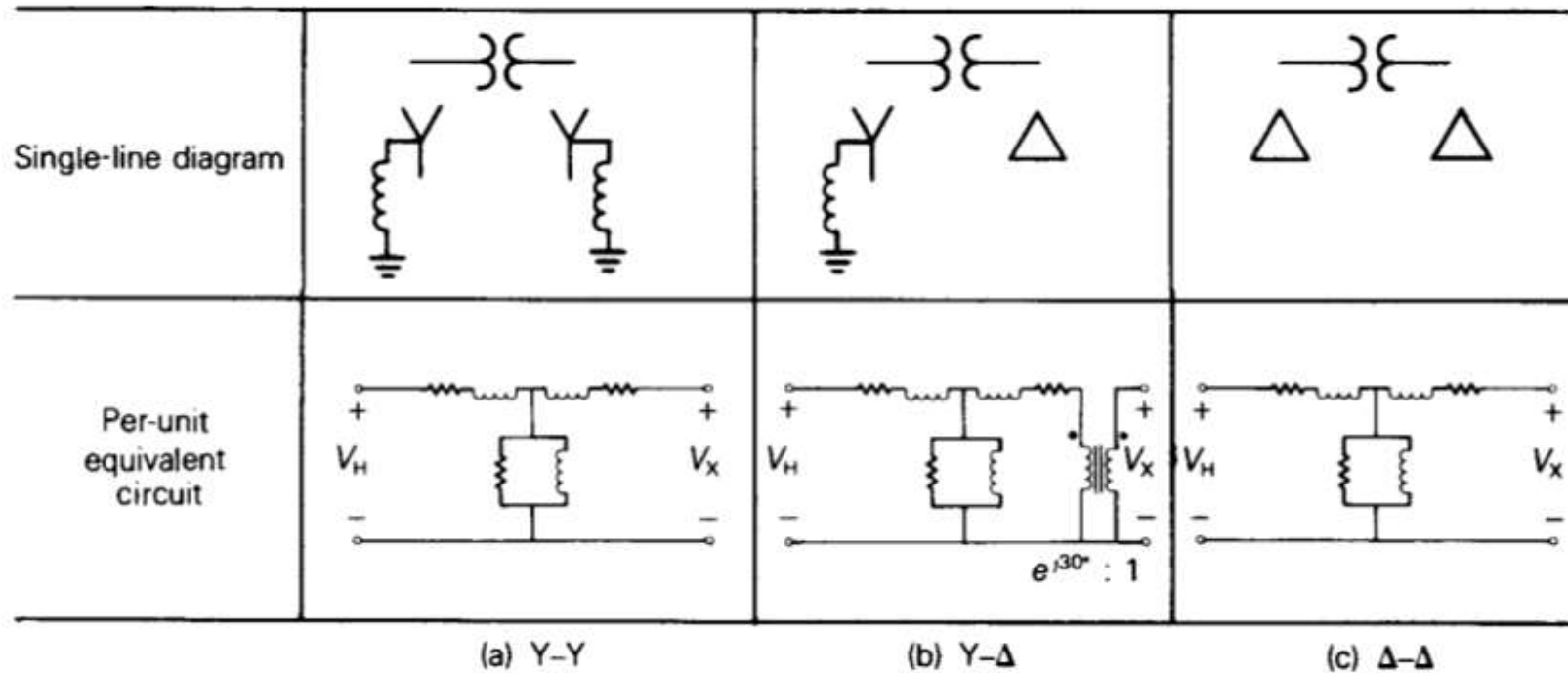



FIGURE 3.17 Per-unit equivalent circuits of practical Y-Y, Y-Δ, and Δ-Δ transformers for balanced three-phase operation

Equivalent Circuit of Transformers

Positive & Negative Sequence Networks


Y-Y and Δ - Δ connected transformers (in per unit)

Assuming Large power transformer

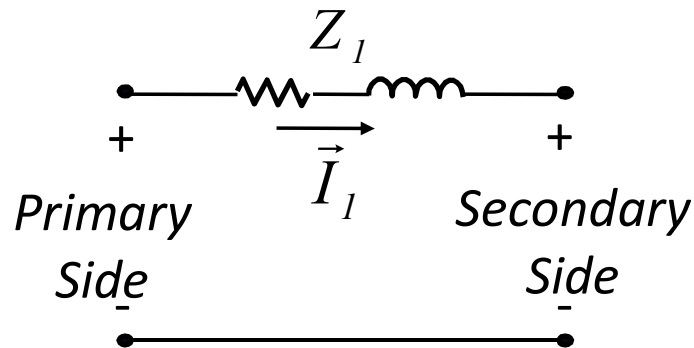

*Positive
Sequence
Network*

$$Z_1 = Z_2$$

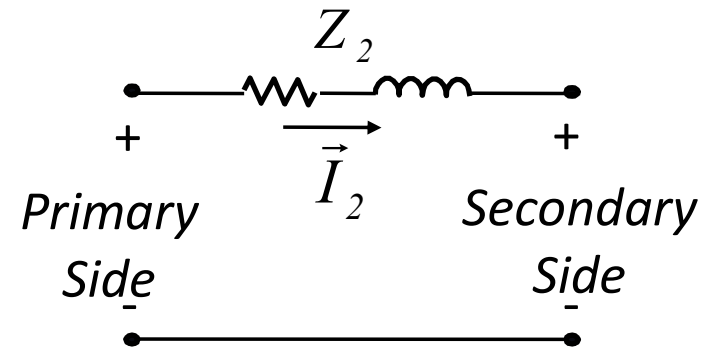


*Negative
Sequence
Network*


Equivalent Circuit of Transformers

Zero-Sequence Network

ZERO-SEQUENCE CURRENTS:

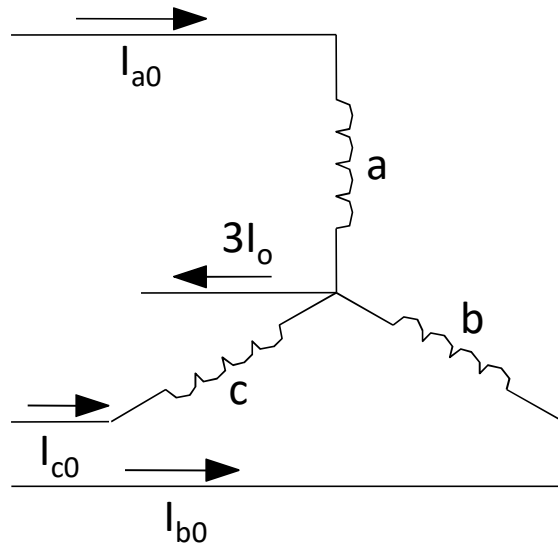

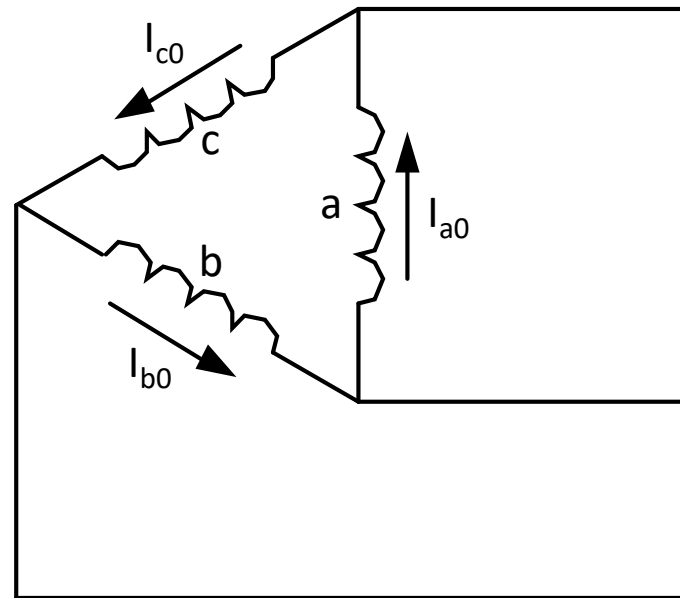The neutral return carries the in-phase zero-sequence currents.




Zero-sequence currents circulates in the delta-connected transformers. There is "balancing ampere turns" for the zero-sequence currents.



Equivalent Circuit of Transformers

*Zero Sequence Network**

Transformer Connection

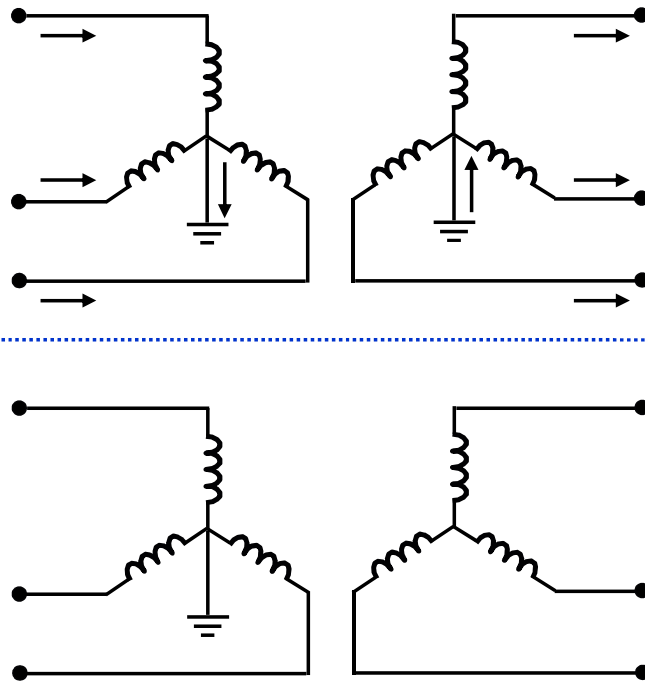

Zero-Sequence Network

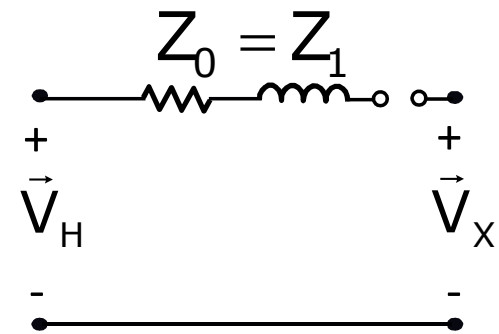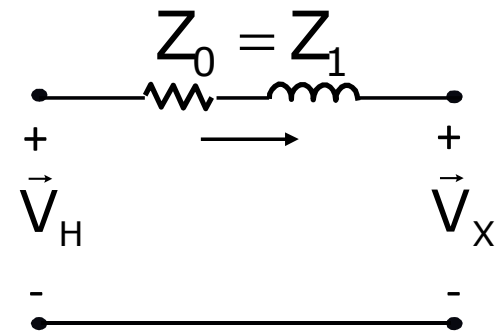


*Excluding 3-phase unit with a 3-legged core.



Equivalent Circuit of Transformers

*Zero Sequence Network **

Transformer Connection

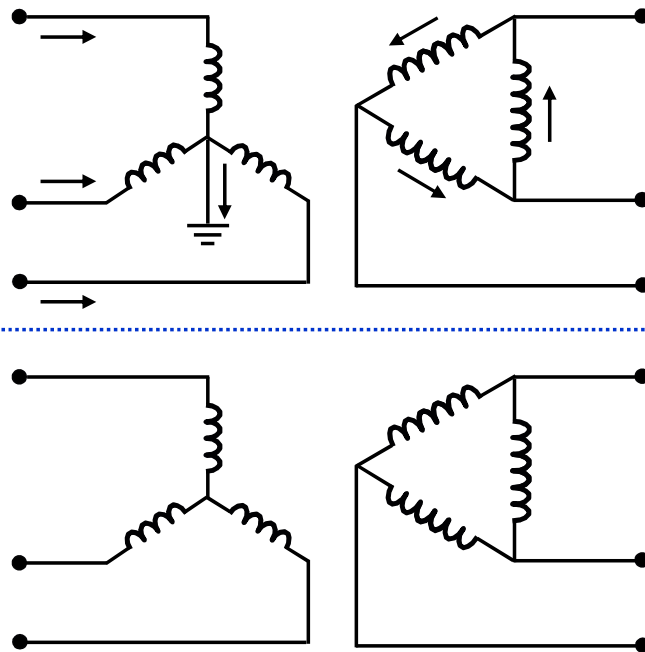

Zero-Sequence Network

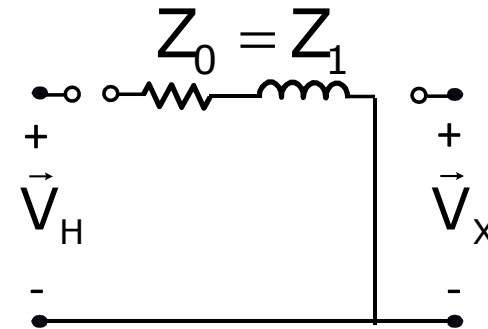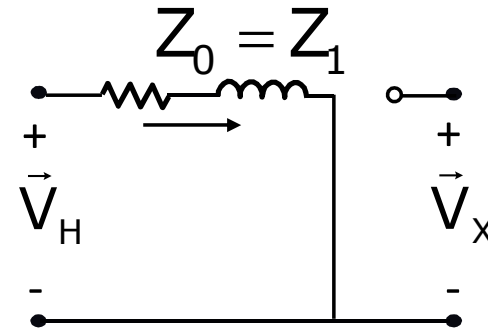


*Excluding 3-phase unit with a 3-legged core.


Equivalent Circuit of Transformers

*Zero Sequence Network **

Transformer Connection

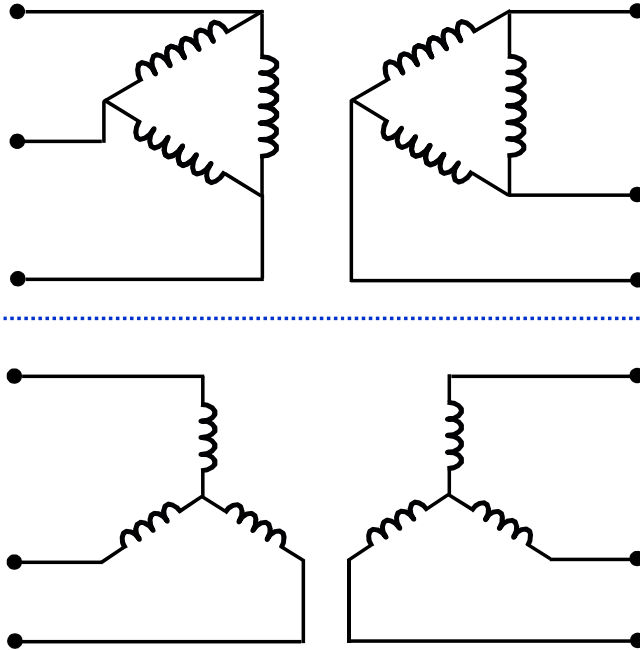


Zero-Sequence Network

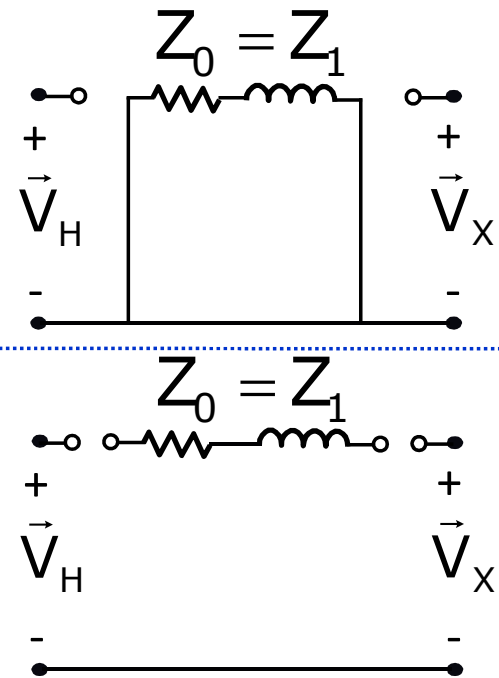


*Excluding 3-phase unit with a 3-legged core.

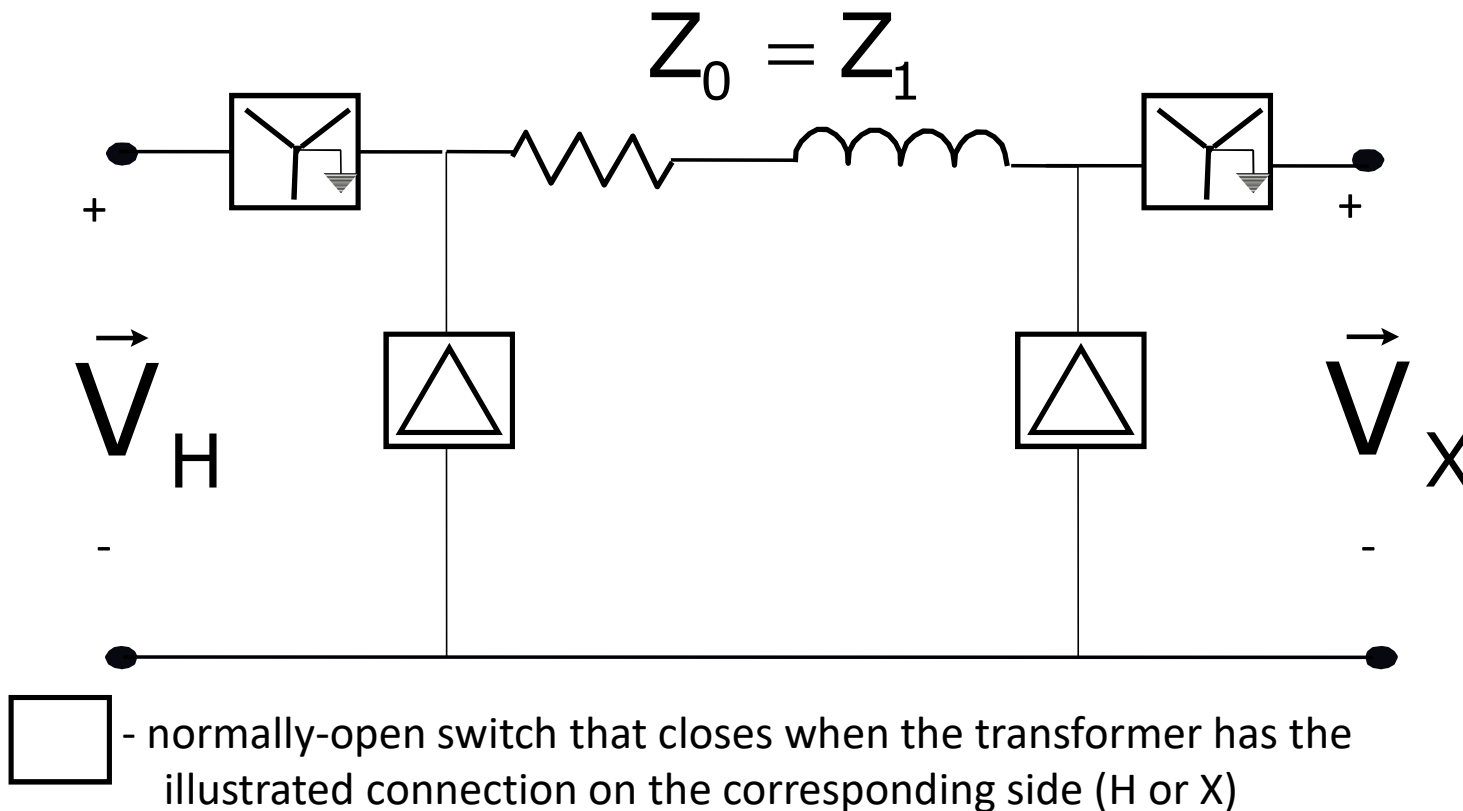A Mnemonic Zero-Sequence Equivalent Circuit of Three-Phase Transformers



Referred Impedances (3-phase transformers)

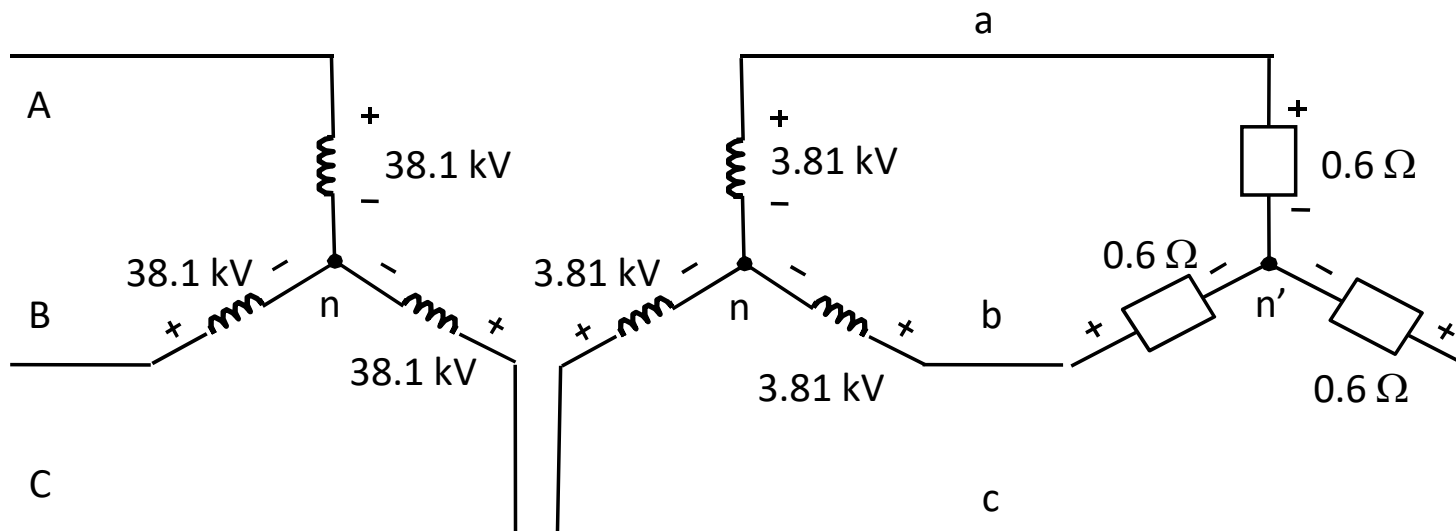Consider a 3-phase wye-connected load, $0.6\text{-}\Omega/\text{phase}$. Three single-phase transformers are used, each rated 25 MVA, 38.1/3.81 kV, connected wye-wye, to serve the 3-phase load.



Referred Impedances (3-phase transformers)


Assuming we have a balanced system, we can consider each $0.6\text{-}\Omega$ resistor to be directly connected across 3.81-kV winding, with or without the neutral conductor. On the high-voltage side the impedance measured from line to neutral is:

$$0.6\Omega \cdot \left(\frac{38.1\text{kV}}{3.81\text{kV}} \right)^2 = 0.6\Omega \cdot \left(\frac{66\text{kV}}{6.6\text{kV}} \right)^2 = 60\Omega$$

Note: 66-kV line-to-line = 38.1-kV line-to-neutral,
and 6.6-kV line-to-line = 3.81-kV line-to-neutral.

Referred Impedances (3-phase transformers)

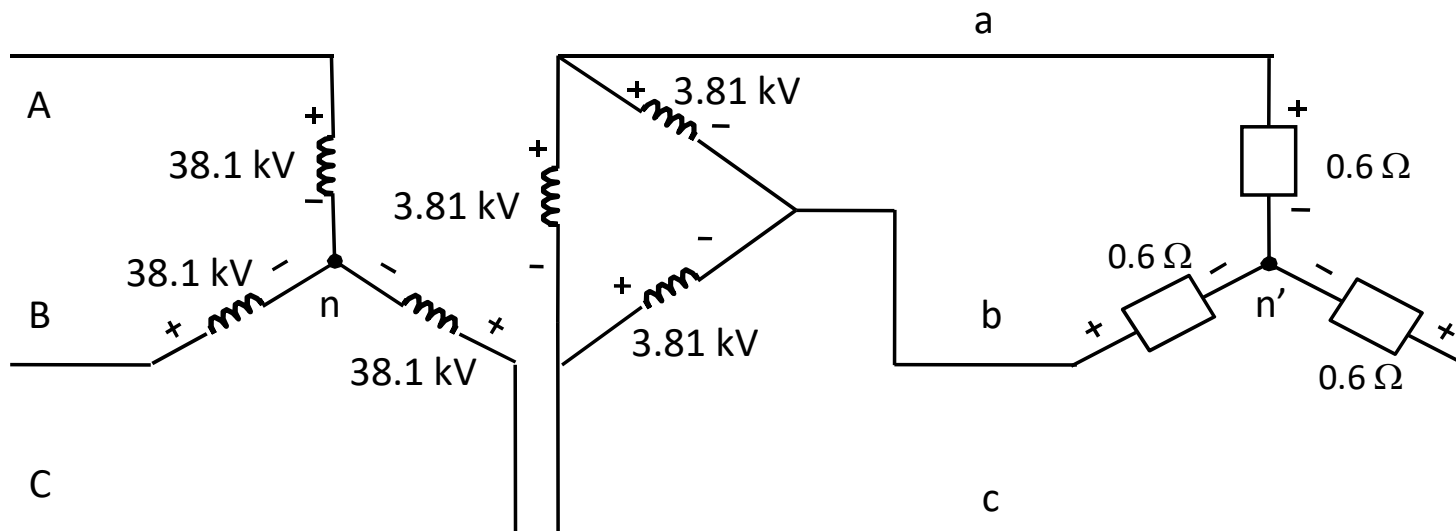Let us consider the same 3-phase wye-connected load, $0.6\text{-}\Omega/\text{phase}$, and the same 3 single-phase transformer (25 MVA, 38.1/3.81 kV). If we connect the transformers wye-delta:



Referred Impedances (3-phase transformers)


With the same assumptions as before, we can convert the low-voltage side of the transformer from delta- to wye-connected; the secondary voltage will change from 3.81 kV_{LL} to 2.2 kV_{LN} = (3.81 kV / √3).

$$0.6\Omega \cdot \left(\frac{38.1kV}{2.2kV} \right)^2 = 0.6\Omega \cdot \left(\frac{66kV}{3.81kV} \right)^2 = 180\Omega$$

Note: To transfer the ohmic value of impedances from one side of a three-phase transformer to the other side, the multiplying factor is the square of the ratios of the line-to-line voltage, regardless of transformer connection.



Concept Test:

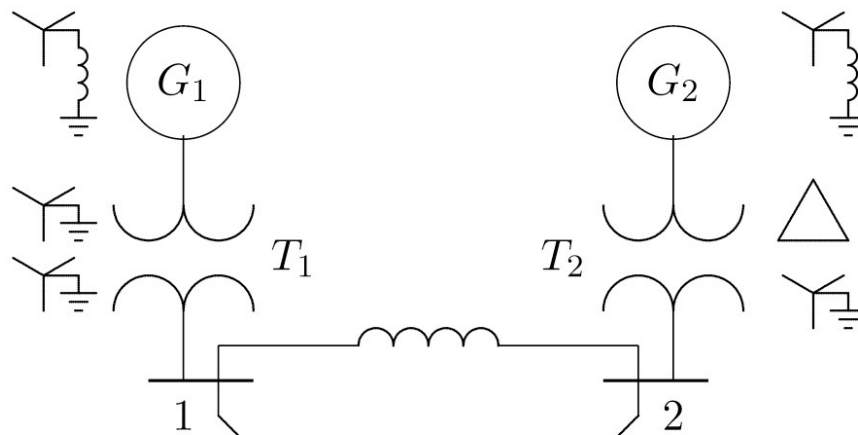1. Draw the positive-sequence impedance diagram for the system shown.
2. Draw the zero-sequence impedance diagram for the system shown



$$\begin{aligned}
 &X_{G1}^{(1)}, X_{G1}^{(0)}, X_{G1n} \\
 &X_{G2}^{(1)}, X_{G2}^{(0)}, X_{G2n} \\
 &X_{T1}^{(1)} = X_{T1}^{(0)} \\
 &X_{T2}^{(1)} = X_{T2}^{(0)} \\
 &X_L^{(1)}, X_L^{(0)}
 \end{aligned}$$

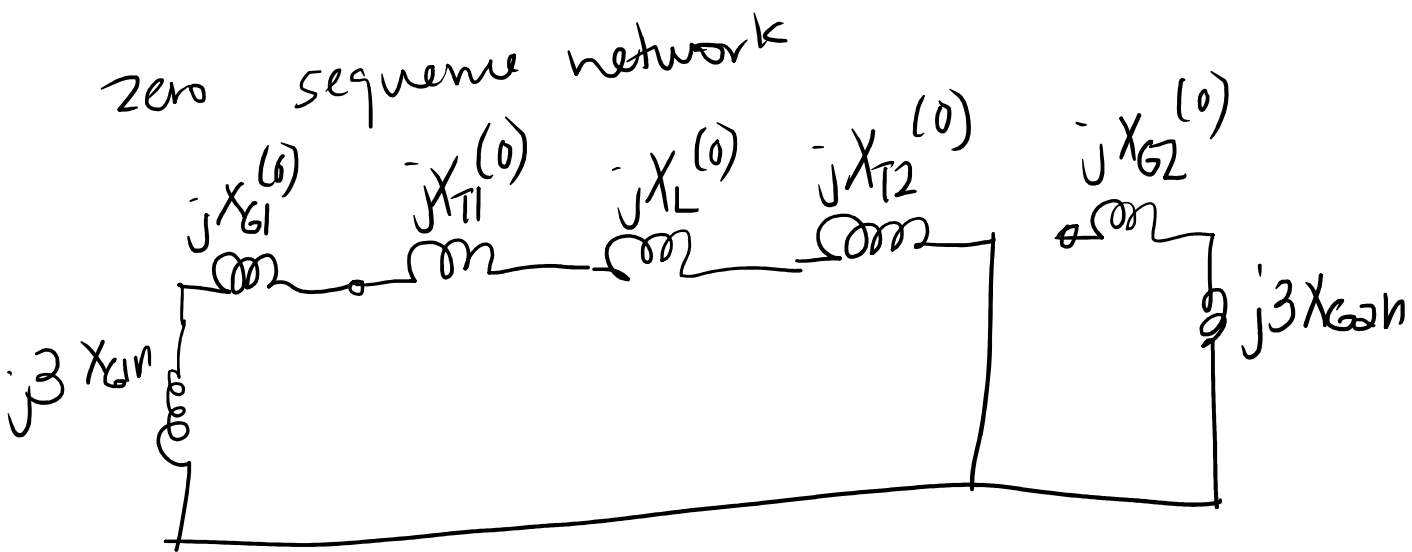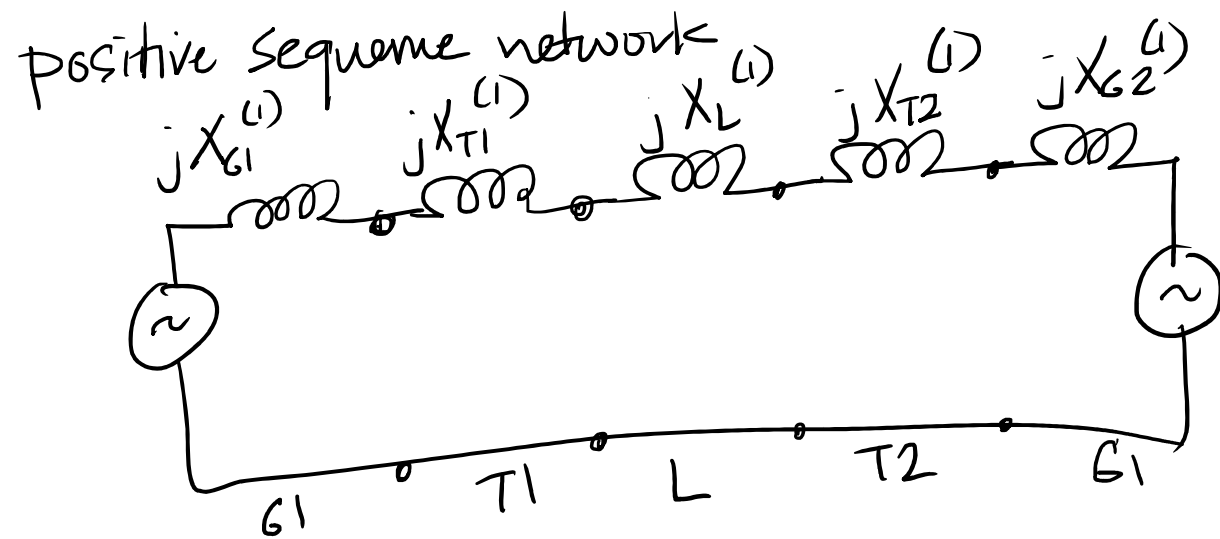Note: we are particularly interested on the generator and transformer models.



END