



EEE 51: Second Semester 2017 - 2018

Lecture 3

Two-Port Networks

Single-Stage Amplifiers




Today

- Two-Port Networks
- Single-Stage Amplifiers



Two-Port Network Reduction

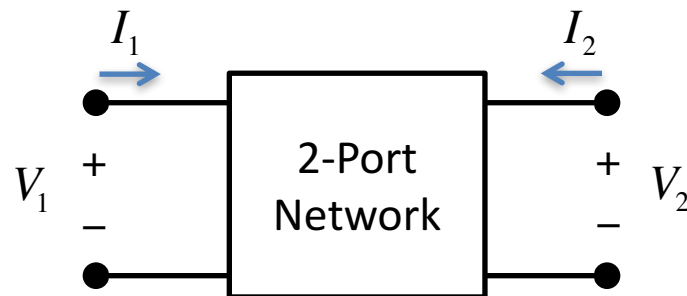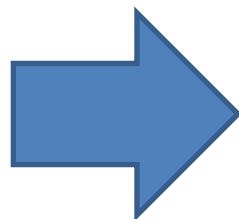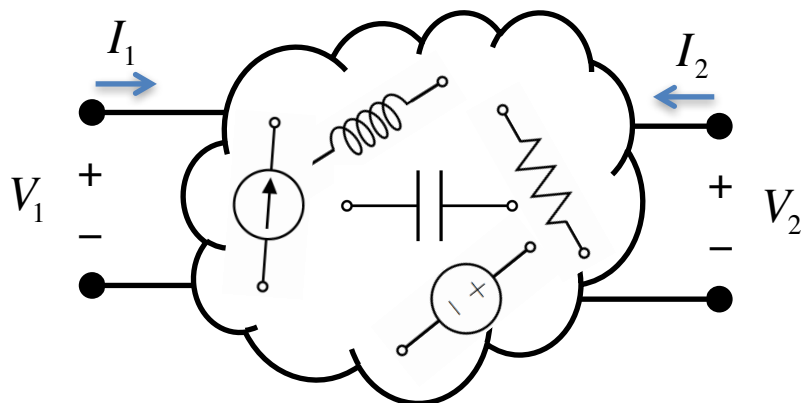- Can reduce any linear circuit into 4 parameters



Given 2 terminal parameters (V or I),
we can get the other 2 (V or I)

Linear \rightarrow R, L, C, dependent sources


How convenient are
these representations
for EEE 51?

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} \quad \begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$


$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \quad \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

The Bilateral Hybrid- π Two-Port Network

Thevenin equivalent:

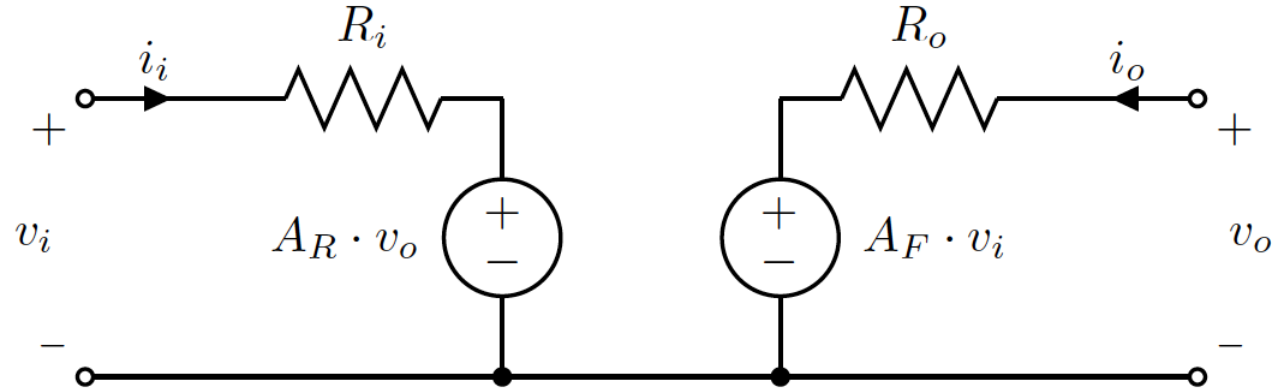

Norton equivalent:

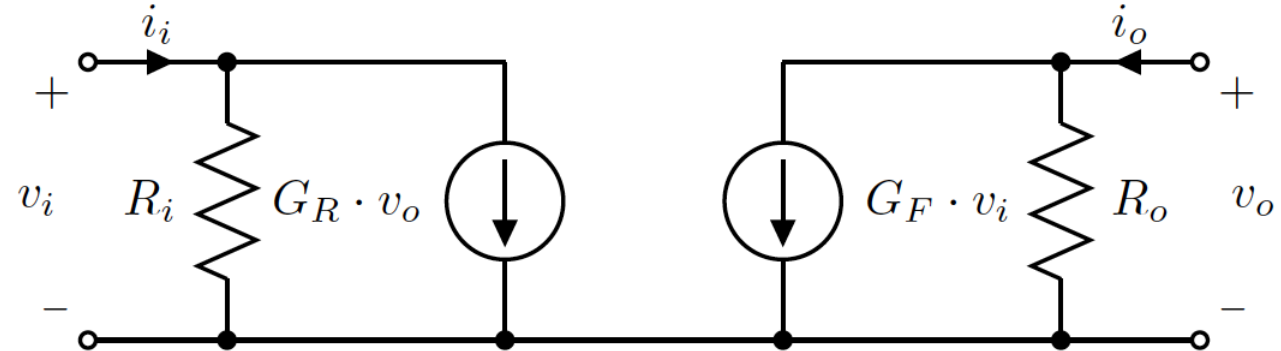


Unilateral equivalents?



The Unilateral Hybrid- π Two-Port Network


- Requires only 3 parameters

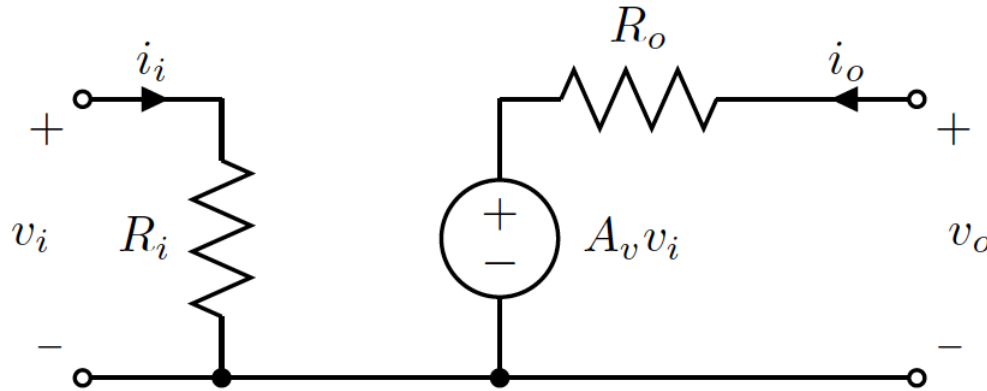

The Thevenin Equivalent
(R_i , A_v , R_o)


The Norton Equivalent
(R_i , G_m , R_o)

Looks very familiar...

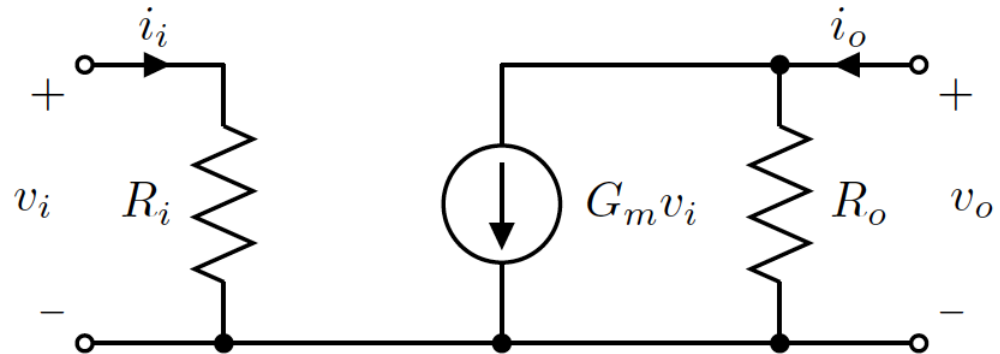


Operating Conditions (1)

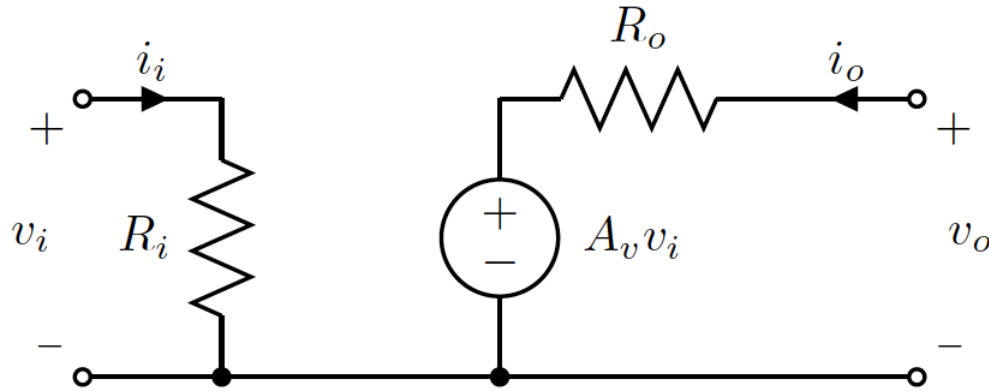- **No-Load** → No power draw at the output



Open circuit
 $i_o = 0$

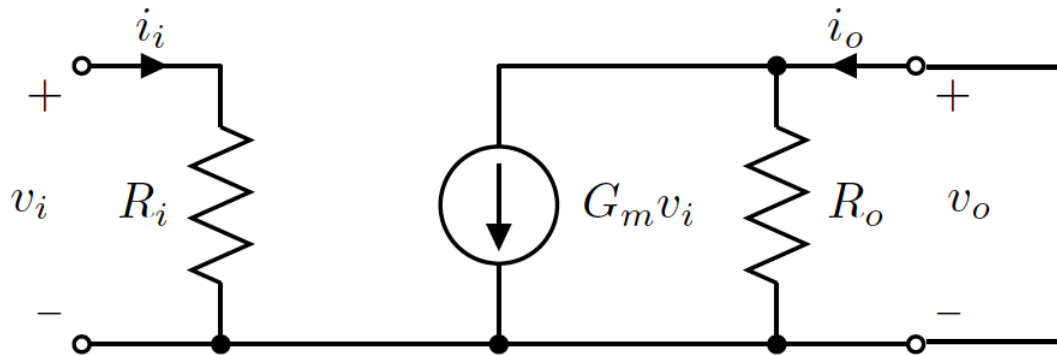


Short circuit
 $v_o = 0$



Operating Conditions (2)

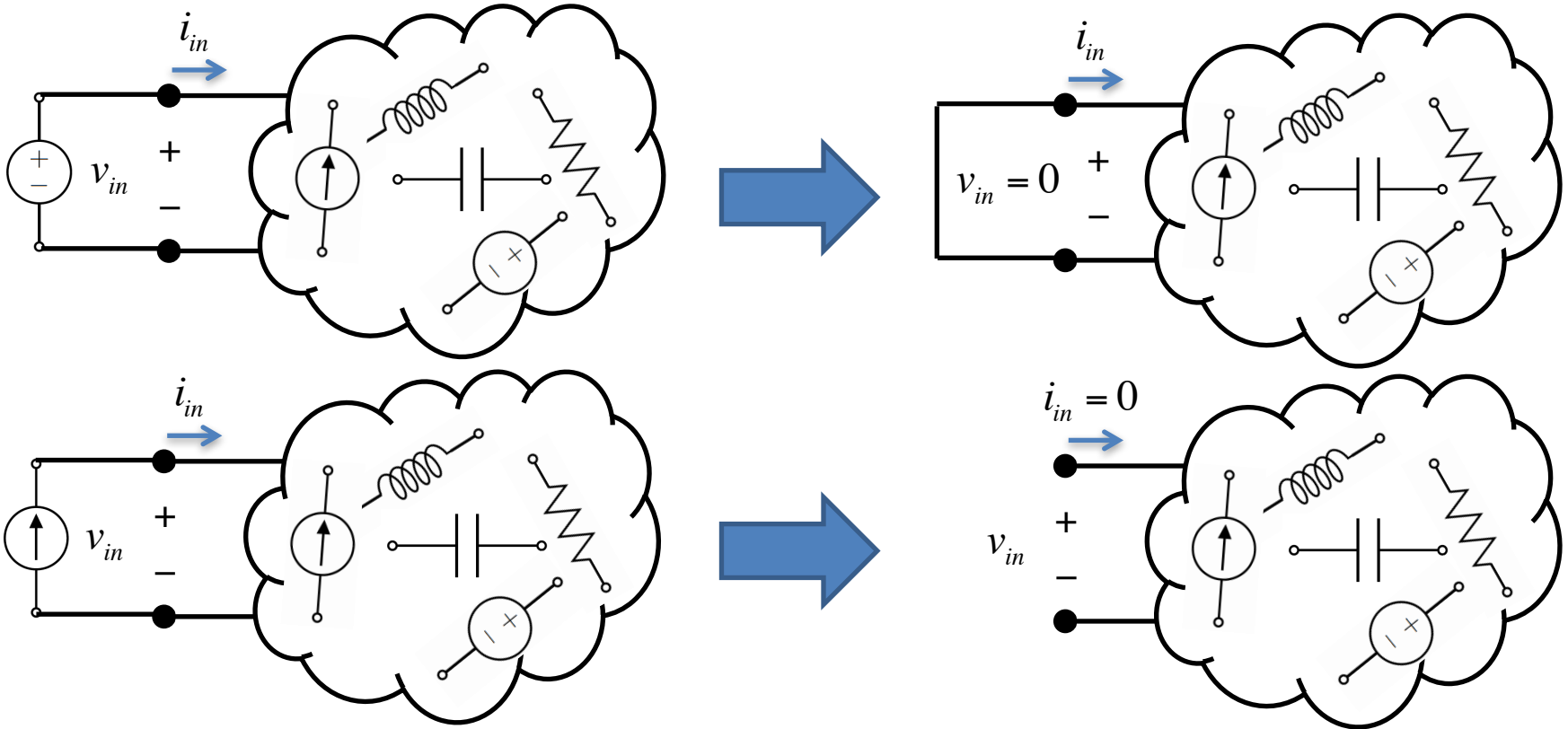- **Zero-Input** → No excitation at the input





Solving for the Hybrid- π Parameters (1)

- Circuit Transconductance

Solving for G_m :

$$G_m = \left. \frac{i_{out}}{v_{in}} \right|_{\text{no-load}}$$

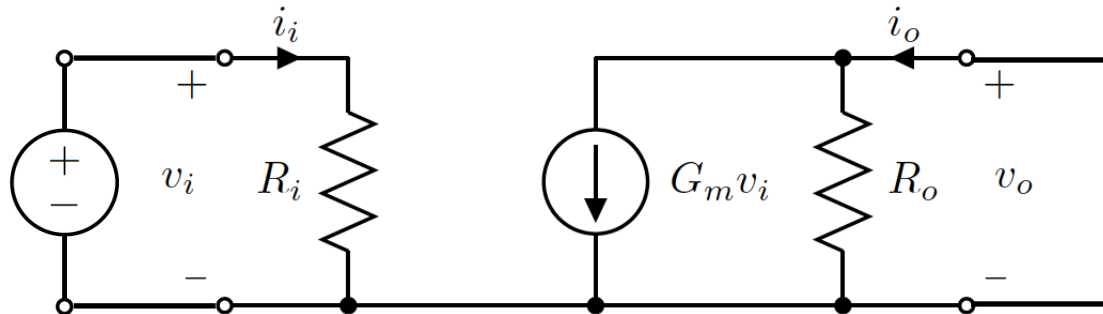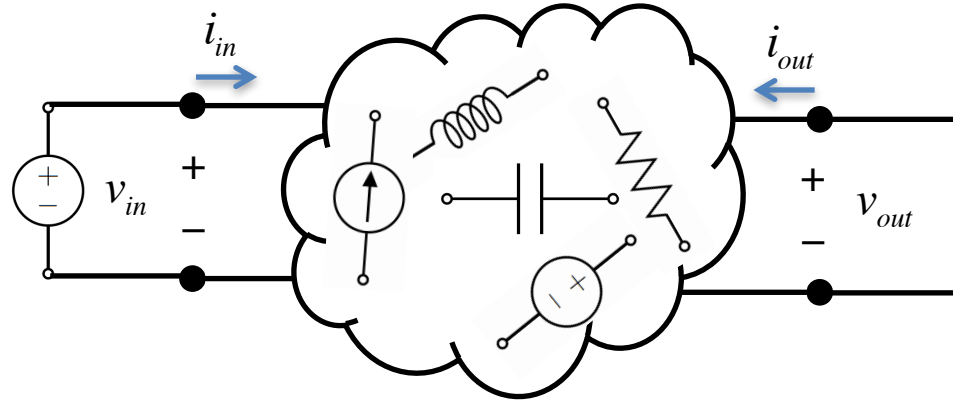


Solving for the Hybrid- π Parameters (2)

- Circuit Voltage Gain

Solving for A_v :

$$A_v = \left. \frac{v_{out}}{v_{in}} \right|_{\text{no-load}}$$

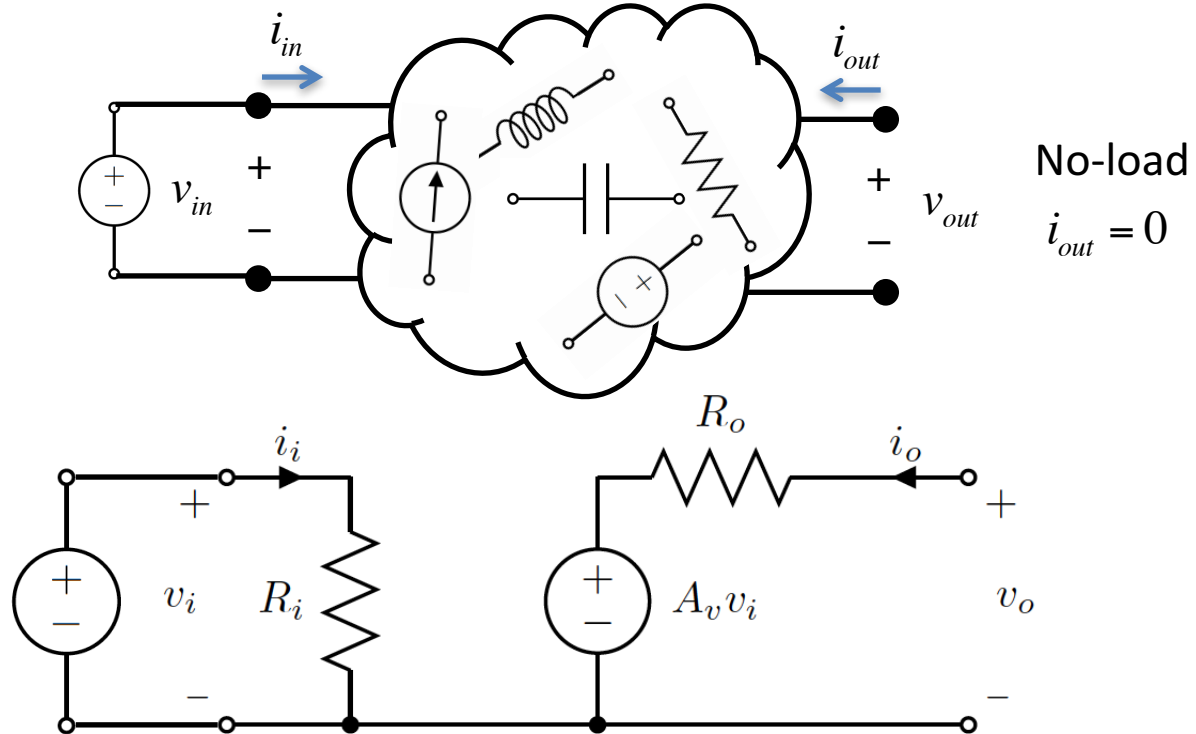

Solving for the Hybrid- π Parameters (3)


- Circuit Output Resistance

Solving for R_o :


Zero-input

$i_{in} = 0$ or

$v_{in} = 0$

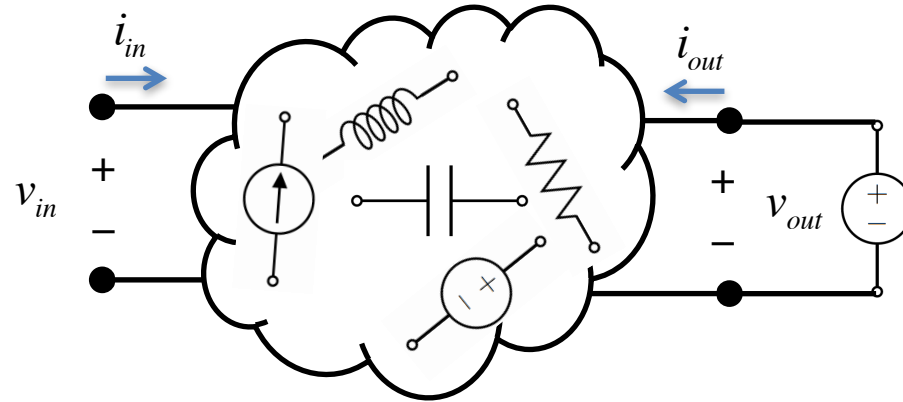

$$R_o = \left. \frac{v_{out}}{i_{out}} \right|_{\text{zero-input}}$$

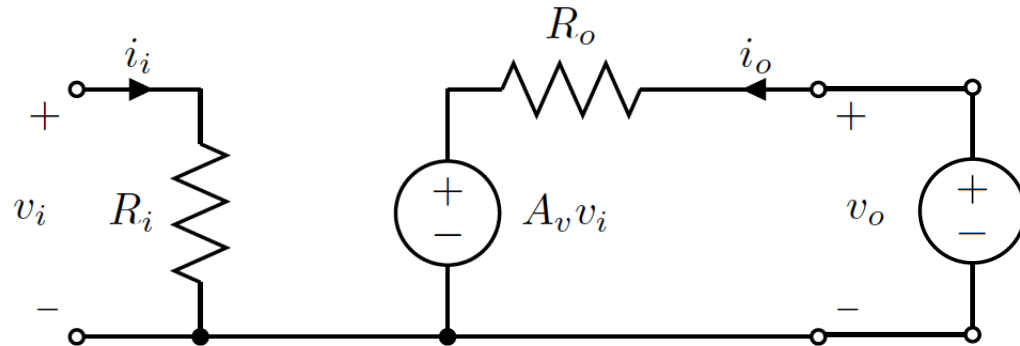


Solving for the Hybrid- π Parameters (4)



- Circuit Input Resistance

Solving for R_i :

$$R_i = \left. \frac{v_{in}}{i_{in}} \right|_{\text{no-load}}$$

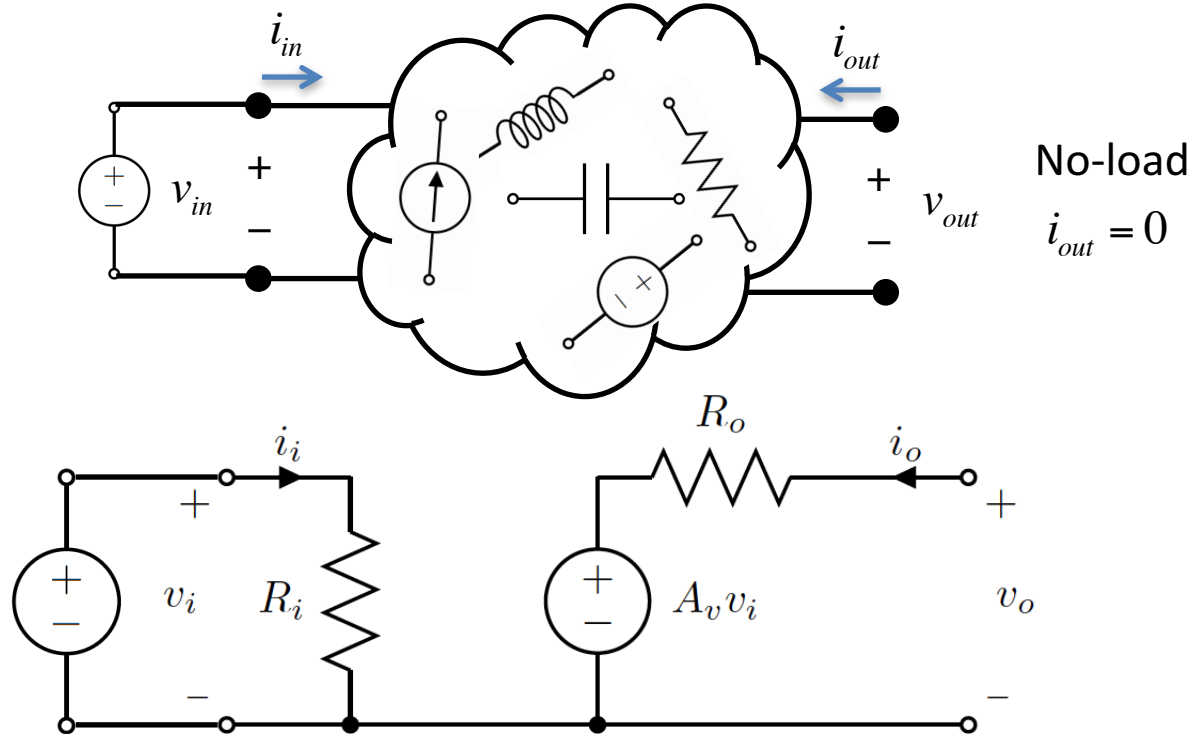

Cascading Two-Port Networks

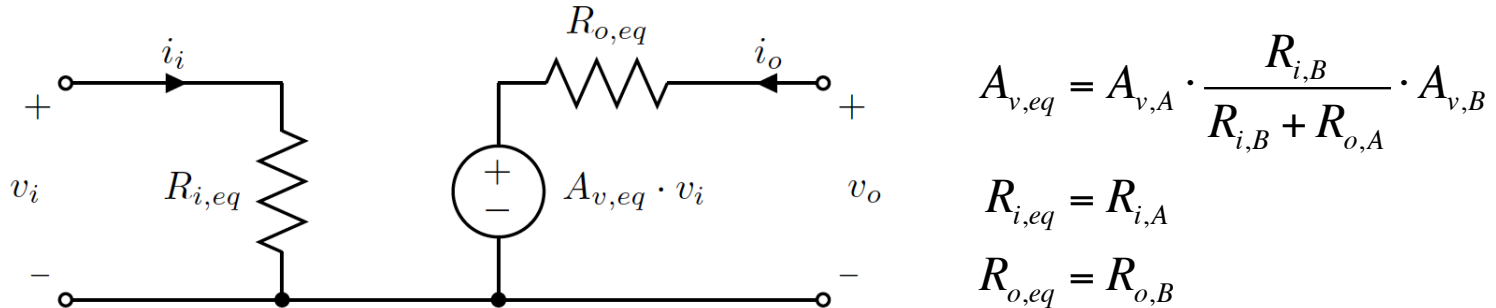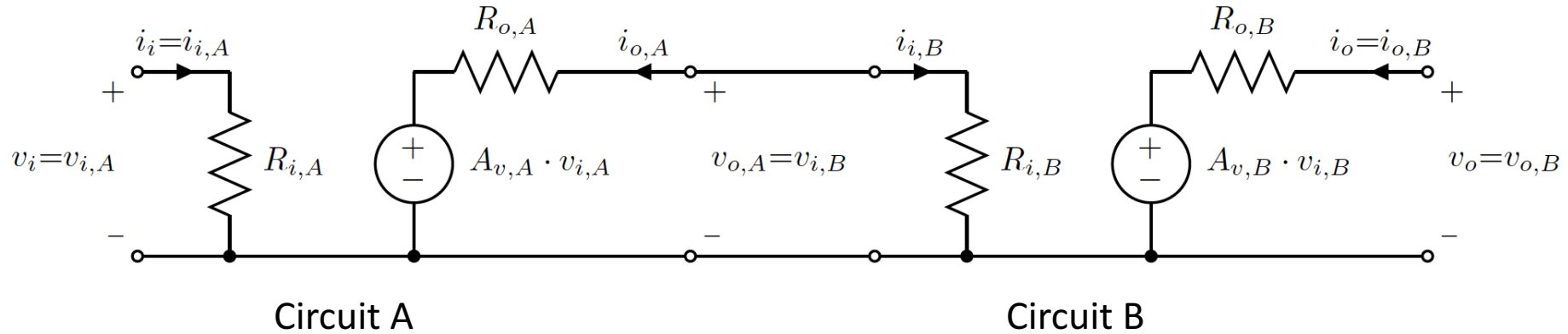


Equivalent 2-Port Circuit taking into account **loading effects**

So Far...

- We can analyze small signals separately from large signals
- We can use 2-port networks to reduce/combine small signal circuits
- Let's look at the small signal behavior of our basic electronic circuit building blocks:
 - Single-stage amplifiers

Choices:

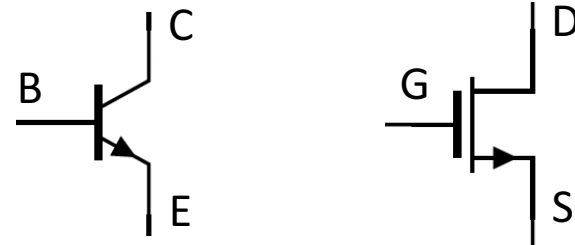


Where do we put in the input?

Where do we get the output?

Where do we start?




Transistor Amplifier Analysis

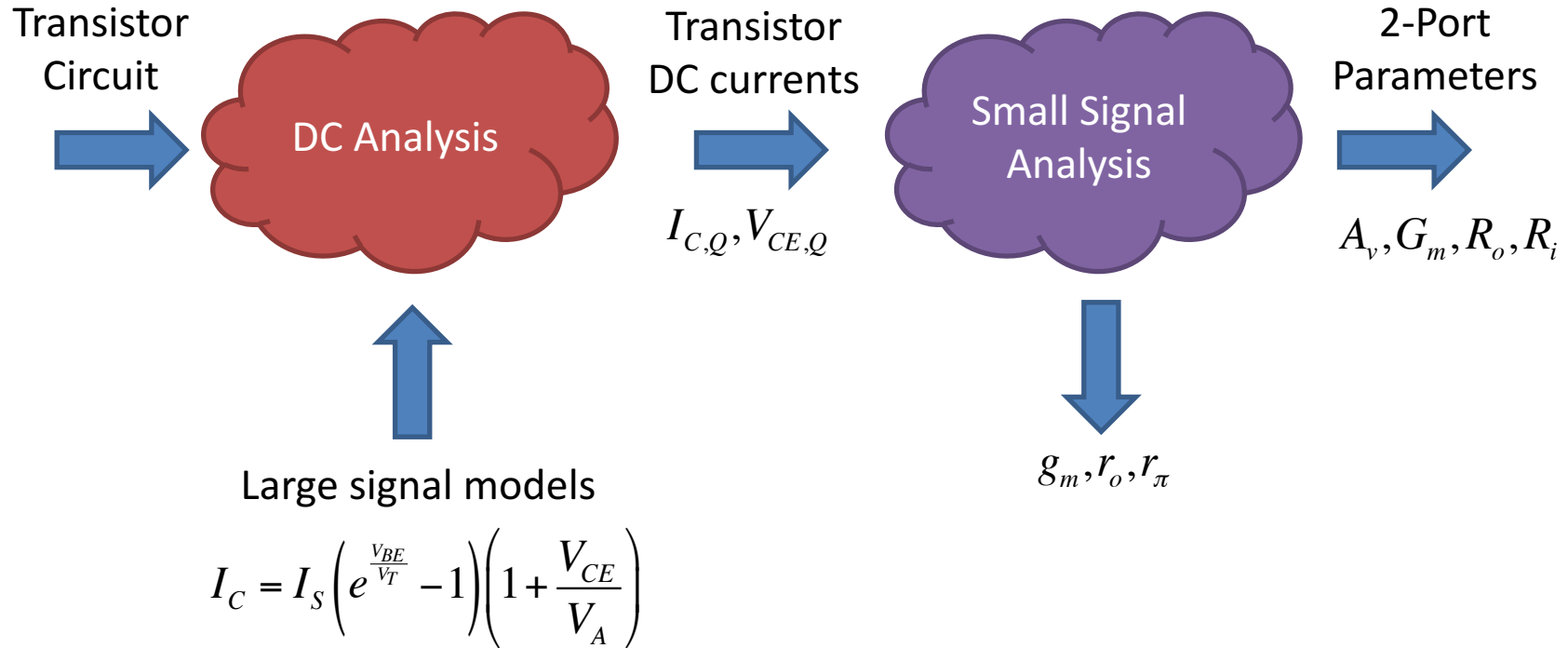


The Basic Common-Emitter (CE) Amplifier

- Full vs. simplified schematics

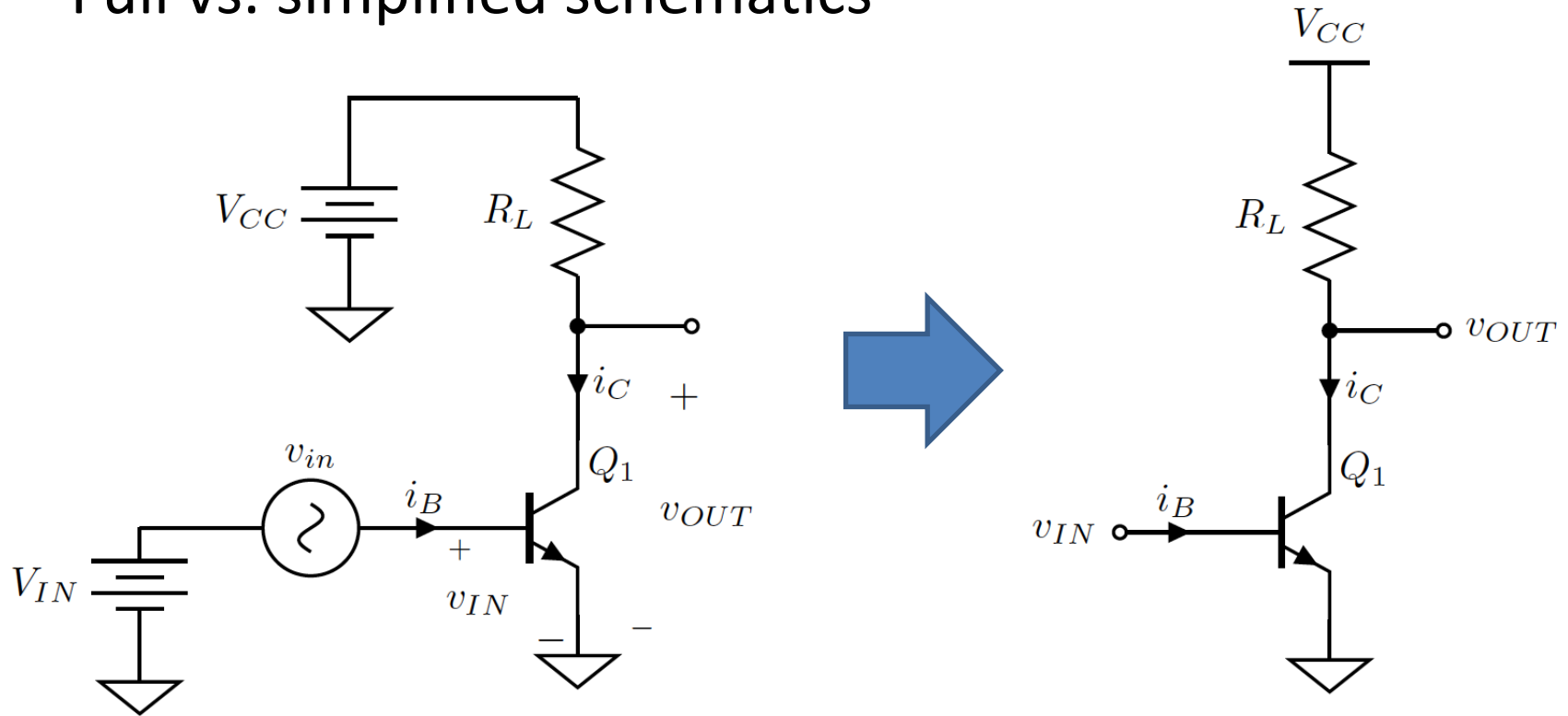

Common-Emitter DC Analysis

- Objective: Determine $I_{C,Q}$

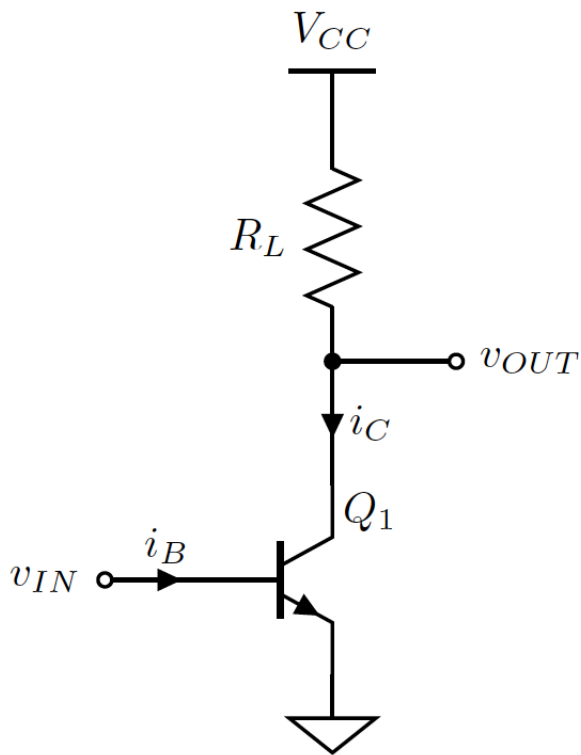

KVL equations \rightarrow 2 equations, 2 unknowns (assumptions?)

$$V_{CC} - I_{C,Q}R_L - V_{CE,Q} = 0$$

$$I_{C,Q} = I_s \left(e^{\frac{v_{IN}}{V_T}} - 1 \right) \left(1 + \frac{V_{CE,Q}}{V_A} \right)$$

In most cases, we will deal with: $V_{OUT} = V_{CE,Q} \ll V_A$


Thus,

$$I_{C,Q} = I_s \left(e^{\frac{v_{IN}}{V_T}} - 1 \right) \quad V_{OUT} = V_{CC} - I_{C,Q}R_L$$
$$= V_{CC} - R_L I_s \left(e^{\frac{v_{IN}}{V_T}} - 1 \right)$$



Common-Emitter Amplifier Small Signal Analysis

- Given $I_{C,Q}$:

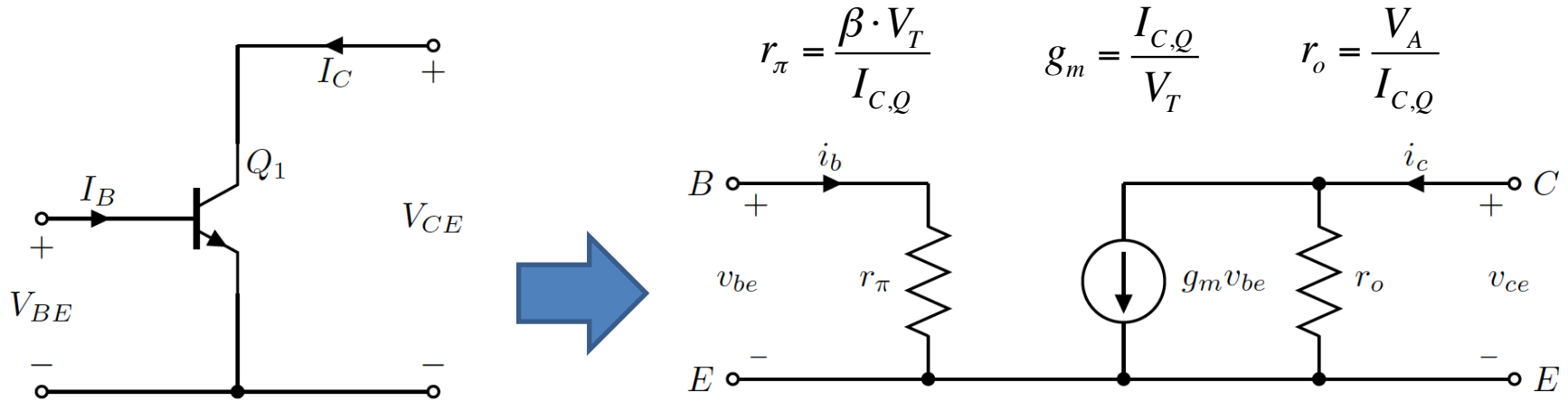


What about the other circuit elements?



- Resistors
- Independent voltage/current sources

Linear Two-Terminal Devices


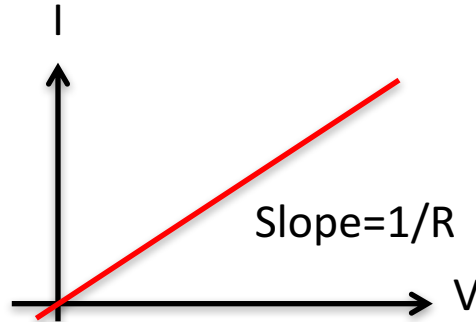
- Small signal conductance / resistance: $R_{\text{small signal}} = \frac{\partial V}{\partial I}$



$$R_{\text{small signal}} = R$$

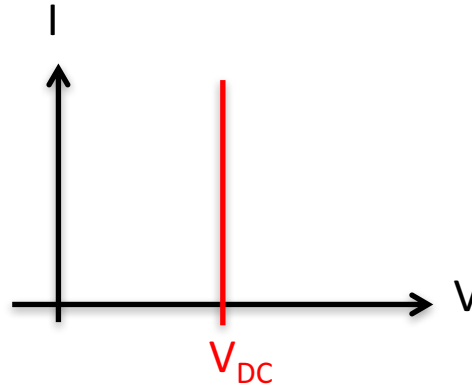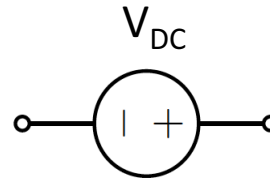


$$R_{\text{small signal}} = 0$$

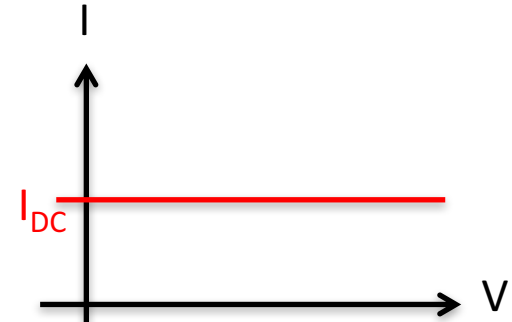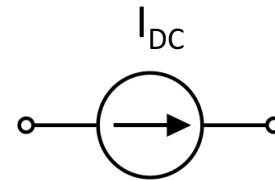




$$R_{\text{small signal}} \rightarrow \infty$$

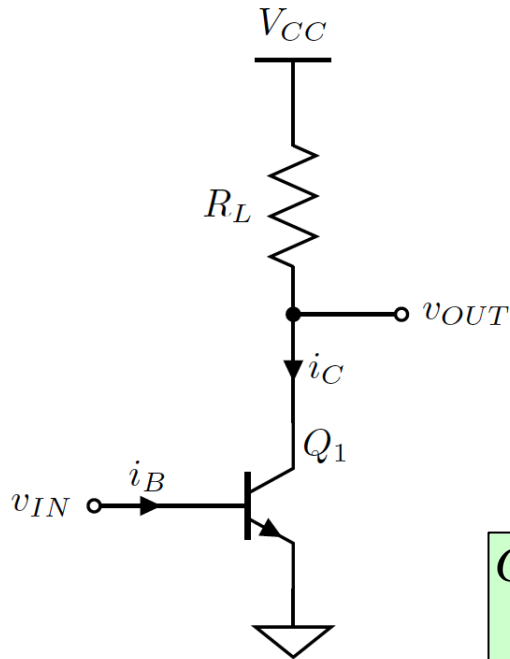CE Amplifier Small Signal Equivalent Circuit





“inverting amplifier”
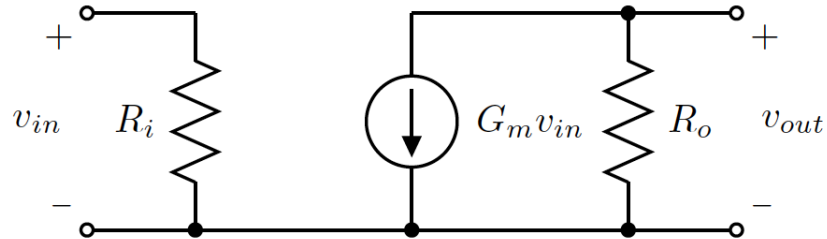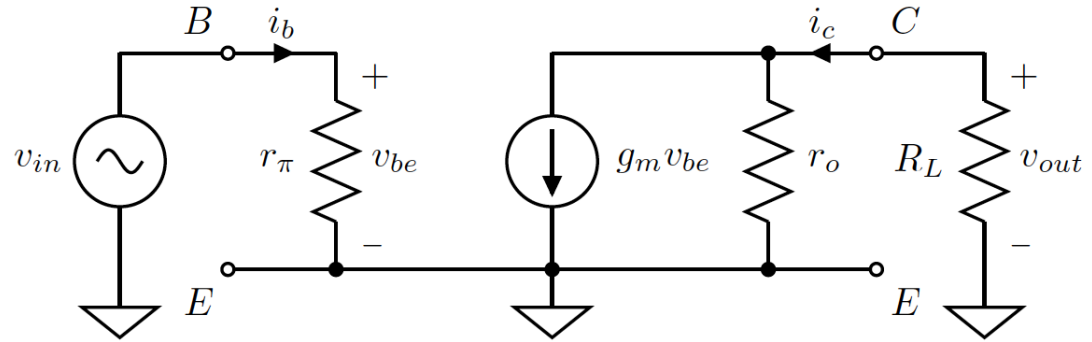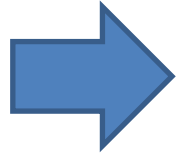
$$\begin{aligned} G_m &= g_m \\ R_i &= r_\pi \\ R_o &= r_o \parallel R_L \\ A_v &= -G_m R_o \\ &= -g_m (r_o \parallel R_L) \end{aligned}$$



Define: Intrinsic Transistor Gain (a_o)

- Ideal bias circuit:

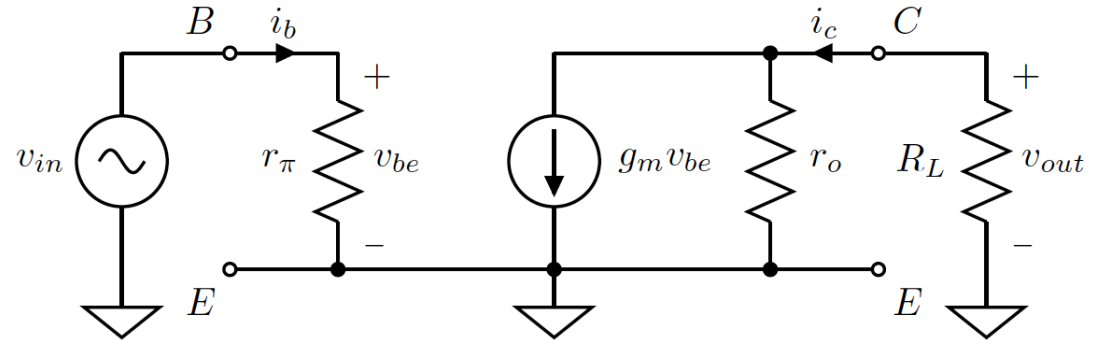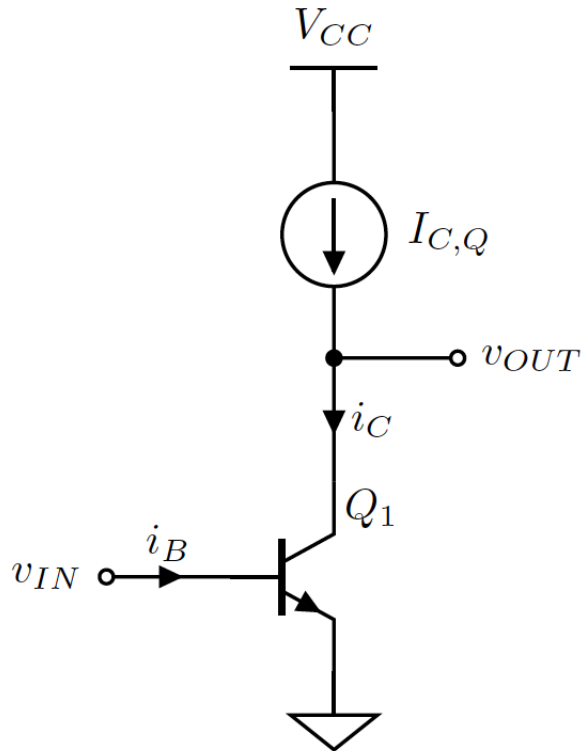

$$G_m = g_m$$

$$R_i = r_{\pi}$$

$$R_o = r_o$$

$$A_v = -G_m R_o = -g_m r_o = a_o$$

$R_L \rightarrow \infty$
Why?


$a_o \rightarrow$ largest voltage gain out of a single transistor

$$a_o = -g_m r_o = -\frac{I_{C,Q}}{V_T} \cdot \frac{V_A}{I_{C,Q}} = -\frac{V_A}{V_T} = -\frac{q \cdot V_A}{kT}$$




How do we interpret voltage gain?

- Large signal transfer characteristic:


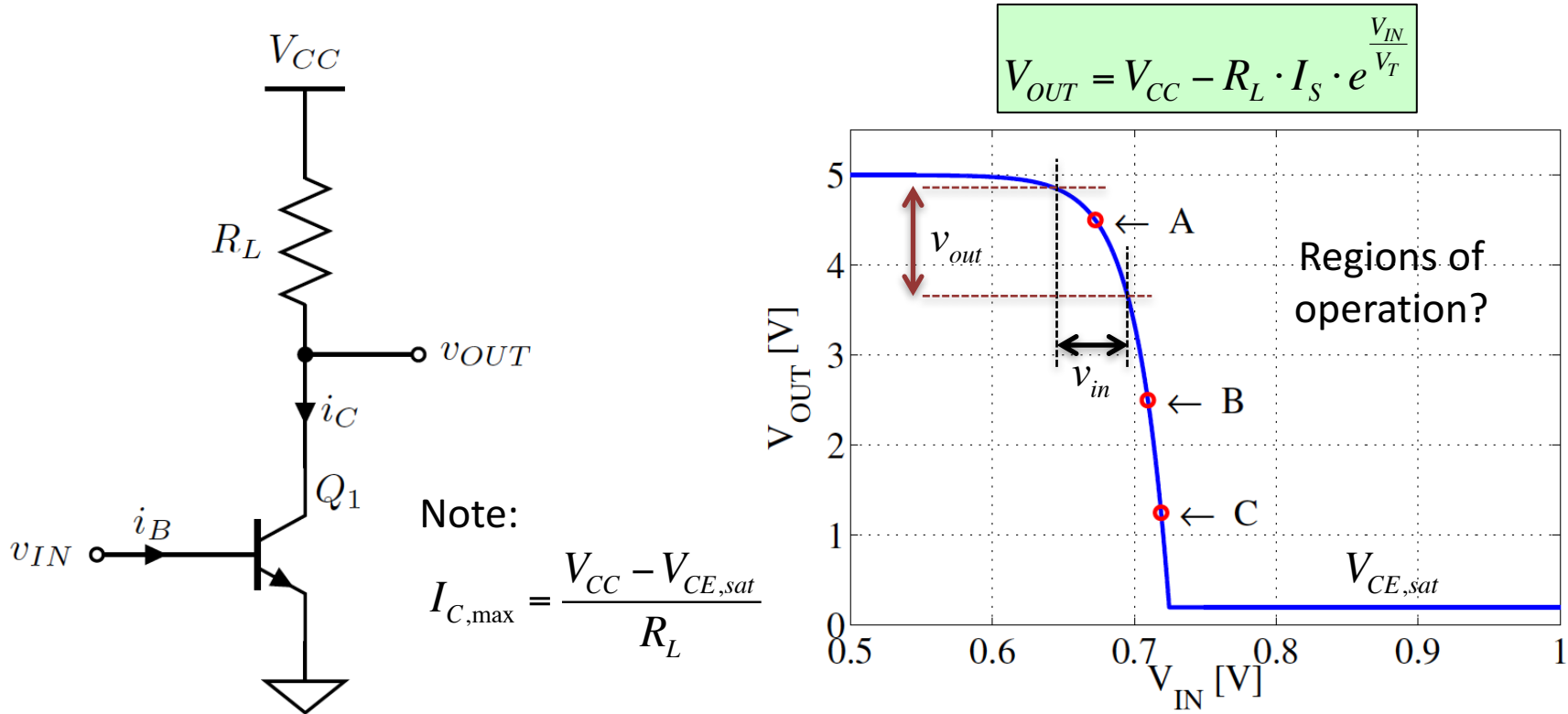


Small Signal Voltage Gain
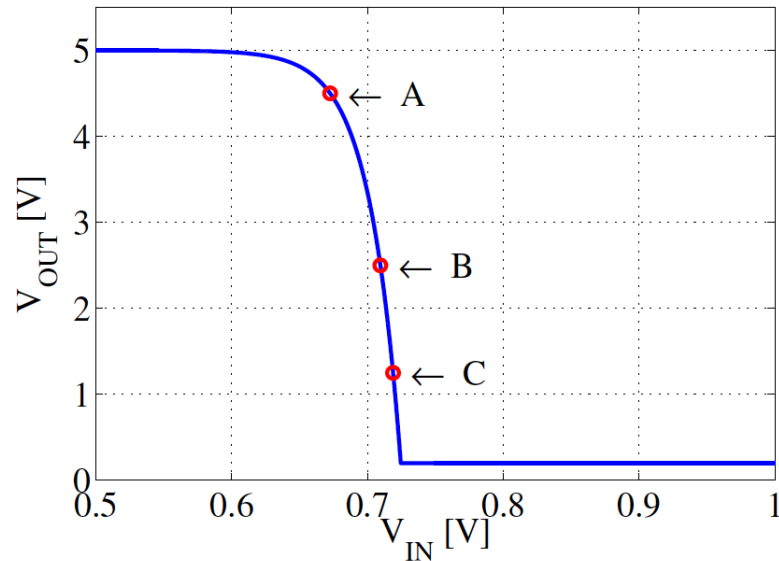
$$V_{OUT} = V_{CC} - R_L \cdot I_S \cdot e^{\frac{V_{IN}}{V_T}}$$


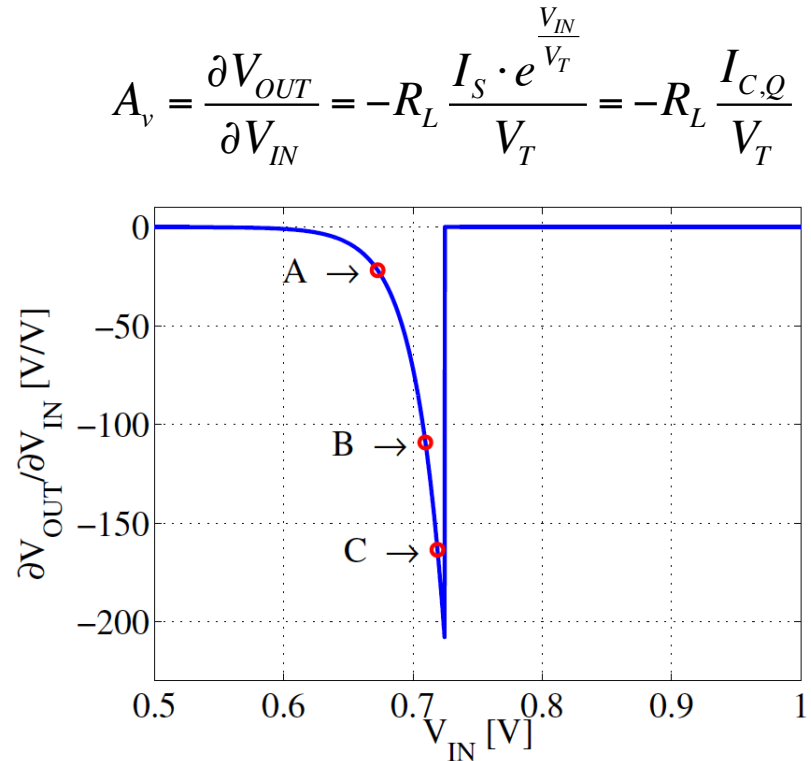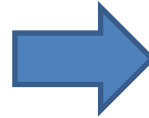
$$A_v = \frac{\partial V_{OUT}}{\partial V_{IN}}$$



Assumptions?



- $V_A \rightarrow \infty$

Compare to $A_v = -g_m (r_o \parallel R_L)$





Choosing the Bias Point?

- Largest gain? → Point C

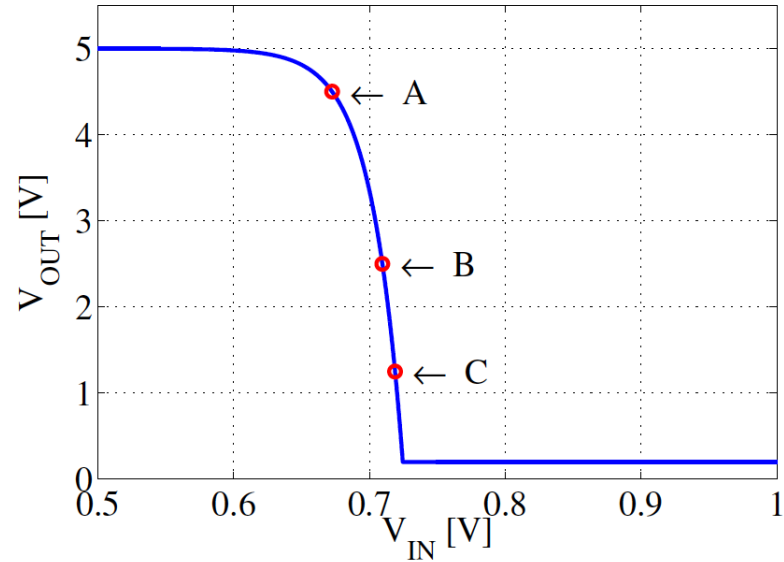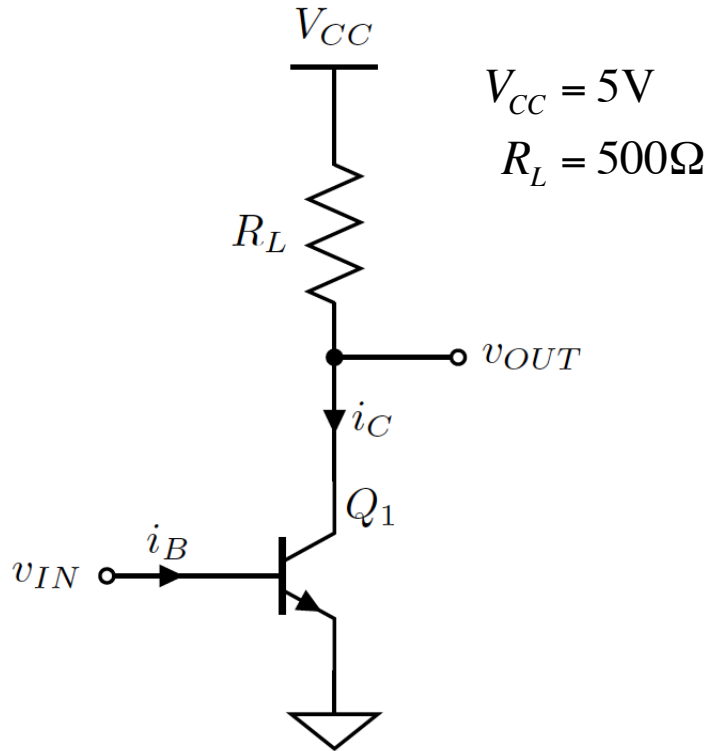

	V_{IN} [mAV]	$I_{C,Q}$ [mA]	V_{OUT} [V]	A_v [$\frac{V}{V}$]
Point A	672.5	1	4.5	-21.7
Point B	709.5	5	2.5	-108.7
Point C	718.9	7.5	1.25	-163.0

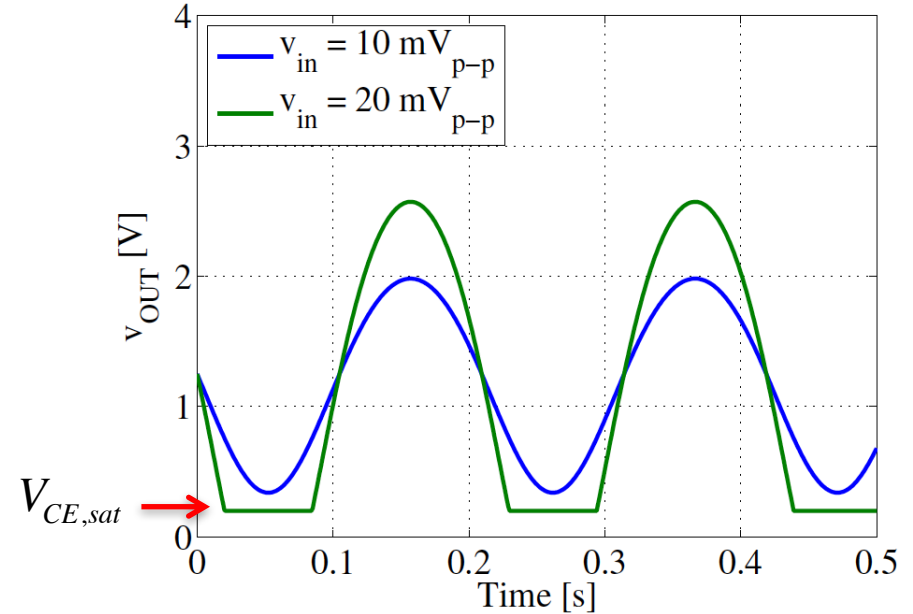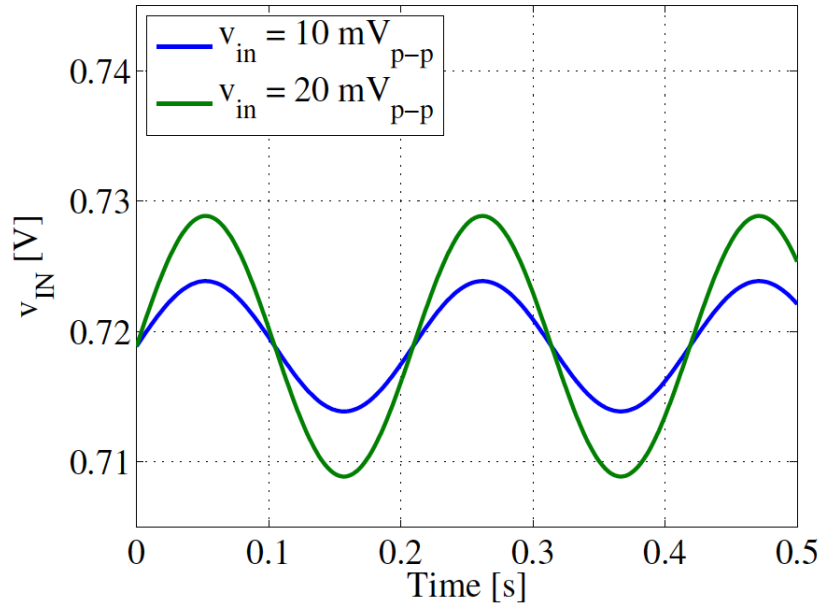Transient Response at Point C: Output Swing





$$V_{CC} = 5V$$

$$R_L = 500\Omega$$

	V_{IN} [mAV]	$I_{C,Q}$ [mA]	V_{OUT} [V]	A_v [$\frac{V}{V}$]
Point A	672.5	1	4.5	-21.7
Point B	709.5	5	2.5	-108.7
Point C	718.9	7.5	1.25	-163.0



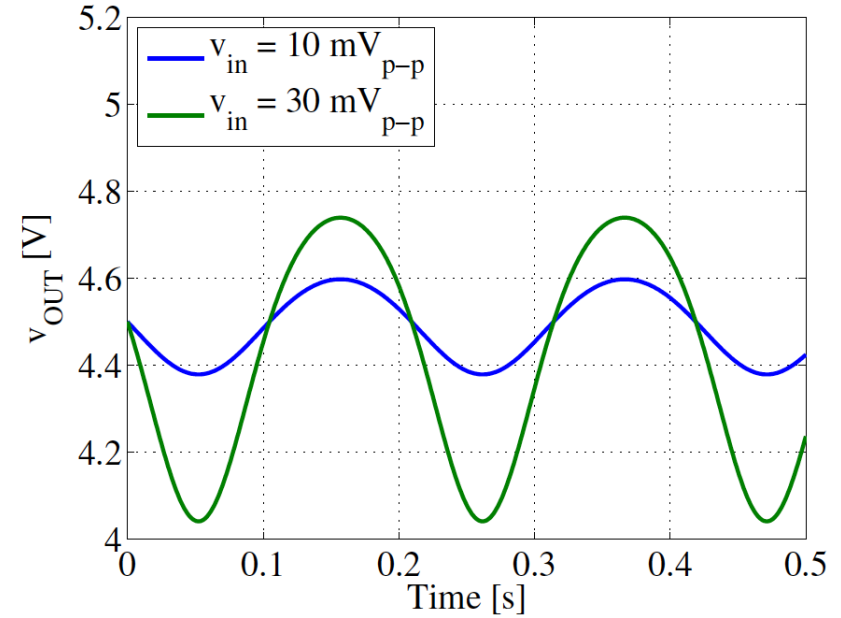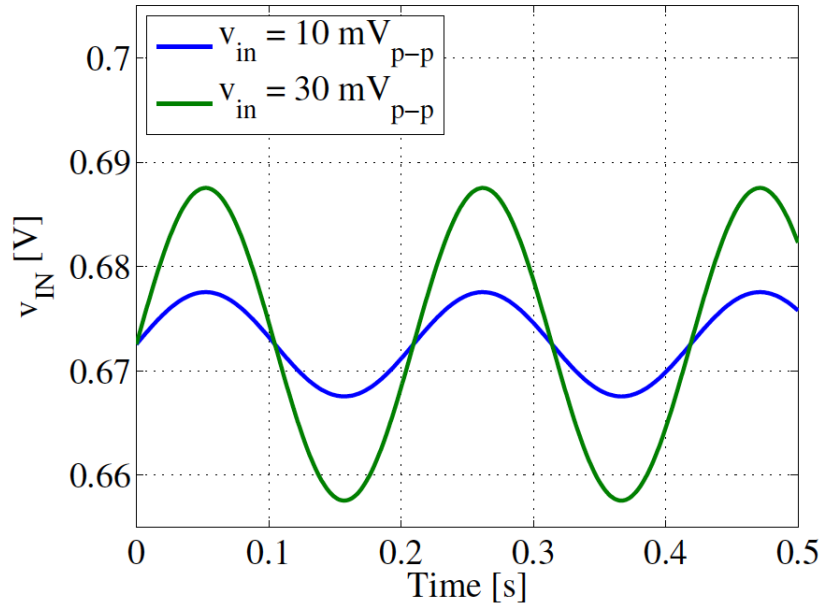Transient Response at Point A: Output Swing





$$V_{CC} = 5V$$

$$R_L = 500\Omega$$

	V_{IN} [mAV]	$I_{C,Q}$ [mA]	V_{OUT} [V]	A_v [$\frac{V}{V}$]
Point A	672.5	1	4.5	-21.7
Point B	709.5	5	2.5	-108.7
Point C	718.9	7.5	1.25	-163.0



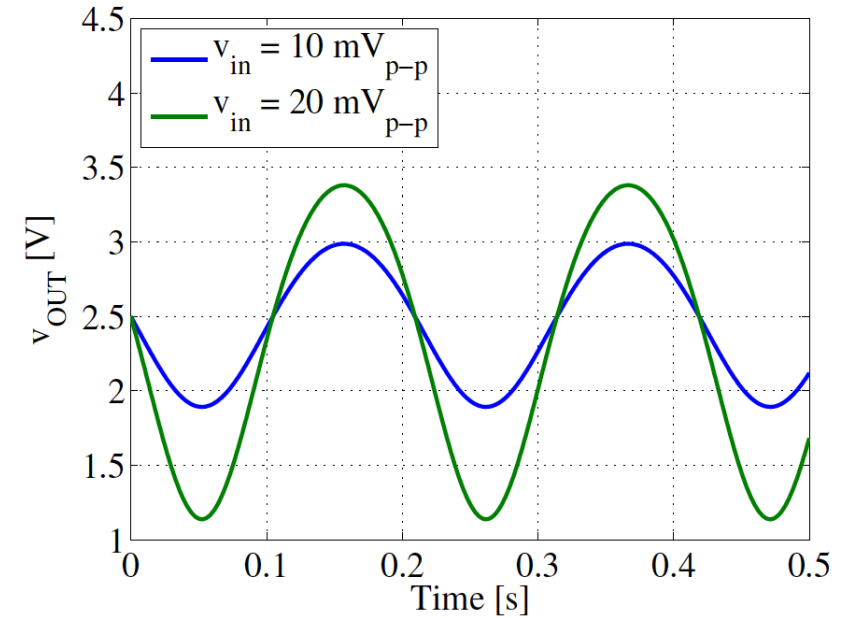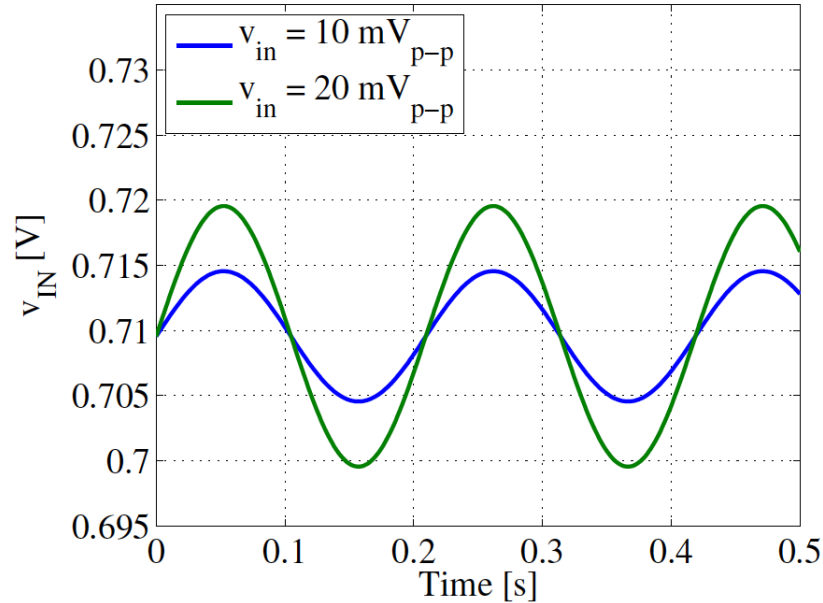Transient Response at Point B: Output Swing



$$V_{CC} = 5V$$



$$R_L = 500\Omega$$

	V_{IN} [mAV]	$I_{C,Q}$ [mA]	V_{OUT} [V]	A_v [$\frac{V}{V}$]
Point A	672.5	1	4.5	-21.7
Point B	709.5	5	2.5	-108.7
Point C	718.9	7.5	1.25	-163.0



Choosing the Bias Point → Swing vs. Distortion


- Depends on what you need

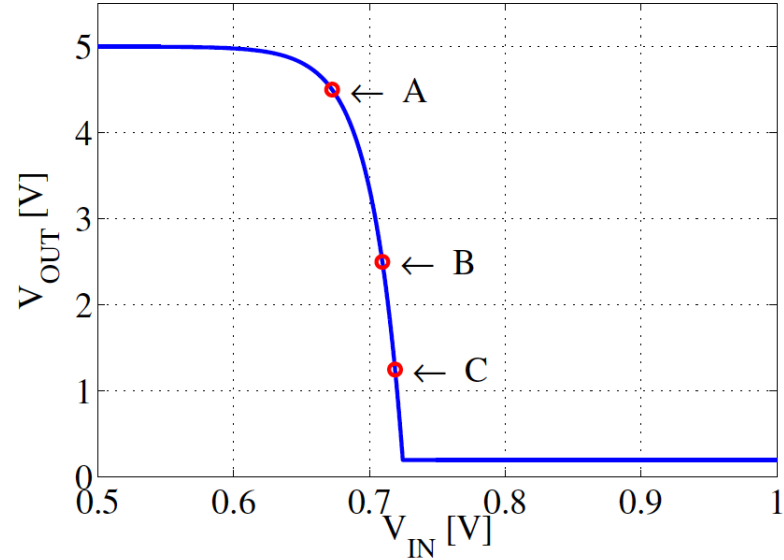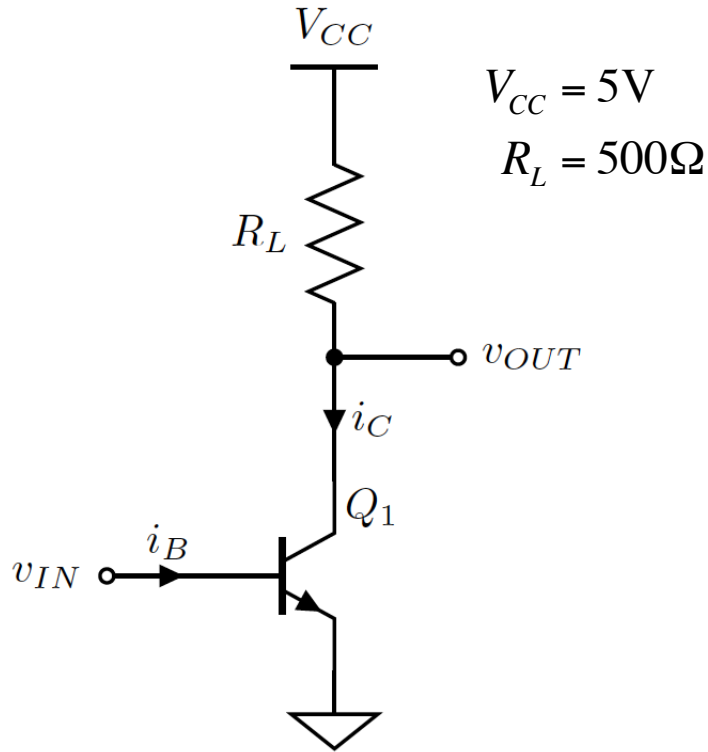

	V_{IN} [mAV]	$I_{C,Q}$ [mA]	V_{OUT} [V]	A_v [$\frac{V}{V}$]
Point A	672.5	1	4.5	-21.7
Point B	709.5	5	2.5	-108.7
Point C	718.9	7.5	1.25	-163.0

Quiescent DC Power

- Amplification requires power input

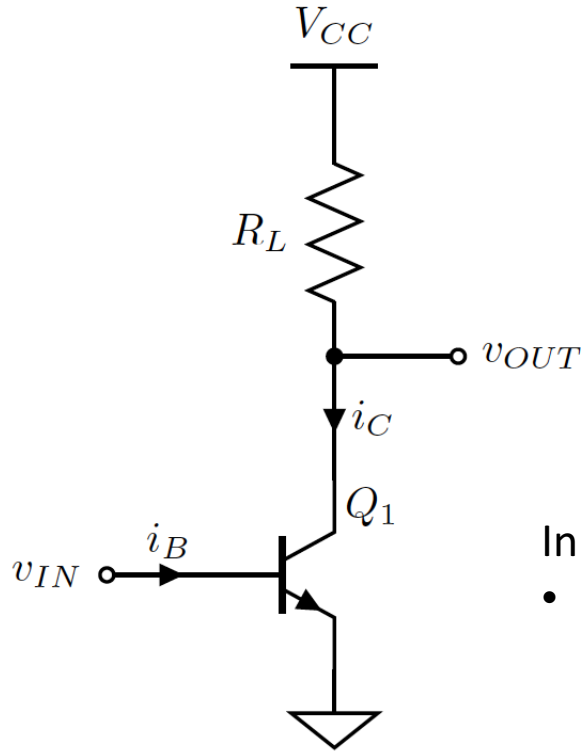

$$\begin{aligned} P_{DC} &= V_{CC}I_{C,Q} + V_{IN}I_{B,Q} \\ &= V_{CC}I_{C,Q} + V_{IN}\frac{I_{C,Q}}{\beta} \\ &= I_{C,Q}\left(V_{CC} + \frac{V_{IN}}{\beta}\right) \end{aligned}$$

In general:

- Higher gain \rightarrow larger $I_{C,Q} \rightarrow$ higher DC power consumption



Next Meeting

- Single-Stage Amplifiers
 - Common-Emitter Biasing
 - Common-Source Amplifier
 - Common-Base / Common-Gate Amplifier
 - Common-Collector / Common-Drain Amplifier

