

# EEE 51 Assignment 10

2nd Semester SY 2018-2019

Due: 5pm Tuesday, May 14, 2019 (Rm. 220)

*Instructions:* Write legibly. Show all solutions and state all assumptions. Write your full name, student number, and section at the upper-right corner of each page. Start each problem on a new sheet of paper. Box or encircle your final answer.

Answer sheets should be color coded according to your lecture section. The color scheme is as follows:

**THQ** – yellow  
**THU** – white  
**WFX** – pink

## 1. Last Push

Figure 1 shows an equivalent circuit of some amplifier with compensation capacitor  $C_x$ . Its loop gain,  $T_o$  is  $2 \times 10^5$ . The components have values  $C_i = 50$  pF,  $R_i = 31.83$  k $\Omega$ ,  $g_m = 100$  mA/V,  $R_o = 15.92$  k $\Omega$ , and  $C_o = 10$  pF. The amplifier also has unknown break frequencies,  $f_i$  and  $f_o$ , and a known break frequency  $f_a = 10$  MHz.

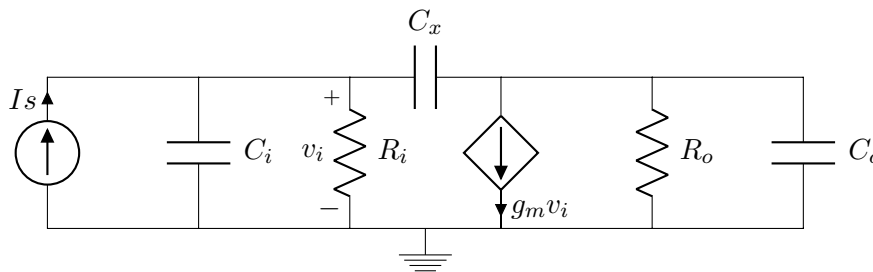


Figure 1: Oscillator

- Solve for break frequencies  $f_i$  (input side) and  $f_o$  (output side) without the compensating capacitance. (2 pts)
- Upon inserting the compensating capacitance  $C_x$ , compute the new break frequency  $f'_o$  (output side). (Assume that  $C_x \gg C_o$ ). (3 pts)
- Solve for the new break frequency  $f'_i$  for a PM of  $45^\circ$  and unity feedback factor ( $f=1$ ) at  $f_a$ . (2 pts)
- Solve for the value of the compensating capacitance  $C_x$ . (Assume that  $C_x \gg C_i$ ). (3 pts)

## 2. Last 51HW problem for real.

Consider the circuit shown in Fig. 2 below. Assume that  $M1$  and  $M2$  are identical with  $\lambda = 0$ . Also, assume that  $R_1 > R_2$  and that all intrinsic capacitances can be ignored and consider only the capacitors that are shown in the figure.

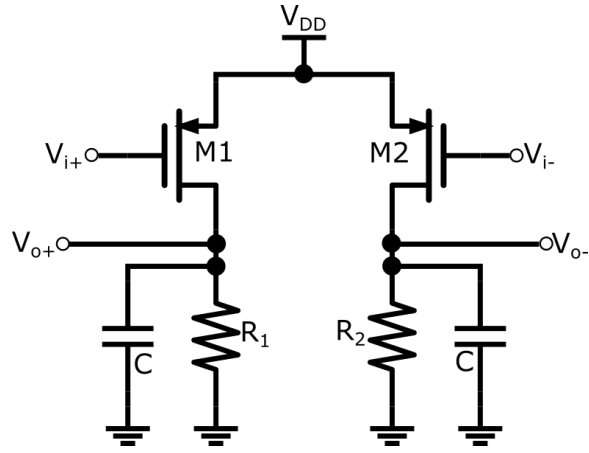


Figure 2: Simple pseudo-differential amplifier circuit

- Find the expression for the transfer functions  $H_1(s) = \frac{v_{o+}}{v_{i+}}$  (1 pt) and  $H_2(s) = \frac{v_{o-}}{v_{i-}}$  (1 pt) in terms of  $R_1$ ,  $R_2$ ,  $C$  and  $g_m$ .
- Roughly sketch the magnitudes of  $H_1$  and  $H_2$  against frequency in the same plot. Label important/relevant plot points. (1 pt)
- Determine the time-domain response of  $V_{o+}$  and  $V_{o-}$  to a voltage step in  $V_{i+}$  and  $V_{i-}$  respectively (1 pt) and sketch both responses on the same plot (1 pt). Label important/relevant plot points.
- Find the transfer function for the differential gain and express it in the form  $H(s) = A \frac{\left(1 + \frac{s}{w_z}\right)}{\left(1 + \frac{s}{w_{p1}}\right)\left(1 + \frac{s}{w_{p2}}\right)}$  (1 pt) and sketch the magnitude of the transfer function vs frequency (2 pts). Label completely.

From your plot in (d), you might have noticed the appearance of a zero. This is due to the mismatch between the left and right side of the circuit ( $R_1 \neq R_2$ ). This phenomenon is what is usually called a "pole-zero doublet". This issue also arises when cancelling a pole by introducing a zero in a two-stage amplifier for example wherein the pole and the zero do not coincide. Suppose the open-loop TF of an 2-stage amplifier is expressed as:

$$H_{open}(s) = \frac{A_0 \left(1 + \frac{s}{w_z}\right)}{\left(1 + \frac{s}{w_{p1}}\right) \left(1 + \frac{s}{w_{p2}}\right)}$$

Ideally if  $w_z = w_{p2}$ , the system seems like a "first-order" system. For this system,

- Determine the transfer function of the amplifier in a unity-gain feedback loop. (1 pt)
- Determine the two poles of the closed transfer function assuming they are widely spaced in terms of  $w_{p1}$ ,  $w_{p2}$ ,  $w_z$  and  $A_0$ . (1 pt)
- BONUS** Assuming  $w_z \approx w_{p2}$  and  $w_{p2} \ll (1 + A_0)w_{p1}$ , determine the time-domain step-response of the closed-loop amplifier. What can we infer from this result? (5 pts)

TOTAL: 25/20 points.