




# **EEE 51: Second Semester 2017 - 2018**



## **Lecture 16**

# Frequency Response

# Magnitude and Phase

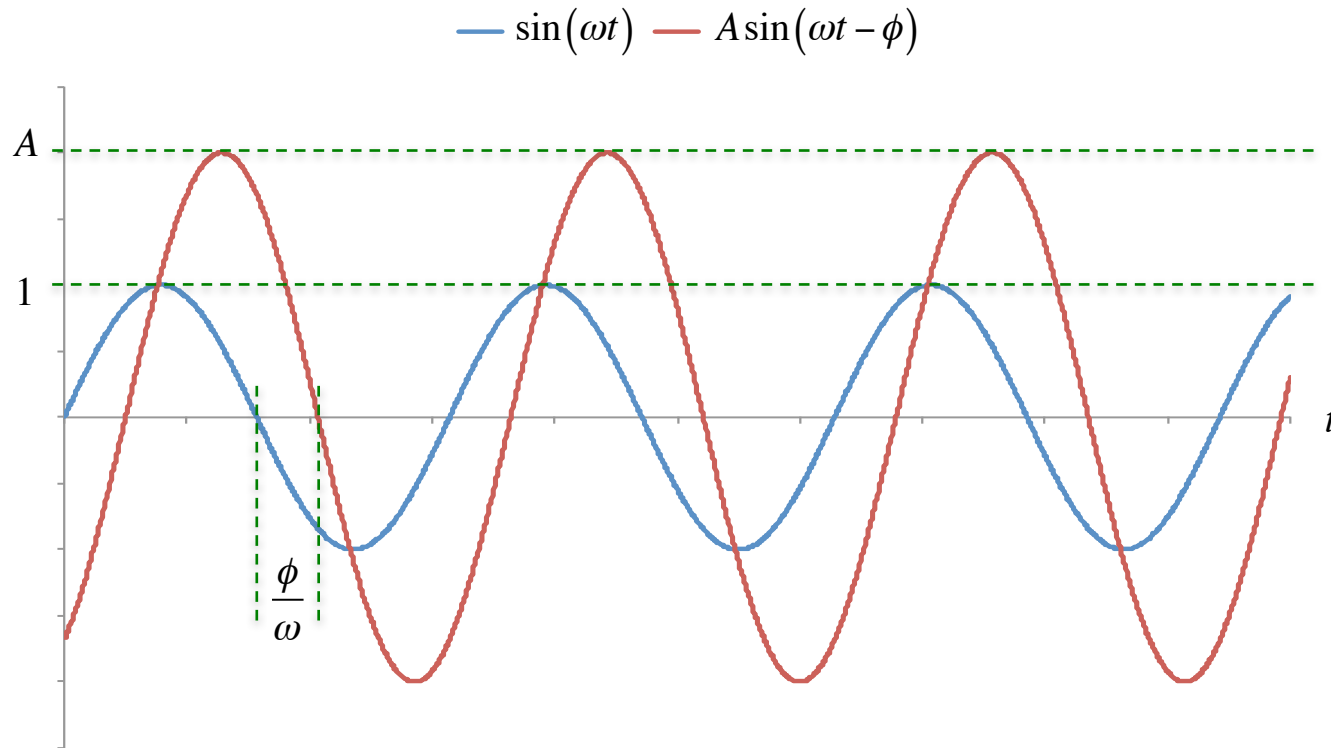
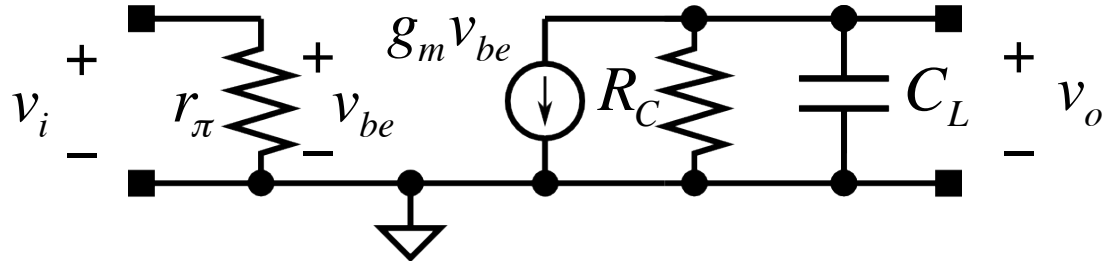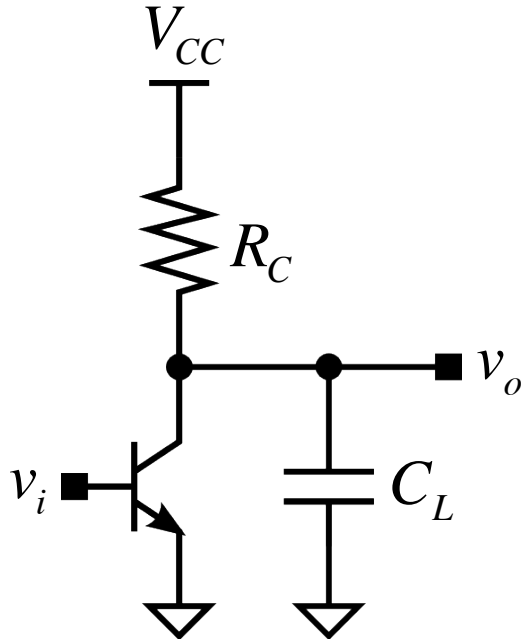
# The Single-Pole Common Emitter Amplifier




$$A_v = \frac{v_o}{v_i} = -g_m \frac{R_C}{1 + sR_C C_L}$$

# Magnitude and Phase Response


$$|A_v| = g_m R_C \frac{1}{\sqrt{1 + \omega^2 (R_C C_L)^2}} = \frac{A_0}{\sqrt{1 + \frac{\omega^2}{\omega_0^2}}}$$

$$A_0 = g_m R_C \quad \omega_0 = \frac{1}{R_C C_L}$$

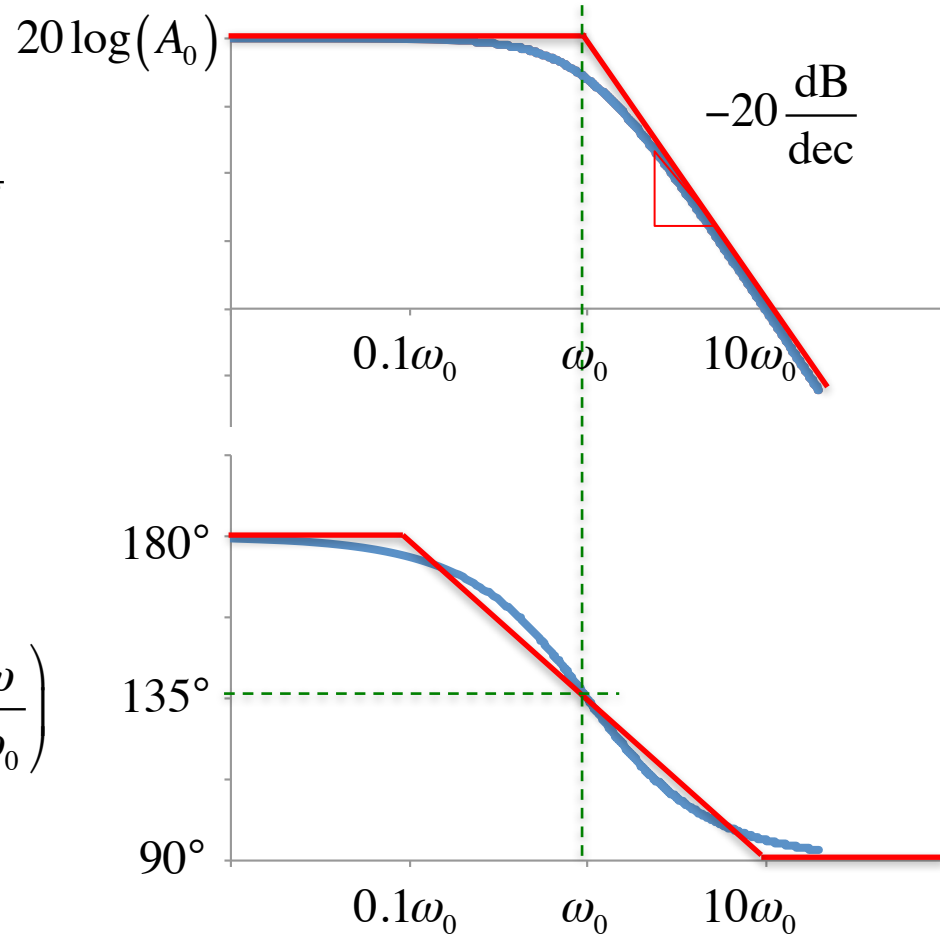
$$\angle A_v = \pi - \tan^{-1}(\omega R_C C_L) = \pi - \tan^{-1}\left(\frac{\omega}{\omega_0}\right)$$




# CE Output Impedance

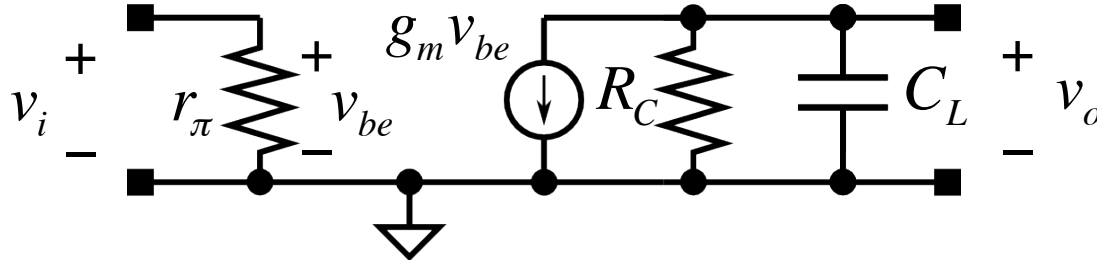

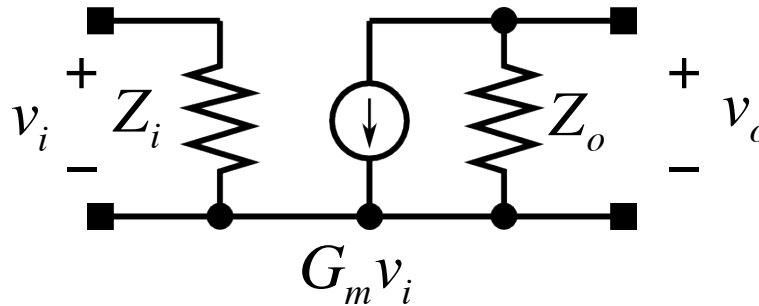
$$Z_o = R_C \parallel \frac{1}{sC_L} = \frac{R_C}{1 + sR_C C_L} \quad G_m = g_m$$



# Pole-Zero Plot: 1-Pole System

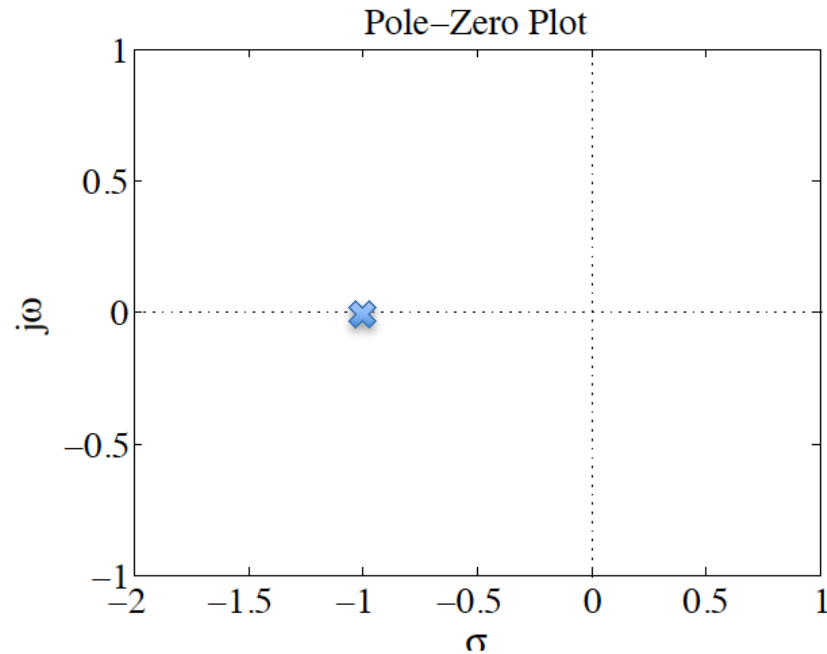


$$H(s) = \frac{1}{1+s}$$

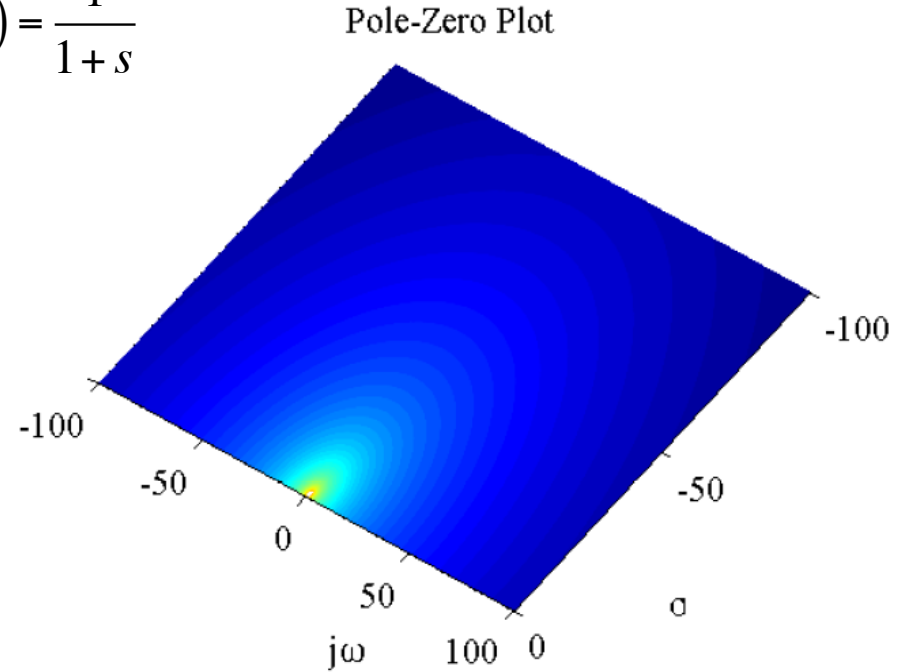


# Pole-Zero Plot: 1-Pole System

$$H(s) = \frac{1}{1+s}$$

Pole-Zero Plot

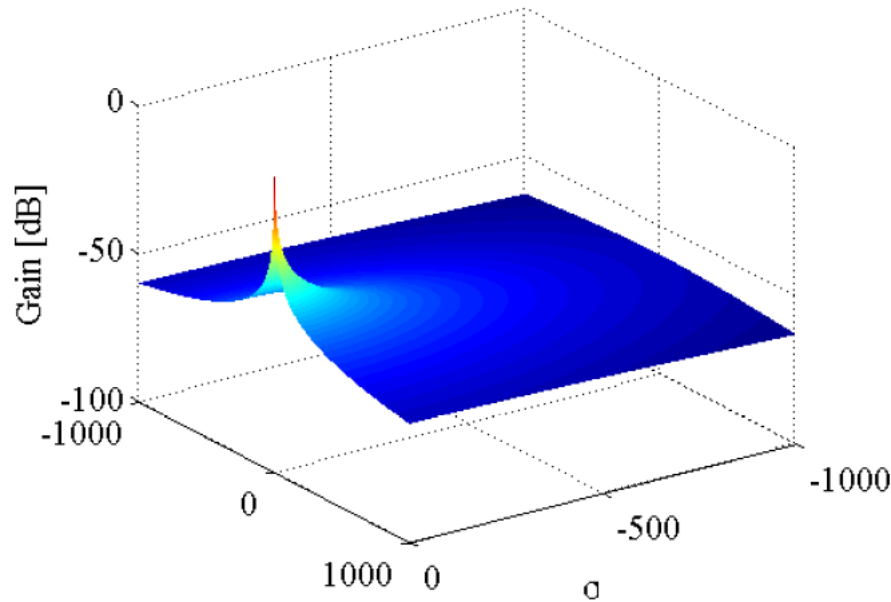


Pole-Zero Plot

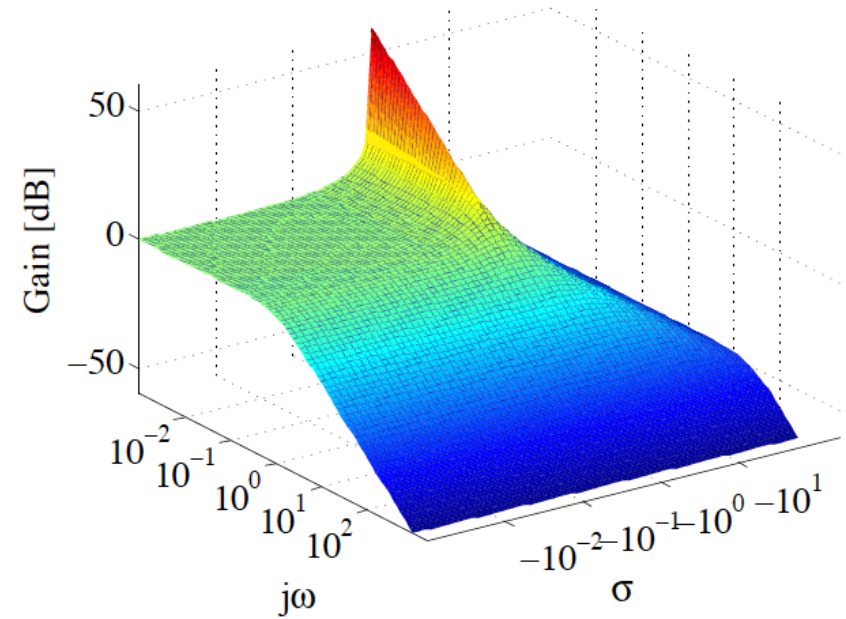


# A Pole and a Zero

$$H(s) = \frac{s}{1+s}$$

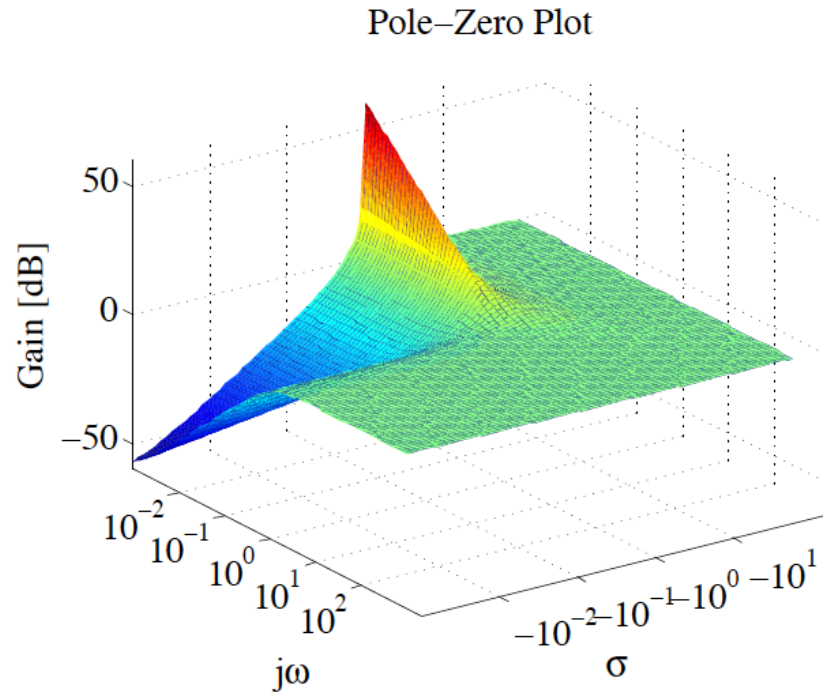




# The CE Amplifier with an Input Pole

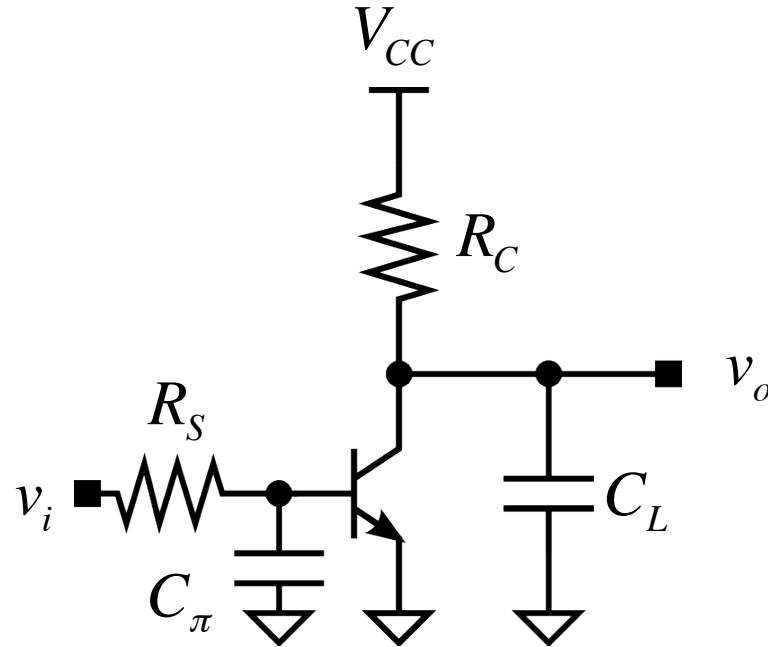

# The CE Amplifier with an Input Pole

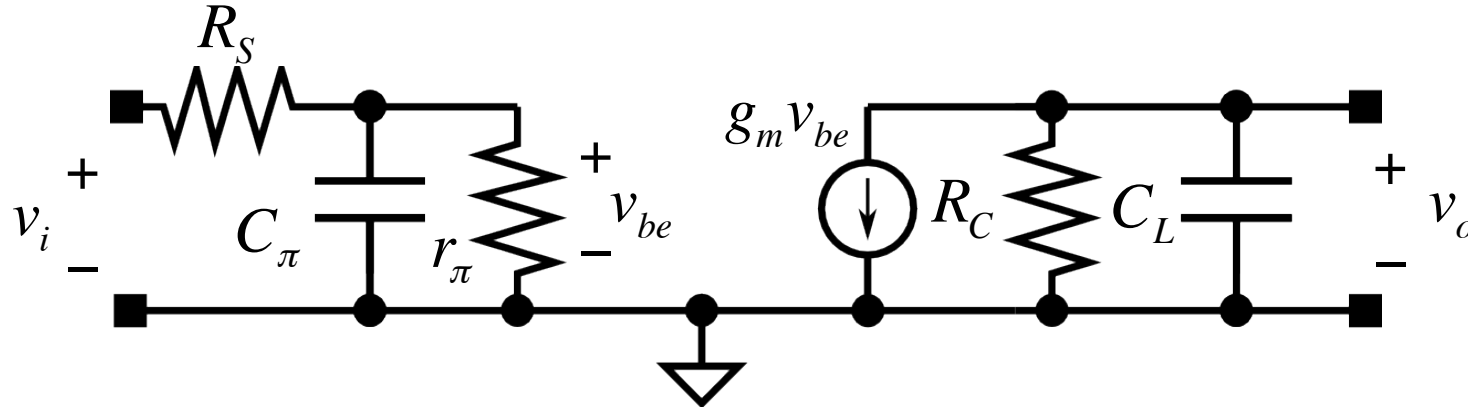

$$\frac{v_{be}}{v_i} = \frac{Z_\pi}{Z_\pi + R_S} = \frac{r_\pi \parallel \frac{1}{sC_\pi}}{r_\pi \parallel \frac{1}{sC_\pi} + R_S} = \frac{\frac{r_\pi}{1 + sr_\pi C_\pi}}{\frac{r_\pi}{1 + sr_\pi C_\pi} + R_S} = \frac{r_\pi}{r_\pi + R_S + sr_\pi R_S C_\pi}$$


$$= \frac{r_\pi}{r_\pi + R_S} \left( \frac{1}{1 + sC_\pi \frac{r_\pi R_S}{r_\pi + R_S}} \right) = A_1 \frac{1}{1 + j \frac{\omega}{\omega_{p1}}}$$

$$A_1 = \frac{r_\pi}{r_\pi + R_S}$$

$$\omega_{p1} = \frac{1}{C_\pi (r_\pi \parallel R_S)}$$



# The CE Amplifier with an Input Pole

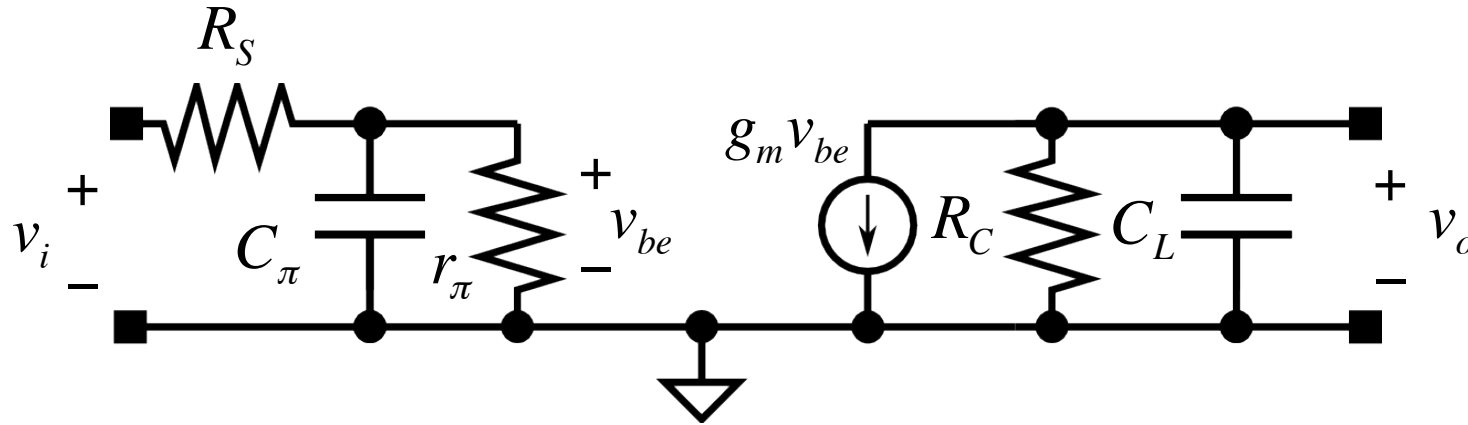


$$\begin{aligned} \frac{v_o}{v_{be}} &= -g_m \left( R_C \parallel \frac{1}{sC_L} \right) = -g_m \frac{R_C \frac{1}{sC_L}}{\frac{1}{sC_L} + R_C} = \frac{R_C}{1 + sR_C C_L} \\ &= g_m R_C \left( \frac{-1}{1 + sR_C C_L} \right) = A_2 \frac{-1}{1 + j \frac{\omega}{\omega_{p2}}} \end{aligned}$$

$$A_2 = g_m R_C$$

$$\omega_{p2} = \frac{1}{R_C C_L}$$



# The CE Amplifier with an Input Pole

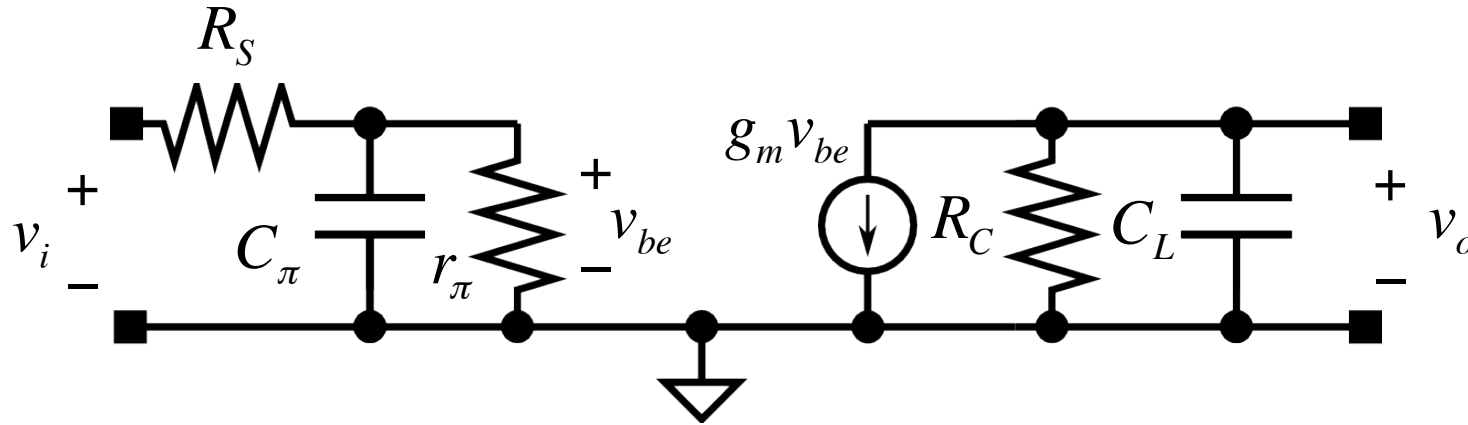

$$A_v = \frac{v_o}{v_i} = \frac{v_o}{v_{be}} \cdot \frac{v_{be}}{v_i} = A_1 A_2 \frac{-1}{\left(1 + j \frac{\omega}{\omega_{p1}}\right) \left(1 + j \frac{\omega}{\omega_{p2}}\right)}$$

$$= A_0 \frac{-1}{\left(1 + j \frac{\omega}{\omega_{p1}}\right) \left(1 + j \frac{\omega}{\omega_{p2}}\right)}$$


$$A_0 = A_1 A_2 = g_m R_C \frac{r_\pi}{r_\pi + R_S}$$

$$\omega_{p1} = \frac{1}{(r_\pi \parallel R_S) C_\pi}$$


$$\omega_{p2} = \frac{1}{R_C C_L} < \omega_{p1}$$




# Magnitude Response

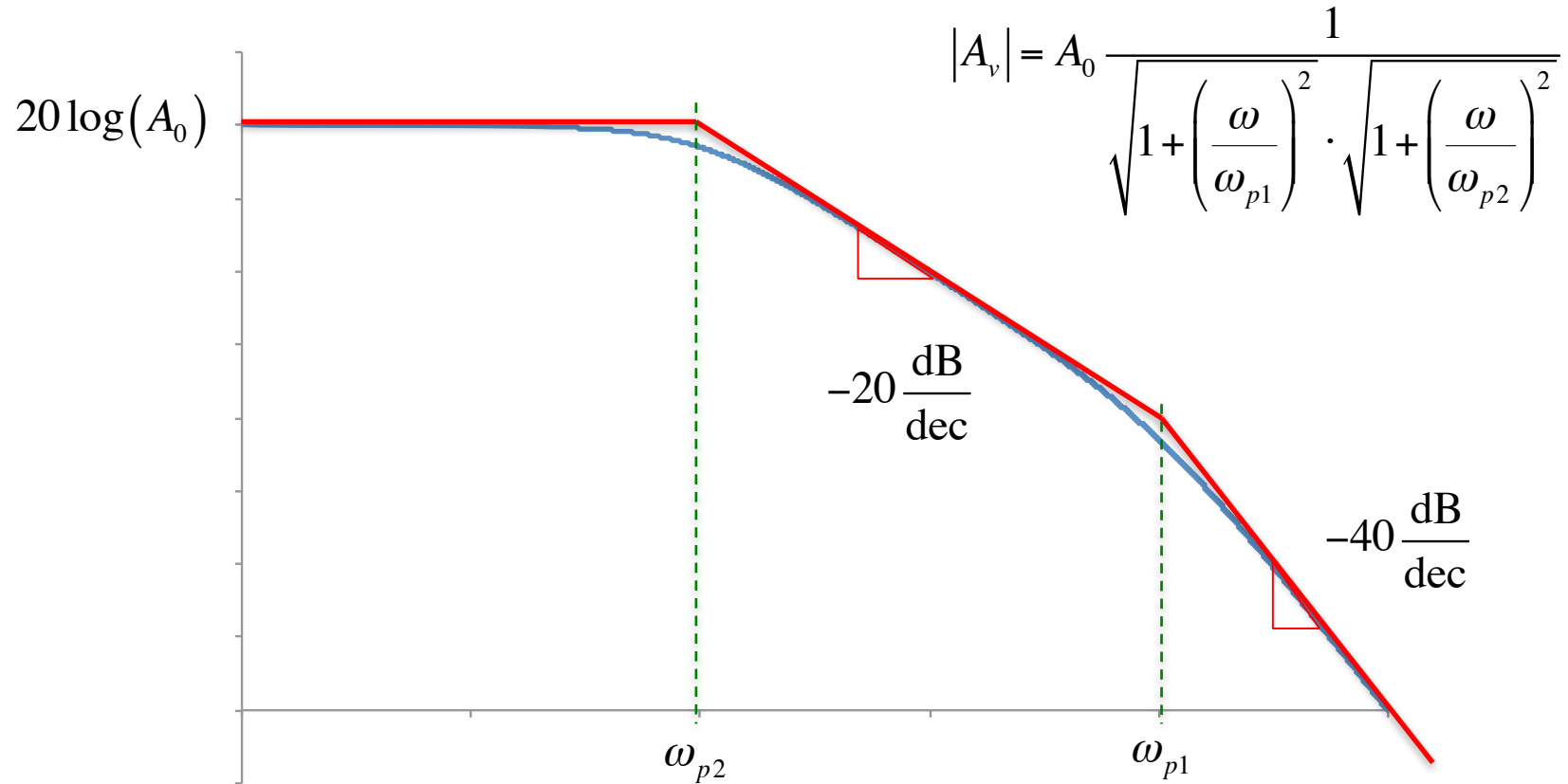


# Phase Response

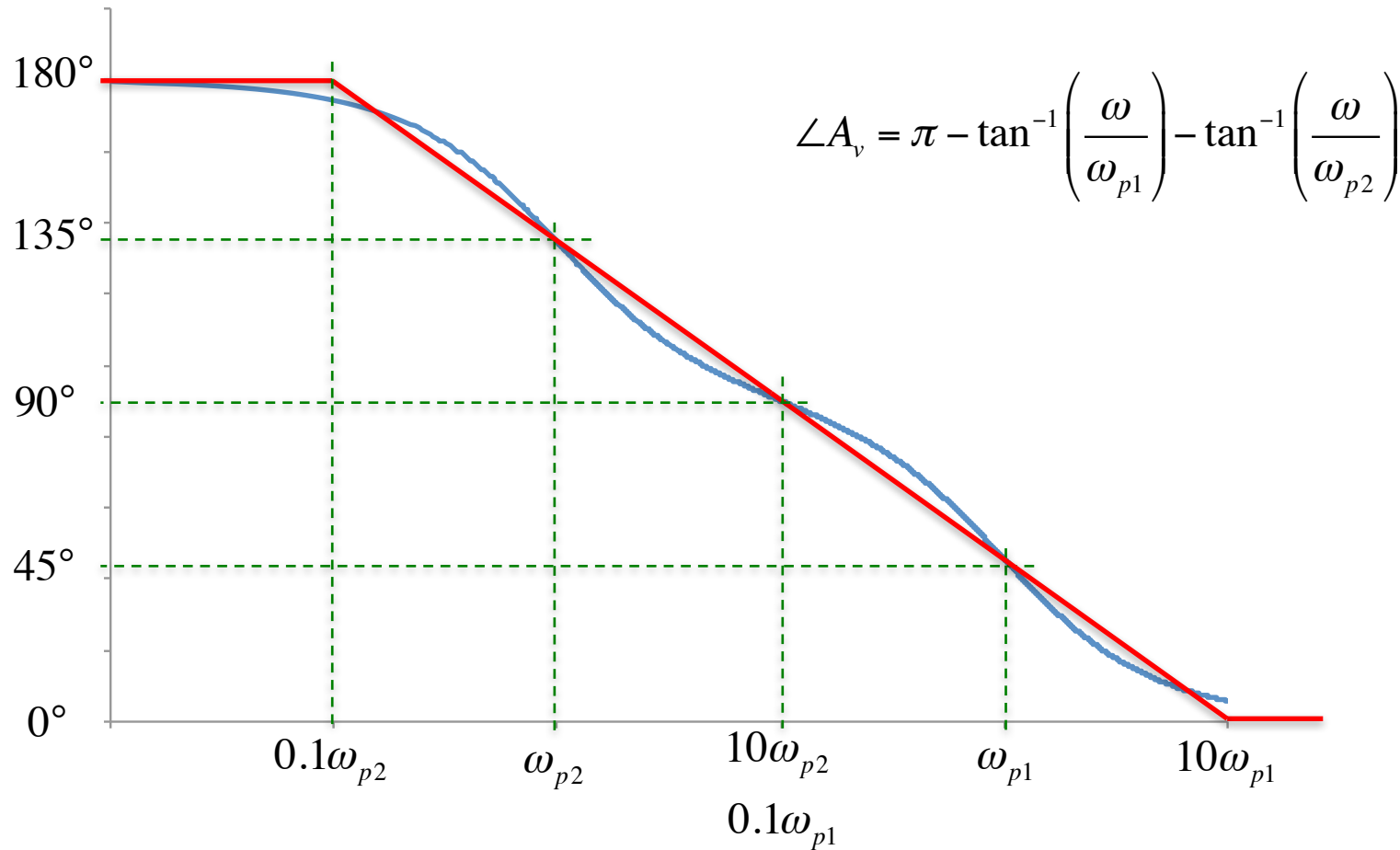

# The Effect of the Miller Capacitance

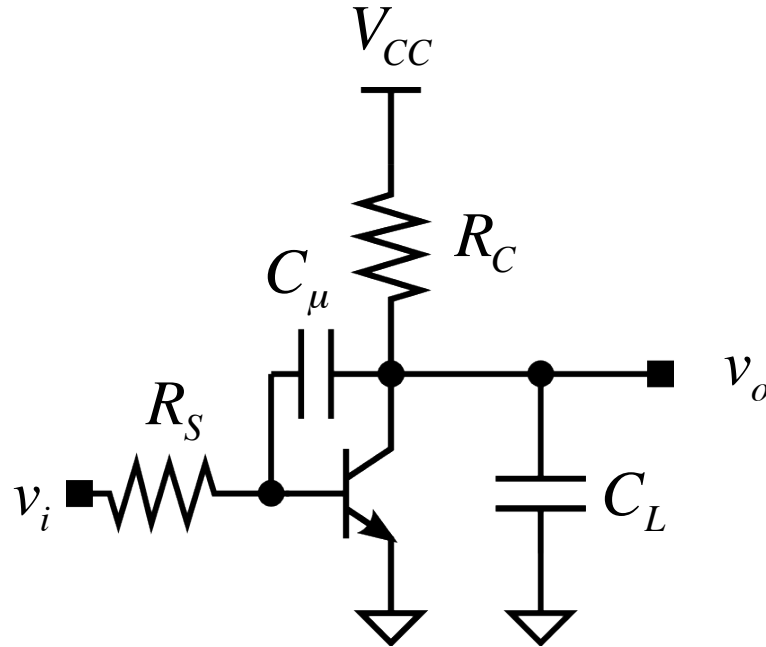

# Small Signal Model

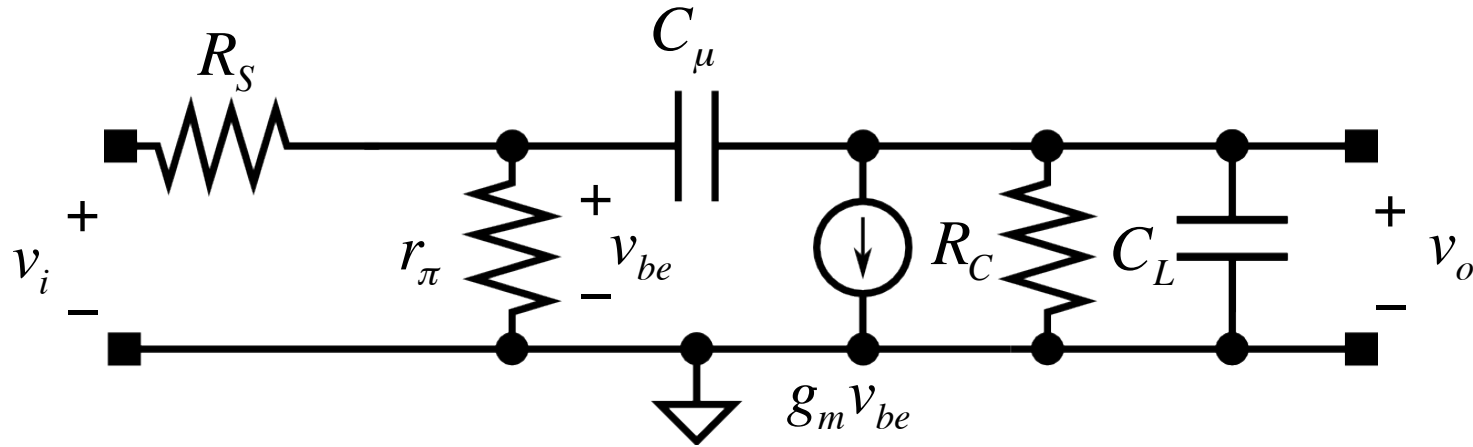


$$v_{be} \left( \frac{1}{R_S} + \frac{1}{r_\pi} + sC_\mu \right) - v_o (sC_\mu) = v_i \left( \frac{1}{R_S} \right)$$

$$-v_{be} (sC_\mu - g_m) + v_o \left( sC_\mu + \frac{1}{R_C} + sC_L \right) = 0$$



# Small Signal Model

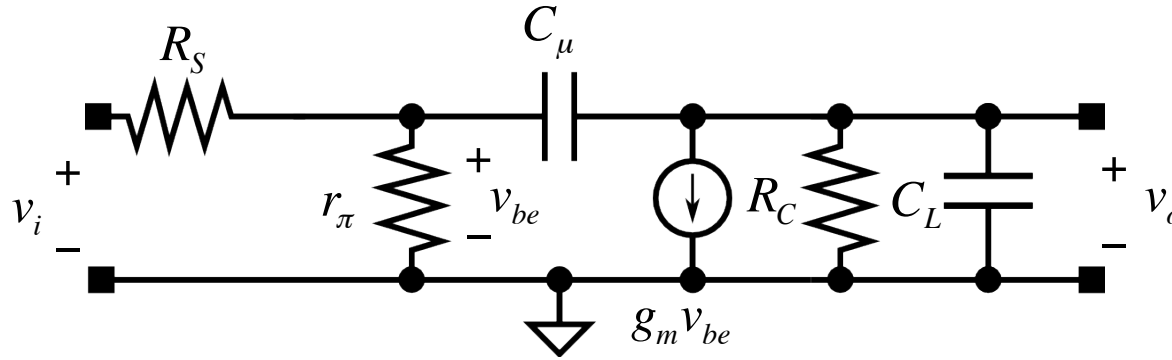


$$-v_{be} \left( sC_\mu - g_m \right) + v_o \left( sC_\mu + \frac{1}{R_C} + sC_L \right) = 0$$

$$\frac{v_o}{v_{be}} = \frac{sC_\mu - g_m}{sC_\mu + \frac{1}{R_C} + sC_L} = \frac{sR_C C_\mu - g_m R_C}{1 + sR_C (C_\mu + C_L)} = -g_m R_C \frac{1 - s \frac{C_\mu}{g_m}}{1 + sR_C (C_\mu + C_L)}$$




# Small Signal Model

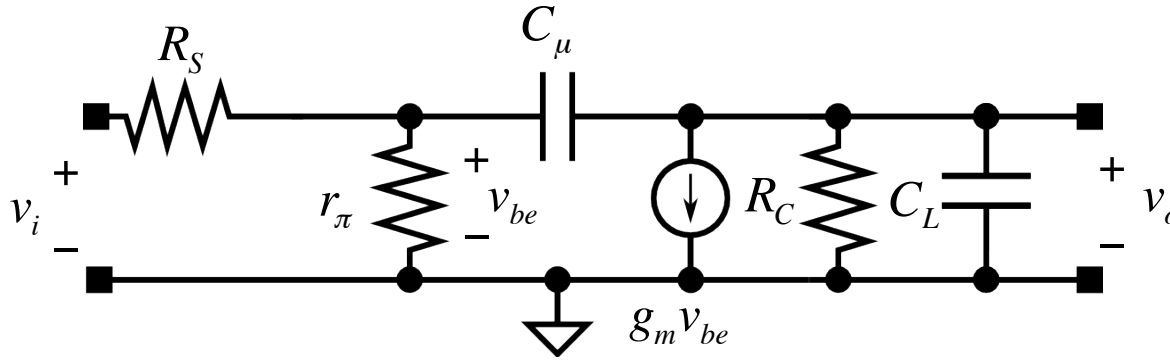

$$v_{be} \left( \frac{1}{R_S} + \frac{1}{r_\pi} + sC_\mu \right) - v_o (sC_\mu) = v_i \left( \frac{1}{R_S} \right) \Rightarrow v_{be} \left( \frac{1 + s(R_S \parallel r_\pi)C_\mu}{R_S \parallel r_\pi} \right) - v_o (sC_\mu) = v_i \left( \frac{1}{R_S} \right)$$

$$\left[ -\frac{1 + sR_C(C_\mu + C_L)}{g_m R_C \left( 1 - s\frac{C_\mu}{g_m} \right)} \left( \frac{1 + s(R_S \parallel r_\pi)C_\mu}{R_S \parallel r_\pi} \right) - sC_\mu \right] v_o = v_i \left( \frac{1}{R_S} \right)$$

# Small Signal Model

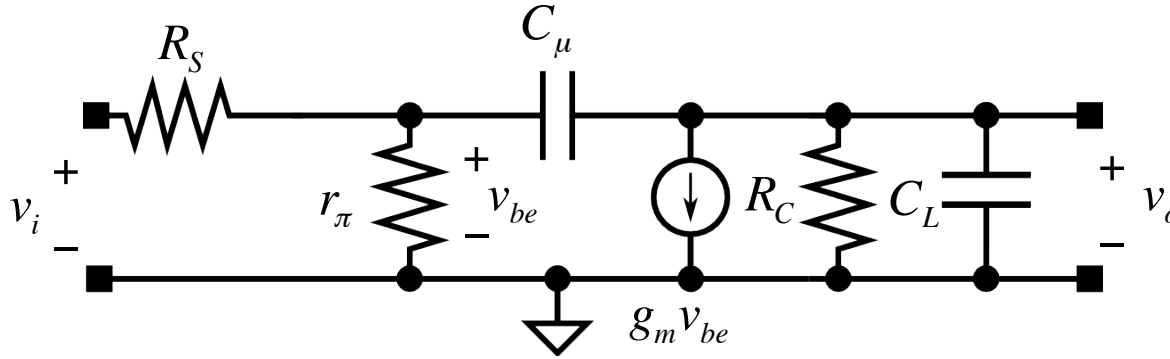


$$\frac{v_o}{v_i} = \frac{R_S \parallel r_\pi}{R_S} \frac{-g_m R_C \left(1 - s \frac{C_\mu}{g_m}\right)}{\left(1 + s R_C (C_\mu + C_L)\right) \left(1 + s (R_S \parallel r_\pi) C_\mu\right) + s C_\mu g_m R_C \left(1 - s \frac{C_\mu}{g_m}\right) (R_S \parallel r_\pi)}$$

$$= \frac{-g_m R_C \frac{r_\pi}{r_\pi + R_S} \left(1 - s \frac{C_\mu}{g_m}\right)}{\left(1 + s R_C (C_\mu + C_L)\right) \left(1 + s (R_S \parallel r_\pi) C_\mu\right) + s C_\mu g_m R_C (R_S \parallel r_\pi) - s^2 C_\mu^2 R_C (R_S \parallel r_\pi)}$$




# Small Signal Model

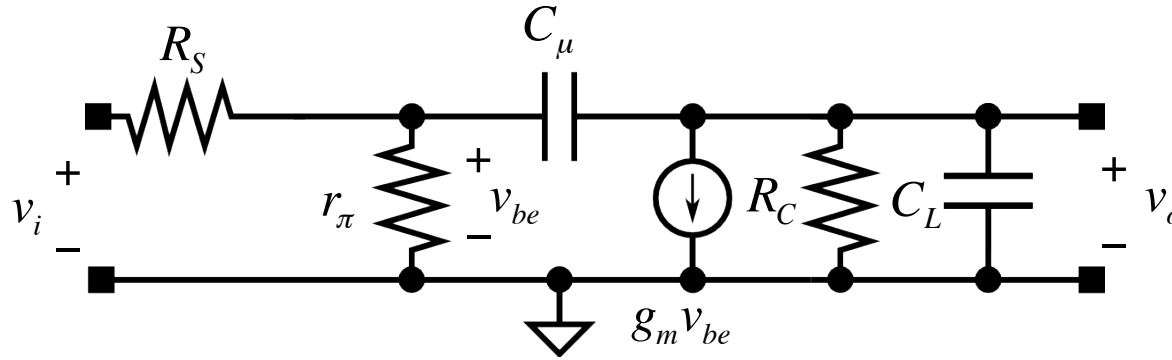

$$\begin{aligned} \frac{v_o}{v_i} &= \frac{-g_m R_C \frac{r_\pi}{r_\pi + R_S} \left(1 - s \frac{C_\mu}{g_m}\right)}{1 + s \left[ R_C (C_\mu + C_L) + (R_S \parallel r_\pi) C_\mu (1 + g_m R_C) \right] + s^2 \left[ (R_S \parallel r_\pi) R_C C_L C_\mu \right]} \\ &= \frac{A_0 \left(1 - \frac{s}{z}\right)}{1 + sX_1 + s^2 X_2} = \frac{A_0 \left(1 - \frac{s}{z}\right)}{\left(1 + \frac{s}{p_1}\right) \left(1 + \frac{s}{p_2}\right)} \end{aligned}$$



# Small Signal Model

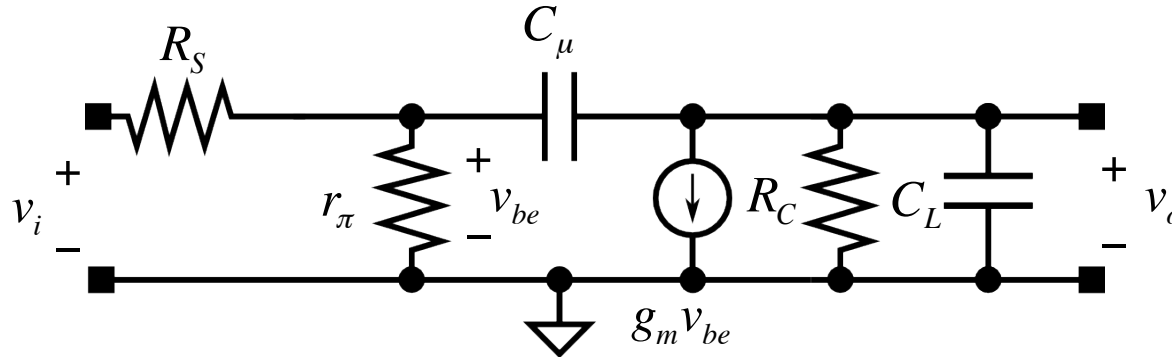

$$\frac{v_o}{v_i} = \frac{-g_m R_C \frac{r_\pi}{r_\pi + R_S} \left(1 - s \frac{C_\mu}{g_m}\right)}{1 + s \left[ R_C (C_\mu + C_L) + (R_S \parallel r_\pi) C_\mu (1 + g_m R_C) \right] + s^2 \left[ (R_S \parallel r_\pi) R_C C_L C_\mu \right]}$$

$$= \frac{A_0 \left(1 - \frac{s}{z}\right)}{\left(1 + \frac{s}{p_1}\right) \left(1 + \frac{s}{p_2}\right)} = \frac{A_0 \left(1 - \frac{s}{z}\right)}{1 + s \left(\frac{1}{p_1} + \frac{1}{p_2}\right) + s^2 \left(\frac{1}{p_1 p_2}\right)}$$



# Small Signal Model


$$\frac{v_o}{v_i} = \frac{-A_0 \left(1 - \frac{s}{z}\right)}{\left(1 + \frac{s}{p_1}\right) \left(1 + \frac{s}{p_2}\right)} = \frac{-A_0 \left(1 - \frac{s}{z}\right)}{1 + s \left(\frac{1}{p_1} + \frac{1}{p_2}\right) + s^2 \left(\frac{1}{p_1 p_2}\right)}$$

$$A_0 = g_m R_C \frac{r_\pi}{r_\pi + R_S}$$


$$\omega_{p1} \approx \frac{1}{R_C (C_\mu + C_L)} \approx \frac{1}{R_C C_L}$$

$$\omega_{p2} \approx \frac{1}{(R_S \parallel r_\pi) C_\mu (1 + g_m R_C)}$$

$$\omega_z = \frac{g_m}{C_\mu}$$

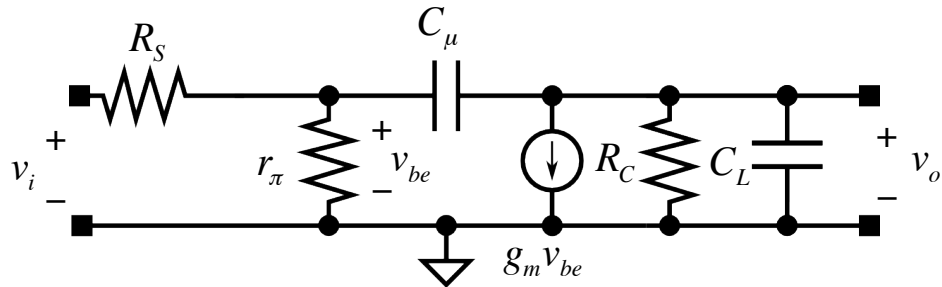

# Magnitude Response

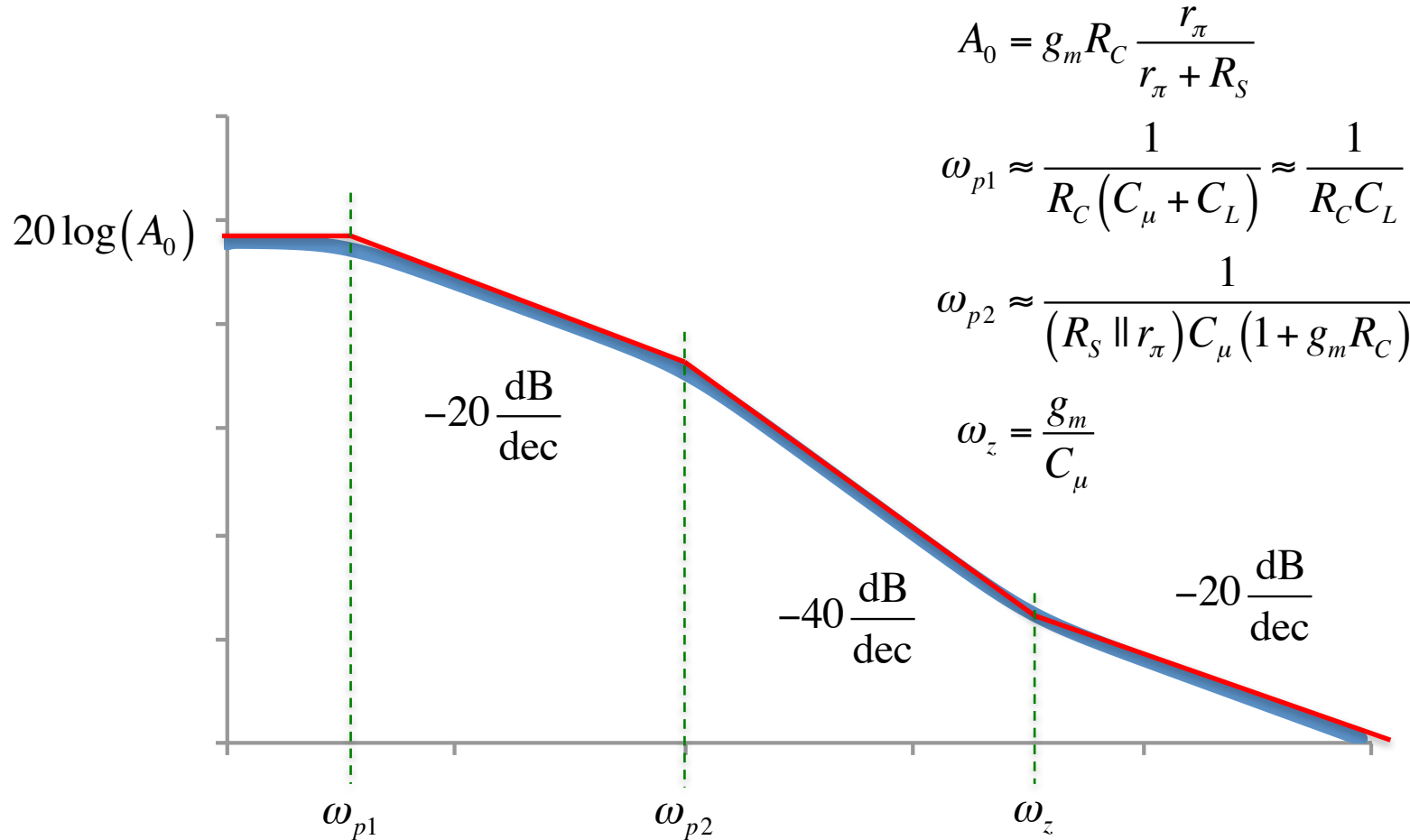


$$A_0 = g_m R_C \frac{r_\pi}{r_\pi + R_S}$$

$$\omega_{p1} \approx \frac{1}{R_C (C_\mu + C_L)} \approx \frac{1}{R_C C_L}$$

$$\omega_{p2} \approx \frac{1}{(R_S \parallel r_\pi) C_\mu (1 + g_m R_C)}$$


$$\omega_z = \frac{g_m}{C_\mu}$$

# Phase Response

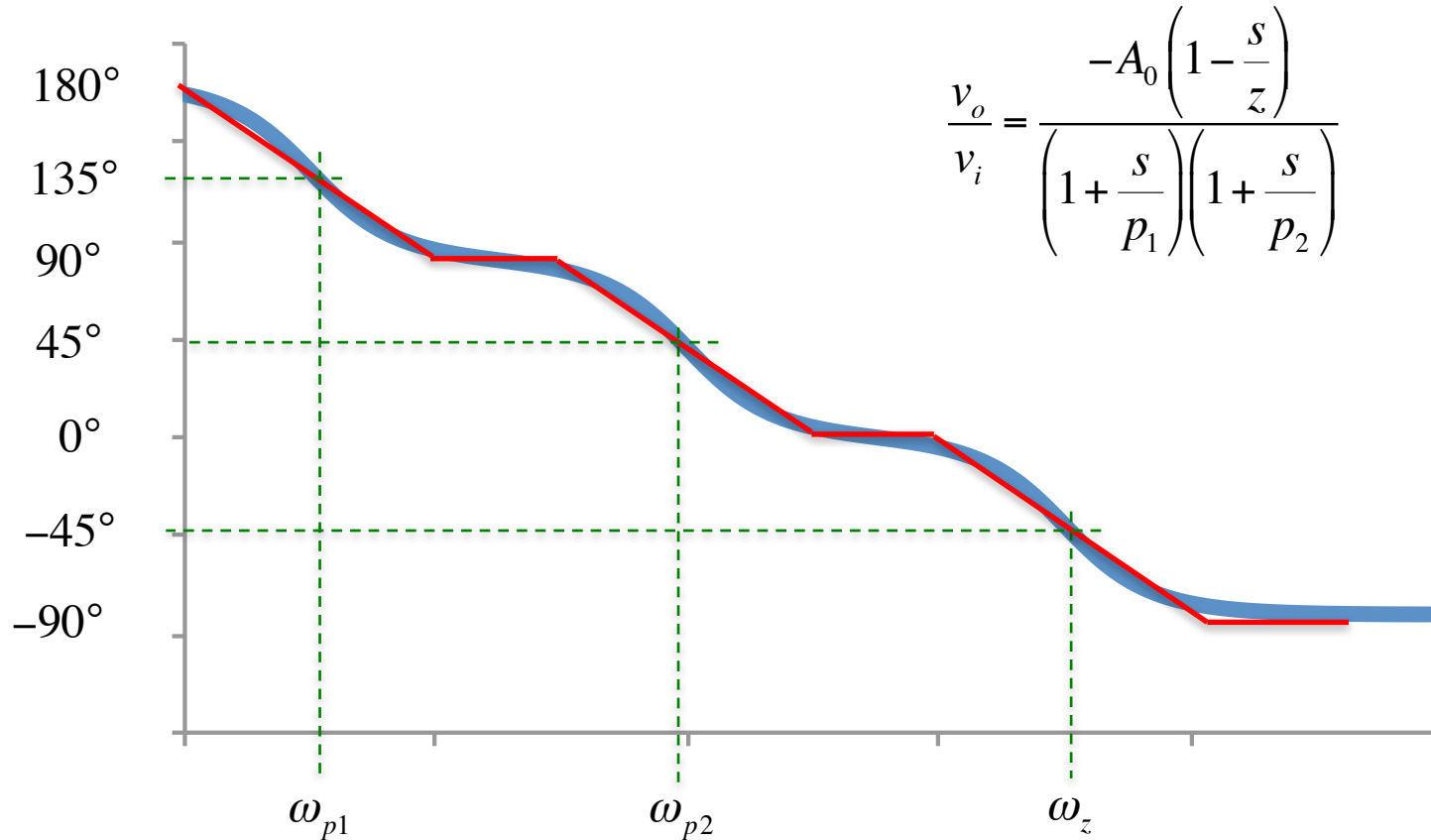




# Using an AC-Coupling Capacitor

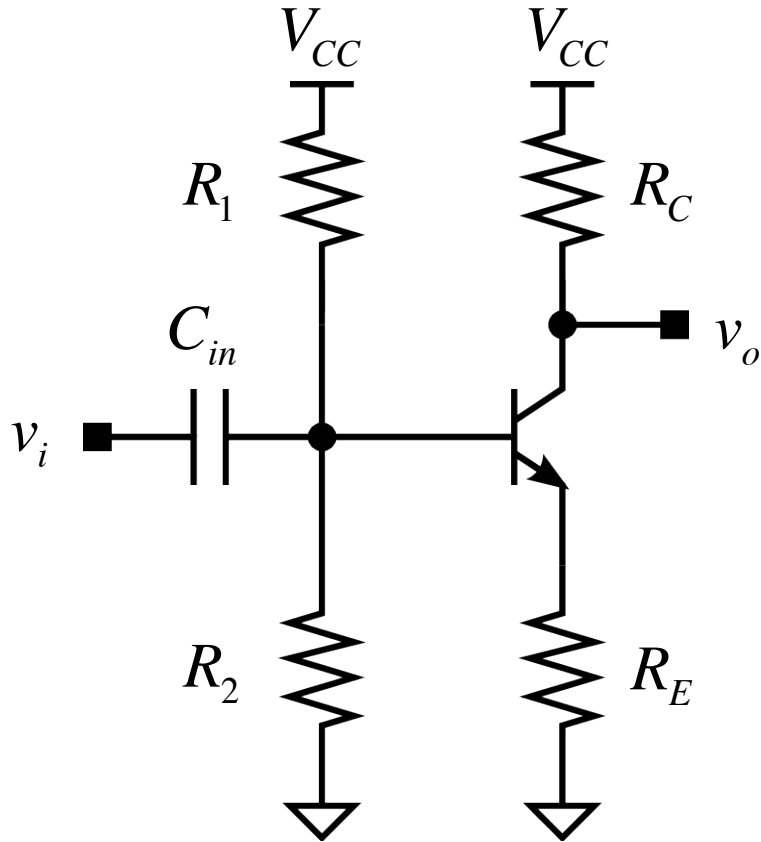
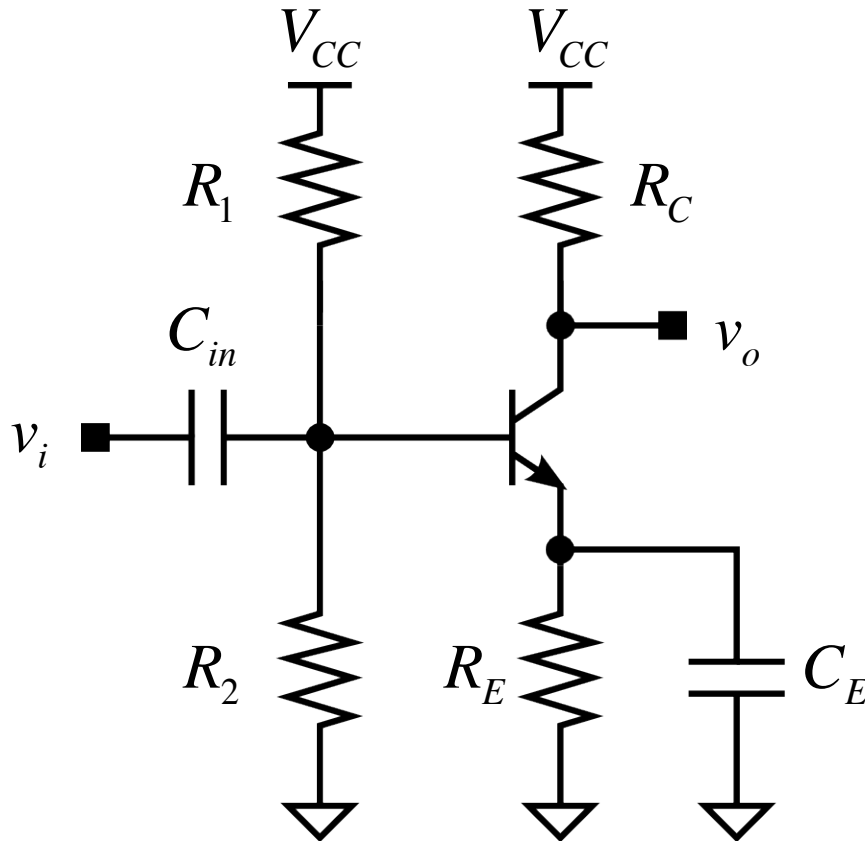
# Bypassing the Emitter Degeneration Resistor



# Next Meeting

- Frequency Response of Amplifiers

