



EEE 51: Second Semester 2017 - 2018


Lecture 22

Feedback Frequency Response and Oscillators

Varying Loop Gain: $f = 0.001$

Two-Pole Amplifier
Frequency Response


PM = 84.8 °

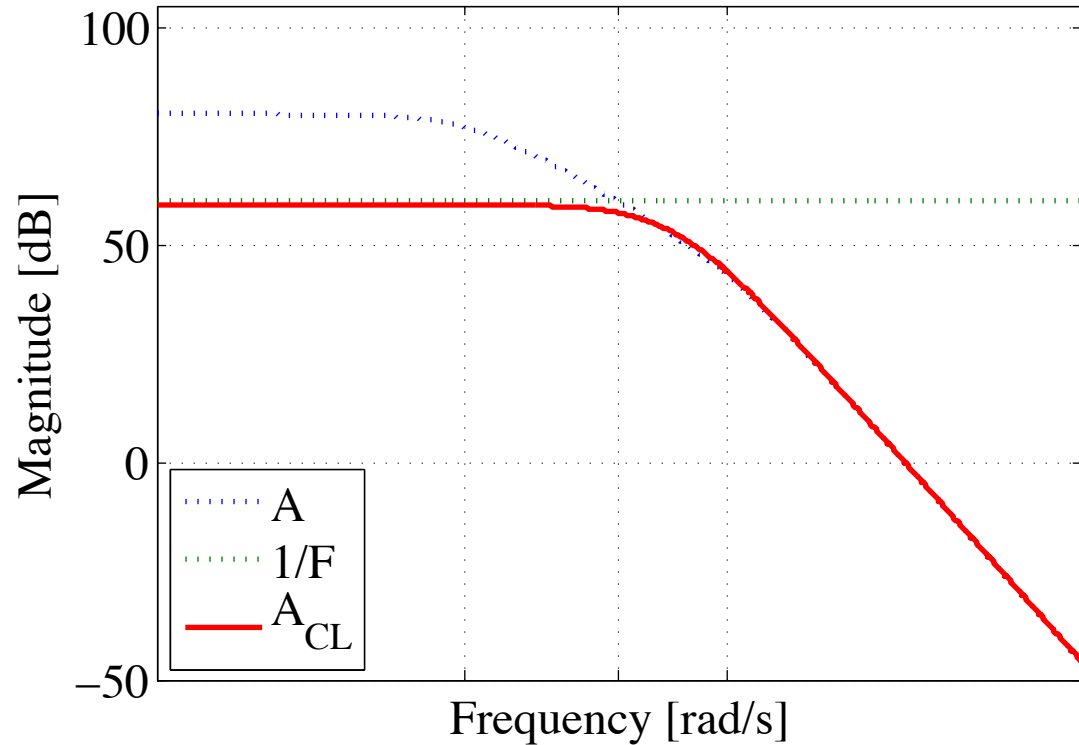

Varying Loop Gain: $f = 0.01$

Two-Pole Amplifier
Frequency Response


PM = 39.6 °

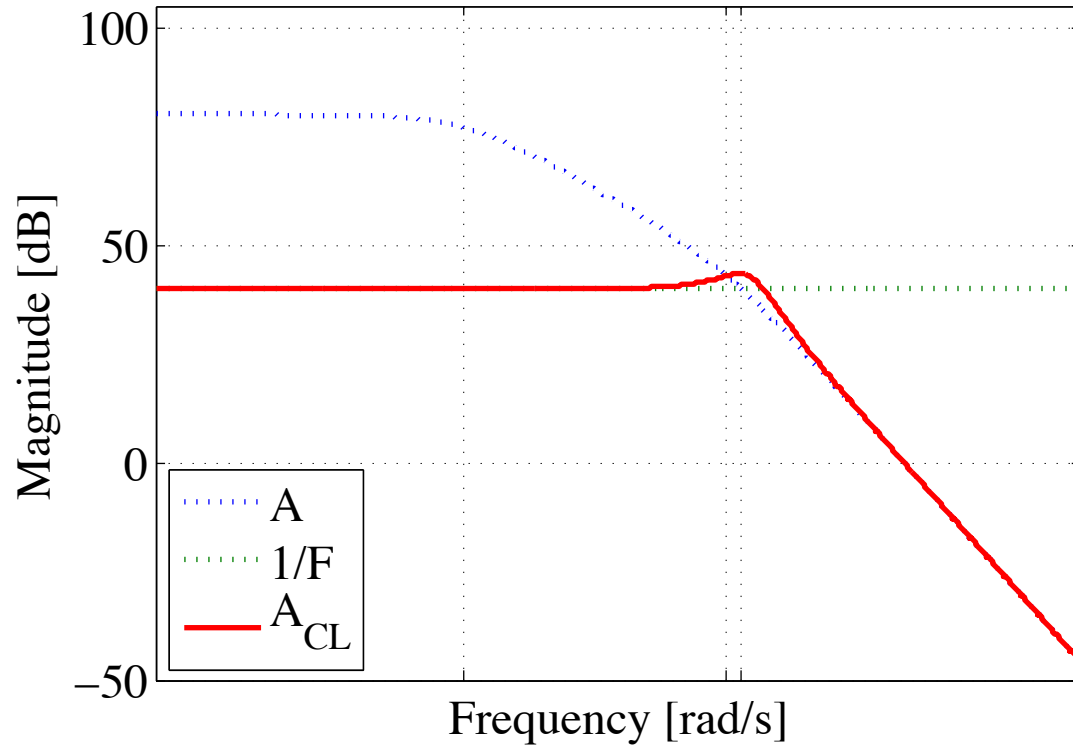

Varying Loop Gain: $f = 0.1$

Two-Pole Amplifier
Frequency Response


PM = 13 °

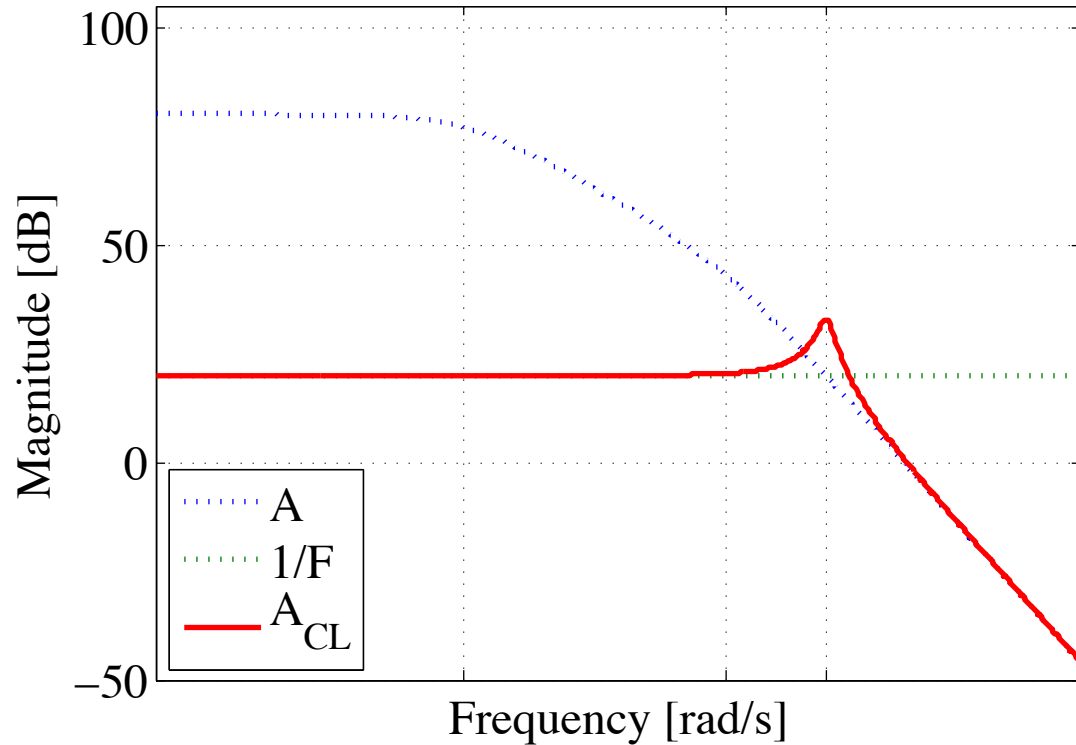


Varying Loop Gain: $f = 1$

Two-Pole Amplifier
Frequency Response

PM = 4.13 °

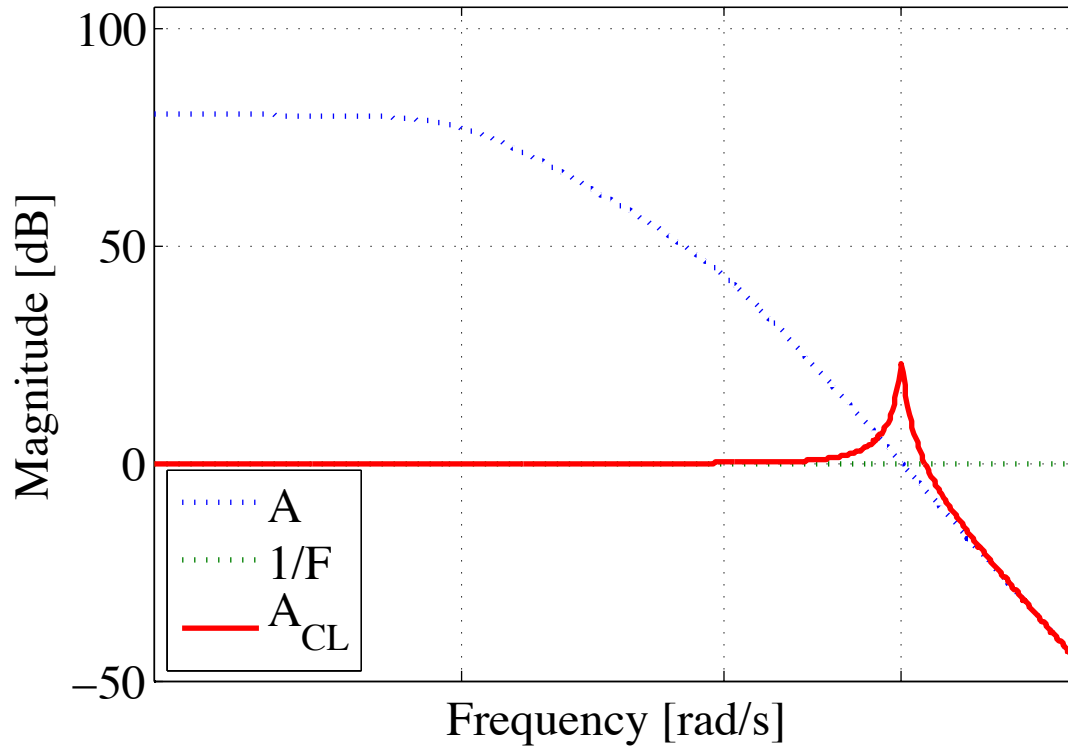


Open Loop Amplifier Step Response

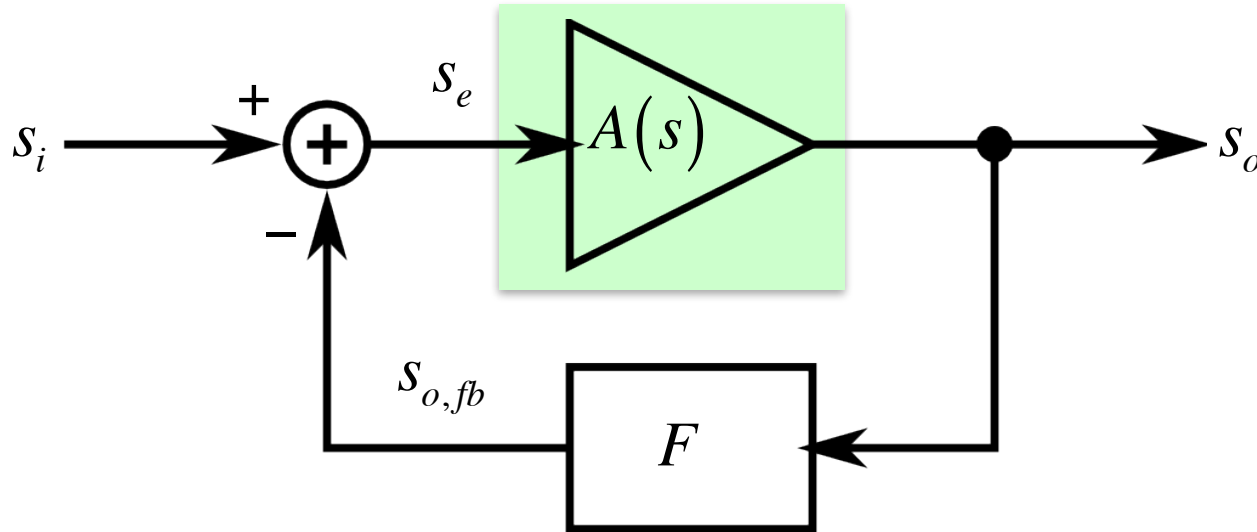


$$v_o(s) = \frac{-A_0}{\left(1 + \frac{s}{\omega_{p1}}\right)\left(1 + \frac{s}{\omega_{p2}}\right)} \cdot \frac{V_{step}}{s}$$

Open Loop Amplifier Step Response

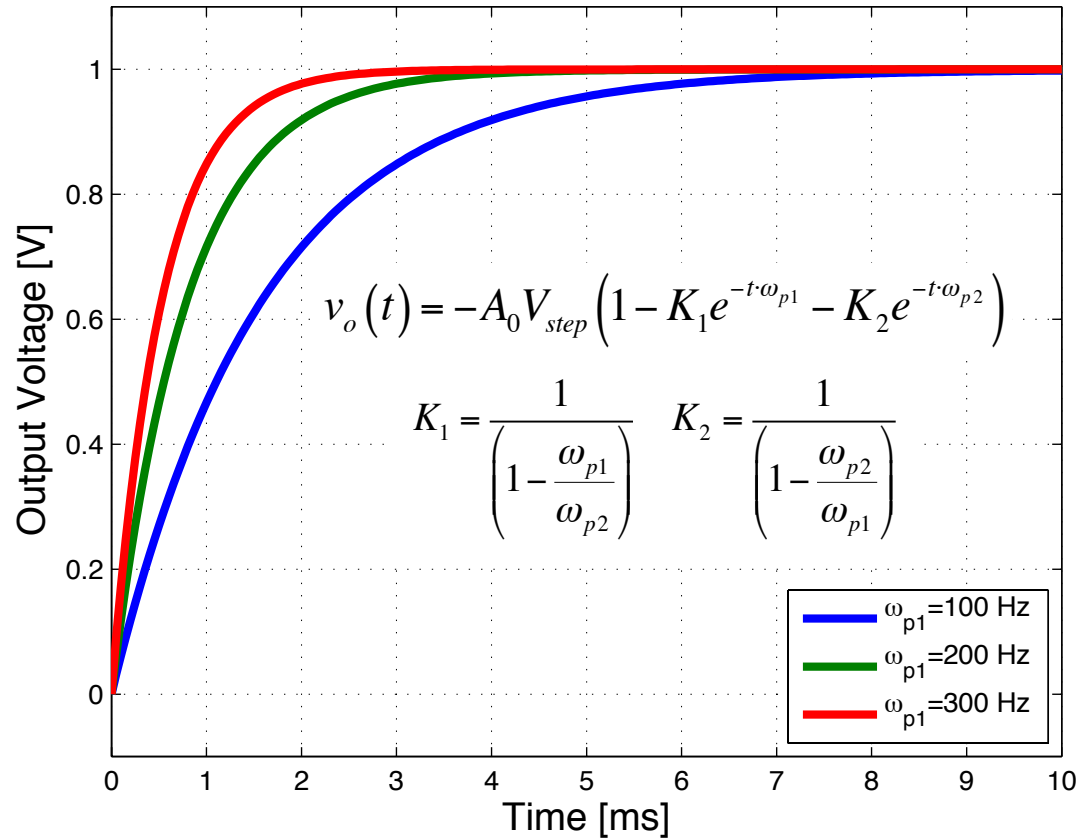

Closed Loop Amplifier Step Response

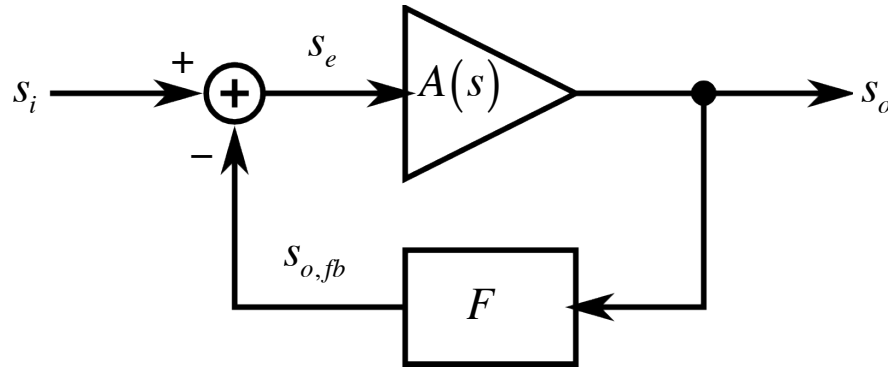

$$T(s) = \frac{A_0 F}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right)}$$

$$\frac{v_o(s)}{v_i(s)} = -\frac{1}{F} \cdot \frac{T(s)}{1+T(s)} = -\frac{1}{F} \cdot \frac{T_0}{1 + T_0 + s \left(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p1}} \right) + s^2 \left(\frac{1}{\omega_{p1} \omega_{p2}} \right)}$$



Closed Loop Amplifier Step Response

$$\begin{aligned}\frac{v_o(s)}{v_i(s)} &= -\frac{1}{F} \cdot \frac{T(s)}{1+T(s)} = -\frac{1}{F} \cdot \frac{T_0}{1+T_0 + s\left(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}}\right) + s^2\left(\frac{1}{\omega_{p1}\omega_{p2}}\right)} \\ &= -\frac{1}{F} \cdot \frac{T_0}{1+T_0} \cdot \frac{1}{1 + s\left(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}}\right)\frac{1}{1+T_0} + s^2\left(\frac{1}{\omega_{p1}\omega_{p2}}\right)\frac{1}{1+T_0}} \\ &= -A_0\omega_{p1}\omega_{p2} \cdot \frac{1}{s^2 + s(\omega_{p1} + \omega_{p2}) + \omega_{p1}\omega_{p2}(1+T_0)}\end{aligned}$$



Closed Loop Amplifier Step Response

$$\frac{v_o(s)}{v_i(s)} = -A_0 \omega_{p1} \omega_{p2} \cdot \frac{1}{s^2 + s(\omega_{p1} + \omega_{p2}) + \omega_{p1} \omega_{p2} (1 + T_0)}$$

Roots of the denominator:

$$\begin{aligned} s &= -\frac{(\omega_{p1} + \omega_{p2})}{2} \pm \frac{\sqrt{(\omega_{p1} + \omega_{p2})^2 - 4\omega_{p1}\omega_{p2}(1 + T_0)}}{2} \\ &= -\frac{(\omega_{p1} + \omega_{p2})}{2} \pm \frac{\sqrt{\omega_{p1}^2 + 2\omega_{p1}\omega_{p2} + \omega_{p2}^2 - 4\omega_{p1}\omega_{p2} - 4\omega_{p1}\omega_{p2}T_0}}{2} \\ &= -\frac{(\omega_{p1} + \omega_{p2})}{2} \pm \frac{\sqrt{\omega_{p1}^2 - 2\omega_{p1}\omega_{p2} + \omega_{p2}^2 - 4\omega_{p1}\omega_{p2}T_0}}{2} \\ &= -\frac{(\omega_{p1} + \omega_{p2})}{2} \pm \frac{\sqrt{(\omega_{p1} - \omega_{p2})^2 - 4\omega_{p1}\omega_{p2}T_0}}{2} \end{aligned}$$



Closed Loop Amplifier Step Response

$$\begin{aligned}s &= -\frac{(\omega_{p1} + \omega_{p2})}{2} \pm \frac{\sqrt{(\omega_{p1} - \omega_{p2})^2 - 4\omega_{p1}\omega_{p2}T_0}}{2} \\&= -\frac{(\omega_{p1} + \omega_{p2})}{2} \pm j\frac{\sqrt{4\omega_{p1}\omega_{p2}T_0 - (\omega_{p1} - \omega_{p2})^2}}{2} \\&= -\rho \pm j\mu\end{aligned}$$

$$\rho = \frac{(\omega_{p1} + \omega_{p2})}{2} \quad \mu = \frac{\sqrt{4\omega_{p1}\omega_{p2}T_0 - (\omega_{p1} - \omega_{p2})^2}}{2}$$



Step Response

$$\begin{aligned}v_o(s) &= -A_0\omega_{p1}\omega_{p2} \cdot \frac{1}{s^2 + s(\omega_{p1} + \omega_{p2}) + \omega_{p1}\omega_{p2}(1 + T_0)} \cdot \frac{V_{step}}{s} \\&= -\frac{A_0\omega_{p1}\omega_{p2}}{(s + [\rho - j\mu])(s + [\rho + j\mu])} \cdot \frac{V_{step}}{s} \\&= -\frac{A_0\omega_{p1}\omega_{p2}}{(\rho^2 + \mu^2)\left(1 + \frac{s}{\rho - j\mu}\right)\left(1 + \frac{s}{\rho + j\mu}\right)} \cdot \frac{V_{step}}{s} \\&= -\frac{A_0}{1 + T_0} \cdot \frac{1}{\left(1 + \frac{s}{\rho - j\mu}\right)\left(1 + \frac{s}{\rho + j\mu}\right)} \cdot \frac{V_{step}}{s}\end{aligned}$$



For Real Roots:

$$\left(\omega_{p1} - \omega_{p2}\right)^2 \geq 4\omega_{p1}\omega_{p2}T_0$$

$$0 = \left(\omega_{p1} - \omega_{p2}\right)^2 - 4\omega_{p1}\omega_{p2}T_0$$

$$0 = \omega_{p1}^2 - 2\omega_{p1}\omega_{p2} + \omega_{p2}^2 - 4\omega_{p1}\omega_{p2}T_0$$

$$0 = \omega_{p1}^2 - 2(1 + 2T_0)\omega_{p1}\omega_{p2} + \omega_{p2}^2$$

$$\begin{aligned}\omega_{p2,c} &= (1 + 2T_0)\omega_{p1} \pm \sqrt{(1 + 2T_0)^2 \omega_{p1}^2 - \omega_{p1}^2} \\ &= (1 + 2T_0)\omega_{p1} \pm \sqrt{(1 + 2T_0)^2 \omega_{p1}^2 - \omega_{p1}^2} \\ &\approx (2T_0 \pm 2T_0)\omega_{p1} = 4T_0\omega_{p1}\end{aligned}$$



For Real Roots:


$$\omega_{p2,c} = 4T_0\omega_{p1}$$

$$\omega_u \cong T_0\omega_{p1}$$

$$\begin{aligned} PM_c &= \angle T(s) - (-180^\circ) \\ &= -\tan^{-1}(T_0) - \tan^{-1}\left(\frac{1}{4}\right) - (-180^\circ) \\ &\approx 90^\circ - \tan^{-1}\left(\frac{1}{4}\right) = \tan^{-1}(4) = 75.96^\circ \end{aligned}$$



Closed Loop Step Response

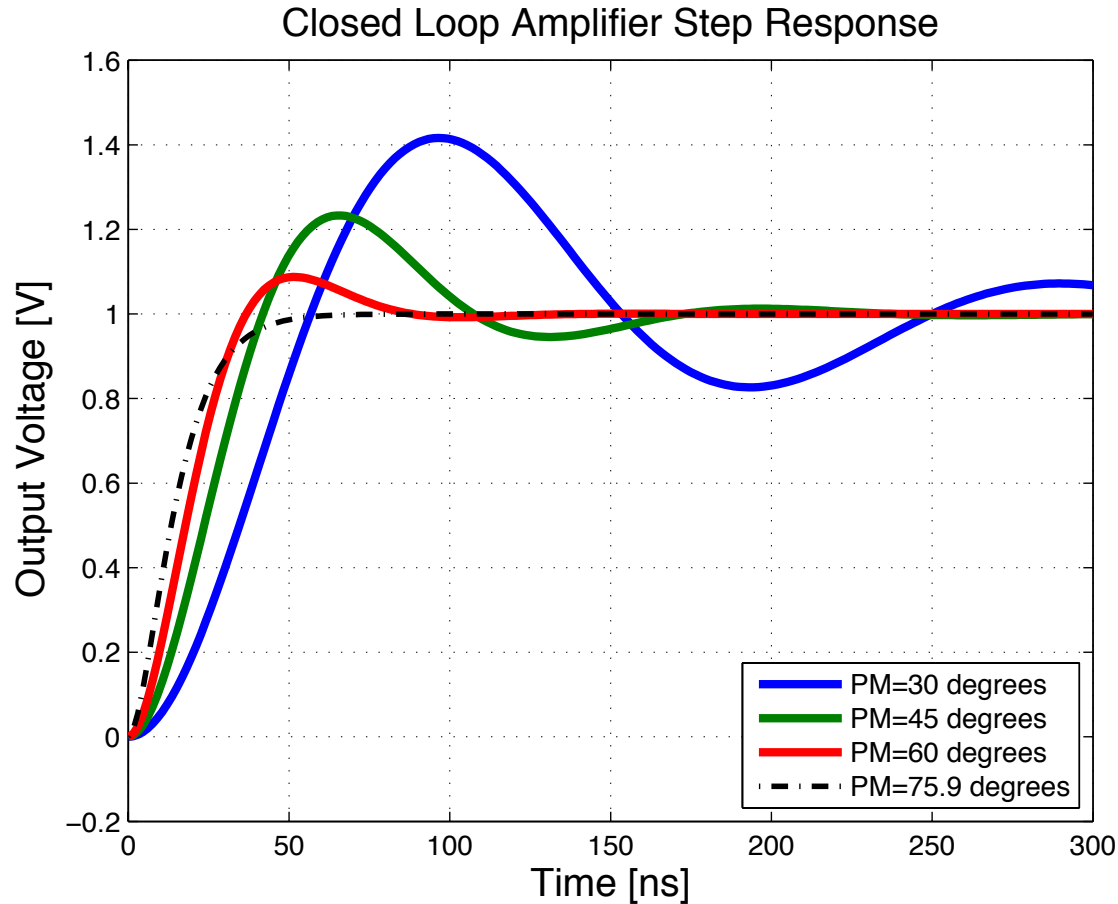


Oscillators

- Sinusoidal Oscillators
 - General Structure
 - RC Oscillators
 - LC Oscillators
 - Crystal Oscillators



Sinusoidal Oscillators

- A Feedback Network:

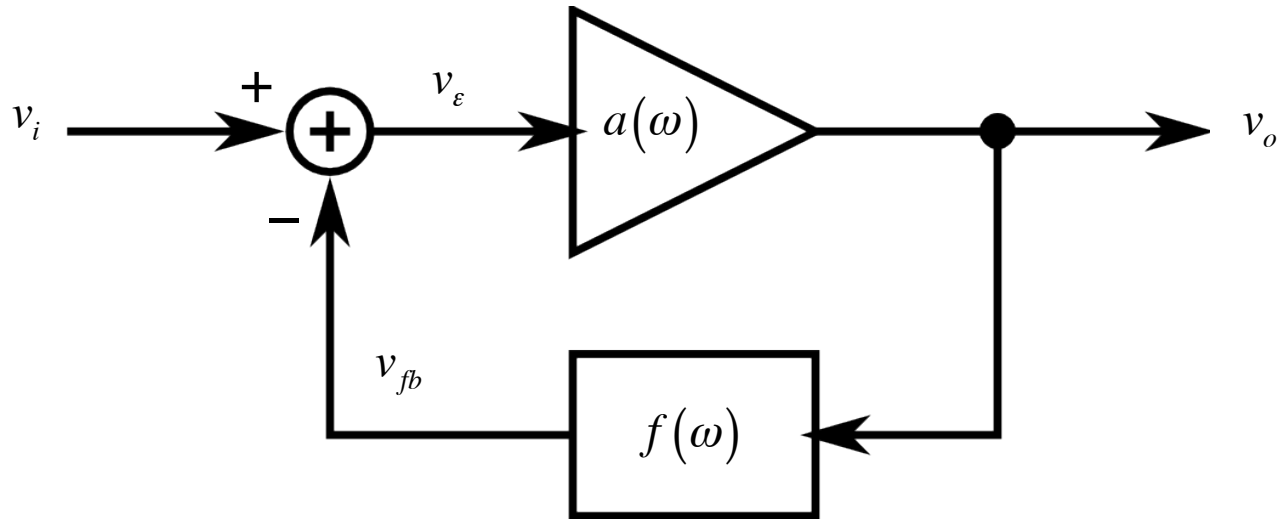


$$A_{CL}(\omega) = \frac{v_o}{v_i} = \frac{a(\omega)}{1 + a(\omega) \cdot f(\omega)} = \frac{a(\omega)}{1 + T(\omega)}$$

$$T(\omega) = a(\omega) \cdot f(\omega)$$



Negative Feedback

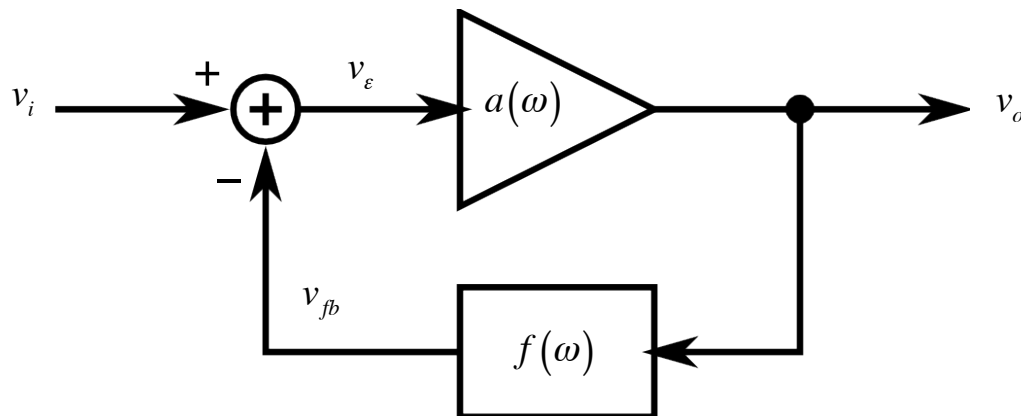

$$A_{CL}(\omega) = \frac{v_o}{v_i} = \frac{a(\omega)}{1 + a(\omega) \cdot f(\omega)} = \frac{a(\omega)}{1 + T(\omega)}$$

Take the case when

$$T(\omega) = a(\omega) \cdot f(\omega) = -1 = 1 \angle 180^\circ$$


The closed-loop gain will be:

$$A_{CL}(\omega) = \frac{v_o}{v_i} = \frac{a(\omega)}{1 + T(\omega)} \rightarrow \infty$$


Thus, for $v_i = 0$, v_o can be non-zero!




Case: $T(\omega) = -1$

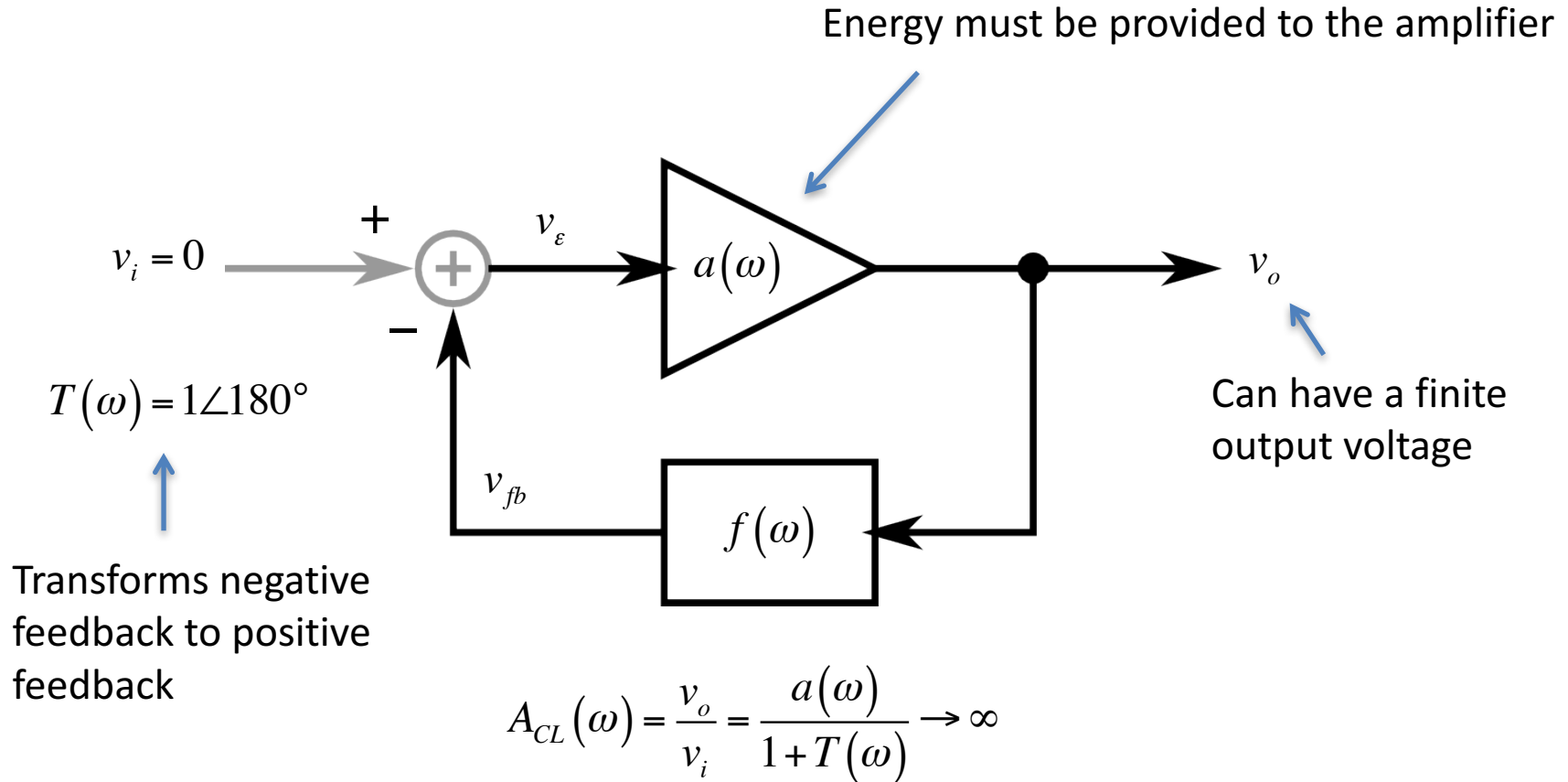

Case: $T(\omega) = -1$

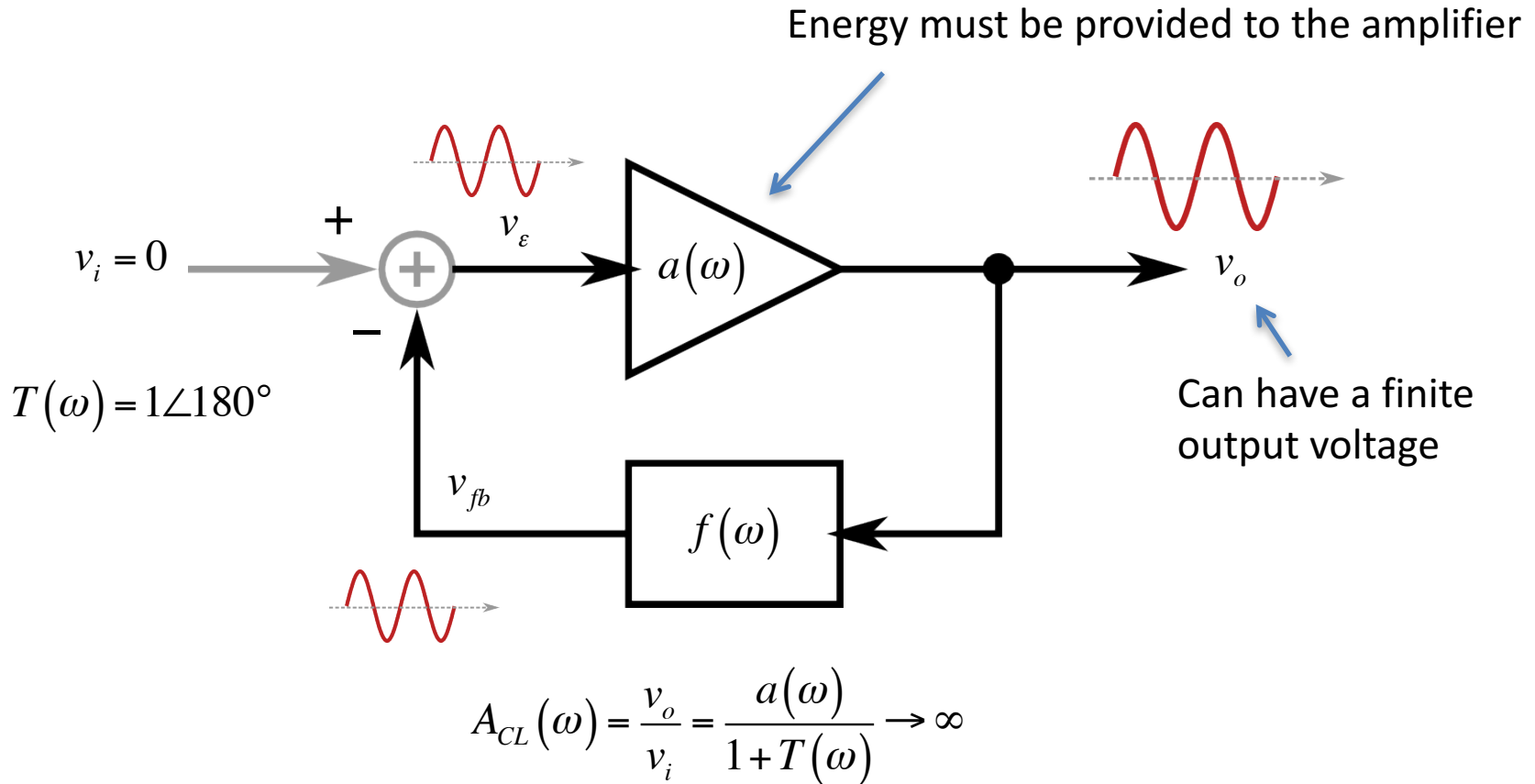

Barkhausen's Criterion

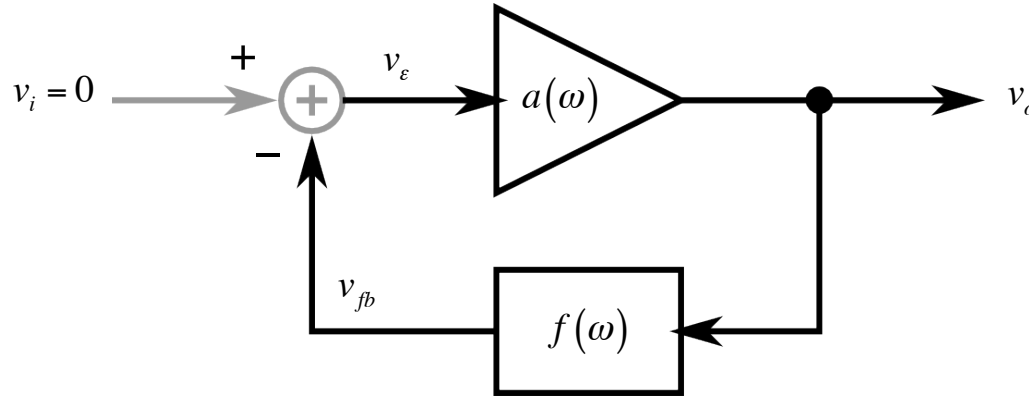



The circuit will be able to sustain steady state oscillations only at frequencies where:

$$|T(\omega)| = |a(\omega) \cdot f(\omega)| = 1$$

$$\angle T(\omega) = 180^\circ \cdot (2n + 1) \quad n \in 0, 1, 2, 3 \dots$$



Barkhausen's Criterion

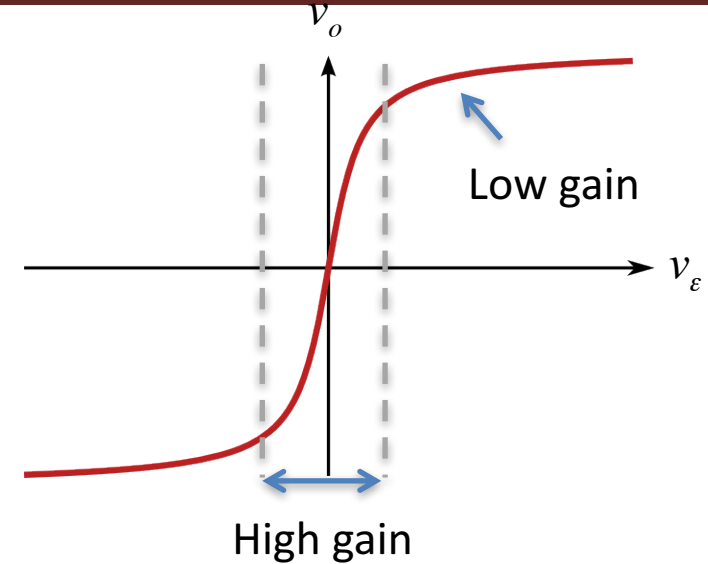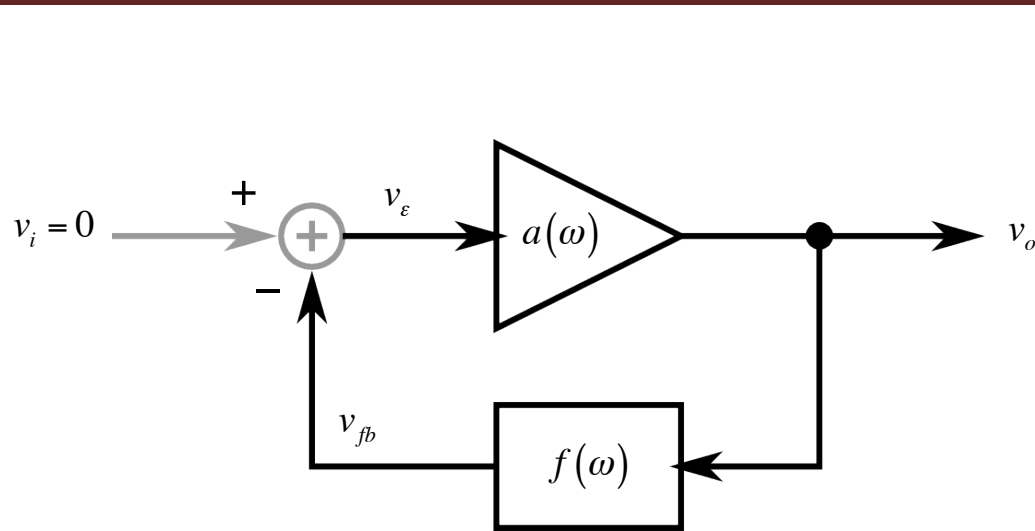


Note: If $|T(\omega)| = |a(\omega) \cdot f(\omega)| \geq 1$ and $\angle T(\omega) = 180^\circ \cdot (2n+1)$ $n \in 0, 1, 2, 3, \dots$

The circuit will meet $|T(\omega)| = 1$ by going nonlinear

- Resulting in reduced amplifier gain

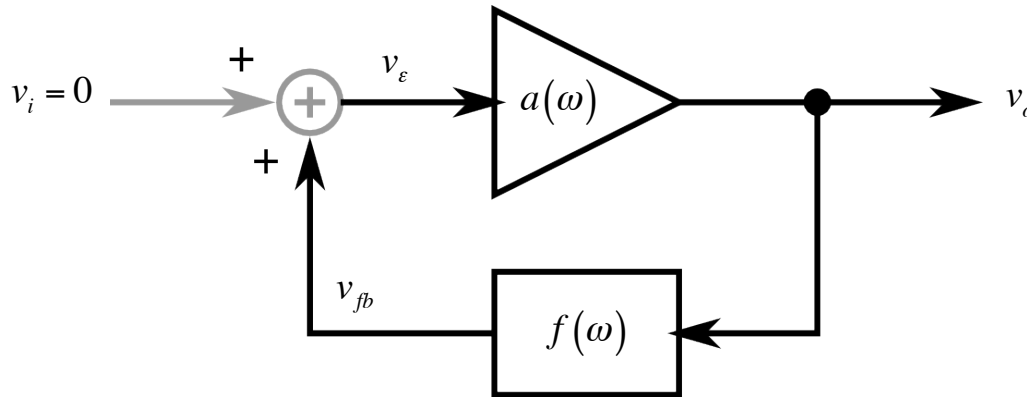Barkhausen's Criterion (Positive Feedback)




The circuit will be able to sustain steady state oscillations only at frequencies where:

$$|T(\omega)| = |a(\omega) \cdot f(\omega)| = 1$$

$$\angle T(\omega) = 360^\circ \cdot n \quad n \in 0, 1, 2, 3, \dots$$



Example: The Phase Shift Oscillator

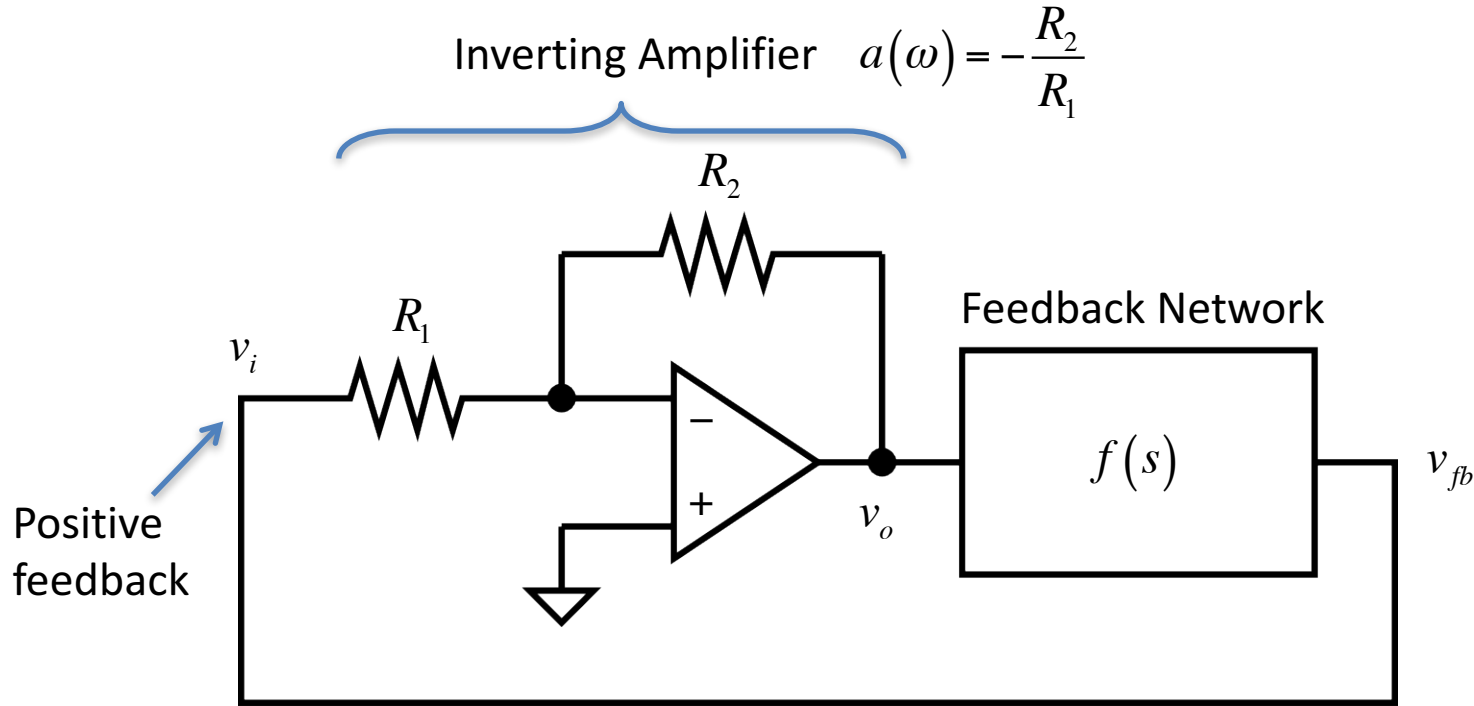


Loop gain needed
to oscillate:

$$T(\omega) = a(\omega) \cdot f(\omega) = -\frac{R_2}{R_1} \cdot f(\omega) = 1 \angle 0^\circ \quad \Rightarrow \quad \angle f(s) = -180^\circ$$

Phase Shift Feedback Network

- Consider the RC circuit

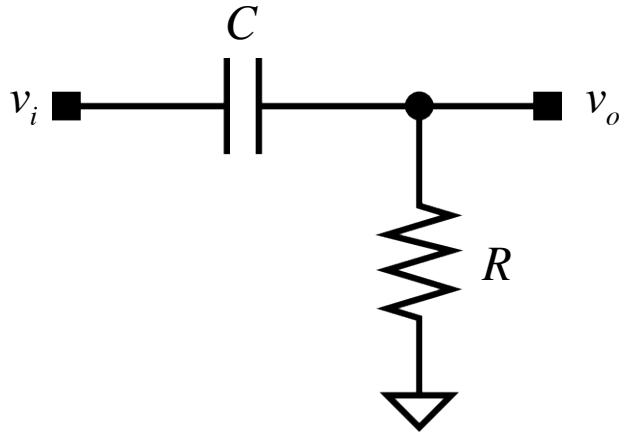

$$\frac{v_o}{v_i} = \frac{sRC}{1 + sRC}$$

Magnitude: $\left| \frac{v_o}{v_i} \right| = \frac{\omega RC}{\sqrt{1 + \omega^2 (RC)^2}}$

Phase: $\angle \frac{v_o}{v_i} = 90^\circ - \tan^{-1} \omega RC$

Low frequencies:

$$\omega \rightarrow 0 \quad \angle \frac{v_o}{v_i} \rightarrow 90^\circ$$

High frequencies:


$$\omega \rightarrow \infty \quad \angle \frac{v_o}{v_i} \rightarrow 0^\circ$$

Need at least 3 stages
to get to -180°



Phase Shift Feedback Network

- Consider the RC circuit

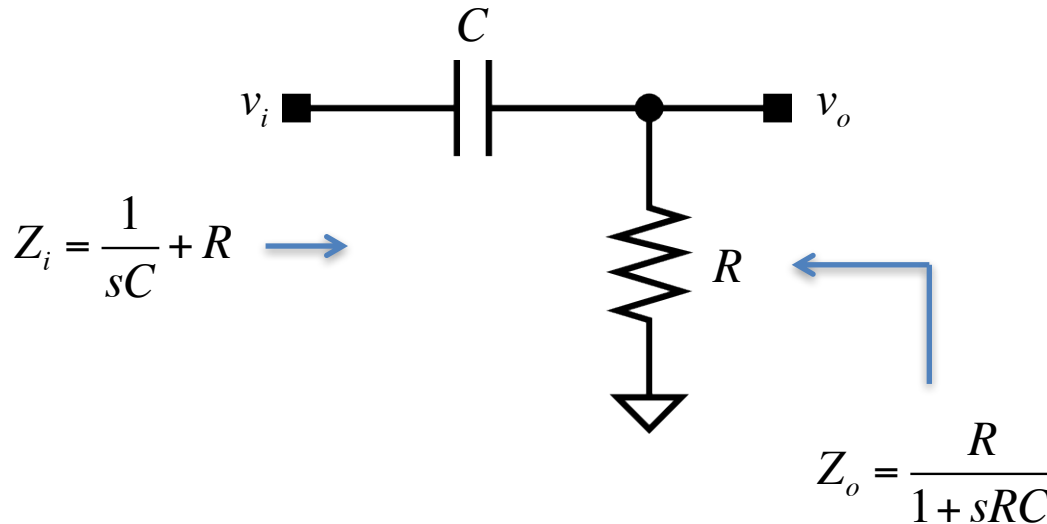


$$\frac{v_o}{v_i} = \frac{sRC}{1 + sRC}$$

$$\left| \frac{v_o}{v_i} \right| = \frac{\omega RC}{\sqrt{1 + \omega^2 (RC)^2}}$$

$$\angle \frac{v_o}{v_i} = 90^\circ - \tan^{-1} \omega RC$$

Phase Shift Feedback Network

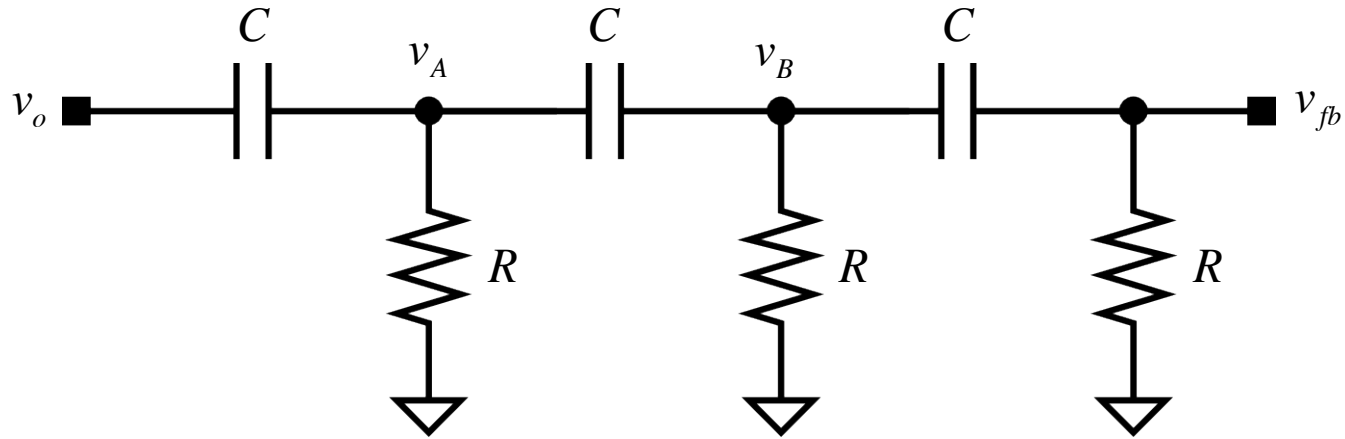


$$f(s) = \frac{v_{fb}}{v_o} = \frac{1}{1 + \frac{6}{sRC} + \frac{5}{s^2(RC)^2} + \frac{1}{s^3(RC)^3}}$$

$$f(\omega) = \frac{v_{fb}}{v_o} = \frac{1}{1 - j\frac{6}{\omega RC} - \frac{5}{\omega^2(RC)^2} + j\frac{1}{\omega^3(RC)^3}} = \frac{1}{\left(1 - \frac{5}{\omega^2(RC)^2}\right) + j\left(\frac{1}{\omega^3(RC)^3} - \frac{6}{\omega RC}\right)}$$



Phase Shift Feedback Network

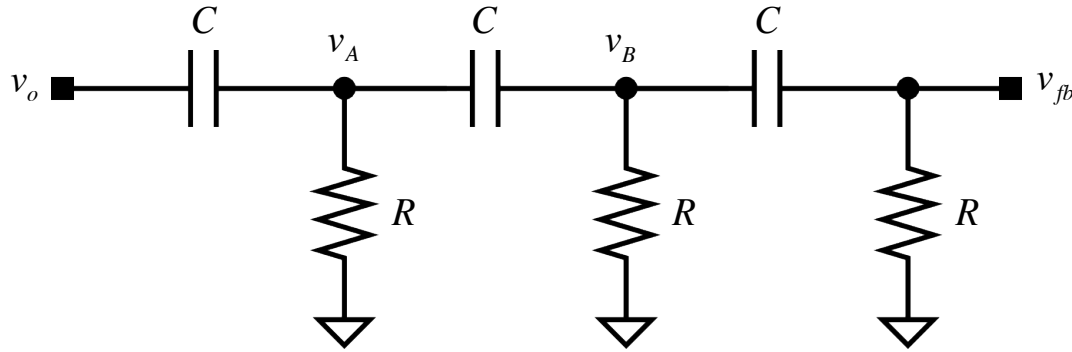

Need: $\angle f(s) = -180^\circ$


$$f(\omega) = \frac{v_{fb}}{v_o} = \frac{1}{\left(1 - \frac{5}{\omega^2 (RC)^2}\right) + j\left(\frac{1}{\omega^3 (RC)^3} - \frac{6}{\omega RC}\right)}$$

For frequency ω_0 , the phase shift of the feedback network will either be 0 or 180° depending on the sign of the real component

$$\frac{1}{\omega_0^3 (RC)^3} - \frac{6}{\omega_0 RC} = 0 \Rightarrow \frac{1}{\omega_0 RC} = \sqrt{6}$$



Phase Shift Feedback Network

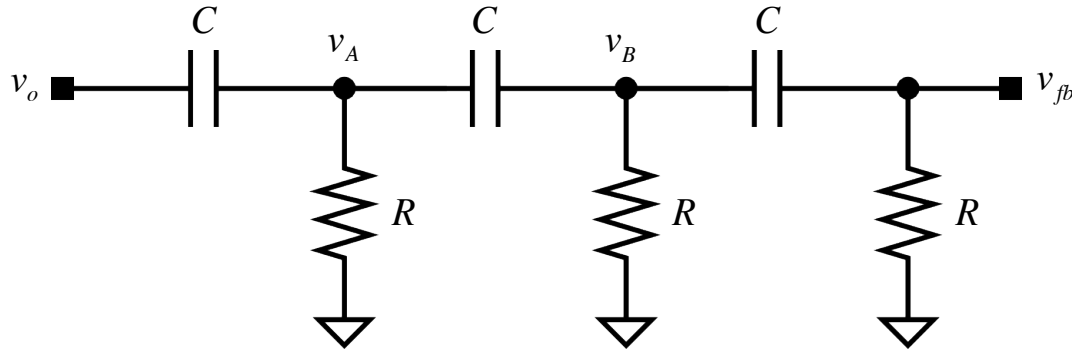

Need: $\angle f(s) = -180^\circ$

$$\frac{1}{\omega_0 RC} = \sqrt{6}$$

$$f(\omega) = \frac{v_{fb}}{v_o} = \frac{1}{\left(1 - \frac{5}{\omega^2 (RC)^2}\right) + j\left(\frac{1}{\omega^3 (RC)^3} - \frac{6}{\omega RC}\right)}$$


- Phase of the feedback network is 180°
- The oscillator can oscillate at frequency ω_0

$$f(\omega_0) = \frac{v_{fb}}{v_o} = \frac{1}{\left(1 - \frac{5}{\omega_0^2 (RC)^2}\right)} = \frac{1}{1 - 5(6)} = -\frac{1}{29}$$

$$\omega_0 = \frac{1}{\sqrt{6}(RC)}$$



Phase Shift Feedback Network

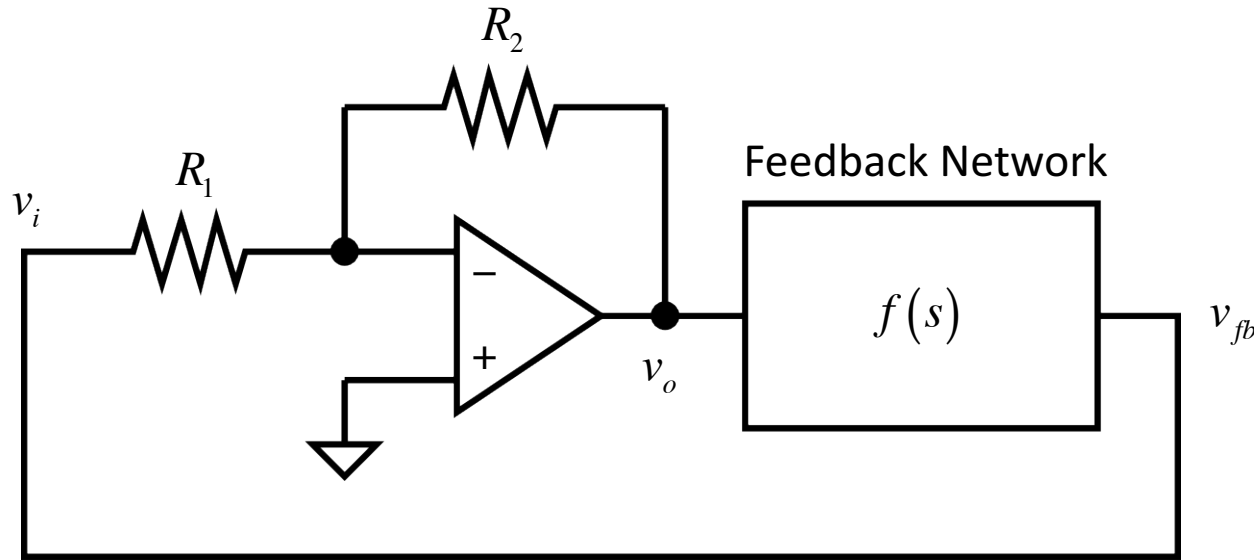

$$f(\omega_0) = -\frac{1}{29}$$

$$\omega_0 = \frac{1}{\sqrt{6}(RC)}$$

What is the required amplifier gain at ω_0 ?

$$T(\omega_0) = a(\omega_0) \cdot f(\omega_0) = -\frac{R_2}{R_1} \cdot \left(-\frac{1}{29}\right) = 1 \angle 0^\circ \quad \Rightarrow \quad \frac{R_2}{R_1} = 29 \quad \text{Or is it } \frac{R_2}{R_1} \geq 29?$$



Next Meeting

- Oscillators

