




EEE 51: Second Semester 2017 - 2018

Lecture 7


Current Mirrors

Today

- Current Mirrors

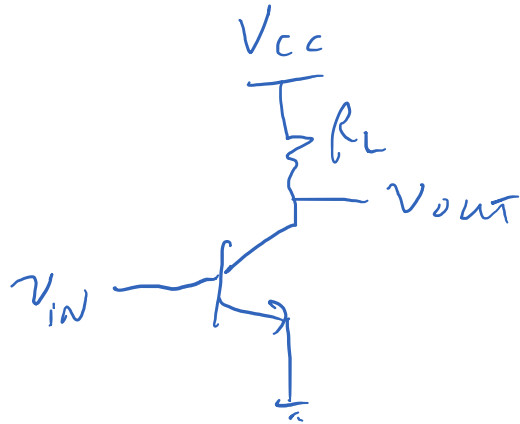

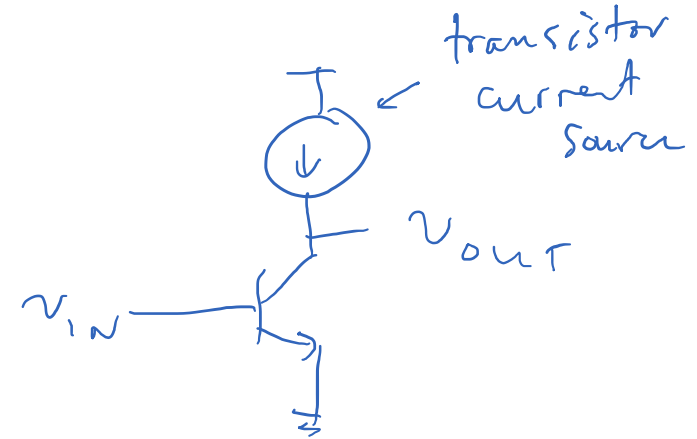
$$A_v = -g_m (r_o \parallel R_L)$$
$$\approx -g_m R_L$$



$$A_v = -g_m r_o$$




Practical Diode Characteristics

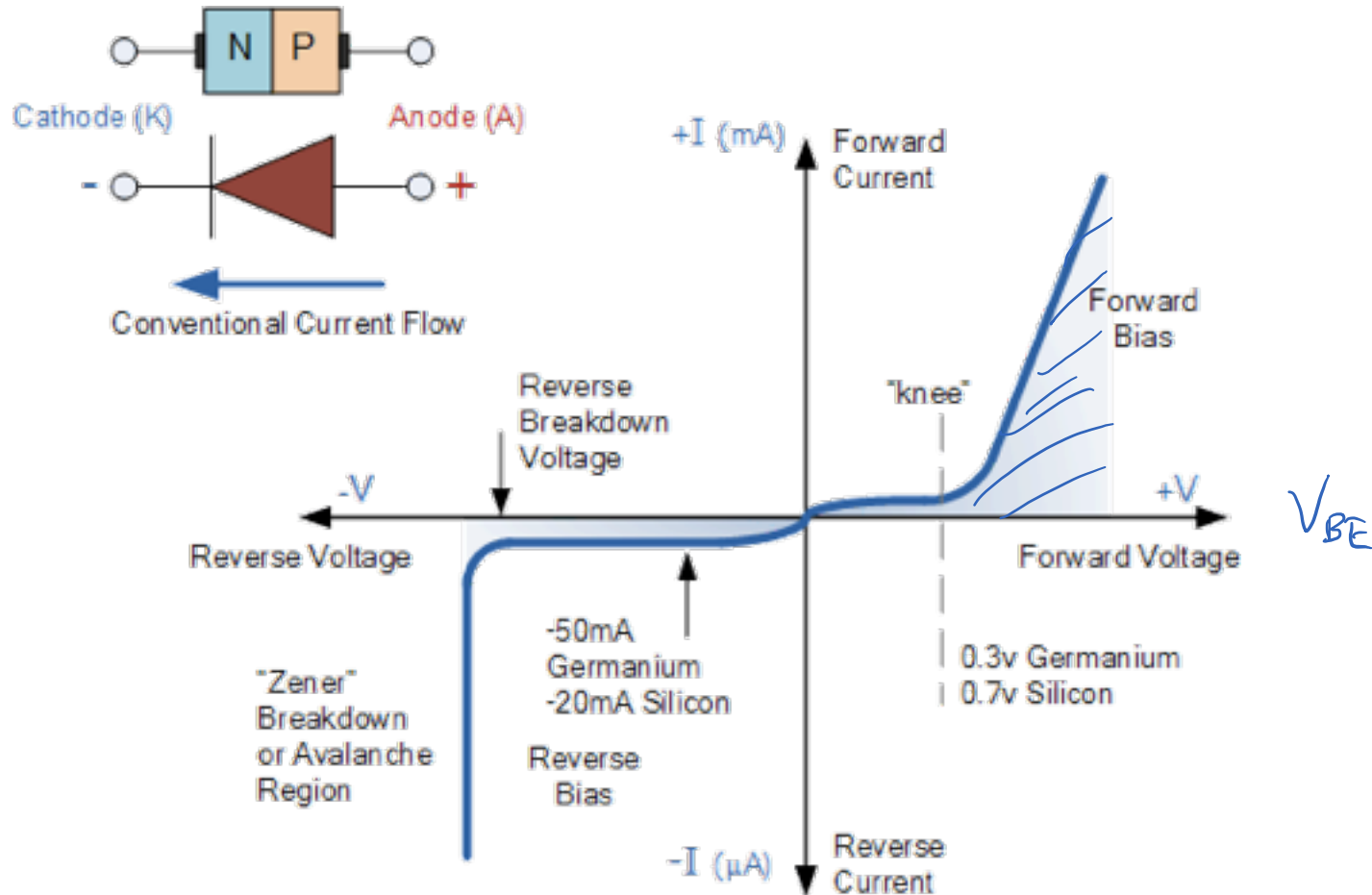

A Simple BJT Current Source

- Provide V_{BE} using a voltage divider

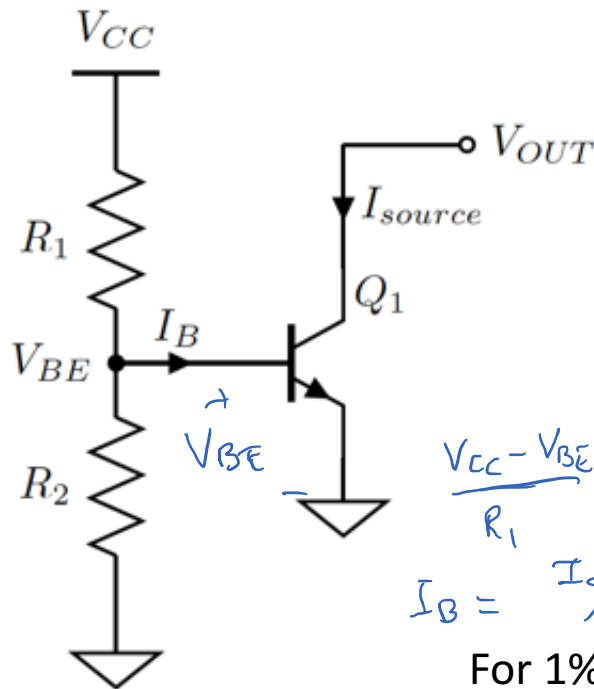Forward Active: V_{BE}/V_T
 $I_C \approx I_S e^{V_{BE}/V_T}$



Example: what if we need 1mA?

$$V_{BE} = V_T \ln \frac{I_C}{I_S} = V_T \ln \frac{1\text{mA}}{2 \times 10^{-16} \text{A}} = 0.7603\text{V}$$

Small changes in V_{BE} :

$$V_{BE} = 0.7703\text{V} \rightarrow I_C = 1.5\text{mA}$$

Also, for $V_{CC} = 5\text{V}$ and $\beta = 200$:


$$R_1 = 10\text{k}\Omega \rightarrow R_2 = 1.8146\text{k}\Omega$$

$$\text{For 1\% error in } I_C, \Delta V_{BE} = 260\mu\text{V} \rightarrow \beta = 200 \pm 9$$



A Simple BJT Current Source

- Provide V_{BE} using a voltage divider

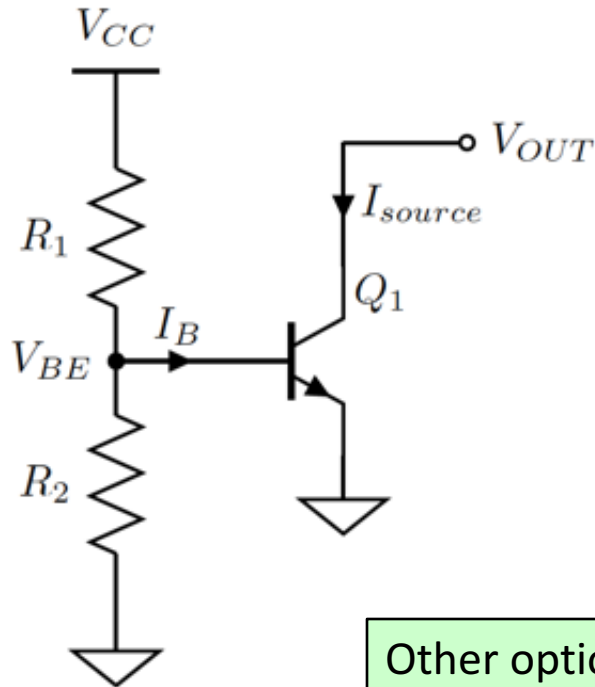

Main issues:


1. Need very precise resistor values
2. Need good β control

Expensive
(if possible at all)

Other options in generating V_{BE} ?



The Diode-Connected Transistor (1)

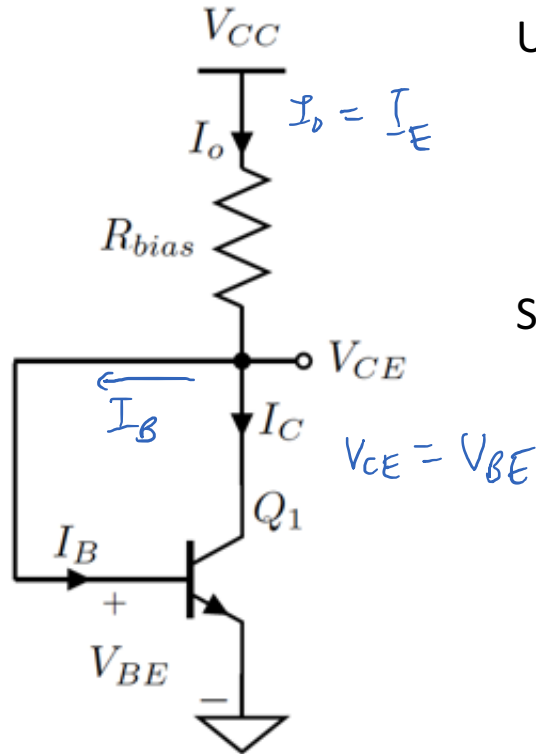

Use R_{bias} to apply a current I_o into the BJT:

$$I_o = I_C + I_B = I_C \cdot \left(1 + \frac{1}{\beta}\right) \rightarrow$$

$$I_C = \frac{I_o}{\left(1 + \frac{1}{\beta}\right)}$$

$$I_C \approx I_S e^{V_{BE}/V_T}$$


Solving for $V_{CE} = V_{BE}$ (assuming $V_A \rightarrow \infty$):

$$V_{BE} = V_T \ln\left(\frac{I_C}{I_S}\right) = V_T \ln\left(\frac{I_o}{I_S} \cdot \frac{\beta}{\beta + 1}\right)$$

How do we generate I_o ?



The Diode-Connected Transistor (2)

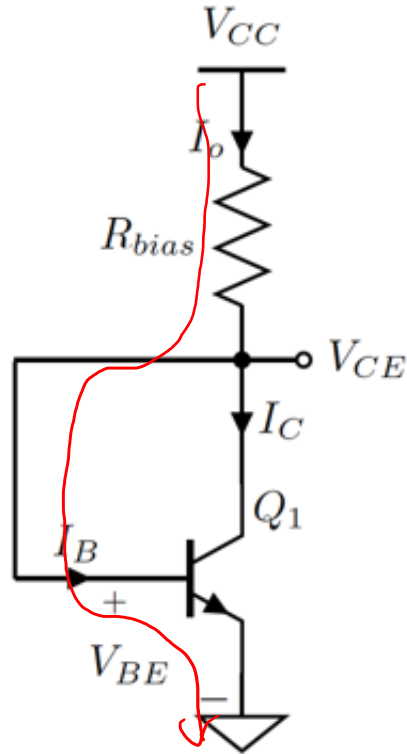

KVL at base loop:

$$V_{CC} - I_o R_{bias} - V_{BE} = 0$$


Thus,

$$R_{bias} = \frac{V_{CC} - V_{BE}}{I_o} = \frac{V_{CC} - V_{BE}}{I_S \cdot e^{\frac{V_{BE}}{V_T}} \cdot \left(1 + \frac{1}{\beta}\right)}$$

We can pick a resistor to generate V_{BE}



A Simple BJT Current Mirror (1)

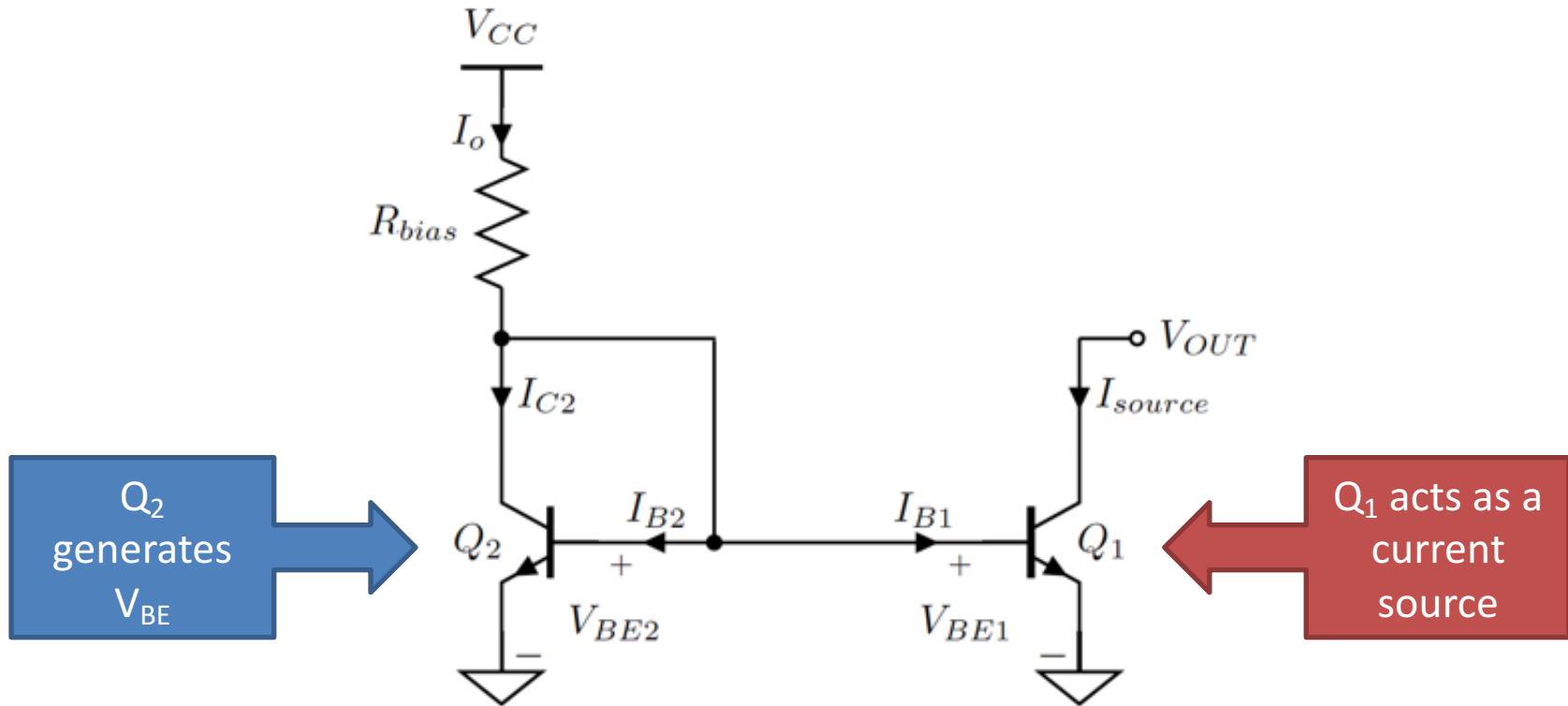

A Simple BJT Current Mirror (2)

$$I_C = I_S e^{V_{BE}/V_T} \left(1 + \frac{V_{CE}}{V_A}\right)$$

* Q_1 & Q_2 must be matched

- $I_{S1} = I_{S2}$, $\beta_1 = \beta_2$,
 $V_{T1} = V_{T2}$, $V_{A1} = V_{A2}$


Basic idea:

$$V_{BE1} = V_{BE2}$$

$$V_{T1} \ln \left(\frac{I_{C1}}{I_{S1} \left(1 + \frac{V_{CE1}}{V_{A1}}\right)} \right) = V_{T2} \ln \left(\frac{I_{C2}}{I_{S2} \left(1 + \frac{V_{CE2}}{V_{A2}}\right)} \right)$$

Recall: $V_{BE} = V_T \ln \left(\frac{I_C}{I_S \left(1 + \frac{V_{CE}}{V_A}\right)} \right)$

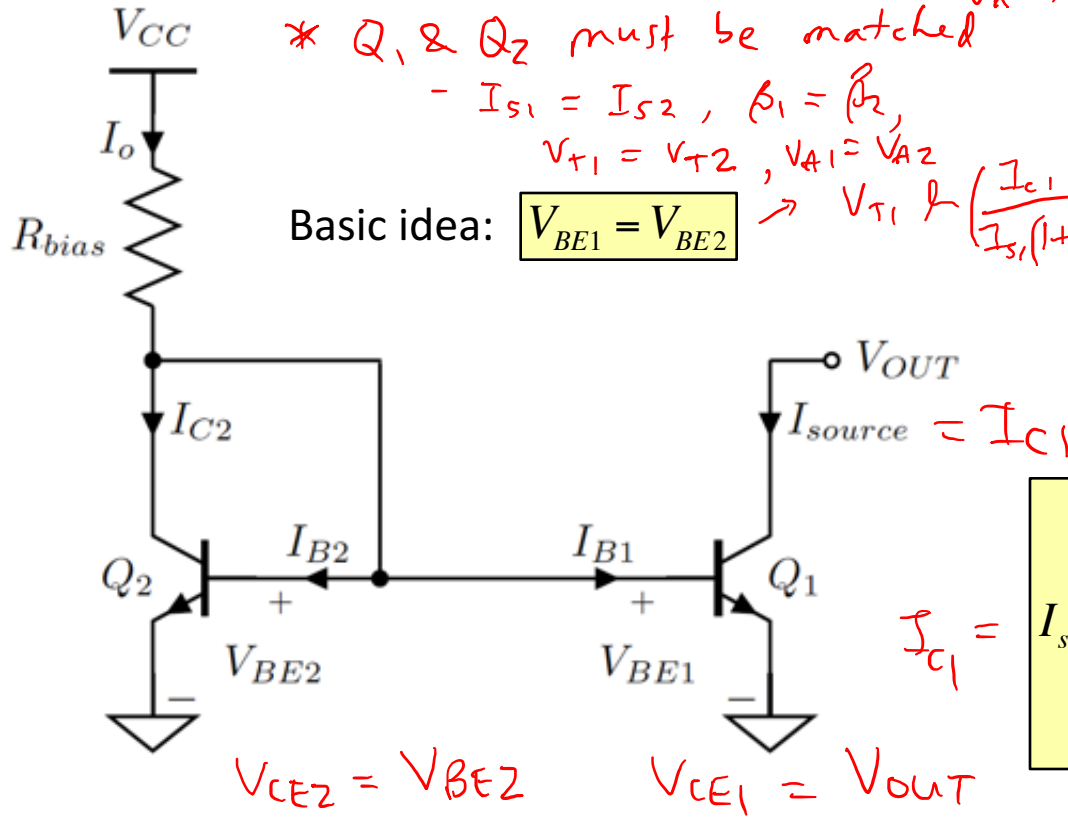
$$\frac{I_{C1}}{\left(1 + \frac{V_{CE1}}{V_A}\right)} = \frac{I_{C2}}{\left(1 + \frac{V_{CE2}}{V_A}\right)}$$



$$I_{source} = I_{C2} \frac{\left(1 + \frac{V_{CE1}}{V_A}\right)}{\left(1 + \frac{V_{CE2}}{V_A}\right)} = I_{C2} \frac{V_A + V_{OUT}}{V_A + V_{BE}}$$



A Simple BJT Current Mirror (3)

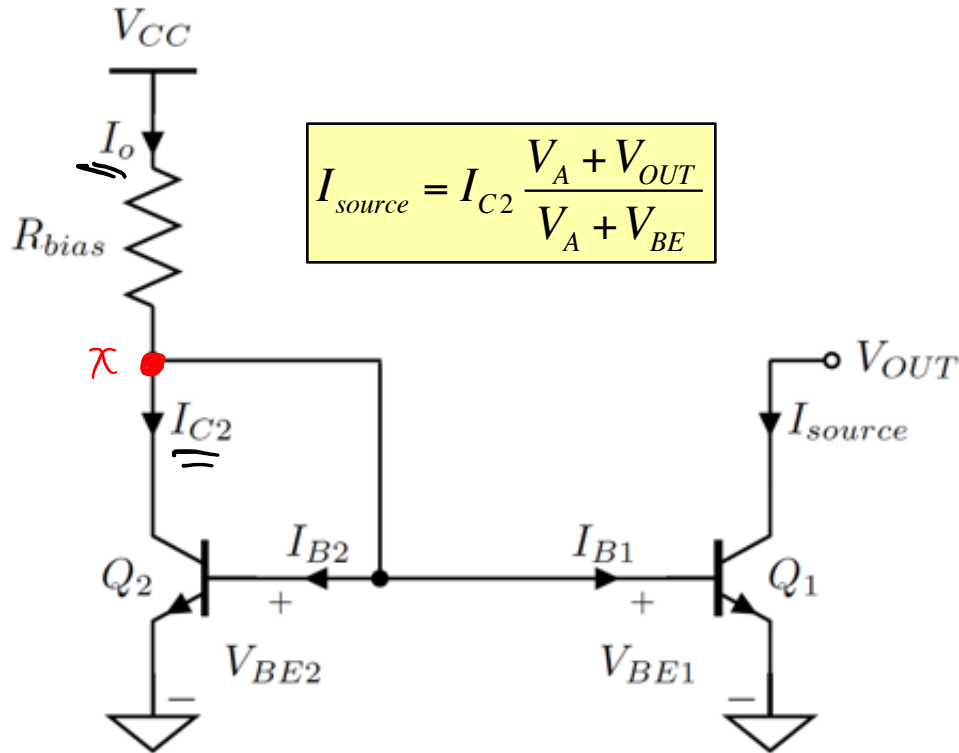


KCL at x:

$$\begin{aligned}
 \rightarrow I_{C2} &= I_o - I_{B1} - I_{B2} = I_o - \frac{I_{source}}{\beta} - \frac{I_{C2}}{\beta} \\
 &= \frac{\beta}{\beta+1} I_o - \frac{I_{source}}{\beta+1}
 \end{aligned}$$

$$I_{source} = I_o \frac{\frac{\beta}{\beta+1} \cdot \frac{V_A + V_{OUT}}{V_A + V_{BE}}}{1 + \frac{1}{\beta+1} \cdot \frac{V_A + V_{OUT}}{V_A + V_{BE}}}$$



A Simple BJT Current Mirror (4)

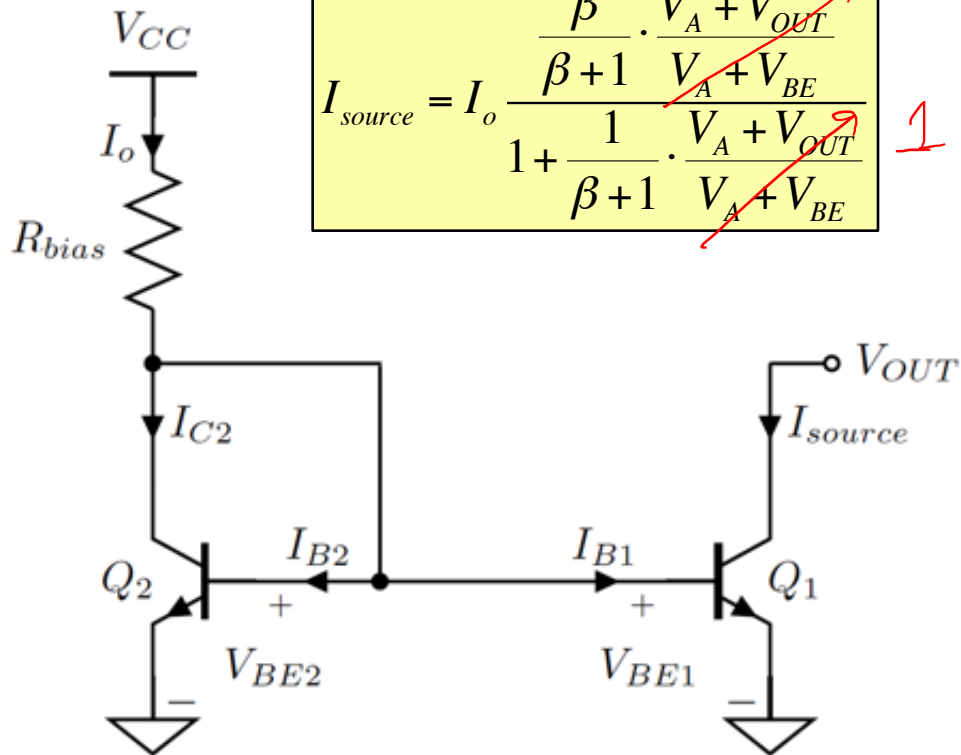

Assume $V_A \rightarrow \infty$

$$I_{source} \approx I_o \frac{\frac{\beta}{\beta+1}}{1 + \frac{1}{\beta+1}} = \frac{I_o}{1 + \frac{2}{\beta}}$$

Assume $V_A \rightarrow \infty$ and $\beta \rightarrow \infty$

$$I_{source} \approx I_o$$


Mirror!

Mirroring Error:

1. Due to the base currents
2. Due to V_{CE} "mismatch"



A Simple BJT Current Mirror (4)

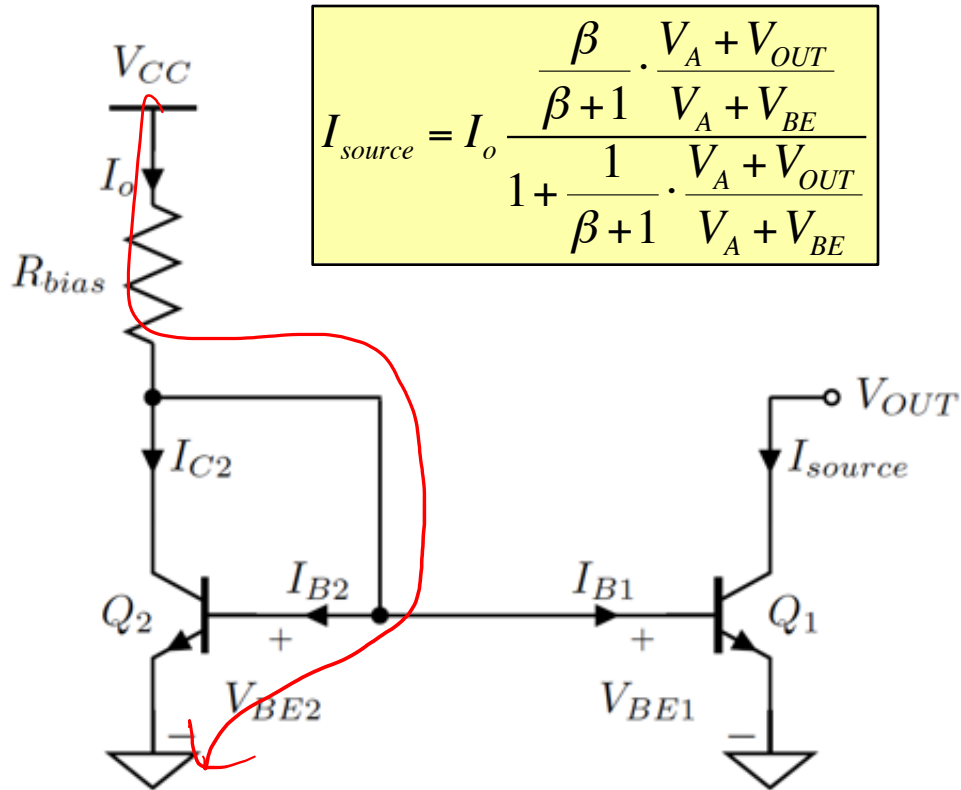

$$I_{source} = I_o \frac{\frac{\beta}{\beta+1} \cdot \frac{V_A + V_{OUT}}{V_A + V_{BE}}}{1 + \frac{1}{\beta+1} \cdot \frac{V_A + V_{OUT}}{V_A + V_{BE}}}$$


What about R_{bias} ?

$$R_{bias} = \frac{V_{CC} - V_{BE}}{I_o}$$

R is linearly
related to I_o and I_{source}
(not exponentially!)



A Simple BJT Current Mirror (5)

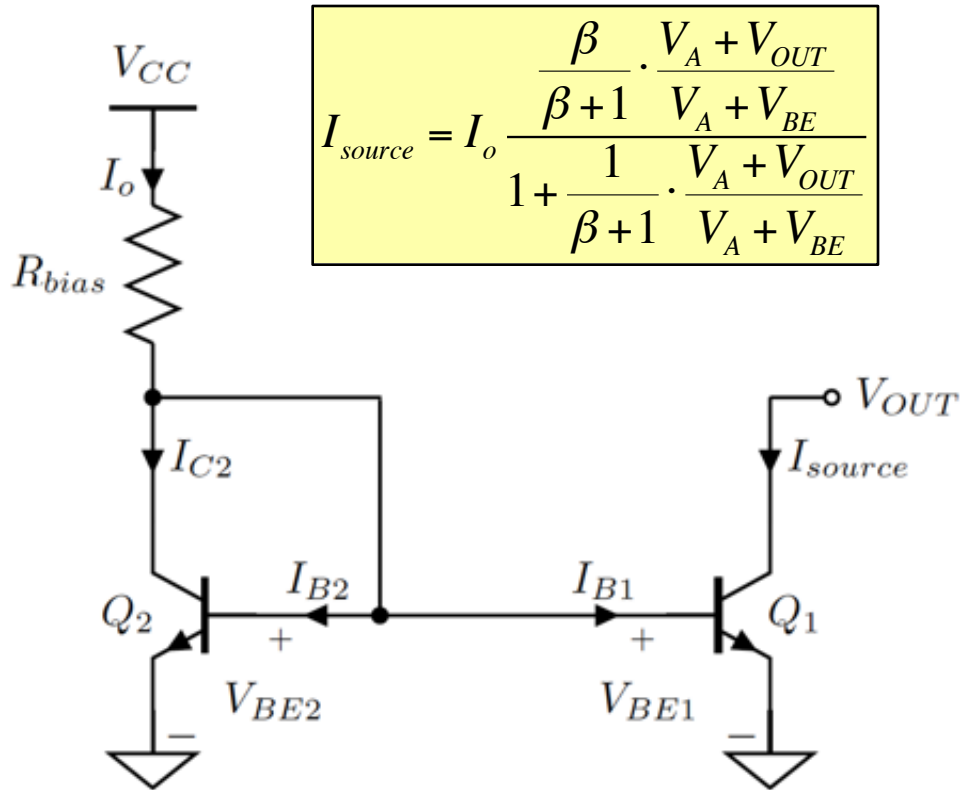

$$I_{source} = I_o \frac{\frac{\beta}{\beta+1} \cdot \frac{V_A + V_{OUT}}{V_A + V_{BE}}}{1 + \frac{1}{\beta+1} \cdot \frac{V_A + V_{OUT}}{V_A + V_{BE}}}$$

Assume $V_A \rightarrow \infty$




$$I_{source} \approx \frac{I_o}{1 + \frac{2}{\beta}}$$

Again, what if we need 1mA?

- We can tolerate β as low as 99 and still get only 1% error!



OUTPUT SWING

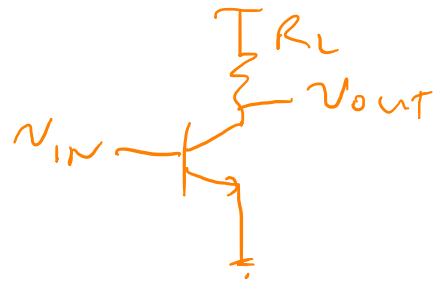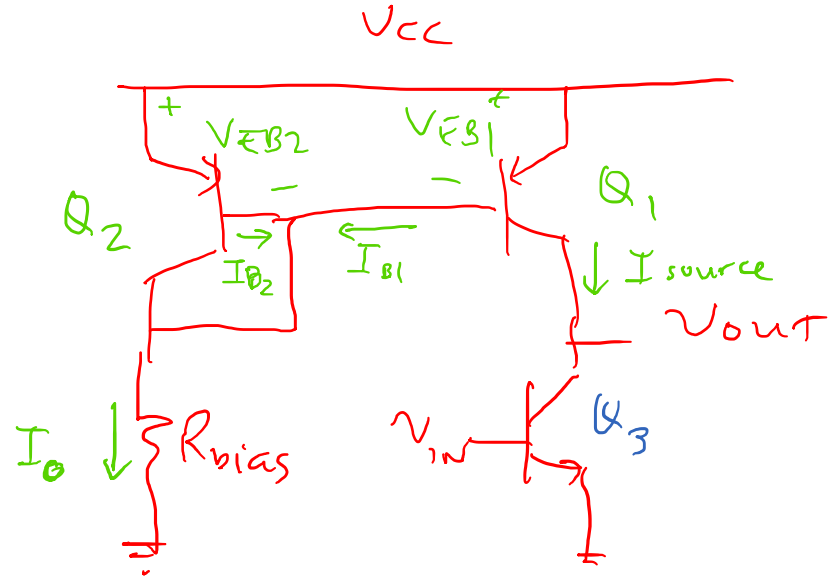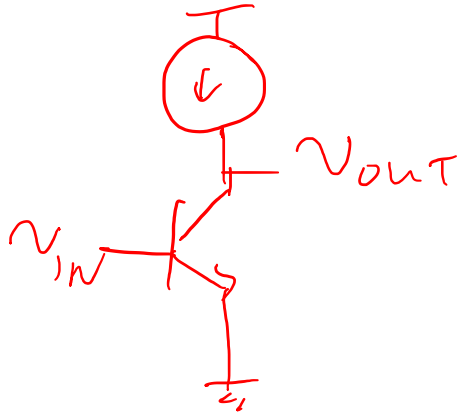


$$V_{OUT, \min} = V_{CE, SAT}$$

$$V_{OUT, \max} = V_{CC}$$

$$V_{OUT, \min} = V_{CE, SAT3}$$



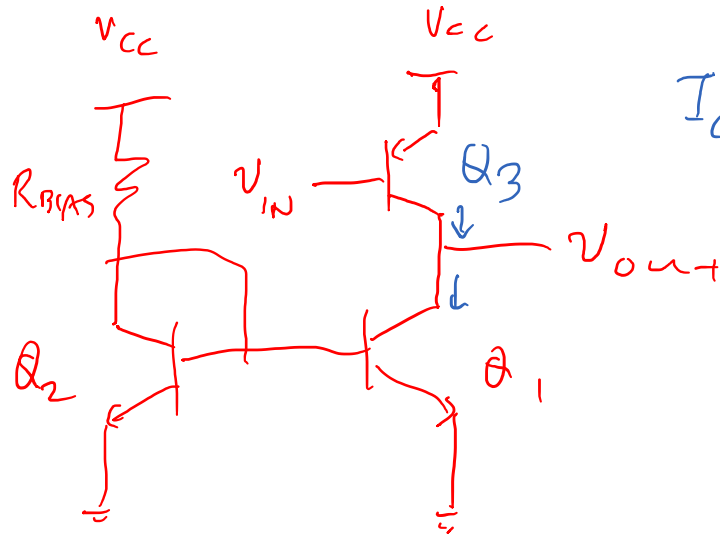
$$V_{OUT, \max} = V_{CC} - V_{EB, SAT1}$$





PNP CE w/ NPN single
current mirror

NPN CE w/ PNP simple CM
 V_{CC}

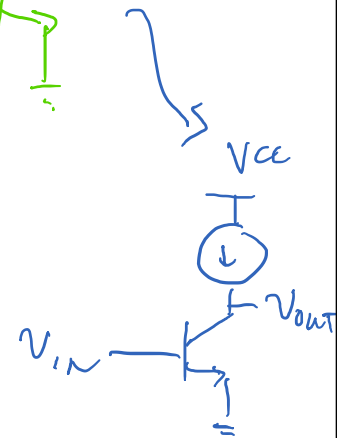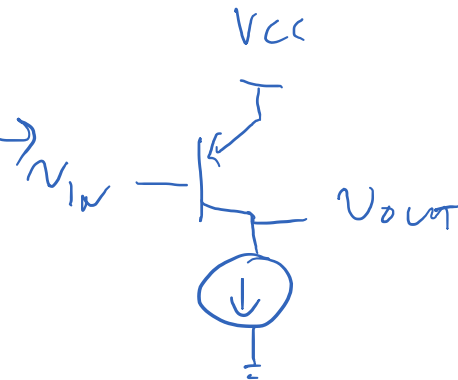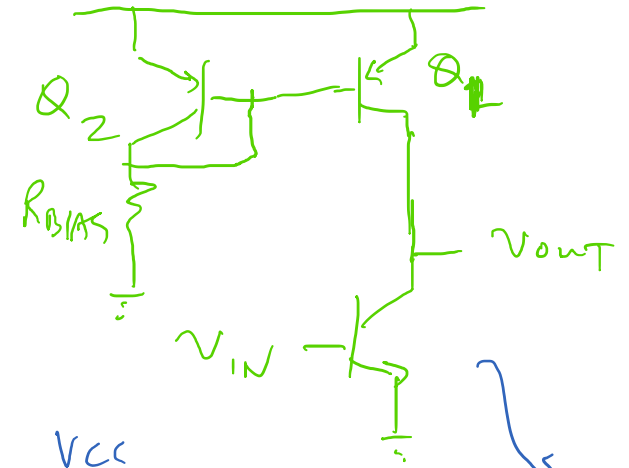

Next Meeting

- Biasing Amplifiers Using Current Sources
- Differential Circuits

