



# **EEE 51: Second Semester 2017 - 2018**

## **Lecture 6**

# Single-Stage Amplifiers

# Current Sources


# Today

- Wrap up single-stage amplifiers
- Current Sources



# The Common-Collector Amplifier

- DC Analysis:

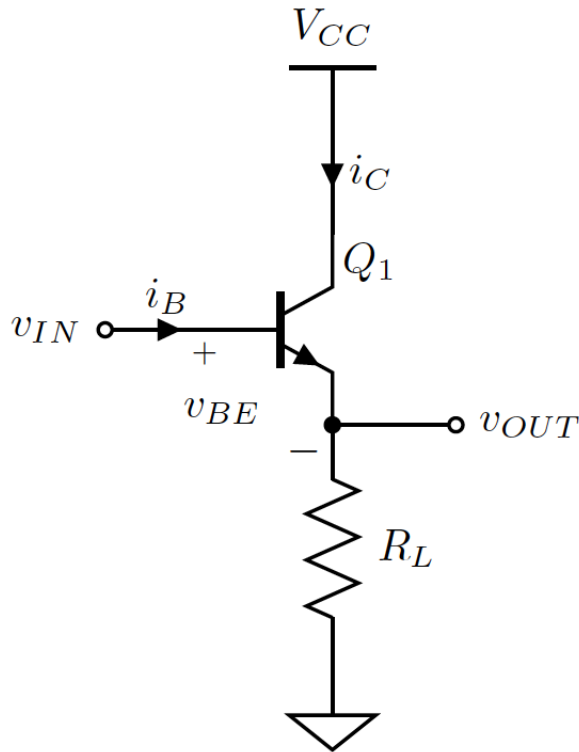

$$V_{IN} - V_{BE,Q} - I_{E,Q} R_L = 0$$
$$V_{IN} - V_T \ln\left(\frac{I_{C,Q}}{I_S}\right) - I_{C,Q} \left(1 + \frac{1}{\beta}\right) R_L = 0$$

Non-linear!

Simplify?  $V_{BE,Q} = 0.7\text{V}$

$$I_{C,Q} = \frac{V_{IN} - 0.7\text{V}}{\left(1 + \frac{1}{\beta}\right) R_L} \approx \frac{V_{IN} - 0.7\text{V}}{R_L}$$

$$V_{OUT} = I_{E,Q} R_L \approx I_{C,Q} R_L = V_{IN} - 0.7\text{V}$$




Emitter follower

Forward-active region check:  $V_{CE} = V_{CC} - V_{OUT} > V_{CE,sat}$




# Common-Collector Small Signal Analysis (1)

$$G_m = \frac{i_{out}}{v_{in}}$$

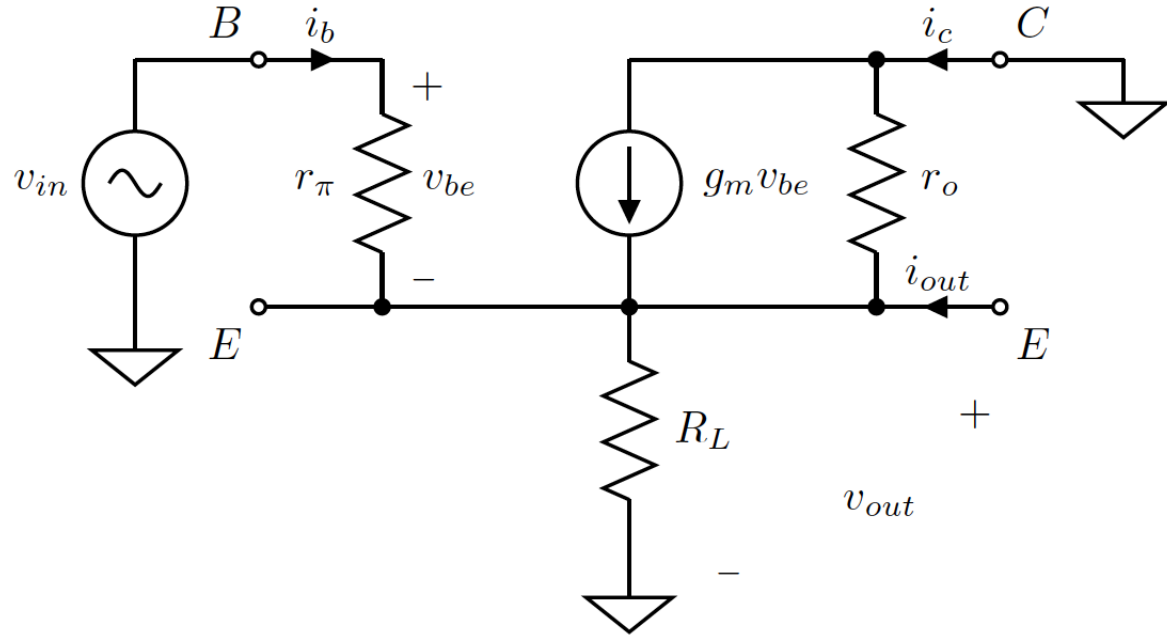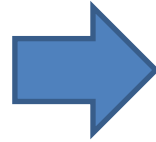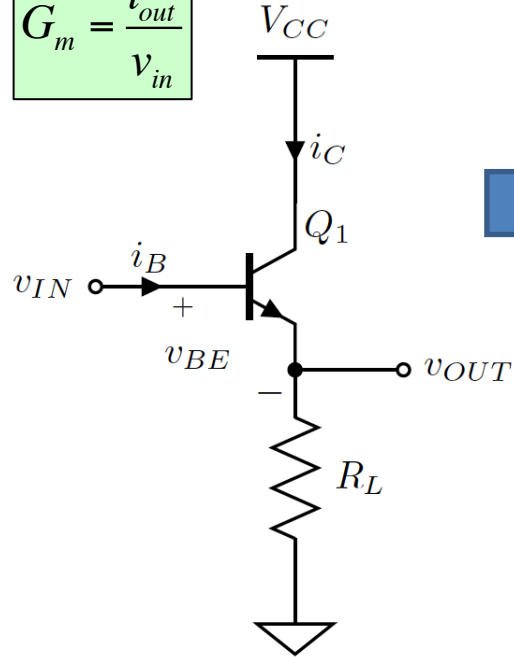


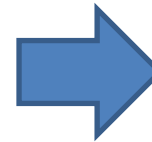Short the output to ground:  $i_{out} = -g_m v_{in} - \frac{v_{in}}{r_{\pi}}$



$$G_m = \frac{i_{out}}{v_{in}} = -g_m - \frac{1}{r_{\pi}} \approx -g_m$$

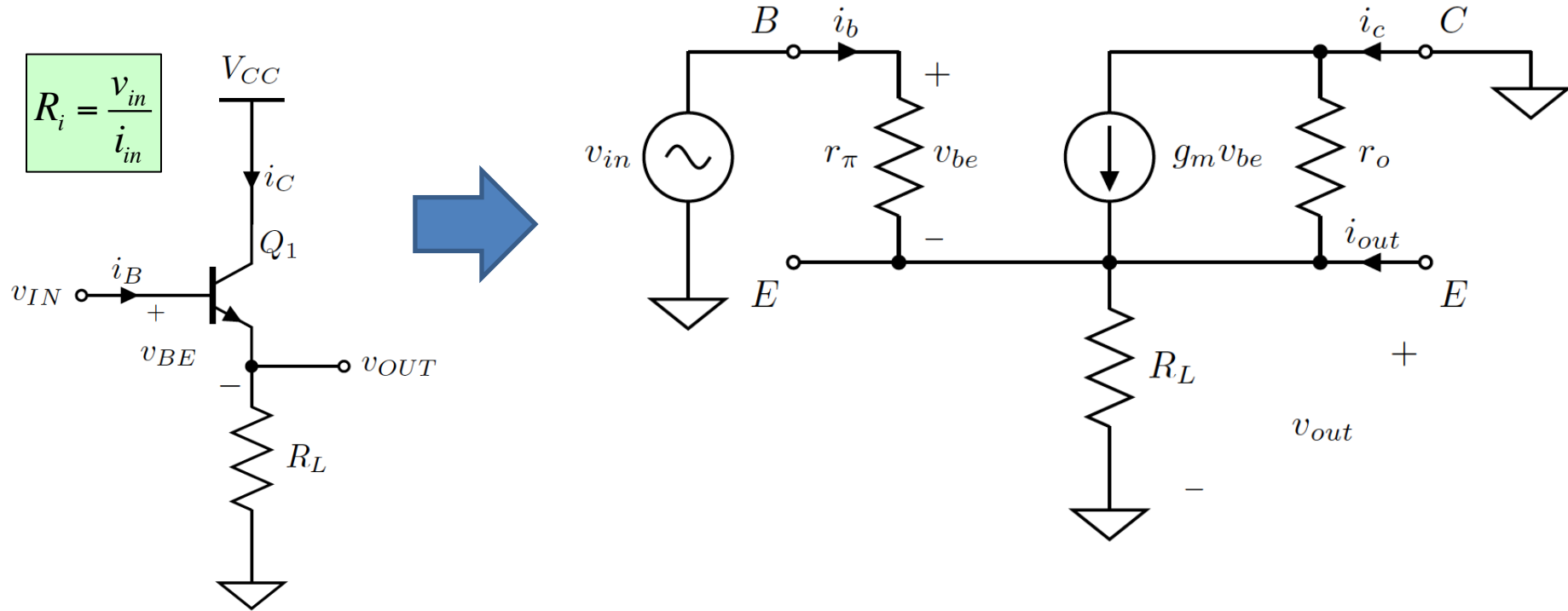
# Common-Collector Small Signal Analysis (2)




Short the output to ground:

$$R_i = r_\pi$$
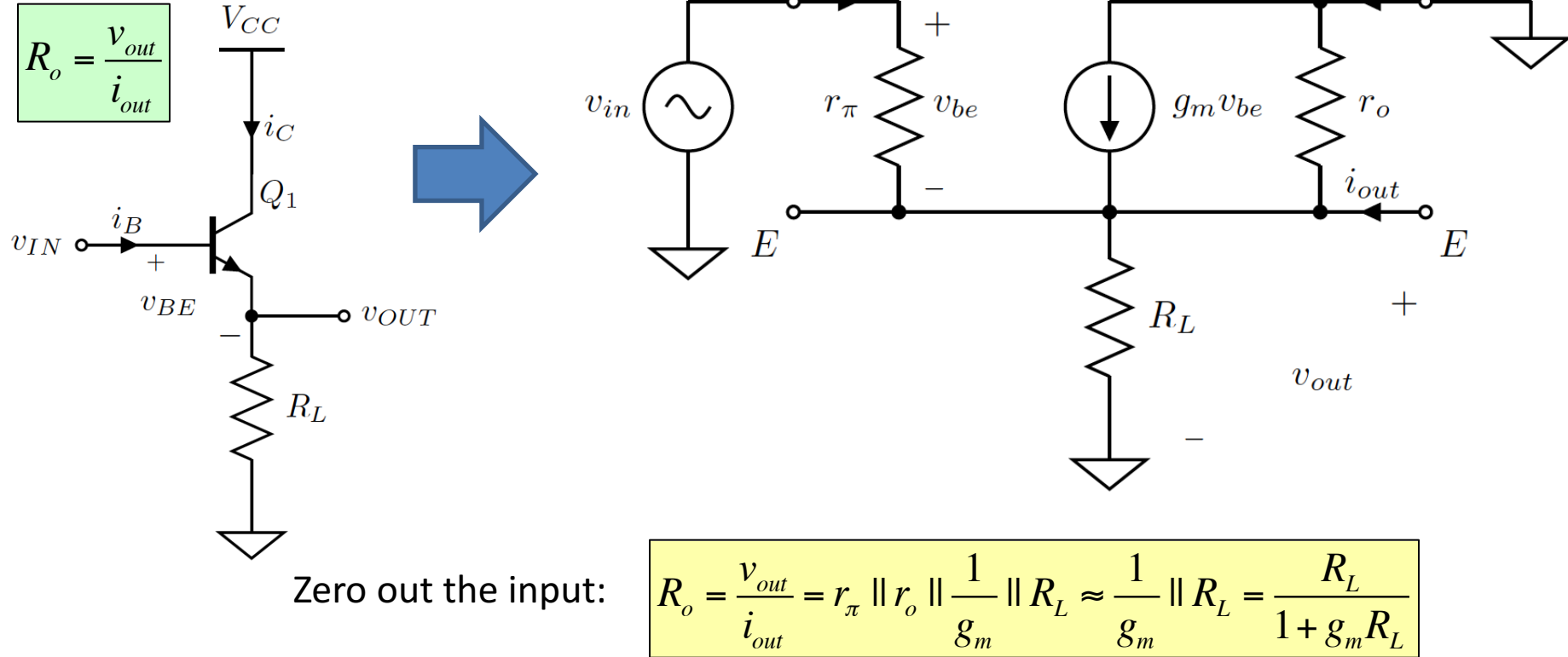
# Common-Collector Small Signal Analysis (3)



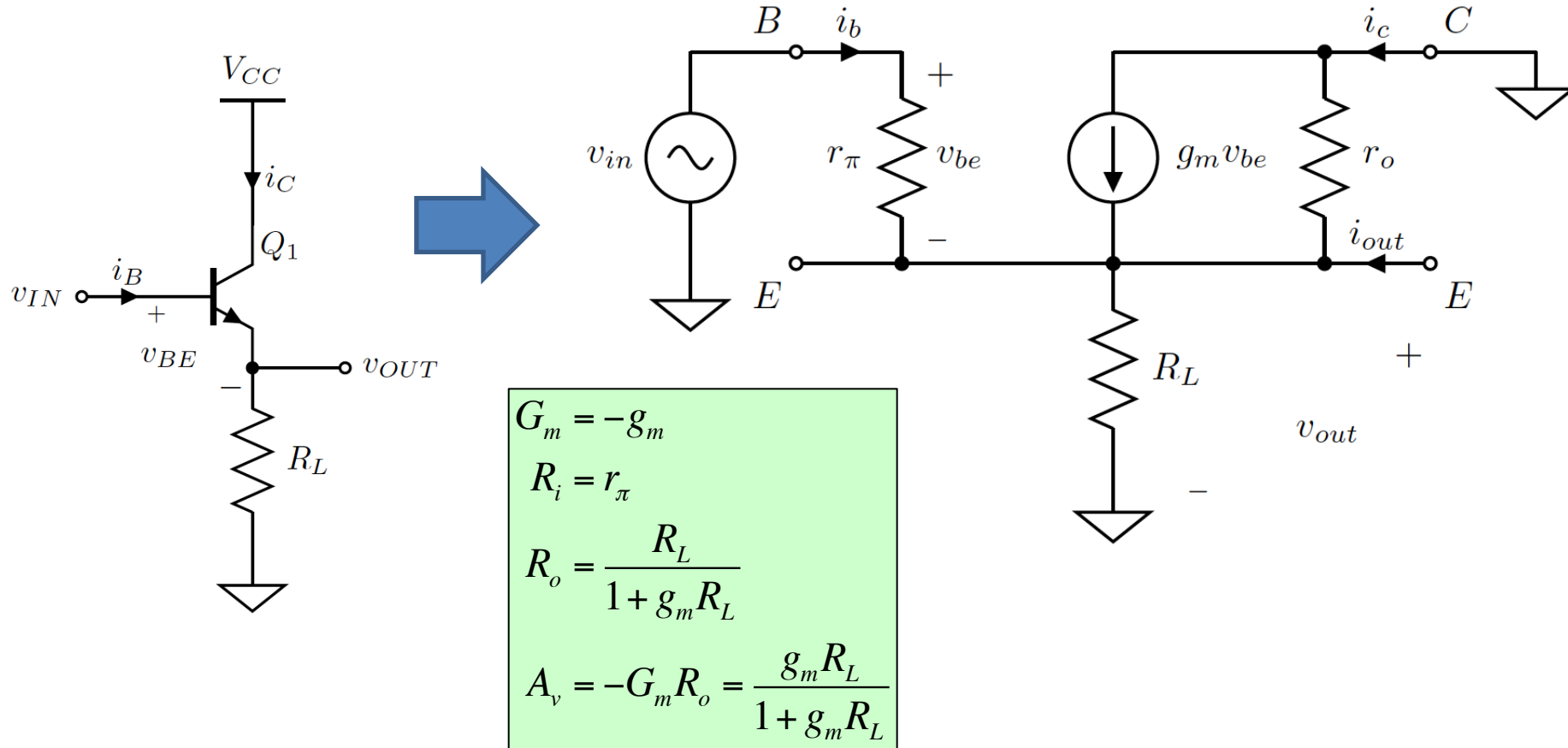
# Common-Collector Small Signal Analysis (4)



# The Common-Drain Amplifier

- DC Analysis:

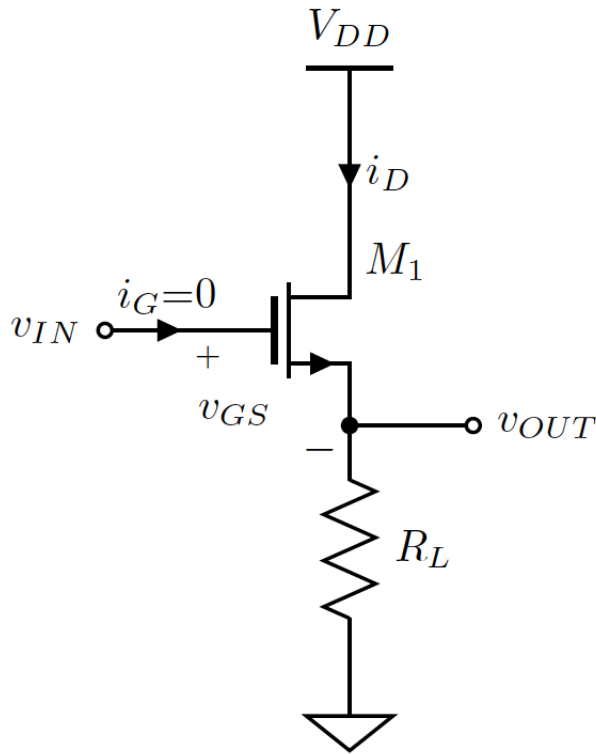

$$V_{IN} - V_{GS,Q} - I_{S,Q}R_L = 0$$

$$V_{IN} - \left( V_{TH} + \sqrt{\frac{I_{D,Q}}{k}} \right) - I_{D,Q}R_L = 0$$

Quadratic

$$V_{OUT} = I_{D,Q}R_L = V_{IN} - V_{GS}$$

$$= V_{IN} - \left( V_{TH} + \sqrt{\frac{I_{D,Q}}{k}} \right)$$

Source follower

Saturation region check:


$$V_{DS} = V_{DD} - V_{OUT} > V_{GS} - V_{TH} = V_{IN} - V_{OUT} - V_{TH}$$

$$V_{DD} > V_{IN} - V_{TH}$$





# Common-Drain Small Signal Model

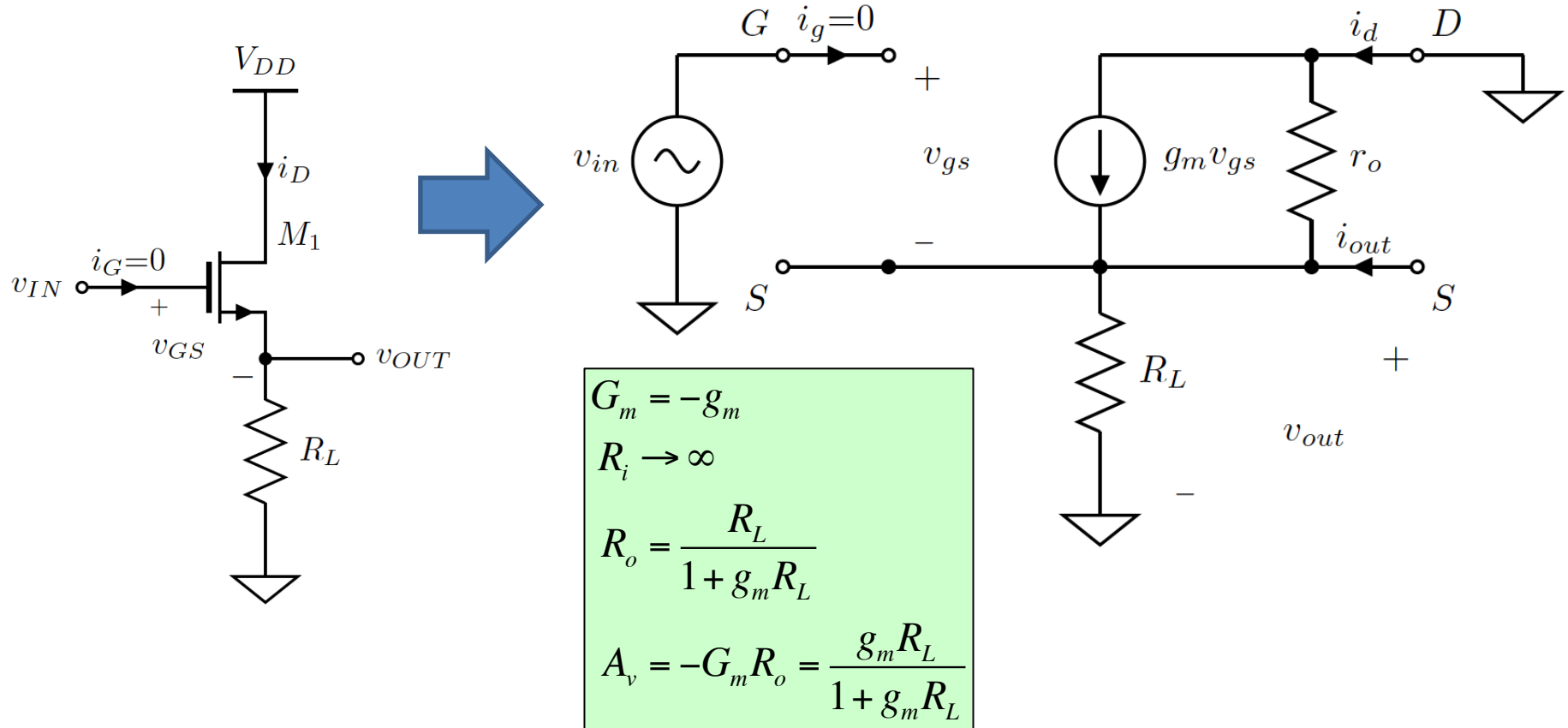

# Single-Stage Amplifiers


	CE/CS	CB/CG	CC/CD
$G_m$	$g_m$	$-g_m$	$-g_m$
$R_o$	$r_o \parallel R_L$	$r_o \parallel R_L$	$\frac{R_L}{1 + g_m R_L}$
$R_i$	$r_\pi$	$\frac{1}{g_m}$	$r_\pi$
$A_v$	$-g_m (r_o \parallel R_L)$	$g_m (r_o \parallel R_L)$	$\frac{g_m R_L}{1 + g_m R_L}$

Can we use this diverse set of characteristics to create better amplifiers?



# Input Resistance Revisited (1)

- Common-Base/Common-Gate Amplifier

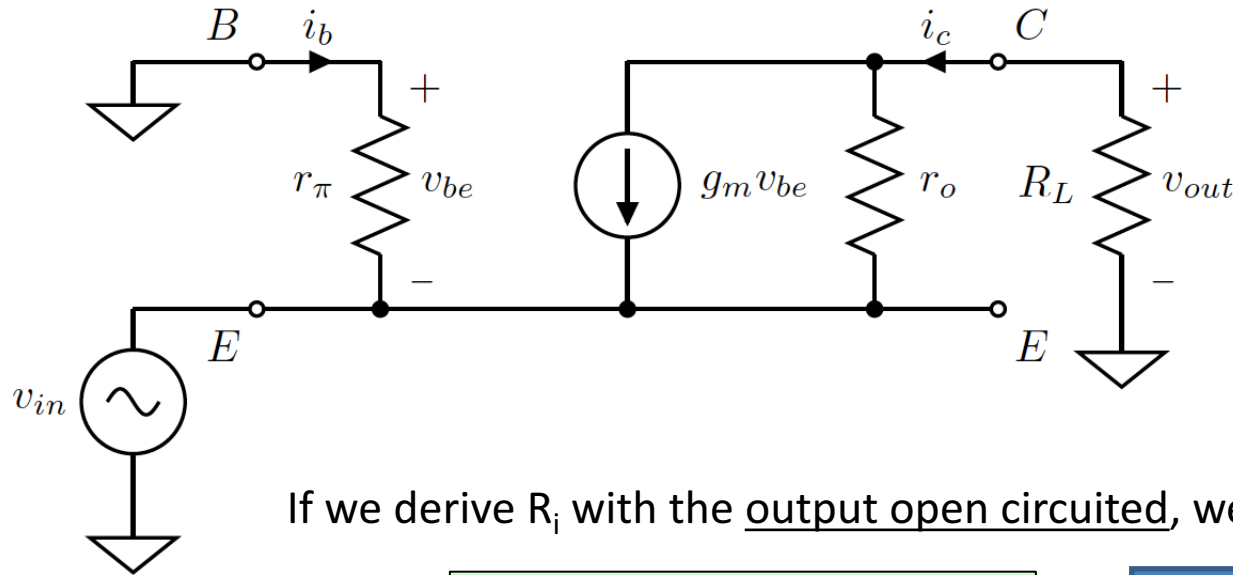

$$R_i = r_\pi \parallel r_o \parallel \frac{1}{g_m} \approx \frac{1}{g_m}$$

Derived assuming  
no-load conditions


If we derive  $R_i$  with the output open circuited, we get:

$$R_i = r_\pi \parallel \frac{1}{g_m} + \frac{R_L}{g_m r_o} \approx \frac{1}{g_m} + \frac{R_L}{g_m r_o}$$

Dependent on  $R_L$ !
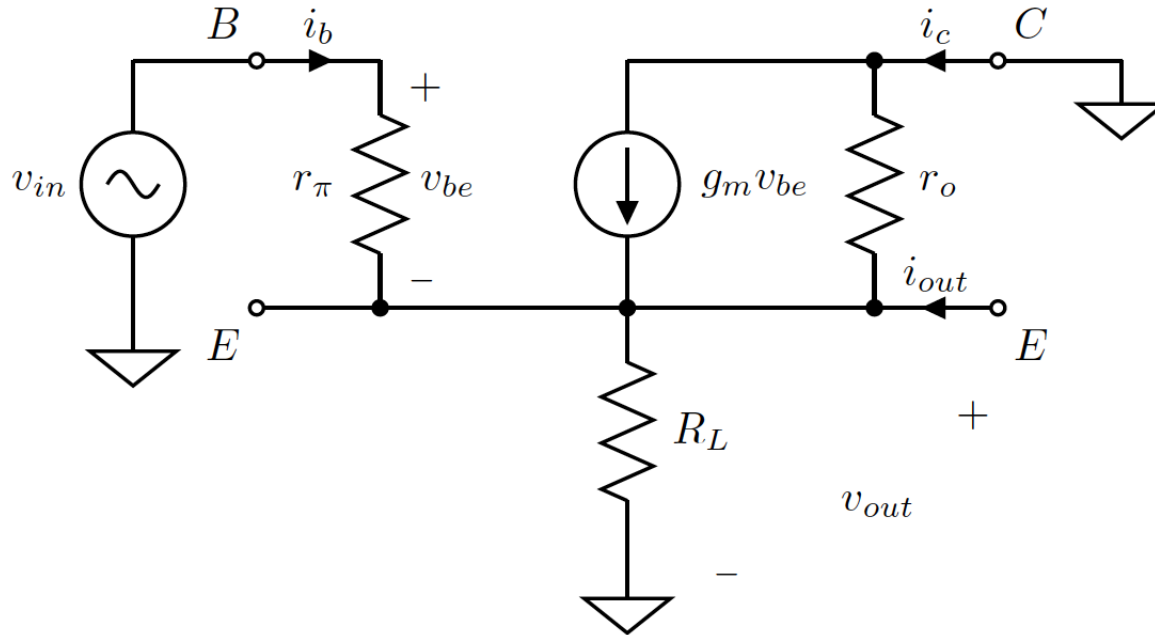
# Input Resistance Revisited (1)

- Common-Collector/Common-Drain Amplifier



$$R_i = r_\pi$$

Derived assuming  
no-load conditions

If we derive  $R_i$  with the  
output open circuited, we get:



$$R_i \approx r_\pi (1 + g_m R_L)$$

Dependent on  $R_L$ !



# Bilateral Behavior

- CB/CG and CC/CD

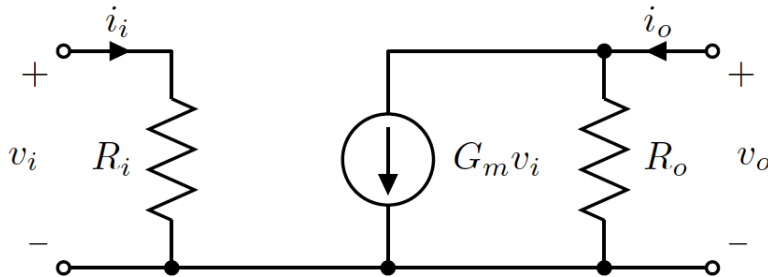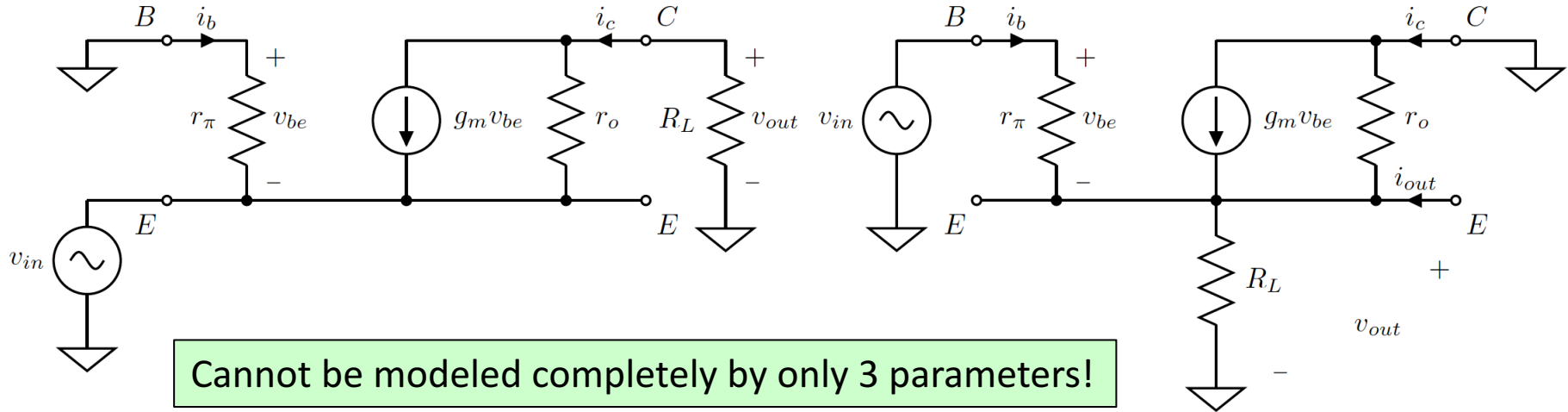


Model results in output  
condition dependent  $R_i$



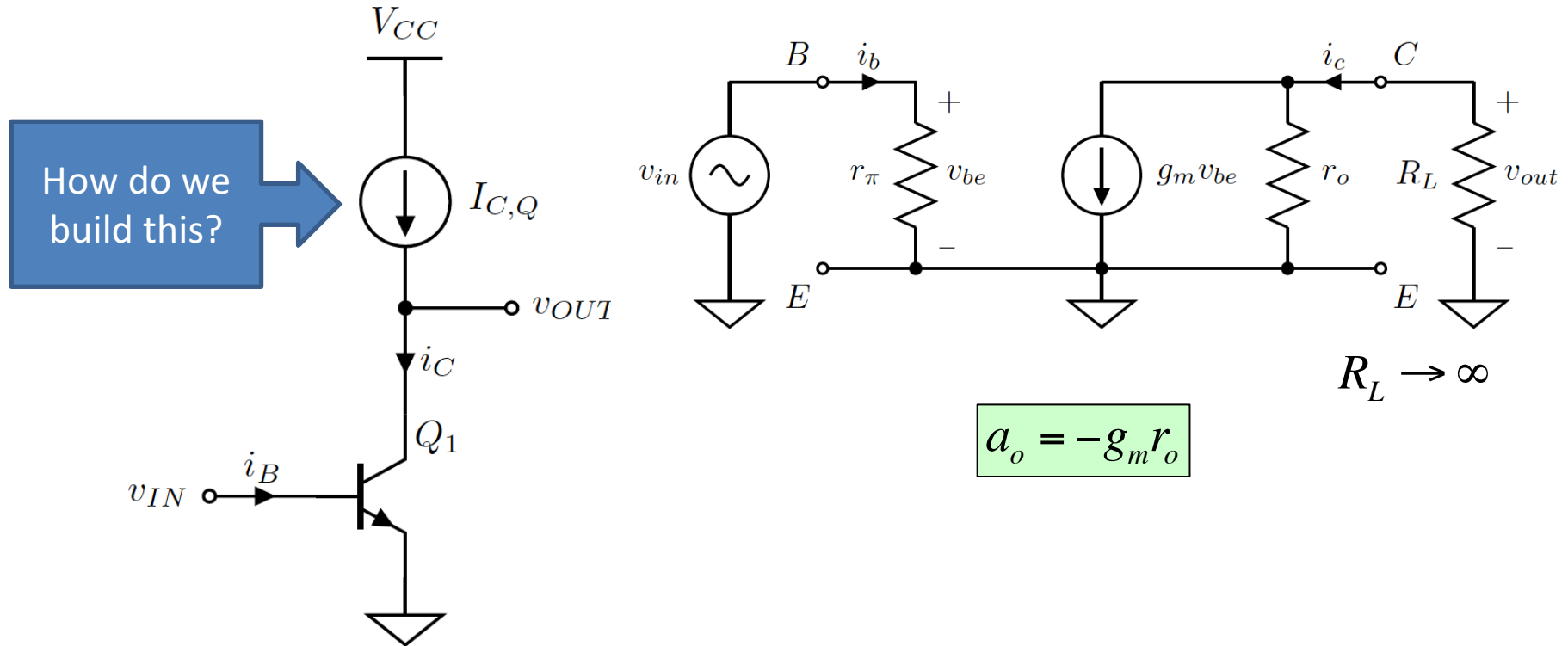
# Current Sources

- Recall: When can we achieve a gain close to  $a_o$ ?



# What Are Current Sources?

- Practical Current Sources

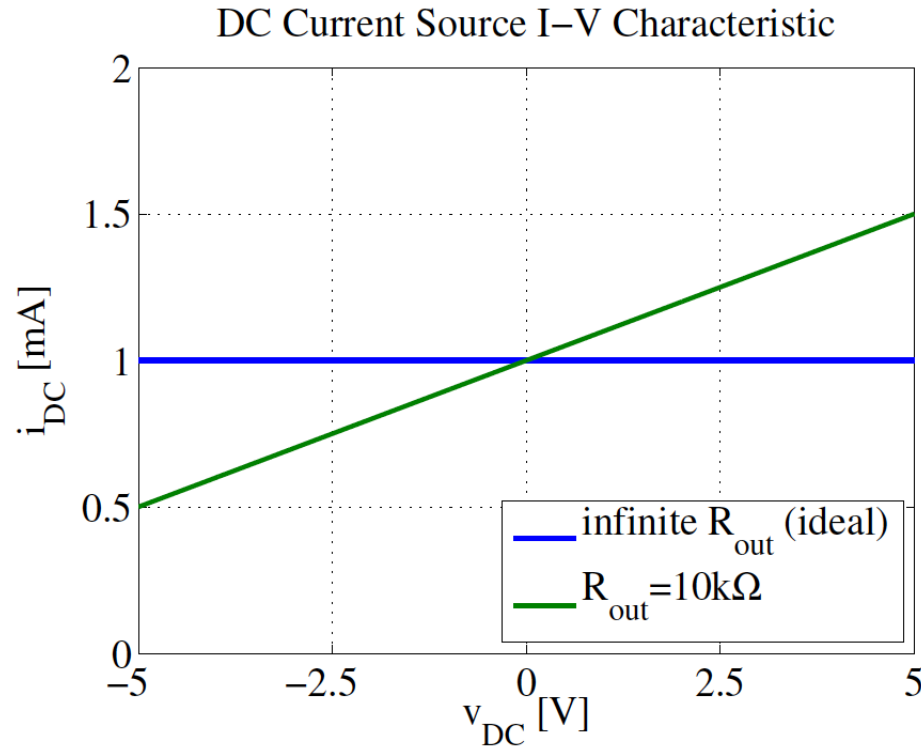

We can't really make a perfect current source (yet)...



But we can get very close

## Current source metrics?

1. Output resistance
2. Minimum output voltage


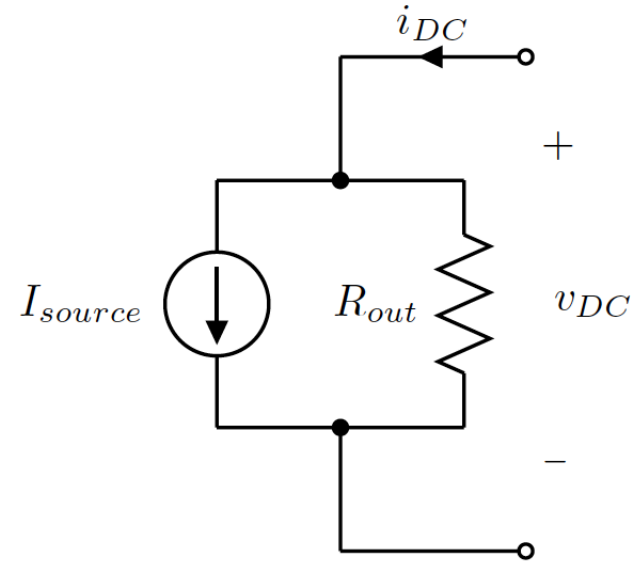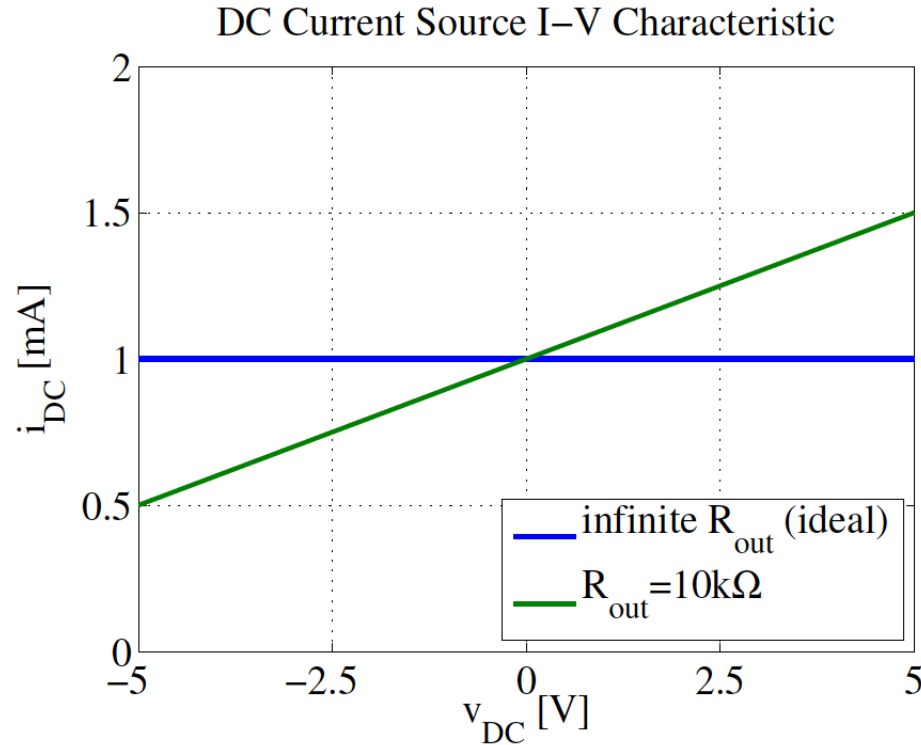
# Current Source Output Resistance, $R_{out}$




$$i_{DC} = I_{source} + \frac{v_{DC}}{R_{out}}$$


Voltage dependent!


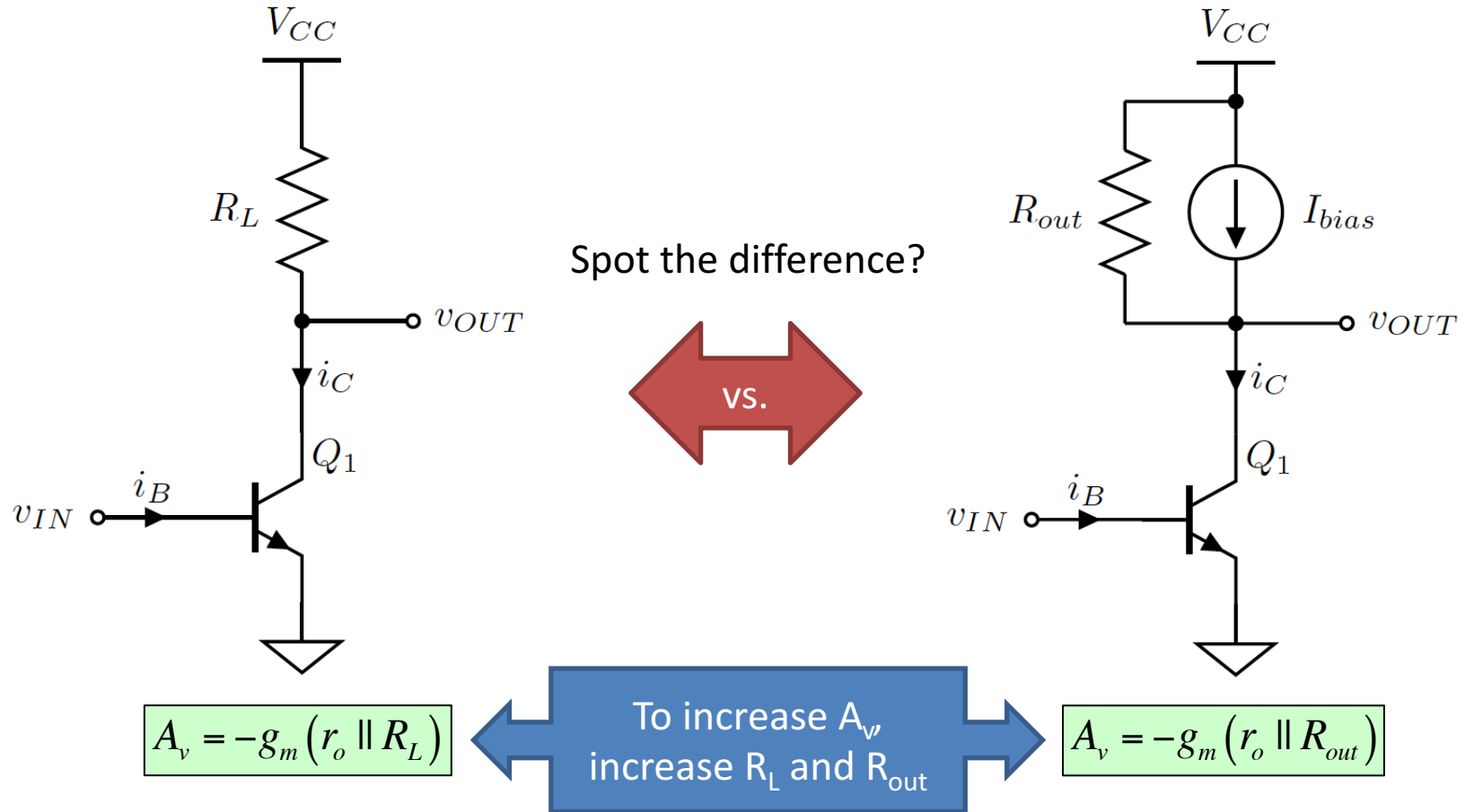
# Implications of Using Current Source for Biasing



# Can We Increase $R_L$ Arbitrarily?

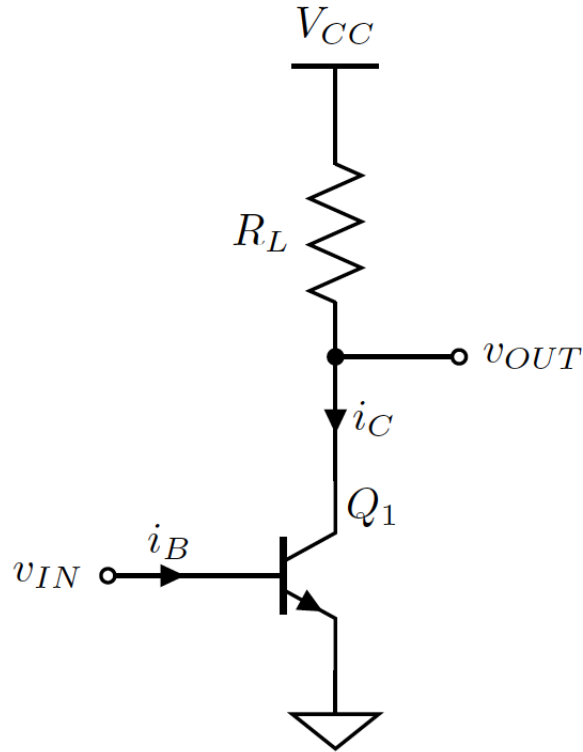

$$A_v = -g_m (r_o \parallel R_L)$$


What happens to the output DC voltage?

$$V_{OUT} = V_{CC} - I_{C,Q} R_L$$

For the same current,  
increasing  $R_L$  reduces  $V_{OUT}$

To remain in the forward-active region:

$$V_{OUT} = V_{CE,Q} > V_{CE,sat}$$

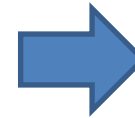

$$R_L < \frac{V_{CC} - V_{CE,sat}}{I_{C,Q}}$$


To increase  $R_L$ , we can increase  $V_{CC}$

→ Is this a good idea?

→ **Tradeoff between  $A_v$  and  $V_{CC}$ !**



# Biasing The BJT Using A Current Source

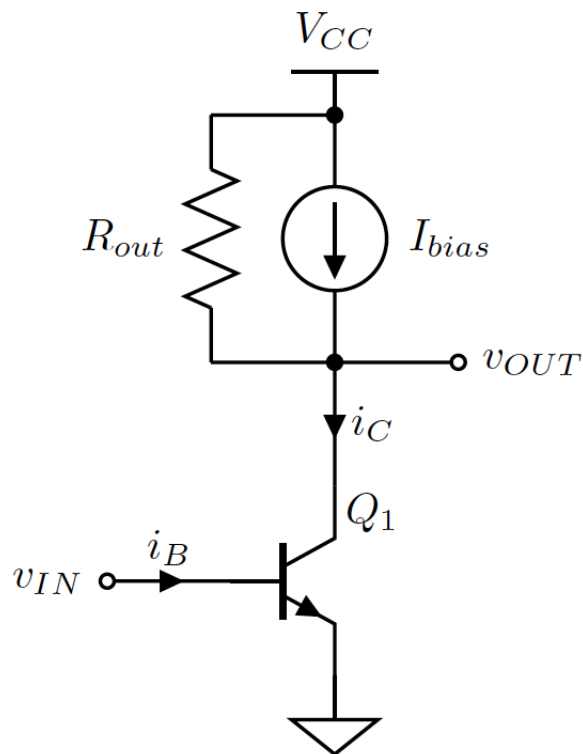

$$A_v = -g_m (r_o \parallel R_{out})$$

Output DC voltage?

$$V_{OUT} = V_{CC} - (I_{C,Q} - I_{bias}) R_L$$


But...

$$R_L \rightarrow \infty \quad \Rightarrow \quad I_{bias} \rightarrow I_{C,Q}$$


Can increase  $R_L$  indefinitely  
without having to increase  $V_{CC}$ !

In practice, this usually means we can  
get away with lower supply voltages if  
we use current sources!

# Resistor vs. Current Source Biasing

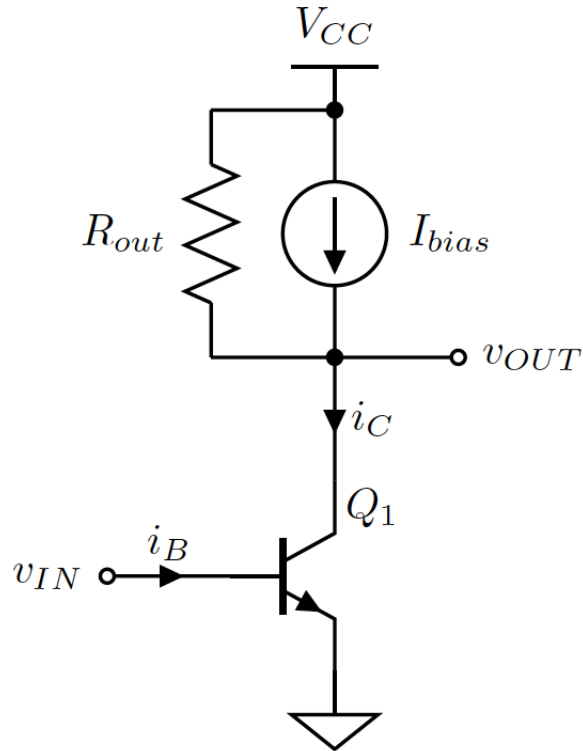

$$A_v = -g_m (r_o \parallel R_{out})$$

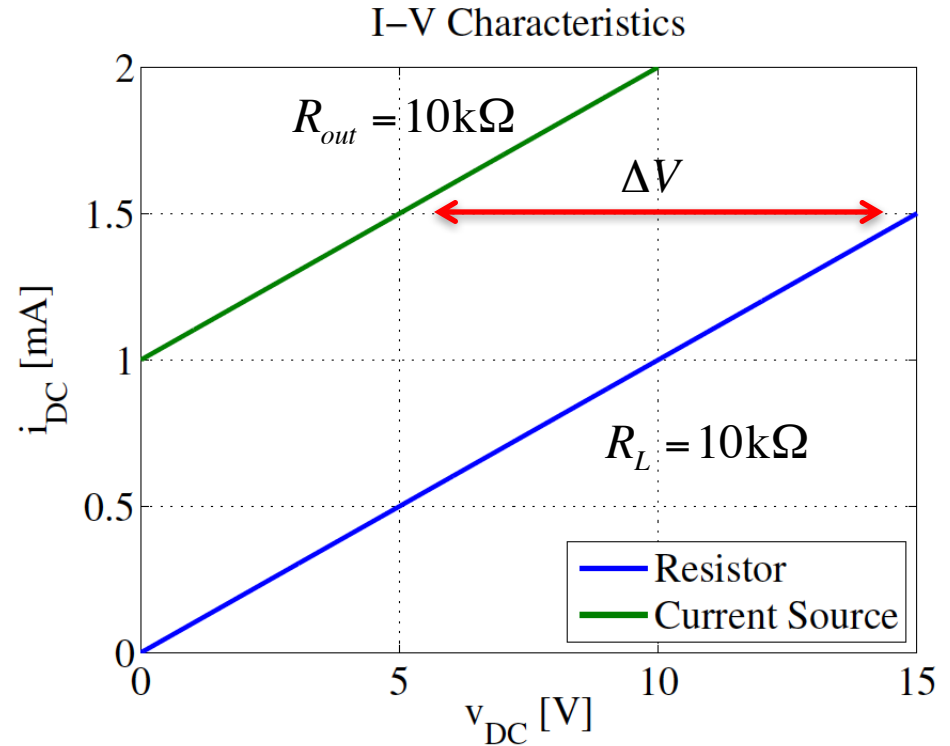


Linear vs. Non-linear


# How Do We Build Current Sources?

- Transistor Output Characteristics (hmmm...)


BJT Output Characteristic

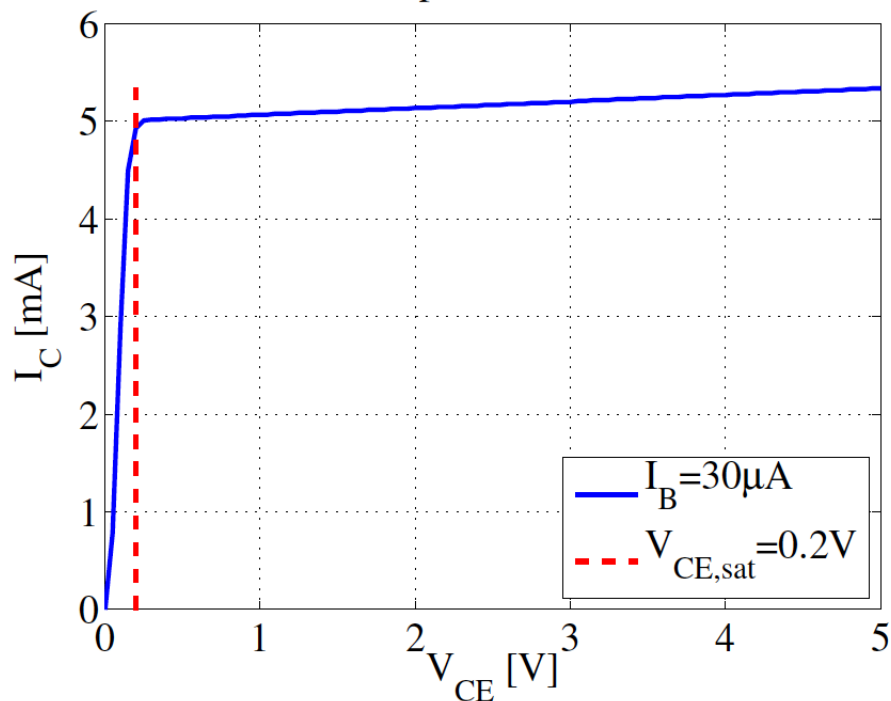

MOS Output Characteristic

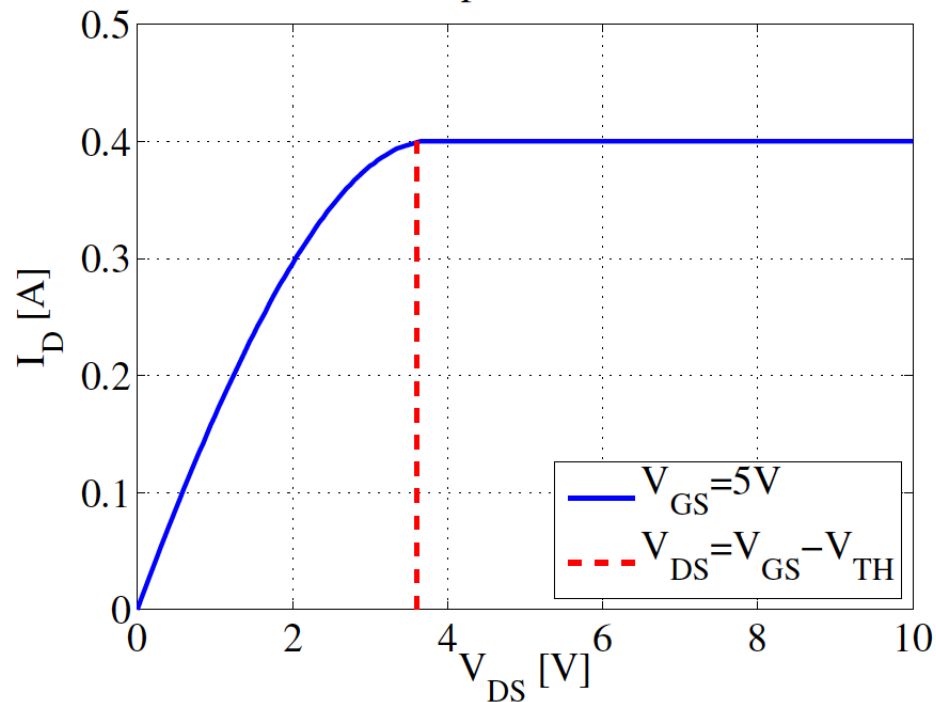


# A BJT Current Source

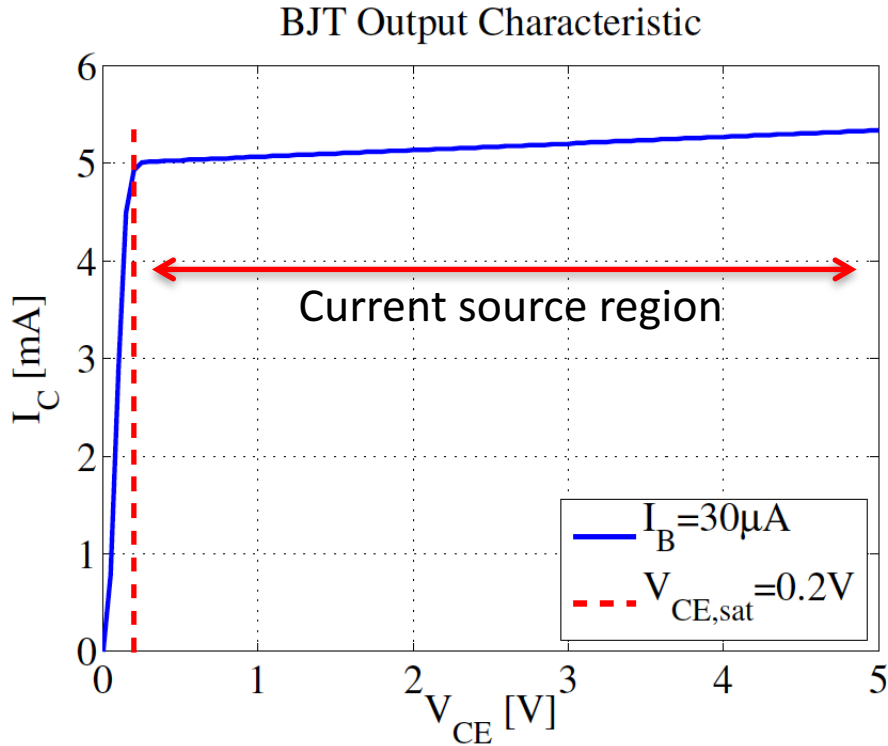

In the forward-active region:

$$I_{source} \approx 5\text{mA}$$
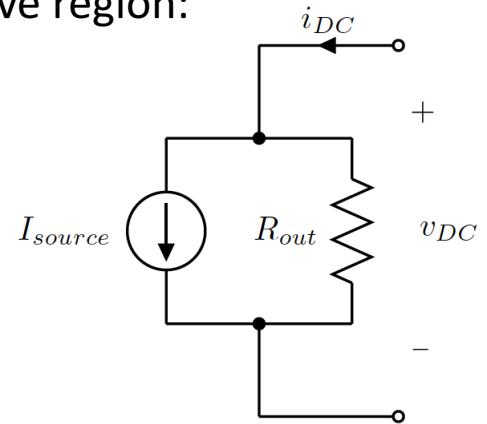
$$R_{out} = \left( \frac{\partial I_C}{\partial V_{CE}} \right)^{-1} = r_o$$




Additional metric:  $V_{min}$

$$V_{min} = V_{CE,sat}$$

# A MOSFET Current Source


MOS Output Characteristic

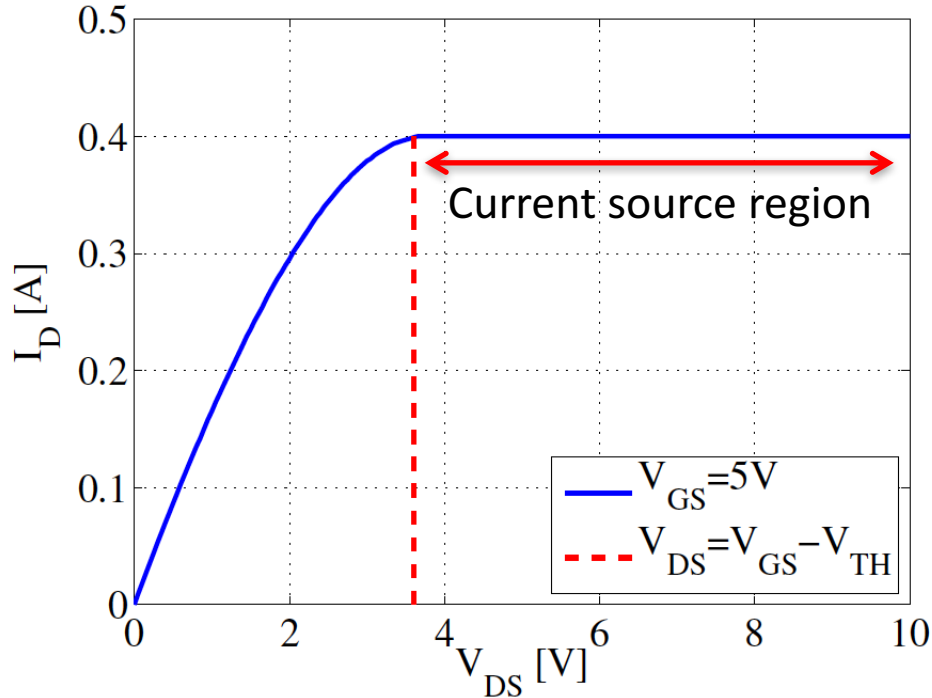

In the saturation region:

$$I_{source} \approx 0.4A$$
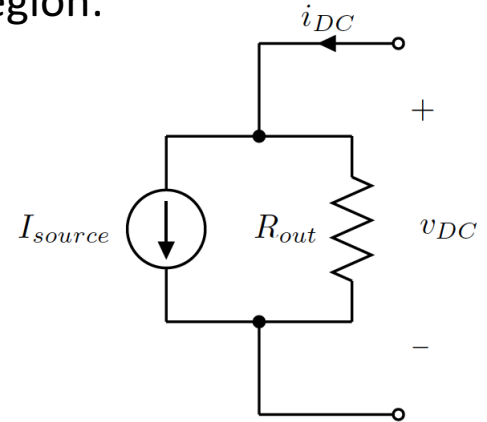
$$R_{out} = \left( \frac{\partial I_D}{\partial V_{DS}} \right)^{-1} = r_o$$




Additional metric:  $V_{min}$

$$V_{min} = V_{GS} - V_{TH}$$
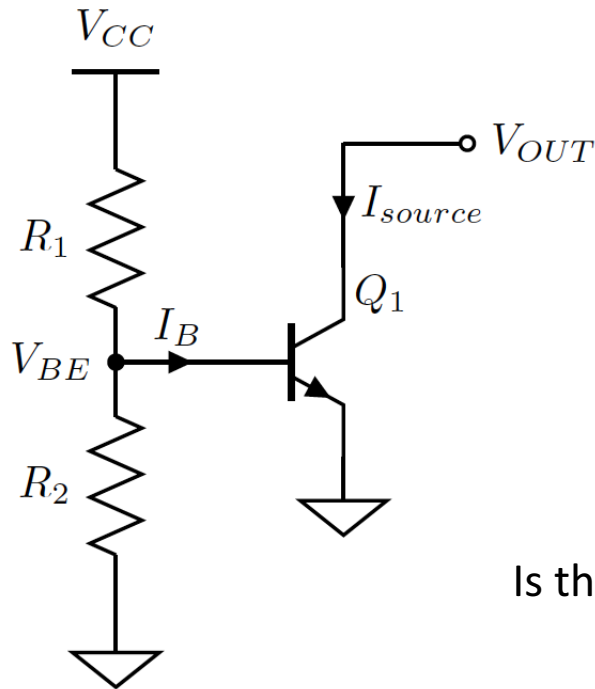
# A Simple BJT Current Source


- Provide  $V_{BE}$  using a voltage divider



?



Is this a good idea?

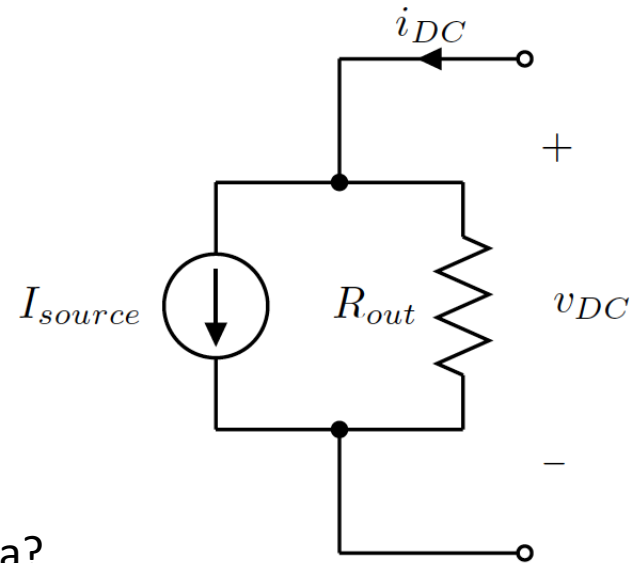



# Next Meeting

- Current Mirrors
- Differential Circuits

