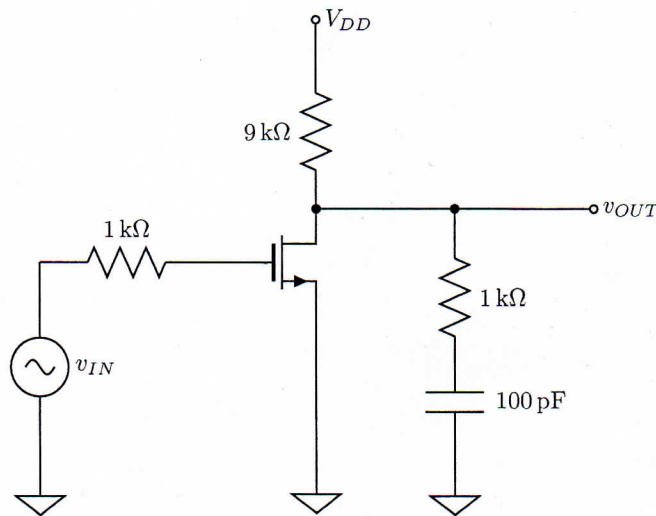


Name:

Section:

Part III:

(16 points) Consider the common source amplifier shown in the figure below. Assume that the transistor has been biased in the saturation region. It has an $I_D = 1 \text{ mA}$, additionally $k = 617 \times 10^{-6} \frac{\text{A}}{\text{V}^2}$, $V_A \rightarrow \infty$, and $C_{gs} = 1 \text{ pF}$. You may ignore all other parasitic capacitors.



1. What is the low frequency gain (v_{out}/v_{in}) for this amplifier? (4 points)

$$v_{in} \xrightarrow{1k} v_{gs} \xrightarrow{g_m v_{gs}} 9k \xrightarrow{v_{out}} \quad g_m = \sqrt{4 \cdot k \cdot I_D} = 1.57 \text{ mS}$$

$$\frac{v_{out}}{v_{in}} = -g_m (9k) = -14.14$$

$$v_{out}/v_{in} = -14.14$$

2. Find the frequency-dependent transfer function ($v_{out}(s)/v_{in}(s)$) for the amplifier. (6 points)

$$v_{in} \xrightarrow{1k} C_{gs} \xrightarrow{v_{gs}} \xrightarrow{g_m v_{gs}} 9k \xrightarrow{v_{out}} \quad Z_x = 9k \parallel \left(1k + \frac{1}{s(100p)} \right) = \frac{9000 (1 + s/10^7)}{(1 + s/10^9)}$$


$$v_{gs} = \frac{1}{1k + \frac{1}{sC_{gs}}} \cdot v_{in} = \frac{v_{in}}{(1 + s/10^9)}$$

$$v_{out} = -g_m z_x \cdot v_{gs} = -g_m \left(\frac{9000 (1 + s/10^7)}{(1 + s/10^6)} \right) \left(\frac{v_{in}}{(1 + s/10^9)} \right)$$


$$\frac{v_{out}}{v_{in}}(s) = \frac{-14.14 (1 + s/10^7)}{(1 + s/10^6) (1 + s/10^9)}$$

$$v_{out}(s)/v_{in}(s) = \frac{-14.14 (1 + s/10^7)}{(1 + s/10^6) (1 + s/10^9)}$$

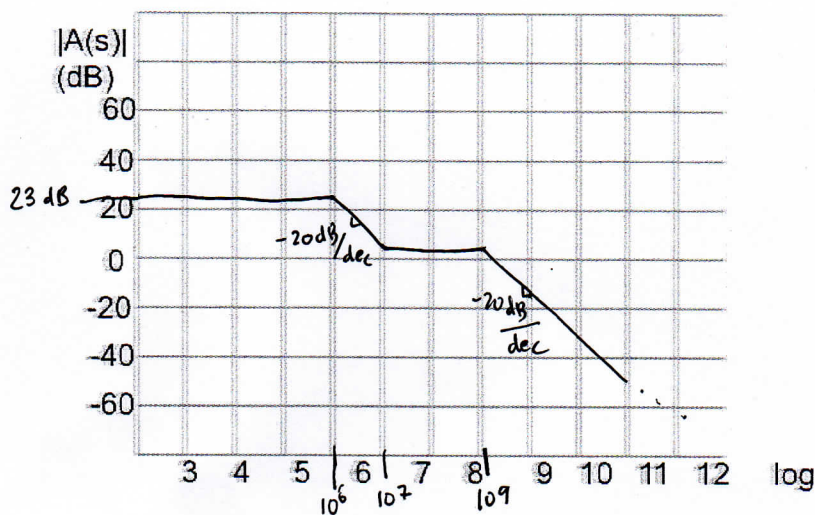3. Draw the bode plot for the amplifier in the space provided below. (6 points)



$$A_0 = 20 \log(14.14) = 23 \text{ dB}$$

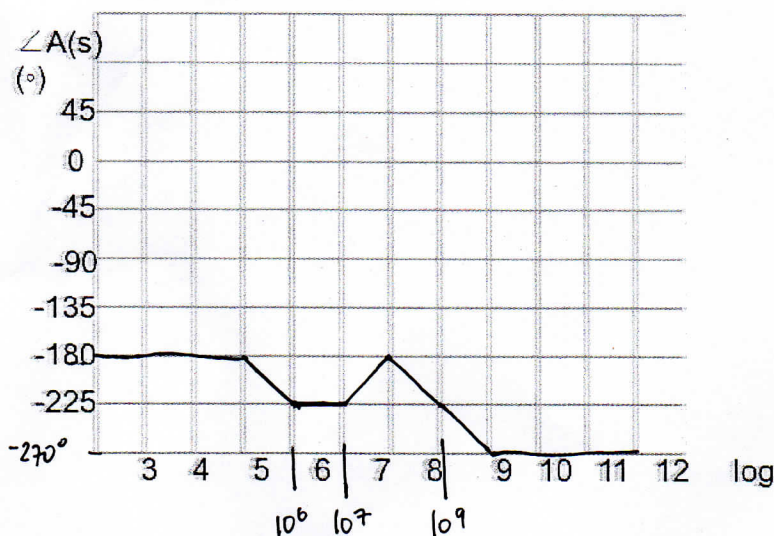

since amp is inverting, start at -180°