



EEE 51: Second Semester 2017 - 2018

Lecture 2




Transistor Models

Today





- Transistor Models
 - Large Signal
 - Small Signal




From Transistors to Transistor Circuits

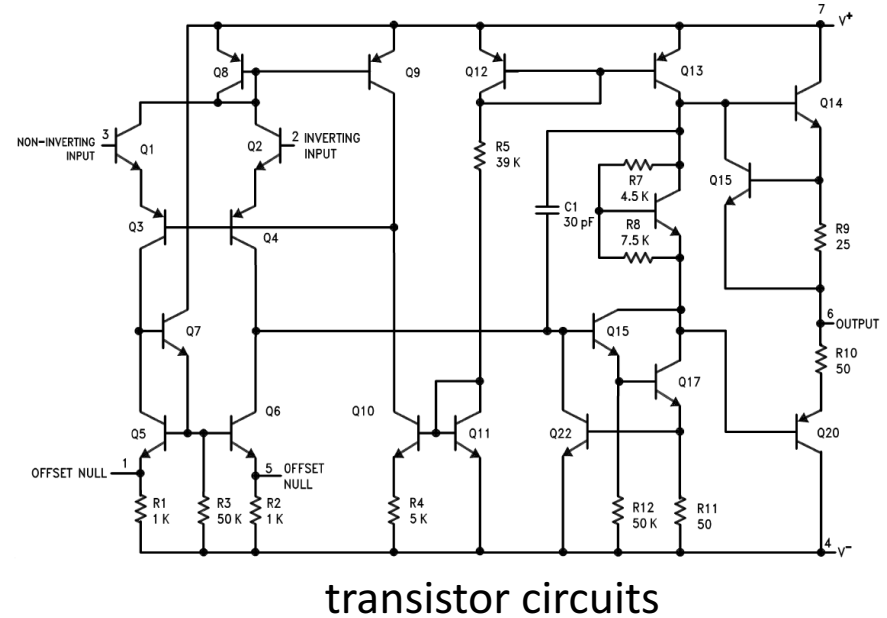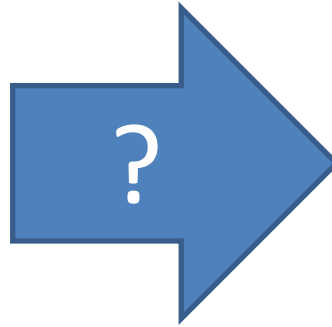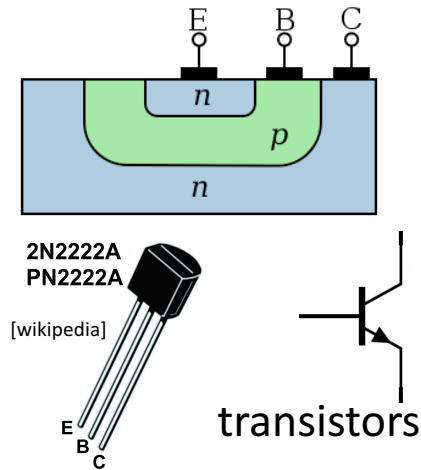

Transistor Models

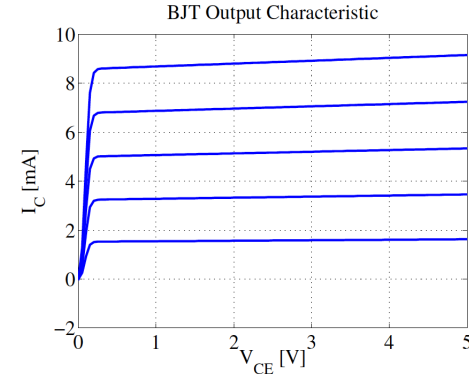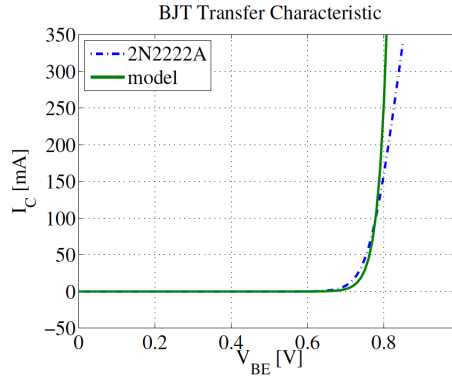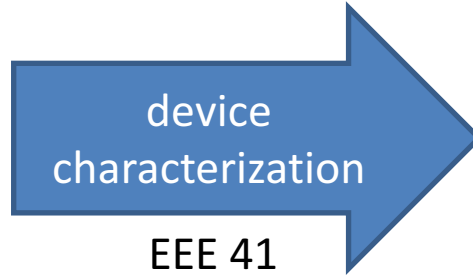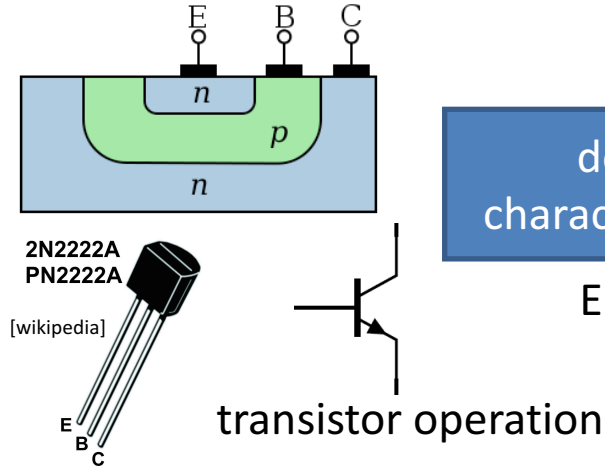


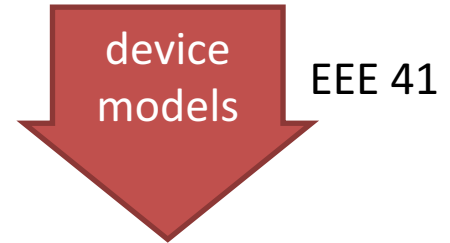large signal terminal behavior (I-V curves)



I-V models (large signal approximation)
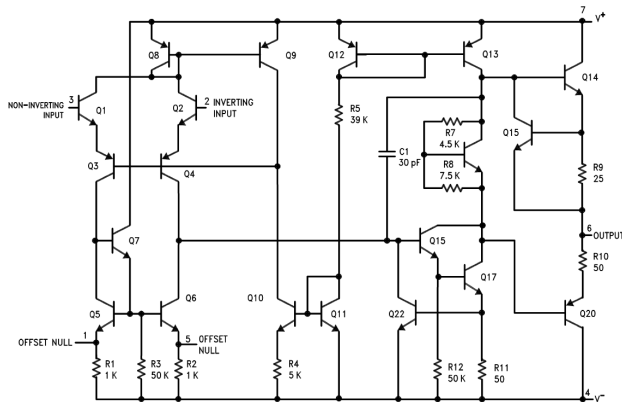
$$I_C = I_S \left(e^{\frac{V_{BE}}{V_T}} - 1 \right) \left(1 + \frac{V_{CE}}{V_A} \right) \quad I_B = \frac{1}{\beta} I_C$$





transistor circuits



Large Signal Models

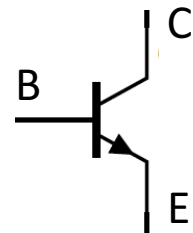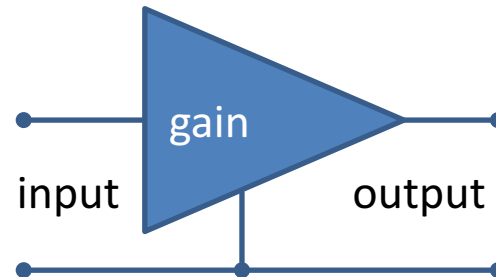
- V and I over **different transistor operating** regions
 - BJT: Forward-active, saturation, cut-off
 - MOSFET: Saturation, linear (ohmic), subthreshold (“cut-off”)
- Large signal model reference → largest “gain” topology
 - Transfer Characteristic
 - Output Characteristic
 - Input Characteristic
 - “Unilateral”
 - “Low” frequency




How many ways can you configure a 3-terminal device?

BJT Transfer Characteristics (I_C vs. V_{BE})
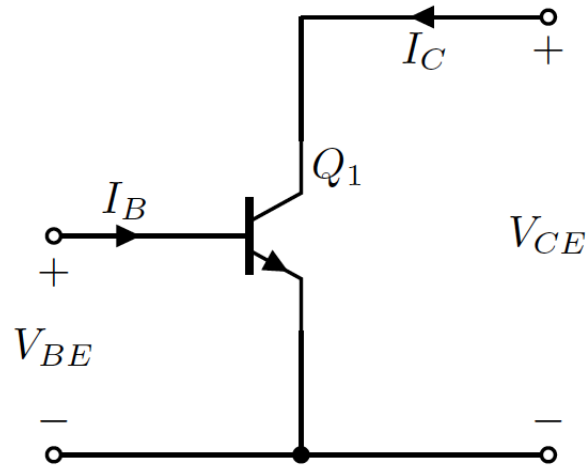
$$I_C = I_S \left(e^{\frac{V_{BE}}{V_T}} - 1 \right) \left(1 + \frac{V_{CE}}{V_A} \right)$$
$$\approx I_S \cdot e^{\frac{V_{BE}}{V_T}}$$





Common-Emitter topology

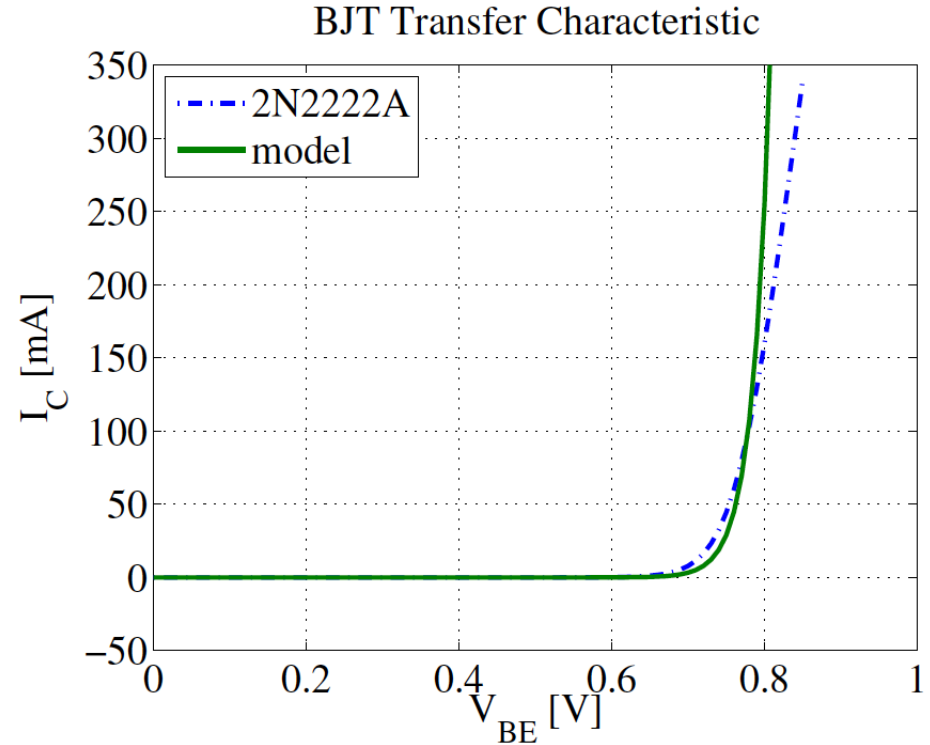

MOSFET Transfer Characteristics (I_D vs. V_{GS})



$$I_D = k \cdot (V_{GS} - V_{TH})^2 (1 + \lambda \cdot V_{DS})$$

$$\approx k \cdot (V_{GS} - V_{TH})^2$$

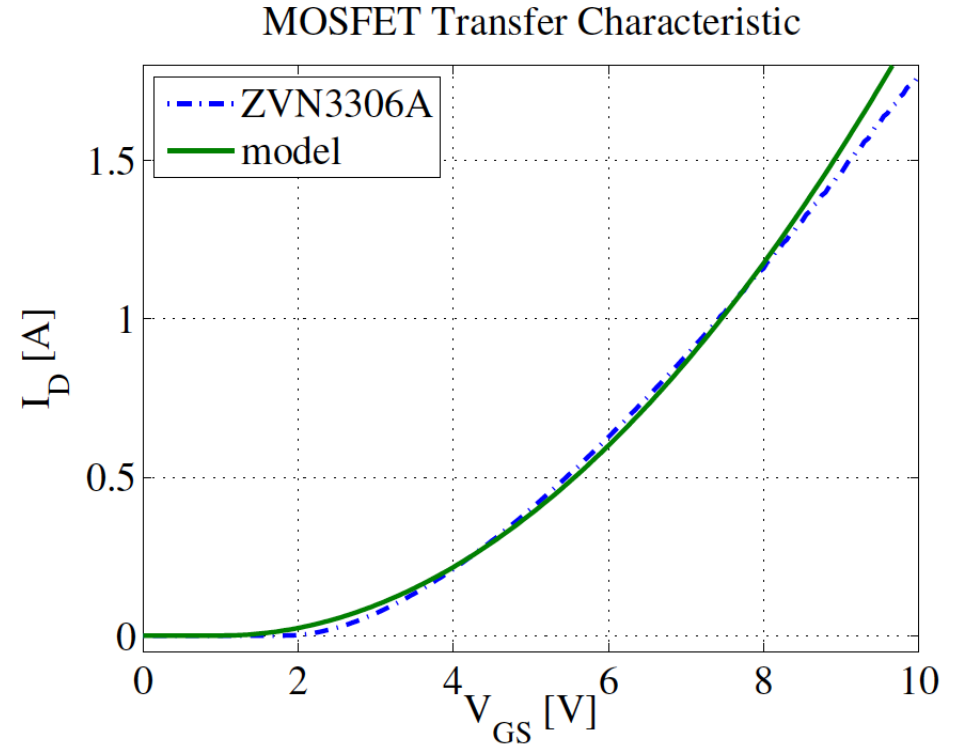
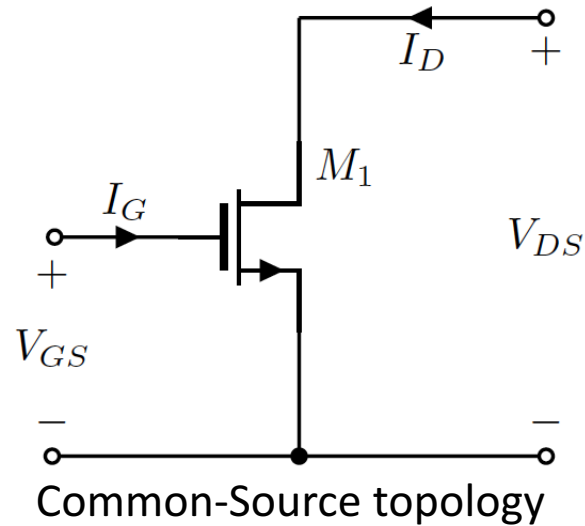


Output Characteristics

BJT Output Characteristic

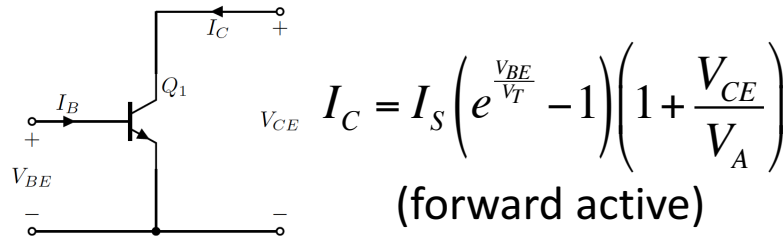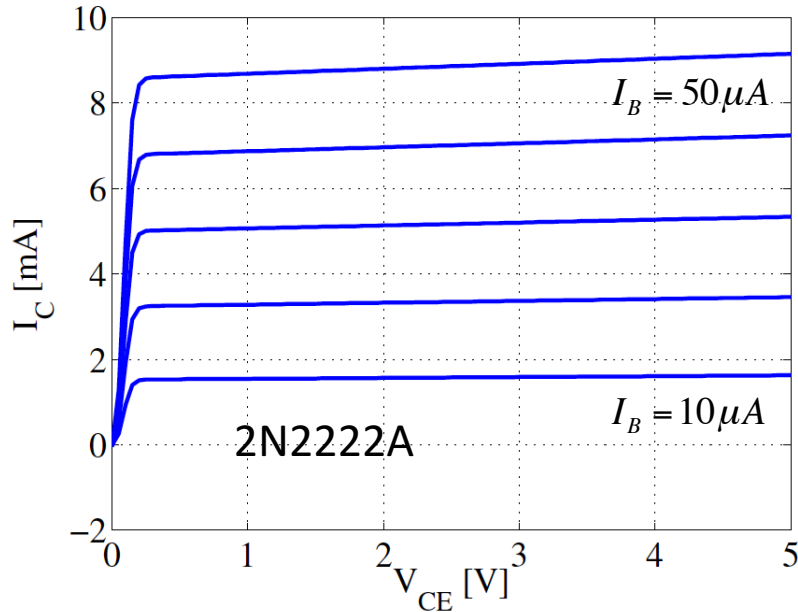


MOS Output Characteristic

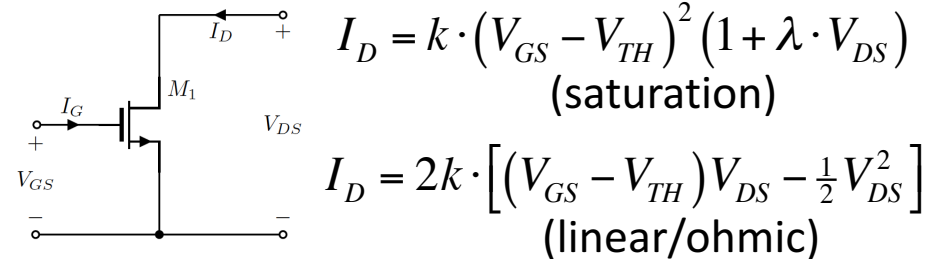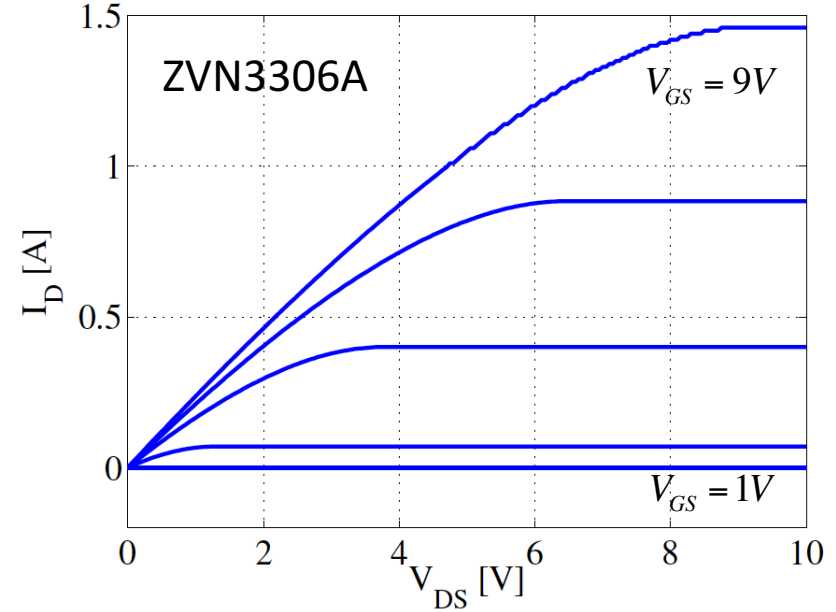


Input Characteristics

BJT

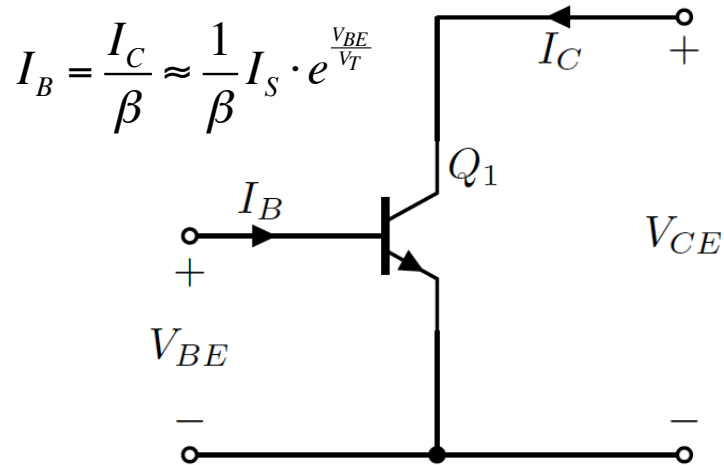

MOSFET

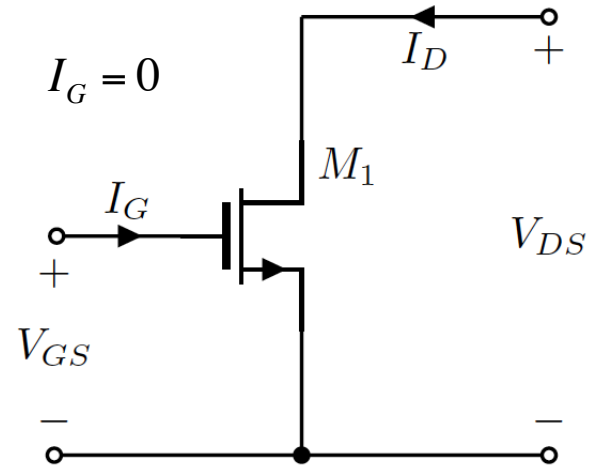

Two Ways to Bridge the Gap


The complex, non-intuitive, non-extendable way...

I-V models
(**large signal** transfer,
input and output
characteristics)

$$I_C = I_S \left(e^{\frac{V_{BE}}{V_T}} - 1 \right) \left(1 + \frac{V_{CE}}{V_A} \right)$$
$$I_B = \frac{1}{\beta} I_C$$

direct application
of KCL and KVL

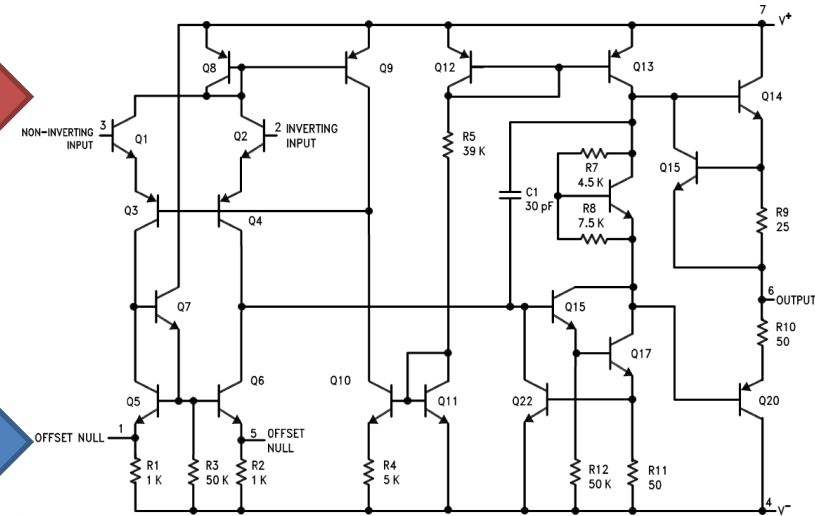linearization +
two-port network
reduction



transistor circuits


EEE 51 way (aka the fun way ☺)

- Allows us to use our EEE 31, 33 skills
- Allows us to break up large circuits into smaller ones
- Gives us more intuition in terms of circuit operation



Linearization (1)


- Consider an amplifier with large gain:

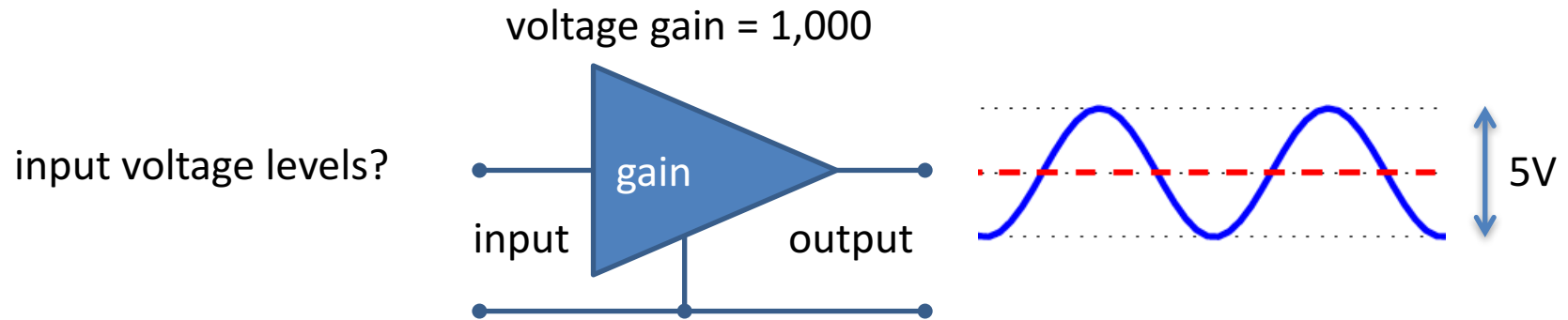


In most amplifier applications, we are interested in the transistor behavior when we apply “small” signals

Linearization (2)

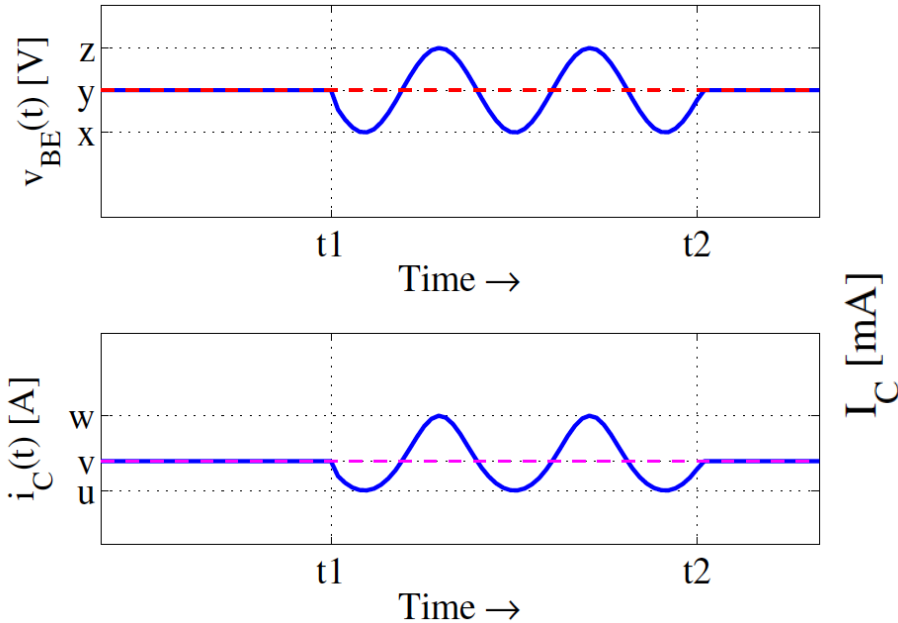- Consider a BJT in the forward active region:



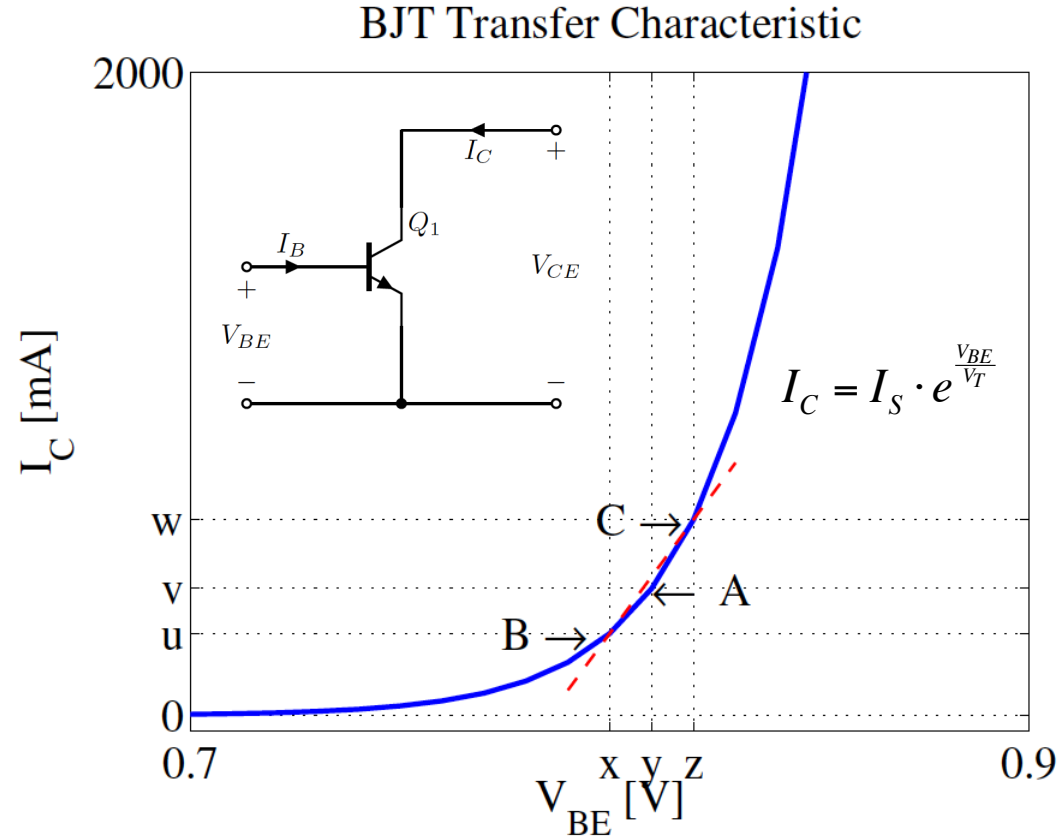A is known as the quiescent DC operating point



Linearization (3)

- So what if the signals are “small”?
 - Recall: Taylor Series expansion

$$f(x) = f(a) + \frac{f'(a)}{1!}(x-a) + \frac{f''(a)}{2!}(x-a)^2 + \frac{f'''(a)}{3!}(x-a)^3 + \dots$$

Example:

$$\begin{aligned} e^x &= e^0 + \frac{e^0}{1!}x + \frac{e^0}{2!}x^2 + \frac{e^0}{3!}x^3 + \dots \\ &= 1 + x + \frac{x^2}{2!} + \frac{x^3}{3!} + \dots \end{aligned}$$



Linearizing the BJT Transfer Characteristic (1)

- Expanding the transfer characteristic


$$i_c = I_{C,Q} + i_c = I_S \cdot e^{\frac{V_{BE,Q} + v_{be}}{V_T}}$$

$$I_{C,Q} + i_c = I_S \cdot e^{\frac{V_{BE,Q}}{V_T}} \cdot e^{\frac{v_{be}}{V_T}} = I_{C,Q} \cdot e^{\frac{v_{be}}{V_T}} \leftarrow \text{nonlinear!}$$

$$= I_{C,Q} \cdot \left(1 + \frac{v_{be}}{V_T} + \frac{v_{be}^2}{2V_T^2} + \frac{v_{be}^3}{6V_T^3} + \dots \right)$$

$$I_{C,Q} + i_c = I_{C,Q} + I_{C,Q} \frac{v_{be}}{V_T} + \frac{I_{C,Q}}{2} \left(\frac{v_{be}}{V_T} \right)^2 + \frac{I_{C,Q}}{6} \left(\frac{v_{be}}{V_T} \right)^3$$
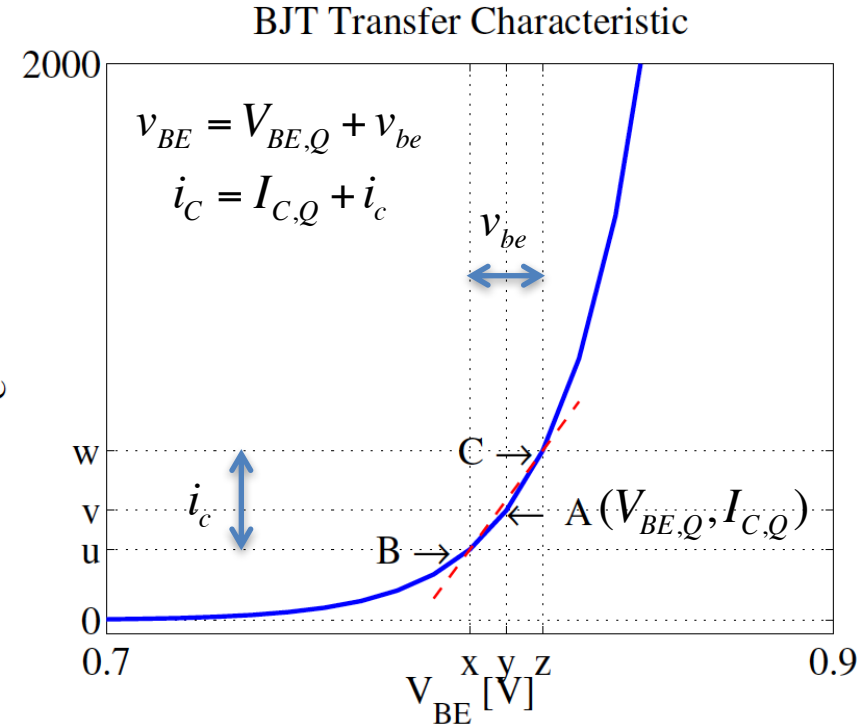
$$i_c = I_{C,Q} \frac{v_{be}}{V_T} + \frac{I_{C,Q}}{2} \left(\frac{v_{be}}{V_T} \right)^2 + \frac{I_{C,Q}}{6} \left(\frac{v_{be}}{V_T} \right)^3 + \dots$$



Linearizing the BJT Transfer Characteristic (2)


- If v_{be} is “small”

$$i_c = I_{C,Q} \frac{v_{be}}{V_T} + \frac{I_{C,Q}}{2} \left(\frac{v_{be}}{V_T} \right)^2 + \frac{I_{C,Q}}{6} \left(\frac{v_{be}}{V_T} \right)^3 + \dots$$

$$\approx I_{C,Q} \frac{v_{be}}{V_T} \quad \leftarrow \text{linear!}$$


“small” means $\rightarrow \frac{v_{be}}{V_T} \ll 1$

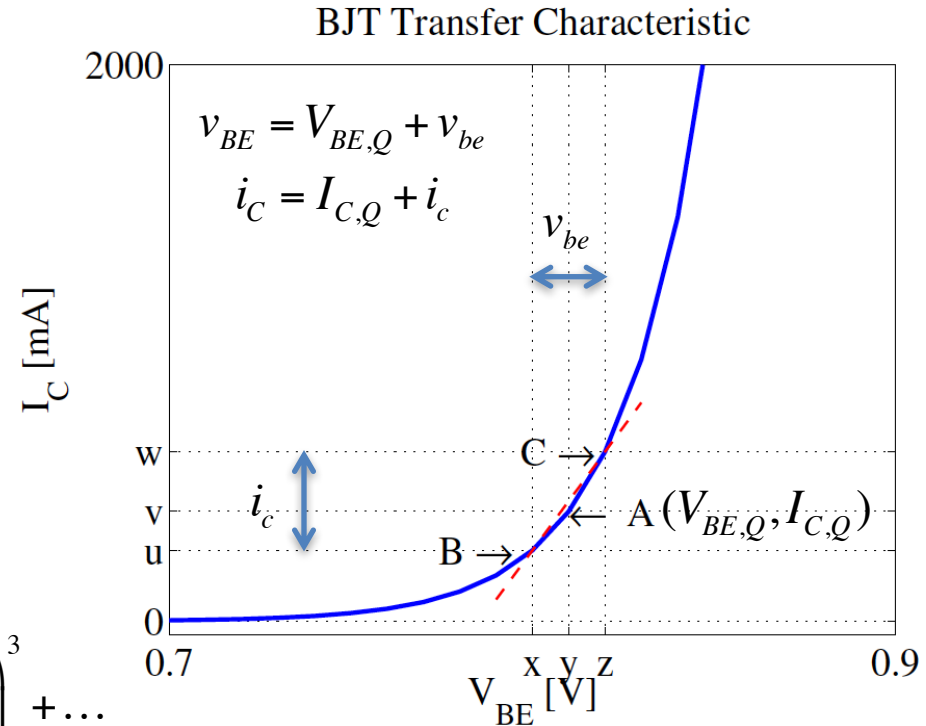Approximation error: $\frac{I_{C,Q}}{2} \left(\frac{v_{be}}{V_T} \right)^2 + \frac{I_{C,Q}}{6} \left(\frac{v_{be}}{V_T} \right)^3 + \dots$



Linearizing the BJT Transfer Characteristic (3)

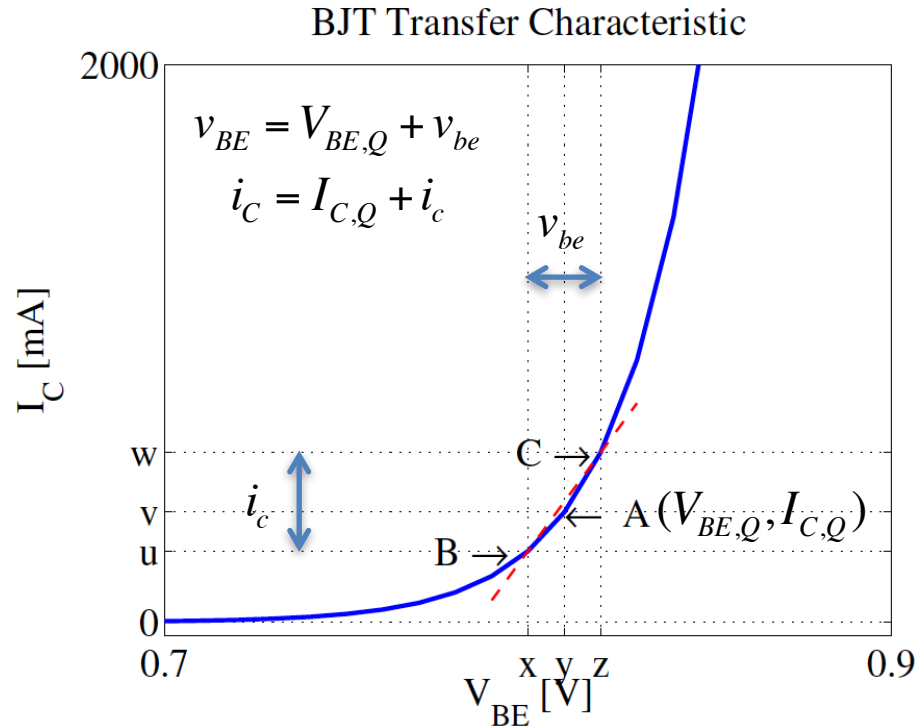- Another way to think about linearization



If we make $v_{be} \rightarrow 0$

$$m = \lim_{v_{be} \rightarrow 0} \frac{i_C(V_{BE,Q} + v_{be}) - i_C(V_{BE,Q})}{V_{BE,Q} + v_{be} - V_{BE,Q}}$$
$$= \left. \frac{\partial I_C}{\partial V_{BE}} \right|_{V_{BE}=V_{BE,Q}}$$

We can make the approximation:


$$i_c = m \cdot v_{be} = \left. \frac{\partial I_C}{\partial V_{BE}} \right|_{V_{BE}=V_{BE,Q}} \cdot v_{be}$$



Linearizing the BJT Transfer Characteristic (4)

- Transconductance

BJT Transfer Characteristic

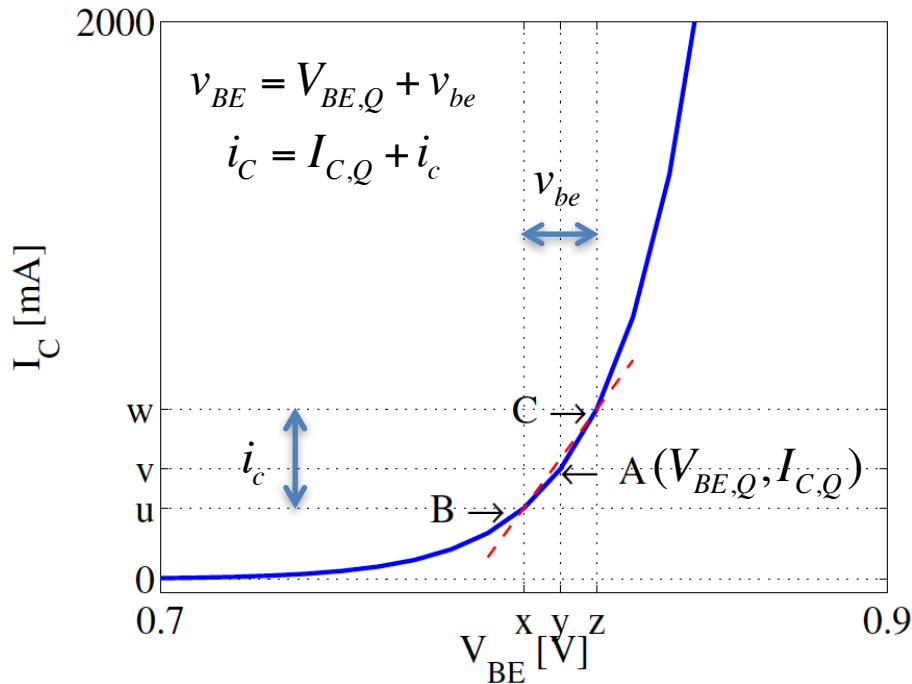

Define transconductance as

$$g_m = \left. \frac{\partial I_C}{\partial V_{BE}} \right|_{V_{BE}=V_{BE,Q}}$$

For small signals

$$i_c = g_m \cdot v_{be}$$




Linearizing the BJT Transfer Characteristic (5)

- BJT transconductance

$$\begin{aligned} g_m &= \left. \frac{\partial I_C}{\partial V_{BE}} \right|_{V_{BE}=V_{BE,Q}} \\ &= \left. \frac{\partial}{\partial V_{BE}} \left(I_S \cdot e^{\frac{V_{BE}}{V_T}} \right) \right|_{V_{BE}=V_{BE,Q}} \\ &= \frac{I_S \cdot e^{\frac{V_{BE,Q}}{V_T}}}{V_T} = \frac{I_{C,Q}}{V_T} \end{aligned}$$

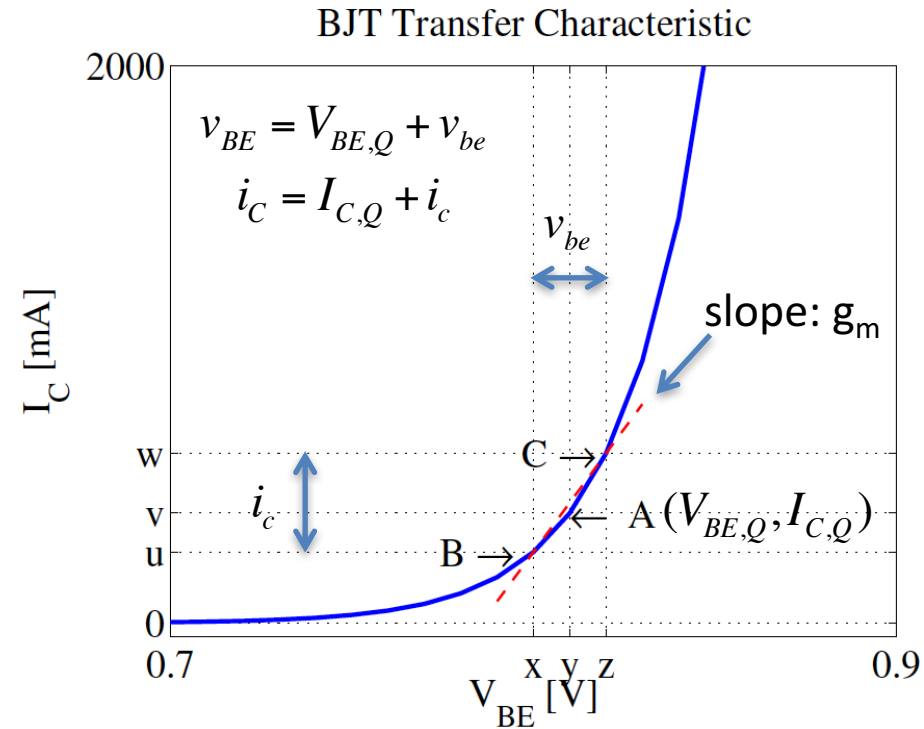Again, we get: $i_c = g_m \cdot v_{be} = \frac{I_{C,Q}}{V_T} \cdot v_{be}$




Linearizing the BJT Transfer Characteristic

- BJT transconductance


$$\begin{aligned} g_m &= \left. \frac{\partial I_C}{\partial V_{BE}} \right|_{V_{BE}=V_{BE,Q}} \\ &= \left. \frac{\partial}{\partial V_{BE}} \left(I_S \cdot e^{\frac{V_{BE}}{V_T}} \right) \right|_{V_{BE}=V_{BE,Q}} \\ &= \frac{I_S \cdot e^{\frac{V_{BE,Q}}{V_T}}}{V_T} = \frac{I_{C,Q}}{V_T} \end{aligned}$$

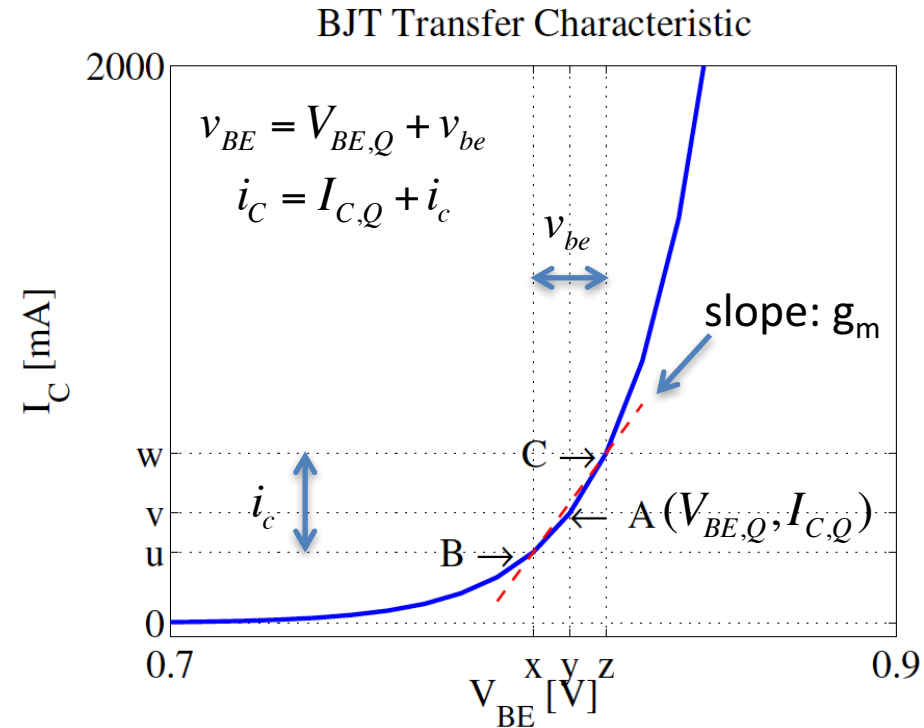Again, we get: $i_c = g_m \cdot v_{be} = \frac{I_{C,Q}}{V_T} \cdot v_{be}$



Does g_m give us the complete picture?

- What else changes i_c ?

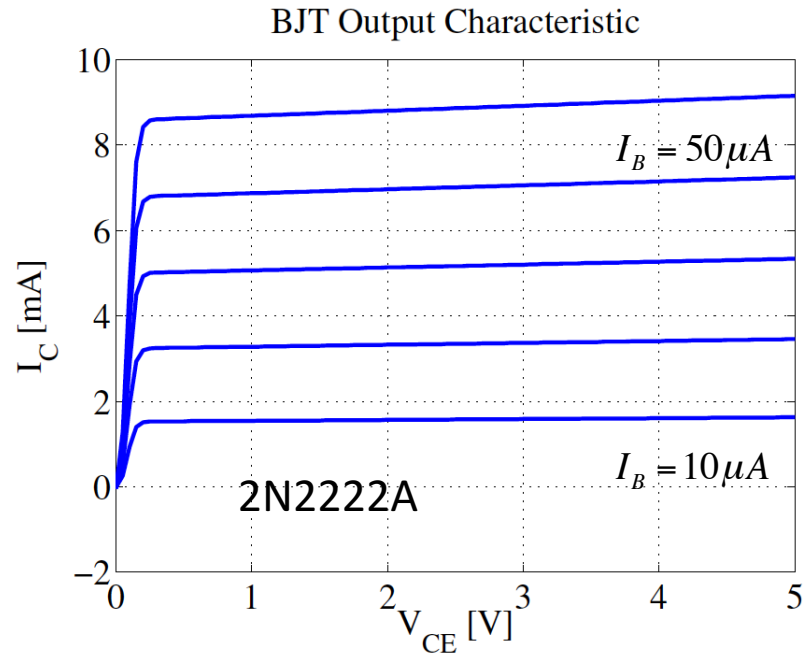

$$I_C = I_S \left(e^{\frac{V_{BE}}{V_T}} - 1 \right) \left(1 + \frac{V_{CE}}{V_A} \right)$$




BJT Transistor Output Resistance

- What happens when there are small changes in V_{CE} ?

$$\begin{aligned} i_c &= \left. \frac{\partial I_C}{\partial V_{CE}} \right|_{V_{CE}=V_{CE,Q}} \cdot v_{ce} \\ &= \frac{\partial}{\partial V_{CE}} \left(I_S \left(e^{\frac{V_{BE}}{V_T}} - 1 \right) \left(1 + \frac{V_{CE}}{V_A} \right) \right) \bigg|_{V_{CE}=V_{CE,Q}} \cdot v_{ce} \\ &= \frac{I_S \left(e^{\frac{V_{BE,Q}}{V_T}} - 1 \right)}{V_A} \cdot v_{ce} = \frac{I_{C,Q}}{V_A} \cdot v_{ce} = g_o \cdot v_{ce} = \frac{v_{ce}}{r_o} \end{aligned}$$

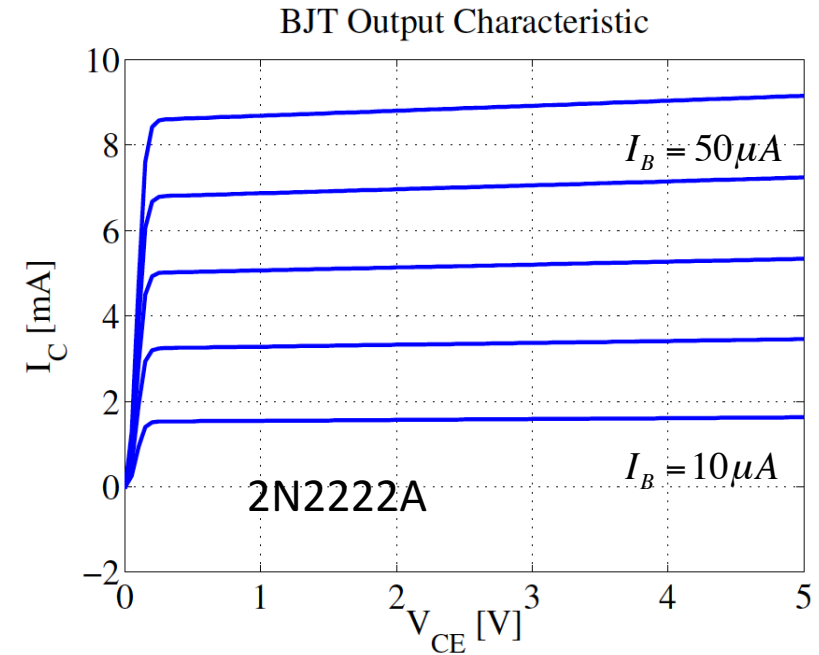Output resistance: $r_o = \frac{V_A}{I_{C,Q}}$



Completing the Picture: Transistor Input Resistance

BJT

- Small signal base current due to v_{be}

$$\begin{aligned} g_{\pi} &= \left. \frac{\partial I_B}{\partial V_{BE}} \right|_{V_{BE}=V_{BE,Q}} \\ &= \left. \frac{\partial}{\partial V_{BE}} \left(\frac{I_C}{\beta} \right) \right|_{V_{BE}=V_{BE,Q}} = \frac{1}{\beta} \cdot \left. \frac{\partial I_C}{\partial V_{BE}} \right|_{V_{BE}=V_{BE,Q}} \\ &= \frac{g_m}{\beta} \\ r_{\pi} &= \frac{1}{g_{\pi}} = \frac{\beta}{g_m} = \frac{\beta \cdot V_T}{I_{C,Q}} \end{aligned}$$



Linearization Result: The Small Signal Model

BJT

- Total i_c :

$$i_c = \left(\left. \frac{\partial I_C}{\partial V_{BE}} \right|_{V_{BE}=V_{BE,Q}} \cdot v_{be} \right) + \left(\left. \frac{\partial I_C}{\partial V_{CE}} \right|_{V_{CE}=V_{CE,Q}} \cdot v_{ce} \right)$$
$$= g_m v_{be} + \frac{v_{ce}}{r_o}$$


- Total i_b :

$$i_b = \left. \frac{\partial I_B}{\partial V_{BE}} \right|_{V_{BE}=V_{BE,Q}} \cdot v_{be} = \frac{v_{be}}{r_\pi}$$



The BJT Small Signal Equivalent Circuit

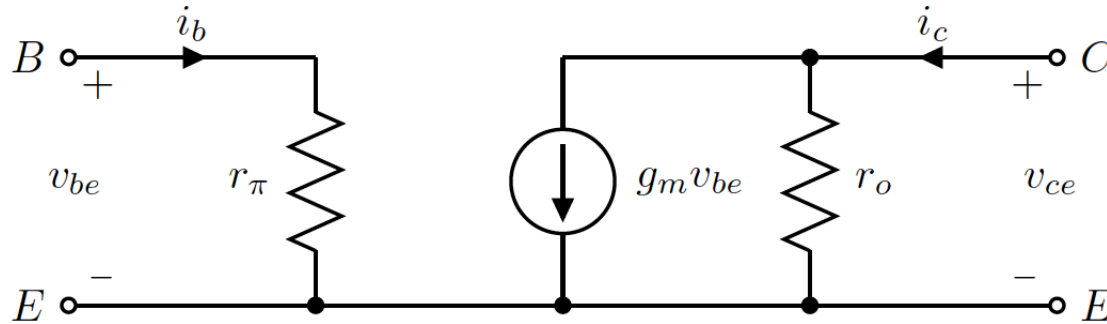- KCL / KVL results in the small signal model



$$i_b = \frac{v_{be}}{r_\pi}$$

$$i_c = g_m v_{be} + \frac{v_{ce}}{r_o}$$

- Linear!
- Fully describes the response of the BJT to **small signal** disturbances about the quiescent point (no DC information!)
- Dependent on the quiescent DC operating point




Linearizing the MOSFET Transfer Characteristic

- MOSFET transconductance

$$\begin{aligned} g_m &= \left. \frac{\partial I_D}{\partial V_{GS}} \right|_{V_{GS}=V_{GS,Q}} \\ &= \left. \frac{\partial}{\partial V_{GS}} \left(k \cdot (V_{GS} - V_{TH})^2 \right) \right|_{V_{GS}=V_{GS,Q}} \\ &= 2k \cdot (V_{GS,Q} - V_{TH}) \end{aligned}$$


We get the linear relationship:
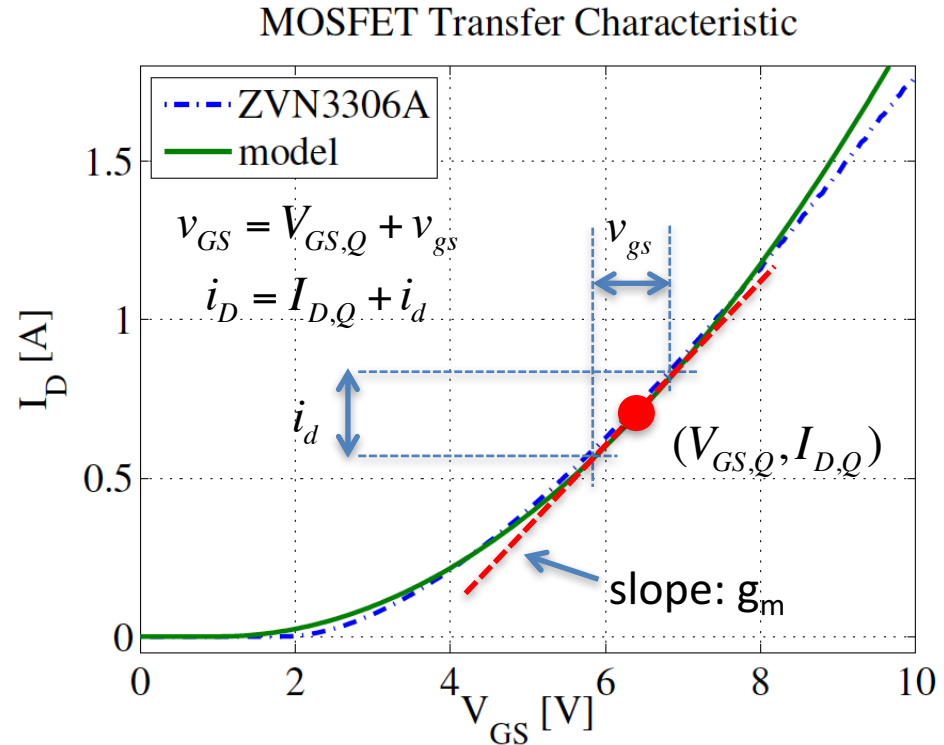
$$i_d = g_m \cdot v_{gs} = 2k \cdot (V_{GS,Q} - V_{TH}) \cdot v_{gs}$$



Does g_m give us the complete picture?

- What else changes i_d ?

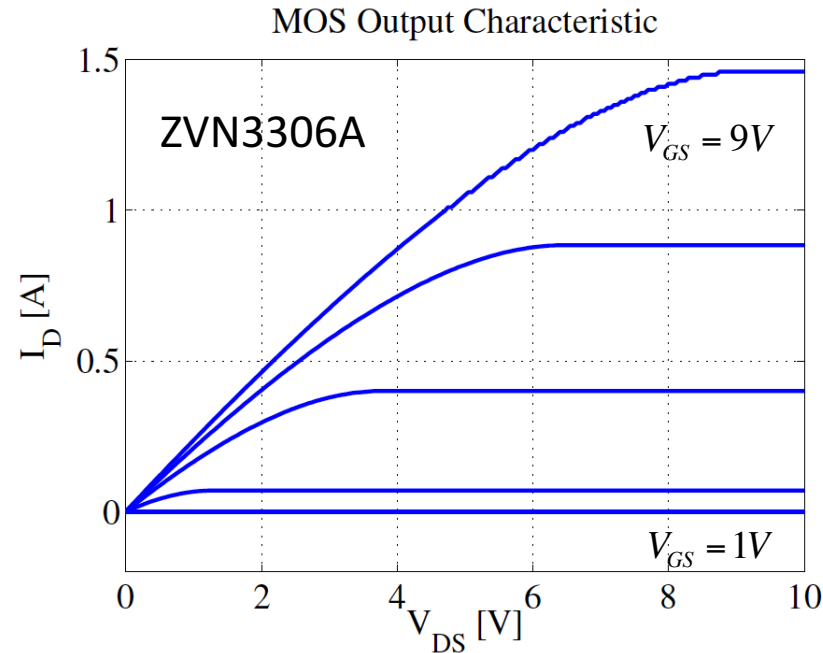


$$I_D = k \cdot (V_{GS} - V_{TH})^2 (1 + \lambda \cdot V_{DS})$$

MOSFET Transistor Output Resistance

- What happens when there are small changes in V_{DS} ?

$$\begin{aligned} i_d &= \left. \frac{\partial I_D}{\partial V_{DS}} \right|_{V_{DS}=V_{DS,Q}} \cdot v_{ds} \\ &= \frac{\partial}{\partial V_{DS}} \left(k \cdot (V_{GS} - V_{TH})^2 (1 + \lambda \cdot V_{DS}) \right) \bigg|_{V_{DS}=V_{DS,Q}} \cdot v_{ds} \\ &= k \cdot (V_{GS} - V_{TH})^2 \lambda \cdot v_{ds} = \lambda I_{D,Q} \cdot v_{ds} \\ &= g_o \cdot v_{ds} = \frac{v_{ds}}{r_o} \end{aligned}$$
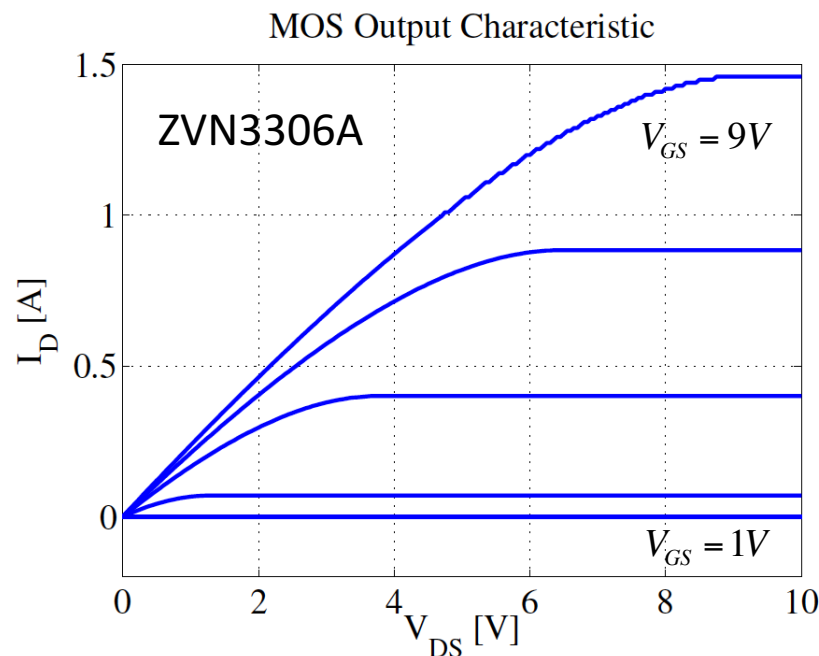
$$\text{Output resistance: } r_o = \frac{1}{\lambda \cdot I_{C,Q}}$$



Completing the Picture: Transistor Input Resistance

MOSFET

- Small signal gate current due to v_{gs}

$$g_{\pi} = \left. \frac{\partial I_G}{\partial V_{GS}} \right|_{V_{GS}=V_{GS,Q}} = 0$$

$$r_{\pi} = \frac{1}{g_{\pi}} \rightarrow \infty$$



Linearization Result: The Small Signal Model

BJT

- Total i_c :

$$i_c = \left(\left. \frac{\partial I_C}{\partial V_{BE}} \right|_{V_{BE}=V_{BE,Q}} \cdot v_{be} \right) + \left(\left. \frac{\partial I_C}{\partial V_{CE}} \right|_{V_{CE}=V_{CE,Q}} \cdot v_{ce} \right)$$
$$= g_m v_{be} + \frac{v_{ce}}{r_o}$$

- Total i_b :

$$i_b = \left. \frac{\partial I_B}{\partial V_{BE}} \right|_{V_{BE}=V_{BE,Q}} \cdot v_{be} = \frac{v_{be}}{r_\pi}$$

MOSFET

- Total i_d :

$$i_d = \left(\left. \frac{\partial I_D}{\partial V_{GS}} \right|_{V_{GS}=V_{GS,Q}} \cdot v_{gs} \right) + \left(\left. \frac{\partial I_D}{\partial V_{DS}} \right|_{V_{DS}=V_{DS,Q}} \cdot v_{ds} \right)$$
$$= g_m v_{gs} + \frac{v_{ds}}{r_o}$$


- Total i_g :

$$i_g = 0$$




The MOSFET Small Signal Equivalent Circuit

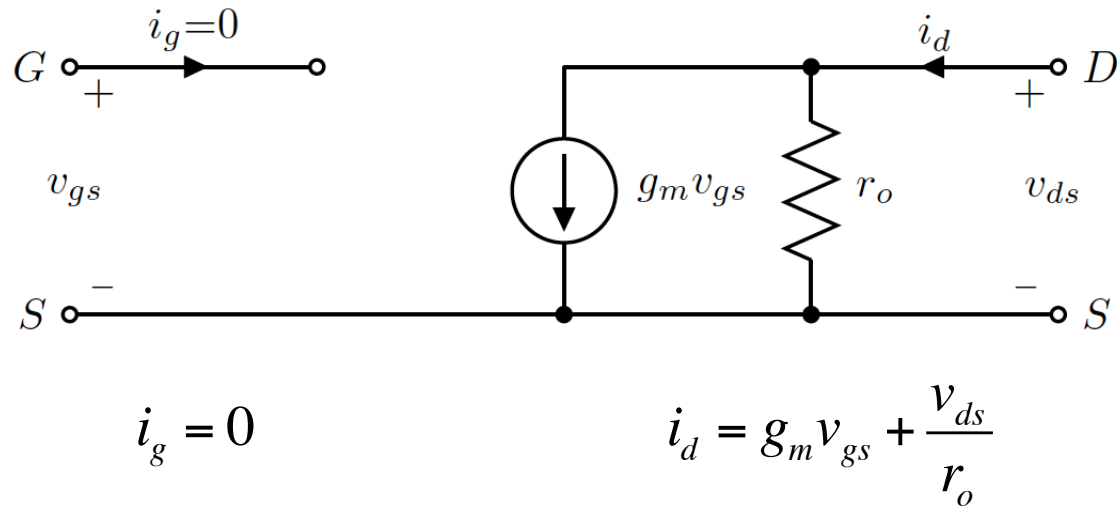- KCL / KVL results in the small signal model




Large Signal vs. Small Signal



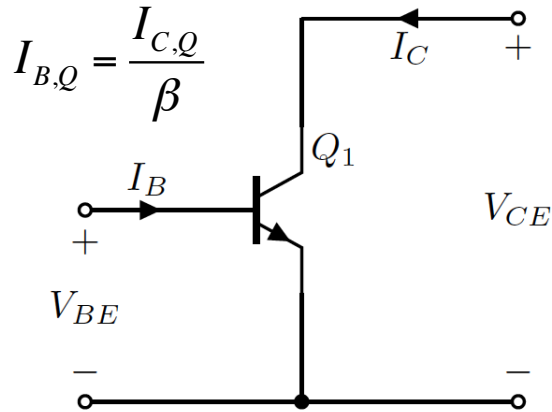
$$I_{C,Q} = I_S \left(e^{\frac{V_{BE,Q}}{V_T}} - 1 \right) \left(1 + \frac{V_{CE,Q}}{V_A} \right)$$



$$i_b = \frac{v_{be}}{r_\pi}$$

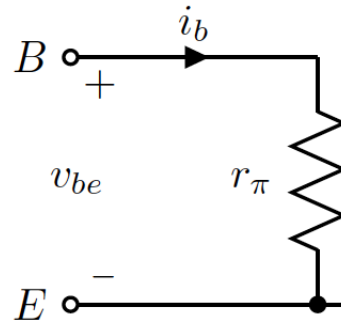

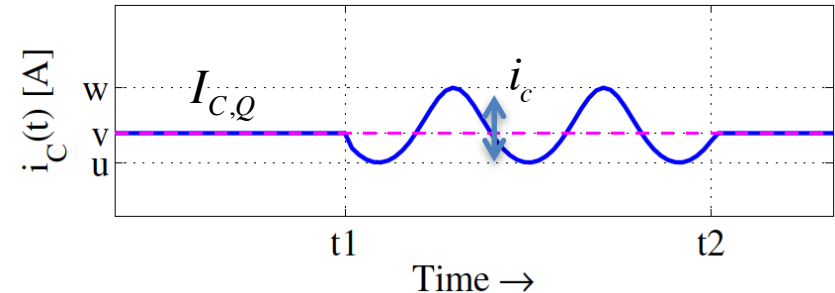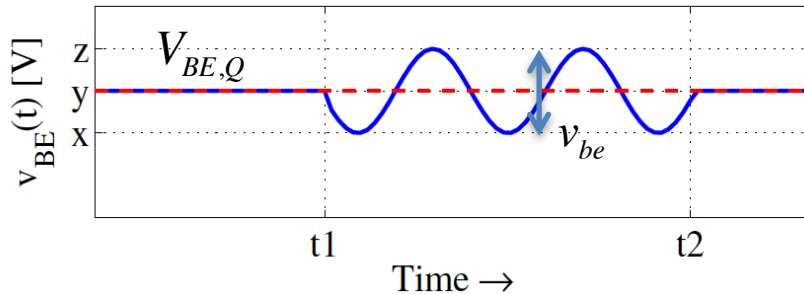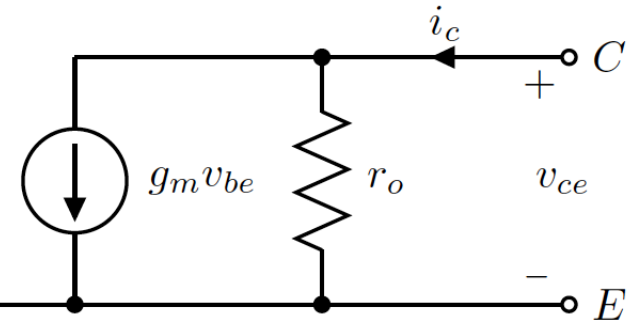
$$i_c = g_m v_{be} + \frac{v_{ce}}{r_o}$$



Small Signal Model Implications

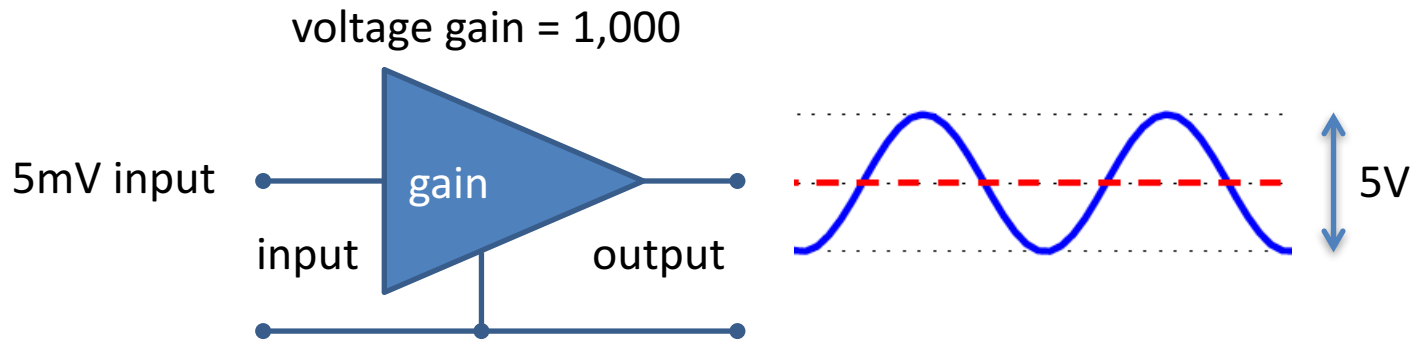- Linear relationships!
 - For small signals
- Linear circuit analysis works!
 - EEE 31 and 33 is useful after all... 😊
 - Can use **two-port network** concepts



Next Meeting

- Review of Two-Port Networks
- Single-Stage Amplifiers

