



EEE 51: Second Semester 2017 - 2018

Lecture 14

Compound Amplifiers; Review

Today

- Compound Amplifiers
 - Cascode Amplifiers
 - Operational Amplifiers




The CE-CB Amplifier (Cascode Amplifier)

- Idea: Current Reuse Biasing

→ Two stages, one bias current!

DC Analysis:

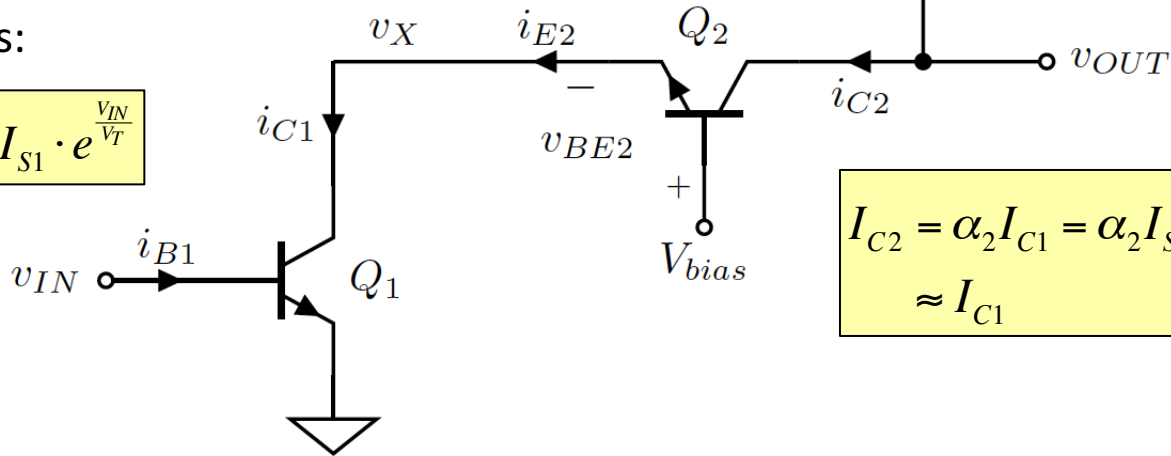
$$I_{C1} = I_{S1} \cdot e^{\frac{v_{IN}}{V_T}}$$



$$I_{C2} = \alpha_2 I_{C1} = \alpha_2 I_{S1} \cdot e^{\frac{v_{IN}}{V_T}} \approx I_{C1}$$

The CE-CB Amplifier (Cascode Amplifier)

- Small Signal Analysis

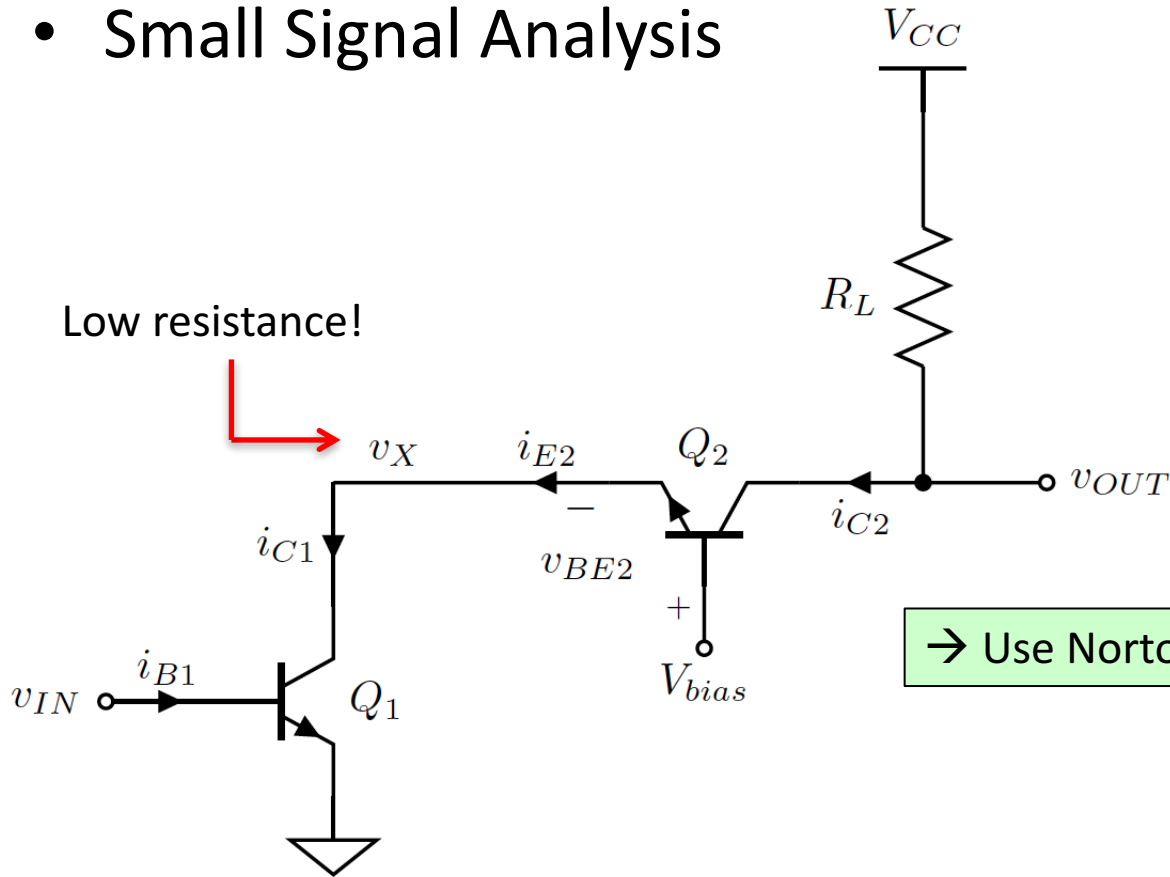

Expect:


- small voltage changes at node X
- large current flowing into the CB stage

→ Use Norton model for the CE stage

Small Signal Analysis

The CB is not unilateral!

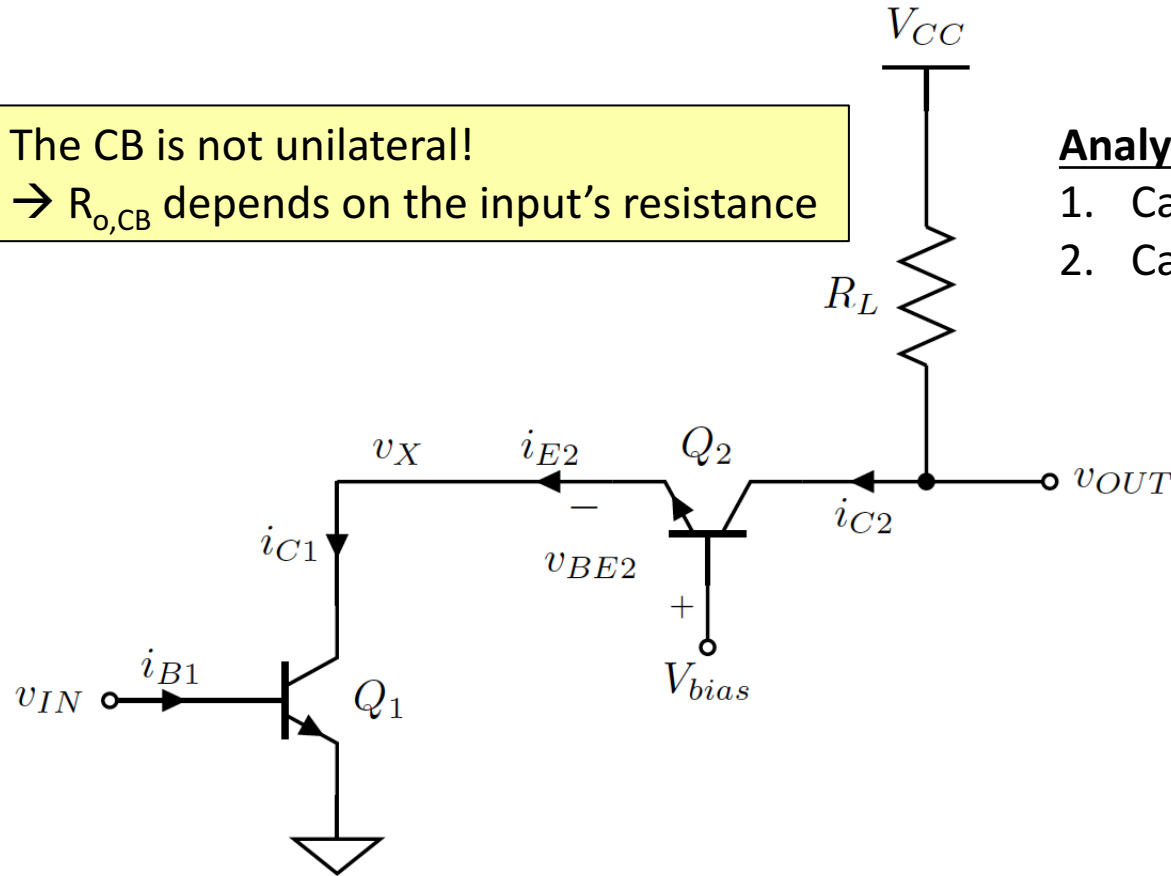→ $R_{o,CB}$ depends on the input's resistance




Analysis steps:

1. Calculate CB output resistance
2. Calculate overall transconductance

Small Signal Equivalent Circuit (1)

- Cascaded CE-CB

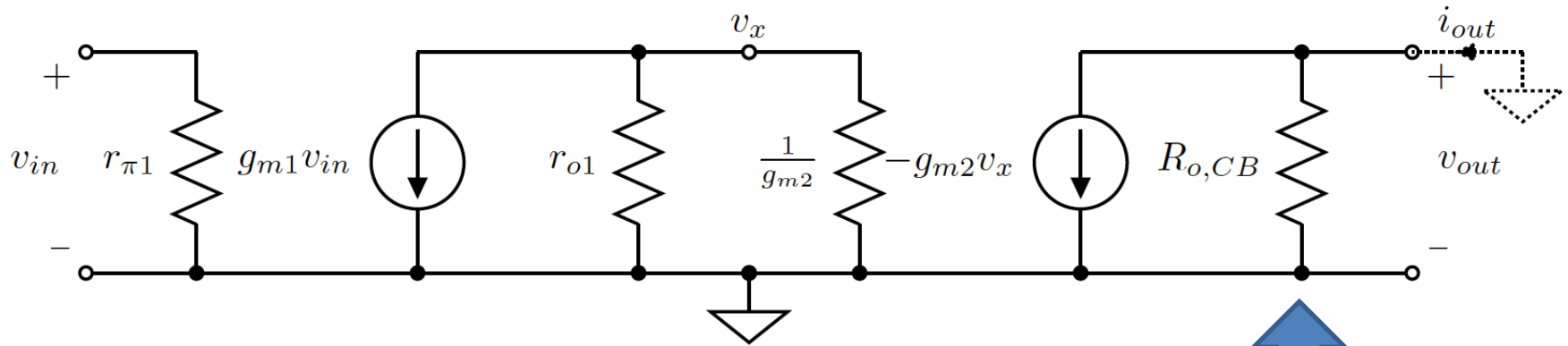


CE stage \rightarrow straightforward

We need to calculate this!



The CB Amplifier driven by a CE Amplifier


- Small signal equivalent circuit

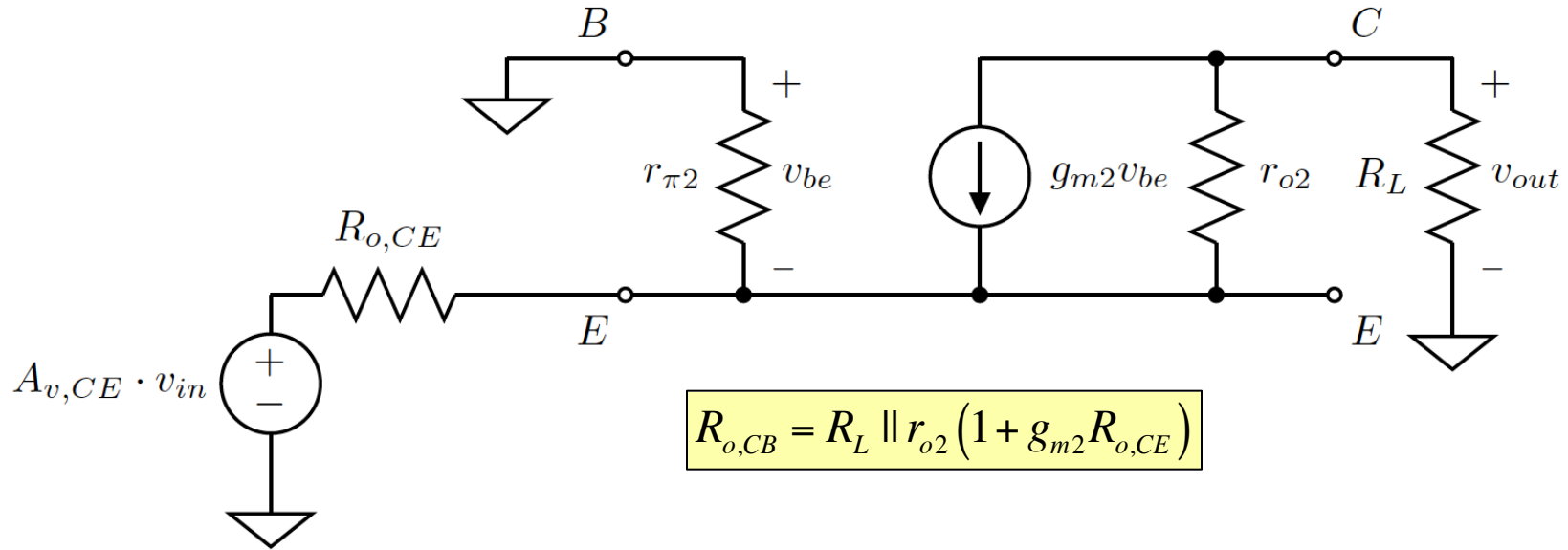

Zero out the input \rightarrow same as the emitter-degenerated circuit!

Small Signal Equivalent Circuit (2)

- Cascaded CE-CB

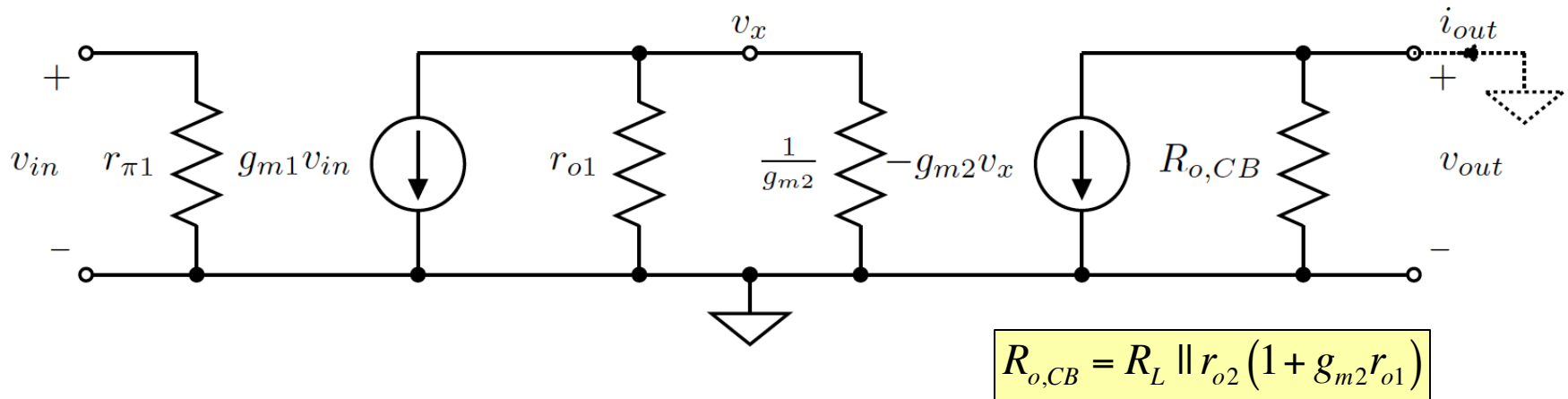


Transconductance:

$$G_{m,casc} = \frac{i_{out}}{v_{in}} = \left(-g_{m1} \cdot \left(r_{o1} \parallel \frac{1}{g_{m2}} \right) \right) \cdot (-g_{m2}) \approx g_{m1} \frac{g_{m2}}{g_{m2}} \approx g_{m1}$$

$$R_{o,CB} = R_L \parallel r_{o2} (1 + g_{m2}r_{o1})$$

Small Signal Equivalent Circuit (3)

- Cascaded CE-CB

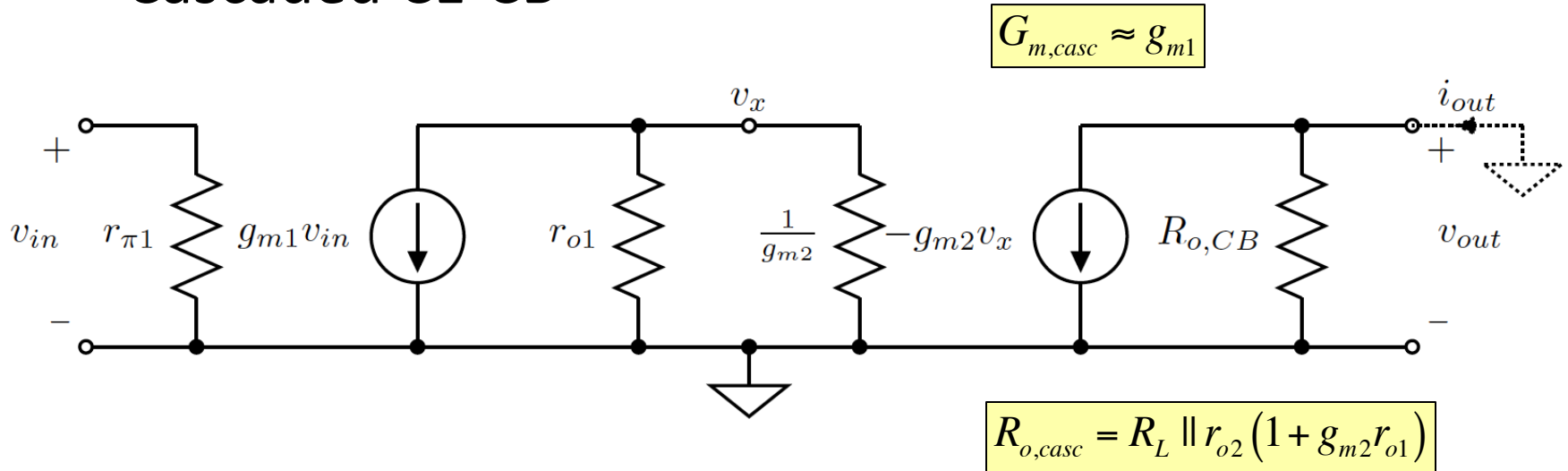


Voltage gain:

$$A_{v,casc} = -G_{m,casc} R_{o,casc} = -g_{m1} \cdot (R_L \parallel r_{o2} (1 + g_{m2} r_{o1}))$$

Small Signal Equivalent Circuit (4)


- Cascaded CE-CB

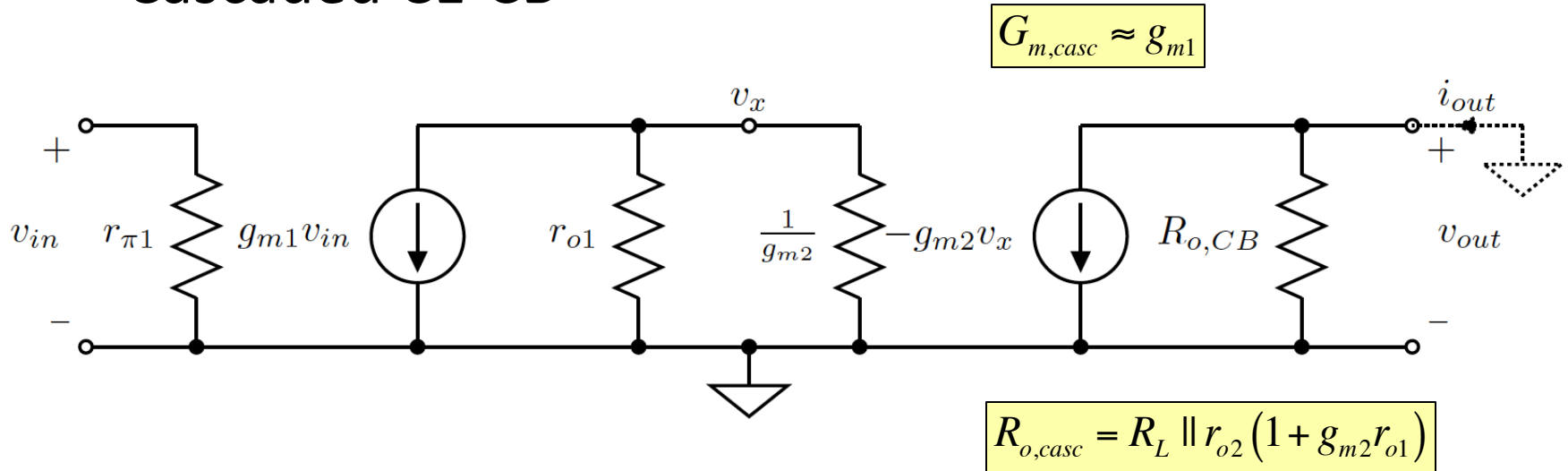

$$a_{o,casc} = -g_{m1} \cdot r_{o2} (1 + g_{m2} r_{o1}) \approx -g_{m1} r_{o1} g_{m2} r_{o2} \approx -g_m^2 r_o^2$$

Operational Amplifiers (1)

- The ideal op-amp

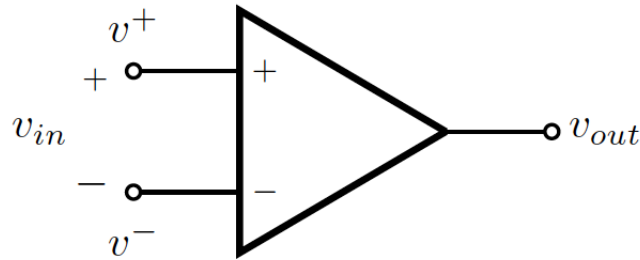

Characteristics:


1. Differential inputs
2. Single-ended output
3. Infinite gain
4. Infinite input resistance
5. Zero output resistance

Can we build an ideal op-amp?




Operational Amplifiers (2)

- Typical components

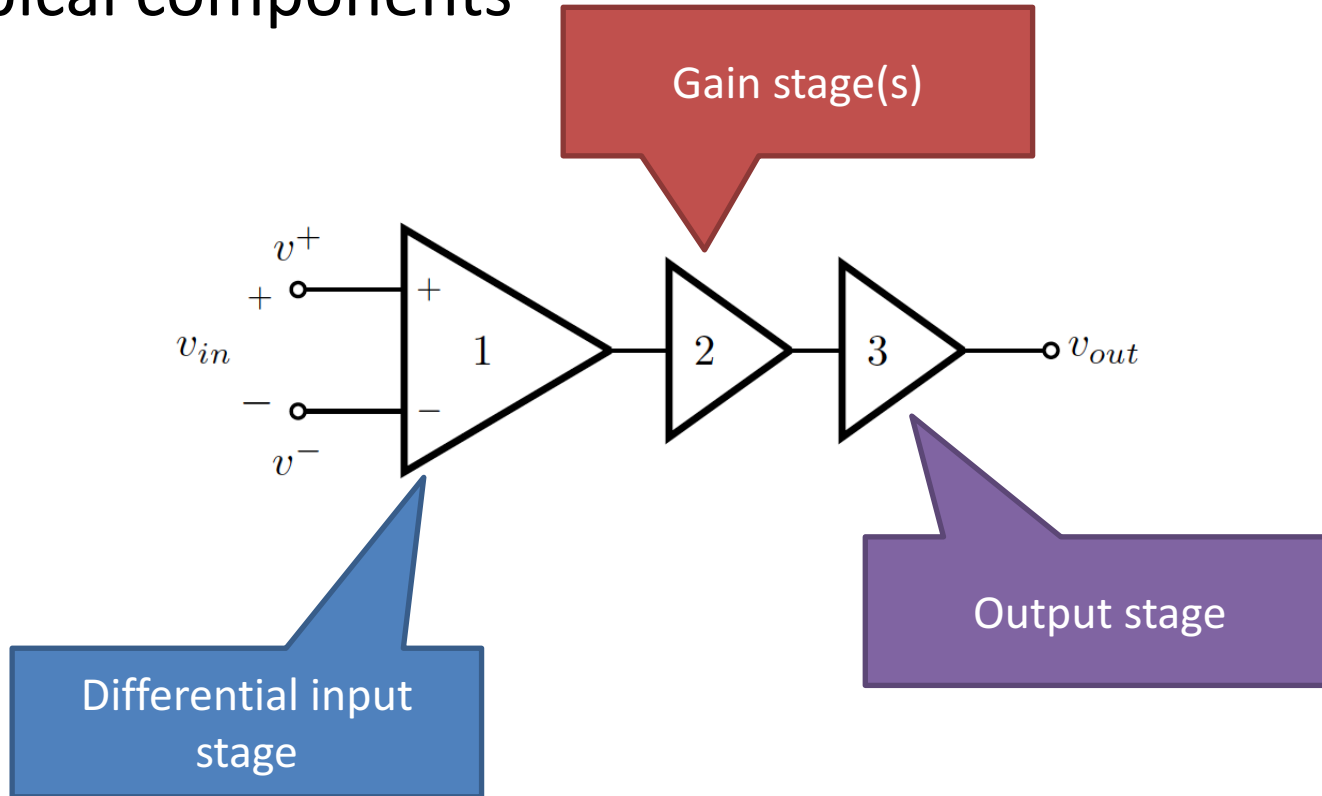

A Simple BJT Operational Amplifier

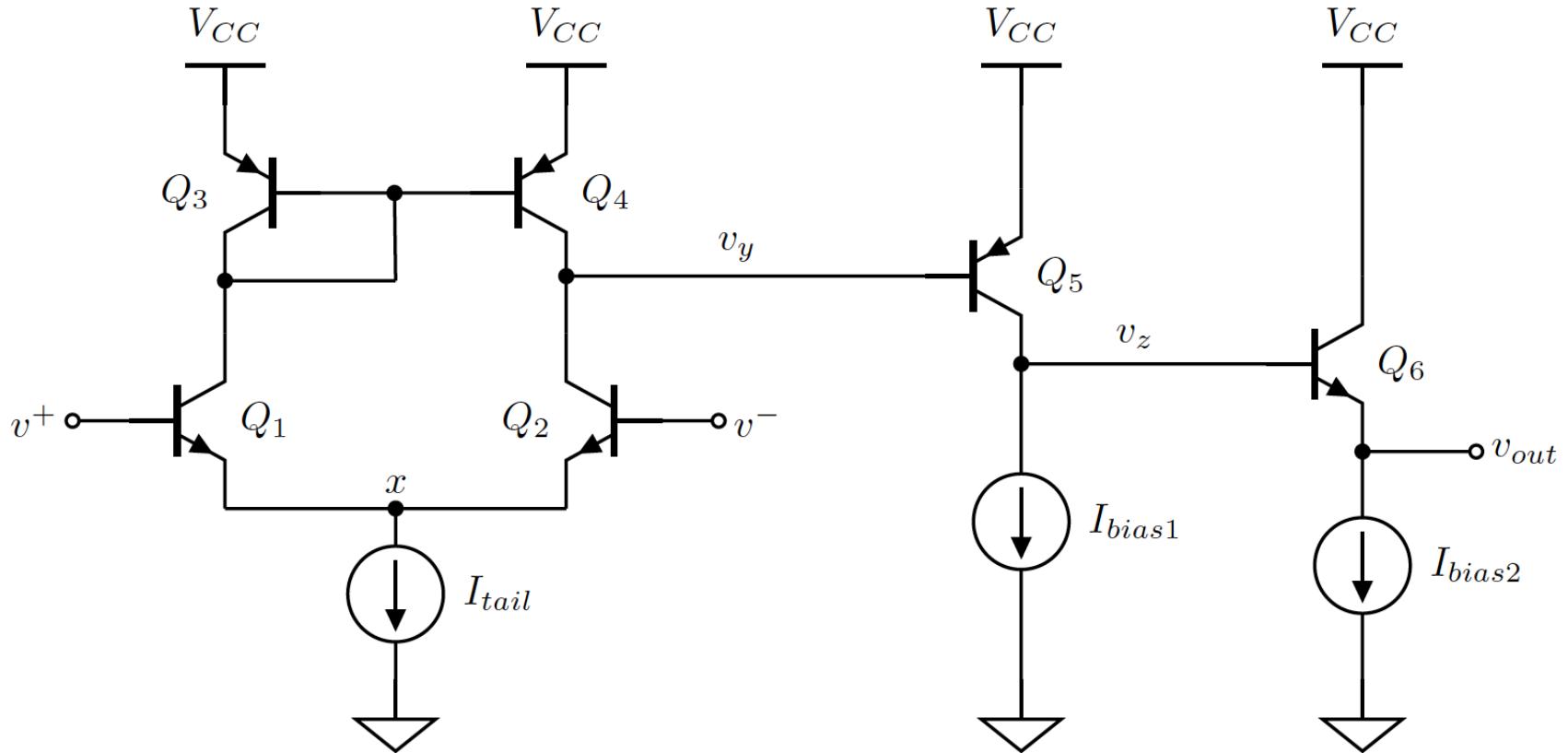



Midterm Review

Exam Coverage





- Transistor Models
 - Large signal
 - Small signal
- Amplifiers
 - Single-stage
 - Differential amplifiers
 - Compound amplifiers
- Current Sources

Midterm Exam:


- March 24, 2018
- 1pm – 4pm
- Bring a pen and calculator



Transistor Models

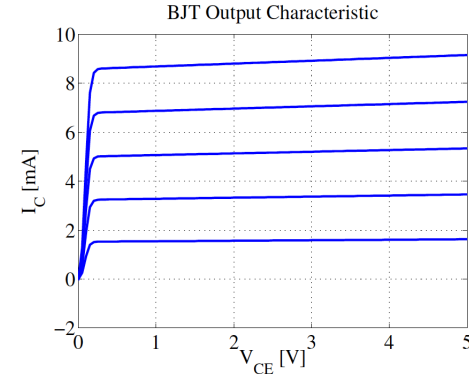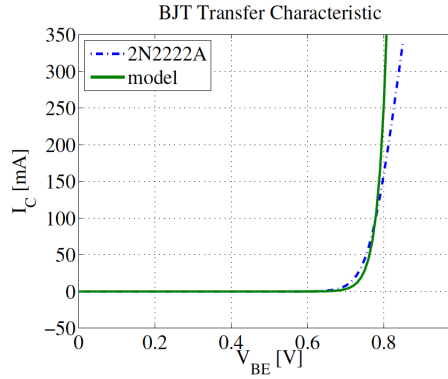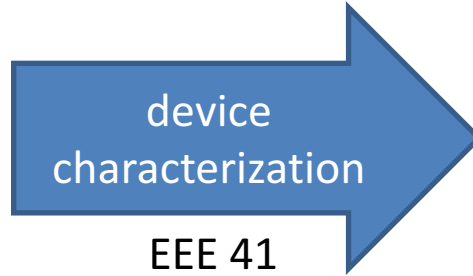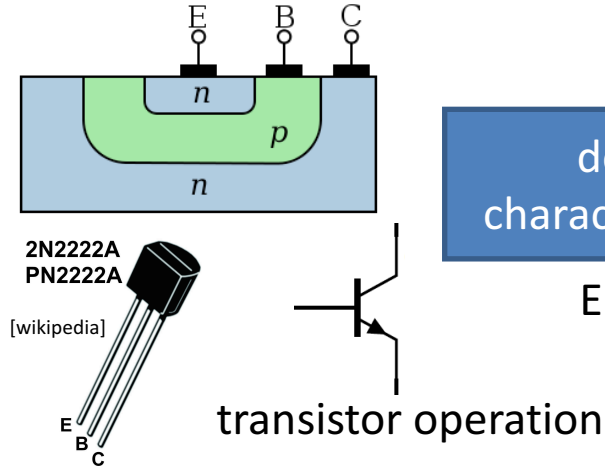


large signal terminal behavior (I-V curves)

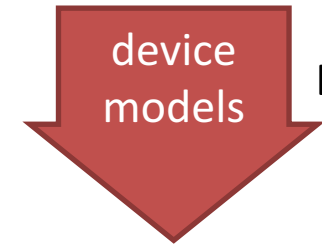

EEE 41

I-V models (large signal approximation)
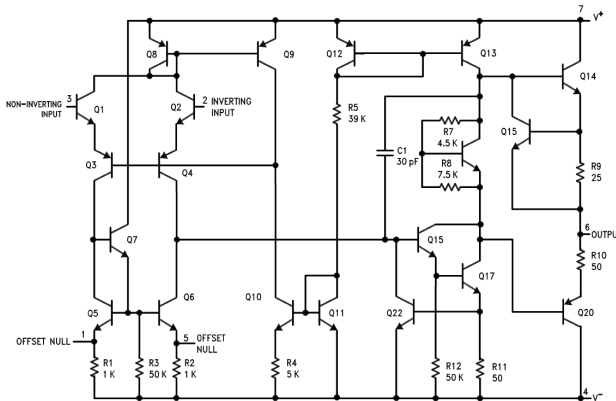
$$I_C = I_S \left(e^{\frac{V_{BE}}{V_T}} - 1 \right) \left(1 + \frac{V_{CE}}{V_A} \right) \quad I_B = \frac{1}{\beta} I_C$$



transistor circuits



Two Ways to Bridge the Gap


The complex, non-intuitive, non-extendable way...

I-V models
(**large signal** transfer,
input and output
characteristics)

$$I_C = I_S \left(e^{\frac{V_{BE}}{V_T}} - 1 \right) \left(1 + \frac{V_{CE}}{V_A} \right)$$
$$I_B = \frac{1}{\beta} I_C$$

direct application
of KCL and KVL

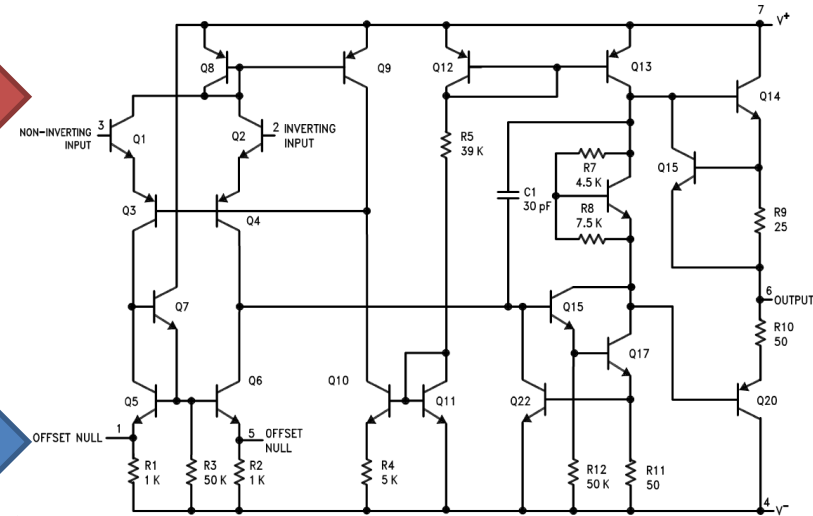linearization +
two-port network
reduction




transistor circuits

EEE 51 way (aka the fun way ☺)

- Allows us to use our EEE 31, 33 skills
- Allows us to break up large circuits into smaller ones
- Gives us more intuition in terms of circuit operation



Transistor Amplifier Analysis

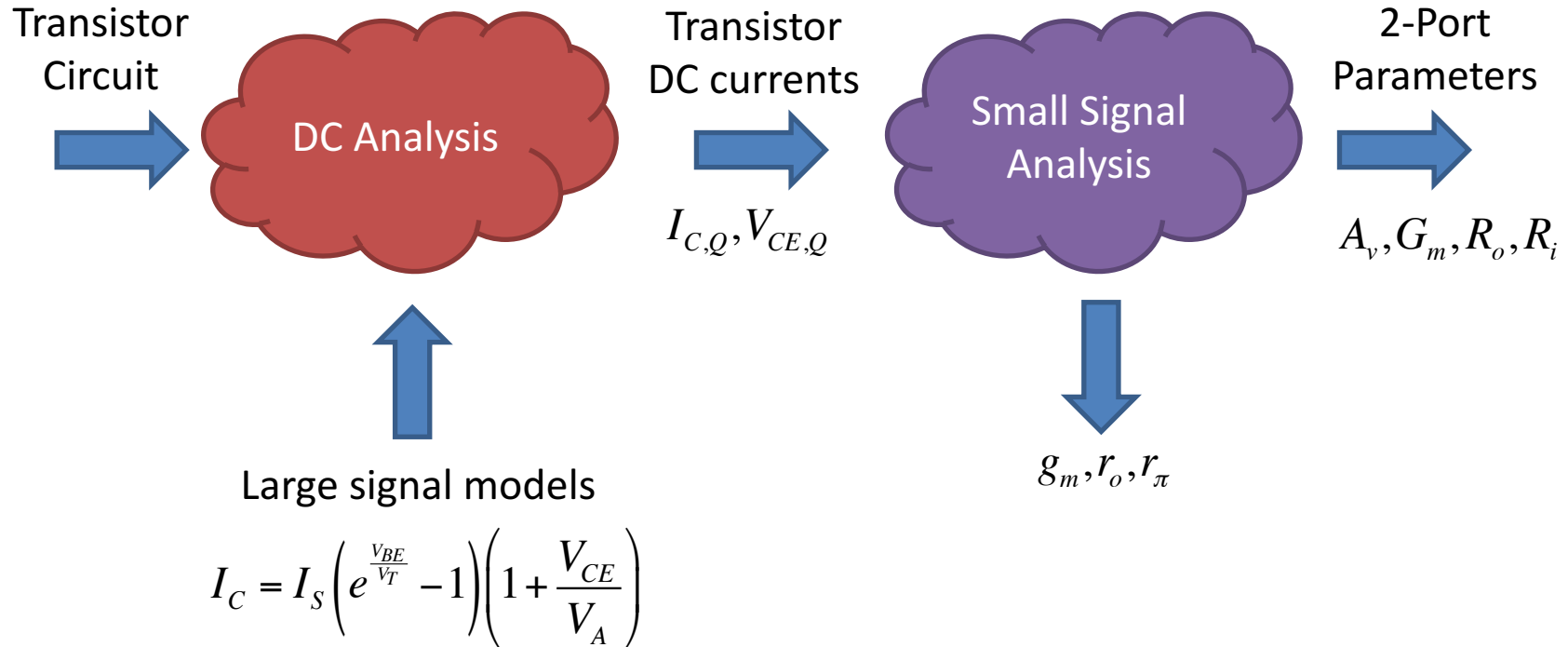


Single-Stage Amplifiers

	CE/CS	CB/CG	CC/CD
G_m	g_m	$-g_m$	$-g_m$
R_o	$r_o \parallel R_L$	$r_o \parallel R_L$	$\frac{R_L}{1 + g_m R_L}$
R_i	r_π	$\frac{1}{g_m}$	r_π
A_v	$-g_m (r_o \parallel R_L)$	$g_m (r_o \parallel R_L)$	$\frac{g_m R_L}{1 + g_m R_L}$


Can we use this diverse set of characteristics to create better amplifiers?



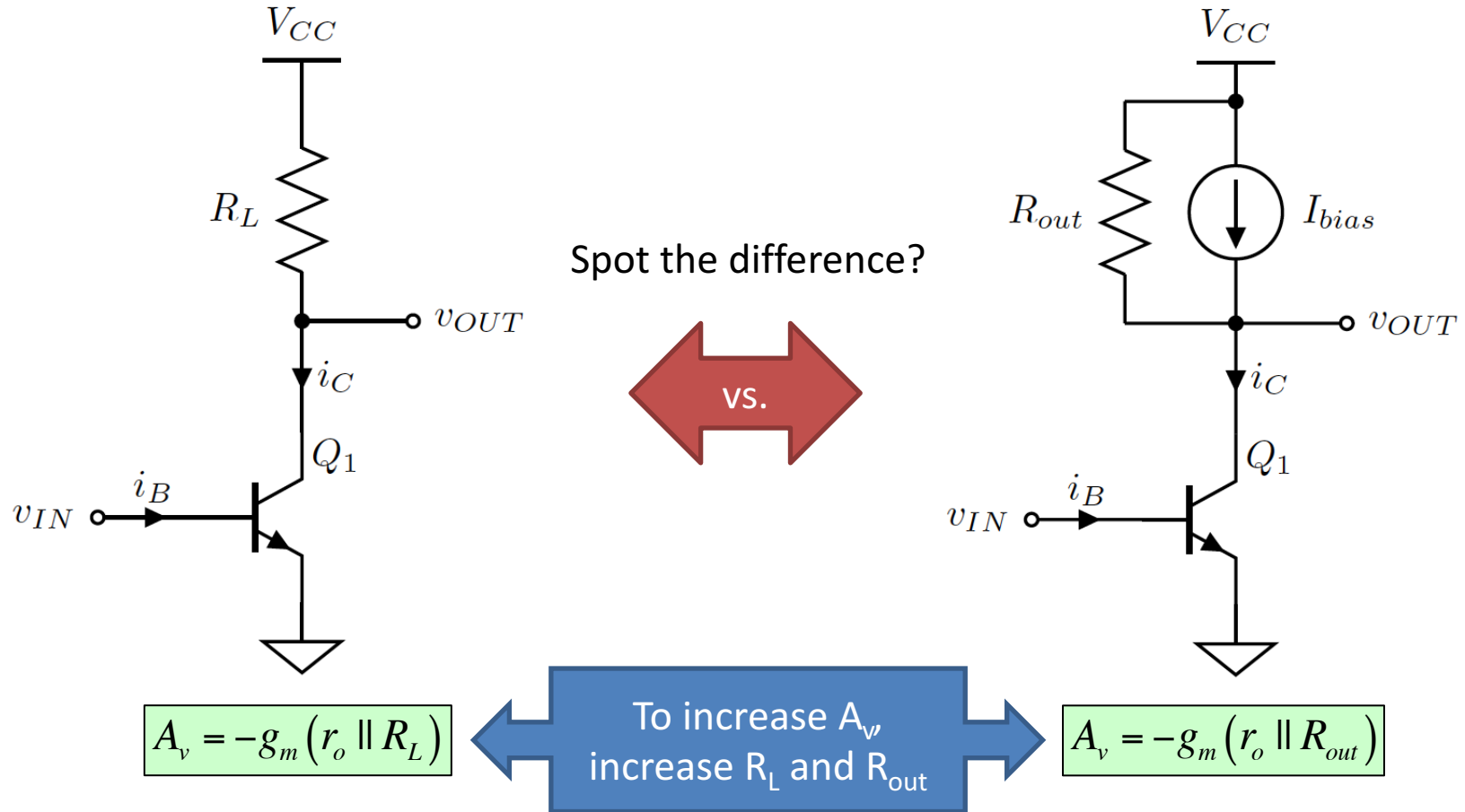Implications of Using Current Source for Biasing




A Simple BJT Current Mirror (1)

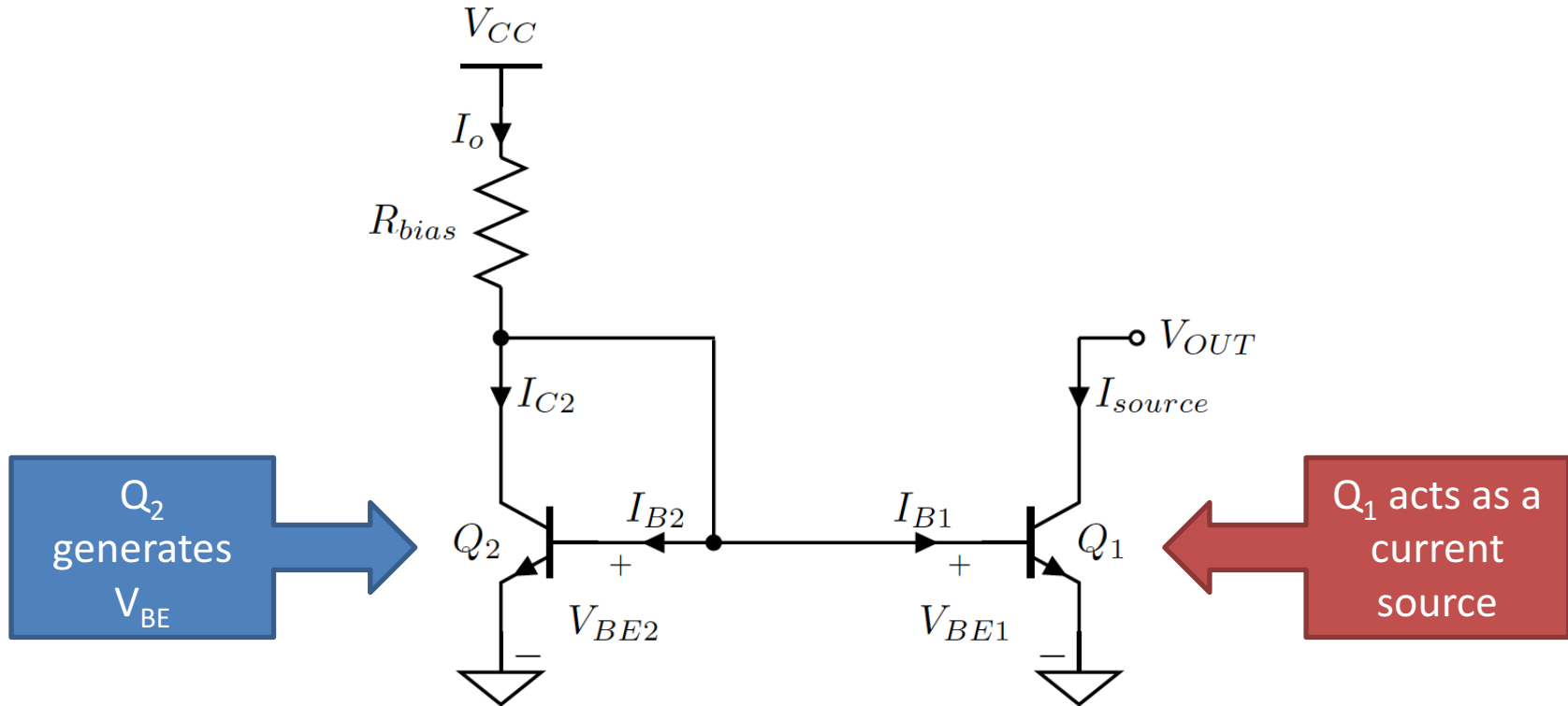

Biasing the Common-Emitter Amplifier (2)

- DC Analysis

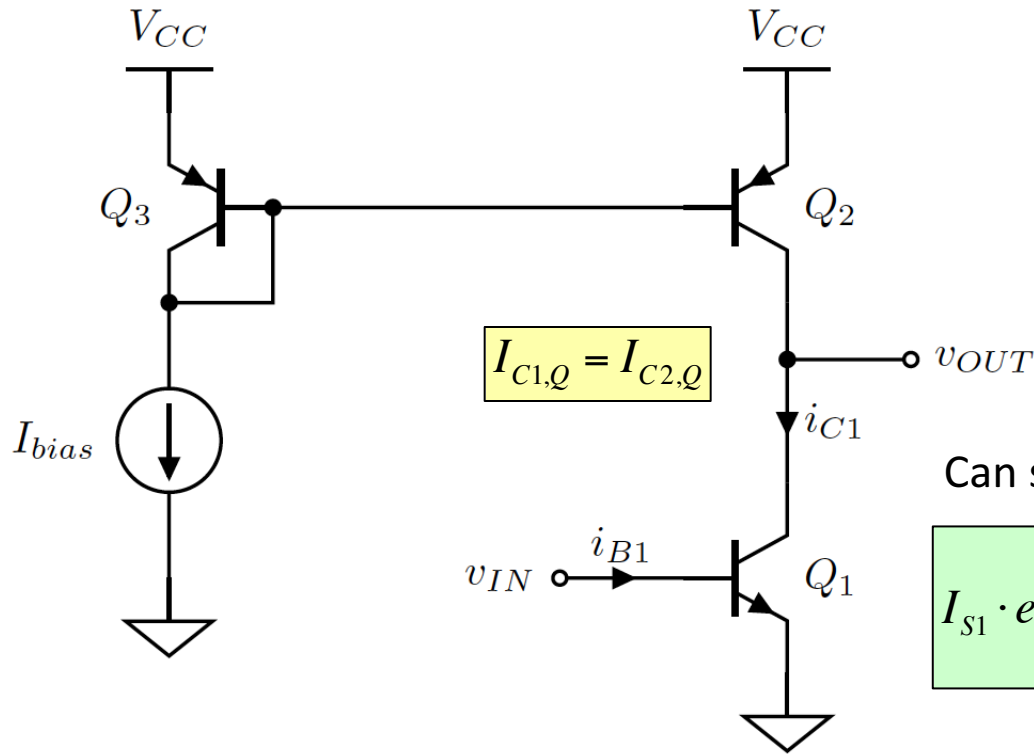

For $V_A \rightarrow \infty$:

$$I_{C,Q} \approx I_{bias}$$

What about V_{OUT} ?

→ Need finite V_A !


→ Why?

Can solve for V_{OUT} :

$$I_{S1} \cdot e^{\frac{V_{IN}}{V_T}} \cdot \left(1 + \frac{V_{OUT}}{V_{A1}}\right) = I_{S2} \cdot e^{\frac{|V_{BE2}|}{V_T}} \cdot \left(1 + \frac{|V_{CC} - V_{OUT}|}{V_{A2}}\right)$$

Biasing the Common-Emitter Amplifier (3)

- Small Signal Model

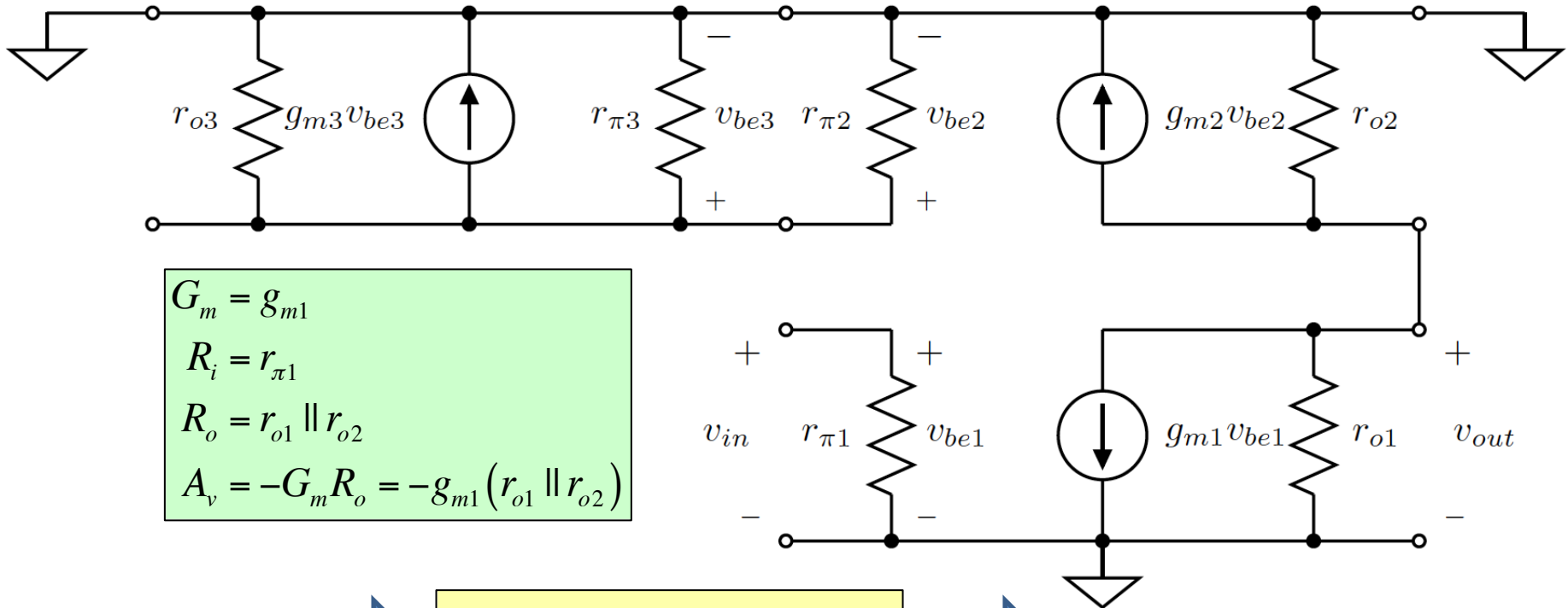




$$\begin{aligned}
 G_m &= g_{m1} \\
 R_i &= r_{\pi 1} \\
 R_o &= r_{o1} \parallel r_{o2} \\
 A_v &= -G_m R_o = -g_{m1} (r_{o1} \parallel r_{o2})
 \end{aligned}$$

If $r_{o1} \approx r_{o2}$ \Rightarrow $A_v = -g_{m1} (r_{o1} \parallel r_{o2}) \approx -\frac{g_{m1} r_{o1}}{2}$ \Rightarrow Already half a_o !




Why Use Differential Signaling? (3)

- Amplify v_{id} , reject v_{ic}

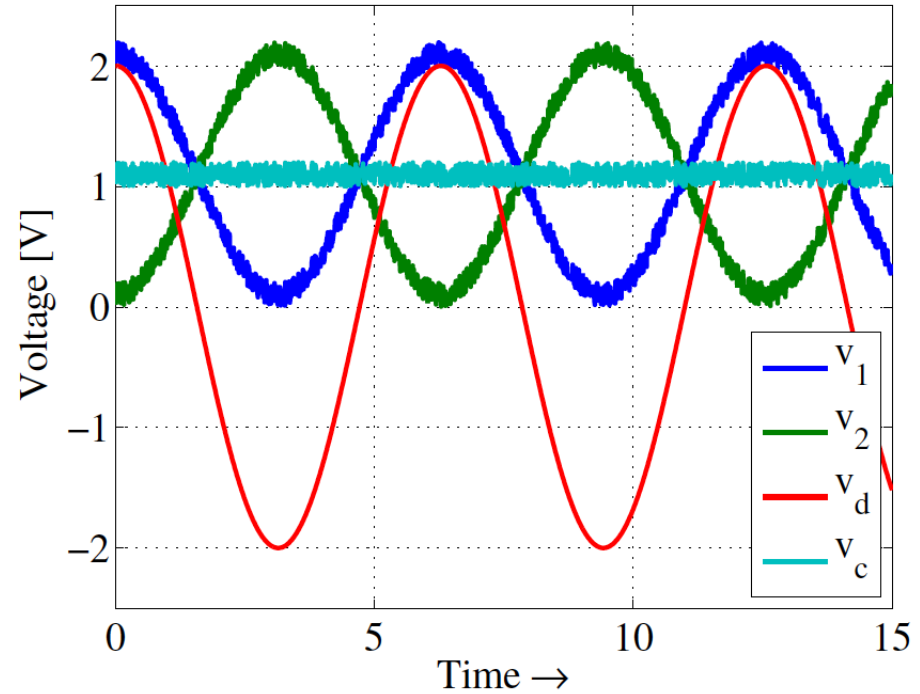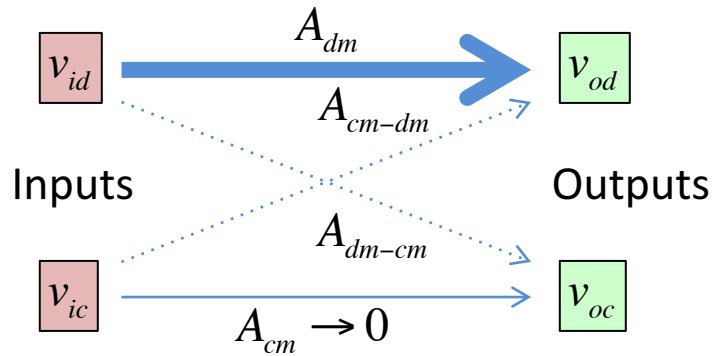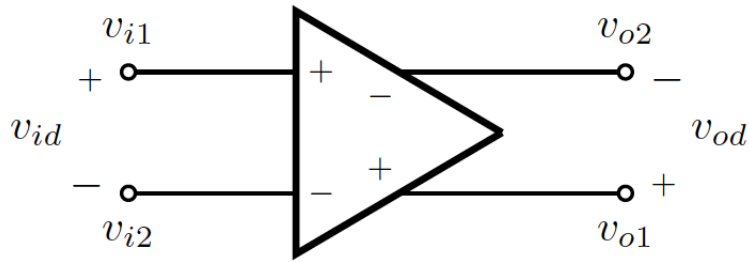



Metric:
Common-Mode
Rejection Ratio

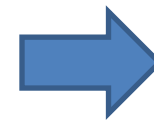

$$CMRR = \left| \frac{A_{dm}}{A_{cm}} \right|$$

Basic Building Block: The Differential Pair (5)


- Transfer Characteristic

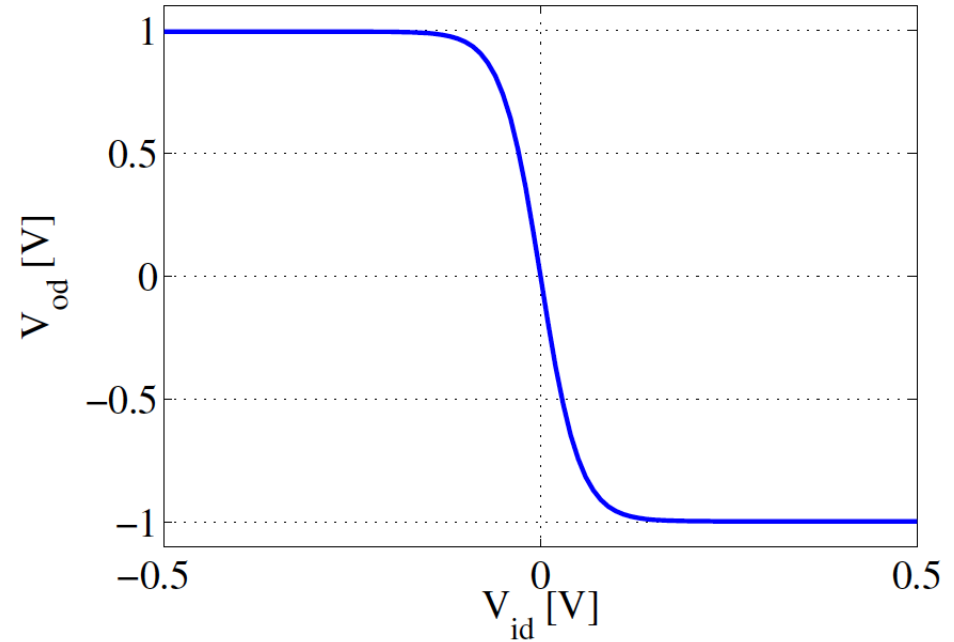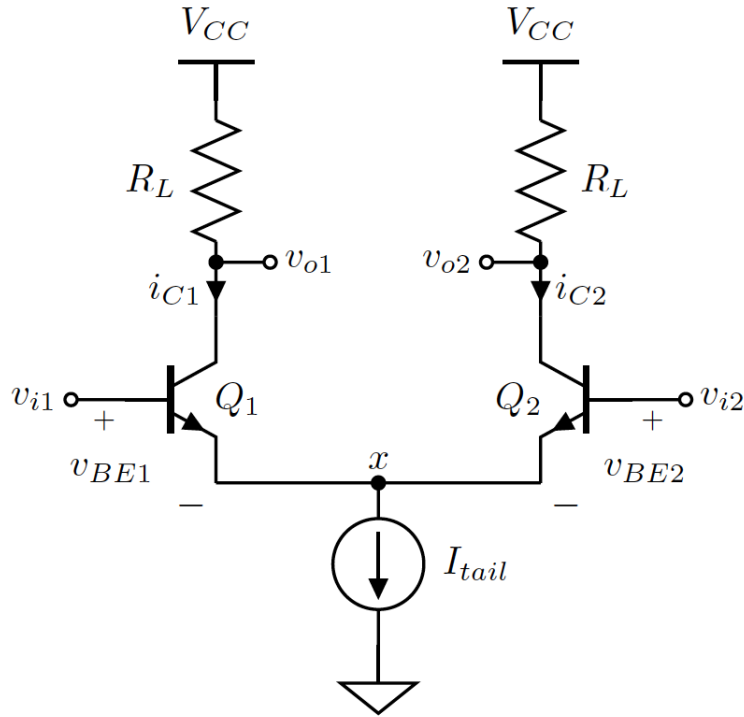

$$V_{od} = \alpha \cdot I_{tail} \cdot R_L \cdot \tanh\left(-\frac{V_{id}}{2 \cdot V_T}\right)$$


Differential vs. Common-Mode

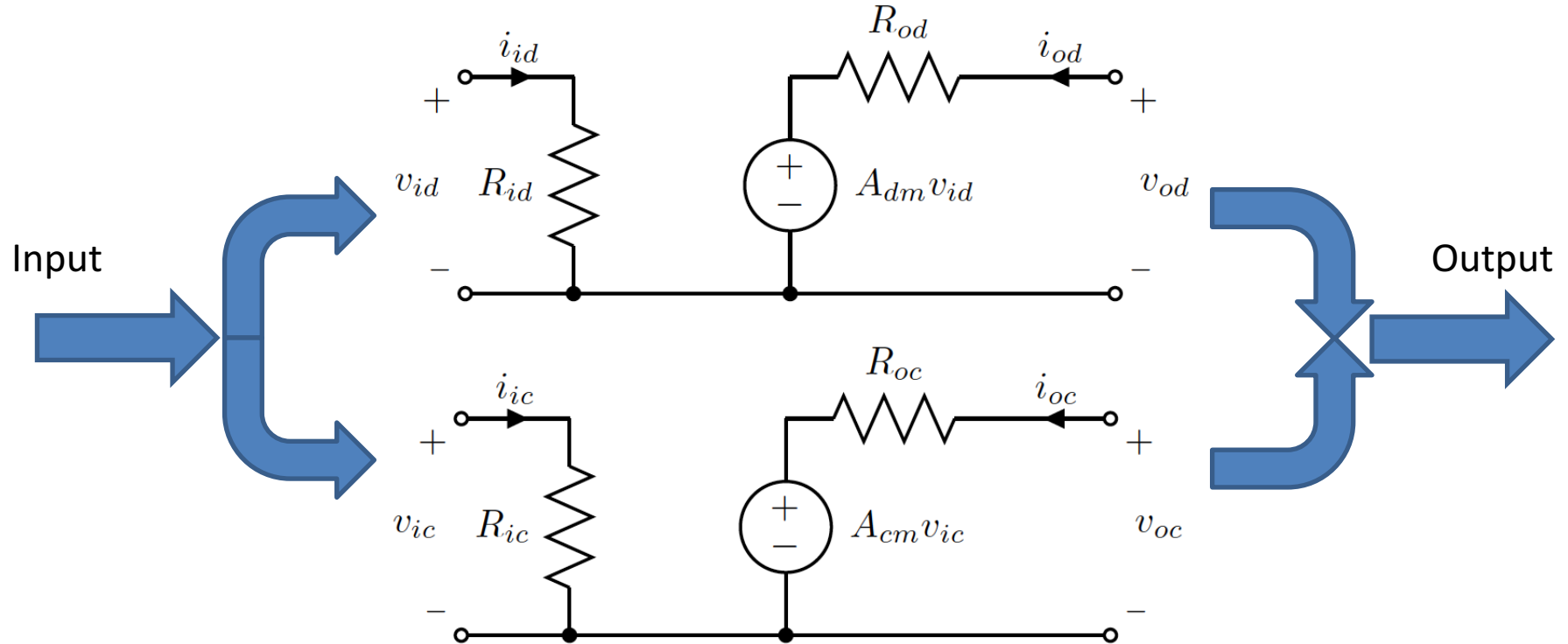- The amplifier processes the two signals differently!




Operational Amplifiers (2)

- Typical components

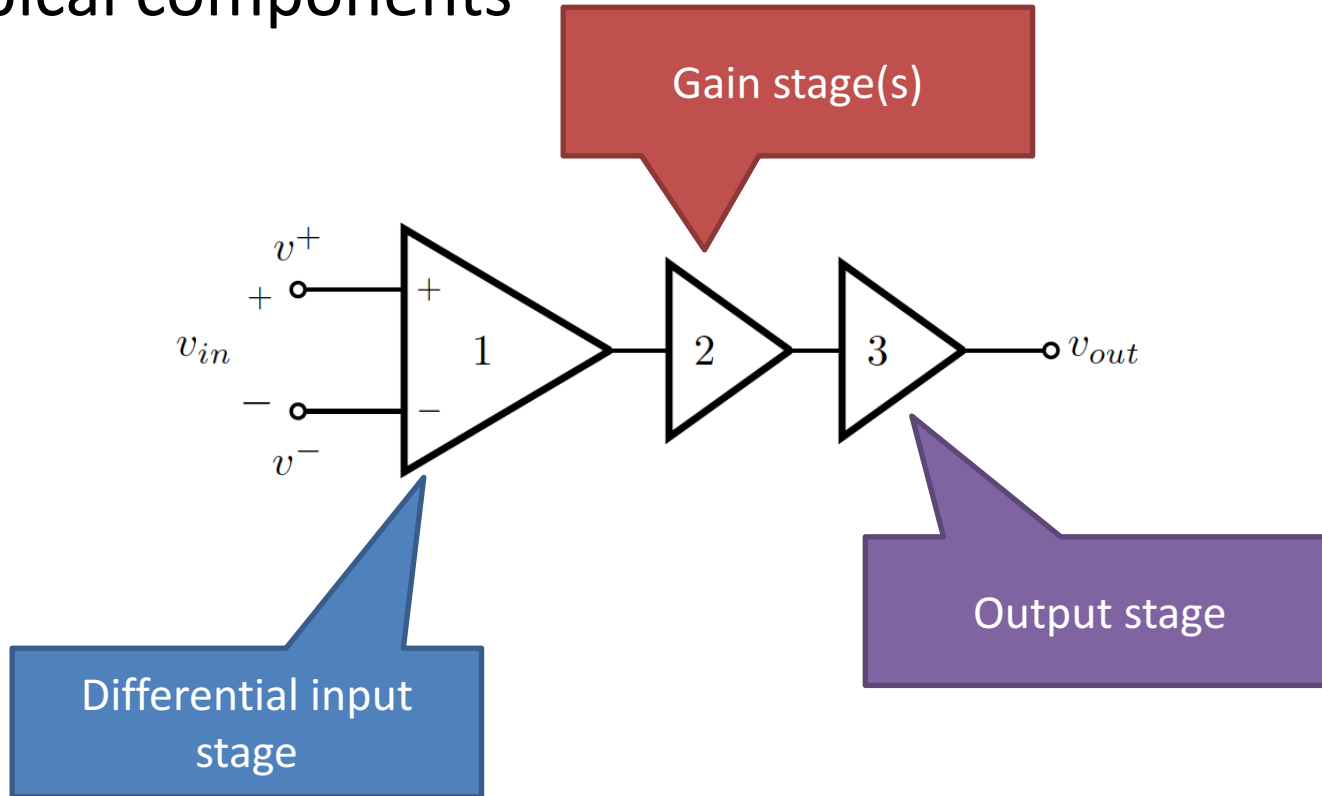

A Simple BJT Operational Amplifier

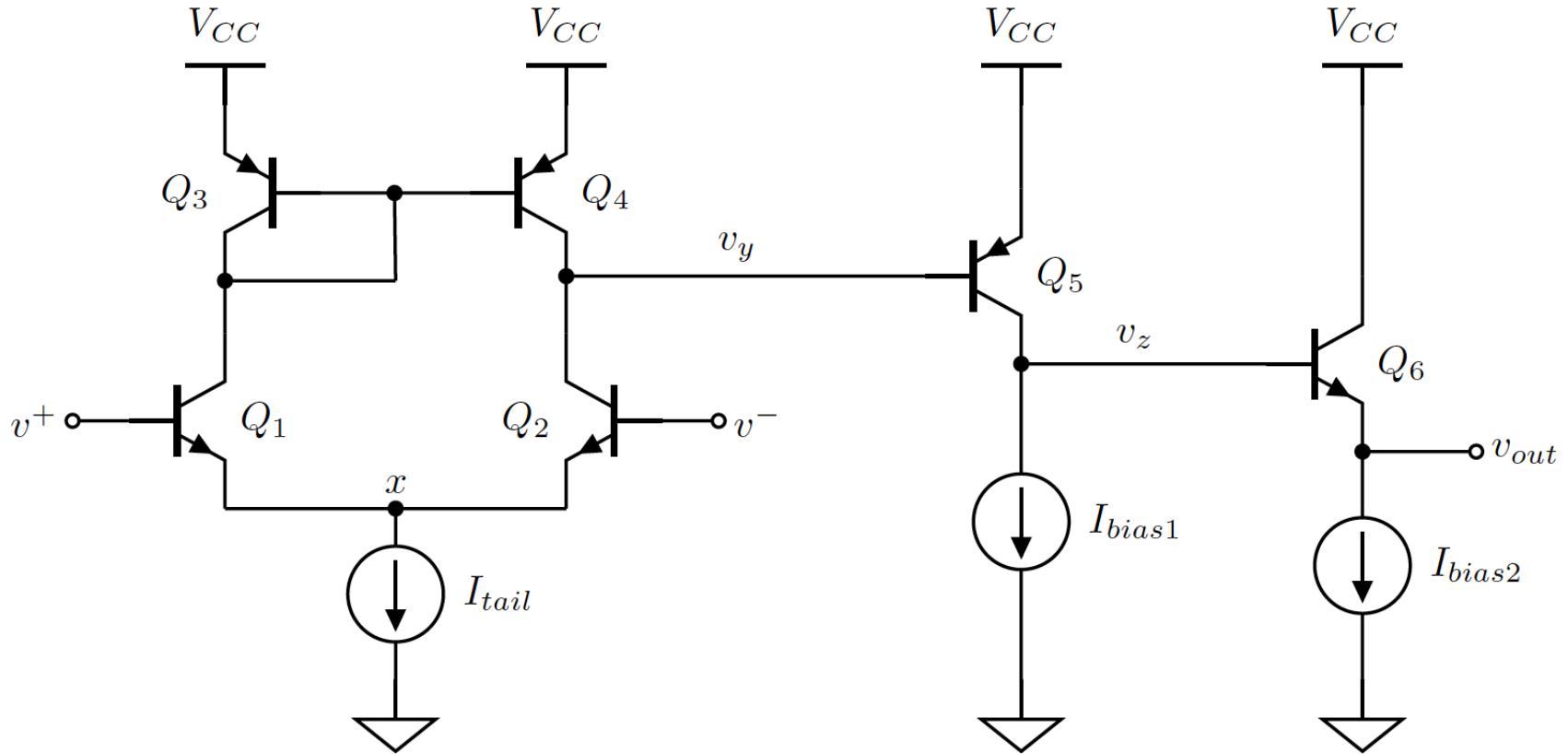

Next Meeting

- Frequency Response of Amplifiers
 - You will need to remember your EEE 35 concepts

