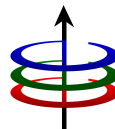


ECE 113: Communication Electronics

Meeting 4: Network Analysis I

February 4, 2019




Circuits at Low Frequencies

- Circuit dimensions are relatively small relative to its wavelength ($\lambda = \frac{c}{f}$)
 - e.g. $f = 100\text{kHz} \rightarrow \lambda = 3\text{km}$
- Voltages and Currents are defined at any point in the circuit
 - Use KVL, KCL and Ohm's Law to analyze these circuits
- Treat as interconnection of lumped passive/active elements

Circuits at High Frequencies


- Circuit dimension becomes comparable with its wavelength
 - e.g. $f = 1\text{GHz} \rightarrow \lambda = 30\text{cm}$
- Measurement of voltages and currents becomes difficult (or almost impossible)
 - Complete circuit analysis requires solving Maxwell's Equations
- It is more convenient to express our circuits (networks) in terms of traveling waves (incident and reflected waves)

Traveling Waves

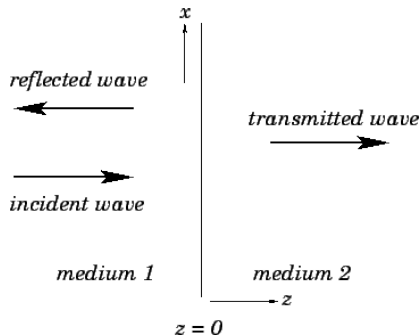

- Voltages and Currents at a specified terminal (port) can be identified as its incident/reflected wave
- At any given terminal/port n , the voltage and current is given by:
 - $V_n = V_n^+ + V_n^-$
 - $I_n = I_n^+ + I_n^-$

N-Port Network

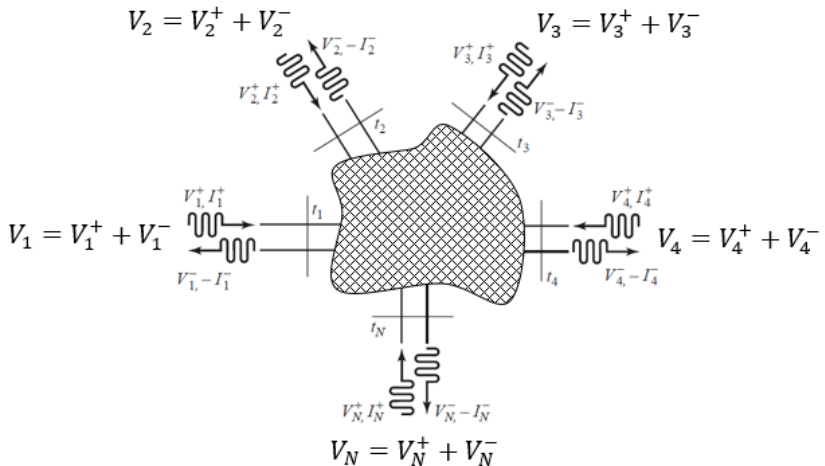

Impedance Parameters


- The impedance matrix $[Z]$ of a network relates the total voltages and currents:

$$\begin{bmatrix} V_1 \\ V_2 \\ \vdots \\ V_N \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} & \cdot & \cdot & Z_{1N} \\ Z_{21} & Z_{22} & \cdot & \cdot & \cdot \\ \cdot & \cdot & \cdot & \cdot & \cdot \\ \cdot & \cdot & \cdot & \cdot & \cdot \\ Z_{N1} & \cdot & \cdot & \cdot & Z_{NN} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ \cdot \\ \cdot \\ I_N \end{bmatrix}$$

- In matrix notation

$$[V]_{N \times 1} = [Z]_{N \times N} [I]_{N \times 1}$$

Z-matrix Elements

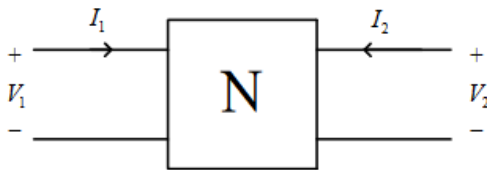

- The elements of the Z-matrix Z_{ij} can be evaluated:

$$Z_{ij} = \frac{V_i}{I_j} \Big|_{I_k=0 \text{ for } k \neq j}$$

- Drive port **j** with current I_j , open circuit all other ports, and measure the open circuit voltage at port **i**.

Admittance Parameters


- The admittance matrix $[Y]$ of a network relates the total voltages and currents

$$\begin{bmatrix} I_1 \\ I_2 \\ \vdots \\ I_N \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} & \cdot & \cdot & Y_{1N} \\ Y_{21} & Y_{22} & \cdot & \cdot & \cdot \\ \cdot & \cdot & \cdot & \cdot & \cdot \\ \cdot & \cdot & \cdot & \cdot & \cdot \\ Y_{N1} & \cdot & \cdot & \cdot & Y_{NN} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ \cdot \\ \cdot \\ V_N \end{bmatrix}$$

- In matrix notation

$$[I]_{N \times 1} = [Y]_{N \times N} [V]_{N \times 1}$$

Y-matrix Elements

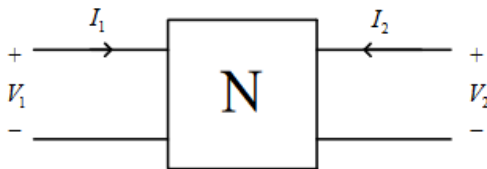

- The elements of the Y-matrix Y_{ij} can be evaluated:

$$Y_{ij} = \frac{I_i}{V_j} \big|_{V_k=0 \text{ for } k \neq j}$$

- Drive port **j** with voltage V_j , short circuit all other ports, and measure the short circuit current at port **i**.

Z and Y Parameters

- Elements of the Z and Y matrices are complex
- Z and Y matrices are inverse of each other: $[Y] = [Z]^{-1}$
- For an N-port network, Y and Z matrices are $N \times N$ in size
 - N^2 independent quantities that characterize an arbitrary N-port network
- # of independent parameters are reduced for special cases
 - Reciprocal and Lossless Networks

Reciprocal Network

- A reciprocal network is a network that does not contain any non-reciprocal (or non-linear) media
 - passive and contains only isotropic materials
 - Results in a **symmetric** matrix

$$Z_{ij} = Z_{ji}$$


$$Y_{ij} = Y_{ji}$$

Lossless Network

- A lossless network is a network with no elements that introduce loss
 - No power is dissipated (i.e. converted to heat or radiation)
 - Results in a purely imaginary matrix

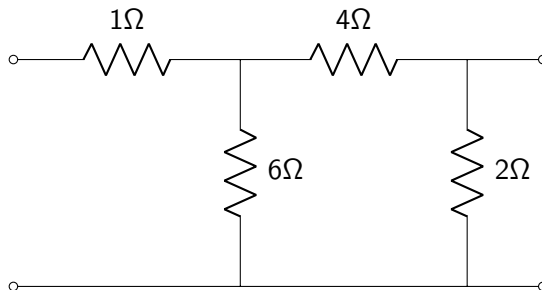Example

- Determine the impedance parameter of the following 2-port network



$$Z = \begin{bmatrix} 4 & 1 \\ 1 & 1.667 \end{bmatrix}$$

Two-Port Networks

- Specialized case of N-port Networks
- Parameter matrices formed are 2×2
- Most RF/Microwave networks are cascaded two-port networks


Transmission Parameters

- Only applicable to two-port networks

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

- Note the direction of I_2
 - opposite direction of current with respect to conventional two-port representations
- relates Port 1 to Port 2

ABCD Matrix Elements

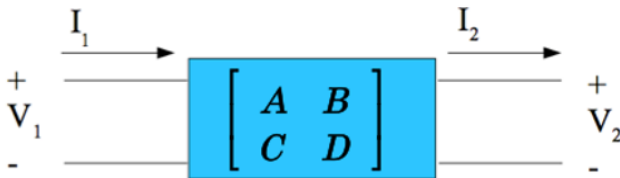

- The elements of the ABCD matrix can be evaluated:


$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0}$$

$$B = \left. \frac{V_1}{I_2} \right|_{V_2=0}$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0}$$

$$D = \left. \frac{I_1}{I_2} \right|_{V_2=0}$$

Cascaded Networks

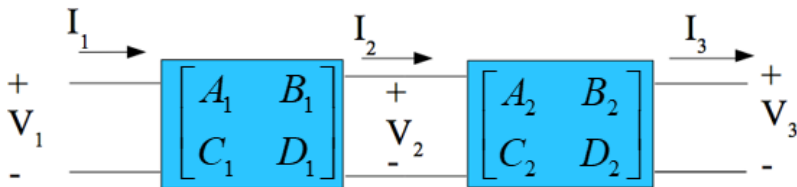


$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

$$\begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} V_3 \\ I_3 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} V_3 \\ I_3 \end{bmatrix}$$

Cascaded Networks

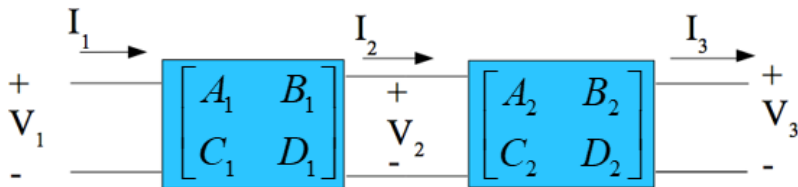

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$


$$\begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} V_3 \\ I_3 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} V_3 \\ I_3 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_1 A_2 + B_1 C_2 & A_1 B_2 + B_1 D_2 \\ C_1 A_2 + D_1 C_2 & C_1 B_2 + D_1 D_2 \end{bmatrix} \begin{bmatrix} V_3 \\ I_3 \end{bmatrix}$$

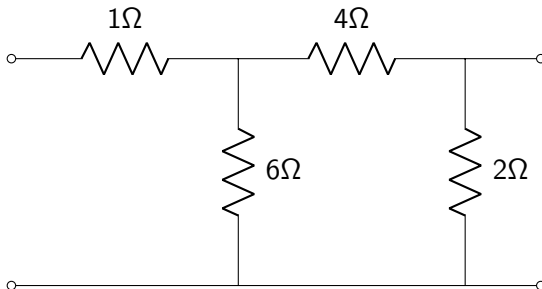Example

- Determine the ABCD parameter of the following 2-port network




END

Consider 2 networks that are cascaded together.

Network A

$$S = \begin{bmatrix} 0 & 0.89 \\ 0.89 & 0 \end{bmatrix}$$

Network B

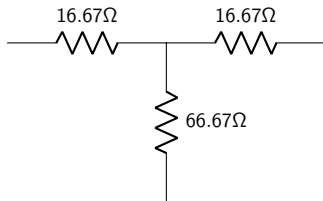

- 1 Obtain the S-parameters for Network B.
- 2 Derive the cascaded S-parameters.
- 3 Describe the function of each network and how it relates to the cascaded network.