

EEE 51 Assignment 2

2nd Semester SY 2018-2019

Due: 5pm Tuesday, February 12, 2019 (Rm. 220)

Instructions: Write legibly. Show all solutions and state all assumptions. Write your full name, student number, and section at the upper-right corner of each page. Start each problem on a new sheet of paper. Box or encircle your final answer.

Answer sheets should be color coded according to your lecture section. The color scheme is as follows:

THQ – yellow
THU – white
WFX – pink

1. Common Collector/Emitter Follower Sziklai Pair.

Figure 1 shows a Sziklai pair used as an emitter follower. The capacitor C_C is just an AC coupling capacitor (open circuit at DC and shorted at AC, the value is irrelevant as of now). For both of the transistors Q_1 and Q_2 , $|V_{be,on}| = 0.65$ V, $|V_{ce,sat}| = 0.2$ V, and $|V_A| \rightarrow \infty$. Moreover, $\beta_1 = 50$ for Q_1 and $\beta_2 = 100$ for Q_2 . The transistors are biased such that the voltage at node B is $V_B = 1.85$ V. Answer the following questions. **DO NOT ASSUME THAT $I_C = I_E$.** Round all of your answers to one (1) decimal place only and use the appropriate unit of measure.

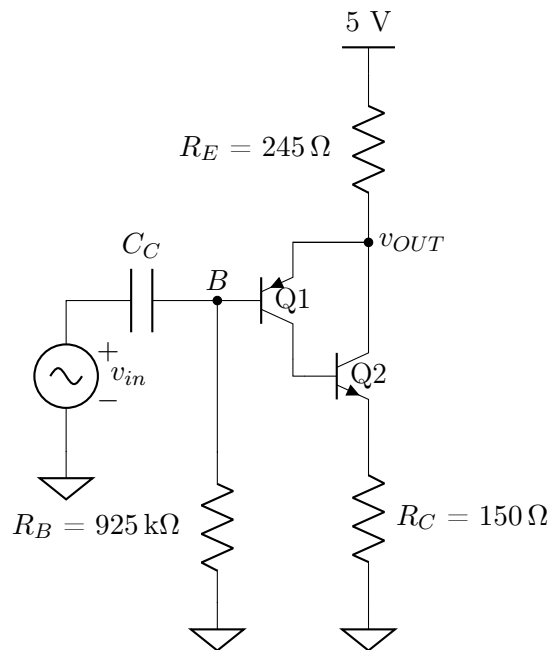


Figure 1: Emitter Follower Sziklai Pair

- Calculate the value of the base current of Q_1 I_{B1} and the emitter current of Q_2 I_{E2} . If I_{E2} is treated as the collector current of the transistor pair, what is the overall current gain β_{SZ} ? (3 pts)
- Determine the value of the DC voltage at the output node. (1 pt)
- Draw the small-signal model of the circuit. Label the transistor terminals, small-signal parameters, external resistors, and their values. (2 pts)
- Find the values of the overall input resistance R_{IN} , transconductance G_M , gain A_V , and output resistance R_O of the whole emitter follower. You may draw additional schematics/diagrams to aid in your solutions. (4 pts)

2. Common Emitter Amplifier with Load.

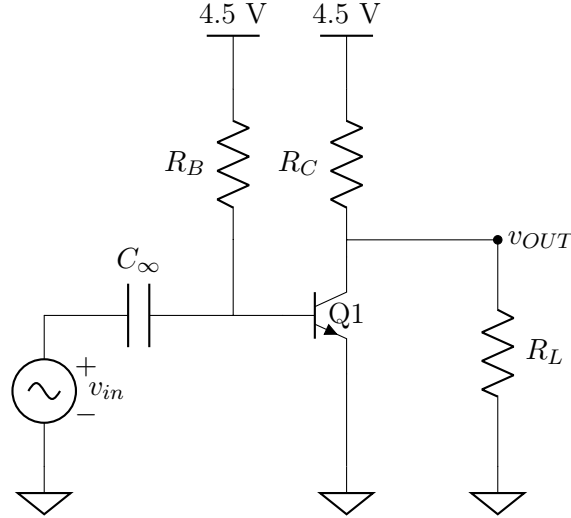


Figure 2: Common Emitter with biasing

Assume $T=300K$ when necessary. For the CE amplifier in fig. 2 with $V_{BE,on} = 0.7V$, $V_{CE,sat} = 0.7V$, $\beta = 200$, $V_A = 100V$, $R_B = 95K\Omega$, $R_C = 204\Omega$, and $R_L = 794\Omega$:

- Calculate the DC biasing parameters:
 - base current (I_B) (0.5 pt)
 - collector current (I_C) (0.5 pt)
 - output voltage (V_{OUT}) (1 pt)
- Draw the small-signal model of the circuit. You may omit R_B . Label the values of each small-signal parameter, and component. (3 pts)
- Compare (a) R_{O1} = parallel combination of r_o , R_C and R_L , with (b) R_{O2} = parallel combination of R_C and R_L . Would r_o significantly affect the effective resistance? How much error relative to R_{O1} would you get, if you simply used R_{O2} rather than R_{O1} to simplify your calculations? Express this number as a percentage. (1.5 pts)
- Calculate the small-signal gain (v_{out}/v_{in}) (1 pt)
- Sketch v_{out} from 0 ms to 2 ms for $v_{in} = 10\sin(2\pi ft)$ mV with $f = 1KHz$. Label the peak voltages, axes, and units. (1.5 pts)
- Should you expect the amplifier to work linearly, with the same gain for $v_{in} = 52\sin(2\pi ft)$ mV, with $f = 1KHz$? Why or why not? Prove mathematically. [Hint: You may revisit the Taylor series expansion of i_C .] (1 pts)

3. MOS Common Source and Common Gate Cascode.

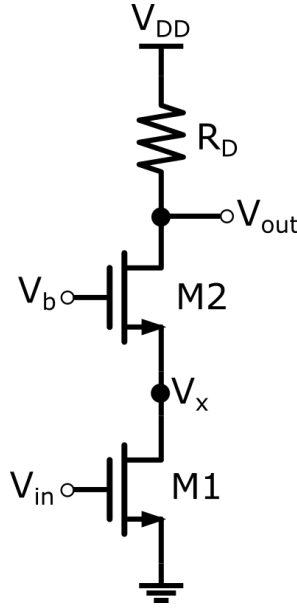


Figure 3: CS-CG Cascode

Consider the circuit shown above. For this problem, use $V_{DD} = 3V$, $I_{D1} = I_{D2} = 1mA$, $k_{M1} = 6.7m\frac{A}{V^2}$, $k_{M2} = 1.4m\frac{A}{V^2}$, $V_{TH1} = V_{TH2} = 0.7V$, $\lambda_{M1} = \lambda_{M2} = 0.1V^{-1}$ and $R_D = 1.5k\Omega$. Express your answers to four (4) decimal places and use the appropriate unit of measure.

- Determine the minimum voltage, V_x , needed to keep M1 in saturation. (1 pt)
- Choose the bias voltage, V_b such that M1 is $50mV$ away from the linear region of operation. (1 pt)
- Draw the small-signal equivalent model of the circuit. Label the transistor terminals, the transistor small-signal parameters and their values. (2 pts)
- Calculate for the overall transconductance, G_m , and output impedance, R_{out} . (5 pts)
- Calculate the small-signal voltage gain. (1 pt)

TOTAL: 30 points.