


# **Lecture**

## Unbalanced Three Phase Systems and Three Phase Power Measurement

### **Agenda**
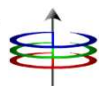
### **Lecture Agenda**

R.D. del Mundo  
Ivan B.N.C. Cruz  
Christian. A. Yap



**Electrical and Electronics Engineering Institute**  
**University of the Philippines**

R. D. del Mundo  
EEE 103 AY2010-11 S2

# How do we measure power?




Real

Reactive power

Limitation

Sensors can only

Real Power

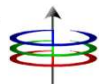


**Electrical and Electronics Engineering Institute**  
**University of the Philippines**

R. D. del Mundo  
EEE 103 AY2010-11 S2

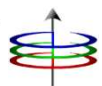
# Lecture Outcomes

at the end of the lecture, the student must be able to ...

- Define what makes a Three Phase system unbalanced.
- Outline how a single-phase wattmeter can be used for single-phase and three phase power measurements.



# UNBALANCED THREE-PHASE SYSTEMS

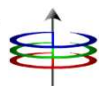


**Electrical and Electronics Engineering Institute**  
**University of the Philippines**

**R. D. del Mundo**  
**EEE 103 AY2010-11 S2**
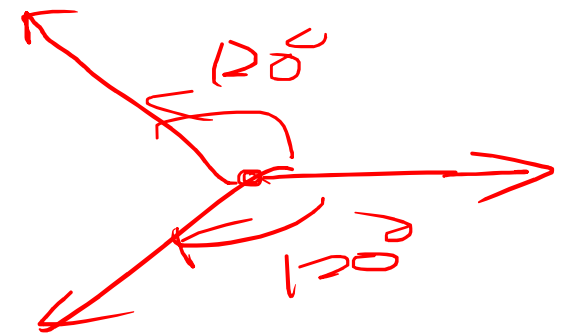
## Unbalanced Three-Phase Systems


An **unbalanced system** contains at least one of the following:


- Unbalanced three-phase source(s);
- Unbalanced loads; or
- Lines have unequal impedances.




Unbalance can be due to:

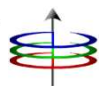- ☞ Difference in magnitudes; and/or
- ☞ Phase angle displacements  $\neq 120^\circ$ .



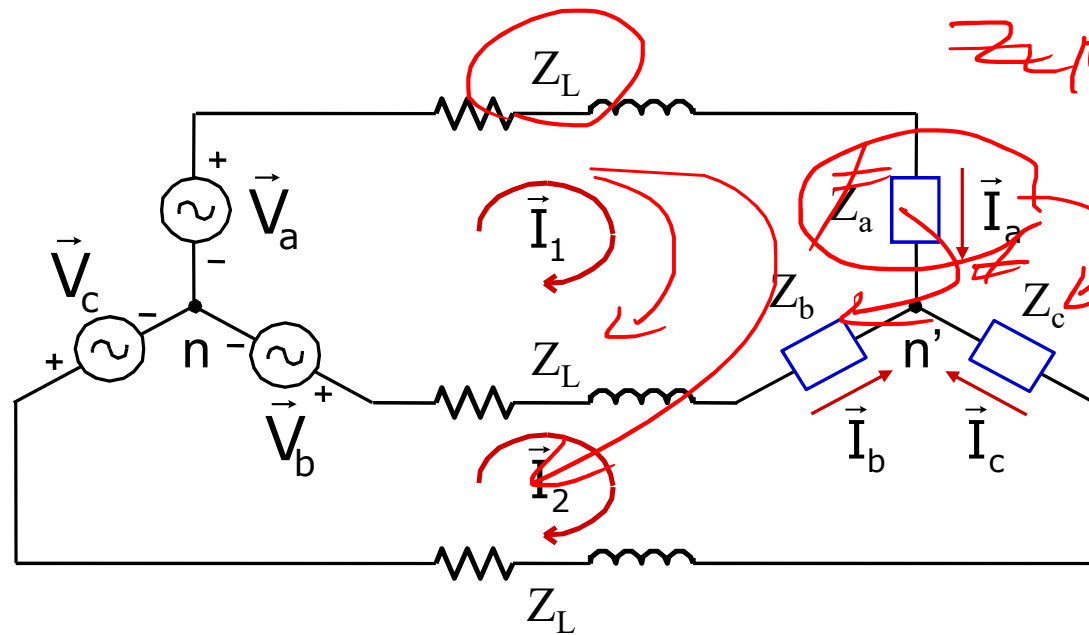

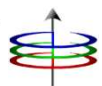- Source phase voltages are not equal
- Load impedances are not equal
- Line impedances are not equal




## Methods of Solution

### 1. Simultaneous Equations → mesh → nodal

#### Network analysis on three phases.


- Simplifying assumption – source is a balanced three-phase source, either
  - Balanced three-phase voltage source; or
  - Balanced three-phase current source.

### 2. Symmetrical Components

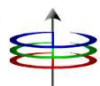

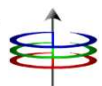
## Review Questions

- An Unbalanced System contains at least one of the following:
  - Unbalanced three-phase source(s);
  - Unbalanced loads; or
  - Lines have unequal impedances.





# POWER MEASUREMENTS

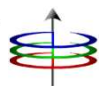


**Electrical and Electronics Engineering Institute**  
**University of the Philippines**

**R. D. del Mundo**  
**EEE 103 AY2010-11 S2**


# The Wattmeter

An instrument that has a potential coil and a current coil so arranged that its deflection is proportional to

$$VI \cos \theta$$

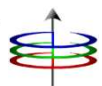

## Single-Phase Power Measurement

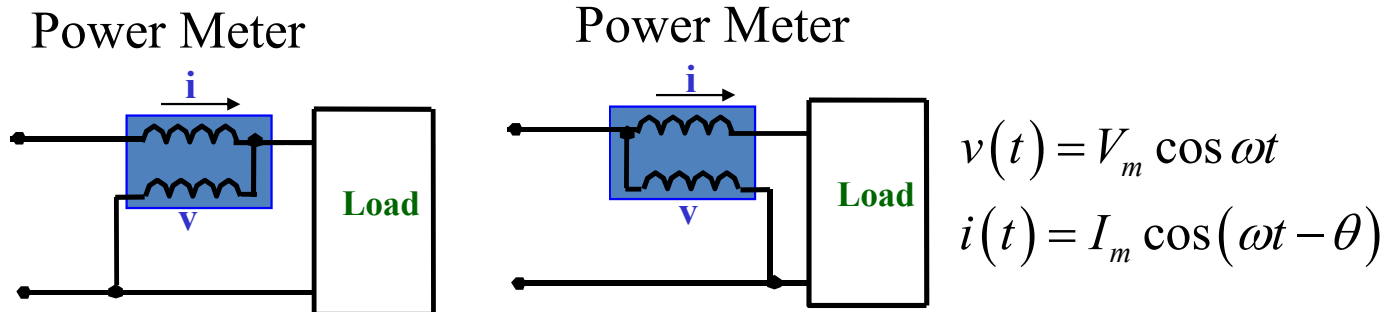


$$\begin{aligned}
 p(t) &= v(t) \cdot i(t) = V_m I_m \cos \omega t \cos(\omega t - \theta) \\
 &= \frac{1}{2} V_m I_m \cos \theta + \frac{1}{2} V_m I_m \cos(2\omega t) + \frac{1}{2} V_m I_m \sin(2\omega t) \sin \theta
 \end{aligned}$$


$$P_{ave} = \frac{1}{T} \int_0^T p(t) dt = \operatorname{Re}\{V \cdot I^*\} = |V||I| \cos \theta$$

$$\cos^2 \omega t = \frac{1}{2} (1 + \cos 2\omega t)$$
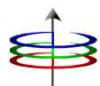
$$\cos \omega t \sin \omega t = \frac{1}{2} \sin 2\omega t$$




## Three-Phase Power Measurement

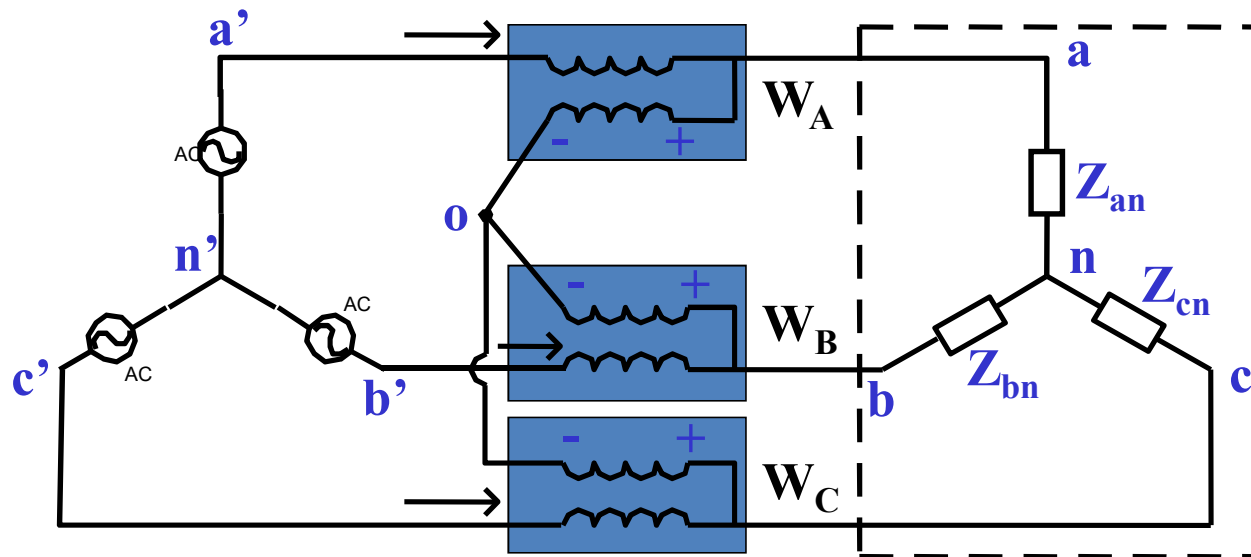
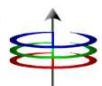
### Three-wattmeter Method for 3-wire 3-phase Systems.

We know that total average power to 3  $\phi$  load over T:

$$P_{abc} = \frac{1}{T} \int_0^T (v_{an} i_{a'a} + v_{bn} i_{b'b} + v_{cn} i_{c'c}) dt$$



### Total average power measured by the 3 wattmeters:

$$P_{meters} = \frac{1}{T} \int_0^T (v_{ao} i_{a'a} + v_{bo} i_{b'b} + v_{co} i_{c'c}) dt$$

### From KVL:

$$v_{ao} = v_{an} - v_{on}$$

$$v_{bo} = v_{bn} - v_{on}$$


$$v_{co} = v_{cn} - v_{on}$$

### For a 3-wire 3-phase system:

$$i_{a'a} + i_{b'b} + i_{c'c} = 0$$

$$P_{meters} = \frac{1}{T} \int_0^T (v_{an} i_{a'a} + v_{bn} i_{b'b} + v_{cn} i_{c'c}) dt$$
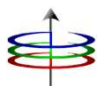
$$- \frac{1}{T} \int_0^T v_{on} (i_{a'a} + i_{b'b} + i_{c'c}) dt \rightarrow 0$$



**For a 3-wire 3-phase system:**

$$P_{3\phi} = \operatorname{Re}\{V_{ao}I_{a'a}^*\} + \operatorname{Re}\{V_{bo}I_{b'b}^*\} + \operatorname{Re}\{V_{co}I_{c'c}^*\}$$

$$= |V_{ao}||I_{a'a}|\cos\theta_a + |V_{bo}||I_{b'b}|\cos\theta_b + |V_{co}||I_{c'c}|\cos\theta_c$$

*which we have shown to be equal to*

$$= |V_{an}||I_{a'a}|\cos\theta_a + |V_{bn}||I_{b'b}|\cos\theta_b + |V_{cn}||I_{c'c}|\cos\theta_c$$


$$P_{3\phi} = \underline{W_A} + \underline{W_B} + \underline{W_C}$$

**For balanced loads:**


$$W_A = W_B = W_C$$


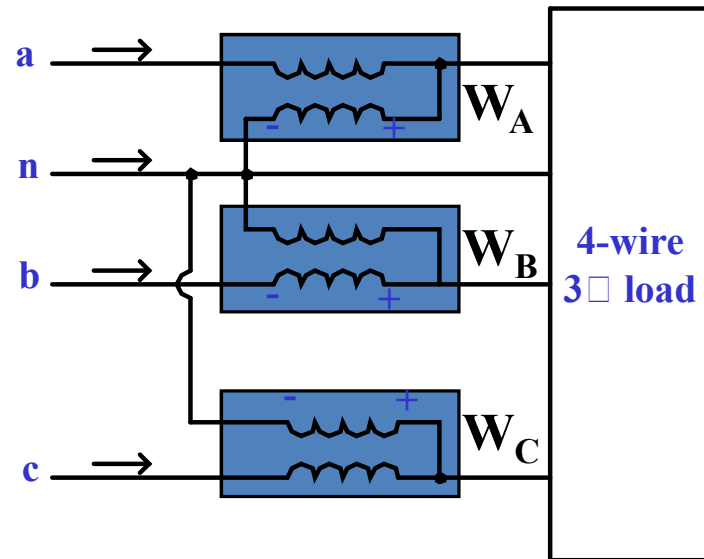
### Three-Wattmeter Method for 4-wire 3-phase systems



$$\begin{aligned}
 P_{3\phi} &= \text{Re} \{ V_{an} I_a^* \} + \text{Re} \{ V_{bn} I_b^* \} + \text{Re} \{ V_{cn} I_c^* \} \\
 &= \underline{|V_{an}|} \underline{|I_a|} \cos \theta_a + \underline{|V_{bn}|} \underline{|I_b|} \cos \theta_b + \underline{|V_{cn}|} \underline{|I_c|} \cos \theta_c \\
 P_{3\phi} &= W_A + W_B + W_C
 \end{aligned}$$

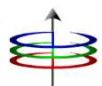

## Two Wattmeter Method for 3-wire 3-phase Wye-Connected Systems

**Recall:**  $p_{3\phi} = v_a i_a + v_b i_b + v_c i_c$

**If the system is 3-wire wye-connected  
(KCL at the neutral point  $n$ ):**


$$p_{3\phi} = v_a i_a + v_b i_b + v_c (-i_a - i_b)$$

$$p_{3\phi} = v_a i_a + v_b i_b - v_c i_a - v_c i_b$$

$$p_{3\phi} = (v_a i_a - v_c i_a) + (v_b i_b - v_c i_b)$$

$$p_{3\phi} = (v_a - v_c) i_a + (v_b - v_c) i_b$$

$$P_{3\phi} = |V_{ac}| |I_a| \cos \theta_{Ia}^{V_{ac}} + |V_{bc}| |I_b| \cos \theta_{Ib}^{V_{bc}}$$

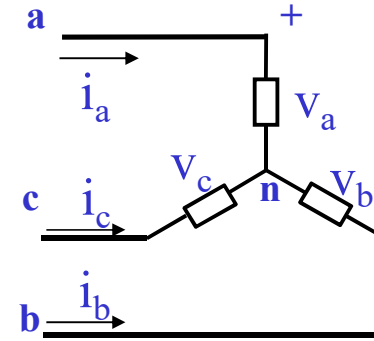

$$i_a + i_b + i_c = 0$$





## Two Wattmeter Method for 3-phase Delta-Connected Systems

**Recall:**  $p_{3\phi} = v_{ab}i_{ab} + v_{bc}i_{bc} + v_{ca}i_{ca}$

**If the system is 3-wire delta-connected (KVL along the delta legs):**


$$p_{3\phi} = (-v_{bc} - v_{ca})i_{ab} + v_{bc}i_{bc} + v_{ca}i_{ca}$$

$$p_{3\phi} = (v_{bc}i_{bc} - v_{bc}i_{ab}) + (v_{ca}i_{ca} - v_{ca}i_{ab})$$

$$p_{3\phi} = v_{bc}(i_{bc} - i_{ab}) + v_{ca}(i_{ca} - i_{ab})$$

$$p_{3\phi} = v_{bc}(i_b) + v_{ca}(-i_a) = v_{ac}i_a + v_{bc}i_b$$


$$P_{3\phi} = |V_{ac}||I_a|\cos\theta_{I_a}^{V_{ac}} + |V_{bc}||I_b|\cos\theta_{I_b}^{V_{bc}}$$

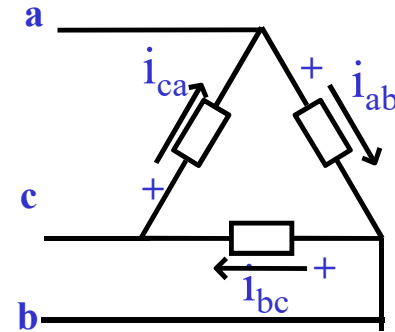

$$v_{ab} + v_{bc} + v_{ca} = 0$$


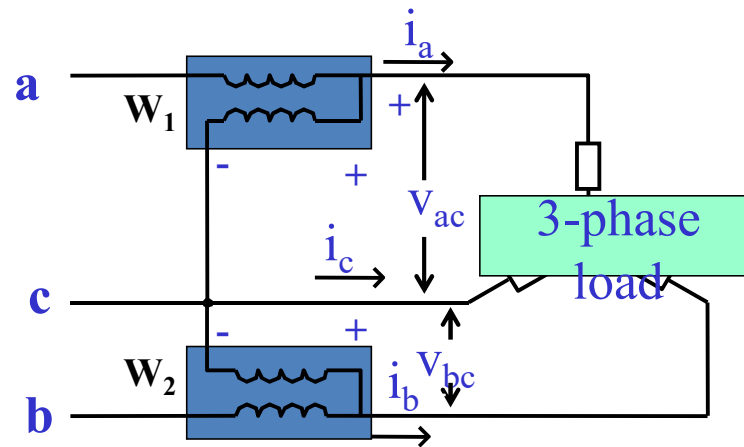
## Two Wattmeter Method for 3-wire 3-phase Systems





$$W_1 = |V_a - V_c| |I_a| \cos \theta_{I_a}^{(V_a - V_c)} = |V_{ac}| |I_a| \cos \theta_{I_a}^{V_{ac}}$$

$$W_2 = |V_b - V_c| |I_b| \cos \theta_{I_b}^{(V_b - V_c)} = |V_{bc}| |I_b| \cos \theta_{I_b}^{V_{bc}}$$

$$P_{3\phi} = W_1 + W_2$$


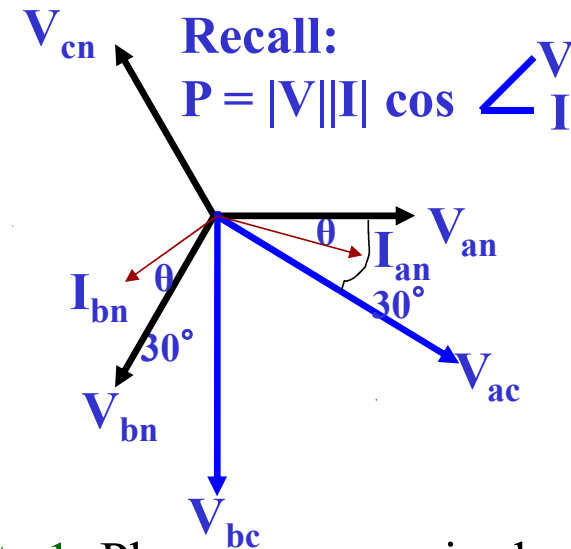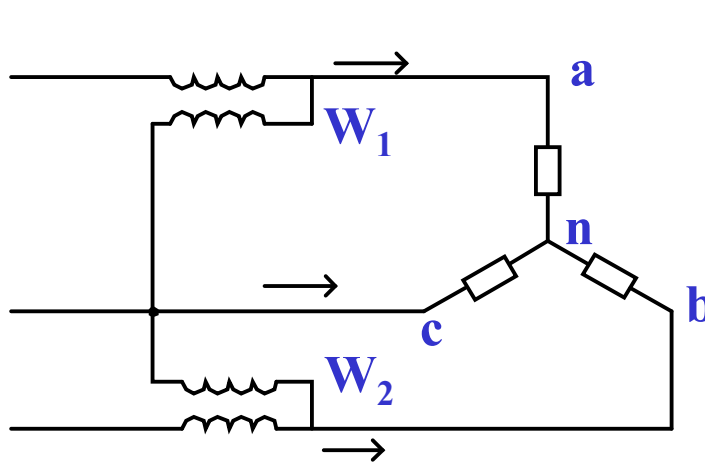
### For a balanced 3-phase Y-connected load:



$$W_1 = |V_{ac}| |I_{an}| \cos (30^\circ - \theta)$$

$$W_2 = |V_{bc}| |I_{bn}| \cos (30^\circ + \theta)$$


$$W_1 = |V_{LL}| |I_L| \cos (30^\circ - \theta)$$

$$W_2 = |V_{LL}| |I_L| \cos (30^\circ + \theta)$$


$$P_{3\phi} = W_1 + W_2$$

**Note 1** Phase sequence is abc.  
 What would happen if phase sequence is acb?

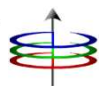**Note 2** PF is assumed lagging.  
 What would happen if PF is leading?



**For a balanced Delta-connected load:**

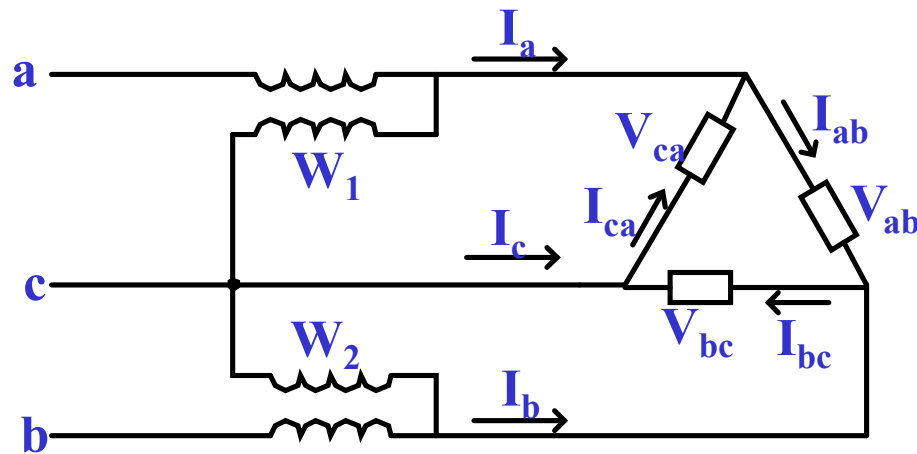


$$W_1 = |V_{ac}| |I_a| \cos (30^\circ - \theta)$$

$$W_2 = |V_{bc}| |I_b| \cos (30^\circ + \theta)$$

$$P_{3p} = W_1 + W_2$$

$$W_1 = |V_{LL}| |I_L| \cos (30^\circ - \theta)$$

$$W_2 = |V_{LL}| |I_L| \cos (30^\circ + \theta)$$

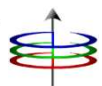

$$W_1 = |V_{LL}| |I_L| \cos (30^\circ - \theta)$$

$$W_2 = |V_{LL}| |I_L| \cos (30^\circ + \theta)$$

$$P_{3p} = W_1 + W_2$$

$\theta$	$\cos(30 - \theta)$	$\cos(30 + \theta)$	$W1 + W2$	$\text{sqrt}(3) \cos \theta$
-90	-0.500	0.500	0.000	0.000
-60	0.000	0.866	0.866	0.866
-45	0.259	0.966	1.225	1.225
-30	0.500	1.000	1.500	1.500
0	0.866	0.866	1.732	1.732
30	1.000	0.500	1.500	1.500
45	0.966	0.259	1.225	1.225
60	0.866	0.000	0.866	0.866
90	0.500	-0.500	0.000	0.000



Consider  $W_1 - W_2$ :

$$W_1 - W_2 = |V||I| \cos(30 - \theta) - |V||I| \cos(30 + \theta)$$


$$= |V||I| [\cos 30 \cos \theta + \sin 30 \sin \theta - \cos 30 \cos \theta + \sin 30 \sin \theta]$$

$$= |V||I| \sin \theta$$


For balanced 3 $\phi$ :  $Q_{3p} = \text{Sqrt}(3)(W_1 - W_2)$

Thus, the for a balanced 3p
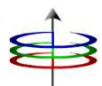
$$\tan \theta = Q_{3p} / P_{3p} = (\text{Sqrt}(3)(W_a - W_b)) / (W_a + W_b)$$




**EXAMPLE:**  $W_1 = 800, W_2 = -400$

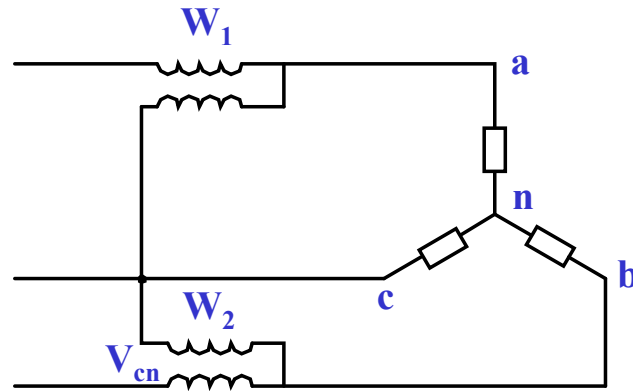

$$P = W_a + W_b = 800 + (-400) = 400 \text{ W}$$
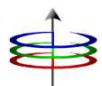
$$Q = \text{Sqrt}(3) (W_a - W_b) = \text{Sqrt}(3) [800 - (-400)] = 2078 \text{ Vars}$$




**CONCEPT TEST****Solve for the power readings in each wattmeter:**

$$V_{ab} = 200\angle 0^\circ$$

$$V_{bc} = 200\angle -240^\circ$$


$$V_{ca} = 200\angle -120^\circ$$

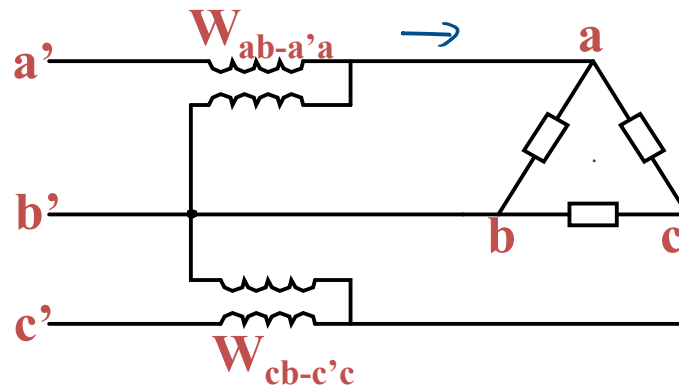*Sequence is negative*

6 kW, 0.8 pf  
Delta-connected  
load

**SOLUTION:**

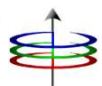
1. Calculate phase voltages (phasor).
2. Calculate phase currents (phasor).
3. Calculate line currents (phasor).
4. Calculate power in each wattmeter.
5. Check with the given total complex power.





Phase Voltages

$$\begin{aligned}
 1) \quad & V_{ab} = 200 \angle 0^\circ \text{ V} \\
 & V_{bc} = 200 \angle -120^\circ \text{ V} \\
 & V_{ca} = 200 \angle -240^\circ \text{ V}
 \end{aligned}$$

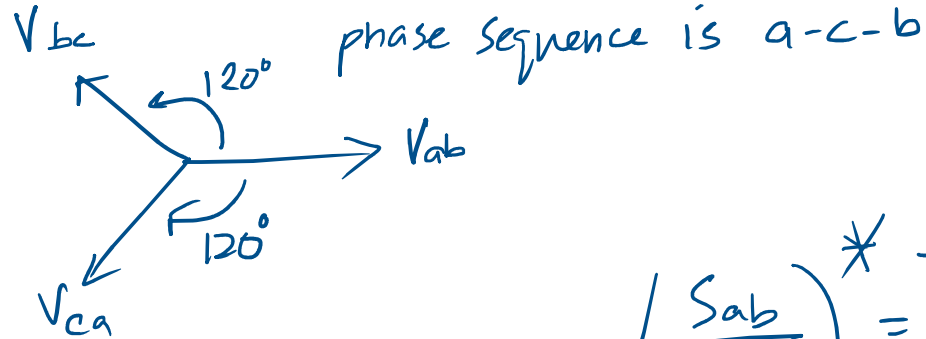Phase Currents

$$\begin{aligned}
 2) \quad & \text{Since system is balanced,} \\
 & P_{3\phi} = 3 V_p I_p \cos \theta_{pf} = 6 \text{ kW} \\
 & \theta_{pf} = 36.87^\circ
 \end{aligned}$$

$$I_p = 12.5$$


$$\begin{aligned}
 I_{ab} &= 12.5 \angle -36.87^\circ \text{ A} \\
 I_{bc} &= 12.5 \angle -83.13^\circ \text{ A} \\
 I_{ca} &= 12.5 \angle -156.87^\circ \text{ A}
 \end{aligned}$$

$$I_{ab} = \left( \frac{S_{ab}}{V_{ab}} \right)^* = \frac{\frac{1}{3} (7.5 \angle -36.87^\circ)}{200 \angle 0^\circ}$$




$$I_{bc} = \left( \frac{S_{bc}}{V_{bc}} \right)^* = \frac{\frac{1}{3} (7.5 \angle -36.87^\circ)}{200 \angle -120^\circ}$$

$$\text{OR } I_{ca} = \left( \frac{S_{ca}}{V_{ca}} \right)^* = \frac{\frac{1}{3} (7.5 \angle -36.87^\circ)}{200 \angle -240^\circ}$$
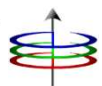
$$\begin{aligned}
 I_{ab} &= 12.5 \angle -36.87^\circ \text{ A} \\
 I_{bc} &= 12.5 \angle -83.13^\circ \text{ A} \\
 I_{ca} &= 12.5 \angle -156.87^\circ \text{ A}
 \end{aligned}$$



# Visualizing Phasors 3.) Line currents

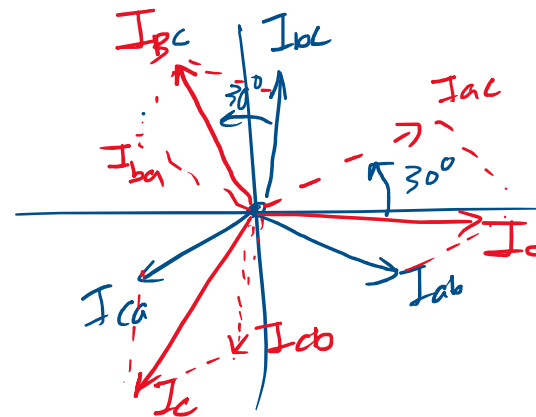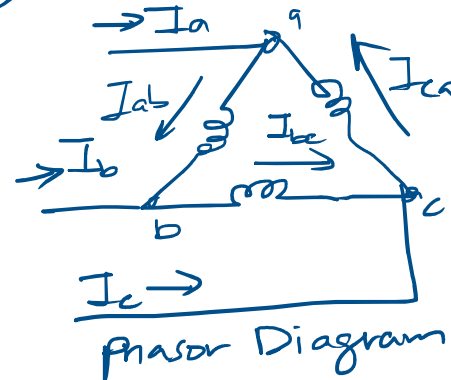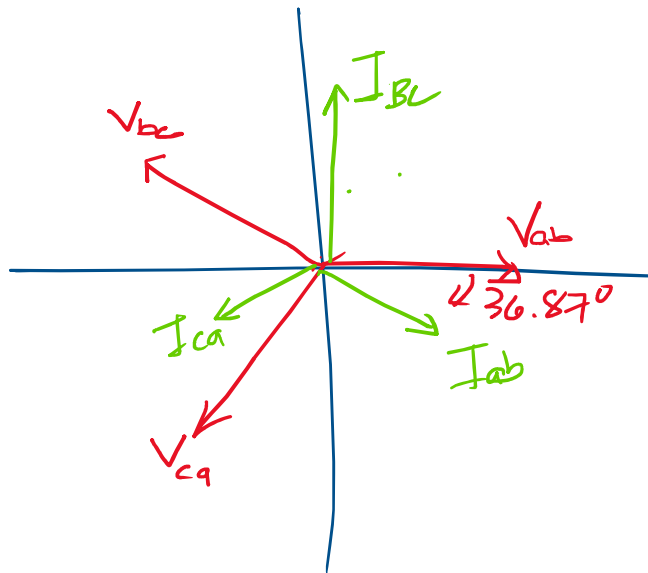

$$\begin{aligned} I_a &= I_{ab} - I_{ca} \\ I_b &= I_{bc} - I_{ab} \\ I_c &= I_{ca} - I_{bc} \end{aligned}$$

$$\text{Let } |I_{ab}| = |I_{bc}| = |I_{ca}| = I_p$$


If  $I_{ab}$  is reference, for any  $I_L$ :

$$I_L = I_p \angle 0^\circ - I_p \angle 120^\circ$$

$$I_L = \sqrt{3} I_p \angle 30^\circ$$

therefore for a-c-b sequence (negative)
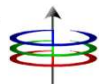
$$I_L = \sqrt{3} I_p \angle \theta + 30^\circ$$



Solving for line current

Method 1

for a-c-b (negative)

$$I_L = \sqrt{3} I_p \angle \theta + 30^\circ$$

$$I_a = 21.65 \angle -6.87^\circ \text{ A}$$

$$I_b = 21.65 \angle 113.13^\circ \text{ A}$$


$$I_c = 21.65 \angle -126.87^\circ \text{ A}$$

Method 2

$$I_a = I_{ab} - I_{ca} = 21.65 \angle -6.87^\circ \text{ A}$$

$$I_b = I_{bc} - I_{ab} = 21.65 \angle 113.13^\circ \text{ A}$$
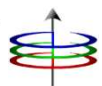
$$I_c = I_{ca} - I_{bc} = 21.65 \angle -126.87^\circ \text{ A}$$





4.) Solving for  $W_1$  &  $W_2$

$$W_1 + W_2 = P_{3\phi} = 6 \text{ kW}$$

$$\sqrt{3}(W_1 - W_2) = Q_{3\phi} = 4.5 \text{ kvars}$$
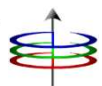
$$W_1 = 4.3 \text{ kW} \quad W_2 = 1.7 \text{ kW}$$



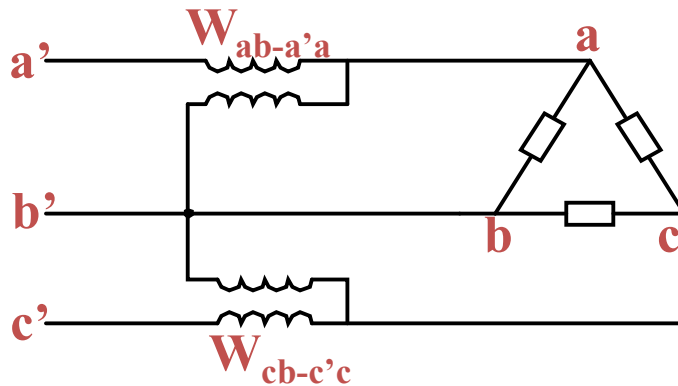

6 kW, 0.8 pf  
Delta-connected  
load

Confirmed


5.) 
$$W_{ab-a'a} = V_{ab} I_a \cos \theta = 200(21.65) \cos(0^\circ - (-6.87^\circ)) = \boxed{4.3k}$$

$$W_{cb-c'c} = V_{cb} I_c \cos \theta = 200(21.65) \cos(-60^\circ - (-126.87^\circ)) = \boxed{1.7k}$$

OR

$$W_1 = V_{LL} I_L \cos(\theta - 30^\circ) = 200(21.65) \cos(36.87^\circ - 30^\circ) = \boxed{4.3k}$$
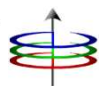
$$W_2 = V_{LL} I_L \cos(\theta + 30^\circ) = 200(21.65) \cos(36.87^\circ + 30^\circ) = \boxed{1.7k}$$



**End of Presentation**

