



EEE 51: Second Semester 2017 - 2018

Lecture 24


Oscillators

Crystal Oscillators

- Crystals are materials that exhibits the piezoelectric effect
 - When stress is applied, voltage is generated between opposite faces of the crystal
 - When a voltage is applied, the crystal deforms at the frequency of the applied voltage
- Mechanical to electrical energy conversion
- Provides stable frequency of oscillation
 - Resonant frequency dependent on physical crystal size
 - 1 ppm/°C or 0.0001%/°C
 - Compare with LC oscillator: ~1% drift




Crystal Strain

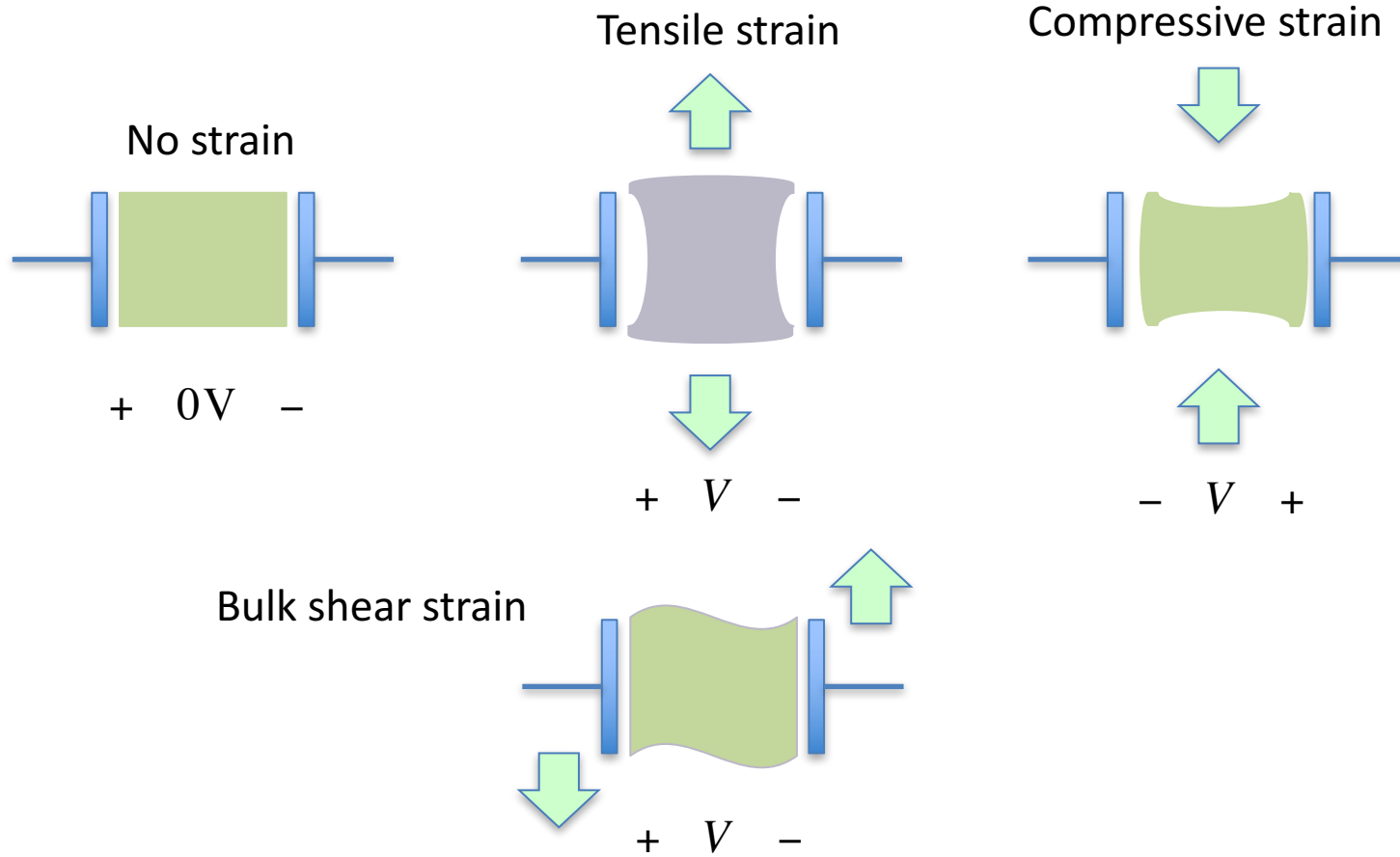

Natural Crystal Frequency

- Proportional to crystal thickness



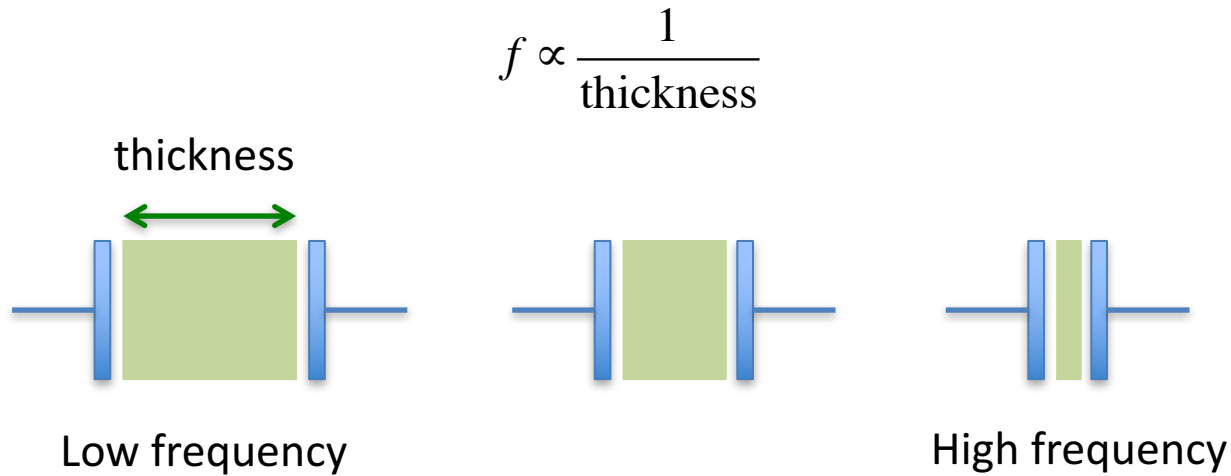


Typical natural frequencies below 20-30 MHz

- For 100 MHz, thickness $\sim 17\mu\text{m}$ thick




The Parallel Resonant Mode
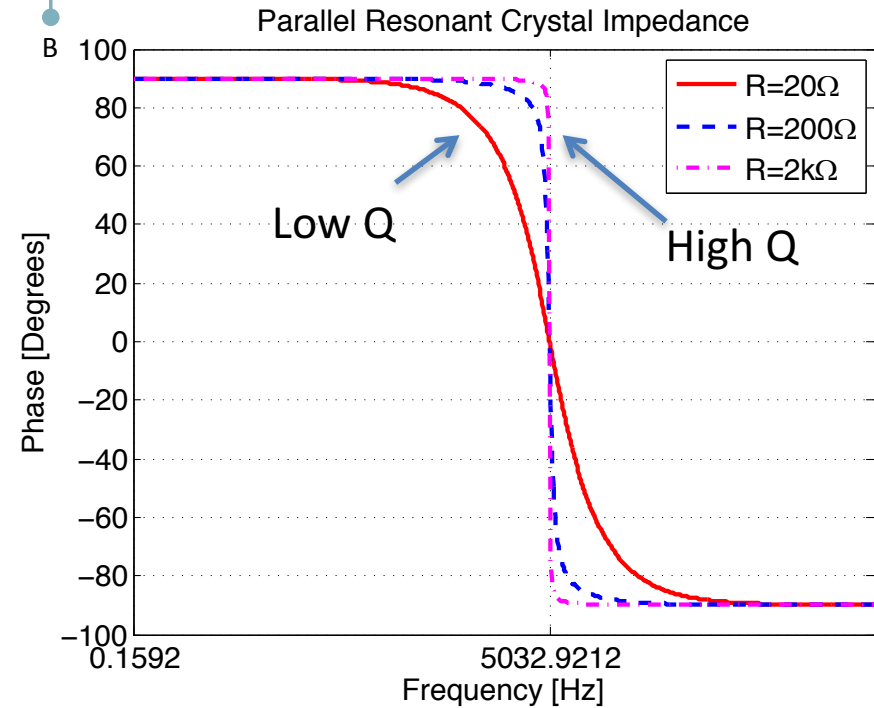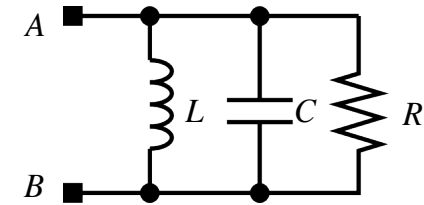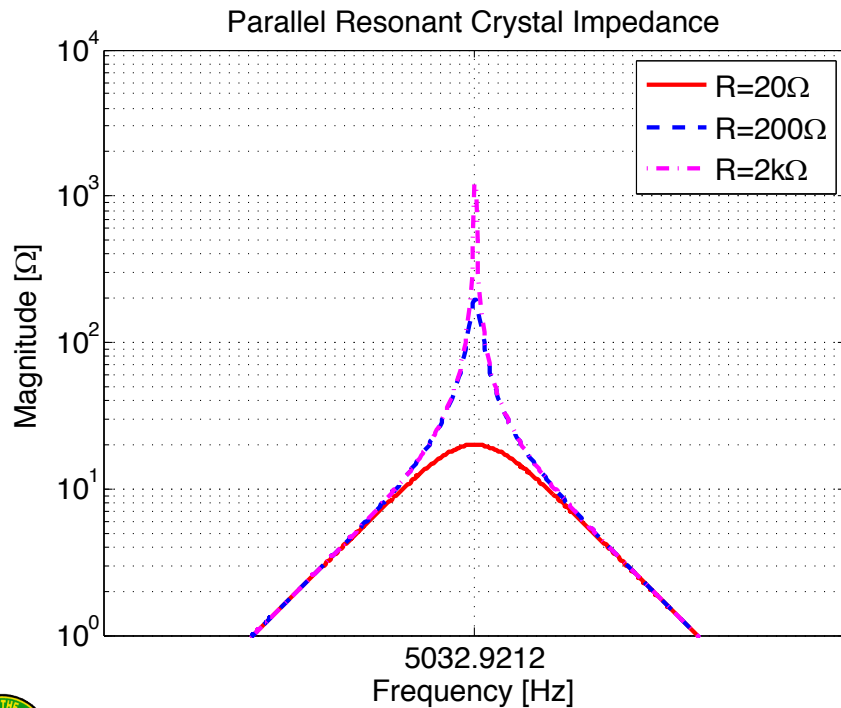
$$L = 1\text{mH} \quad C = 1\mu\text{F}$$




The Series Resonant Mode
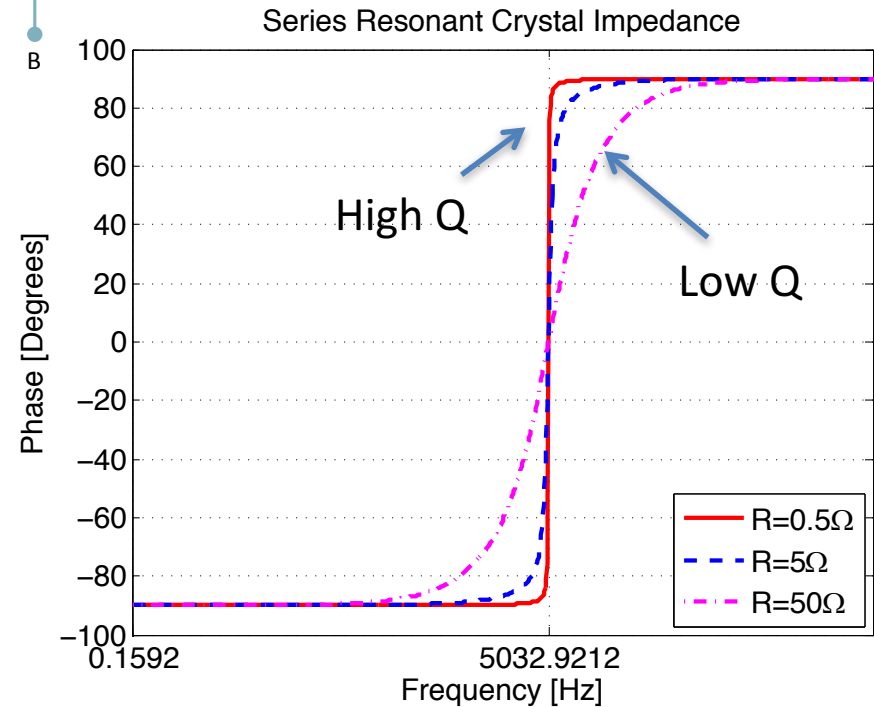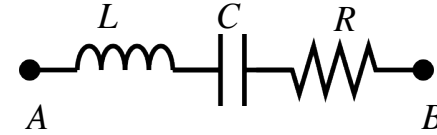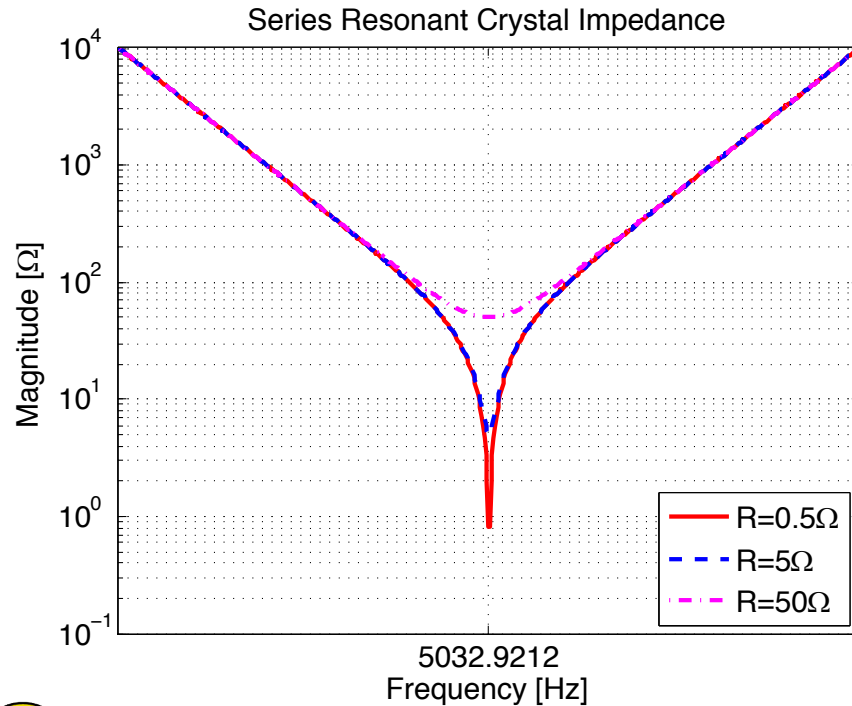
$$L = 1\text{mH} \quad C = 1\mu\text{F}$$



Electrical Equivalent Circuit

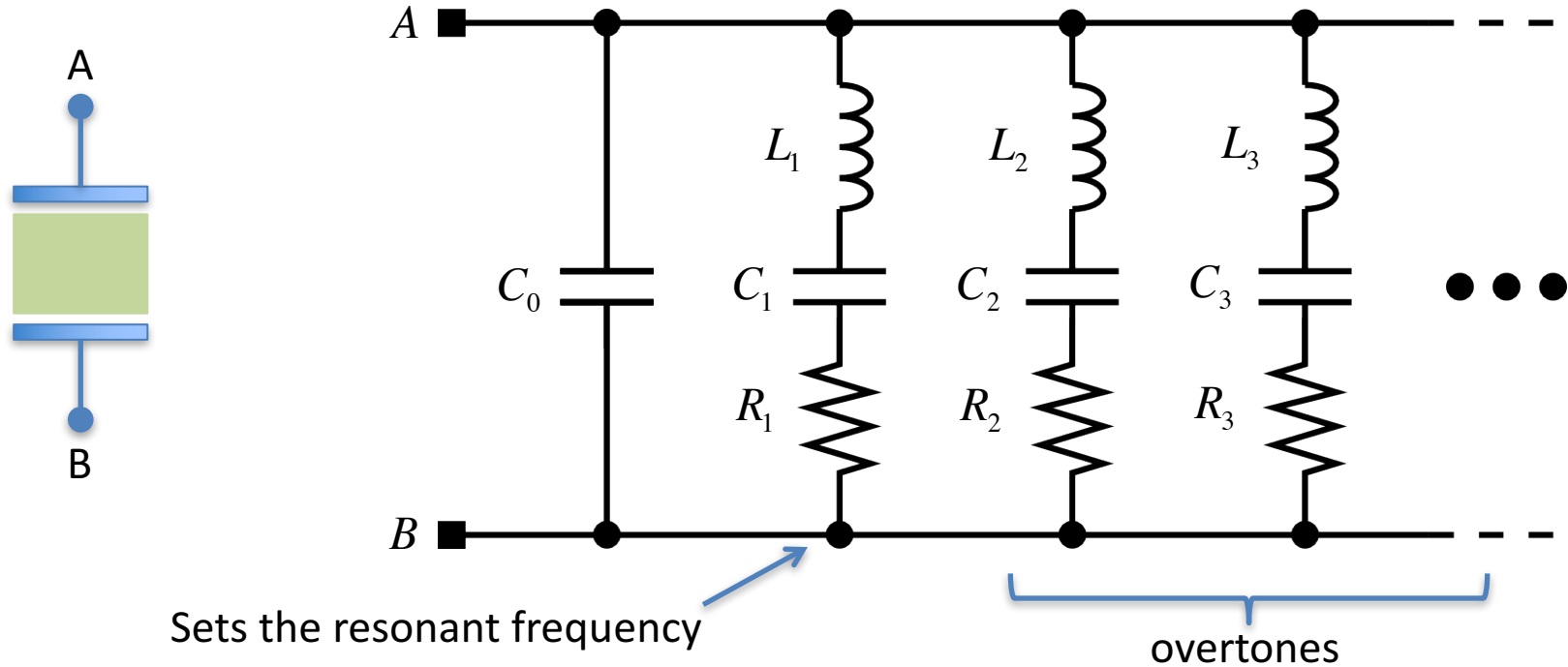


$C_0 \equiv$ parallel capacitances due to contacts and wires

$L_i, C_i \equiv$ mechanical energy storage (mass & spring effects)

$R_i \equiv$ electrical losses due to mechanical effects (e.g. friction)


Crystal Equivalent Circuit

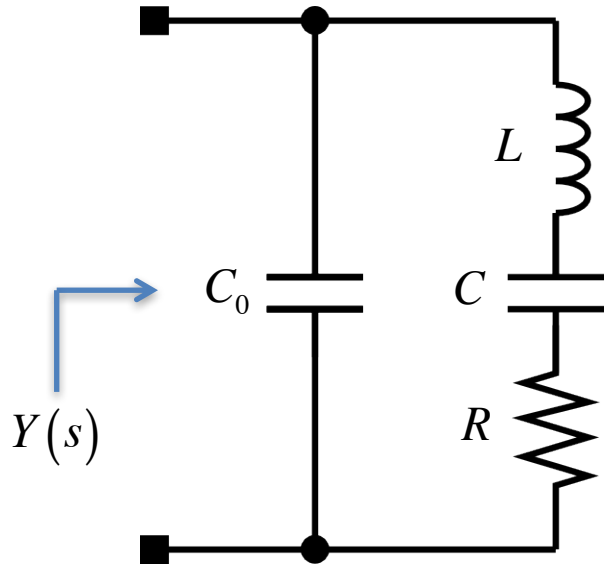


$$\omega_0 = \frac{1}{\sqrt{LC}} \quad Z(s) = \frac{1}{Y(s)}$$

$$Y(s) = sC_0 + \frac{1}{sL + \frac{1}{sC} + R} = sC_0 + \frac{sC}{s^2LC + sRC + 1}$$
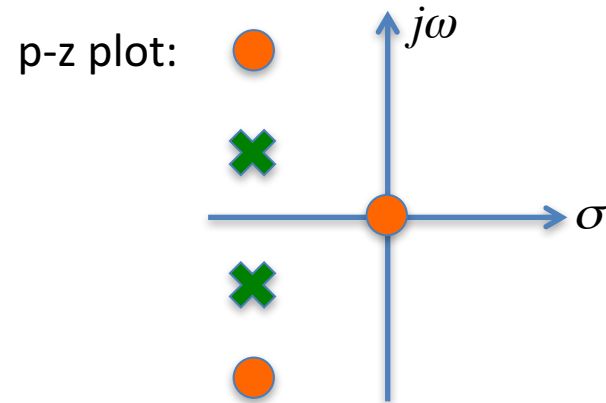
$$= \frac{sC_0 \left[s^2 + s\frac{R}{L} + \left(\frac{C}{C_0} + 1 \right) \omega_0^2 \right]}{s^2 + s\frac{R}{L} + \omega_0^2}$$




Crystal Equivalent Circuit

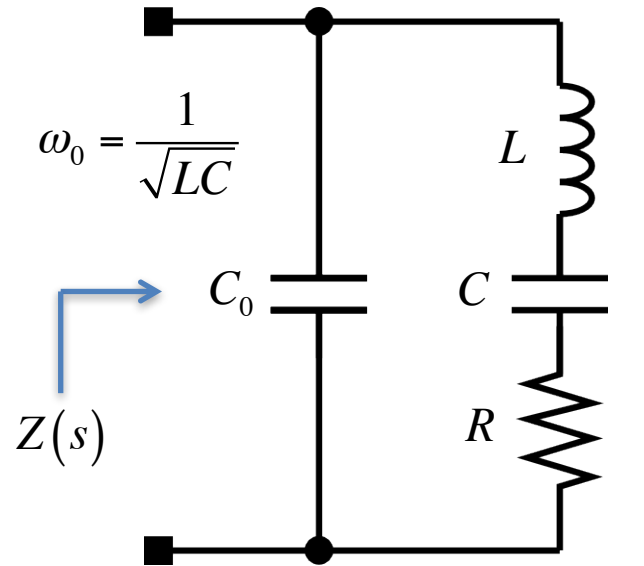

$$Z(s) = \frac{s^2 + s\frac{R}{L} + \omega_0^2}{sC_0 \left[s^2 + s\frac{R}{L} + \left(\frac{C}{C_0} + 1 \right) \omega_0^2 \right]}$$

$$L = 10\text{H} \quad C = C_0 = 3.2\text{fF} \quad R \approx \frac{5 \times 10^8}{f_0}$$

Crystal Equivalent Impedance

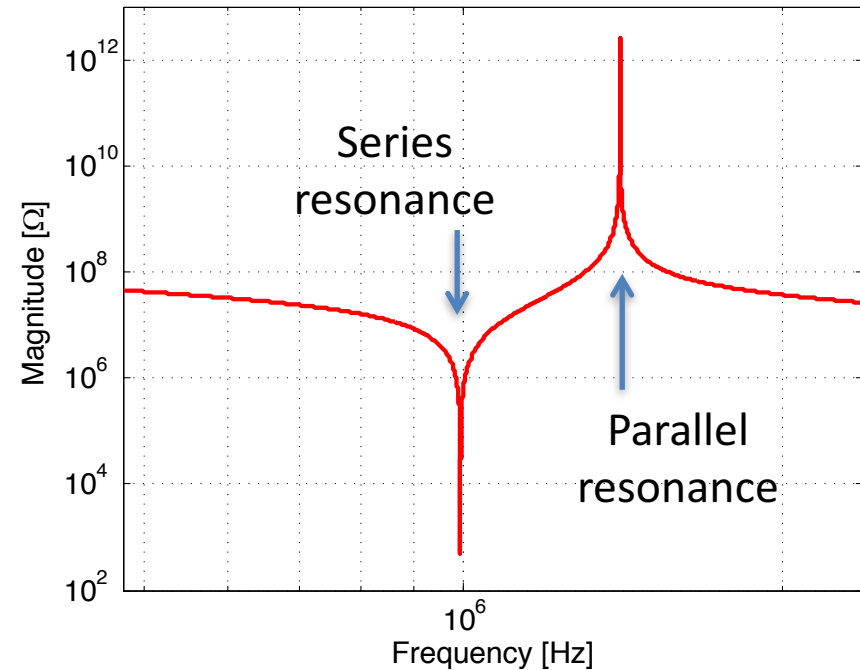


How can we use this to create an oscillator?


Crystal Equivalent Circuit

$$L = 10\text{H} \quad C = C_0 = 3.2\text{fF} \quad R \approx \frac{5 \times 10^8}{f_0}$$

Crystal Equivalent Impedance

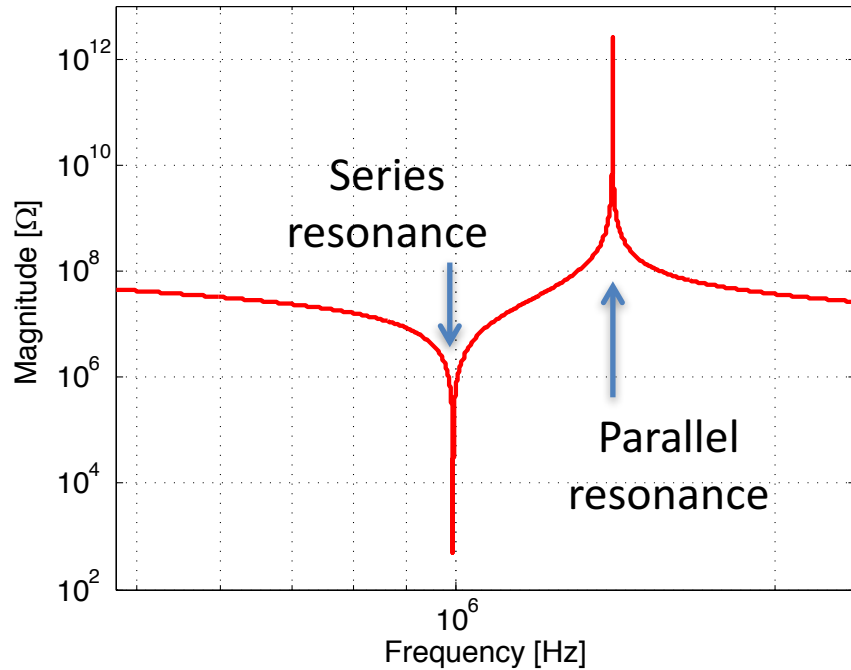


Crystal Equivalent Impedance

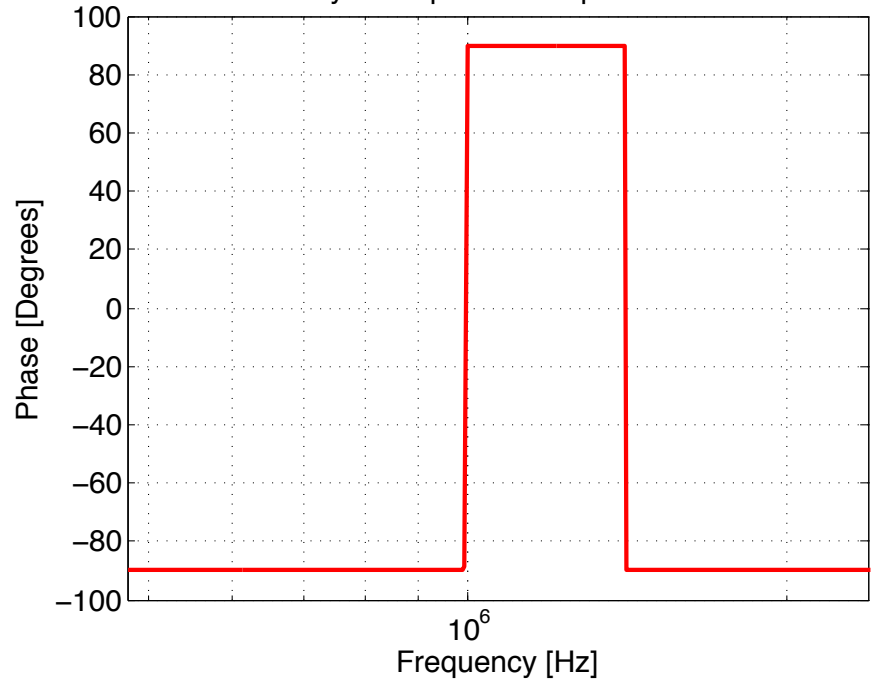

How can we use this to create an oscillator?



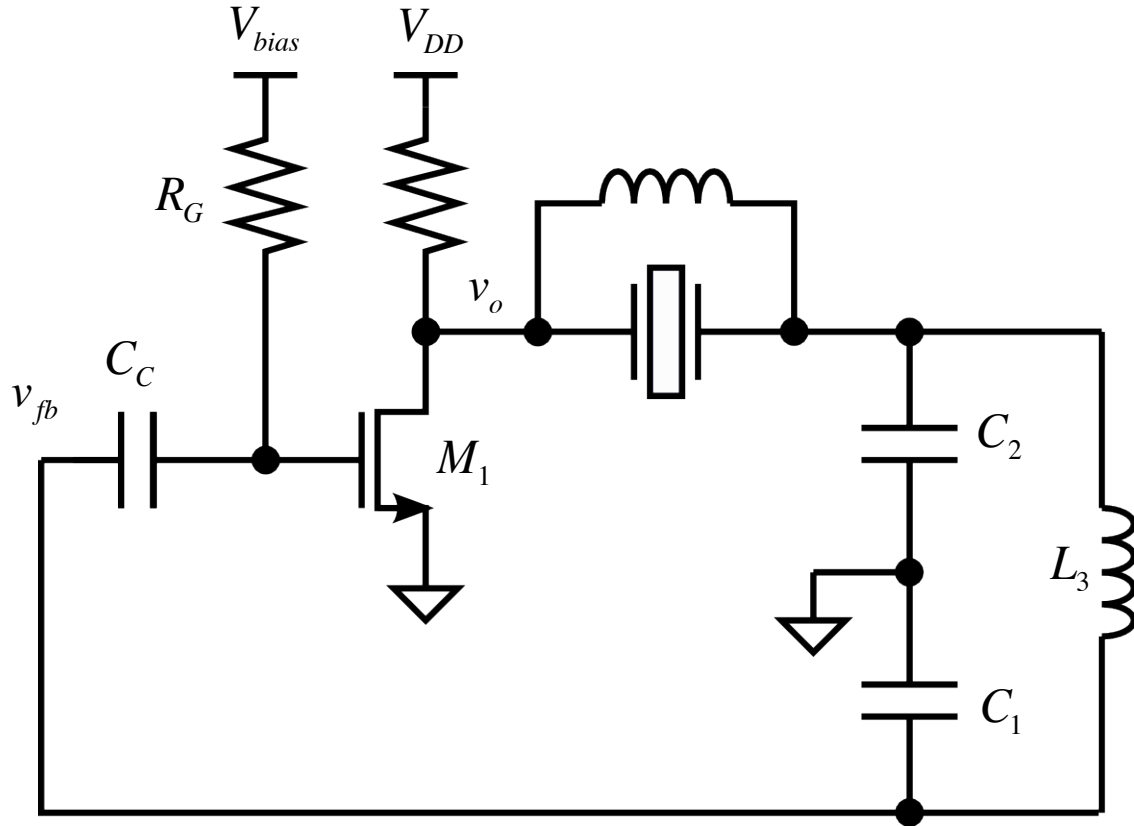
Direct Application: A Colpitts Crystal Oscillator



- The crystal is used to close the feedback loop only at the desired frequency
- The parallel inductance is used to cancel out the crystal parallel capacitance C_0
 - Only the series RLC branch controls the feedback path



Another Colpitts Crystal Oscillator

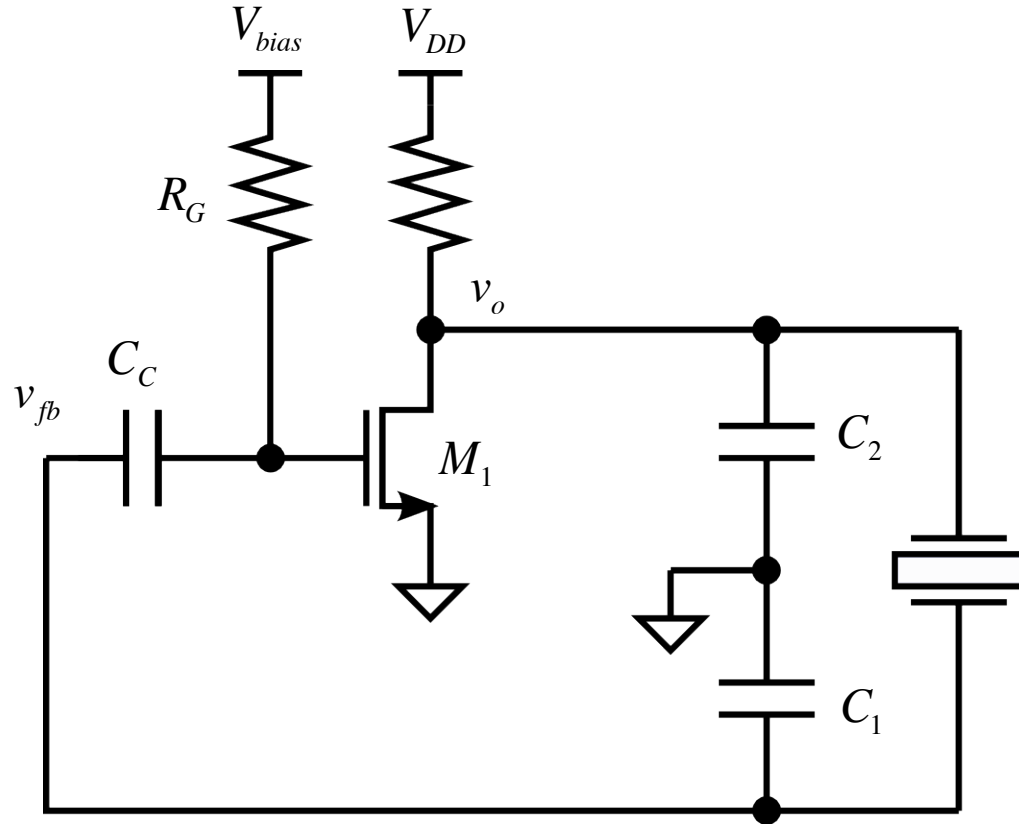


- The crystal is used as an inductance
- The oscillation frequency is set to be a little above series resonance
 - The crystal impedance is inductive
- Note that the crystal series resonant frequency is not the same as the output oscillation frequency
 - Crystal is cut to oscillate at a specified load capacitance



Negative Resistance Oscillators

- What happens in an ideal LC circuit?


Ideal

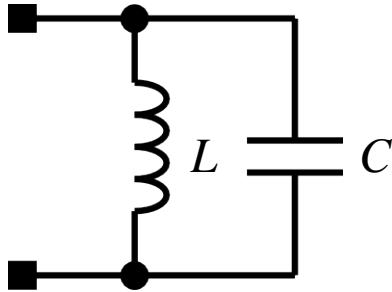

The circuit will oscillate at


$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Real

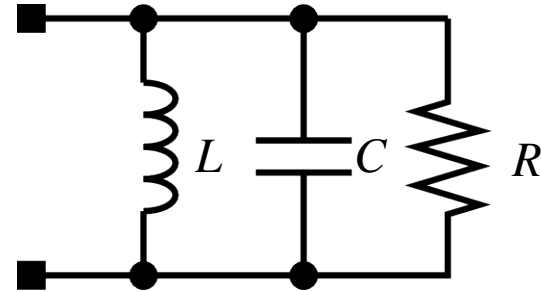

This circuit will also oscillate but the oscillations will die out due to the resistance R

Example:

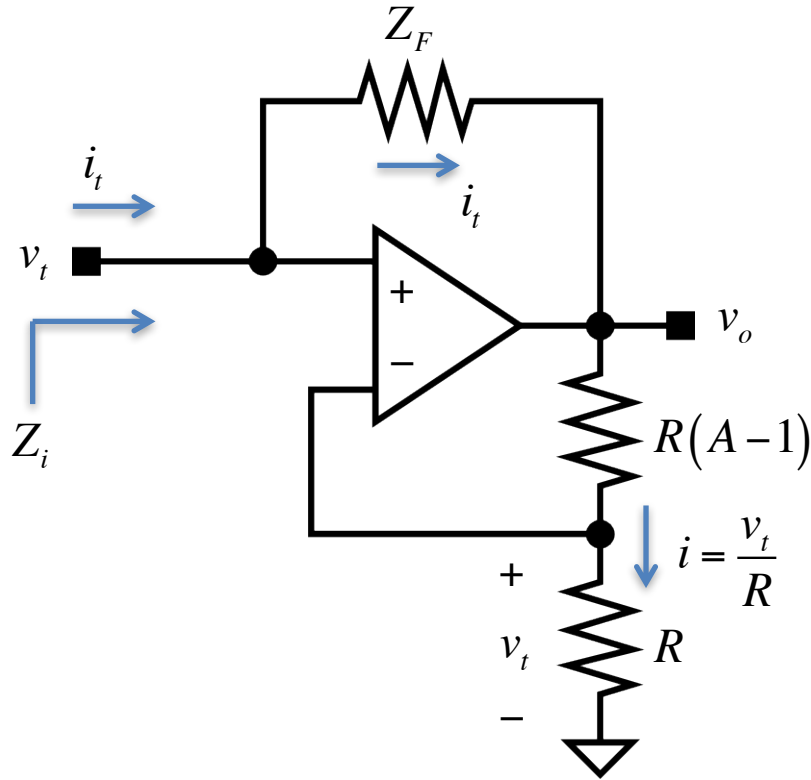

$$v_o = v_t + i \cdot R(A-1) = v_t + \frac{v_t}{R} \cdot R(A-1) = v_t \cdot A$$

Thus,

$$i_t = \frac{v_t - A \cdot v_t}{Z_F}$$


$$Z_i = \frac{v_t}{i_t} = \frac{Z_F}{1-A}$$

For $A = 2$:

$$Z_i = -Z_F$$



Negative Resistance Oscillators

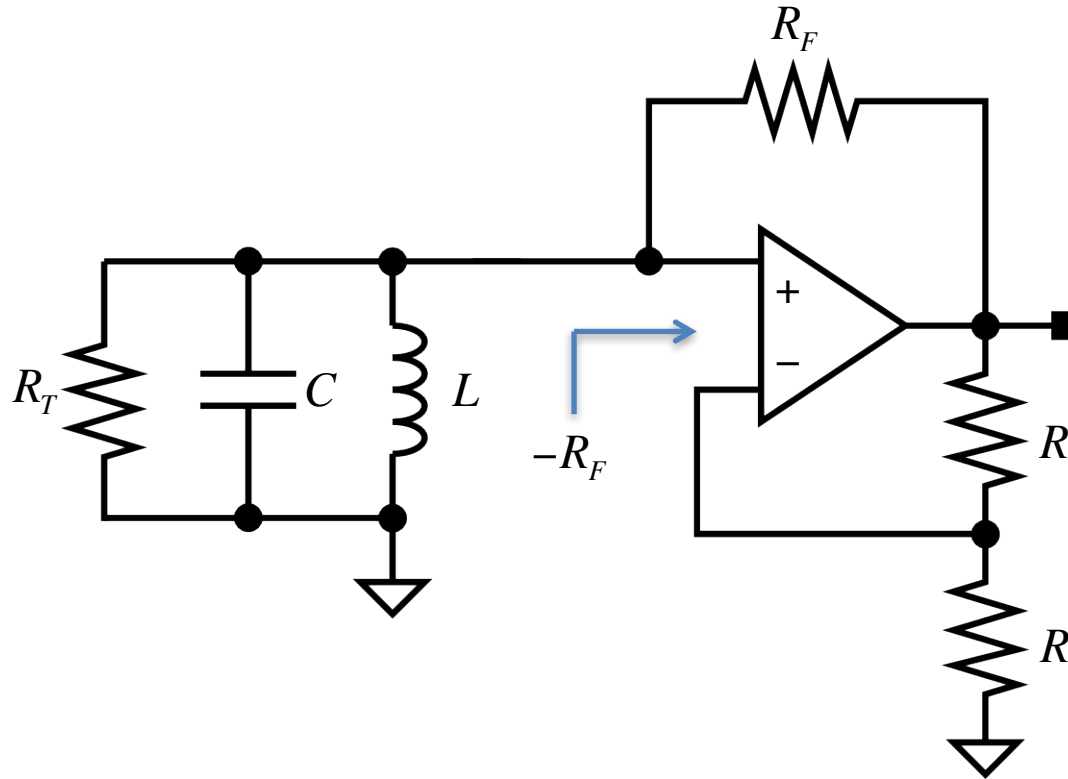


$$R_T > R_F$$

$$\frac{1}{R_{eff}} = \frac{1}{R_T} - \frac{1}{R_F}$$

The effective resistance seen by the LC circuit is negative

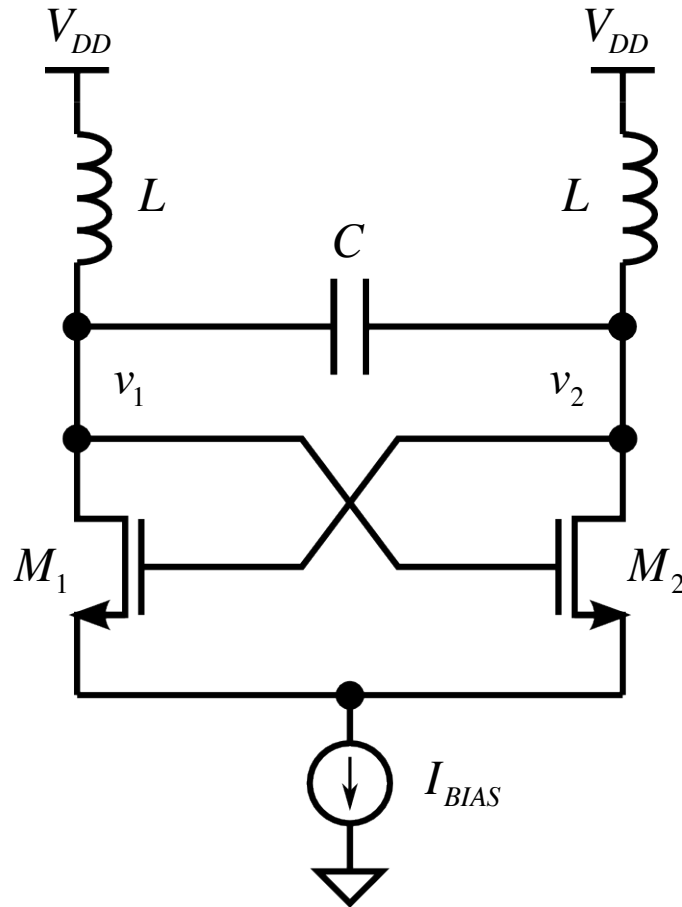
Differential Negative Resistance Oscillator



How do we analyze this?

- Get the small signal impedance between v_1 and v_2 without the LC network
- Convert to the single ended equivalent


MOS Differential Cross-Coupled Pair

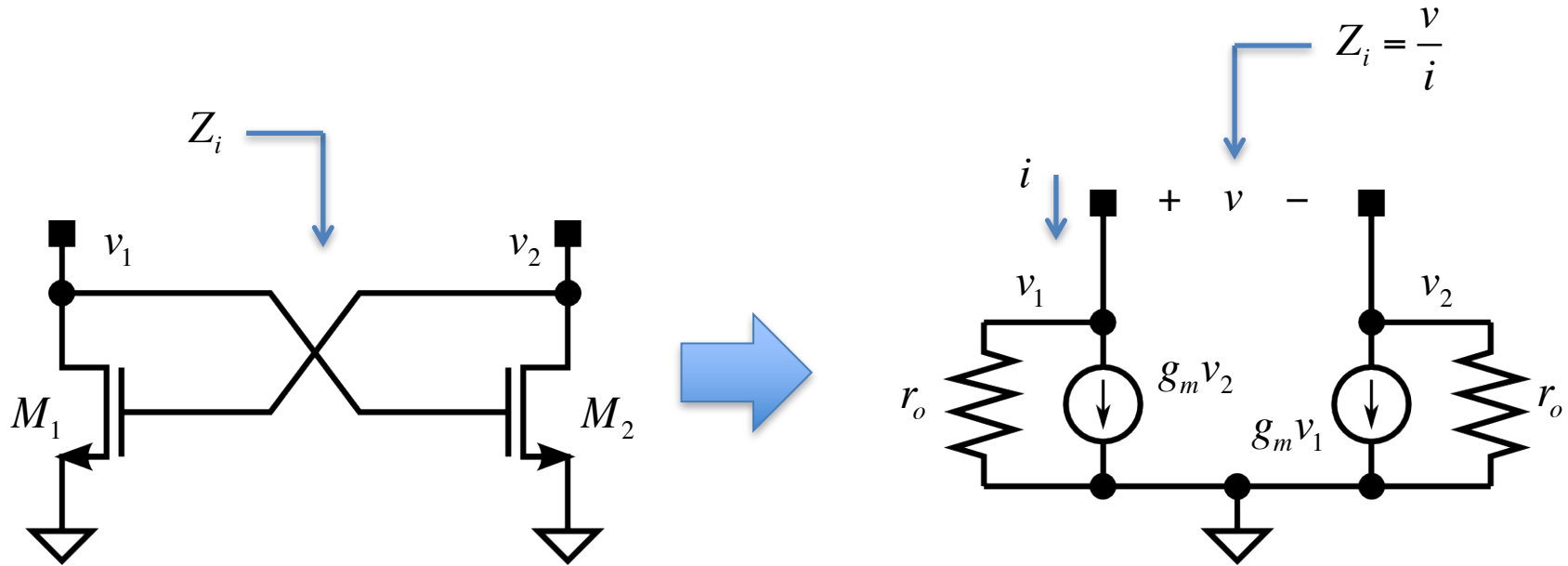

$$i = g_m v_2 + \frac{v_1}{r_o} = -g_m v_1 - \frac{v_2}{r_o} \Rightarrow v_1 \left(g_m + \frac{1}{r_o} \right) = -v_2 \left(g_m + \frac{1}{r_o} \right)$$

$$v_1 = -v_2$$

MOS Differential Cross-Coupled Pair

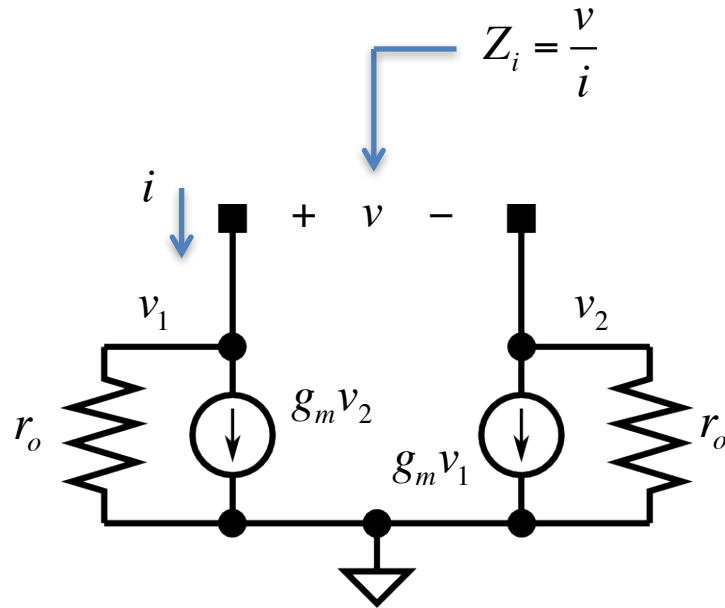


Since $v_1 = -v_2$ and $v = v_1 - v_2 = 2v_1$

$$i = -g_m v_1 + \frac{v_1}{r_o} = v_1 \left(-g_m + \frac{1}{r_o} \right)$$


$$= \frac{v}{2} \left(-g_m + \frac{1}{r_o} \right)$$

$$Z_i = \frac{v}{i} = \frac{2}{-g_m + \frac{1}{r_o}} \approx -\frac{2}{g_m}$$

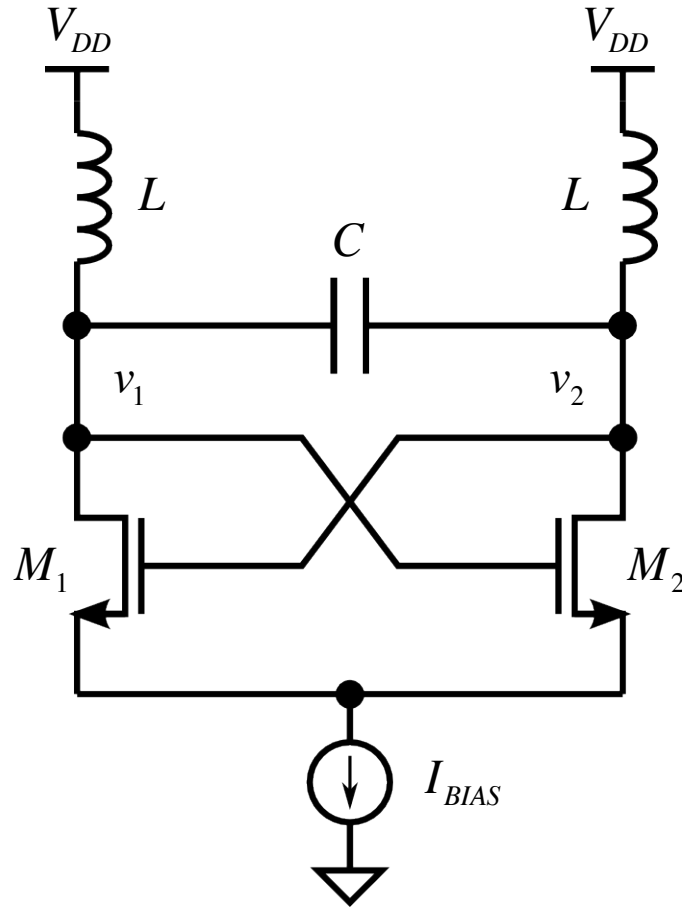Differential Negative Resistance Oscillator



The differential half circuit:

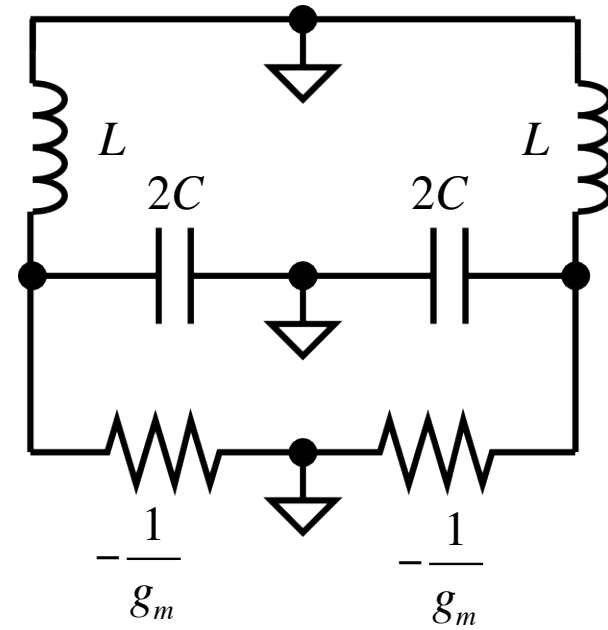

$$\omega_0 = \frac{1}{\sqrt{2LC}}$$

Reminder

- Final Exam:
 - May 24, 2018 (THURSDAY)
 - 1 – 4 pm
 - Bring: pen, calculator

