




# **EEE 51: Second Semester 2017 - 2018**

## **Lecture 12**

# Differential to Single-Ended Conversion
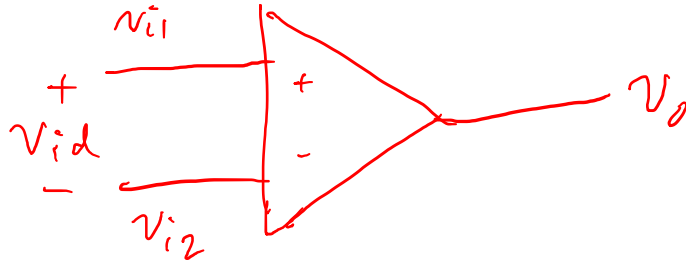
# Today

- Small signal analysis of differential circuits
- Differential to single-ended conversion




# The Differential-Mode Half Circuit


$$(v_{ic} = 0)$$

$$v_{i1} = v_{ic} + v_{id}/2$$

$$v_{i2} = v_{ic} - v_{id}/2$$

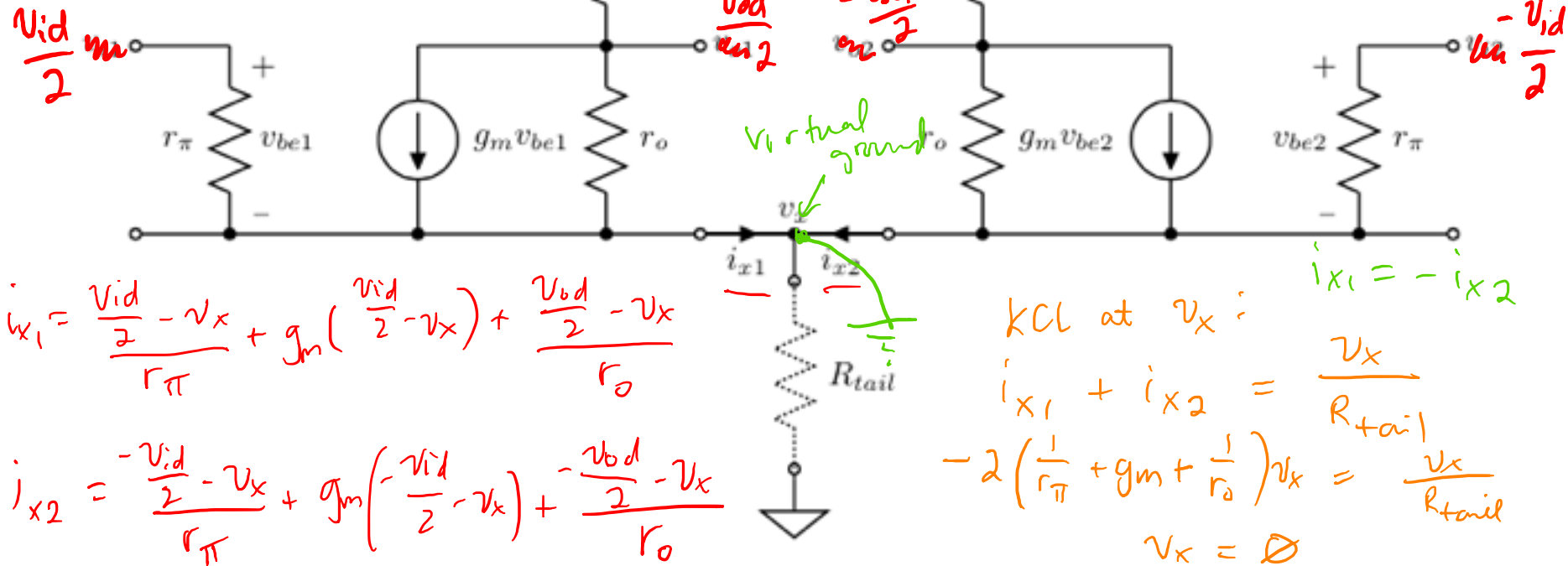

# The Differential Half Circuit

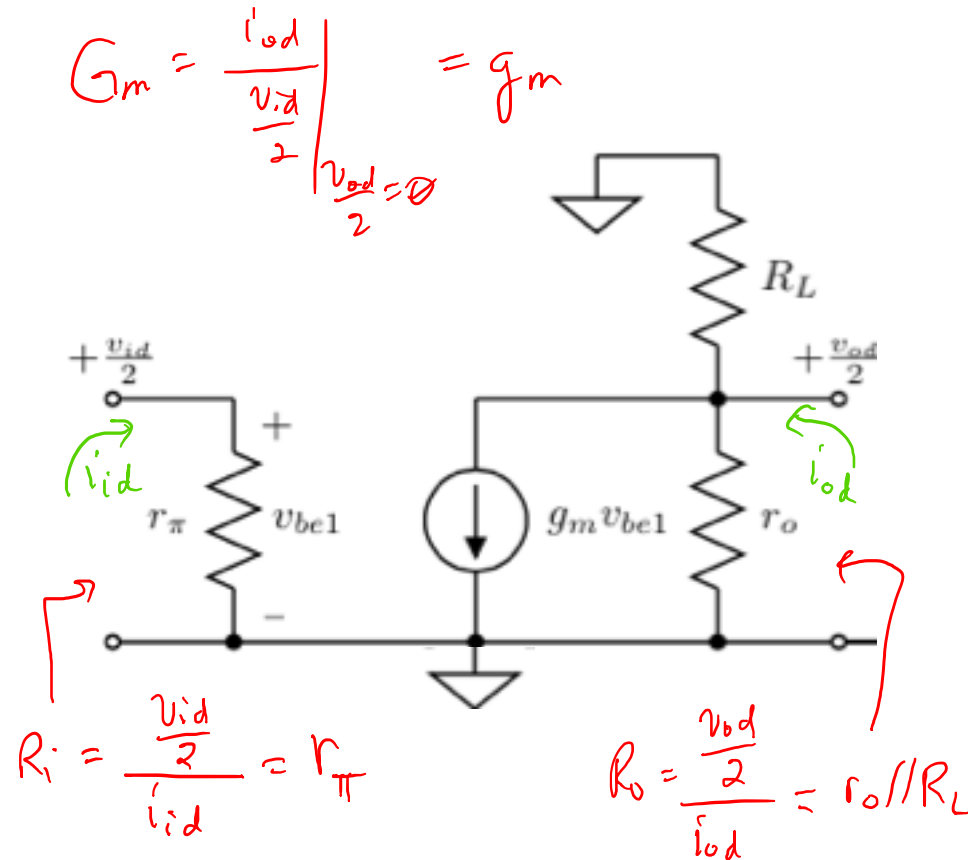

$$A_{dm} = \frac{+\frac{v_{od}}{2}}{+\frac{v_{id}}{2}} = \frac{v_{od}}{v_{id}} = -g_m \cdot (r_o \parallel R_L)$$


$$R_{id} = \frac{v_{id}}{i_{id}} = 2 \cdot r_{\pi}$$

$$R_{od} = \frac{v_{od}}{i_{od}} = 2 \cdot (r_o \parallel R_L)$$


$$G_{md} = \frac{i_{od}}{v_{id}} = \frac{g_m}{2} = \frac{-A_{dm}}{R_{od}}$$



# The Common-Mode Half Circuit

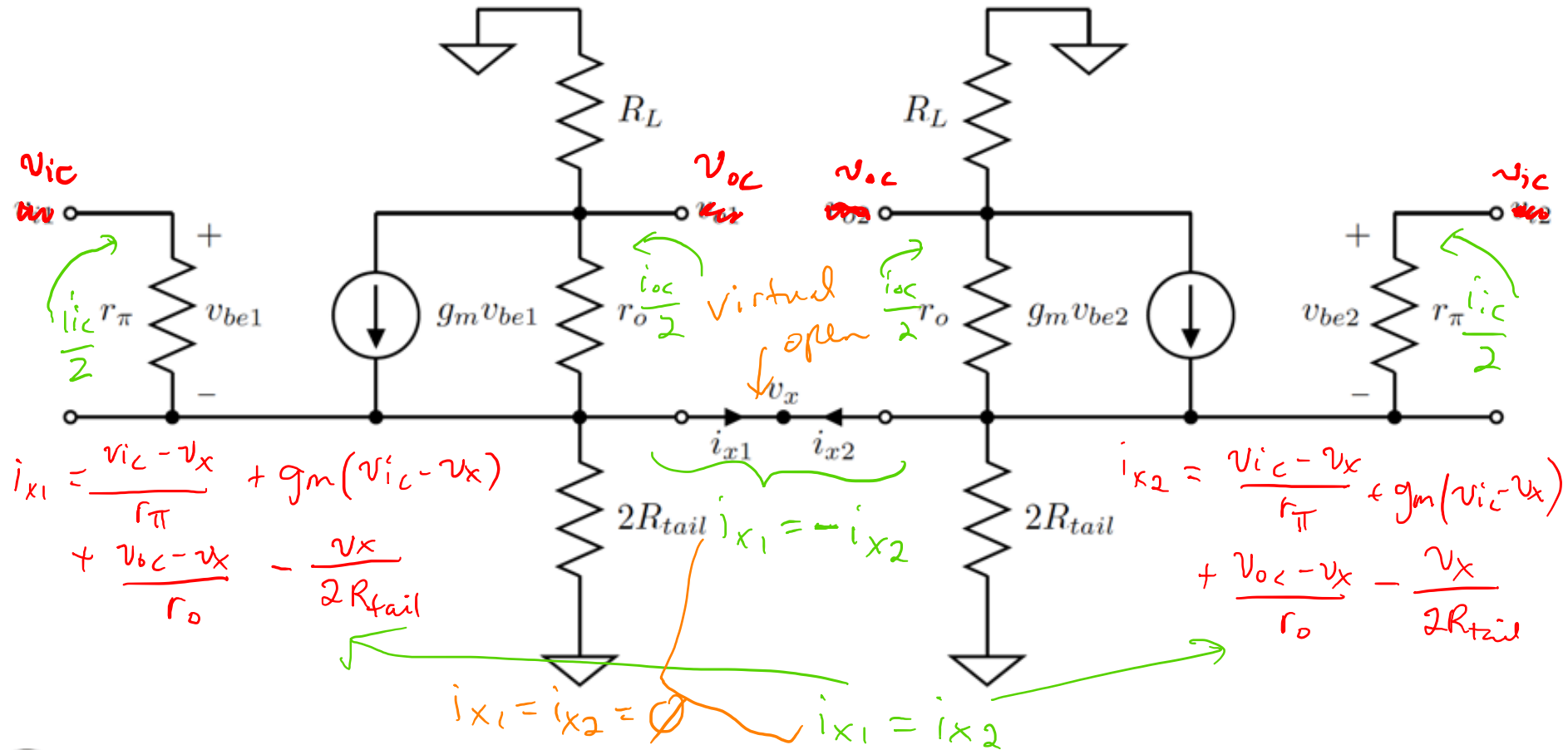

# The Common-Mode Half Circuit

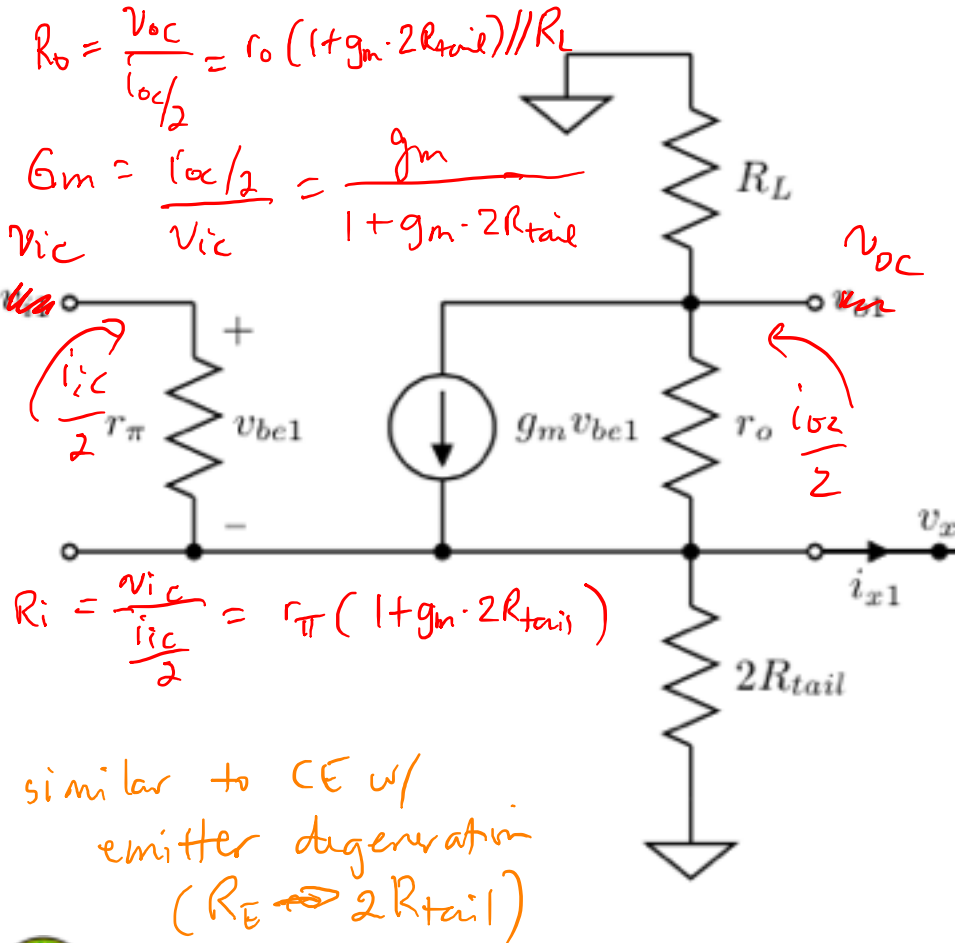

$$A_{cm} = \frac{v_{oc}}{v_{ic}} = -\frac{g_m R_L}{1 + 2 \cdot g_m R_{tail}}$$


$$R_{ic} = \frac{v_{ic}}{i_{ic}} = \frac{r_\pi (1 + 2 \cdot g_m R_{tail})}{2}$$

$$R_{oc} = \frac{v_{oc}}{i_{oc}} = \frac{r_o (1 + 2 \cdot g_m R_{tail}) \parallel R_L}{2}$$


$$G_{mc} = \frac{i_{oc}}{v_{ic}} = \frac{2g_m}{(1 + 2 \cdot g_m R_{tail})}$$


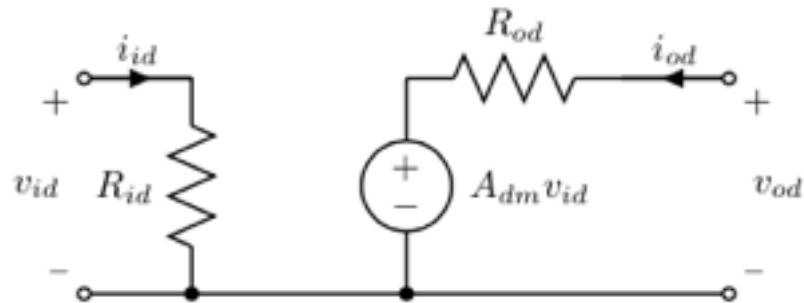
# Small-signal model of differential amplifier



(a) Differential-mode

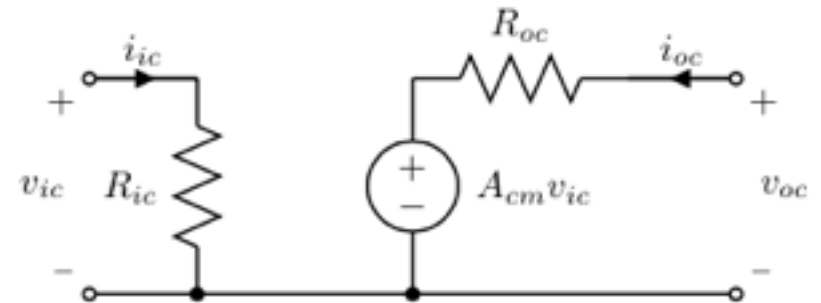


(b) Common-mode

$$v_{o1} = v_{oc} + \frac{v_{od}}{2}$$

$$v_{o2} = v_{oc} - \frac{v_{od}}{2}$$


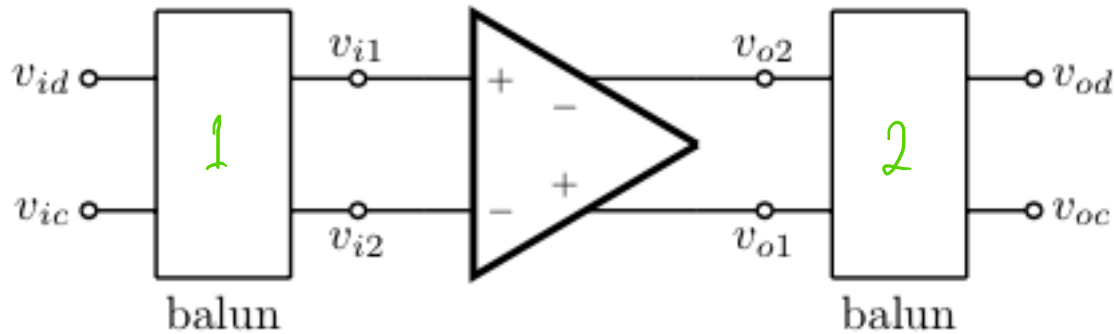
# The Balun (Balanced - Unbalanced Circuit)




$$\begin{aligned}\text{balun 1; } v_{i1} &= v_{ic} + \frac{v_{id}}{2} \\ v_{i2} &= v_{ic} - \frac{v_{id}}{2}\end{aligned}$$

$$\begin{aligned}\text{balun 2; } v_{oc} &= \frac{v_{o1} + v_{o2}}{2} \\ v_{od} &= v_{o1} - v_{o2}\end{aligned}$$







# The Balun

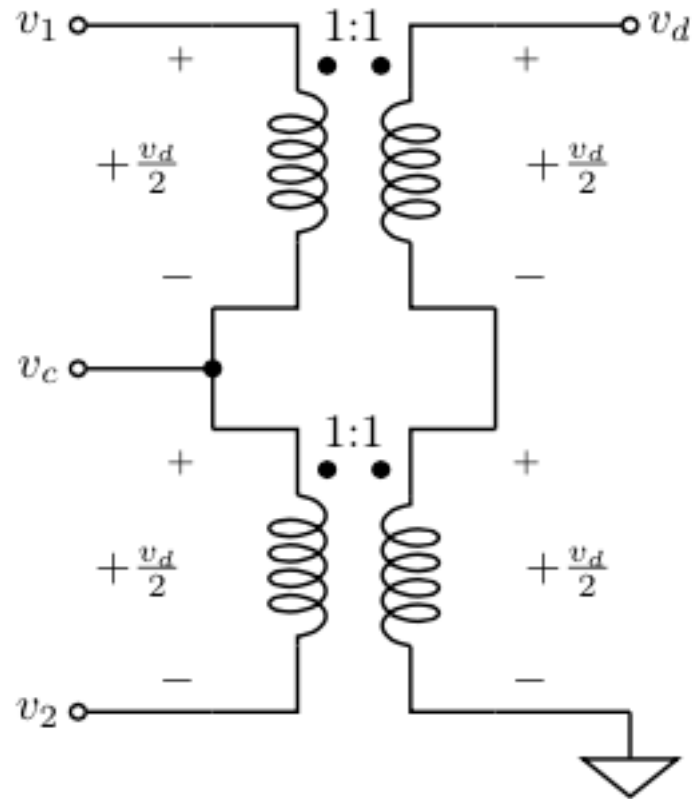

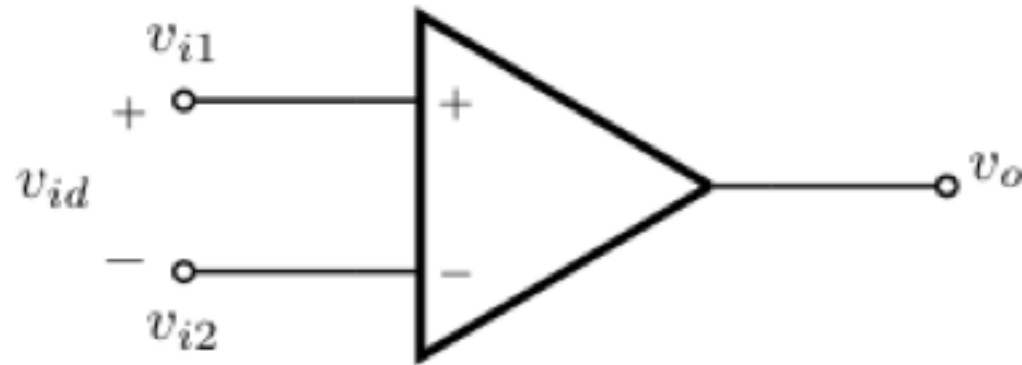
# Differential to Single-Ended Conversion



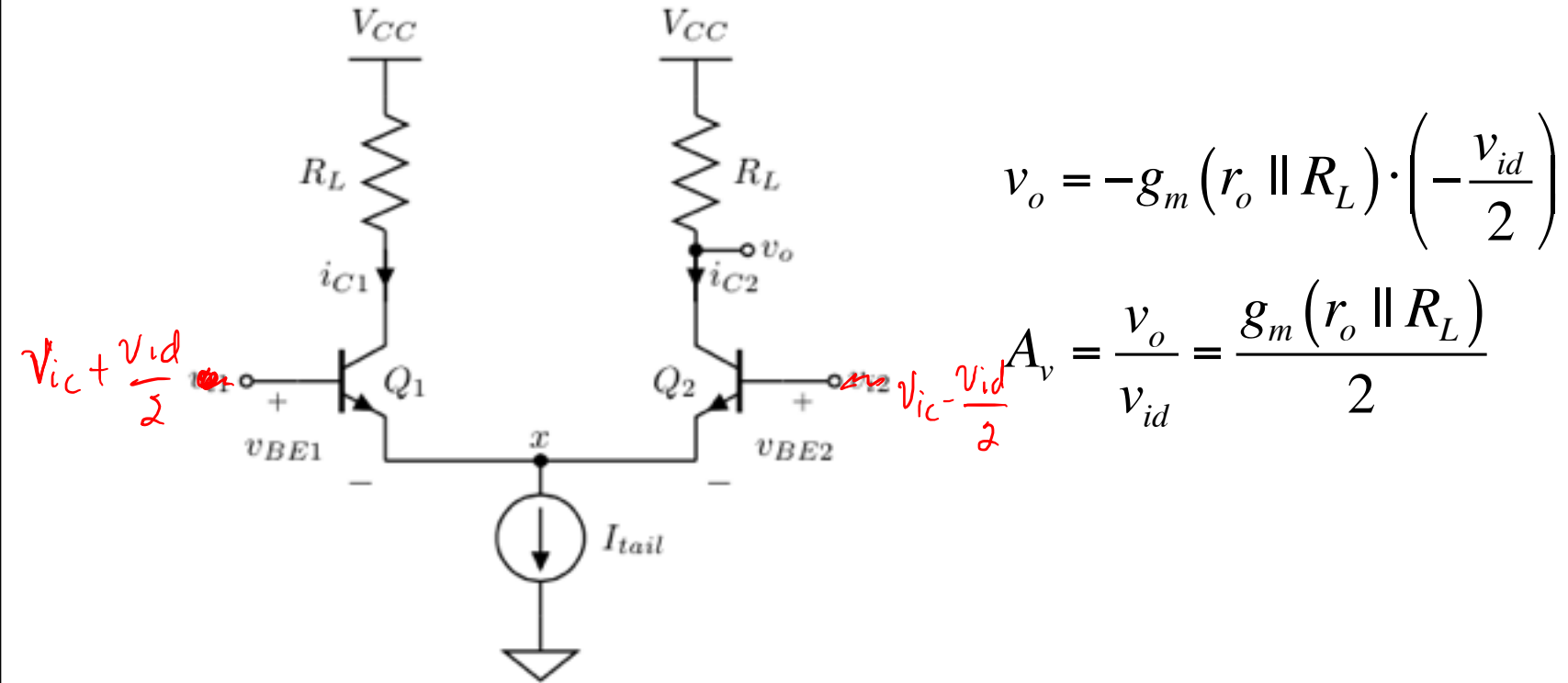
# Differential to Single-Ended Conversion



# The Current Mirror Revisited

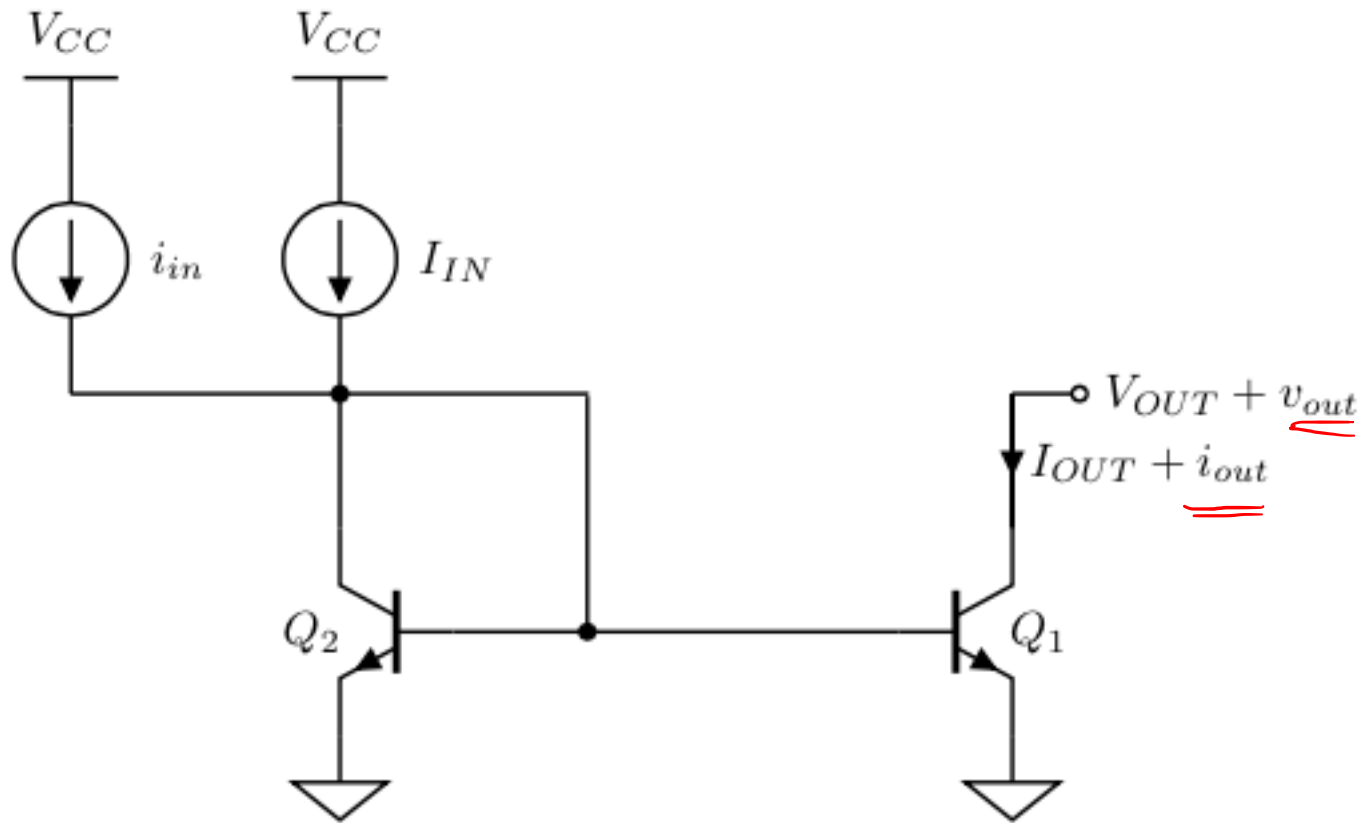

# The Current Mirror Revisited

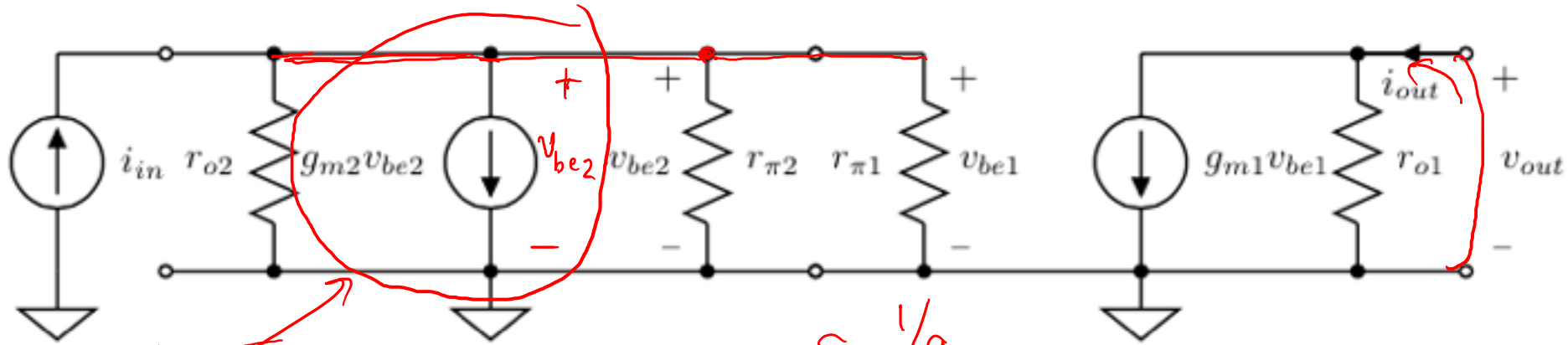

$$v_{be1} = v_{be2} = i_{in} \cdot \left( \frac{1}{g_{m2}} \parallel r_{o2} \parallel r_{\pi1} \parallel r_{\pi2} \right) \approx \frac{i_{in}}{g_{m2}}$$

at no load ;  
( $v_{out} = 0$ )


$$\underline{i_{out}} \approx g_{m1} v_{be1} = \frac{g_{m1}}{g_{m2}} \cdot \underline{i_{in}} \approx \underline{i_{in}}$$

$$g_{m1} = g_{m2}$$


$$\rightarrow \frac{i_{out}}{i_{in}} = 1$$




# Current Mirror Loads

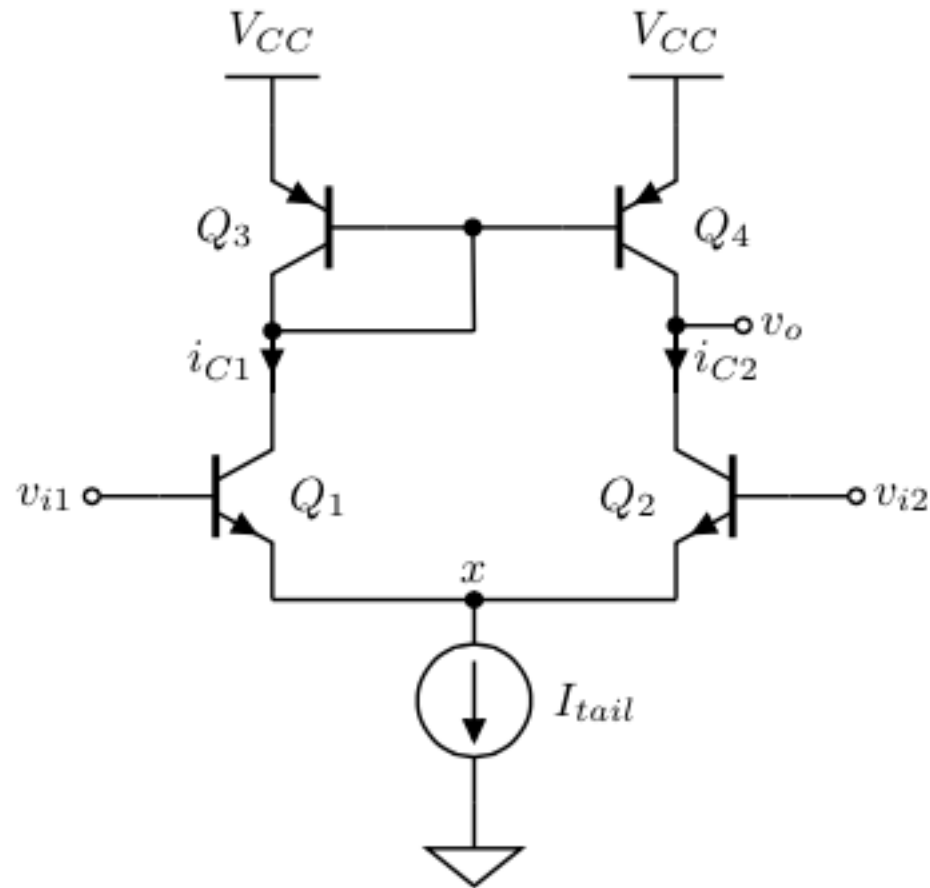

# Current Mirror Loads

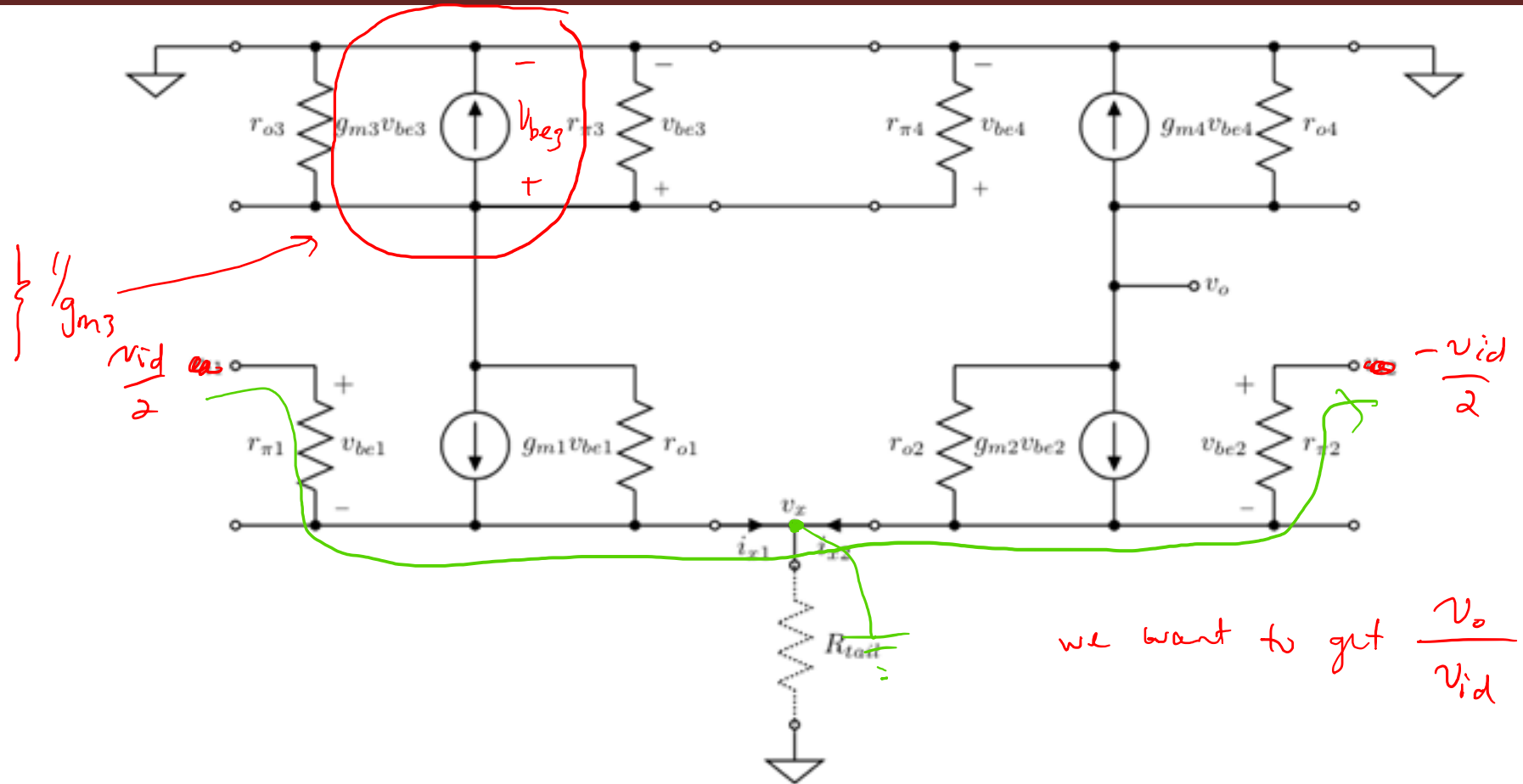

# Current Mirror Loads

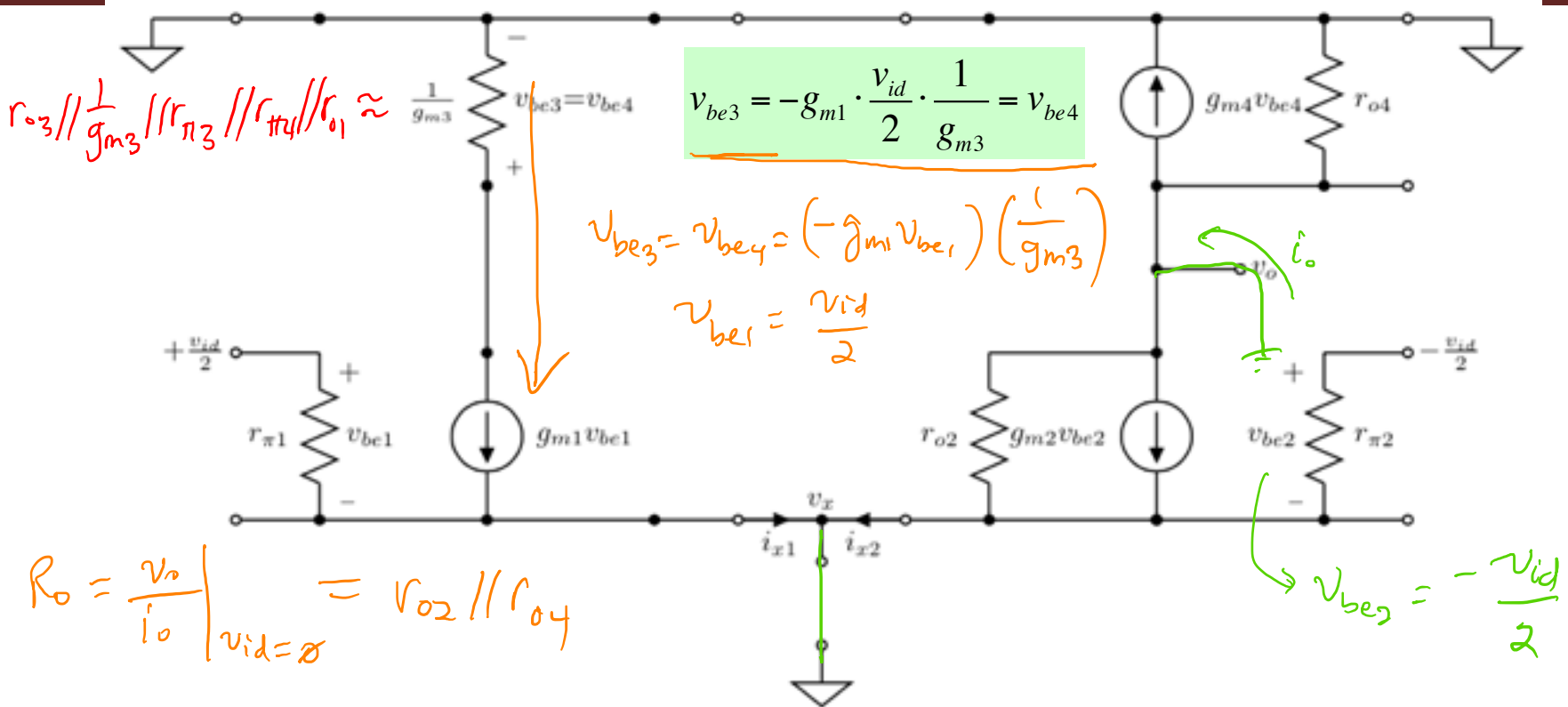

at no load,  $i_o = g_{m4} \cdot \underline{v_{be4}} + g_{m2} \cdot \underline{v_{be2}} = -g_{m4} \cdot g_{m1} \cdot \frac{v_{id}}{2} \cdot \frac{1}{g_{m3}} - g_{m2} \cdot \frac{v_{id}}{2}$

( $v_{out} = 0$ )





# Current Mirror Loads

$$i_o = g_{m4} \cdot v_{be4} + g_{m2} \cdot v_{be2} = -\cancel{g_{m4}} \cdot g_{m1} \cdot \frac{v_{id}}{2} \cdot \frac{1}{\cancel{g_{m3}}} - g_{m2} \cdot \frac{v_{id}}{2}$$


If  $g_{m1} = g_{m2} = g_m$  and  $g_{m3} = g_{m4}$ ,

$$i_o = -g_m \cdot v_{id} \quad ; \quad \frac{i_o}{v_{id}} = -g_m$$

$$G_m = -g_m$$

$$\rightarrow R_o = (r_{o2} \parallel r_{o4})$$
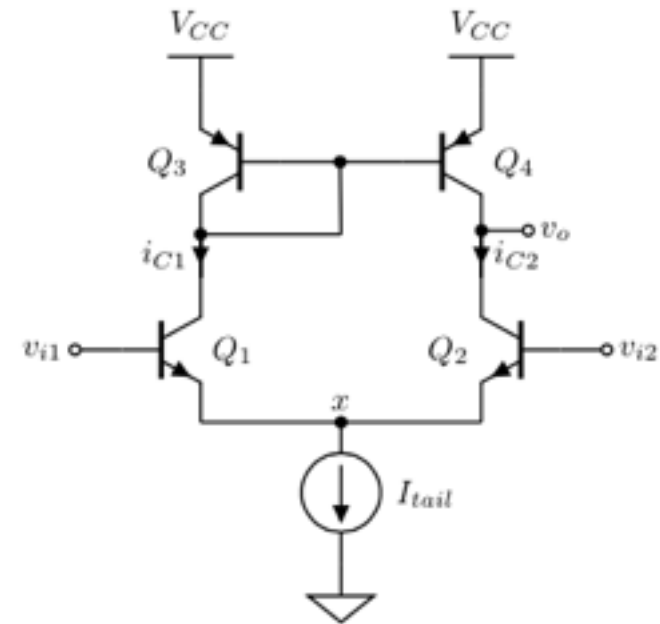
$$A_v = \frac{v_o}{v_{id}} = -G_m R_o = +g_m (r_{o2} \parallel r_{o4})$$



# Next Meeting

- Compound Amplifiers

