



EEE 51: Second Semester 2017 - 2018

Lecture 8

Differential Circuits


Today

- Finish Up Current Mirrors
- Amplifiers Biased Using Current Mirrors
- Differential Circuits



A Simple MOSFET Current Mirror

- No gate currents!

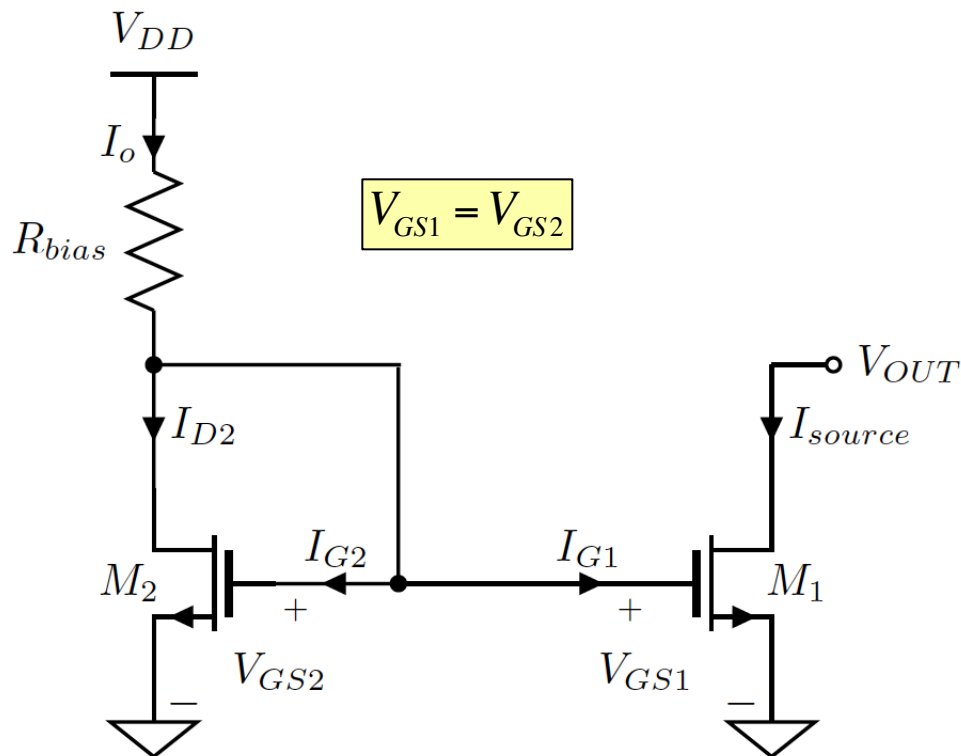

Recall: $V_{GS} = V_{TH} + \sqrt{\frac{I_D}{k(1 + \lambda V_{DS})}}$

$\Rightarrow \frac{I_{D1}}{(1 + \lambda V_{DS1})} = \frac{I_{D2}}{(1 + \lambda V_{DS2})}$

$I_{source} = I_{D2} \frac{(1 + \lambda V_{DS1})}{(1 + \lambda V_{DS2})} = I_o \frac{(1 + \lambda V_{OUT})}{(1 + \lambda V_{GS})}$

Assume $\lambda=0$

$I_{source} \approx I_o$

Mirror!


Mirroring Error:

\rightarrow Due to V_{DS} "mismatch" only




Current Mirror Small Signal Model

- Small Signal Output Resistance?

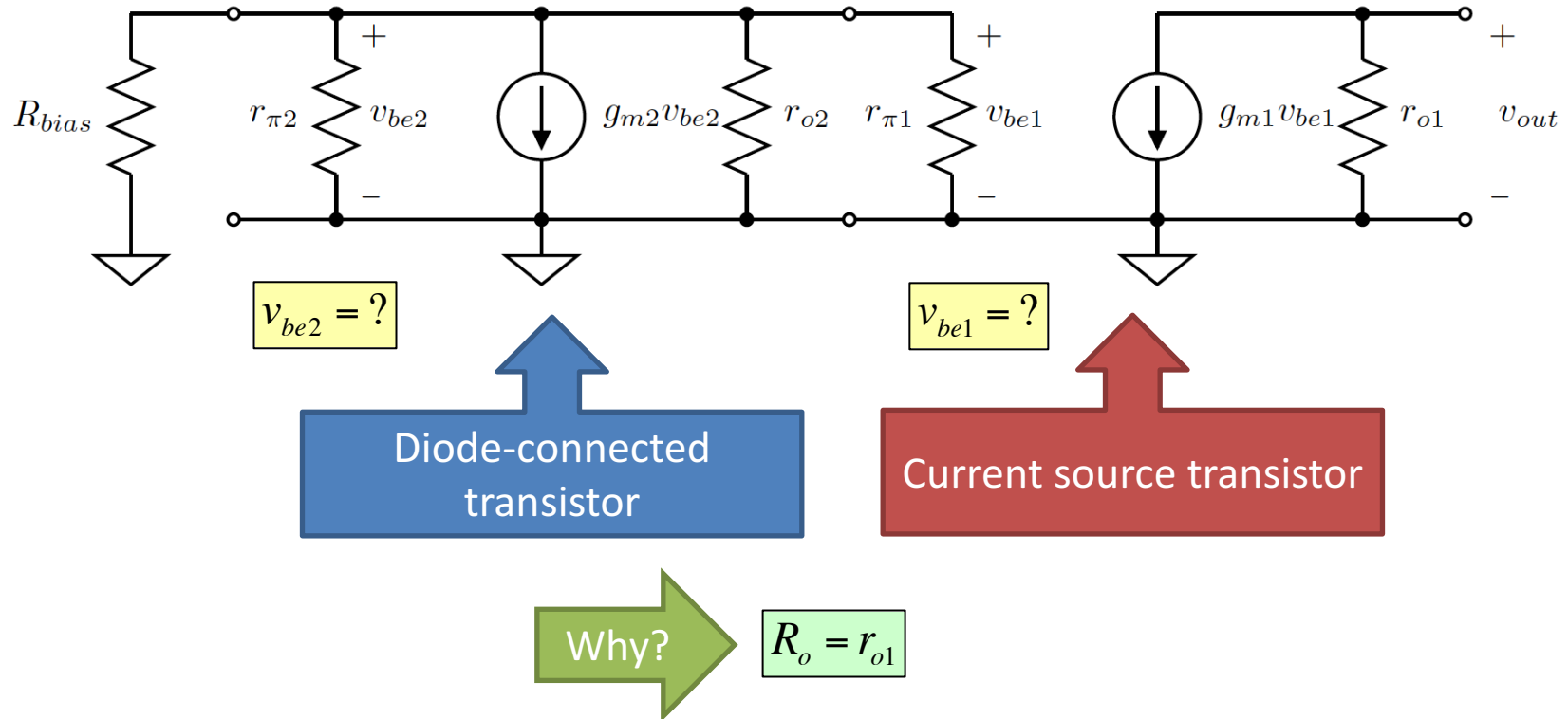


Biasing the Common-Emitter Amplifier (1)

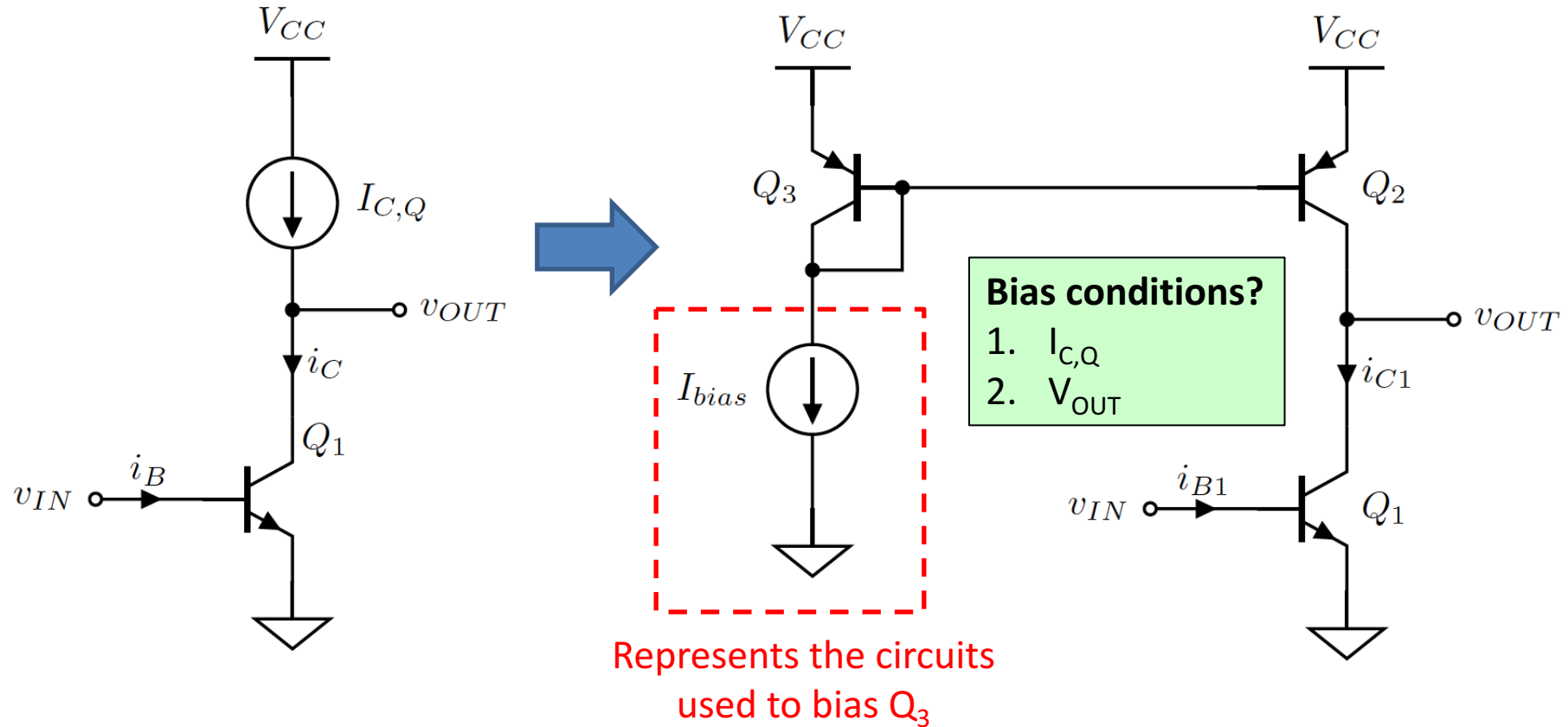

Biasing the Common-Emitter Amplifier (2)

- DC Analysis

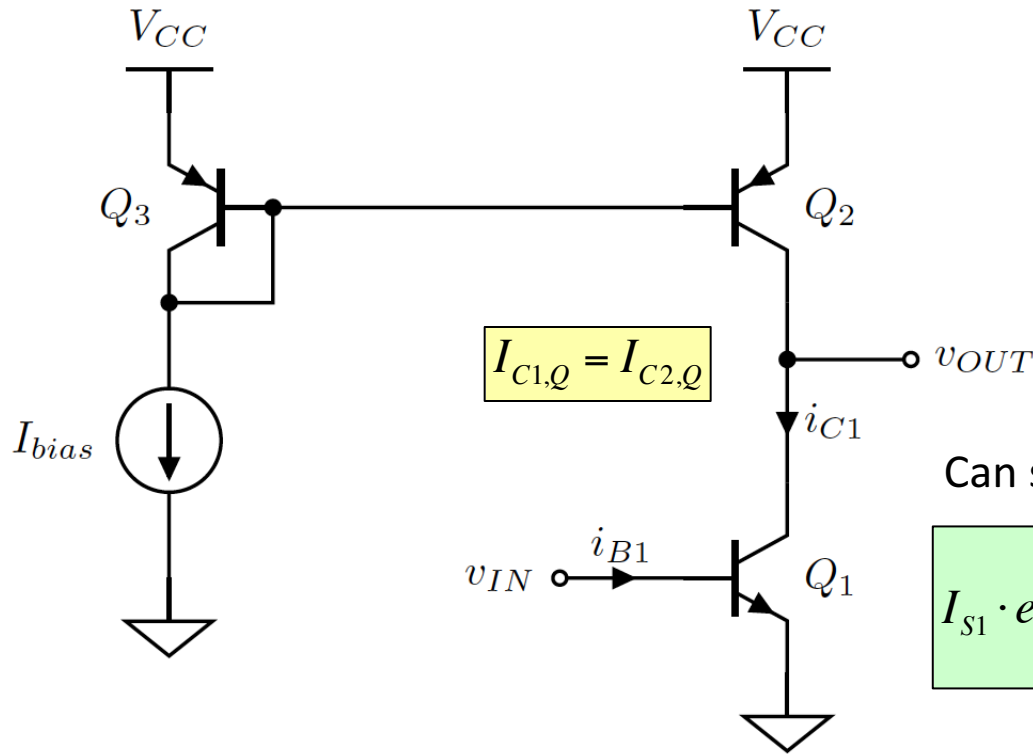

For $V_A \rightarrow \infty$:

$$I_{C,Q} \approx I_{bias}$$

What about V_{OUT} ?

→ Need finite V_A !


→ Why?

Can solve for V_{OUT} :

$$I_{S1} \cdot e^{\frac{V_{IN}}{V_T}} \cdot \left(1 + \frac{V_{OUT}}{V_{A1}}\right) = I_{S2} \cdot e^{\frac{|V_{BE2}|}{V_T}} \cdot \left(1 + \frac{|V_{CC} - V_{OUT}|}{V_{A2}}\right)$$

Biasing the Common-Emitter Amplifier (3)

- Small Signal Model

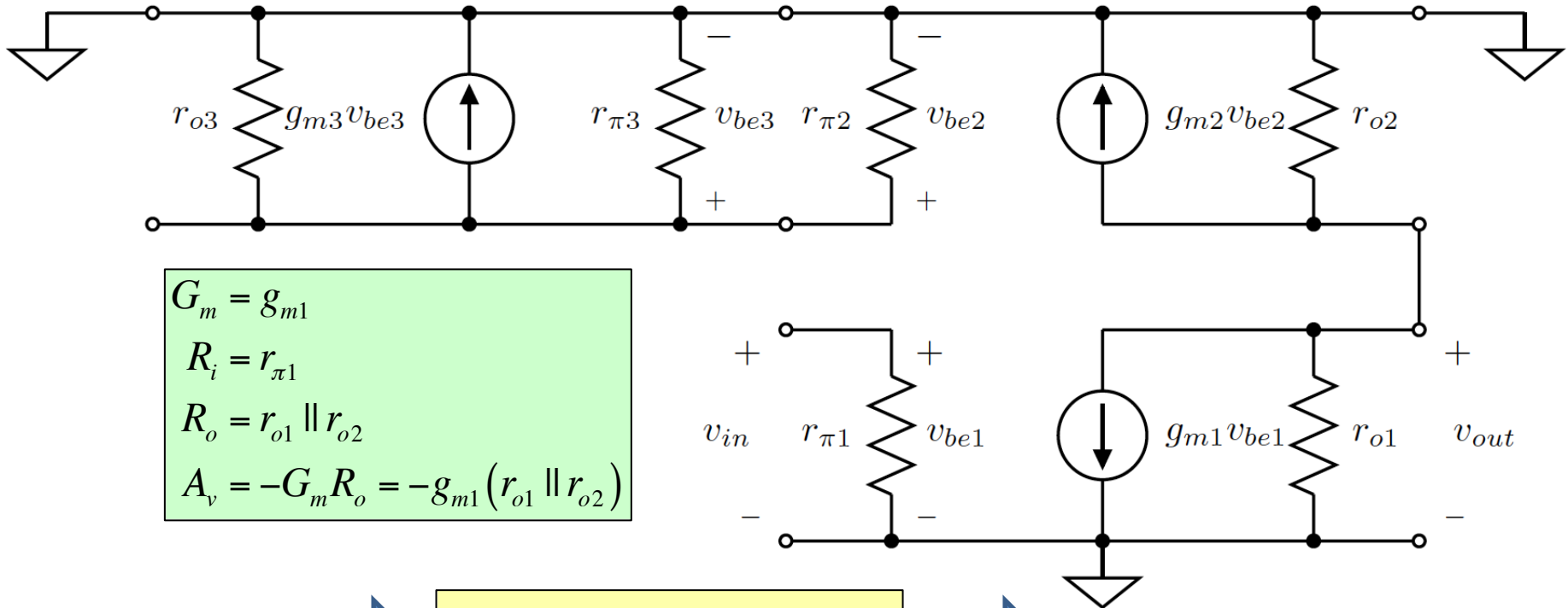

If $r_{o1} \approx r_{o2}$ \Rightarrow $A_v = -g_{m1} (r_{o1} \parallel r_{o2}) \approx -\frac{g_{m1} r_{o1}}{2}$ \Rightarrow Already half a_o !


Differential Circuits

- Building Blocks (so far...)
 - Single-stage amplifiers
 - Current mirrors
 - **Differential Pair**




Differential Signals (1)

- Consider a pair of wires

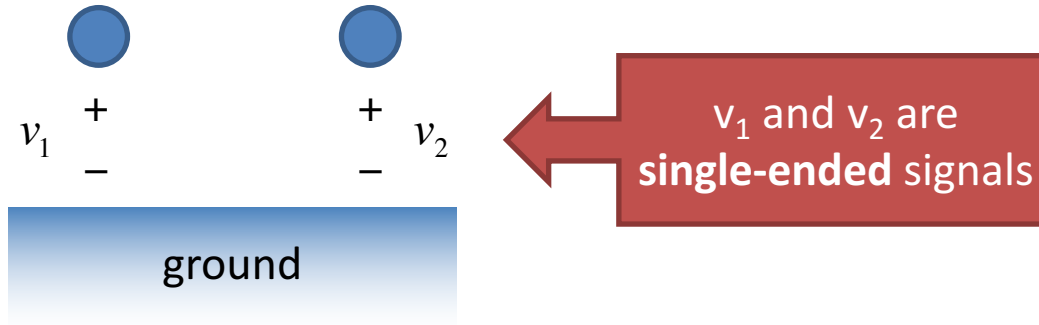

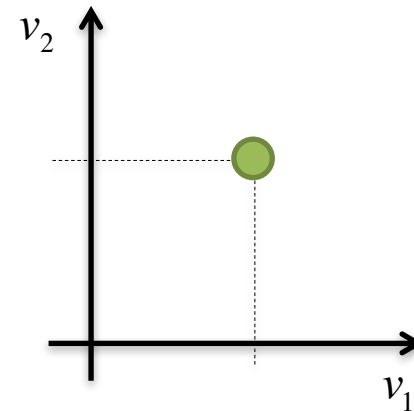
In this case, with two wires, to completely describe the system, we need both v_1 and v_2



How about another set of coordinates?

Differential Signals (2)



- Definitions

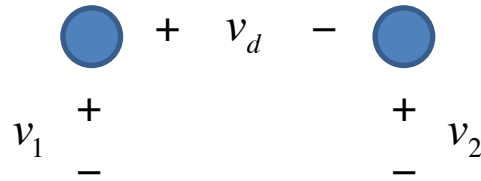

Same point, different
coordinate system


Differential voltage

$$v_d = v_1 - v_2$$

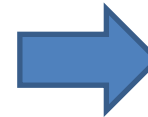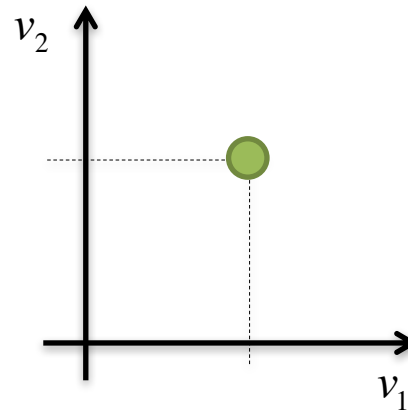


Common-mode voltage

$$v_c = \frac{v_1 + v_2}{2}$$

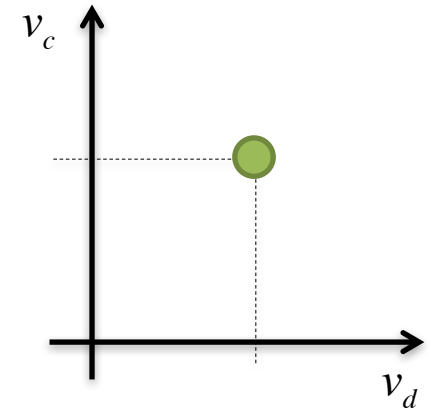



Differential Signals (3)

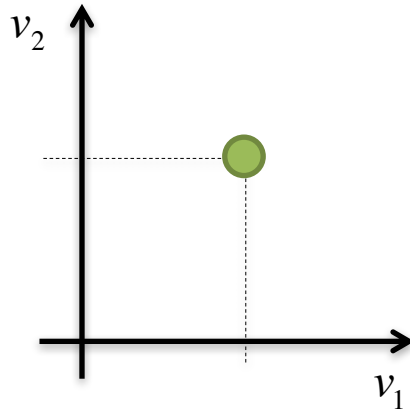- Can easily go from single-ended to differential



$$v_1 = v_c + \frac{v_d}{2}$$

$$v_2 = v_c - \frac{v_d}{2}$$

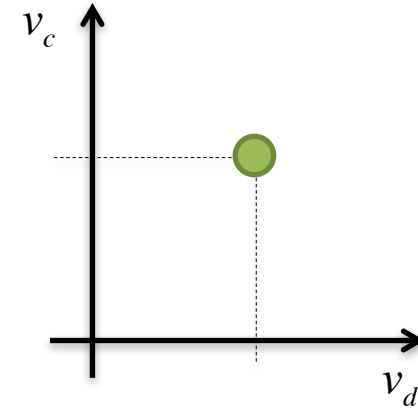
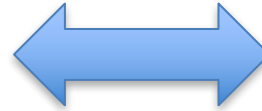


$$v_d = v_1 - v_2$$

$$v_c = \frac{v_1 + v_2}{2}$$

Differential Amplifiers: Gain Definitions

- A Fully-Differential Amplifier

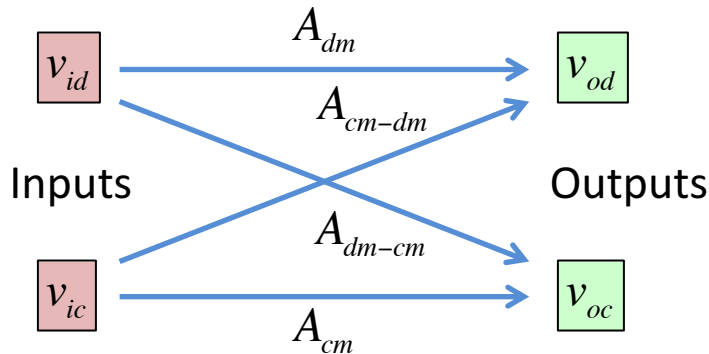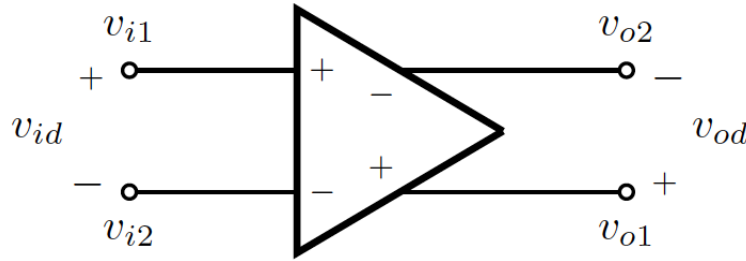

Works with differential signals

$$A_{dm} = \left. \frac{v_{od}}{v_{id}} \right|_{v_{ic}=0} \quad A_{cm} = \left. \frac{v_{oc}}{v_{ic}} \right|_{v_{id}=0}$$

$$A_{dm-cm} = \left. \frac{v_{oc}}{v_{id}} \right|_{v_{ic}=0} \quad A_{cm-dm} = \left. \frac{v_{od}}{v_{ic}} \right|_{v_{id}=0}$$




$$\begin{aligned} v_{od} &= A_{dm} v_{id} + A_{cm-cm} v_{ic} \\ v_{oc} &= A_{dm-cm} v_{id} + A_{cm} v_{ic} \end{aligned}$$

Inversion comes for FREE!






Why Use Differential Signaling? (1)

- Differential vs. single-ended signals

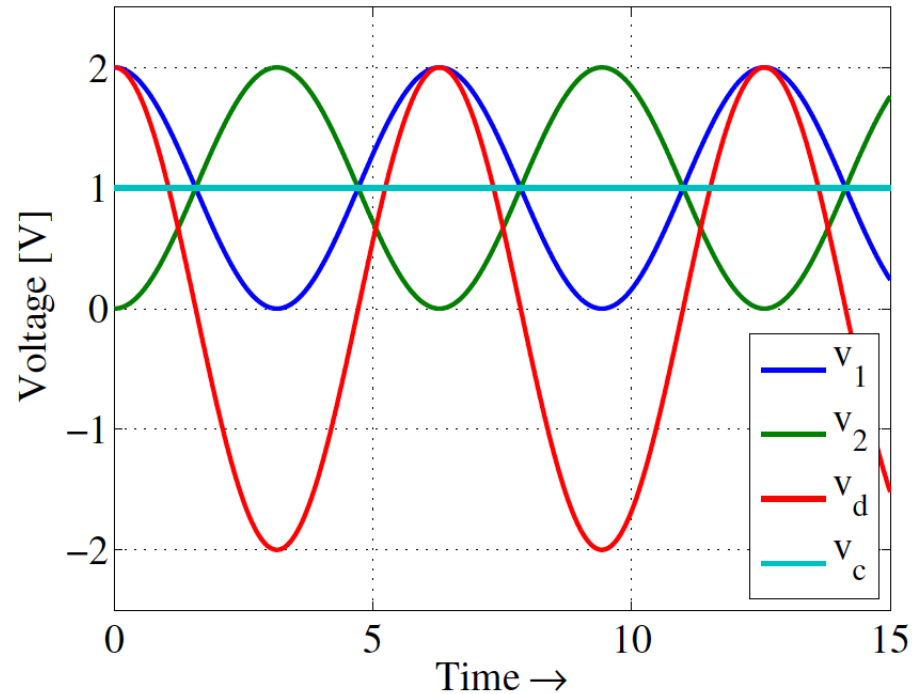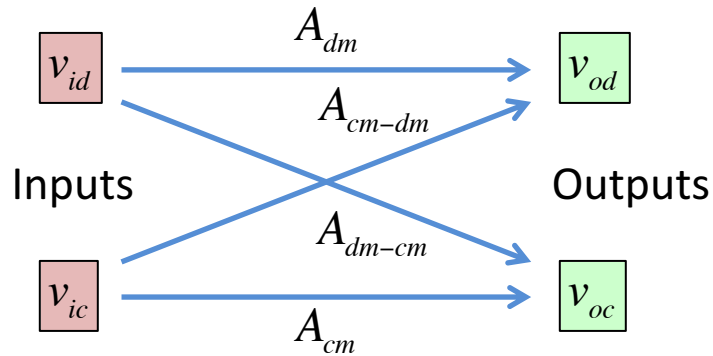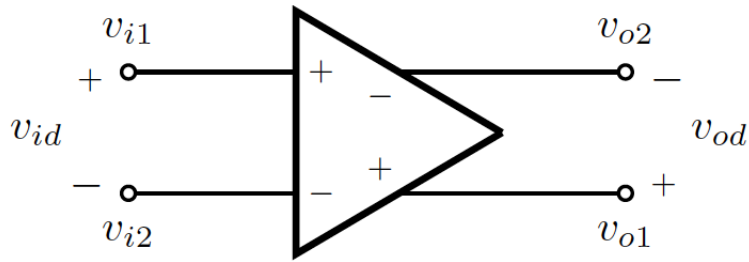

Why Use Differential Signaling? (2)

- Common-mode noise or interference

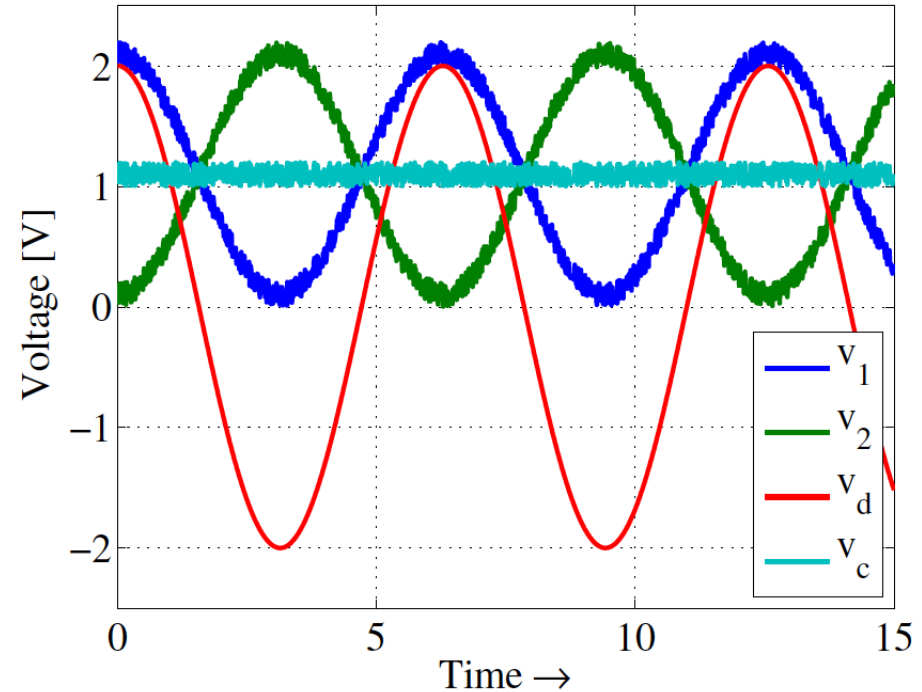
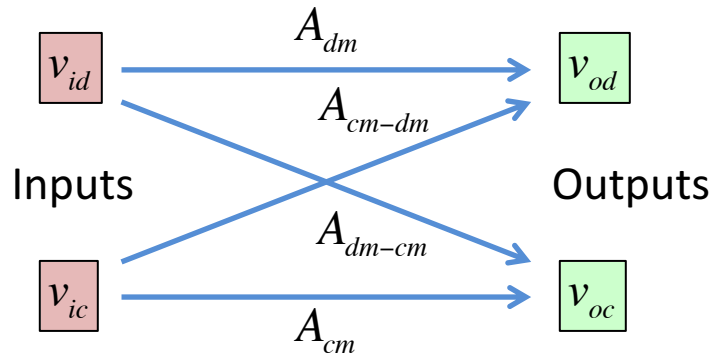
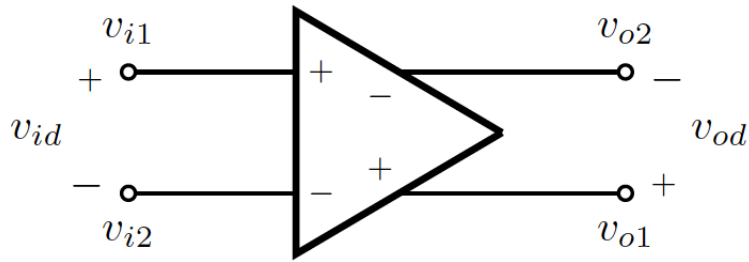


Anything common to both v_1 and v_2 will not be seen in v_{id} !




Why Use Differential Signaling? (3)

- Amplify v_{id} , reject v_{ic}

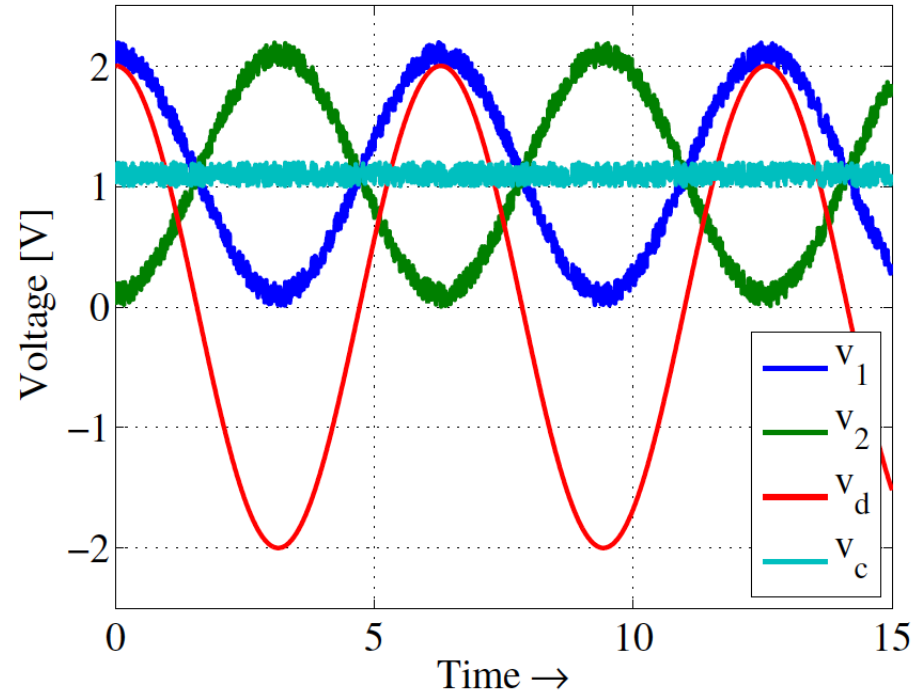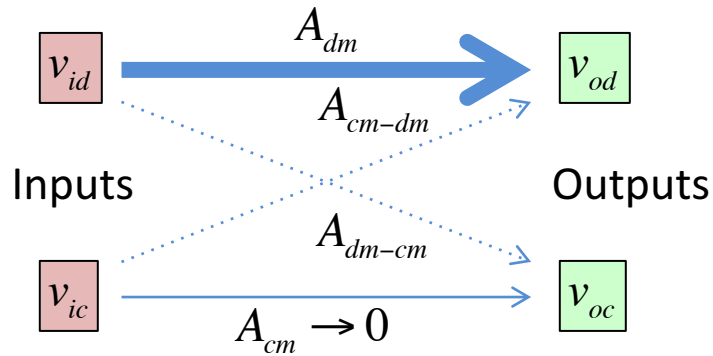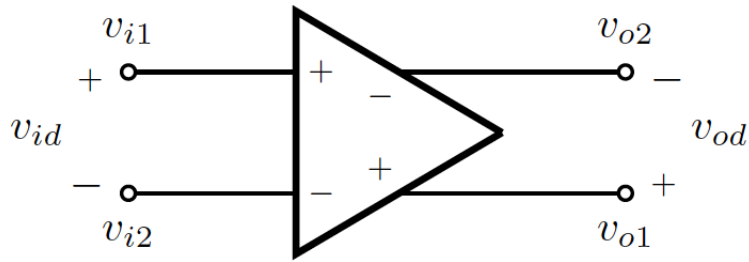


Metric:
Common-Mode
Rejection Ratio

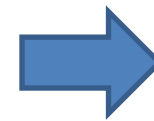

$$CMRR = \left| \frac{A_{dm}}{A_{cm}} \right|$$

Basic Building Block: The Differential Pair (1)

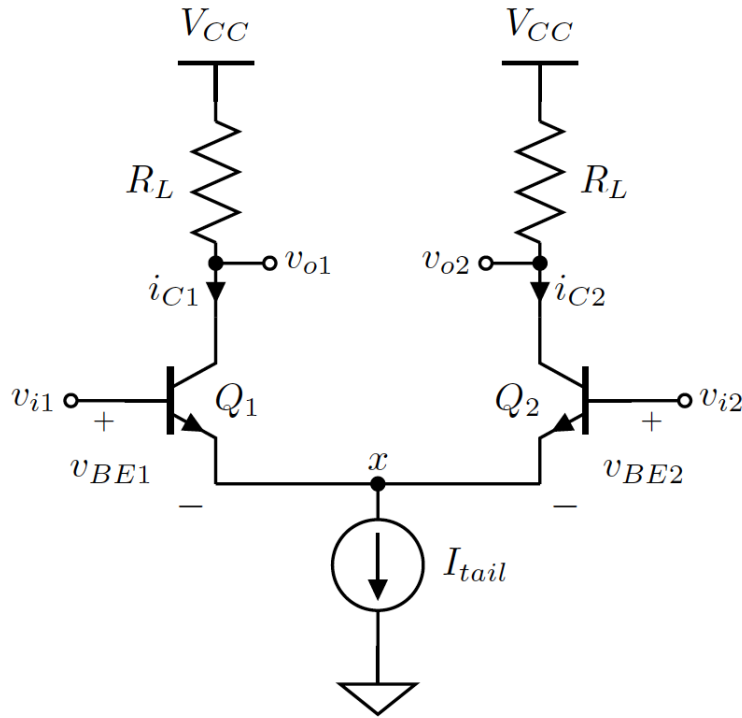- BJT: The emitter-coupled pair DC Analysis



KVL at the input loop: $V_{i1} - V_{BE1} + V_{BE2} - V_{i2} = 0$

$$V_{i1} - V_{i2} = V_{BE1} - V_{BE2}$$


$$V_{id} = V_T \ln\left(\frac{I_{C1}}{I_S}\right) - V_T \ln\left(\frac{I_{C2}}{I_S}\right) = V_T \ln\left(\frac{I_{C1}}{I_{C2}}\right)$$



$$I_{C1} = I_{C2} \cdot e^{\frac{V_{id}}{V_T}}$$

Basic Building Block: The Differential Pair (2)

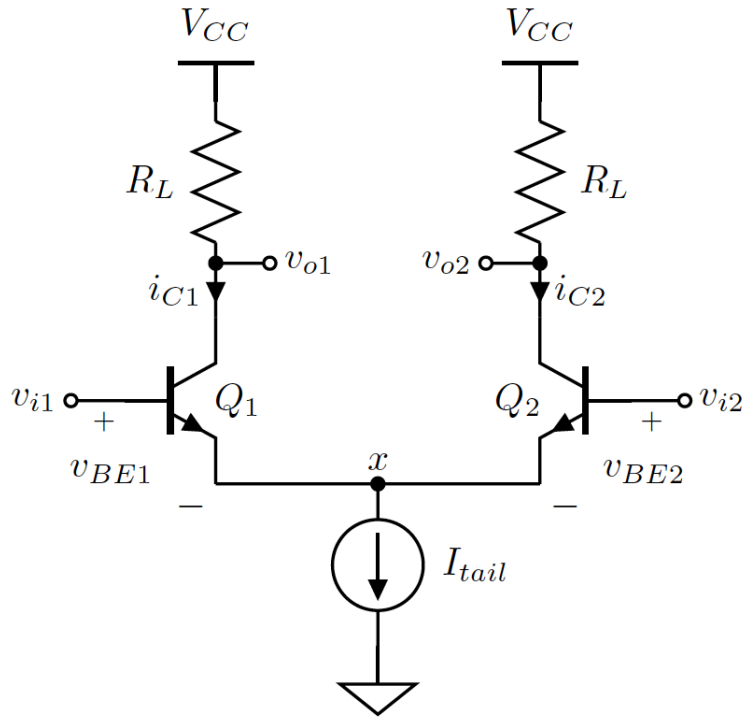- BJT: The emitter-coupled pair DC Analysis



KCL at node x:
$$I_{tail} = I_{E1} + I_{E2} = \frac{I_{C1} + I_{C2}}{\alpha}$$

Recall:

$$I_{C1} = I_{C2} \cdot e^{\frac{V_{id}}{V_T}}$$




$$I_{C1} = \frac{\alpha \cdot I_{tail}}{1 + e^{-\frac{V_{id}}{V_T}}}$$


$$I_{C2} = \frac{\alpha \cdot I_{tail}}{1 + e^{+\frac{V_{id}}{V_T}}}$$

Basic Building Block: The Differential Pair (3)

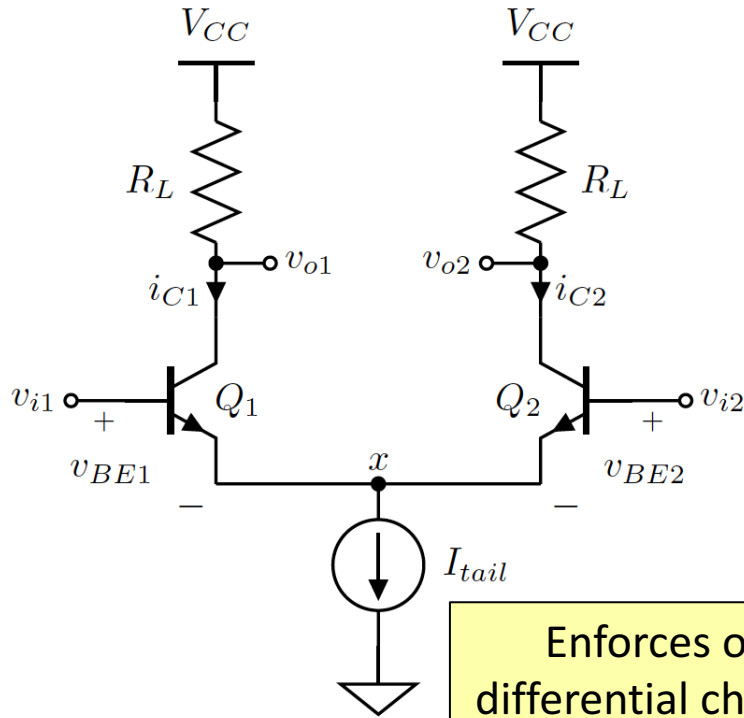- BJT: The emitter-coupled pair DC Analysis



Enforces only
differential changes!

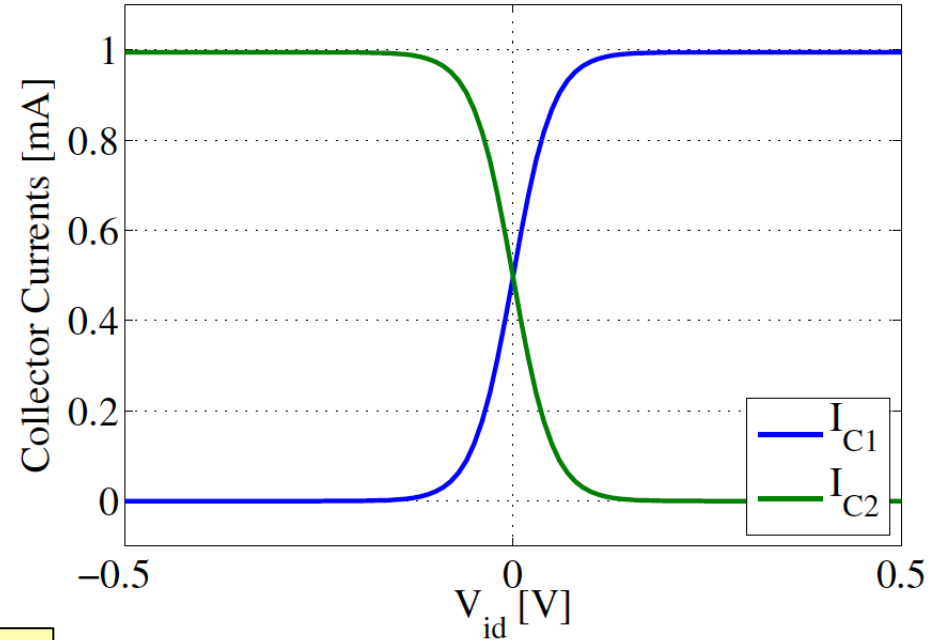


$$I_{C1} = \frac{\alpha \cdot I_{tail}}{1 + e^{\frac{-V_{id}}{V_T}}}$$

$$I_{C2} = \frac{\alpha \cdot I_{tail}}{1 + e^{\frac{+V_{id}}{V_T}}}$$

Basic Building Block: The Differential Pair (4)

- Output Voltage

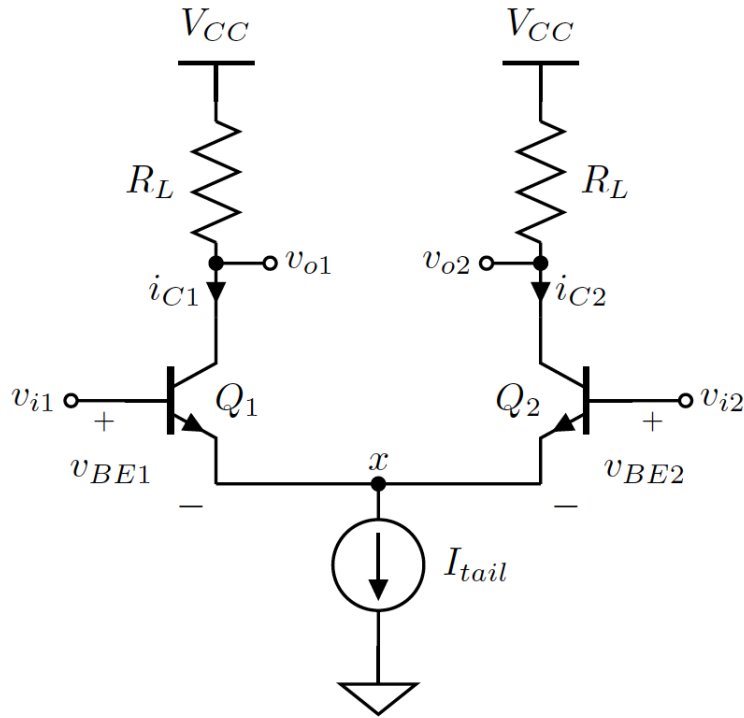

$$I_{C1} = \frac{\alpha \cdot I_{tail}}{1 + e^{-\frac{V_{id}}{V_T}}}$$

$$I_{C2} = \frac{\alpha \cdot I_{tail}}{1 + e^{+\frac{V_{id}}{V_T}}}$$



KVL at the
output loop:

$$V_{od} = V_{o1} - V_{o2} = R_L (I_{C2} - I_{C1})$$

$$\begin{aligned} V_{od} &= \alpha \cdot I_{tail} \cdot R_L \cdot \left(\frac{1}{1 + e^{+\frac{V_{id}}{V_T}}} - \frac{1}{1 + e^{-\frac{V_{id}}{V_T}}} \right) \\ &= \alpha \cdot I_{tail} \cdot R_L \cdot \tanh \left(-\frac{V_{id}}{2 \cdot V_T} \right) \end{aligned}$$

Basic Building Block: The Differential Pair (5)

- Transfer Characteristic

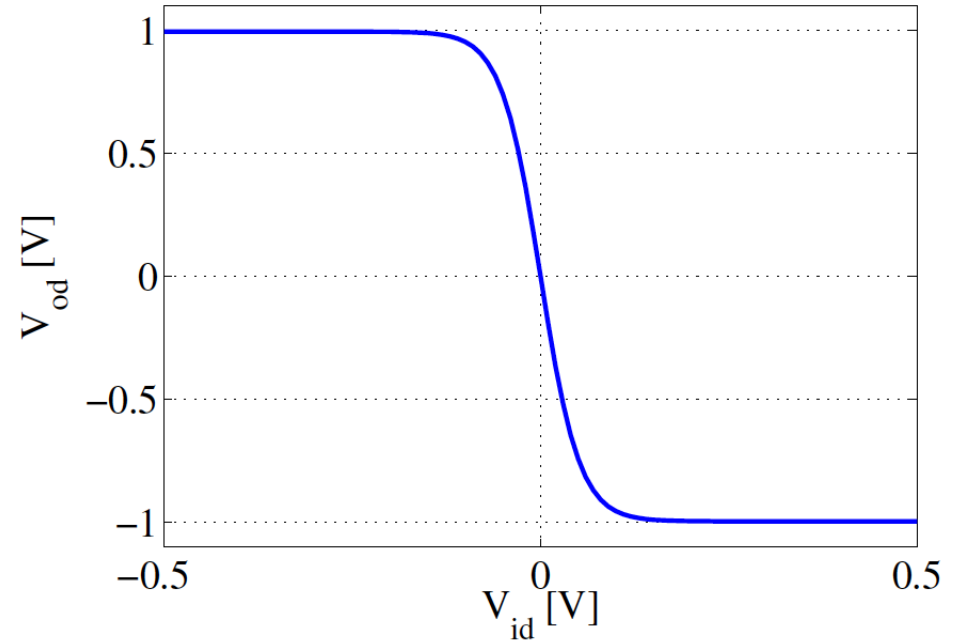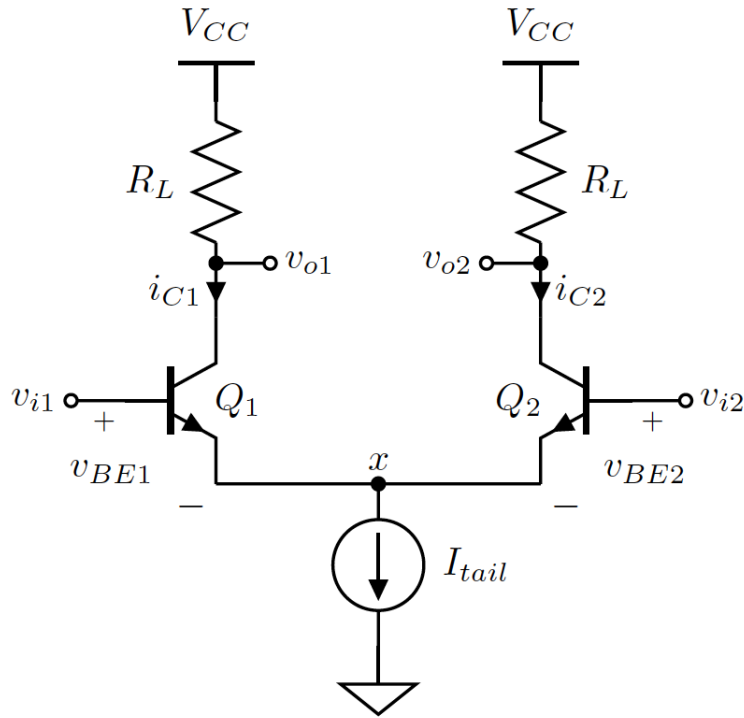

$$V_{od} = \alpha \cdot I_{tail} \cdot R_L \cdot \tanh\left(-\frac{V_{id}}{2 \cdot V_T}\right)$$

Next Meeting

- Continue with Differential Circuits

