

# Lecture

## Three Phase Power Equations

### Agenda

- **Lecture**


R.D. del Mundo  
Ivan B.N.C. Cruz  
Christian. A. Yap



**Electrical and Electronics Engineering Institute**  
**University of the Philippines**

R. D. del Mundo  
EEE 103 AY2010-11 S2

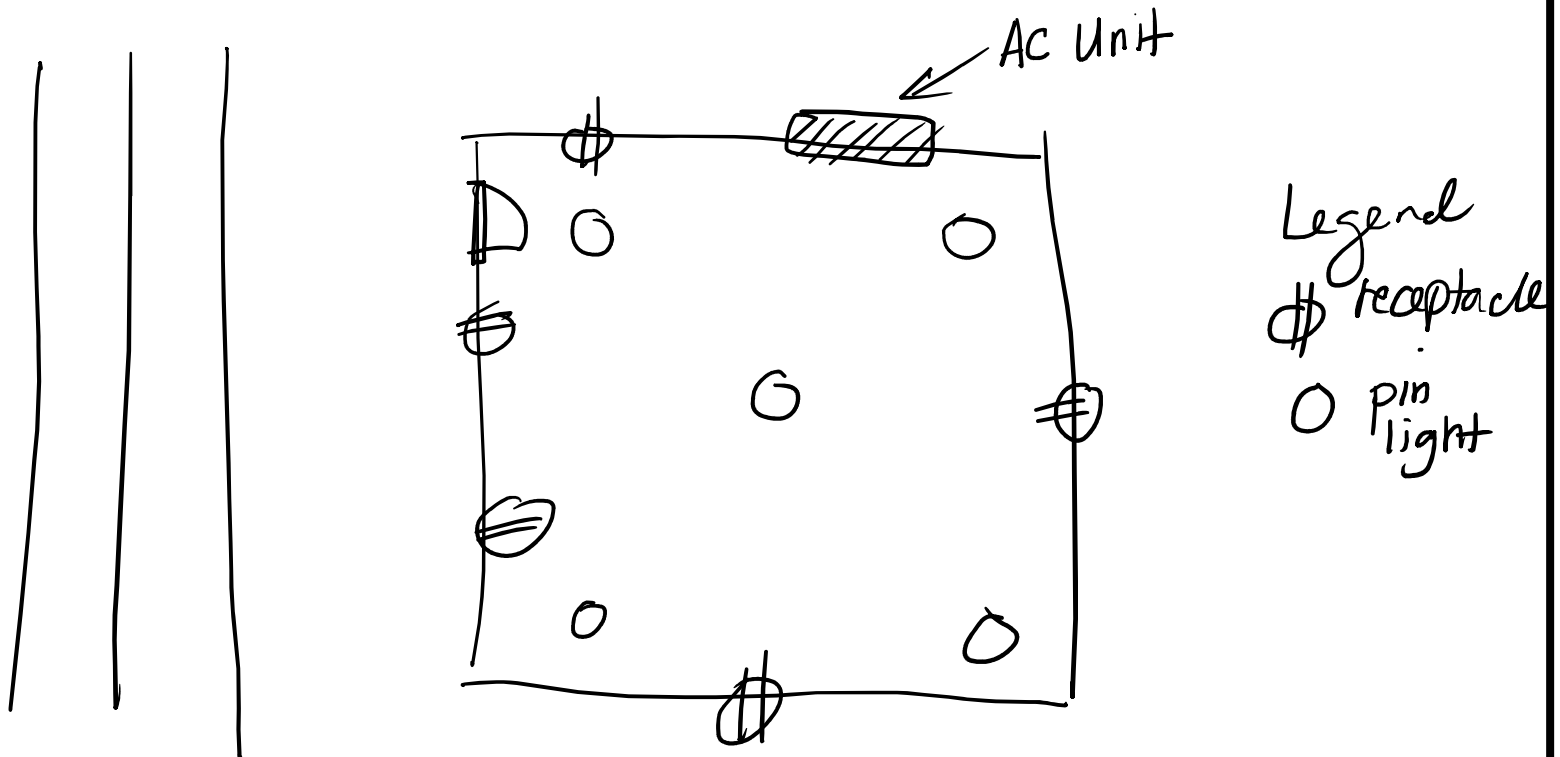
# How is power in three phase systems distributed?


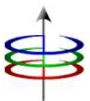
# Lecture Outcomes

at the end of the lecture, the student must be able to ...

- Formulate and Solve Complex Power Equations in Three-Phase AC Systems



## Single-Phase Power Equations

For a single-phase system:

$$P_p = V_p I_p \cos\theta$$

$$Q_p = V_p I_p \sin\theta$$

$$S_p = V_p I_p^* = P_p + jQ_p$$

where:

$V_p$  = magnitude of voltage per phase

$I_p$  = magnitude of current per phase

$\theta$  = phase angle displacement between  $V_p$  and  $I_p$



## Three-Phase Power Equations

For a three-phase system:

$$P_{3\phi} = 3V_p I_p \cos \theta$$

$$Q_{3\phi} = 3V_p I_p \sin \theta$$

$$S_{3\phi} = 3V_p I_p^* = P_{3\phi} + jQ_{3\phi}$$

**Note:**  $V_p$  and  $I_p$  are per-phase (per leg) quantities; the equations here hold whether the system is wye- or delta-connected.



## Three-Phase Power Equations

For a wye-connected system:

$$V_p = \frac{V_{LL}}{\sqrt{3}}$$

$$I_p = I_L$$

For a delta-connected system:

$$V_p = V_{LL}$$

$$I_p = \frac{I_L}{\sqrt{3}}$$

Whether wye- or delta-connected:


$$P_{3\phi} = \sqrt{3} V_L I_L \cos \theta$$

$$Q_{3\phi} = \sqrt{3} V_L I_L \sin \theta$$

$$S_{3\phi} = P_{3\phi} + jQ_{3\phi}$$

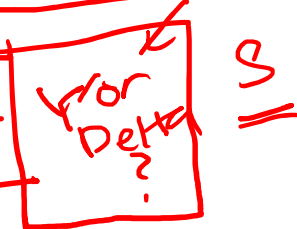**Note:**  $\theta$  is the angle between  $V_p$  and  $I_p$ , NOT between  $V_L$  and  $I_L$ .





## Conventions for this Class

Unless otherwise stated, for our class:

- “Power” = Real Power.

Take note of the context:

- ☞ Total three-phase real power, if for three-phase systems.
- ☞ Single-phase real power, if for single-phase systems.

- “Current” = Line current (rms value only).
- “Voltage” = Line-to-line voltage (rms value only).

Note: These definitions will prove useful once we get to per unit systems.





## EXAMPLE

A three-phase motor draws 20-kVA at 0.707 pf lag from a 220-V source. A wye connected capacitor bank is connected in parallel with the motor to improve the power factor. Determine the following:


- (a) Motor Line current (3 pts)
- (b) The kVA rating of capacitors to make the combined load have pf = 0.90 lag.(4 pts)
- (c) Line current of combined load (3 pts)





Motor	Capacitor	Total
$P_M = 14.14 \text{ kW}$ $Q_M = 14.14 \text{ kVar}$	$P_C = 0$ $Q_C = -X$	$P_{Tot} = 14.14 \text{ kW}$ $Q_{tot} = 14.14 \text{ kvars} - X$
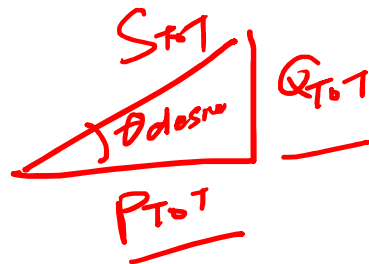
$$\cos \theta_{desired} = 0.9 \text{ pf}$$



$$\tan \theta_{desired} = \frac{Q_{tot}}{P_{tot}}$$

$$\tan \cos^{-1} 0.9 = \frac{14.14 \text{ k} - X}{14.14 \text{ kW}}$$

$$X = ? = \underline{7.43 \text{ kvars}}$$

$$\text{Rating of capacitors} = \underline{\underline{7.43 \text{ kvars}}}$$



$$\vec{I}_L = \vec{I}_M + \vec{I}_C = 52.49 \angle -45^\circ + 19.486 \angle 90^\circ$$

$$\vec{I}_M = 52.49 \angle -45^\circ = \text{---} \checkmark$$


$$\vec{I}_C = ?$$

$$Q = \sqrt{3} V_L I_L = -7.43 \text{ kvars}$$

$$|I_C| = \frac{-7.43 \text{ kvars}}{-\sqrt{3} (220)} = 19.486$$

$$\vec{I}_C = 19.486 \angle 90^\circ$$



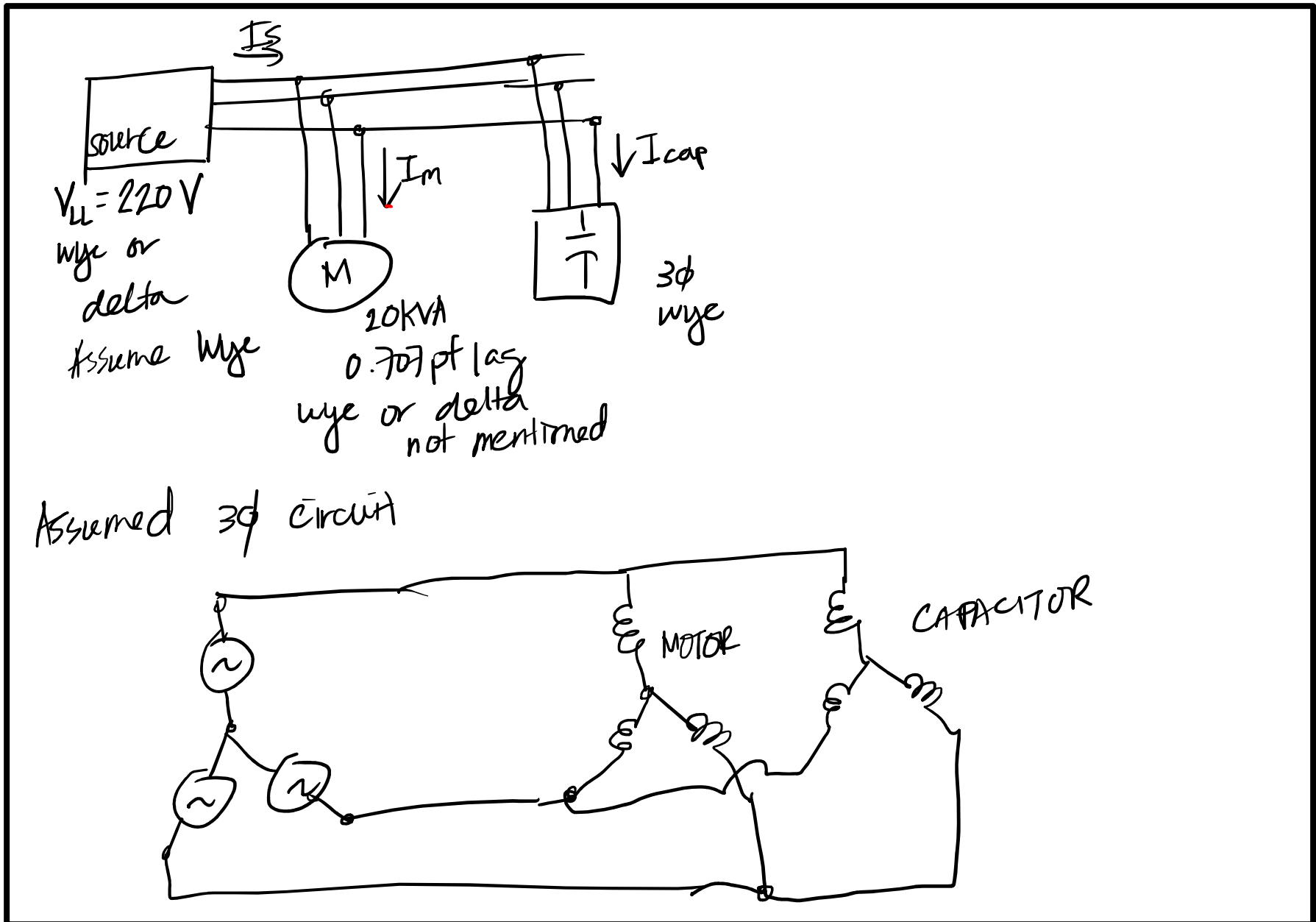

1) Equivalent circuit

Recall  $S = VI^*$

$$I_m = \left( \frac{S_m}{V} \right)^*$$

$$S_m = \frac{20}{3} \angle \cos^{-1} 0.707 \text{ kVA}$$

$$I_m = \frac{\frac{20}{3} \angle -\cos^{-1} 0.707 \text{ kVA}}{\frac{220}{\sqrt{3}} \angle 0^\circ \text{ V}} \quad |I_m| = 52.99 \text{ A}$$

(b)  $\text{pf} = \cos \theta \text{ pf} = \cos \left( \tan^{-1} \frac{Q_s}{P_s} \right) = 0.9$

$$Q_s = Q_m + Q_c = Q_m + Q_c$$

$$P_s = P_m + P_c = P_s$$

$$\cos \left( \tan^{-1} \left( \frac{Q_m + Q_c}{P_c} \right) \right) = 0.9 \rightarrow \tan \cos^{-1} 0.9 = \frac{Q_m + Q_c}{P_c}$$

$$Q_c = P_c \tan \cos^{-1} 0.9 + Q_m$$

$$Q_c = \frac{20}{3} (0.707) \tan \cos^{-1} 0.9 + \frac{20}{3} \tan \cos^{-1} 0.707$$


## HOMEWORK 2

A three-phase line, which has an impedance of  $(2 + j4) \Omega$  per phase, feeds two balanced three-phase loads that are connected in parallel. One of the loads is Y-connected with an impedance of  $(30 + j40) \Omega$  per phase, and the other is  $\Delta$ -connected with an impedance of  $(60 - j45) \Omega$  per phase. The line is energized at the sending end from a 60-Hz, three-phase, balanced voltage source of  $120\sqrt{3}$  V (rms, line-to-line). Determine (a) the current, real power, and reactive power delivered by the sending-end source; (b) the line-to-line voltage at the load; (c) the current per phase in each load; and (d) the total three-phase real and reactive powers absorbed by each load and by the line. Check that the total three-phase complex power delivered by the source equals the total three-phase power absorbed by the line and loads.



# SUMMARY

- Formulating Three Phase Power Equations

