

EEE 51 Assignment 9

2nd Semester SY 2017-2018

Due: 5pm Tuesday, May 8, 2018 (Rm. 220)

Instructions: Write legibly. Show all solutions and state all assumptions. Write your full name, student number, and section at the upper-right corner of each page. Start each problem on a new sheet of paper. Box or encircle your final answer.

Answer sheets should be colored according to your lecture section. The color scheme is as follows:

THQ – yellow

THR – blue

THU – white

THX – green

WFX – pink

1. **What is Feedback?** Chaeyoung is an engineer who is building a communication system. She wants to reduce the effect of noise from unwanted nearby signals by using a negative feedback circuit, which is shown in Figure 1. Assume that the op amp is ideal, and $\beta \rightarrow \infty$ for the transistor.

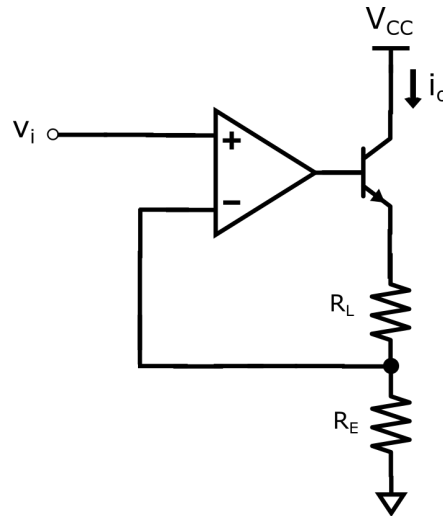


Figure 1: Tzuyu's negative feedback circuit

- (a) What is the quantity being sampled (i.e. what is the output quantity): voltage or current? [0.5 pt]
 - (b) What is the quantity being mixed with the input: voltage or current? [0.5 pt]
 - (c) From your answers in (a) and (b), what type of feedback topology is being used? [1 pt]
 - (d) Recall that the forward gain, A , is the ratio of the output signal (s_o) to the error signal (s_e). Express A in terms of R_L and R_E . [2 pts]
 - (e) On the other hand, the feedback factor F is the ratio of the signal being fed back to the input (s_{fb}) to the output signal (s_o). Express F in terms of R_L and R_E . [2 pts]
 - (f) Given your answers in (d) and (e), what is the closed loop gain, A_{CL} ? [2 pts]
2. **Frequency response of a common emitter amplifier with feedback.** A common emitter amplifier is shown in Figure 2. Given that $V_{CC} = 12\text{ V}$, $V_{IN} = 5\text{ V}$, $V_A = 100\text{ V}$, $I_S = 1\text{ fA}$, $R_S = 10\text{ k}\Omega$, $R_C = 500\text{ }\Omega$, $R_f = 1\text{ k}\Omega$, and $\beta = 50$, answer the following questions.

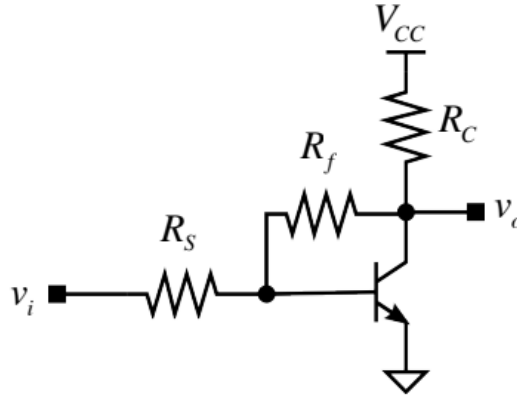


Figure 2: Common Emitter Amplifier with Capacitive Load

- (a) Draw the equivalent small-signal circuit for both open-loop and closed-loop circuits. (Ignore parasitic capacitances.) [4 pts]
 - (b) What is the small-signal open-loop gain of the amplifier? [3 pts]
 - (c) What is the small-signal closed-loop gain of the amplifier? [3 pts]
3. **Analysis of a feedback amplifier.** Consider the feedback amplifier shown in Fig. 3. Provided that all transistors have $\beta \rightarrow \infty$, $V_{be,on} = 0.7V$, $V_A \rightarrow \infty$, an input DC voltage of 1V and an output DC voltage of 1.5V,

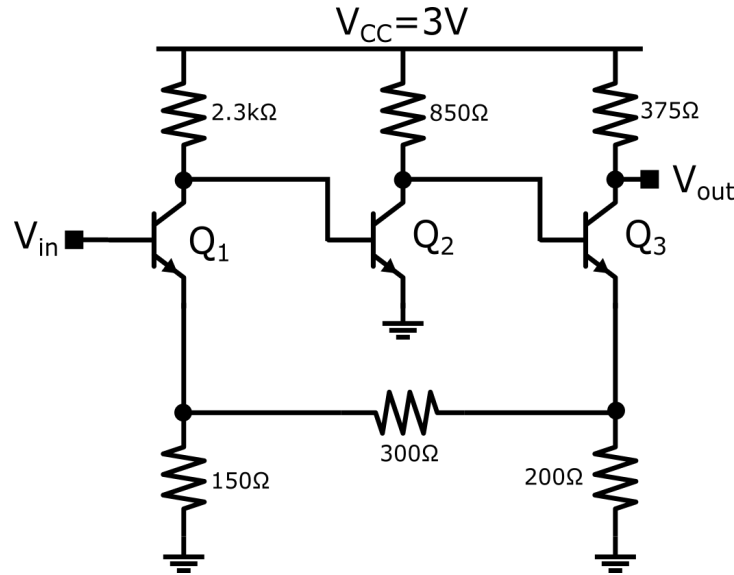


Figure 3: Basic feedback amplifier

- (a) Determine the collector currents and transconductances of Q_1 , Q_2 and Q_3 . [1 pt]
- (b) What type of feedback topology is used in this circuit? Draw the feedback network. [2 pts]
- (c) Find the feedback factor, F , the input and output resistances of the feedback network. [3 pts]
- (d) Draw the small signal model of the amplifier. [2 pts]
- (e) Determine the open-loop gain of the amplifier. [2 pts]
- (f) What is the loop gain of the feedback network? [1 pt]
- (g) What is the closed-loop gain of the amplifier? [1 pt]

TOTAL: 30 points.