




EEE 51: Second Semester 2017 - 2018

Lecture 17

Frequency Response


Gain-Bandwidth Product (GBP)

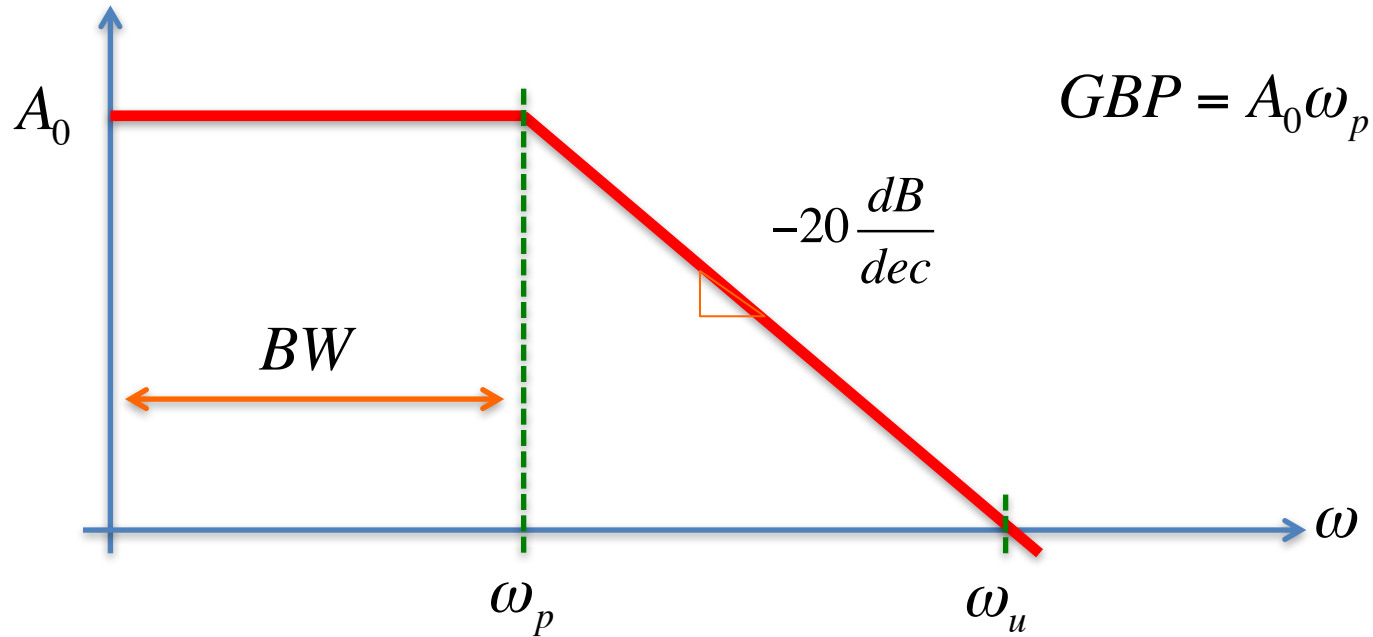

$$|A| = 1 = \frac{A_0}{\sqrt{1 + \left(\frac{\omega_u}{\omega_p}\right)^2}} = \frac{A_0^2}{1 + \left(\frac{\omega_u}{\omega_p}\right)^2} \approx \frac{A_0^2}{\left(\frac{\omega_u}{\omega_p}\right)^2} \Rightarrow \omega_u = A_0 \omega_p = GBP$$




Gain-Bandwidth Product (GBP)

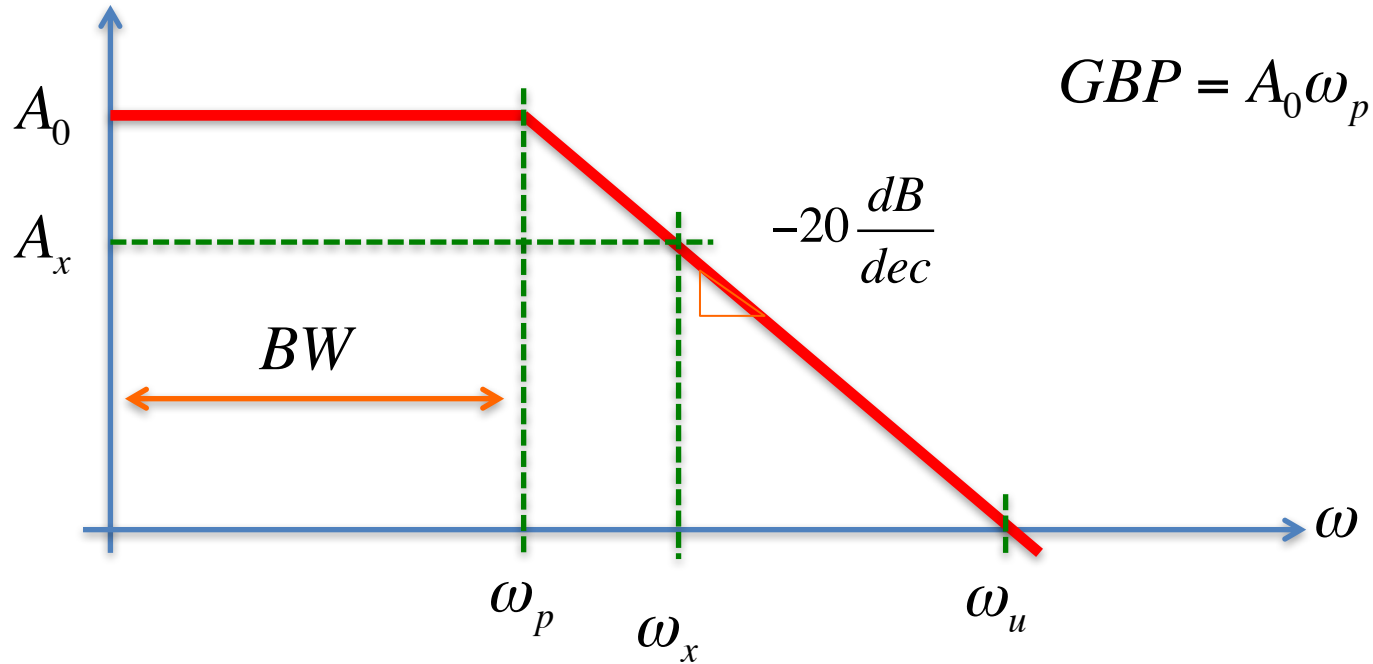


$$|A|^2 = A_x^2 = \frac{A_0^2}{1 + \left(\frac{\omega_x}{\omega_p}\right)^2} \approx \frac{A_0^2}{\left(\frac{\omega_x}{\omega_p}\right)^2} \Rightarrow A_x \omega_x = A_0 \omega_p = GBP$$

Common Source Amplifier

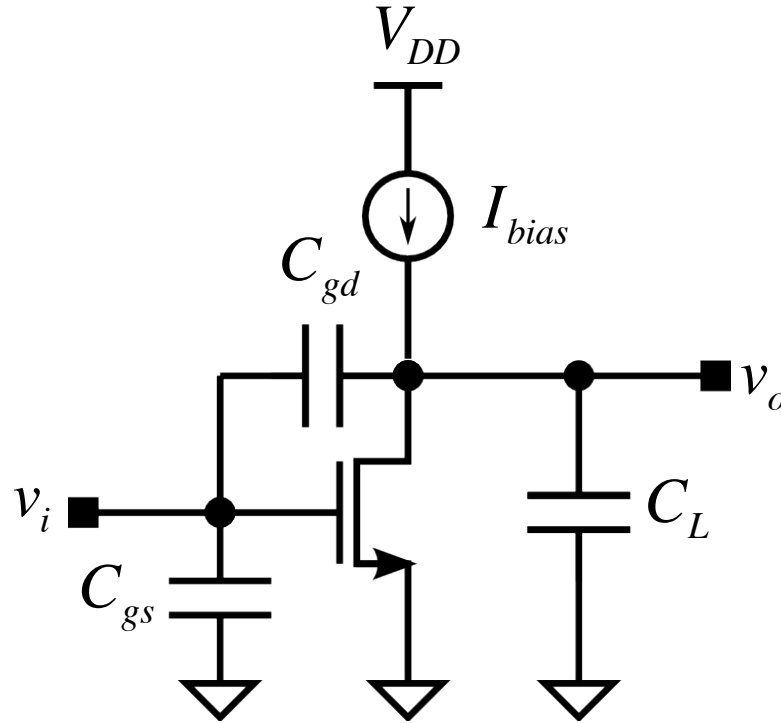

Common Source Amplifier

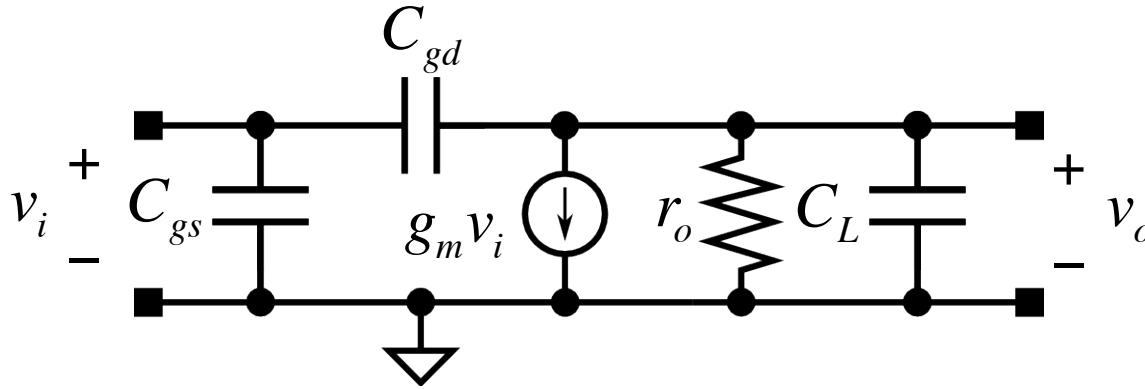


$$v_o \left(\frac{1}{r_o} + sC_L + sC_{gd} \right) - v_i sC_{gd} + g_m v_i = 0$$

$$\frac{v_o}{v_i} = \frac{-g_m + sC_{gd}}{\frac{1}{r_o} + s(C_L + C_{gd})} = \frac{-g_m r_o \left(1 - s \frac{C_{gd}}{g_m} \right)}{1 + s r_o (C_L + C_{gd})} = \frac{-A_0 \left(1 - \frac{s}{z} \right)}{\left(1 + \frac{s}{p} \right)}$$



Common Source Amplifier

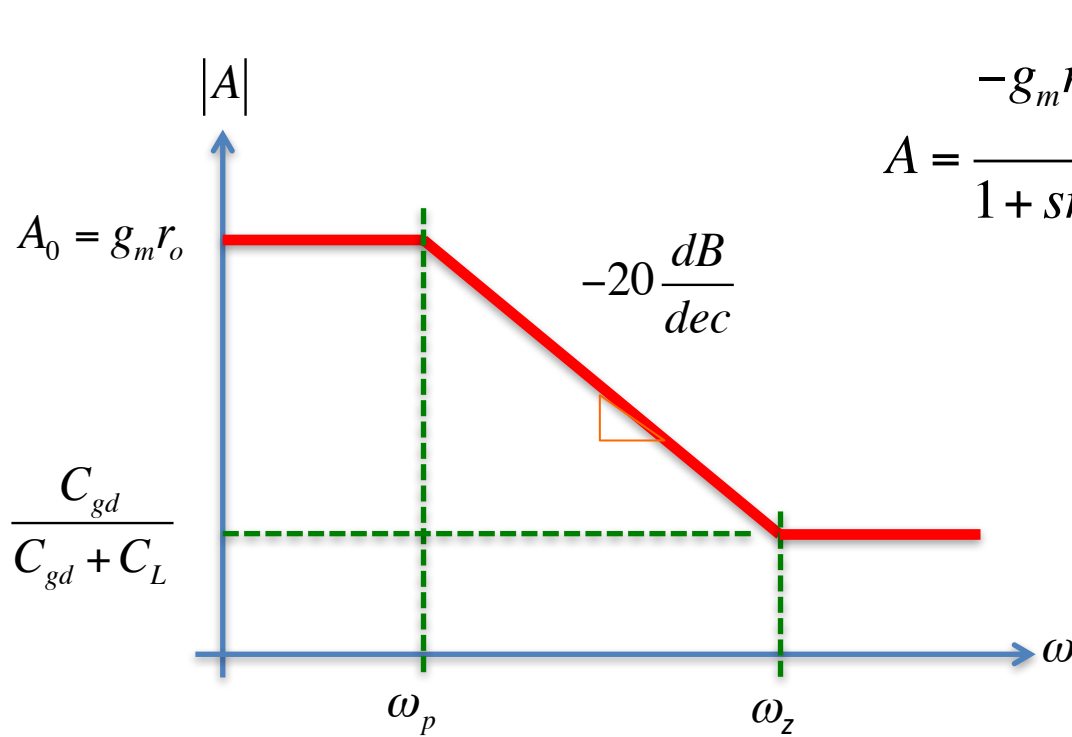

$$A = \frac{-g_m r_o \left(1 - s \frac{C_{gd}}{g_m} \right)}{1 + s r_o (C_L + C_{gd})} = \frac{-A_0 \left(1 - \frac{s}{z} \right)}{\left(1 + \frac{s}{p} \right)}$$


$$A_0 = g_m r_o$$

$$\omega_p = \frac{1}{r_o (C_L + C_{gd})}$$

$$\omega_z = \frac{g_m}{C_{gd}}$$



Common Source Amplifier

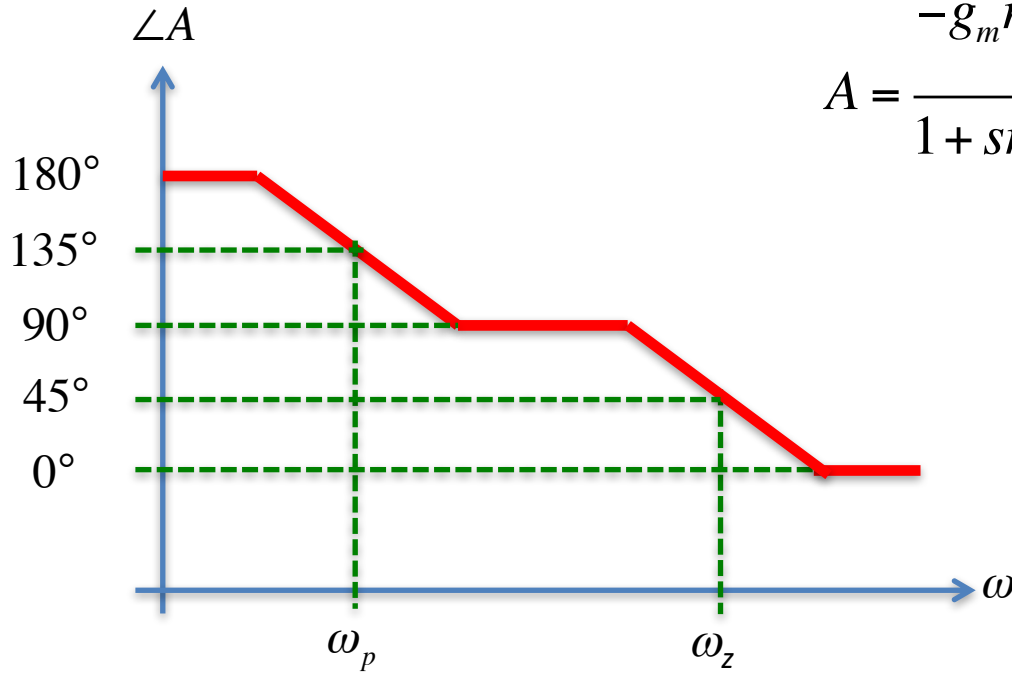

$$A = \frac{-g_m r_o \left(1 - s \frac{C_{gd}}{g_m}\right)}{1 + s r_o (C_L + C_{gd})} = \frac{-A_0 \left(1 - \frac{s}{z}\right)}{\left(1 + \frac{s}{p}\right)}$$


$$A_0 = g_m r_o$$

$$\omega_p = \frac{1}{r_o (C_L + C_{gd})}$$

$$\omega_z = \frac{g_m}{C_{gd}}$$



Common Source Amplifier Input Impedance

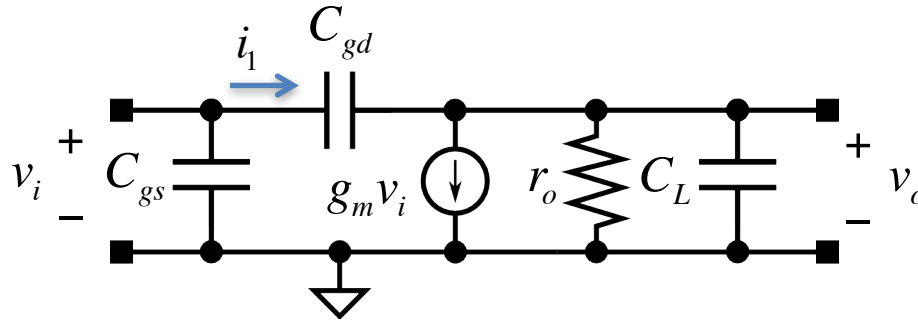


$$A = \frac{-g_m r_o \left(1 - s \frac{C_{gd}}{g_m} \right)}{1 + s r_o (C_L + C_{gd})}$$


$$i_1 = (v_i - v_o) s C_{gd} = v_i \left(1 - \frac{v_o}{v_i} \right) s C_{gd} = v_i (1 - A) s C_{gd}$$

$$\frac{v_i}{i_1} = \frac{1}{s(1 - A)C_{gd}}$$
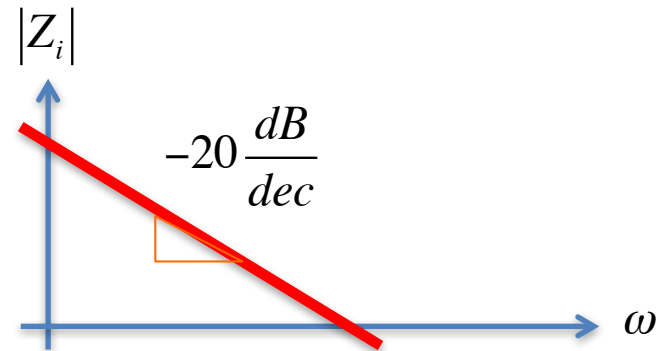
$$Z_i = \frac{1}{s[C_{gs} + (1 - A)C_{gd}]}$$




Common Source Amplifier Output Impedance

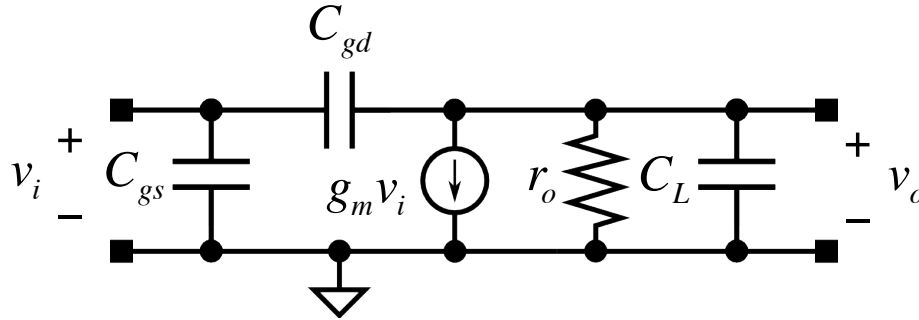


$$A = \frac{-g_m r_o \left(1 - s \frac{C_{gd}}{g_m} \right)}{1 + s r_o (C_L + C_{gd})}$$
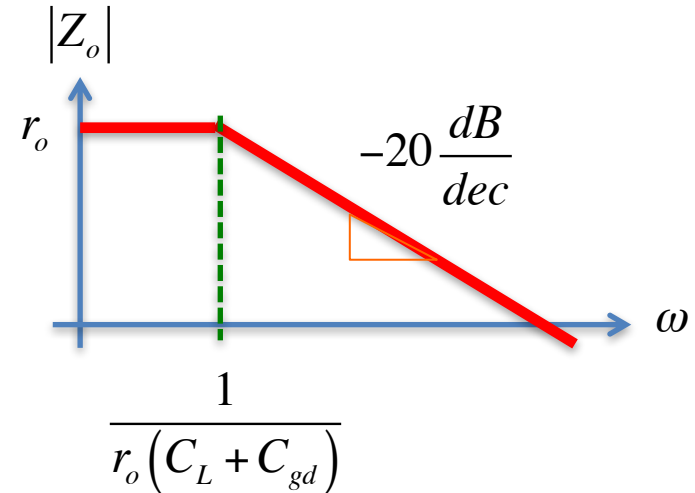
$$Z_o = r_o \parallel \frac{1}{s(C_L + C_{gd})} = \frac{r_o}{1 + s r_o (C_L + C_{gd})}$$




CS Amplifier Effective Transconductance

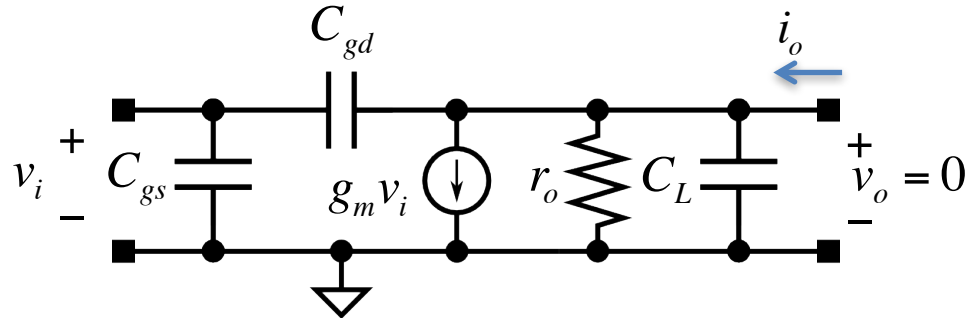


$$i_o = g_m v_i - v_i s C_{gd}$$

$$G_m = \frac{i_o}{v_i} = g_m - s C_{gd} = g_m \left(1 - s \frac{C_{gd}}{g_m} \right)$$

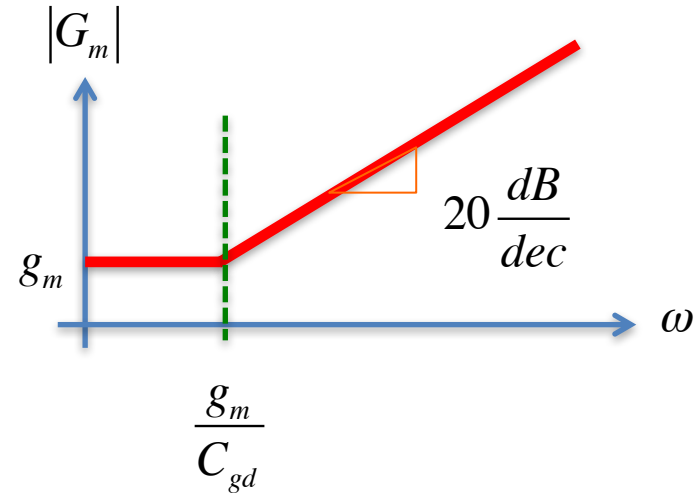
$$A = \frac{-g_m r_o \left(1 - s \frac{C_{gd}}{g_m} \right)}{1 + s r_o (C_L + C_{gd})}$$



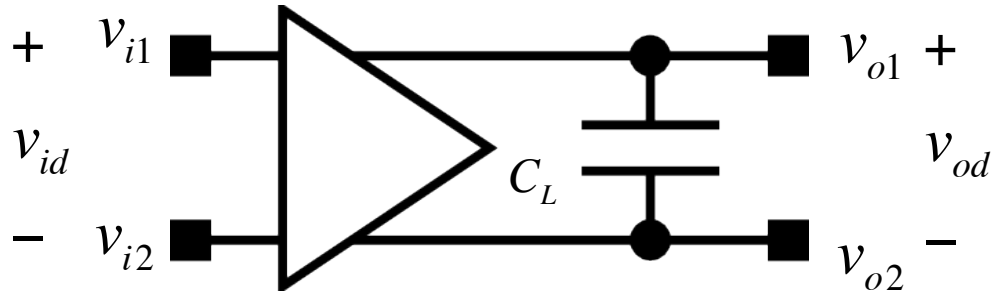
Differential Amplifier Frequency Response



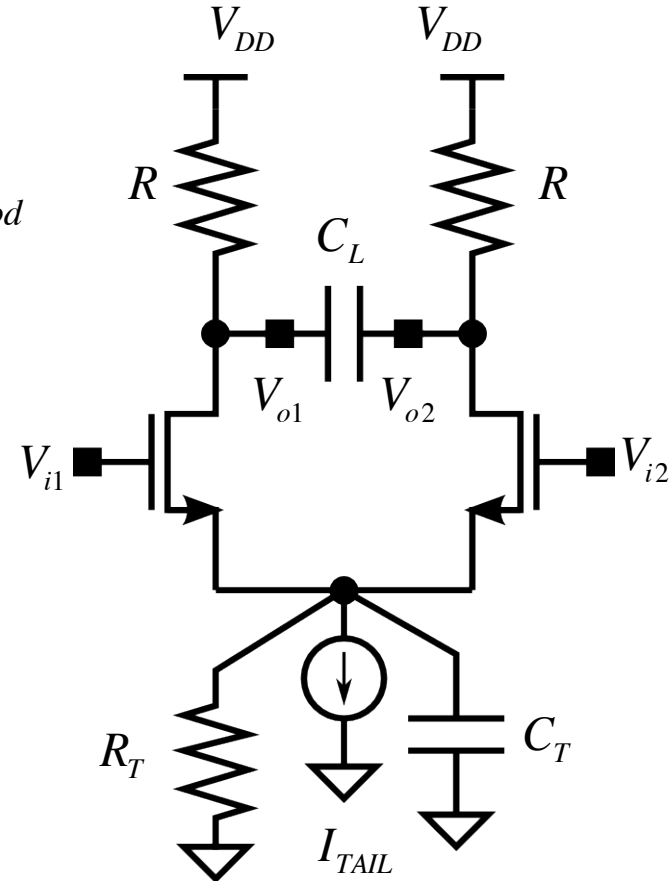Differential-Mode Gain?
Common-Mode Gain?




Differential Mode Half Circuit

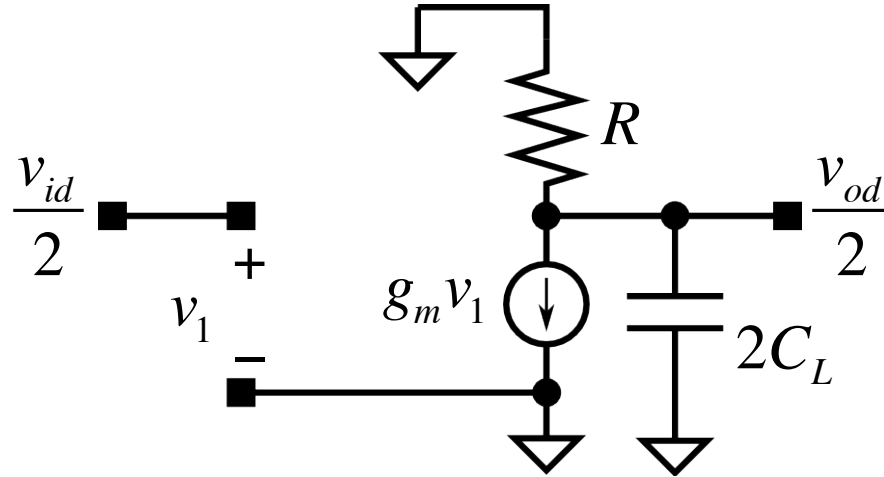

$$A_{dm} = \frac{-g_m R}{1 + s(2RC_L)}$$

Common Mode Half Circuit

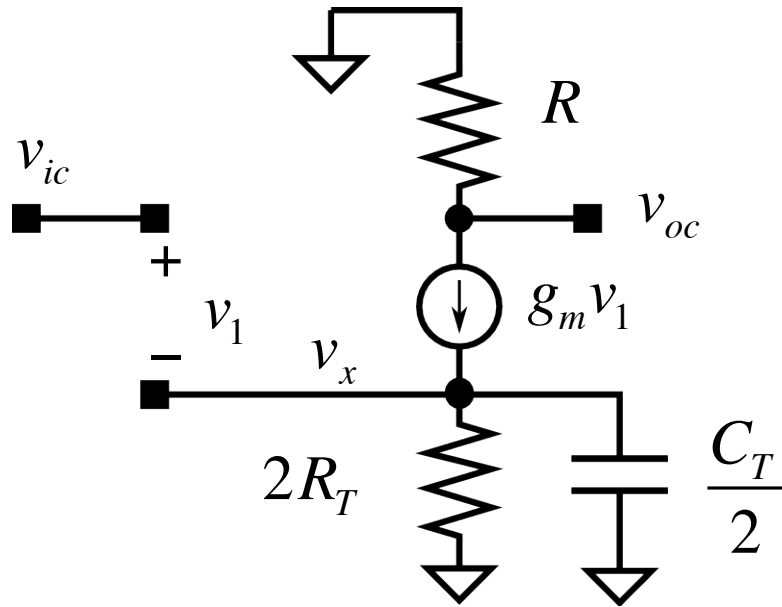


$$v_x \left(\frac{1}{2R_T} + s \frac{C_T}{2} \right) - g_m (v_{ic} - v_x) = 0$$



$$v_o \left(\frac{1}{R} \right) + g_m (v_{ic} - v_x) = 0$$

$$A_{cm} = \frac{-g_m R}{1 + 2g_m R_T} \left(\frac{1 + sR_T C_T}{1 + s \frac{R_T C_T}{1 + 2g_m R_T}} \right)$$

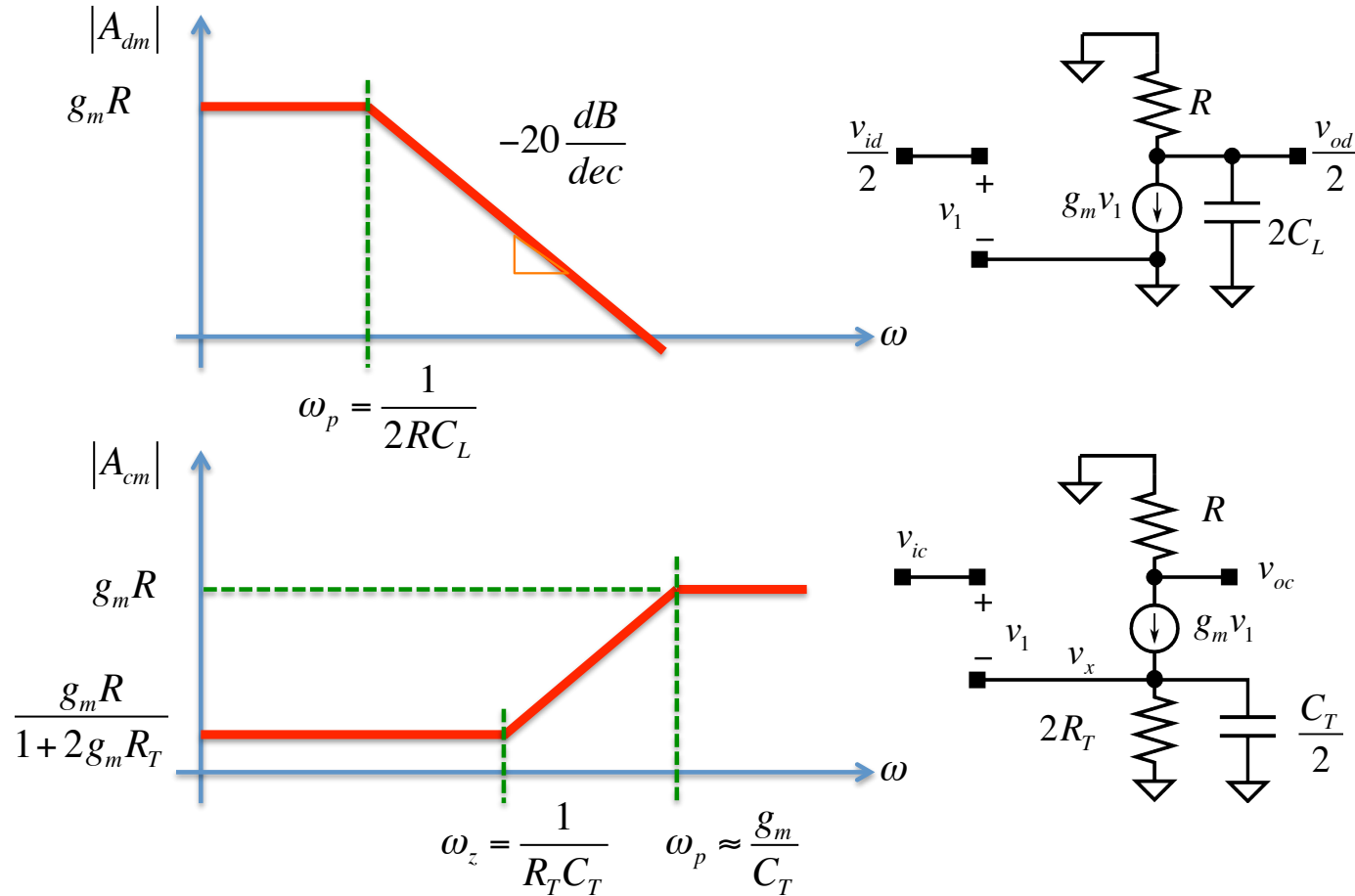Differential Amplifier Frequency Response




Tuned CE Amplifier

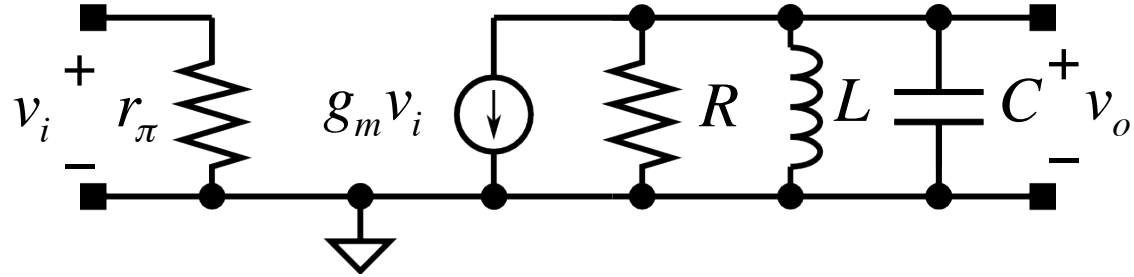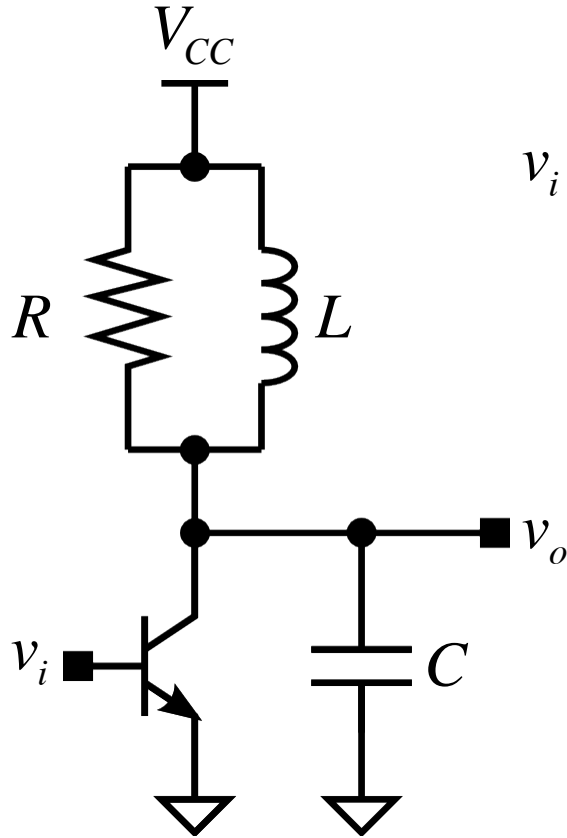

$$A_v = \frac{v_o}{v_i} = -g_m \left(R \parallel sL \parallel \frac{1}{sC} \right)$$

Tuned CE Amplifier

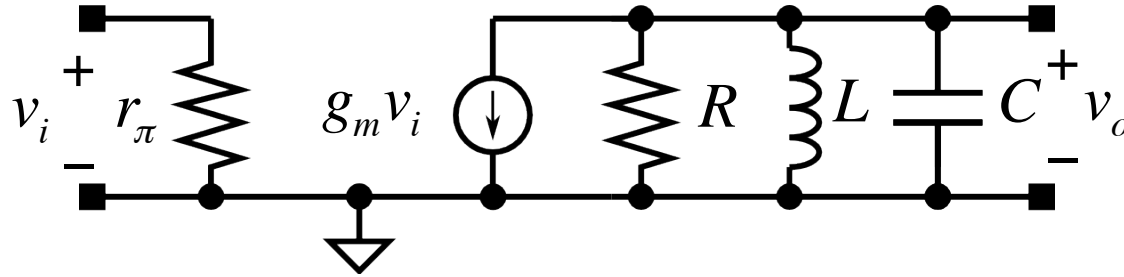

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$a = \frac{1}{2RC}$$


$$A_v = -g_m \left(R \parallel sL \parallel \frac{1}{sC} \right)$$

$$= -g_m R \frac{sL}{s^2 RLC + sL + R} = -g_m R \frac{s \frac{1}{RC}}{s^2 + s \frac{1}{RC} + \frac{1}{LC}}$$

$$= -g_m R \frac{2as}{s^2 + 2as + \omega_0^2}$$



Tuned CE Amplifier

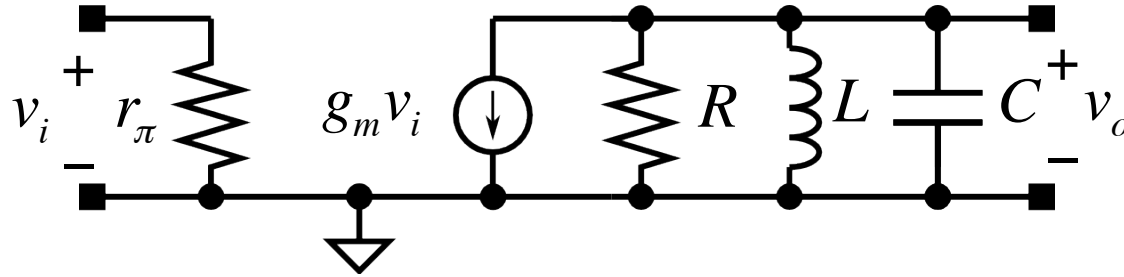

$$\omega_0 = \frac{1}{\sqrt{LC}}$$


$$a = \frac{1}{2RC}$$

$$|A_v| = \left| -g_m R \frac{2as}{s^2 + 2as + \omega_0^2} \right| = g_m R \left| \frac{j2a\omega}{j2a\omega + (\omega_0^2 - \omega^2)} \right|$$

$$= g_m R \frac{2a\omega}{\sqrt{(2a\omega)^2 + (\omega_0^2 - \omega^2)^2}}$$



Tuned CE Amplifier Bandwidth

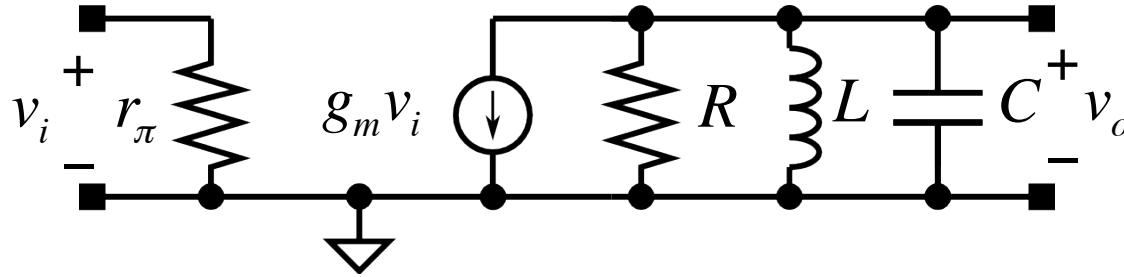

$$\omega_0 = \frac{1}{\sqrt{LC}}$$


$$a = \frac{1}{2RC}$$

$$|A_v| = g_m R \frac{2a\omega}{\sqrt{(2a\omega)^2 + (\omega_0^2 - \omega^2)^2}}$$

$$|A_{v,3dB}| = \frac{g_m R}{\sqrt{2}} \Rightarrow (\omega_0^2 - \omega^2)^2 = (2a\omega)^2$$



Tuned CE Amplifier Bandwidth

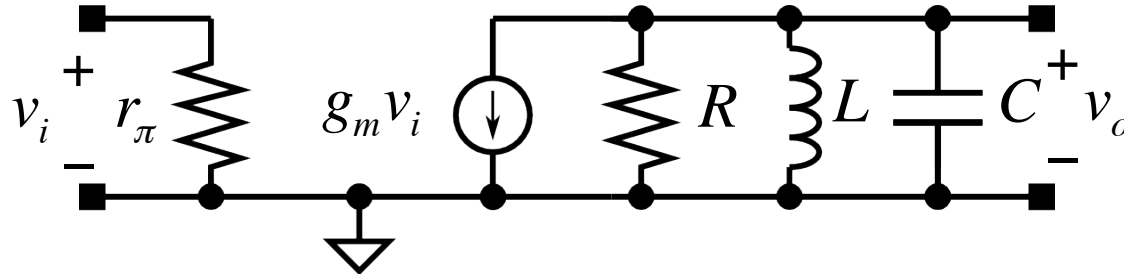


$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$a = \frac{1}{2RC}$$

$$(\omega_0^2 - \omega^2)^2 = (2a\omega)^2$$

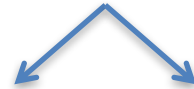
$$\pm(\omega_0^2 - \omega^2) = \pm 2a\omega$$



$$\omega^2 + 2a\omega - \omega_0^2 = 0$$

$$\omega^2 - 2a\omega - \omega_0^2 = 0$$

Tuned CE Amplifier Bandwidth

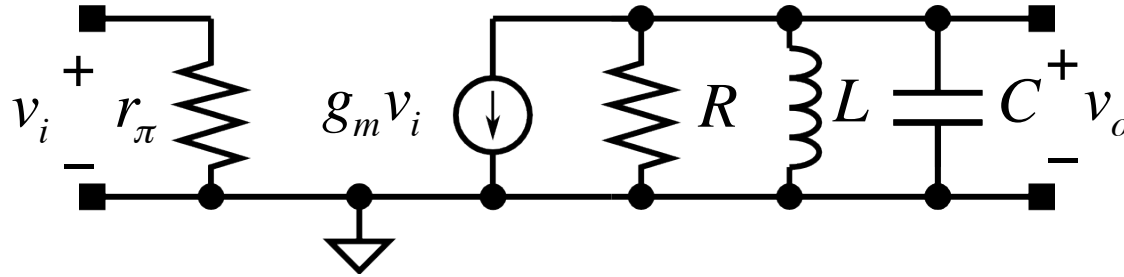

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$a = \frac{1}{2RC}$$

$$\omega^2 + 2a\omega - \omega_0^2 = 0$$

$$\omega^2 - 2a\omega - \omega_0^2 = 0$$

$$\omega = \frac{-2a \pm \sqrt{(2a)^2 + 4\omega_0^2}}{2}$$


$$= \begin{cases} -a + \sqrt{a^2 + \omega_0^2} \\ -a - \sqrt{a^2 + \omega_0^2} \end{cases}$$

$$\omega = \frac{2a \pm \sqrt{(2a)^2 + 4\omega_0^2}}{2}$$

$$= \begin{cases} a + \sqrt{a^2 + \omega_0^2} \\ a - \sqrt{a^2 + \omega_0^2} \end{cases}$$



Tuned CE Amplifier Bandwidth

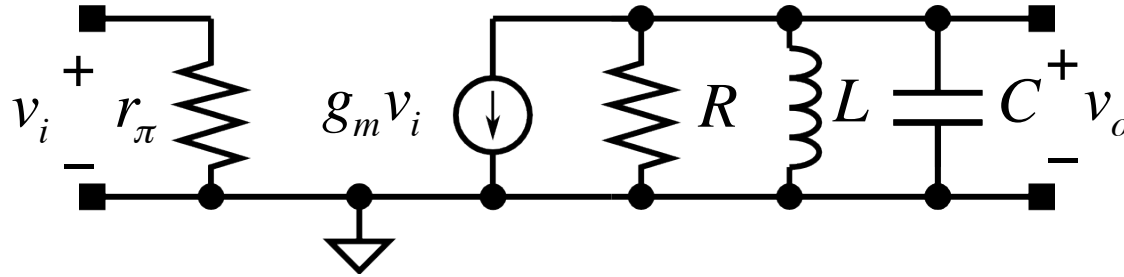

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$a = \frac{1}{2RC}$$

$$\omega_1 = -a + \sqrt{a^2 + \omega_0^2}$$

$$\omega_2 = a + \sqrt{a^2 + \omega_0^2}$$



$$BW = \omega_2 - \omega_1 = 2a$$

$$\begin{aligned} \omega_1 \omega_2 &= \left(-a + \sqrt{a^2 + \omega_0^2} \right) \left(a + \sqrt{a^2 + \omega_0^2} \right) \\ &= -a^2 + a\sqrt{a^2 + \omega_0^2} - a\sqrt{a^2 + \omega_0^2} + a^2 + \omega_0^2 \\ &= \omega_0^2 \end{aligned}$$

$$\omega_0 = \sqrt{\omega_2 \omega_1}$$



Magnitude Response

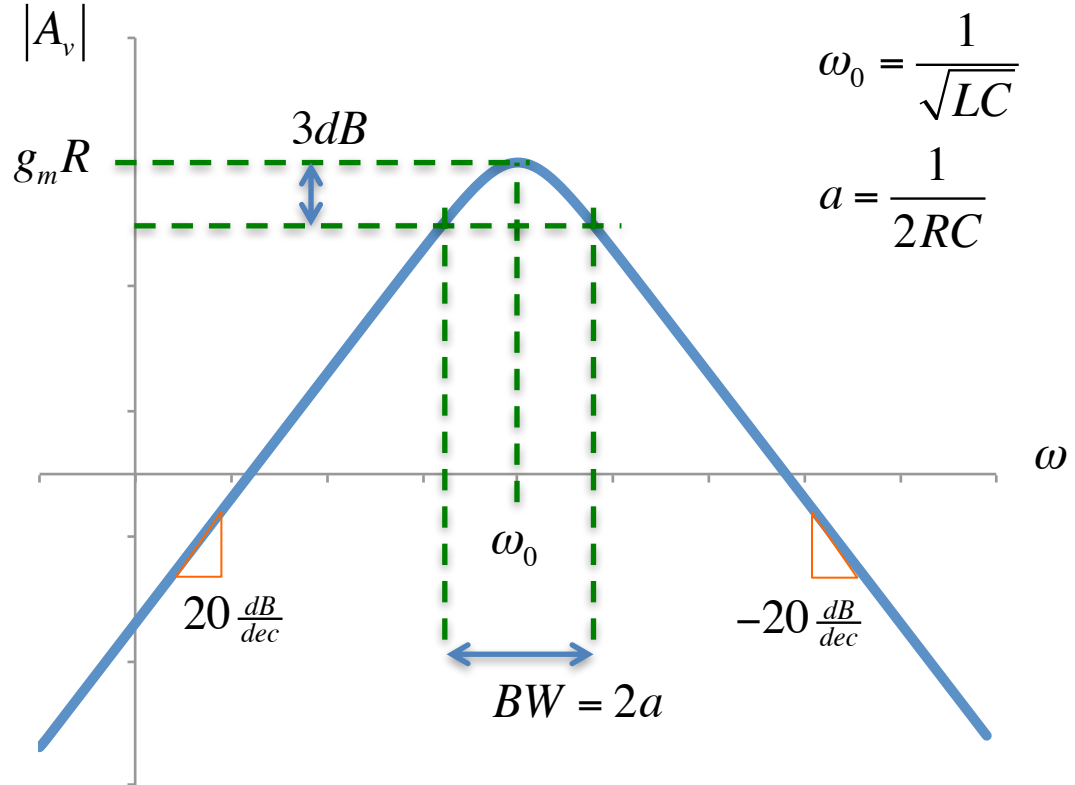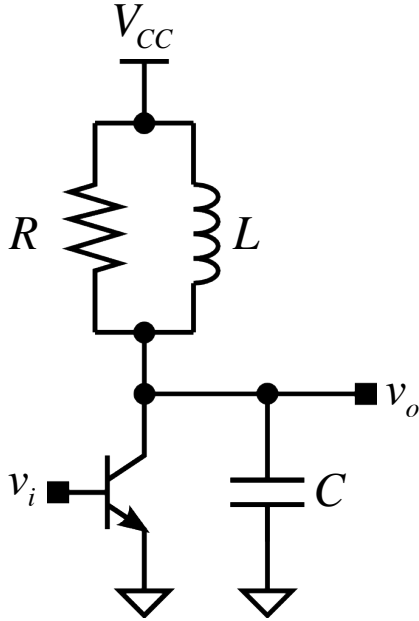

Next Meeting

- Feedback Amplifiers

