

EEE 51 Assignment 4

2nd Semester SY 2017-2018

Due: 5pm Tuesday, Feb. 27, 2018 (Rm. 220)

Instructions: Write legibly. Show all solutions and state all assumptions. Write your full name, student number, and section at the upper-right corner of each page. Start each problem on a new sheet of paper. Box or encircle your final answer.

Answer sheets should be color coded according to your lecture section. The color scheme is as follows:

THQ	–	yellow
THR	–	blue
THU	–	white
THX	–	green
WFX	–	pink

1. **MOSFET-BJT Amplifier Design.** Figure 1 shows an amplifier configuration that uses current mirrors to generate the DC voltages needed by M_1 and Q_2 with only one DC voltage supply. The output DC voltage requirement is 2.5 V at room temperature, while using a single 5 V supply voltage and M_1 having a quiescent DC drain current of 1 mA. Assume that the given capacitor and inductor elements are ideal and have infinitely large values.

Given $\beta = 300$, $|I_S| = 1 \text{ fA}$, and $|V_A| = 100 \text{ V}$ for the PNP transistors and $k = 2 \frac{\text{mA}}{\text{V}^2}$, $\lambda = 0.1 \text{ V}^{-1}$, and $V_{TH} = 1 \text{ V}$ for the NMOS transistors:

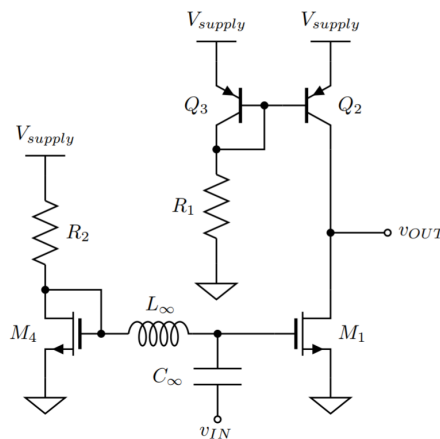


Figure 1: MOSFET-BJT Amplifier

- (a) Determine the required R_1 and R_2 . [4 pts]
- (b) Determine the small signal gain, $A_V = \frac{v_{out}}{v_{in}}$, of the amplifier. [3 pts]
2. **BJT Current Mirror with Emitter Resistors.** A current mirror was constructed as shown in Figure 2 with a resistor R_A used to generate a bias current. Q_1 and Q_2 are used to mirror that current and generate I_{OUT} . The current mirror has already been biased such that both transistors are in forward active over some range of output voltage, and so $r_{\pi 1}$, $r_{\pi 2}$, r_{o1} , r_{o2} , g_{m1} , g_{m2} are known to be some set of values, as well as R_A , R_B and R_C .

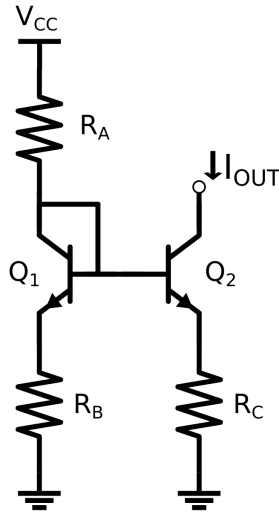


Figure 2: BJT Current Mirror

- Draw the small-signal equivalent circuit. Label all parameters, voltages, currents necessary. Label terminal names, and if possible, label the nodes mapping to the pins of the transistors. [3 pts]
- Determine the output resistance R_o in terms of the small-signal parameters and resistor values. Do not omit terms based on common assumptions. If possible, show a detailed step by step solution and simplify or expand terms for clarity. [4 pts]

3. **MOSFET Cascode Current Mirror.** Given the cascode current mirror below, determine the following:

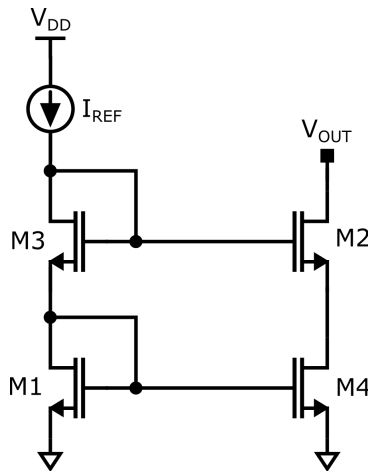


Figure 3: MOSFET Cascode Current Mirror

- Draw the *simplified* small-signal equivalent circuit. State all assumptions and properly label all parameters, voltages, and terminal names. [3 pts]
- Determine the circuit's output resistance R_o in terms of the transistor g_m and r_o . [3 pts]

TOTAL: 20 points.