



# **EEE 51: Second Semester 2017 - 2018**

## **Lecture 15**


# Frequency Response

# Frequency Characteristics of Transistor Circuits

- Due to frequency-dependent impedances
  - Capacitors, inductors
- BJT Parasitic Capacitances
  - Junction capacitances
  - Nonlinear (voltage dependent)
  - Base-Charging capacitance ( $C_b$ )
  - Base-Emitter junction capacitance ( $C_{je}$ )
  - Base-Collector junction capacitance ( $C_{\mu}$ )



# BJT Capacitances

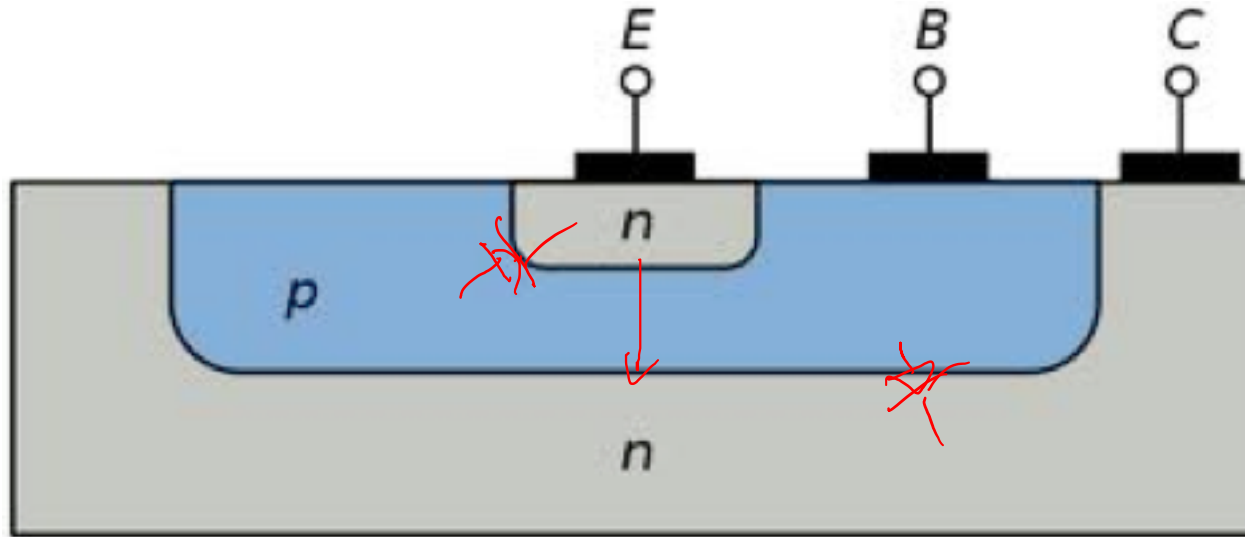

[[http://commons.wikimedia.org/wiki/File:Npn\\_bjt\\_cross\\_section.svg](http://commons.wikimedia.org/wiki/File:Npn_bjt_cross_section.svg)]




# BJT Base-Charging Capacitance

- Capacitance due to the change in majority carrier charge inside the base of the BJT
  - Cancels out the change in minority carriers in the base due to  $v_{BE}$
  - $\sim 100$ 's of fF

$\uparrow$   
 $10^{-15}$
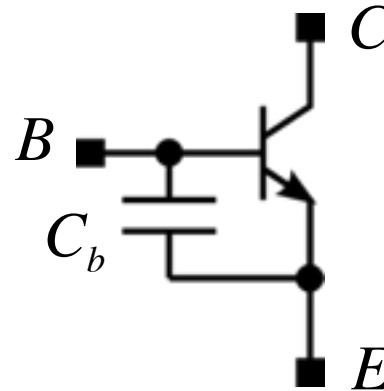
$$C_b = \tau_F g_m = \tau_F \frac{I_{C,Q}}{V_T}$$



- $\tau_F$  – forward base transit time
  - Represents the average time (per carrier) spent crossing the base




# BJT Base-Emitter Junction Capacitance

- PN junction capacitance  $\sim 10$ 's of fF
- In a BJT in the forward active region, BE junction is forward-biased

$$C_{je} = \frac{C_{je0}}{\sqrt{1 - \frac{V_{BE}}{V_{j,BE}}}}$$


$$C_{je} \approx 2C_{je0}$$

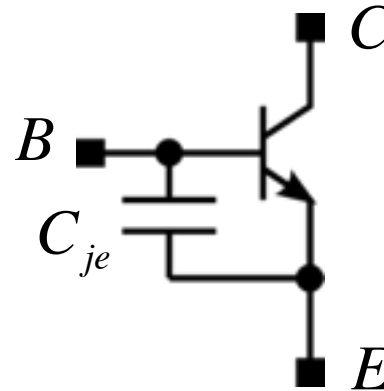
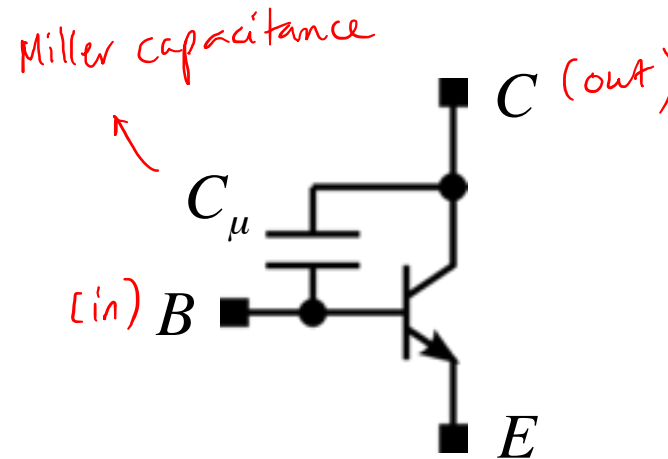
# BJT Base-Collector Junction Capacitance

- PN junction capacitance 5 to 10 fF
- Reversed-biased in forward active BJTs


$$C_{\mu} = \frac{C_{\mu 0}}{\sqrt{1 + \frac{V_{CB}}{V_{j,CB}}}}$$



Can be amplified by the Miller effect


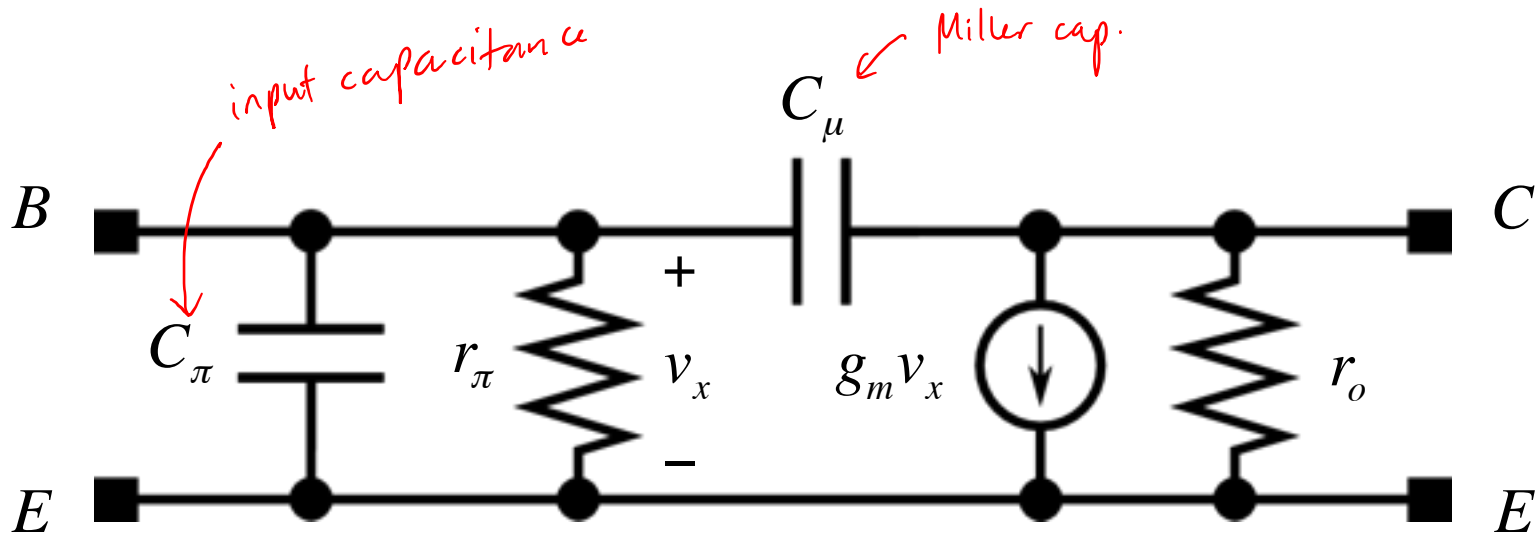
# BJT Small Signal Model (with Capacitances)



$$C_\pi = C_b + C_{je}$$

$$C_b = \tau_F g_m$$


$$C_{je} = \frac{C_{je0}}{\sqrt{1 - \frac{V_{BE}}{V_{j,BE}}}}$$

$$C_\mu = \frac{C_{\mu0}}{\sqrt{1 + \frac{V_{CB}}{V_{j,CB}}}}$$




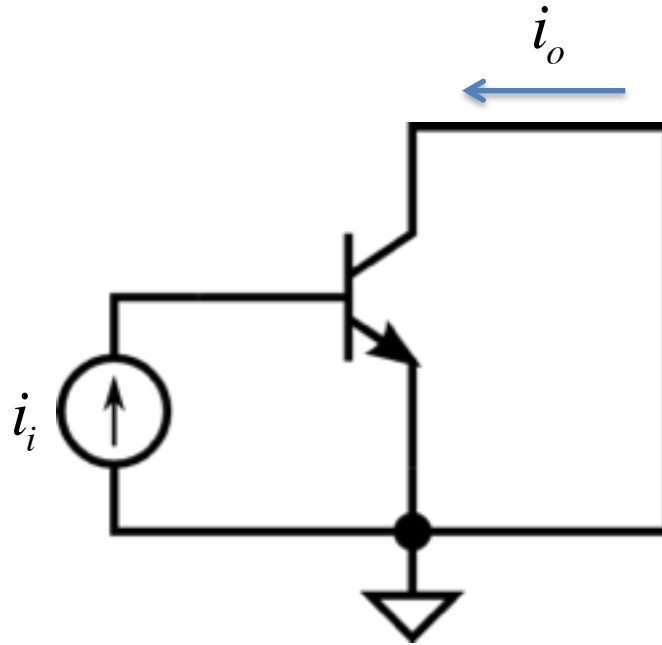
# BJT Transition Frequency ( $f_T$ )

- Frequency at which the short-circuit common emitter current gain falls to unity





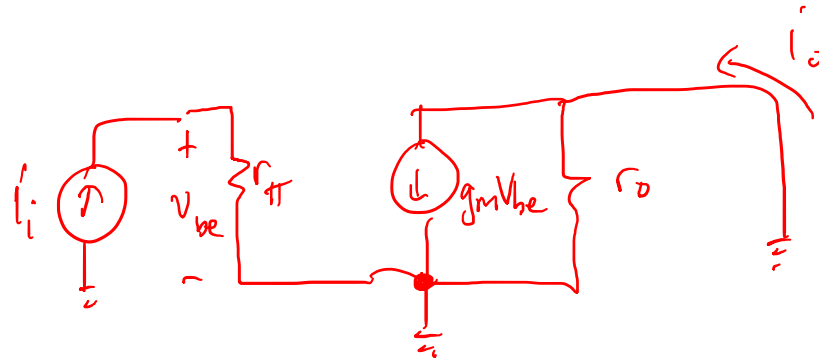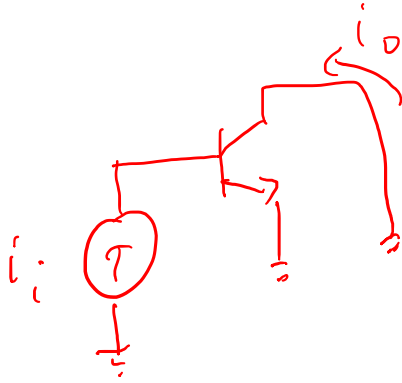

$$i_o = g_m V_{be} \approx g_m (i_i \cdot r_{\pi})$$

$$\frac{i_o}{i_i} = g_m r_{\pi} = g_m \cdot \frac{\beta}{g_m} = \underline{\underline{\beta}} > 1$$




# BJT $f_T$

- Small signal model

$$\textcircled{1}: i_o = g_m v_x + (-v_x \cdot j\omega C_\mu)$$
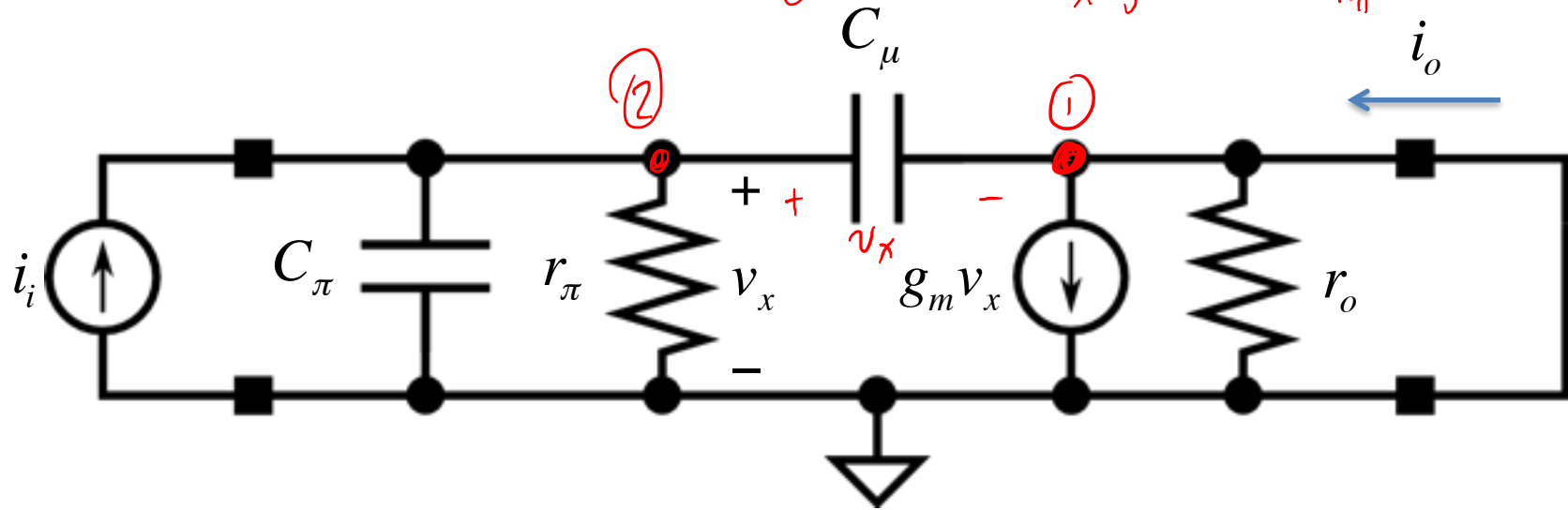
$$\textcircled{2}: i_i = v_x \cdot j\omega C_\pi + \frac{v_x}{r_\pi} + v_x \cdot j\omega C_\mu$$



$$\frac{i_o}{i_i} = 1 \Rightarrow \omega_T \approx \frac{g_m}{C_\mu + C_\pi} = 2\pi f_T$$



$$\frac{I_o}{I_i} = \frac{g_m - j\omega C_m}{\frac{1}{r_\pi} + j\omega(C_m + C_\pi)} \cdot \frac{r_\pi}{r_\pi} = \frac{g_m r_\pi - j\omega C_m r_\pi}{1 + j\omega(C_m + C_\pi)r_\pi}$$

at what  $\omega = \omega_T$  does  $\left| \frac{I_o}{I_i} \right| = 1$

$$\frac{\sqrt{(g_m r_\pi)^2 + (\omega_T C_m r_\pi)^2}}{\sqrt{1 + \omega_T^2 (C_m + C_\pi)^2 r_\pi^2}} = 1$$

$$(g_m r_\pi)^2 - 1 = \omega_T^2 r_\pi^2 [(C_m + C_\pi)^2 - (C_m)^2]$$

approx:  $(g_m r_\pi)^2 = \omega_T^2 r_\pi^2 (C_m + C_\pi)^2$

$$\omega_T^2 \approx \frac{g_m^2}{(C_m + C_\pi)^2}$$

$$\omega_T \approx \frac{g_m}{C_m + C_\pi}$$




# MOS Capacitances

- MOS parasitic capacitances
  - Nonlinear
- Gate oxide capacitance (“parallel plate”)
- Gate overlap capacitance (fringe)
- Drain/Source-Bulk junction capacitance (PN junction)



# MOS Capacitances

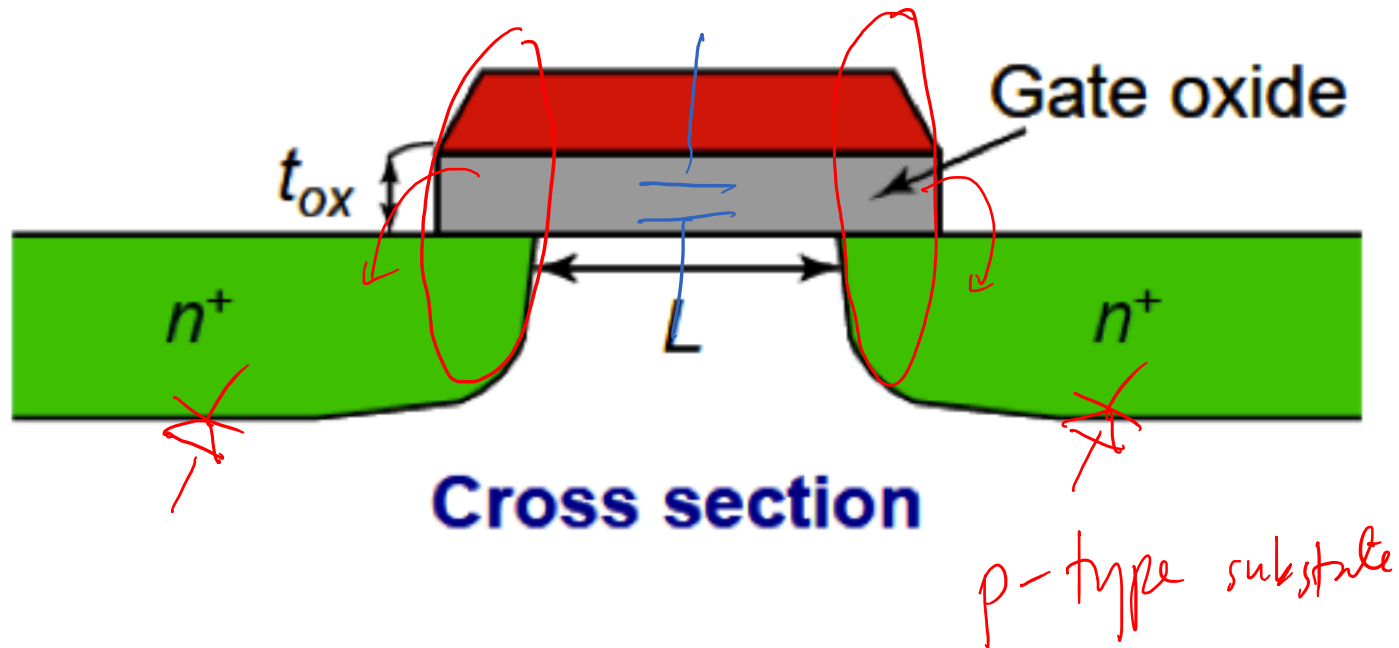

# MOS Capacitances


- Gate Capacitance
  - Dependent on the thickness of the gate oxide and area of the gate
  - Nonlinear
    - Dependent on the gate and source/drain voltages
- Gate Overlap Capacitance
  - “parallel-plate” and fringing fields



# MOS Gate-Source Capacitance


- Components:
  - gate “parallel plate” capacitance
  - Gate-source overlap capacitance

*→ dominant value*

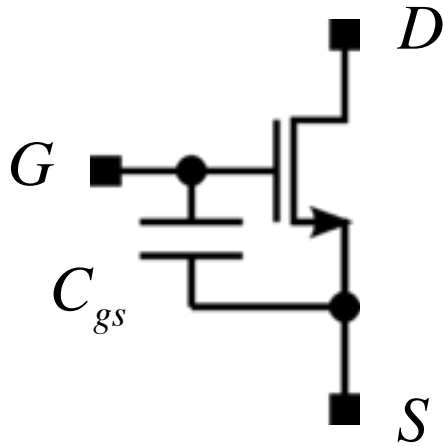
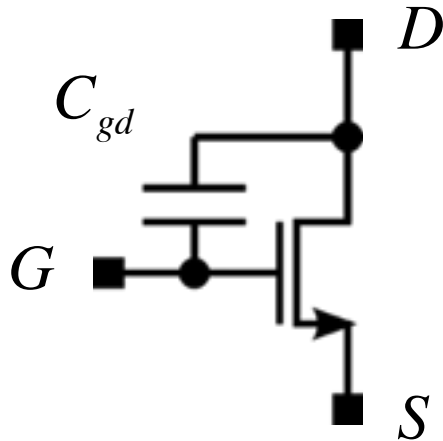
# MOS Gate-Drain Capacitance


- Composed of the overlap capacitance between the gate and drain





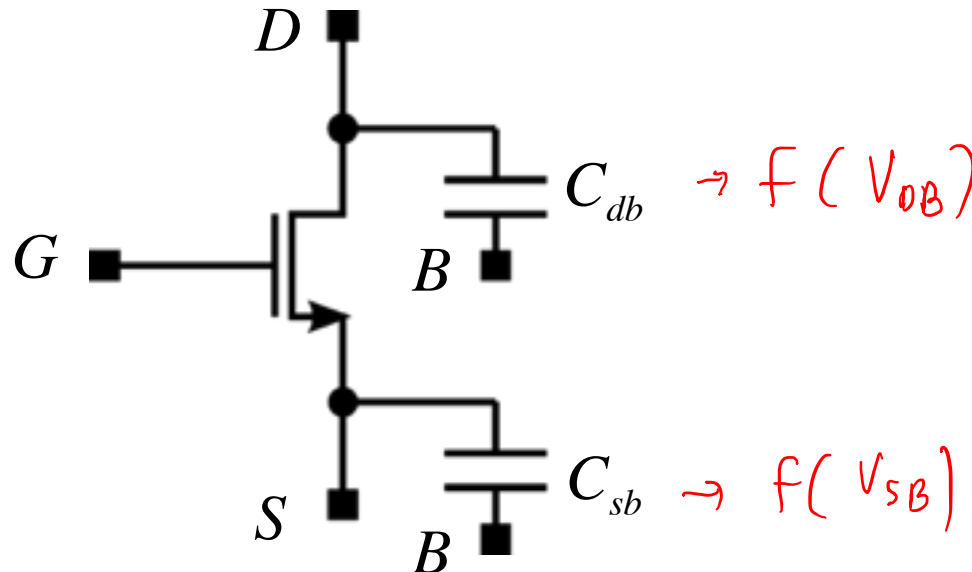
# MOS Source/Drain Junction Capacitance

- Formed by the drain/source PN junction (to the substrate)
- Normally reversed biased



MOSFET small signal (w/ caps)

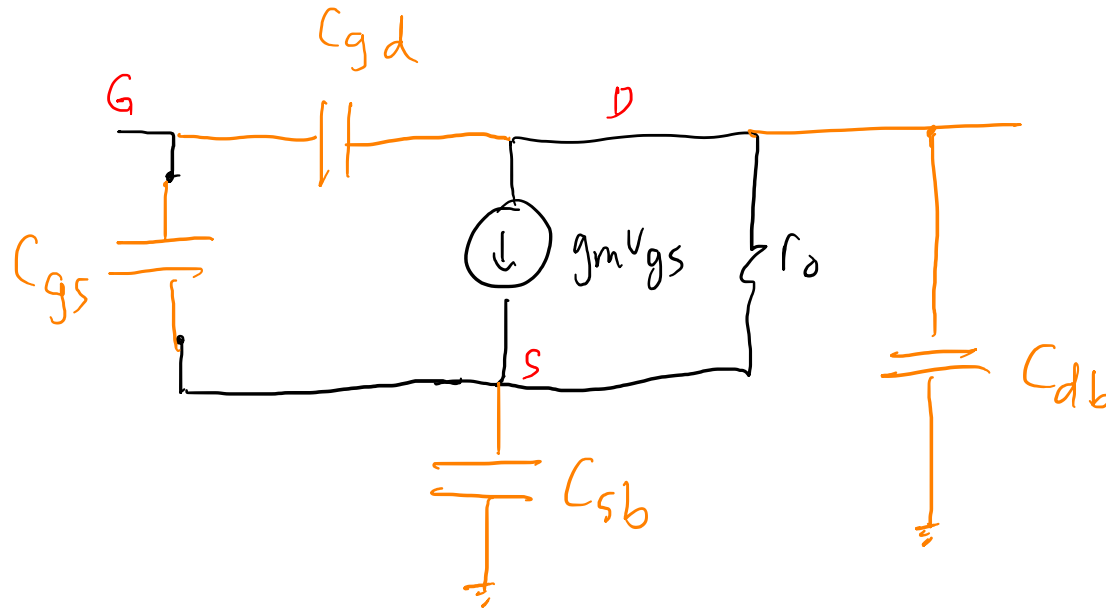


in saturation:  $C_{gs} > C_{gd} > C_{sb}/C_{db}$



# Capacitance Effects

- A Simple RC Circuit

$$s = \sigma + j\omega$$

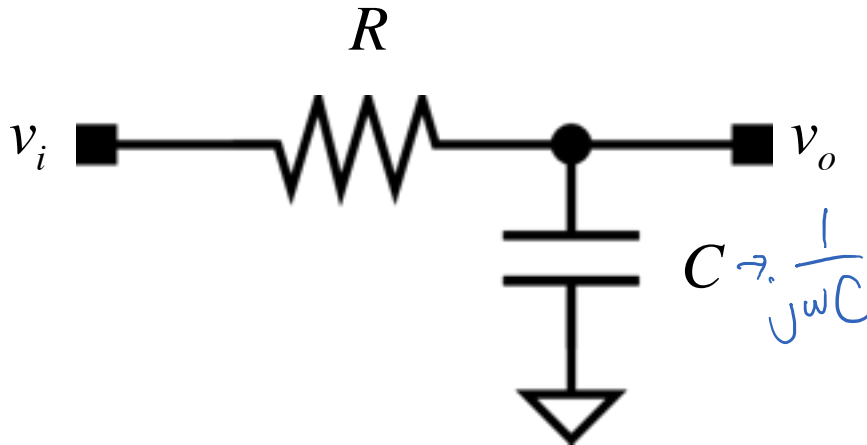


applying voltage division:

$$v_o = \frac{\frac{1}{sC}}{\frac{1}{sC} + R} v_i = \frac{1}{1 + sRC} v_i$$

$$A_v(\omega) = \frac{v_o}{v_i} = \frac{1}{1 + sRC} \Big|_{s=j\omega}$$



# Frequency Response

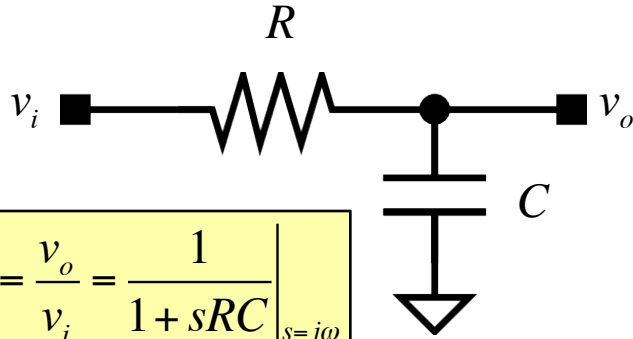

$$A_v(\omega) = \frac{v_o}{v_i} = \frac{1}{1 + sRC} \Big|_{s=j\omega}$$


$$= \frac{1}{1 + j\omega RC}$$

$$|A_v(\omega)| = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$$

$$= \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_0}\right)^2}}$$

where  $\omega_0 = \frac{1}{RC}$


Linear Plot

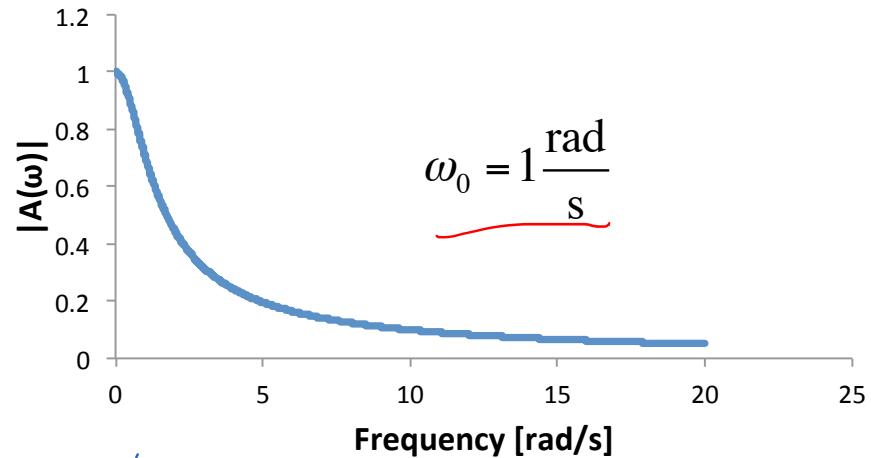

- ①:  $\omega < \omega_0$  ,  $|A_v(\omega)| \rightarrow 1$
- ②:  $\omega = \omega_0$  ,  $|A_v(\omega)| = \frac{1}{\sqrt{2}}$
- ③:  $\omega > \omega_0$  ,  $|A_v(\omega)| \rightarrow \frac{\omega_0}{\omega} \rightarrow 0$




# Frequency Response

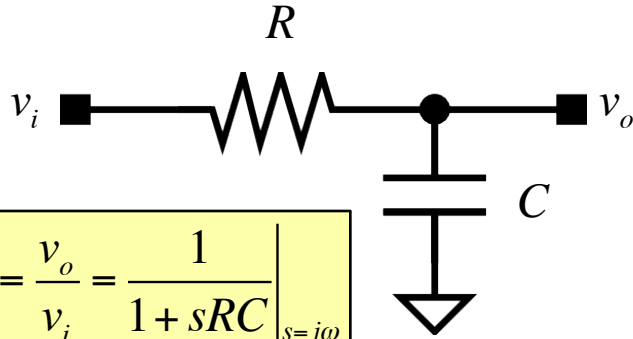

$$A_v(\omega) = \frac{v_o}{v_i} = \frac{1}{1 + sRC} \Big|_{s=j\omega}$$


$$\begin{aligned} |A_v(\omega)| &= \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}} \\ &= \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_0}\right)^2}} \end{aligned}$$

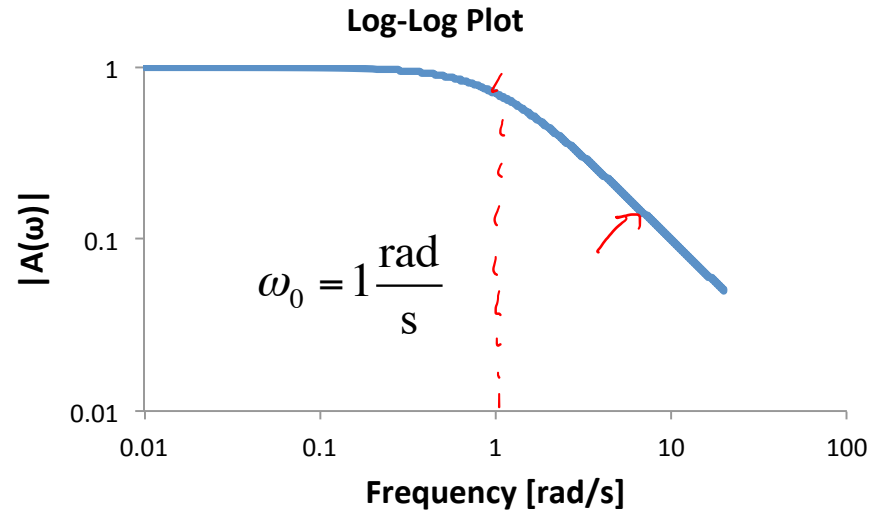


# Decibels (dB)

- Voltage gain:


$$\begin{aligned} |A_{v,dB}(\omega)| &= 20 \log \left( \left| \frac{v_o}{v_i} \right| \right) \\ &= 20 \log \left( \frac{1}{\sqrt{1 + \left( \frac{\omega}{\omega_0} \right)^2}} \right) \end{aligned}$$

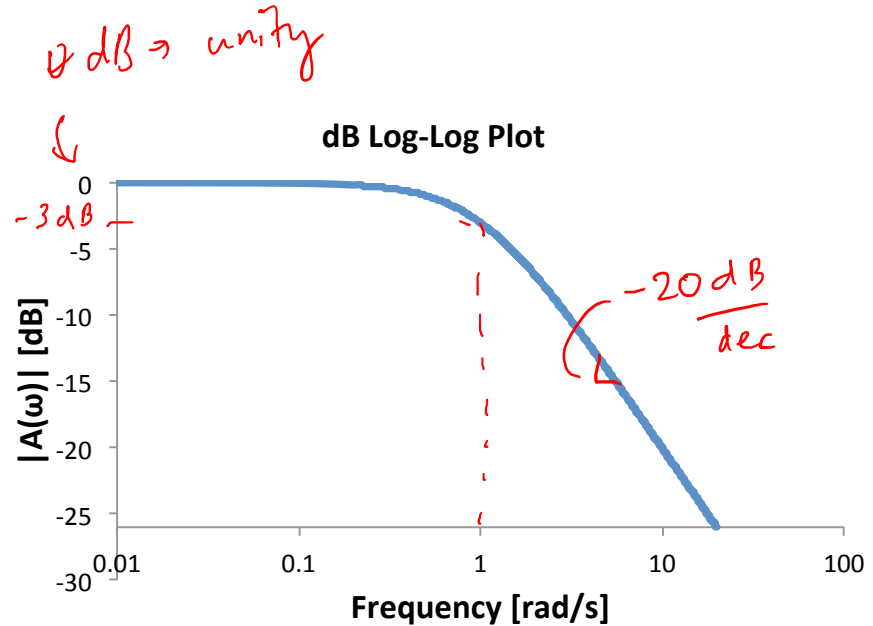

# Frequency Response: Magnitude

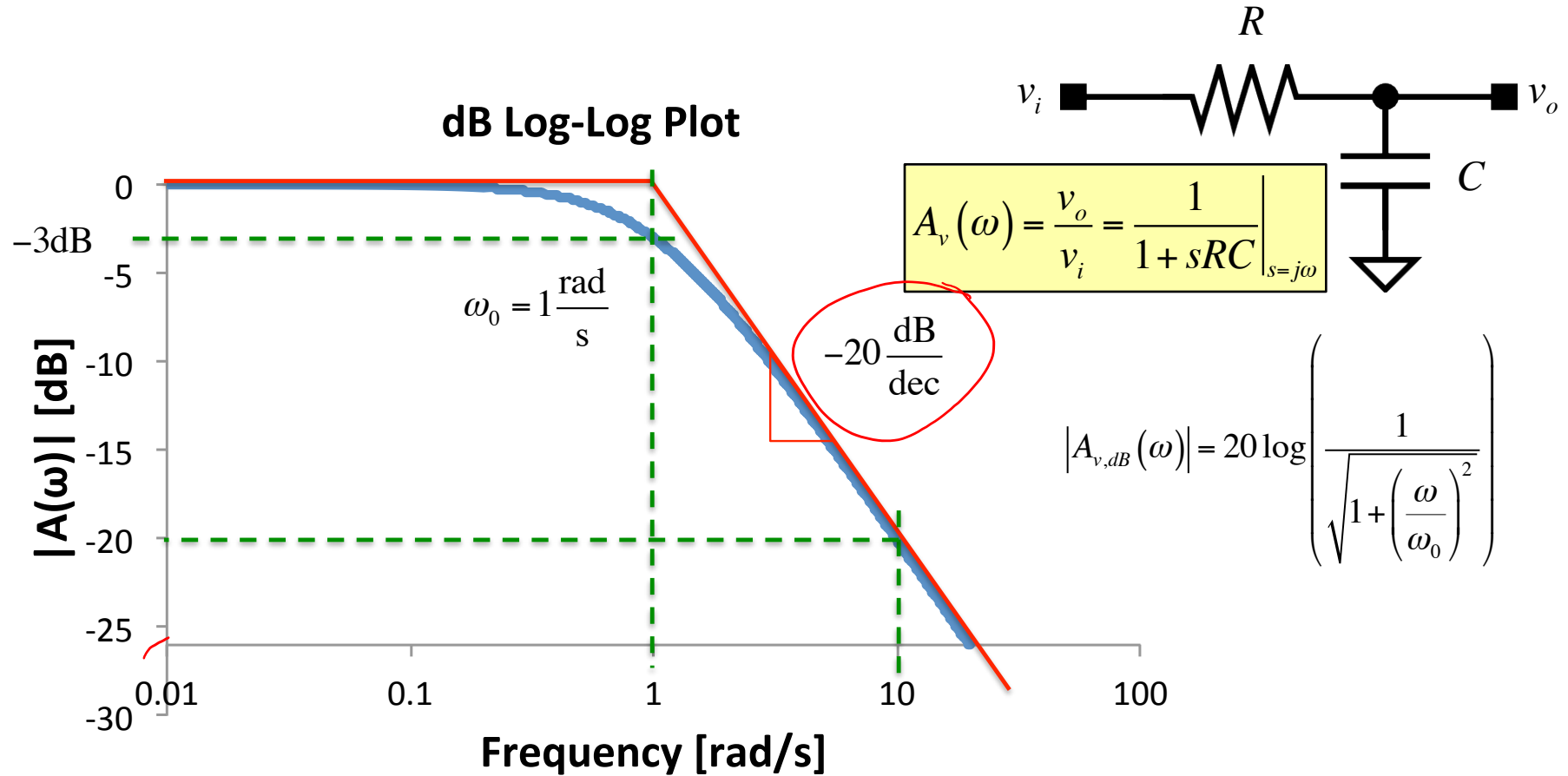

# Phase Response

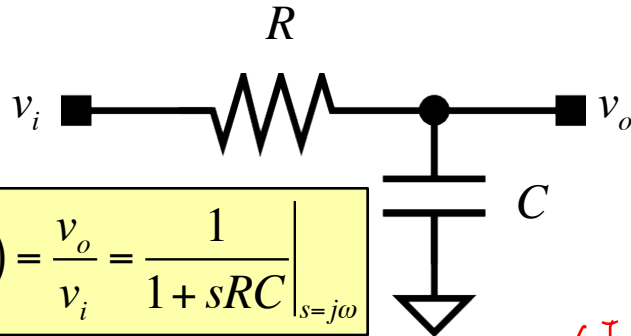

$$A_v(\omega) = \frac{v_o}{v_i} = \frac{1}{1 + sRC} \Big|_{s=j\omega}$$

$$A_v(\omega) = \frac{N(\omega)}{D(\omega)}$$


$$\angle A_v(\omega) = \tan^{-1} \left( \frac{\text{Im}(N(\omega))}{\text{Re}(N(\omega))} \right) - \tan^{-1} \left( \frac{\text{Im}(D(\omega))}{\text{Re}(D(\omega))} \right)$$

$$\angle A_v(\omega) = \tan^{-1} \left( \frac{\text{Im}[A(\omega)]}{\text{Re}[A(\omega)]} \right)$$

$$= \tan^{-1} \left( \frac{0}{1} \right) - \tan^{-1} \left( \frac{\omega RC}{1} \right)$$


$$= -\tan^{-1}(\omega RC) = -\tan^{-1} \left( \frac{\omega}{\omega_0} \right)$$

Phase Log-Log Plot

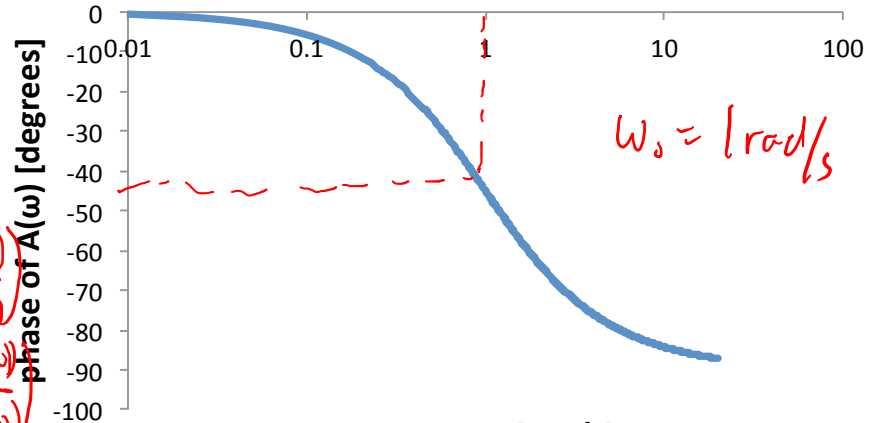

$$\omega_0 = 1 \text{ rad/s}$$

Frequency [rad/s]

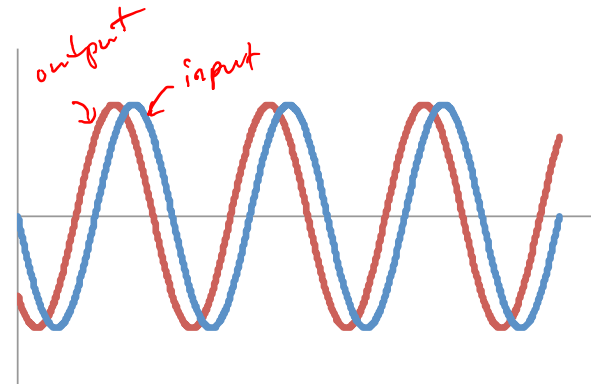


- $\omega < \omega_0$  :  $\angle A_v(\omega) \rightarrow 0^\circ$
- $\omega = \omega_0$  :  $\angle A_v(\omega) = -45^\circ$
- $\omega > \omega_0$  :  $\angle A_v(\omega) \rightarrow -90^\circ$






# Phase Response

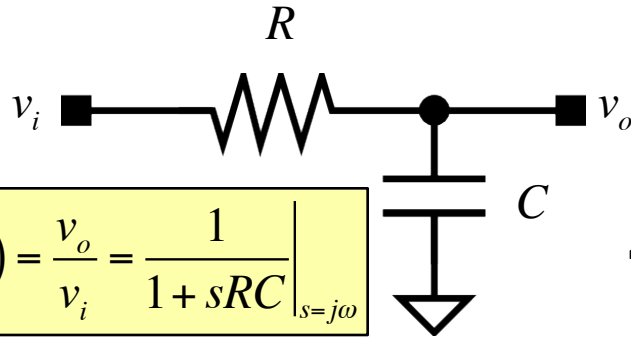


$$A_v(\omega) = \frac{v_o}{v_i} = \frac{1}{1 + sRC} \Big|_{s=j\omega}$$

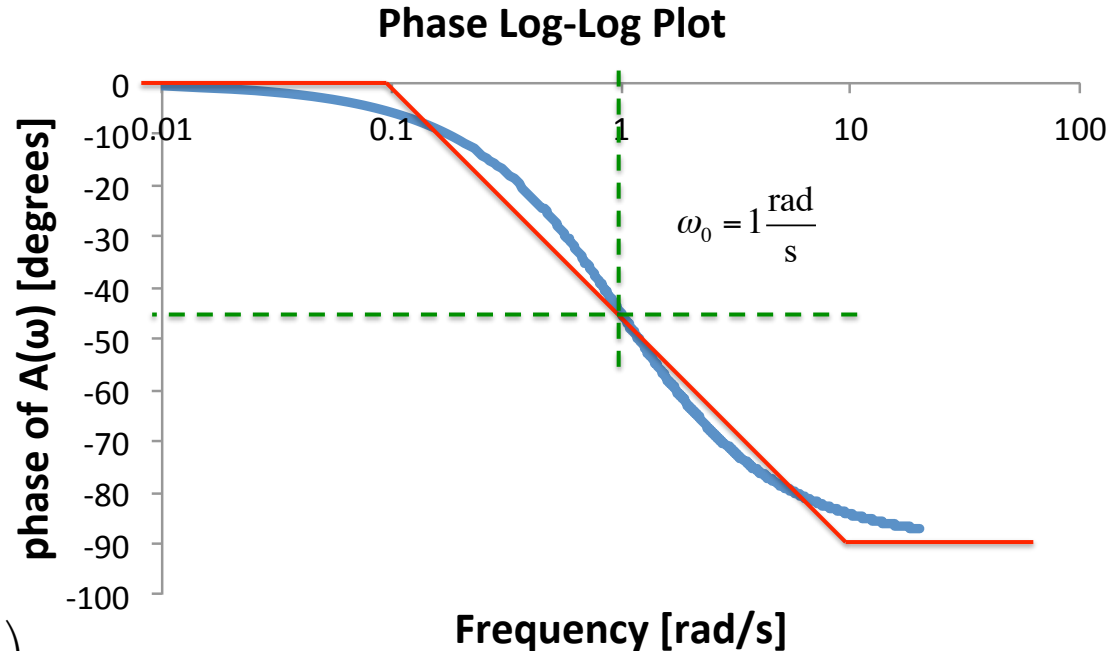
$$\begin{aligned} \angle A_v(\omega) &= \tan^{-1} \left( \frac{\text{Im}[A(\omega)]}{\text{Re}[A(\omega)]} \right) \\ &= \tan^{-1} \left( \frac{0}{1} \right) - \tan^{-1} \left( \frac{\omega RC}{1} \right) \\ &= -\tan^{-1}(\omega RC) = -\tan^{-1} \left( \frac{\omega}{\omega_0} \right) \end{aligned}$$



# Magnitude and Phase

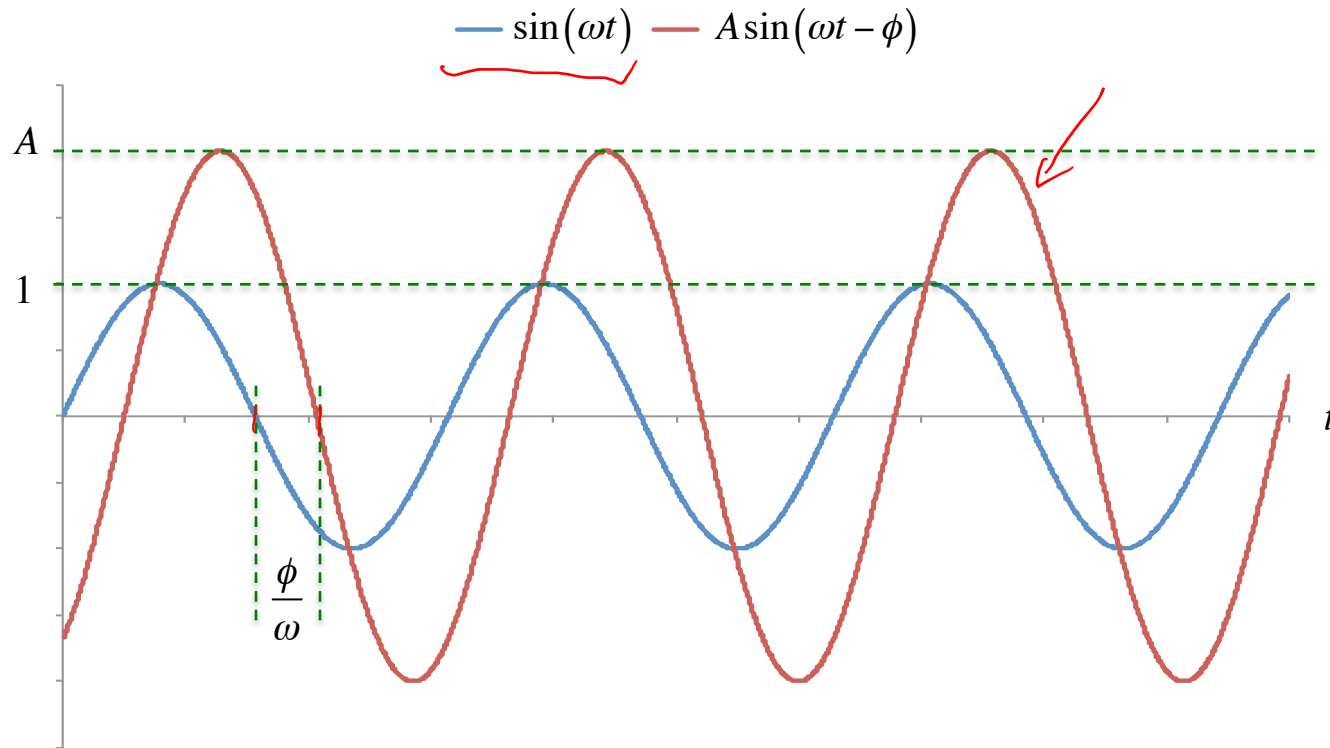

# Another RC Example

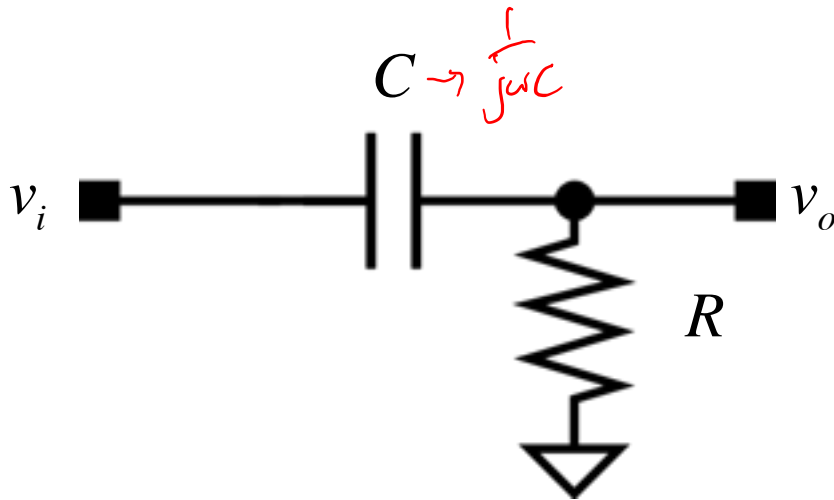

applying voltage division:

$$v_o = \frac{R}{\frac{1}{sC} + R} v_i = \frac{sRC}{1 + sRC} v_i$$


$$A_v(\omega) = \frac{v_o}{v_i} = \frac{sRC}{1 + sRC} \Big|_{s=j\omega}$$

zero

pole




# Frequency Response: Magnitude Response

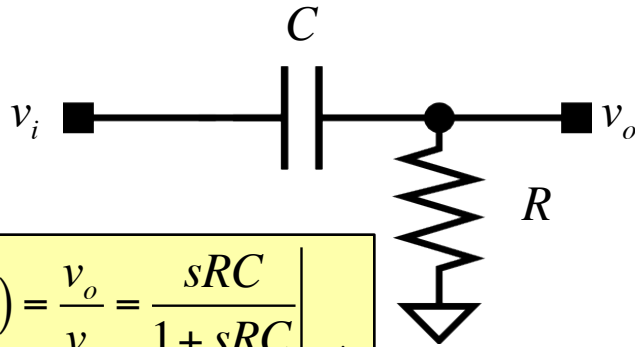


$$A_v(\omega) = \frac{v_o}{v_i} = \frac{sRC}{1 + sRC} \Big|_{s=j\omega}$$

$$\begin{aligned} |A_v(\omega)| &= \frac{\omega RC}{\sqrt{1 + \omega^2 R^2 C^2}} \\ &= \frac{\omega}{\omega_0} \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_0}\right)^2}} \end{aligned}$$

- $\omega < \omega_0$  :  $|A_v(\omega)| \rightarrow 0$
- $\omega = \omega_0$  :  $|A_v(\omega)| \rightarrow \frac{1}{\sqrt{2}}$
- $\omega > \omega_0$  :  $|A_v(\omega)| \rightarrow 1$

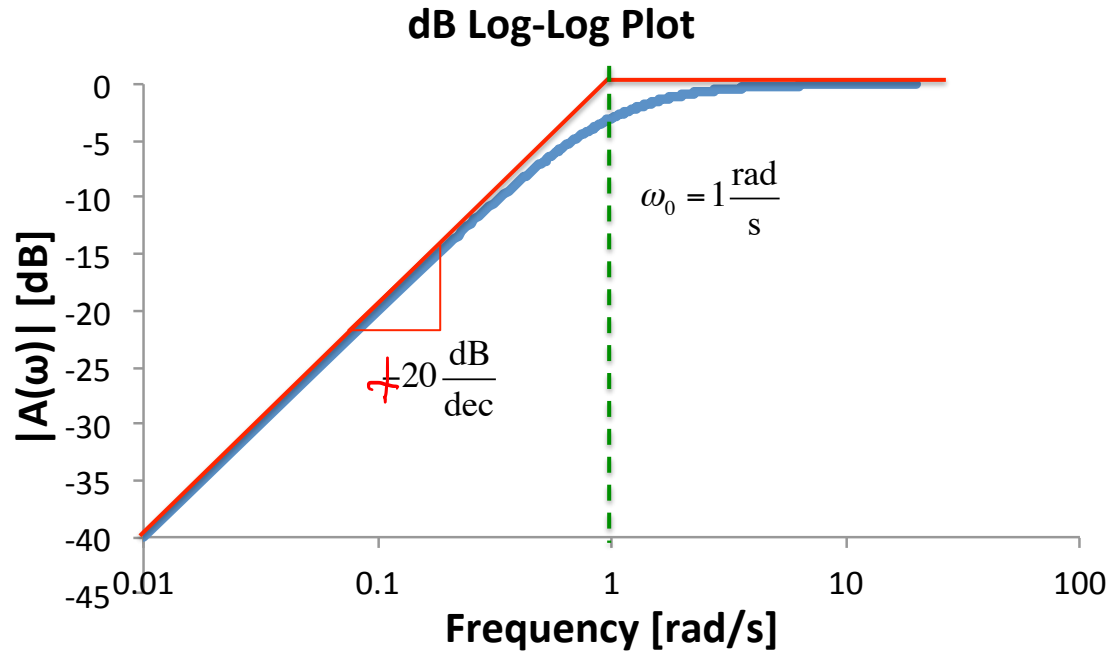

# Phase Response

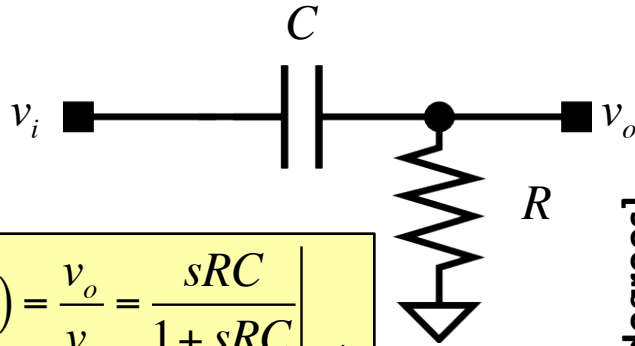


$$A_v(\omega) = \frac{v_o}{v_i} = \frac{sRC}{1 + sRC} \Big|_{s=j\omega}$$

$$\begin{aligned} \angle A_v(\omega) &= \tan^{-1} \left( \frac{\text{Im}[A(\omega)]}{\text{Re}[A(\omega)]} \right) \\ &= \tan^{-1} \left( \frac{sRC}{1} \right) - \tan^{-1} \left( \frac{\omega RC}{1} \right) \end{aligned}$$

$$= 90^\circ - \tan^{-1}(\omega RC) = 90^\circ - \tan^{-1} \left( \frac{\omega}{\omega_0} \right)$$

Phase Log Plot

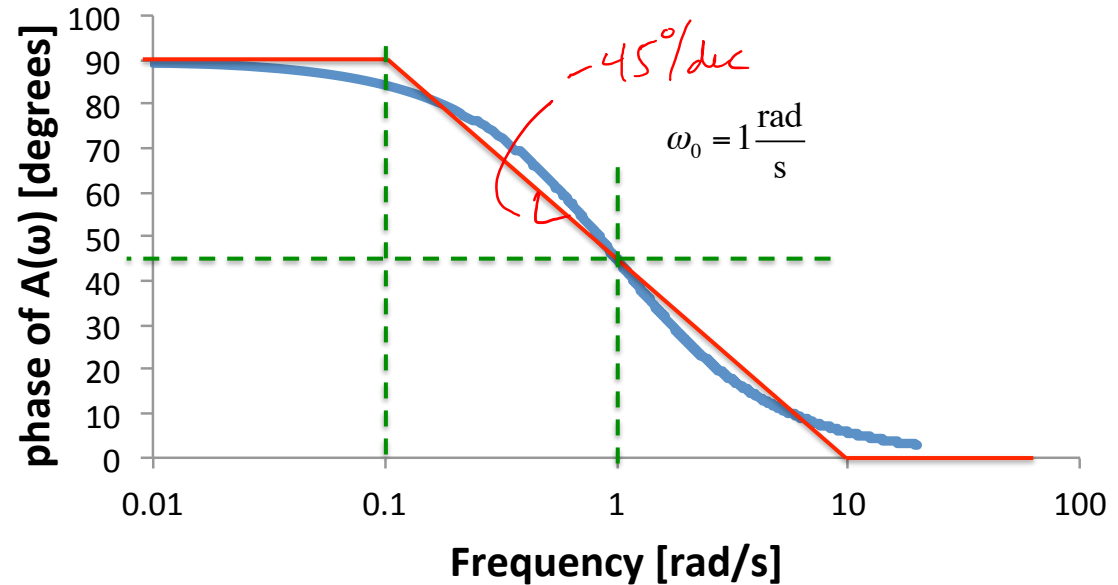

- $\omega < \omega_0$  :  $\angle A_v(\omega) \rightarrow 90^\circ$
- $\omega = \omega_0$  :  $\angle A_v(\omega) = 45^\circ$
- $\omega > \omega_0$  :  $\angle A_v(\omega) \rightarrow 0^\circ$



# A General Zero Term

$$20 \log |A(\omega)| = 20 \log \left[ \sqrt{1 + \left( \frac{\omega}{\omega_0} \right)^2} \right]$$


$$A(\omega) = 1 + j \frac{\omega}{\omega_0}$$

$$B(\omega) = 1 - \frac{j\omega}{\omega_0}$$


$$\angle B(\omega) = \tan^{-1} \left( \frac{-\omega}{\omega_0} \right) = -\tan^{-1} \left( \frac{\omega}{\omega_0} \right)$$

$$\angle A(\omega) = \tan^{-1} \left( \frac{\omega}{\omega_0} \right)$$

dB Log-Log Plot

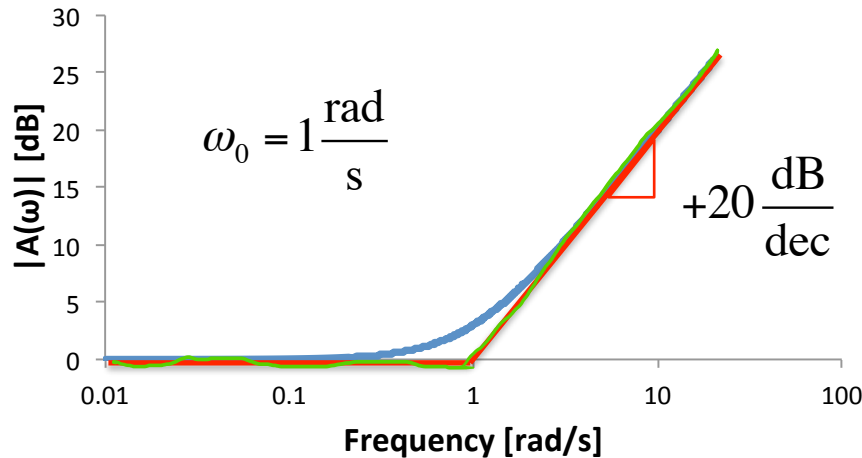

Phase Log Plot

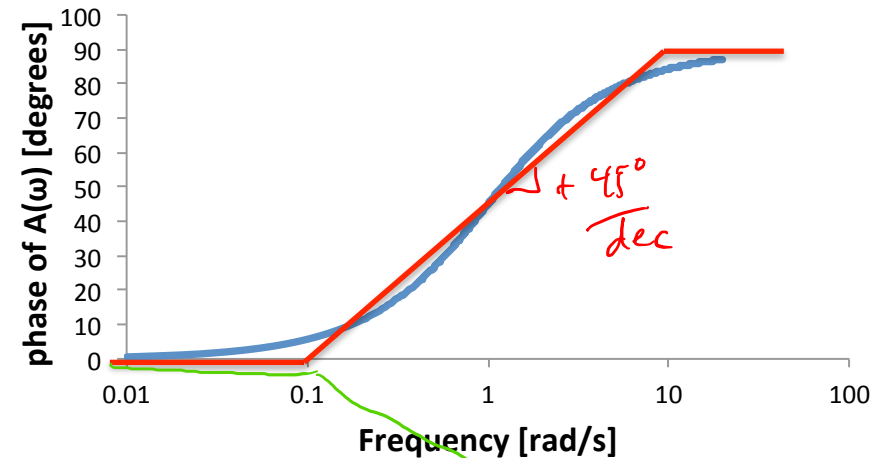

# Generalized Transfer Function

- Factor the numerator and denominator to get the poles and zeros of the system

$$A(s) = A_0 \frac{\overset{\text{DC gain}}{\downarrow} \left(1 + \frac{s}{z_1}\right) \left(1 + \frac{s}{z_2}\right) \cdots \left(1 + \frac{s}{z_N}\right)}{\left(1 + \frac{s}{p_1}\right) \left(1 + \frac{s}{p_2}\right) \cdots \left(1 + \frac{s}{p_D}\right)}$$

$$A(\omega) = A_0 \frac{\left(1 + j \frac{\omega}{\omega_{z_1}}\right) \left(1 + j \frac{\omega}{\omega_{z_2}}\right) \cdots \left(1 + j \frac{\omega}{\omega_{z_N}}\right)}{\left(1 + j \frac{\omega}{\omega_{p_1}}\right) \left(1 + j \frac{\omega}{\omega_{p_2}}\right) \cdots \left(1 + j \frac{\omega}{\omega_{p_D}}\right)}$$



# Magnitude Response Using the dB Scale

$$|A_{dB}(\omega)| = 20 \log \left[ \left| A_0 \frac{\left(1 + j \frac{\omega}{\omega_{z_1}}\right) \left(1 + j \frac{\omega}{\omega_{z_2}}\right) \cdots \left(1 + j \frac{\omega}{\omega_{z_N}}\right)}{\left(1 + j \frac{\omega}{\omega_{p_1}}\right) \left(1 + j \frac{\omega}{\omega_{p_2}}\right) \cdots \left(1 + j \frac{\omega}{\omega_{p_D}}\right)} \right| \right]$$

$$= 20 \log [A_0] + \sum_N 20 \log \left[ \left| 1 + j \frac{\omega}{\omega_{z_i}} \right| \right] + \sum_D 20 \log \left[ \left| \frac{1}{1 + j \frac{\omega}{\omega_{p_i}}} \right| \right]$$

$$- \sum_D 20 \log \left[ \left| 1 + j \frac{\omega}{\omega_{p_i}} \right| \right]$$





# Phase Response

$$A(\omega) = A_0 \frac{\left(1 + j\frac{\omega}{\omega_{z_1}}\right)\left(1 + j\frac{\omega}{\omega_{z_2}}\right)\cdots\left(1 + j\frac{\omega}{\omega_{z_N}}\right)}{\left(1 + j\frac{\omega}{\omega_{p_1}}\right)\left(1 + j\frac{\omega}{\omega_{p_2}}\right)\cdots\left(1 + j\frac{\omega}{\omega_{p_D}}\right)}$$

$A_0 > 0$

$$\angle A(\omega) = \sum_N \angle \left(1 + j\frac{\omega}{\omega_{z_i}}\right) + \sum_D \angle \left(\frac{1}{1 + j\frac{\omega}{\omega_{p_i}}}\right)$$

$A_0 < 0$

$$\angle A(\omega) = 180^\circ +$$



# Next Meeting

- Frequency Response of Amplifiers

