


# Lecture 5

## Balanced Three Phase Systems
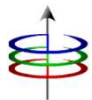
### —Agenda

- **Lecture**



R.D. del Mundo  
Ivan B.N.C. Cruz  
Christian. A. Yap



**Electrical and Electronics Engineering Institute**  
**University of the Philippines**

**R. D. del Mundo**  
**EEE 103 AY2010-11 S2**


# Three Phase Voltages and Current

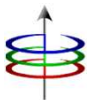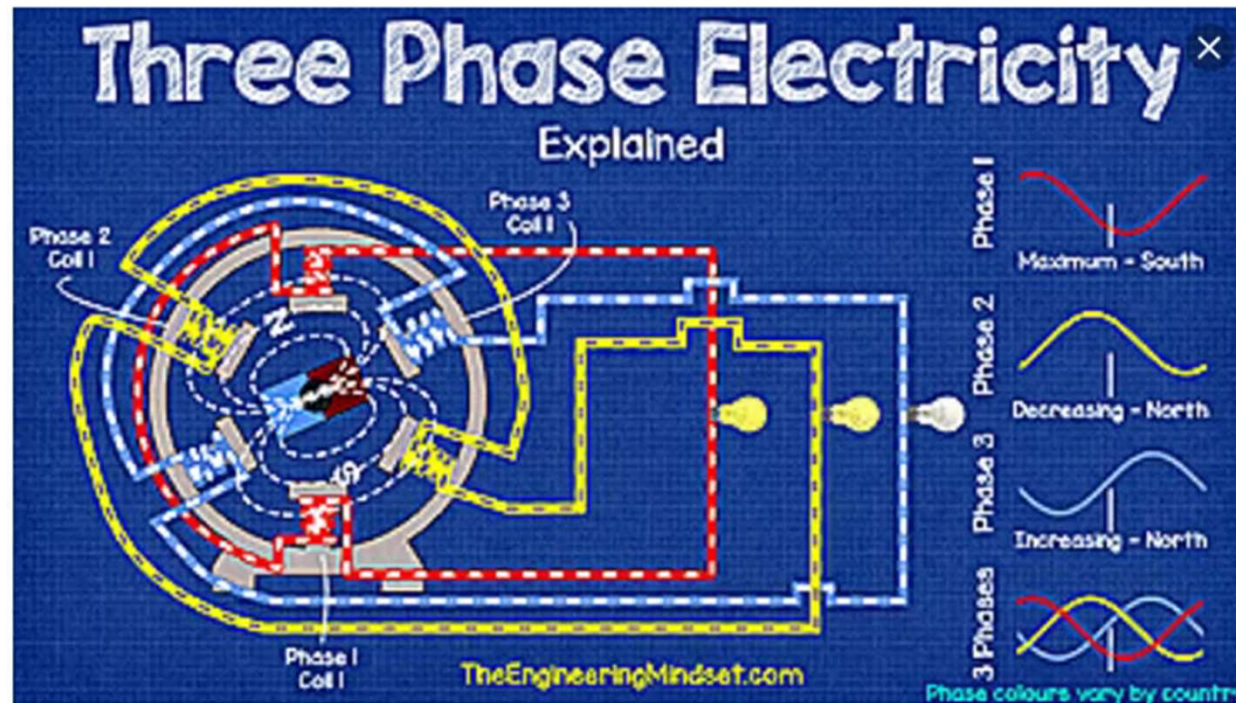
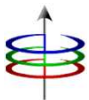
# Lecture Outcomes


at the end of the lecture, the student must be able to ...

- Identify Balanced Three Phase System Components
- Compute the Voltages and Currents in a balanced three phase system.






# Things to Watch out For.

- The Operator “a’
- Neutral Conductor

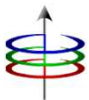

# BALANCED THREE-PHASE SYSTEMS

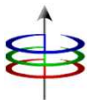

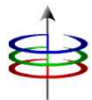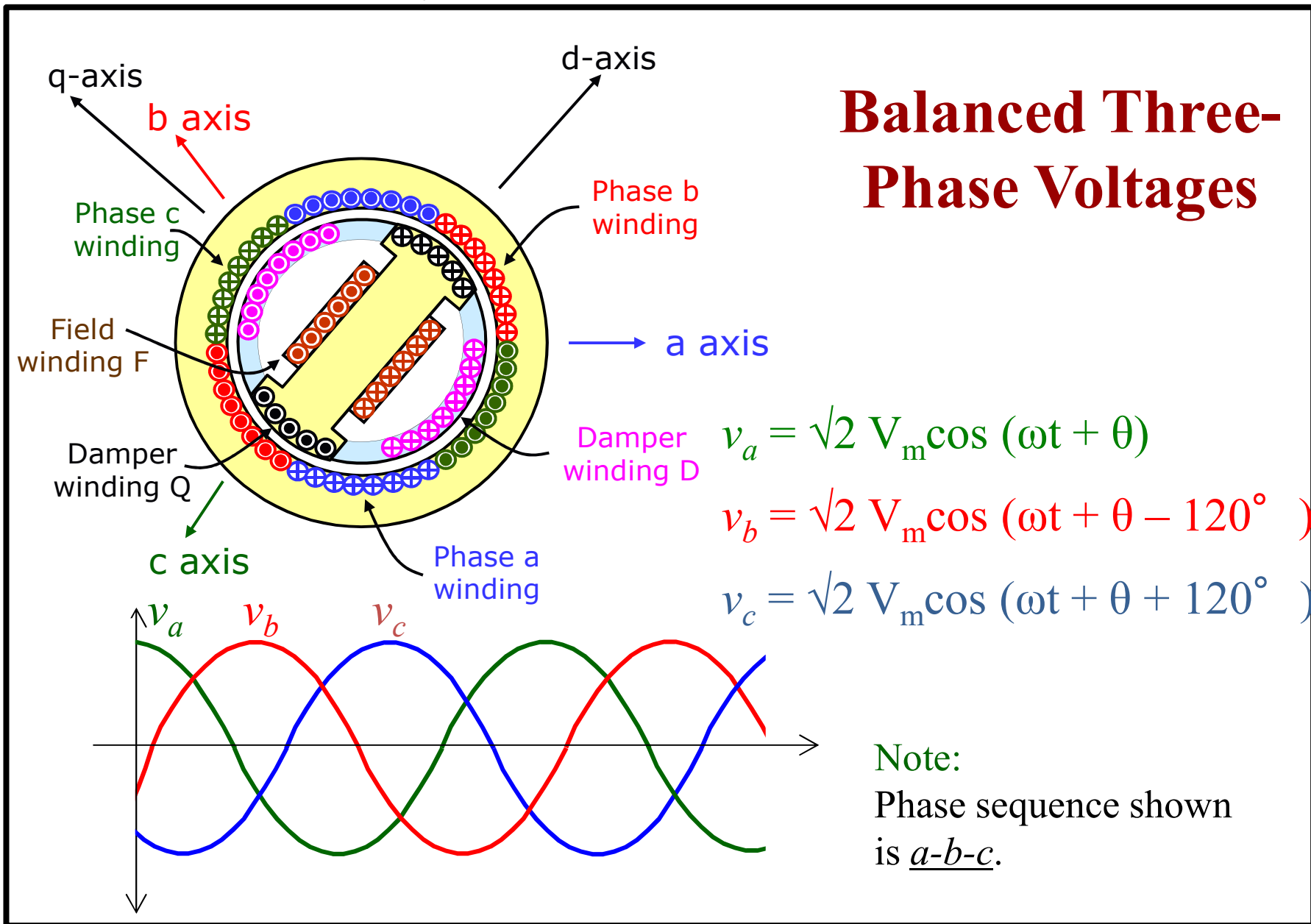



## Balanced Three-Phase Voltages

Transforming to phasors, we get

$$\vec{V}_a = V \angle \theta$$

$$\vec{V}_b = V \angle \theta - 120^\circ$$
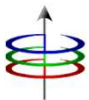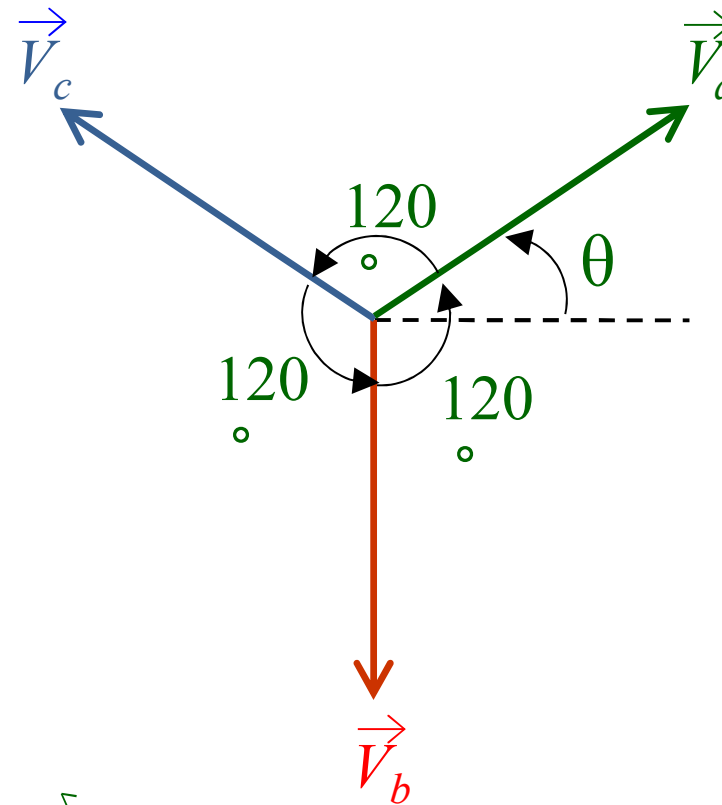
$$\vec{V}_c = V \angle \theta + 120^\circ$$



## Balanced Three-Phase Currents

The currents

$$i_a = \sqrt{2} I_m \cos (\omega t + \theta)$$

$$i_b = \sqrt{2} I_m \cos (\omega t + \theta - 120^\circ)$$

$$i_c = \sqrt{2} I_m \cos (\omega t + \theta + 120^\circ)$$



are three-phase balanced.

In phasor form, we get

$$\vec{I}_a = I \angle \theta$$

$$\vec{I}_b = I \angle \theta - 120^\circ$$
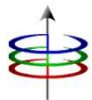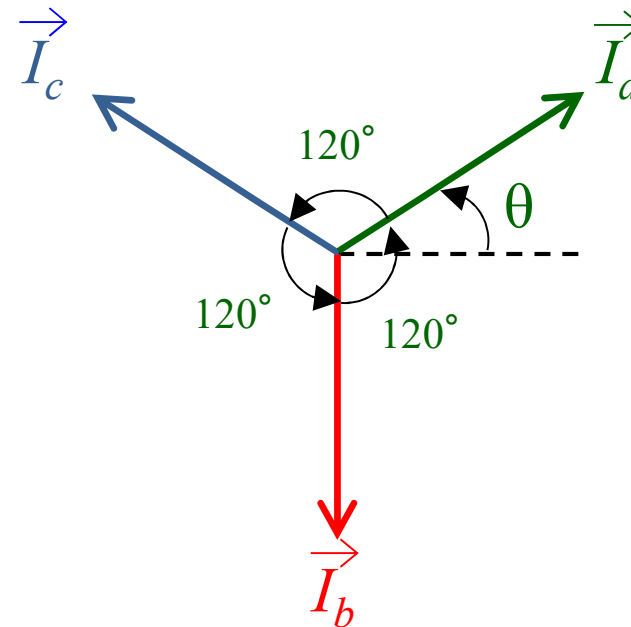
$$\vec{I}_c = I \angle \theta + 120^\circ$$





## Balanced Three-Phase System


A **balanced three-phase system** consists of :

1. Balanced three-phase sinusoidal sources;
2. Balanced three-phase loads; and
3. The connecting wires have equal impedances.

A **balanced three-phase load** has:

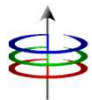
- a) Equal impedances per phase; or
- b) Equal P and Q per phase.

**Note:** The load may be connected in wye or delta.




# Three Phase System Components

- Sources
- Loads
- Lines

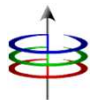


# Three-Phase Sources

## Wye-Connected Source

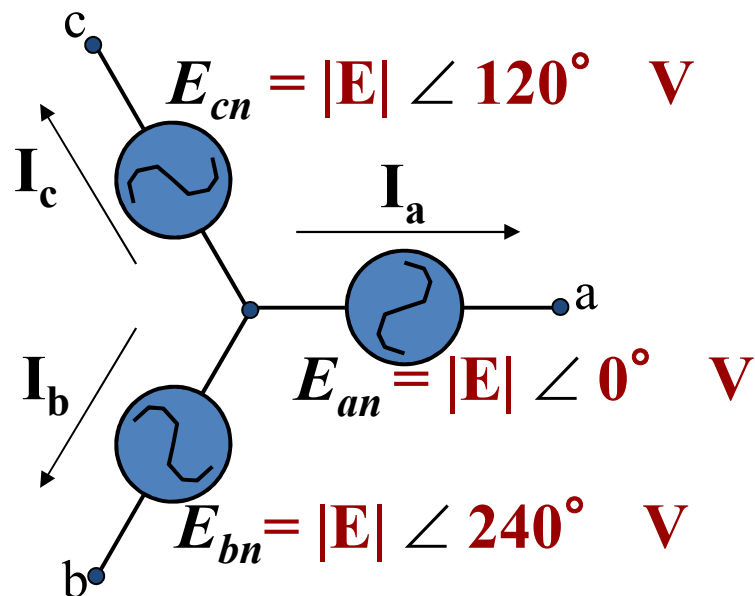


## Delta-Connected Source

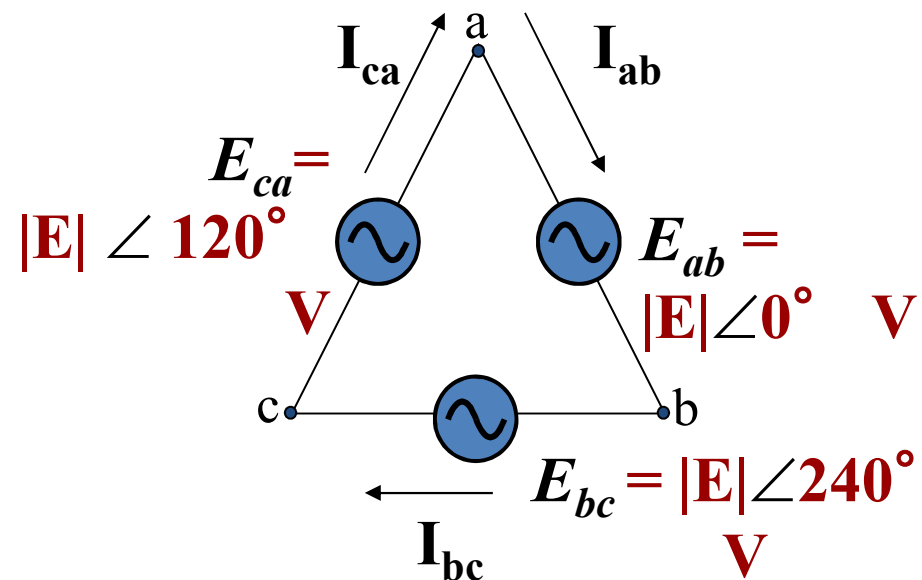



Note 1: The synchronous generator is a three-phase machine designed to generate balanced three-phase voltages.

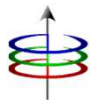Note 2: Neutral point  $n$  exists only for wye-connected systems.




# Three-Phase Loads

## Wye-Connected Load

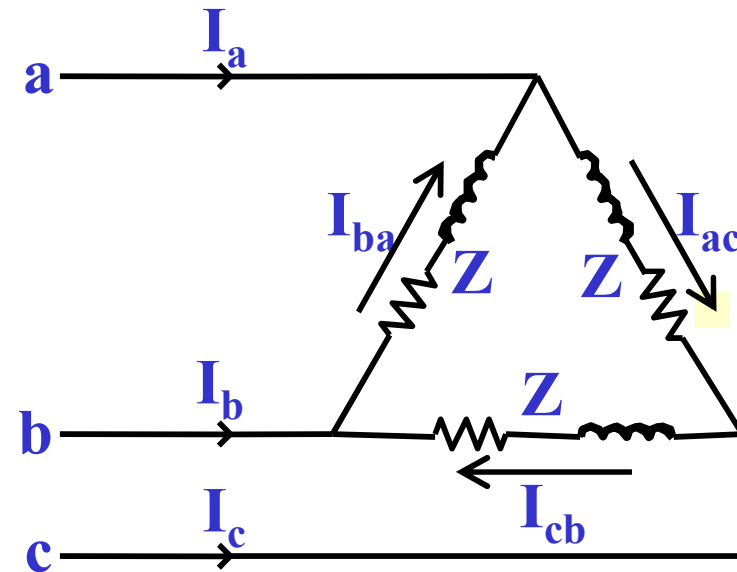
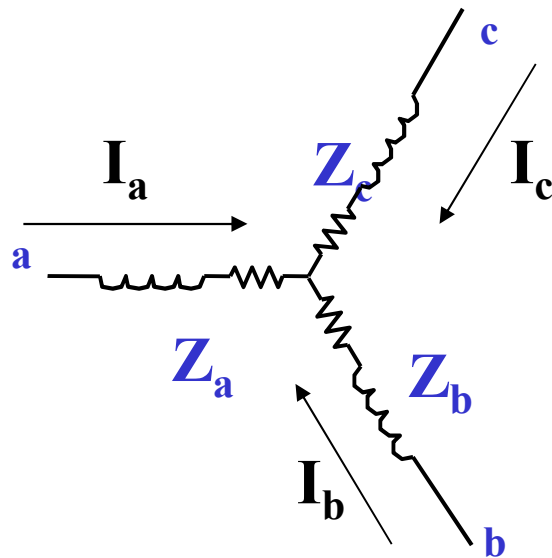

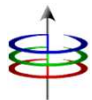
## Delta-Connected Load

Note: Neutral point  $n'$  exists only for wye-connected systems.



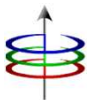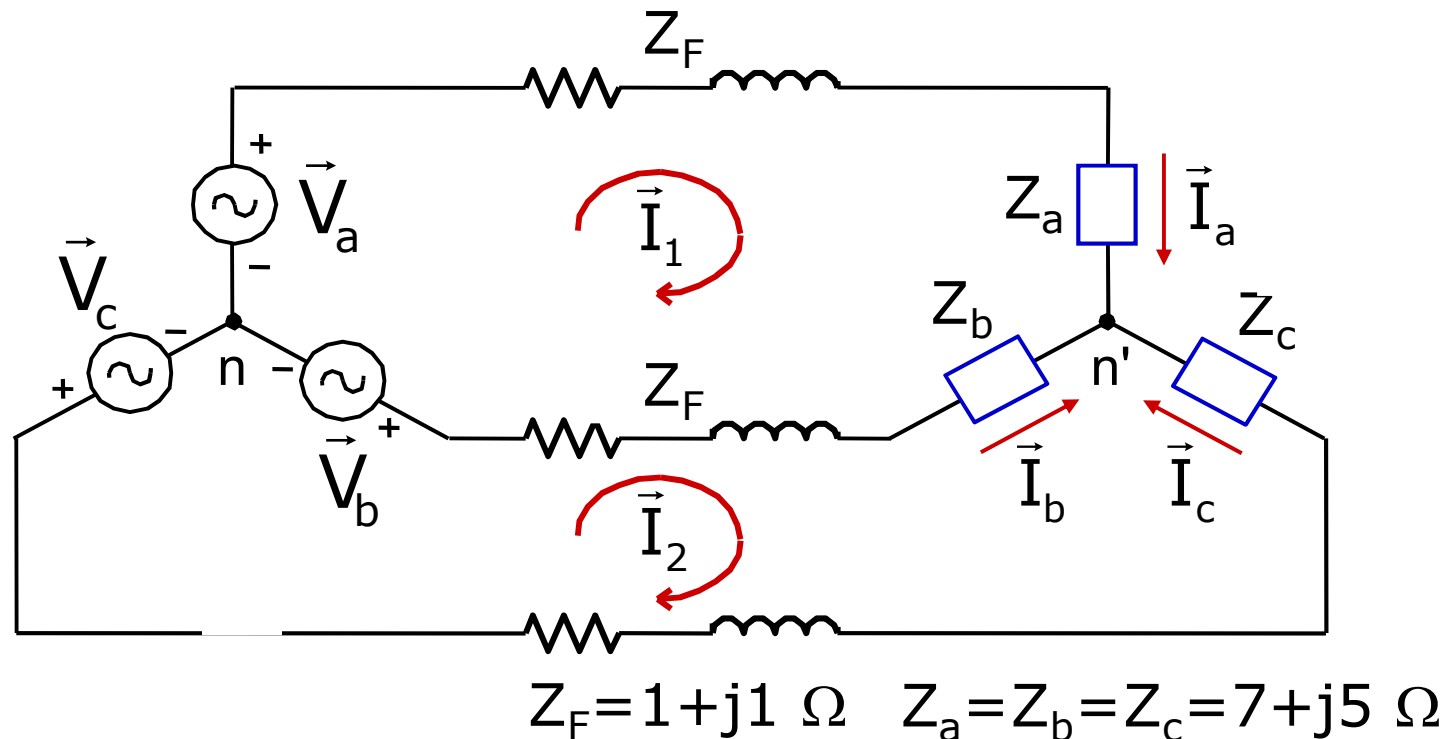Given  $V_a=200/0^\circ$  volts,  $V_b=200/-120^\circ$  volts and  $V_c=200/120^\circ$  volts. Find the phasor currents  $I_a$ ,  $I_b$  and  $I_c$ . Also, find  $P$  and  $Q$  supplied to  $Z_a$ ,  $Z_b$  and  $Z_c$  and the load power factor.



Mesh equations using loop currents  $I_1$  and  $I_2$ .

$$V_a - V_b = 2(Z_f + Z_L)I_1 - (Z_f + Z_L)I_2$$

$$V_b - V_c = -(Z_f + Z_L)I_1 + 2(Z_f + Z_L)I_2$$

Substitution gives


$$300 + j173.2 = (16 + j12)I_1 - (8 + j6)I_2$$

$$-j346.4 = -(8 + j6)I_1 + (16 + j12)I_2$$

Solving simultaneously we get

$$I_1 = 20 \angle -36.87^\circ \text{ A}$$
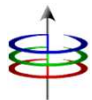
$$I_2 = 20 \angle -96.87^\circ \text{ A}$$




Solving for currents  $I_a$ ,  $I_b$  and  $I_c$ :

$$I_a = I_1 = 20 \angle -36.87^\circ \text{ A}$$

$$I_b = I_2 - I_1 = 20 \angle -156.87^\circ$$
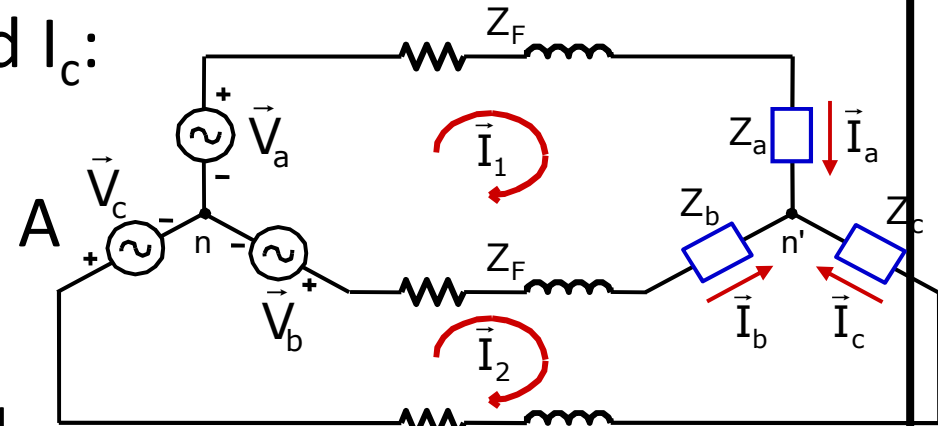
$$I_c = -I_2 = 20 \angle 83.13^\circ \text{ A}$$



**Note:** Currents  $I_a$ ,  $I_b$  and  $I_c$  are balanced.


Try to get the sum of the currents. What is it equal to?

Power and Reactive Power supplied to load impedances  $Z_a$ ,  $Z_b$  and  $Z_c$ .

$$P_a = P_b = P_c = |I|^2 R = (20)^2 (7) = 2800 \text{ Watts}$$

$$Q_a = Q_b = Q_c = |I|^2 X = (20)^2 (5) = 2000 \text{ VARs}$$

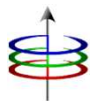**Note:** These equations for P and Q are correct if R and X are used



# The Operator “ $a$ ”



**Define:**  $a = 1 \angle 120^\circ = 1e^{j2\pi/3} = -0.5 + j0.866$

$a^2 = 1 \angle 240^\circ = 1e^{j4\pi/3} = -0.5 - j0.866$

$a^3 = 1 \angle 360^\circ = 1e^{j2\pi} = 1 \angle 0^\circ = 1$

**Note:**  $1 + a + a^2 = 0$

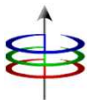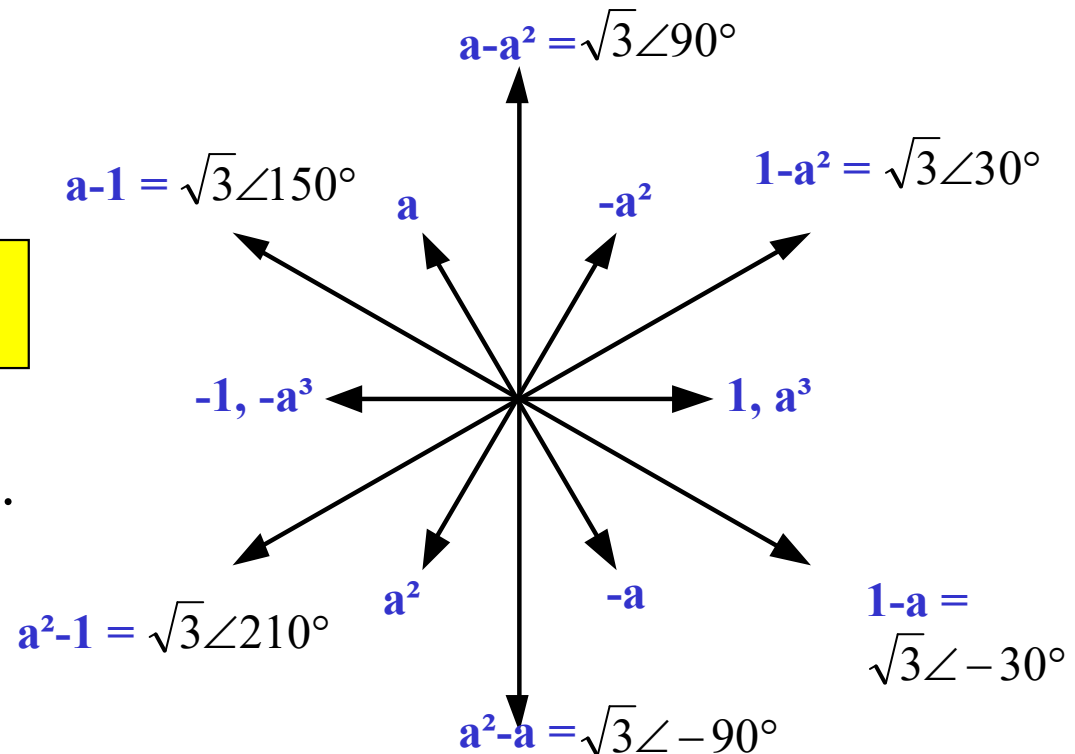The sum of three-phase balanced phasors is zero.





## Definitions: Voltages in Three-Phase Systems

### Line-to-Line Voltage ( $V_{LL}$ )

The voltage across any two line terminals.


### Line-to-Neutral Voltage ( $V_{LN}$ )

The voltage across any one line terminal and neutral.
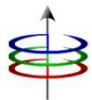
### Phase Voltage ( $V_p$ )



The voltage across any one leg of a 3-phase system.

- Wye-connected:  $V_p = V_{LN}$
- Delta-connected:  $V_p = V_{LL}$



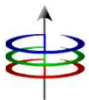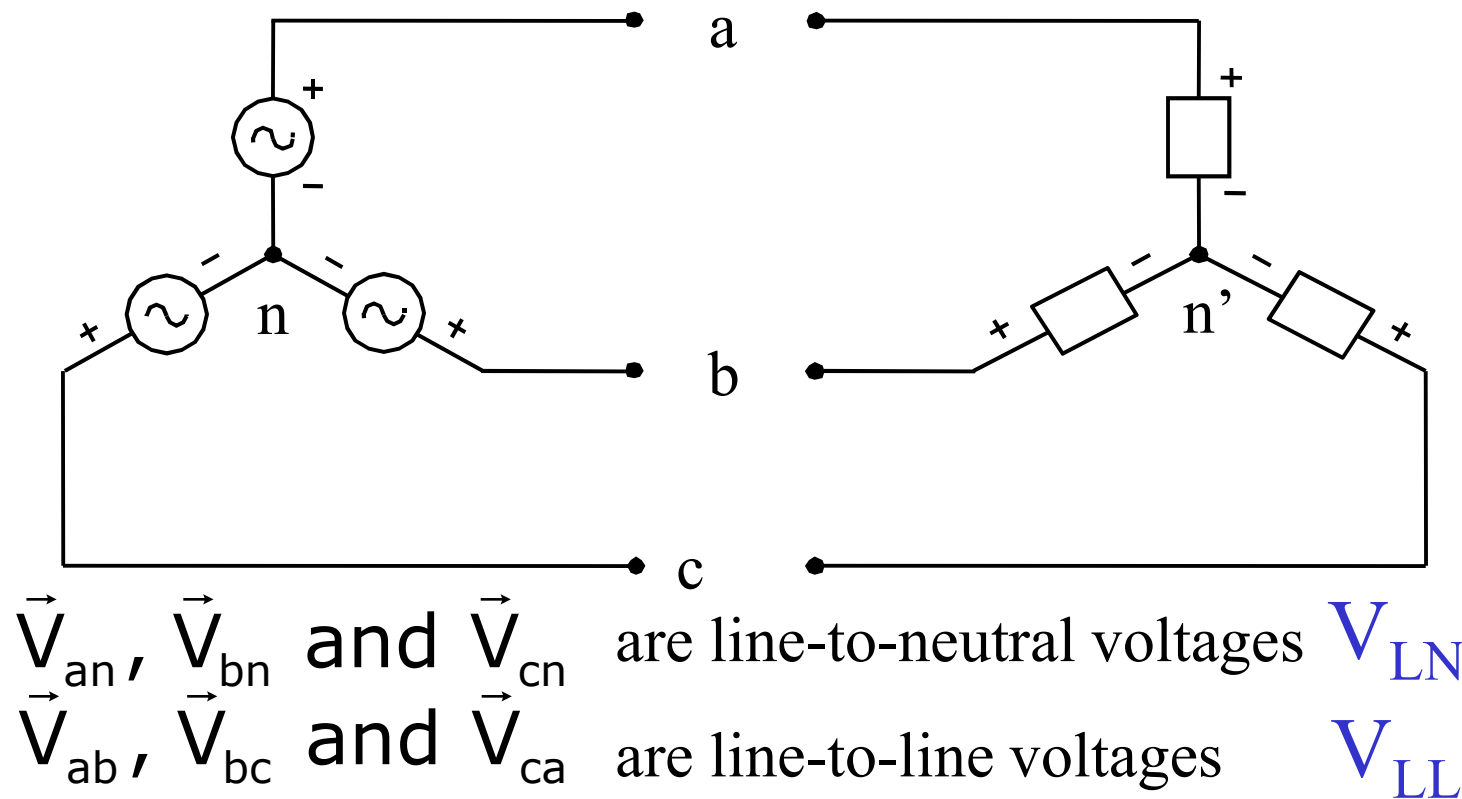
## Line-to-Line, Line-to-Neutral, and Phase Voltages

Consider a three-phase wye-connected generator or a three-phase wye-connected load.




# For a Delta Connected System?

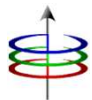

For a balanced WYE-connected three-phase system, from KVL:

$$\begin{aligned}
 V_{ab} &= V_{an} + V_{nb} \\
 &= V_{an} - V_{bn} \\
 &= V \angle 0^\circ - V \angle -120^\circ \\
 &= V (1 - a^2) \\
 V_{ab} &= V (\sqrt{3} \angle 30^\circ)
 \end{aligned}$$

$$|V_{LL}| = \sqrt{3} |V_{LN}|$$

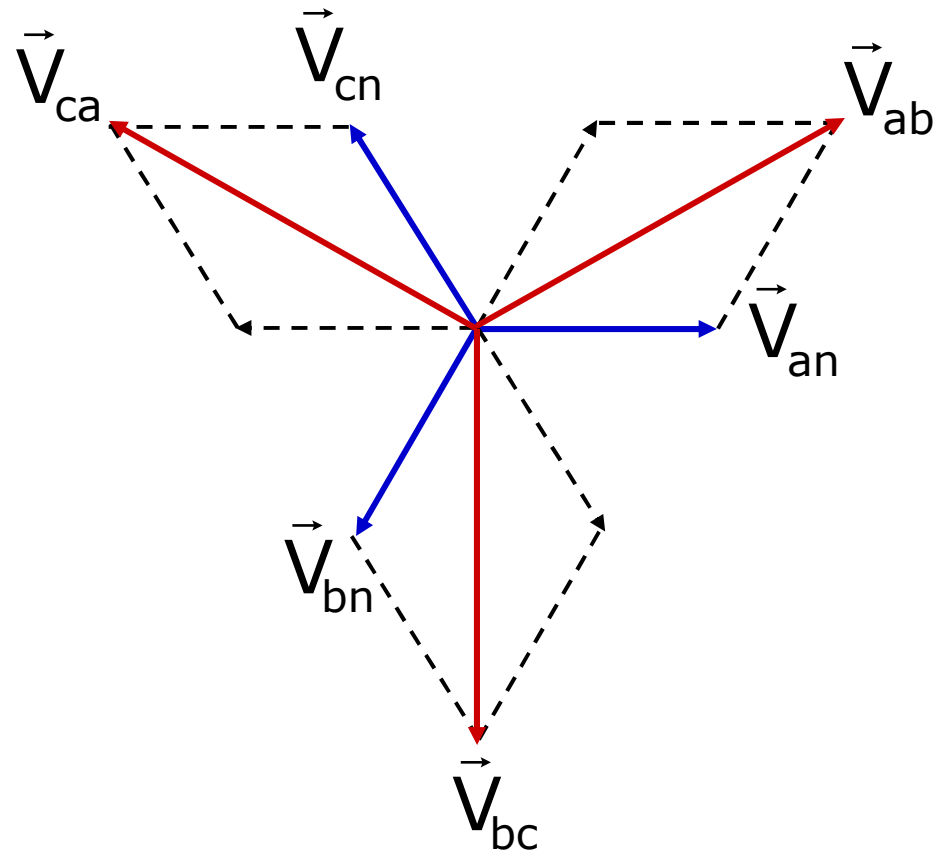

## Definitions: Currents in Three-Phase Systems

### Line Current ( $I_L$ )


The current flowing through lines from source to load.

### Phase Current ( $I_P$ )

The current flowing through any one leg of the system.


- Wye connection:  $I_P = I_L$
- Delta connection:  $I_P = \frac{I_L}{\sqrt{3}}$

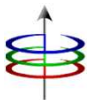Note: There is no definition for “Line-to-Line Current.”



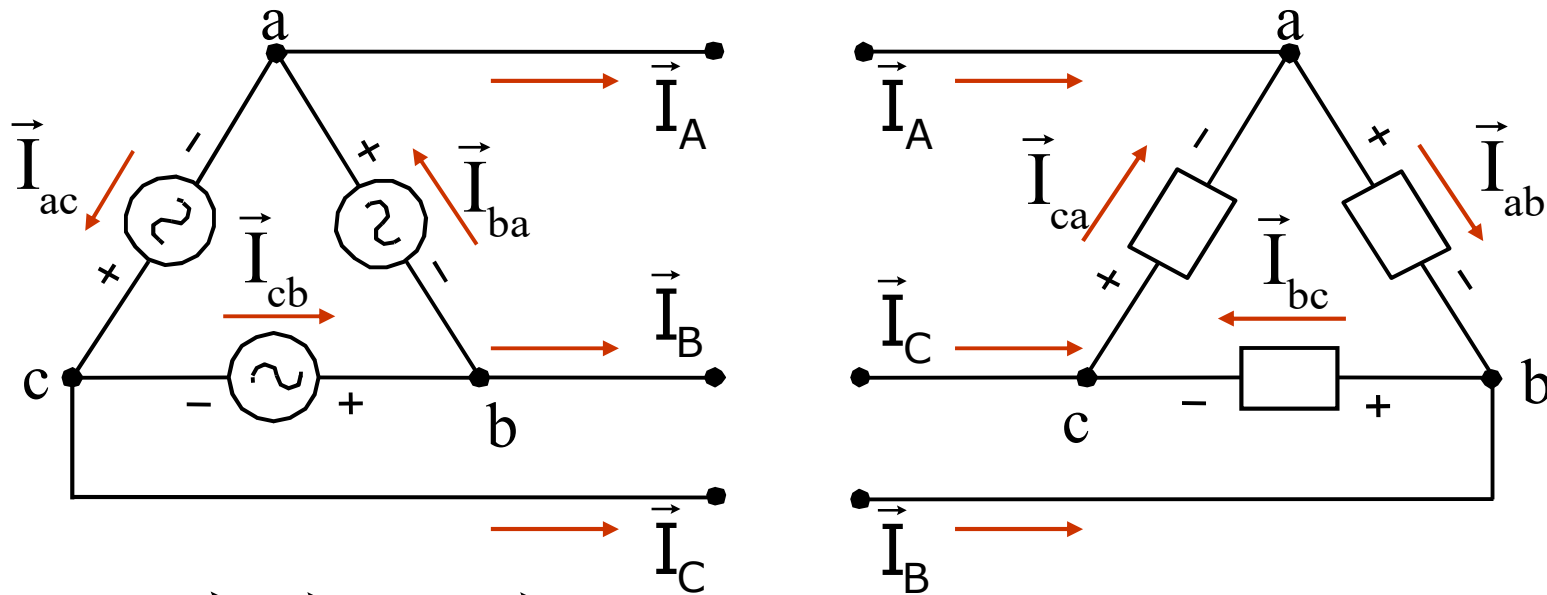
## Line and Phase Currents

Consider a three-phase delta-connected generator or a three-phase delta-connected load.



$\vec{I}_{ab}$ ,  $\vec{I}_{bc}$  and  $\vec{I}_{ca}$  are phase currents  $I_\phi$  or  $I_P$

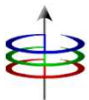
$\vec{I}_A$ ,  $\vec{I}_B$  and  $\vec{I}_C$  are line currents  $I_L$



For the balanced DELTA-connected  
three-phase load,  
from KCL:

$$\begin{aligned}
 I_A &= I_{ab} - I_{ca} \\
 &= I \angle 0^\circ - I \angle 120^\circ \\
 &= I (1 \angle 0^\circ - 1 \angle 120^\circ) \\
 &= I (1 - a) \\
 I_A &= I (\sqrt{3} \angle -30^\circ)
 \end{aligned}$$

$$|I_L| = \sqrt{3} |I_P|$$

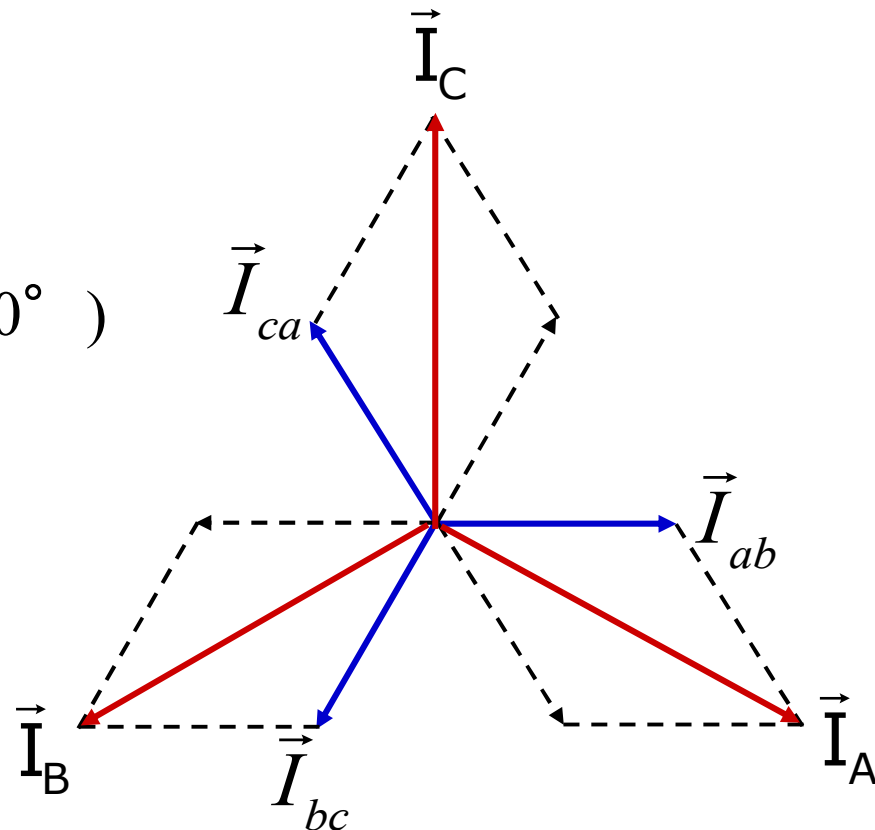

# Voltage and Current Equations

For balanced three-phase systems:

Wye - connected


$$|V_{LL}| = \sqrt{3} |V_{LN}|$$

$$I_p = I_L$$

Delta - connected

$$V_P = V_{LL}$$



$$I_p = \frac{I_L}{\sqrt{3}}$$

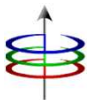



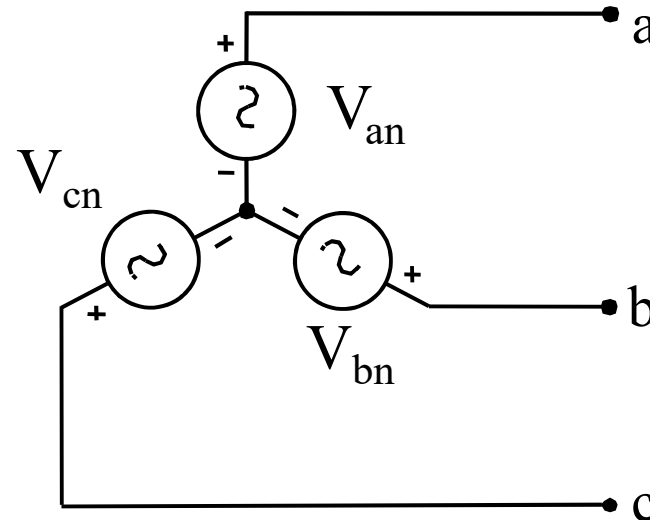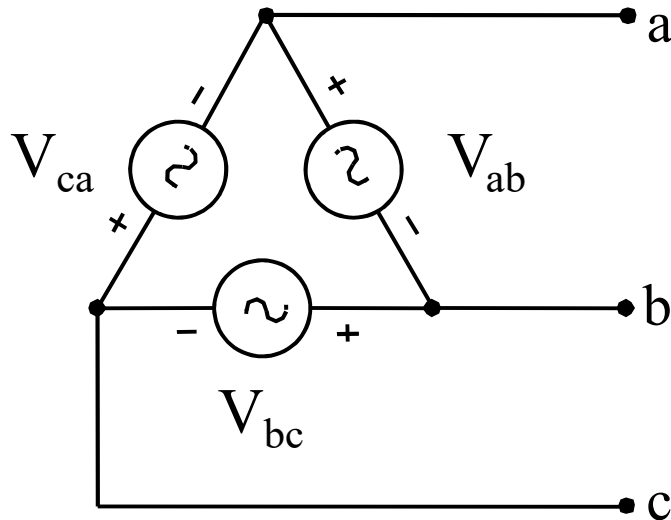
## Δ-Y Conversion for Generators

Given a balanced 3-phase delta connected generator, what is its equivalent wye ?




**Note:** The line-to-line voltages must be the same.

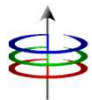If  $V_{ab} = V_L \angle \alpha$ , then  $V_{an} = (1/\sqrt{3}) V_L \angle \alpha - 30^\circ$


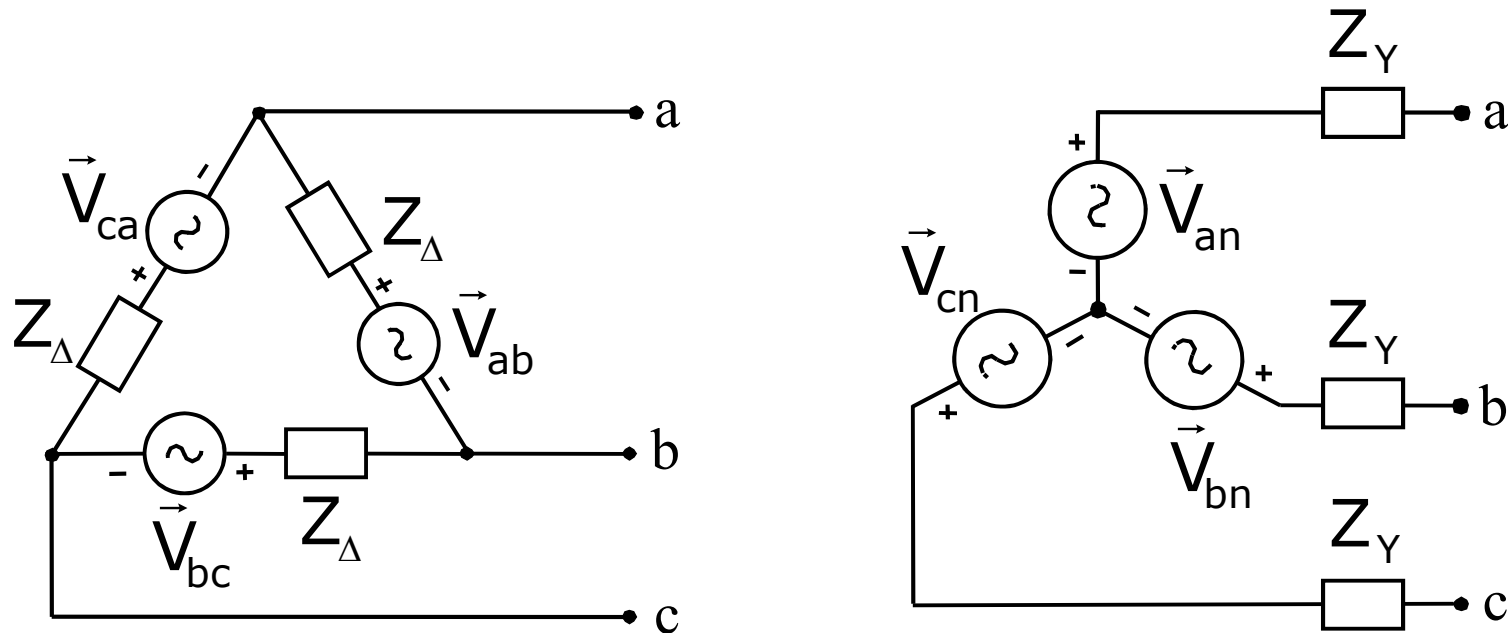
## Conversion for a Generator with Z


Given  $\vec{V}_{ab}$  and  $Z_{\Delta}$ , find  $\vec{V}_{an}$  and  $Z_Y$



We get



$$\vec{V}_{an} = \left( \frac{1}{\sqrt{3}} \angle -30^\circ \right) \vec{V}_{ab}$$

$$Z_Y = \frac{1}{3} Z_{\Delta}$$

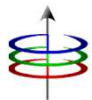

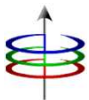
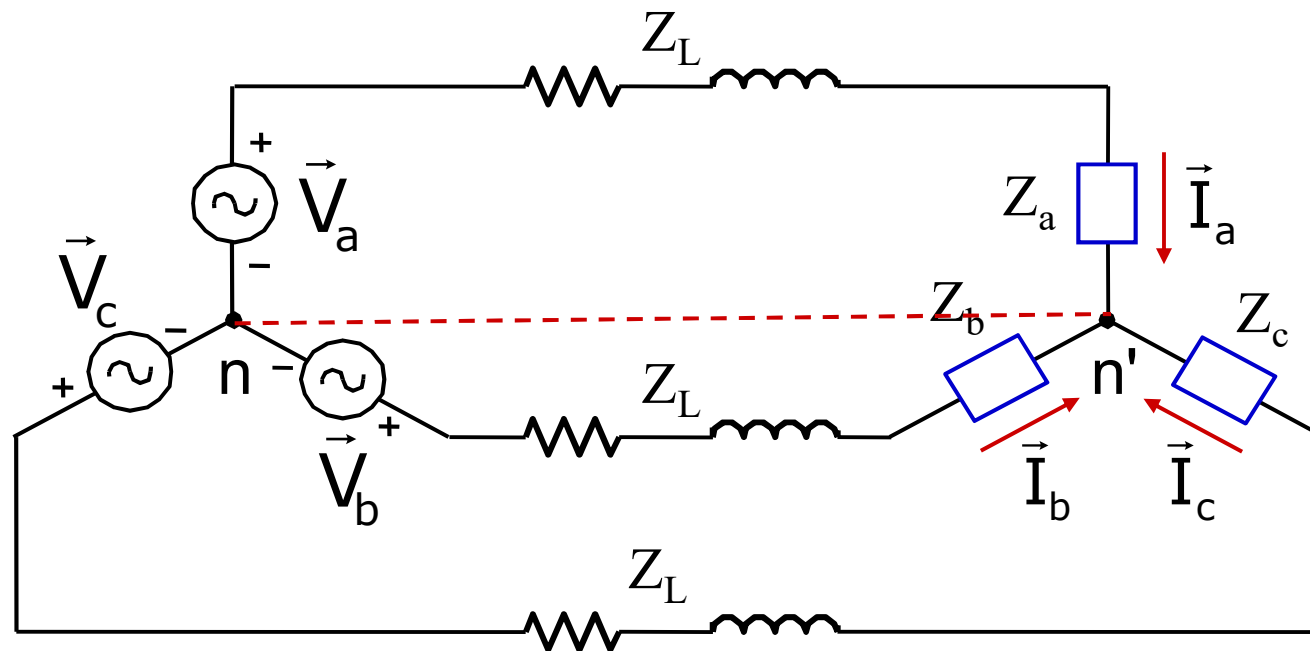
# The Neutral Conductor

Consider a balanced three-wire three-phase system with wye-connected generator and loads.





# The Neutral Conductor

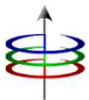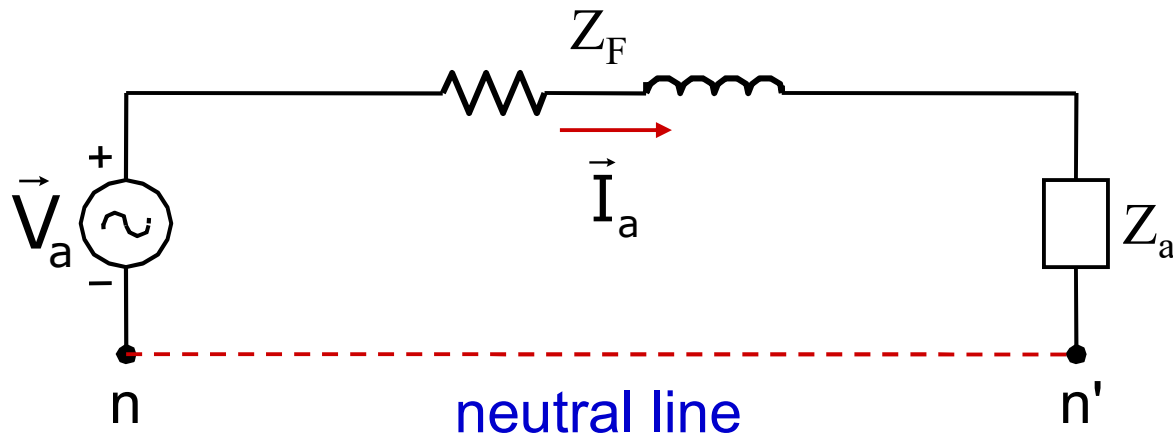1. The sum of balanced phasors is zero.
2. If a neutral conductor is connected between  $n$  and  $n'$ , no current will flow through the neutral conductor.
3. The nodes  $n$  and  $n'$  are at the same potential!
4. ☐ We can analyze the circuit using single-phase analysis.


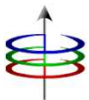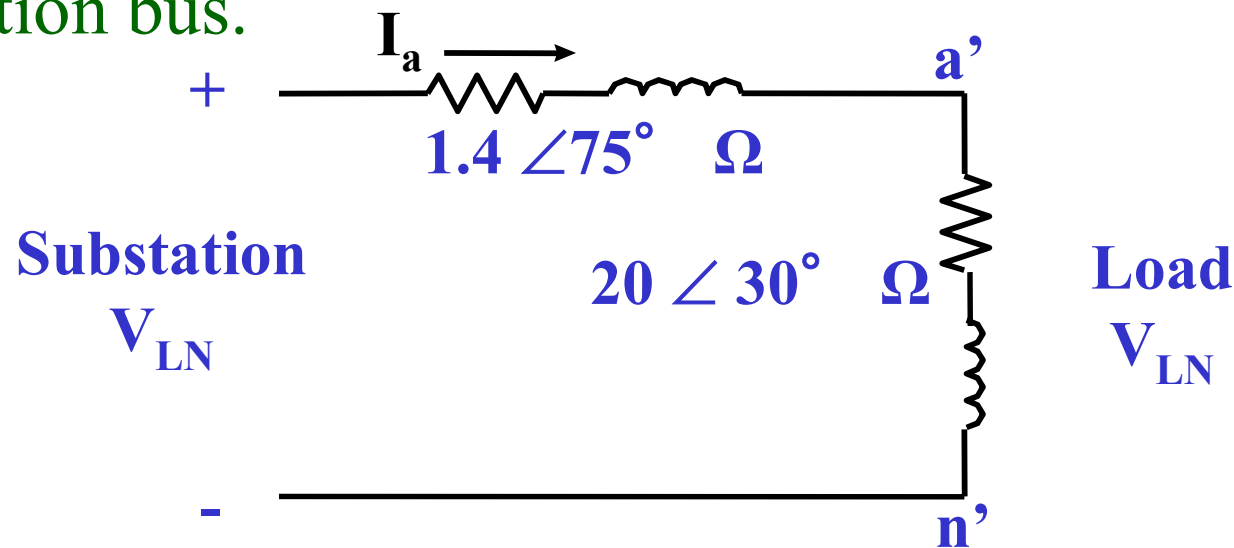
## Example

The terminal voltage of a wye-connected load consisting of three equal impedances of  $20 \angle 30^\circ \Omega$  is 4.4 kV line-to-line. The impedance of each of the three lines connecting the load to a bus at a substation is  $Z_L = 1.4 \angle 75^\circ$ . Find the line-to-line voltage at the substation bus.



The magnitude of voltage-to-neutral at the load is:


$$V_{a'n'} = \frac{4400}{\sqrt{3}} = 2540 \text{ V } \angle 0^\circ \text{ (as reference)}$$

$$I_{a'n'} = \frac{2540 \angle 0^\circ}{20 \angle 30^\circ} = 127 \text{ A } \angle -30^\circ$$

The line-to-neutral voltage at the substation is:

$$\begin{aligned} V_{a'n'} + I_{a'n'} \cdot Z_L &= 2540 \angle 0^\circ + 127 \angle -30^\circ (1.4 \angle 75^\circ) \\ &= 2666 + j125.7 \\ &= 2670 \angle 2.70^\circ \text{ V} \end{aligned}$$

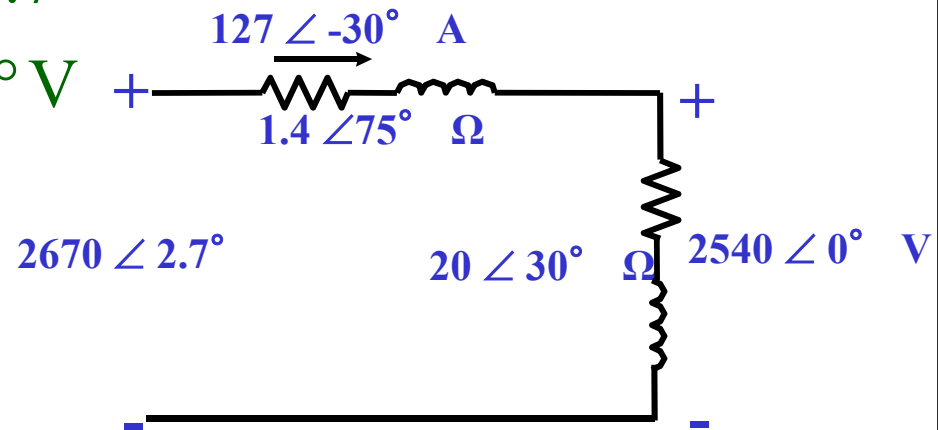The voltage magnitude  
at the substation is  
 $4.62 \text{ kV } \approx 2.67\sqrt{3}$



## Homework

Balanced 3-phase system with  $V_{ab} = 173.2 \angle 0^\circ$  and wye-connected load with  $Z_{\text{LOAD}} = 10 \angle 20^\circ \Omega$ . Assume a-b-c phase sequence.

1. Draw the described balanced three phase system. Don't forget to properly label the voltages and currents
2. Determine **all** phasor voltages and currents.

