

# EEE 51 Assignment 6

2nd Semester SY 2018-2019

Due: 5pm Tuesday, March 19, 2019 (Rm. 220)

*Instructions:* Write legibly. Show all solutions and state all assumptions. Write your full name, student number, and section at the upper-right corner of each page. Start each problem on a new sheet of paper. Box or encircle your final answer.

Answer sheets should be color coded according to your lecture section. The color scheme is as follows:

**THQ** – yellow  
**THU** – white  
**WFX** – pink

## 1. Single-Ended Operational Amplifier.

A single-ended operational amplifier was created with a topology slightly similar to the LF35 op amp which is shown in Figure 1. You are tasked to verify the approximate characteristics of the design at  $T = 300\text{ K}$ . The MOSFETs have  $k = \frac{\mu C_{ox}}{2} \frac{W}{L} = 250\text{ }\mu\text{A/V}^2$  and  $\lambda = 0.001\text{ V}^{-1}$ . The BJTs have the following:  $\beta = 100$  and  $V_A = 50\text{ V}$ . Assume that the current sources and diodes are ideal ( $V_{min} = 0\text{ V}$  and  $R \rightarrow \infty$  for the current sources; and  $V_f = 0.7\text{ V}$ ,  $R_{ON} = 0\text{ }\Omega$ , and  $R_{OFF} \rightarrow \infty$  for the diodes) and that the transistors are in their necessary operating regions (saturation for MOSFETs and forward active for BJTs). **Show your complete solution and round off to the required value to merit a maximum of full points.**

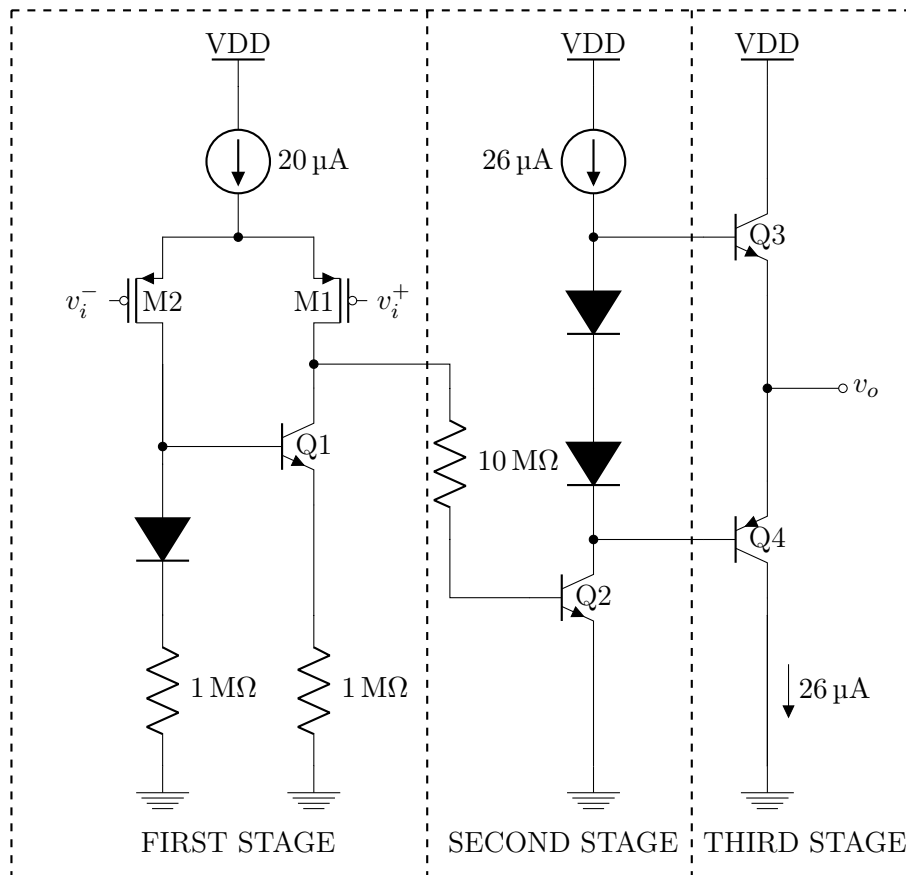


Figure 1: The Single-Ended Operational Amplifier

- (a) What should be the value (rounded to the nearest ten thousands) of the load resistance to get maximum power? (2 pts)
- (b) Find the value of the following rounded to the nearest whole number:
- Gain of the first stage with respect to  $v_i^+$  (ie:  $A_{v1} = \frac{v_{o1}^-}{v_i^+}$ ) (2 pts)
  - Gain of the second stage (2 pts)
  - Gain of the third stage (2 pts)
- (c) Give the value of the differential gain ( $\frac{v_o}{v_{id}}$ ) approximate to the nearest ten thousands. (2 pts)

- Subscribe2PewDiePie

2. **Simple Two-stage Operational Amplifier.** Consider the circuit shown in Fig. 2. Given the following:  $V_{DD} = 3V$ ,  $I_{REF} = 1mA$ ,  $k_p = 6.25mA/V^2$ ,  $k_n = 19.75mA/V^2$ ,  $V_{th,n} = 0.7V$ ,  $|V_{th,p}| = 0.8V$ .

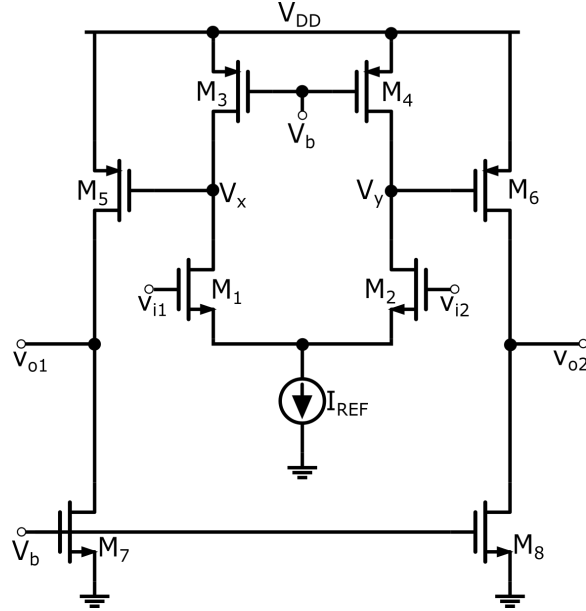


Figure 2: 2-stage Operational Amplifier Circuit

- (a) What is the CM voltage level needed at the drains of  $M_3$  and  $M_4$  so that the current through the  $M_5$ - $M_7$  and  $M_6$ - $M_8$  is  $1mA$ ? [2 pts]
- (b) Keeping the values obtained in (a), what is the maximum input CM level? [2 pts]
- (c) For all transistors, evaluate the following:
- The drain-to-source currents,  $I_{DS}$ . [0.5 pts]
  - The gate-to-source voltages,  $|V_{GS}|$ . [1 pt]
  - $g_m$ . [1 pts]
  - $r_o$ . Use  $\lambda_n = 0.1V^{-1}$  and  $\lambda_p = 0.2V^{-1}$ . [0.5 pt]

For simplicity, compile your answers into a tabular format as shown below:

Parameter	M1	M2	M3	M4	M5	M6	M7	M8
$I_{DS}$								
$ V_{GS} $								
$g_m$								
$r_o$								

- (d) Calculate the overall voltage gain of the circuit. [2 pts]
- (e) What is the maximum output swing? [1 pt]

TOTAL: 20 points.