


Lecture

Complex Power Equations and Computations

Agenda

- **Lecture**

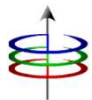R.D. del Mundo
Ivan B.N.C. Cruz
Christian. A. Yap




Electrical and Electronics Engineering Institute
University of the Philippines



R. D. del Mundo
EEE 103 AY2010-11 S2

Visualizing Phasors

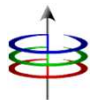- <http://www.swarthmore.edu/NatSci/echeeve1/Ref/phasors/phasors.html>



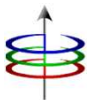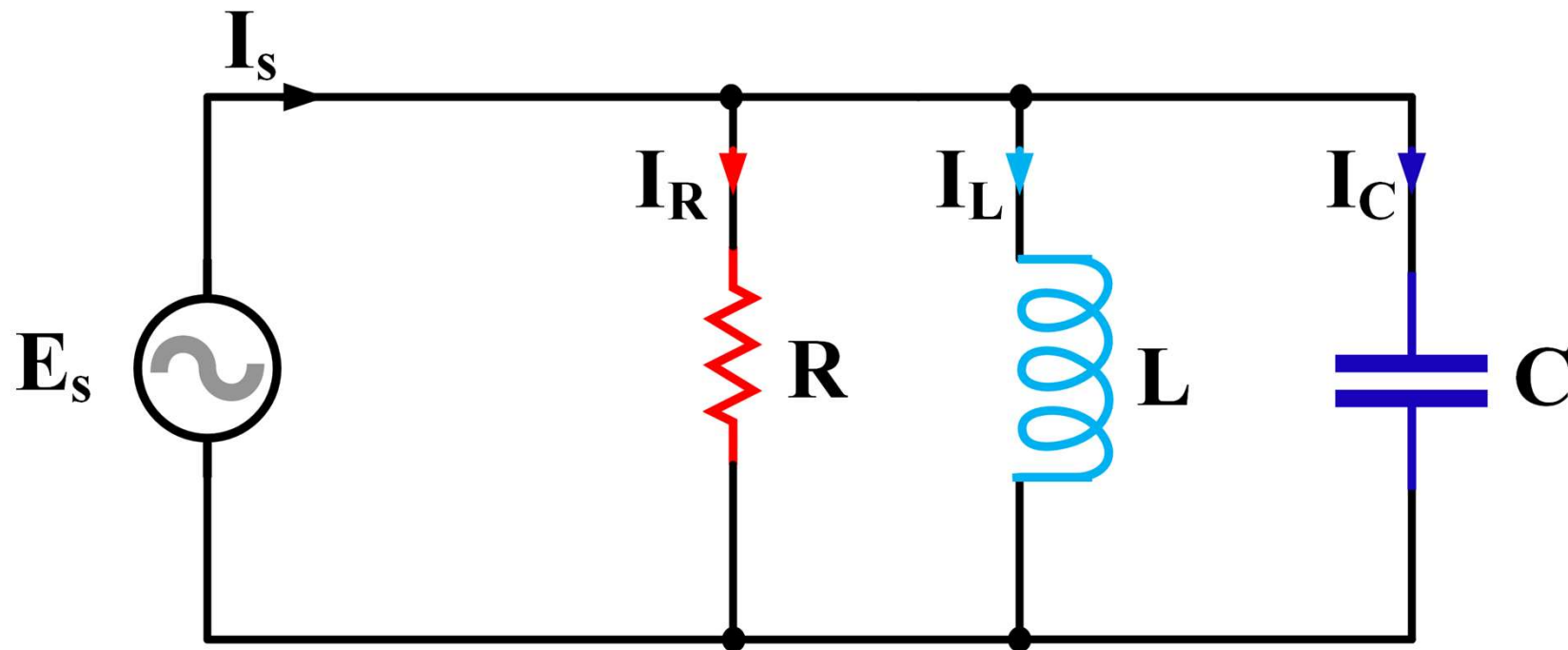
What is the difference between real and reactive power?




Lecture Outcomes

at the end of the lecture, the student must be able to ...

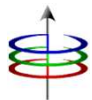
- Formulate Complex Power Equations in AC Circuits
- Solve Problems using Complex Power Equations



POWER IN SINGLE-PHASE AC CIRCUITS

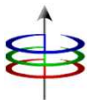

Instantaneous Power

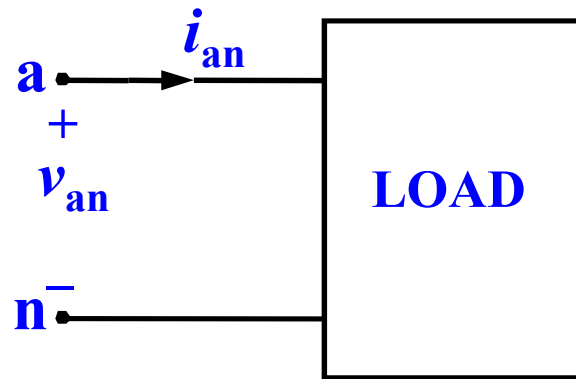


$$v_{an} = V_{\max} \cos(\omega t)$$
$$i_{an} = I_{\max} \cos(\omega t - \theta)$$

The product of voltage and current at any instant of time is called instantaneous power, and is given by,

$$p = v_{an} i_{an} = V_{\max} I_{\max} \cos(\omega t) \cos(\omega t - \theta)$$

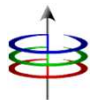A positive p indicates a transfer of energy from the source to the network, while a negative p corresponds to a transfer of energy from the network to the source.



Average Power

Consider the ideal case where the passive network consists only of an inductive element, and apply to the network a sinusoidal voltage of the form,


$$v = V_m \sin \omega t$$

The resulting current will have the form,


$$i = I_m \sin (\omega t - \pi/2)$$

Then the power at any instant of time is

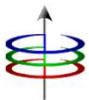
$$p = vi = V_m I_m [\sin (\omega t)][\sin (\omega t - \pi/2)]$$



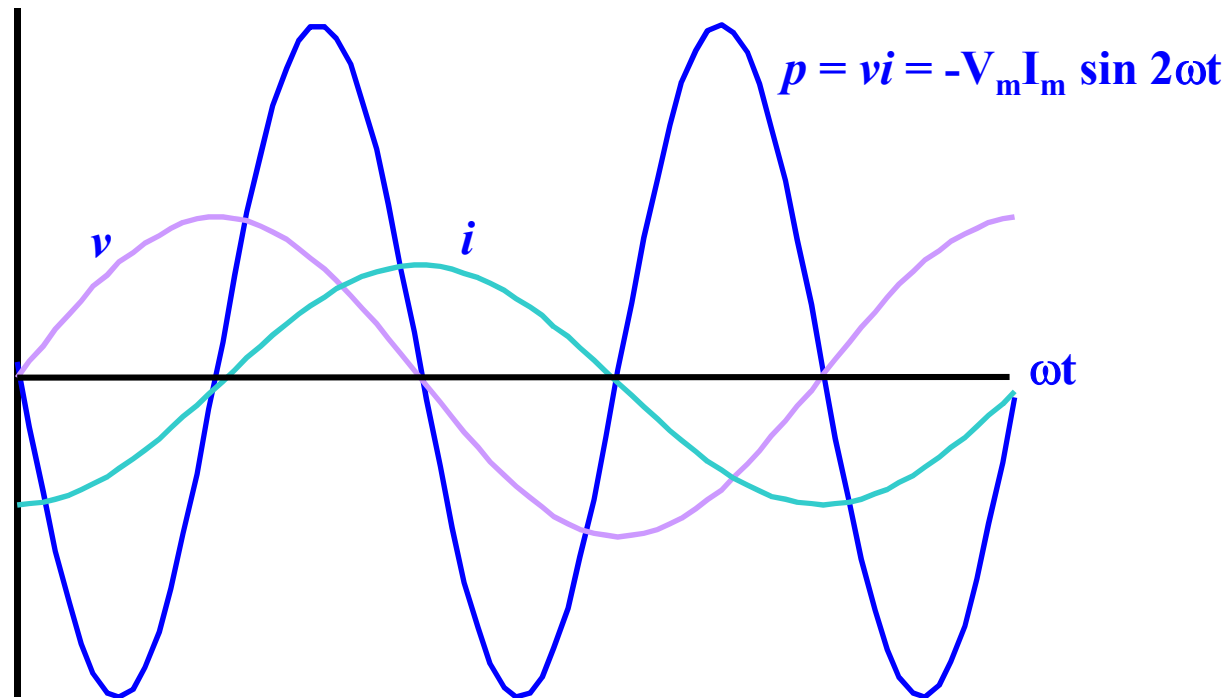
Since $\sin(\omega t - \pi/2) = -\cos \omega t$ and $\sin x \cos x = \sin 2x$, we have,



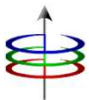When v and i are both positive, the power p is positive and energy is delivered from the source to the inductance. When v and i have opposite sign, the power p is negative and energy is returning from the inductance to the source.



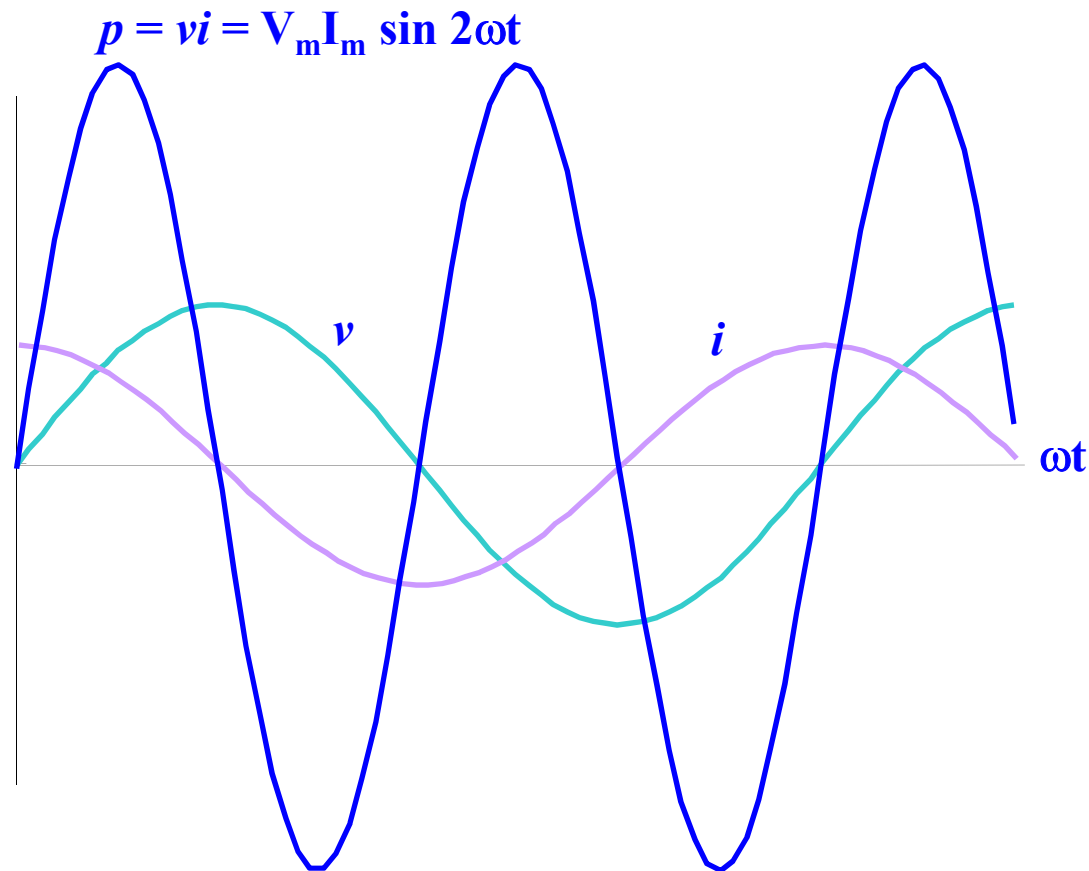In the ideal case of a pure capacitive network, analogous results can also be obtained.





Apply now a voltage $v = V_m \sin \omega t$ to a network containing only resistance. The resulting current is $i = I_m \sin \omega t$, and the corresponding power is,

$$p = vi = V_m I_m \sin^2 \omega t$$

Since $\sin^2 x = \frac{1}{2} (1 - \cos 2x)$, we have,
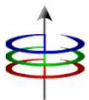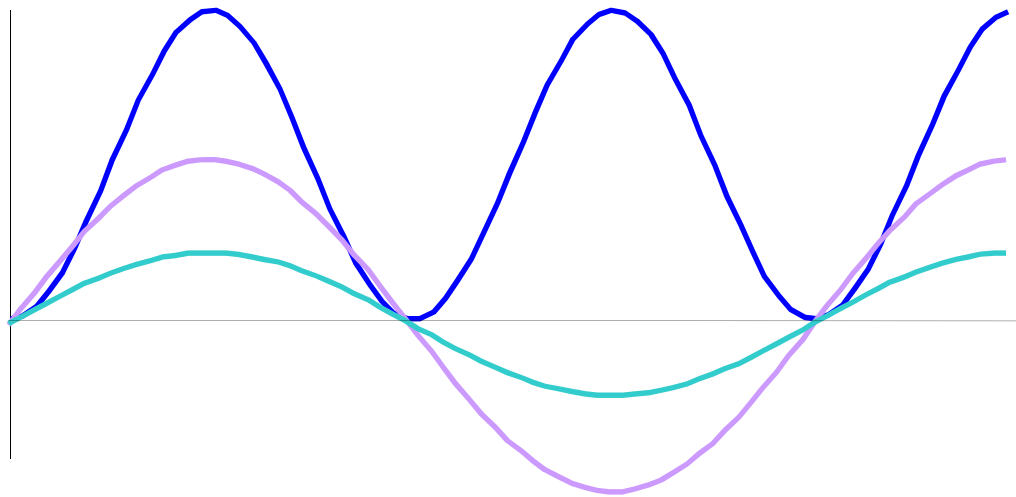
$$p = \frac{1}{2} V_m I_m (1 - \cos 2\omega t)$$



Finally, consider the case of a general passive network. For an applied sinusoidal voltage $v = V_m \sin \omega t$, we have a resulting current $i = I_m \sin (\omega t + \theta)$. The phase angle will be positive or negative depending on the capacitive or inductive character of the network. Then,

$$p = vi = V_m I_m \sin \omega t \sin (\omega t + \theta)$$


Note:

$$\sin \alpha \sin \beta = \frac{1}{2} [\cos (\alpha - \beta) - \cos (\alpha + \beta)]$$

$$\cos (-\alpha) = \cos \alpha$$

Therefore,
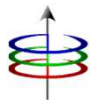
$$p = \frac{1}{2} V_m I_m [\cos \theta - \cos (2\omega t + \theta)]$$



Average Power


The instantaneous power p consists of a sinusoidal term $-\frac{1}{2} V_m I_m \cos(2\omega t + \theta)$ which has an average value of zero and a constant term $\frac{1}{2} V_m I_m \cos \theta$.

Then, the average value of p is,

$$P = \frac{1}{2} V_m I_m \cos \theta = VI \cos \theta$$


where $V = V_m/\sqrt{2}$ and $I = I_m/\sqrt{2}$ are the effective values of the phasors V and I respectively.

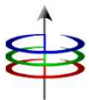The term $\cos \theta$ is called the Power Factor (pf). The angle θ is the angle between V and I , and its value is between $\pm 90^\circ$.




Review

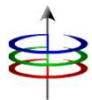- For a general passive network, the power factor depends only on the resistance value of that network. True or False?



Transitioning from Time Domain to Frequency

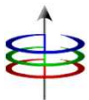
- Phasors makes use of the Power Triangle Concept to simplify power calculations



COMPLEX POWER AND THE POWER TRIANGLE

$$\text{Complex Power} = \text{Voltage} \times \text{Current}^*$$

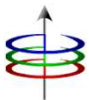- Delivering bulk power (large amount of energy in short time) will require large current.
- Delivering the same bulk power in higher voltage will result in lower current.




Complex Power

The Complex Power (S) can be obtained from the product VI^* . It's real part equals the average power P and it's imaginary part is equal to the reactive power Q .

Consider, $V = |V|\angle\alpha$ and $I = |I|\angle\beta$

$$\begin{aligned} S &= VI^* = |V| e^{j\alpha} |I| e^{-j\beta} \\ &= |V| |I| e^{j(\alpha - \beta)} \\ &= |V| |I| \angle(\alpha - \beta) \\ &= |V| |I| \cos(\alpha - \beta) + j|V| |I| \sin(\alpha - \beta) \\ &= |V| |I| \cos\theta + j|V| |I| \sin\theta \\ &= P + jQ \end{aligned}$$

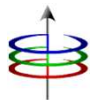

Complex Power


The equations associated with the average, apparent and reactive power can be developed geometrically on a right triangle called the power triangle.

Apparent Power (S) = voltage x current
= VI


Average Power (P) = voltage x in-phase component of current
= VI cos θ

Reactive Power Q = voltage x quadrature comp. of current
= VI sin θ

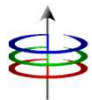
(note: Average Power is also called Real Power or Active Power)



Power Triangle

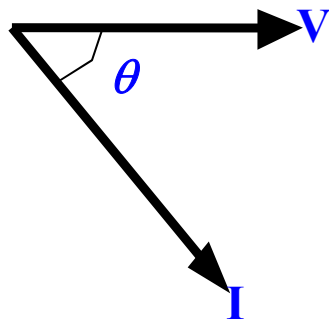


$$P = VI \cos \theta$$

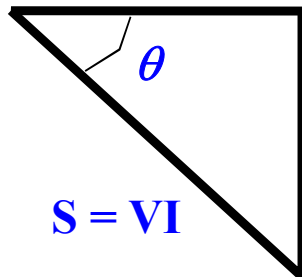


$$Q = VI \sin \theta$$

lagging

Inductive Circuit

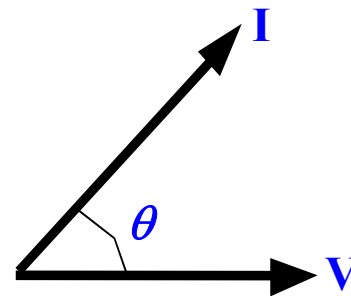

$$S = VI$$

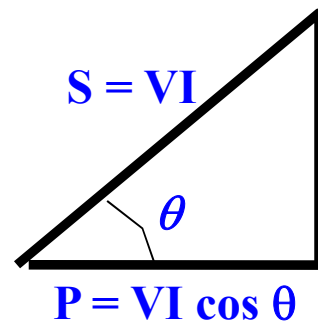

$$Q = VI \sin \theta$$


leading

Capacitive Circuit

Power Factor

$$PF = \frac{\text{Real Power } (P)}{\text{Apparent Power } (S)}$$
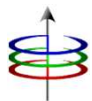
$$= \frac{VI \cos \theta}{VI} = \cos \theta$$




Power Factor


Power Factor

Measure of Efficient Utilization of Power
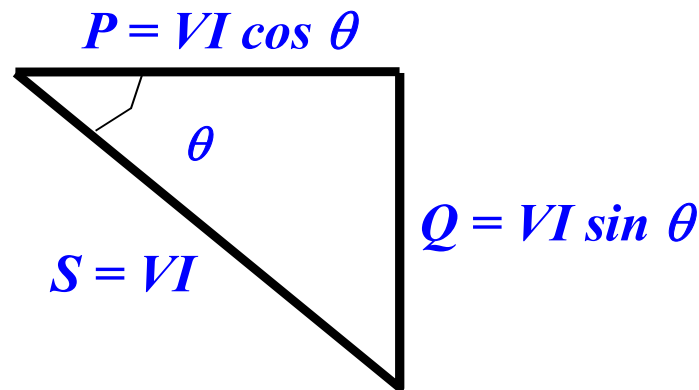
$$PF = \frac{\text{Real Power}(P)}{\text{Apparent Power}(S)} = \frac{VI \cos \theta}{VI}$$



$$PF = \cos \theta$$

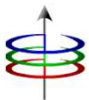

Example

Given a circuit with an impedance $\mathbf{Z} = 3 + j4$ and an applied phasor voltage $\mathbf{V} = 100\angle 30^\circ$, draw the power triangle.

Solution:


$$\mathbf{I} = \mathbf{V}/\mathbf{Z} = (100\angle 30^\circ) / (5\angle 53.1^\circ) = 20\angle -23.1^\circ$$

$$|\mathbf{S}| = \mathbf{VI} = 100(20) = 2000 \text{ VA}$$

$$\mathbf{P} = \mathbf{VI} \cos \theta = 2000 \cos 53.1^\circ = 1200 \text{ W}$$

$$\mathbf{Q} = \mathbf{VI} \sin \theta = 2000 \sin 53.1^\circ = 1600 \text{ VARs lagging}$$
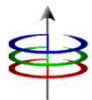
$$\text{pf} = \cos \theta = \cos 53.1^\circ = 0.6 \text{ lagging}$$



Example

Alternative Solution:

$$\begin{aligned} S &= VI^* = (100 \angle 30^\circ)(20 \angle 23.1^\circ) \\ &= 2000 \angle 53.1^\circ \\ &= 1200 + j1600 \end{aligned}$$



We get,

$$P = 1200 \text{ W}$$

$$Q = 1600 \text{ VAr s lagging}$$

$$S = 2000 \text{ VA and}$$

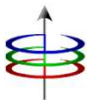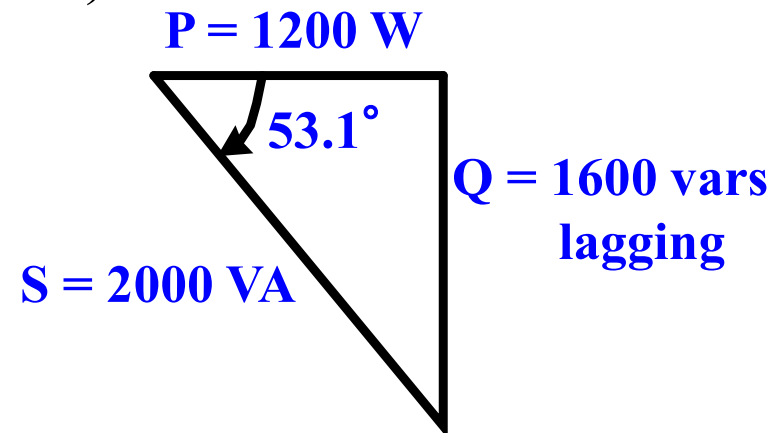
$$\text{pf} = \cos 53.1^\circ = 0.6 \text{ lagging}$$




Concept Test! Again? Yes! Again!

- Work by pairs or individually
- Box your final answer

A small manufacturing plant is located 2 km down a transmission line, which has a series reactance of $0.5 \Omega/\text{km}$. The line resistance is negligible. The line voltage at the plant is $480/\underline{0^\circ}$ V (rms), and the plant consumes 120 kW at 0.85 power factor lagging. Determine the voltage and power factor at the sending end of the transmission line by using (a) a complex power approach and (b) a circuit analysis approach.
any approach.

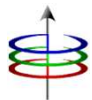

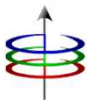- Sending end voltage = $682.4 \angle 21.49^\circ$ V
- Sending end power factor = 0.6 lagging



Summary

- Average Power
- Power Triangle
- Power Factor

