




EEE 51: Second Semester 2017 - 2018

Lecture 20

Feedback Frequency Response

Feedback Frequency Response

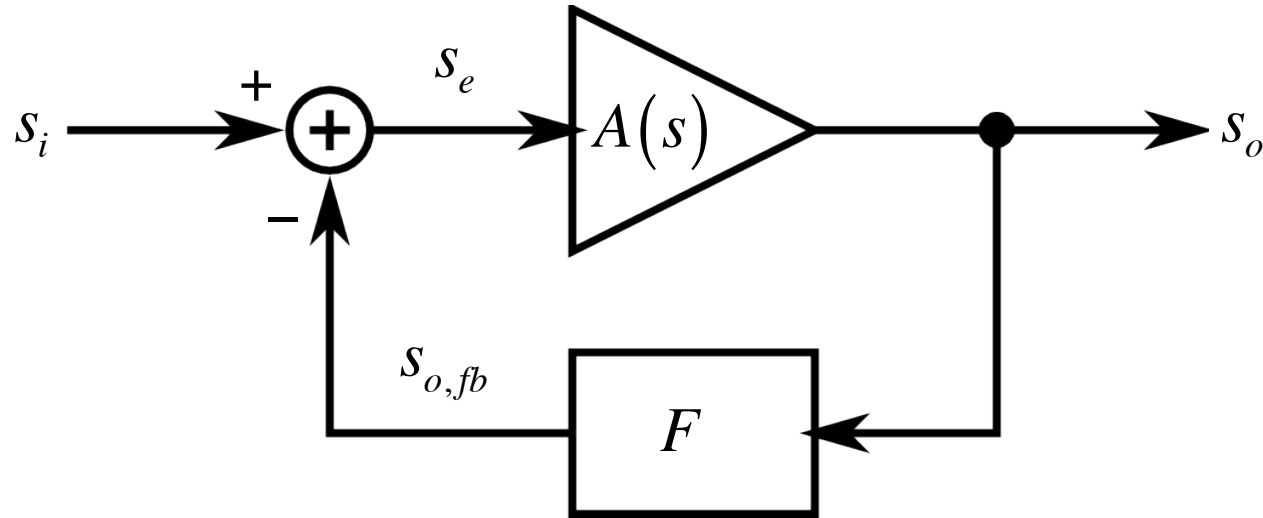


$$A_{CL}(s) = \frac{s_o}{s_i} = ?$$




Loop Gain

$$T(s) = A(s) \cdot F$$

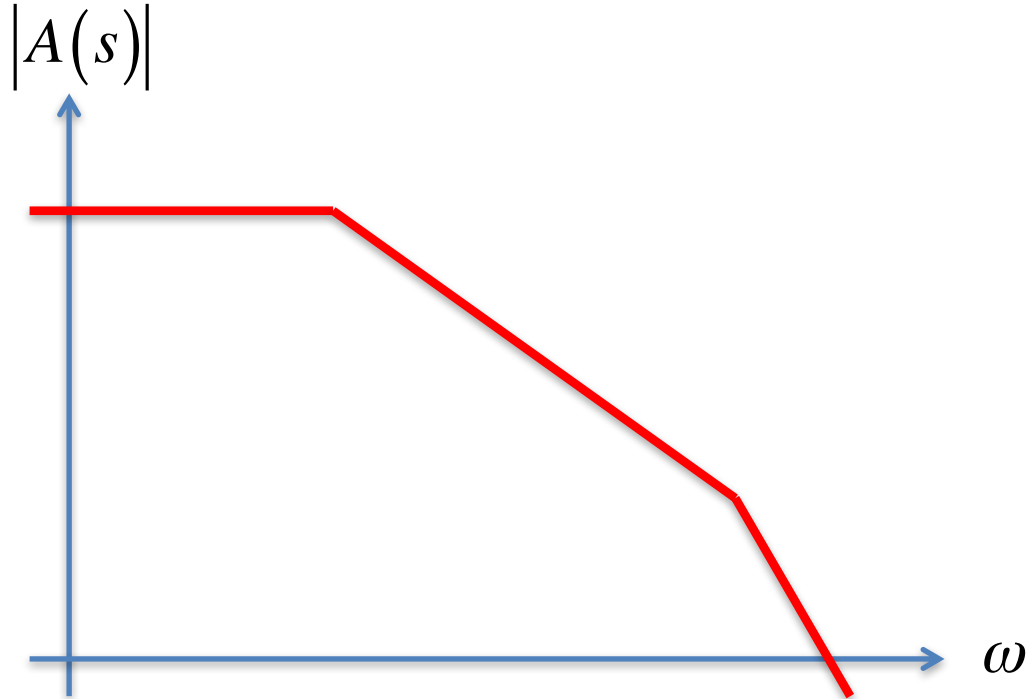


Closed-Loop Gain
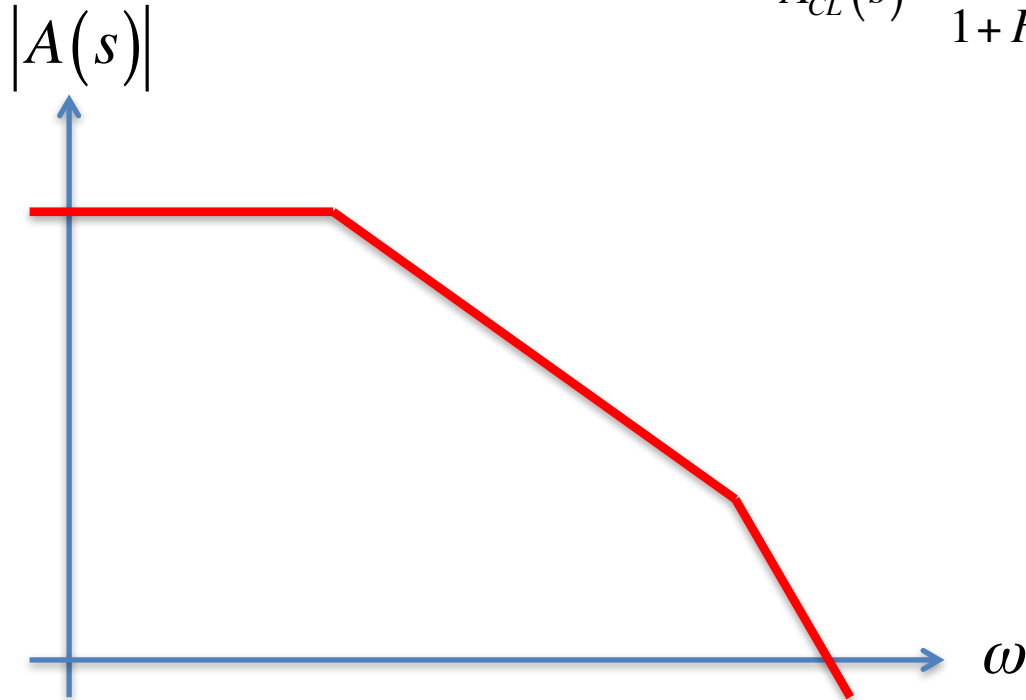
$$A_{CL}(s) = \frac{A(s)}{1 + FA(s)} = \frac{A(s)}{1 + T(s)} = \frac{1}{F} \cdot \frac{T(s)}{1 + T(s)}$$




Frequency Response

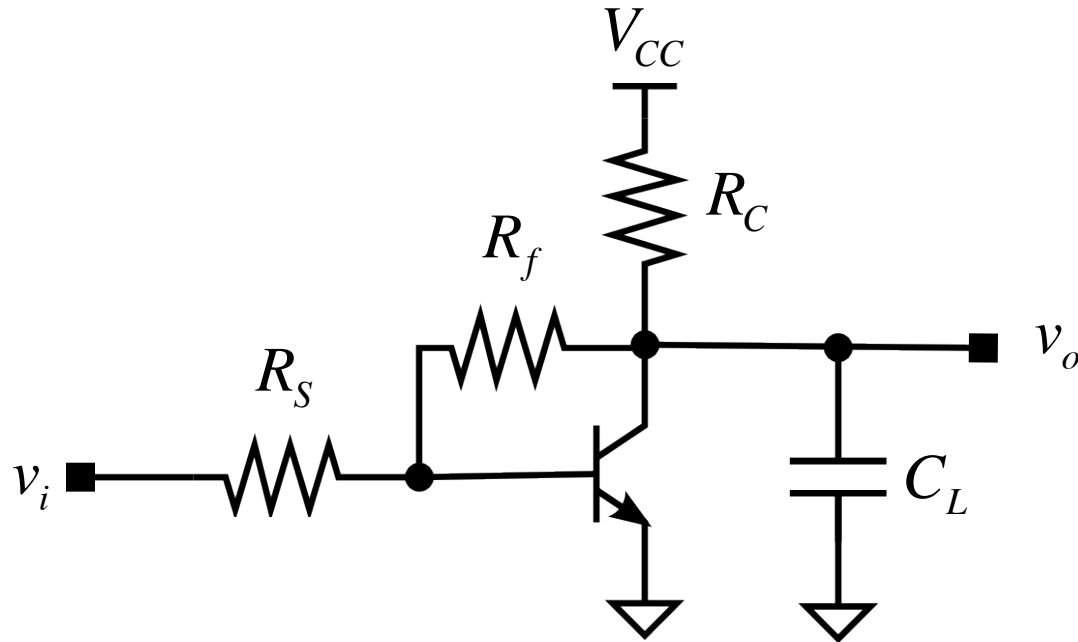


How many poles in the forward gain?
How many poles in the loop gain?



Shunt-Shunt Small Signal Model

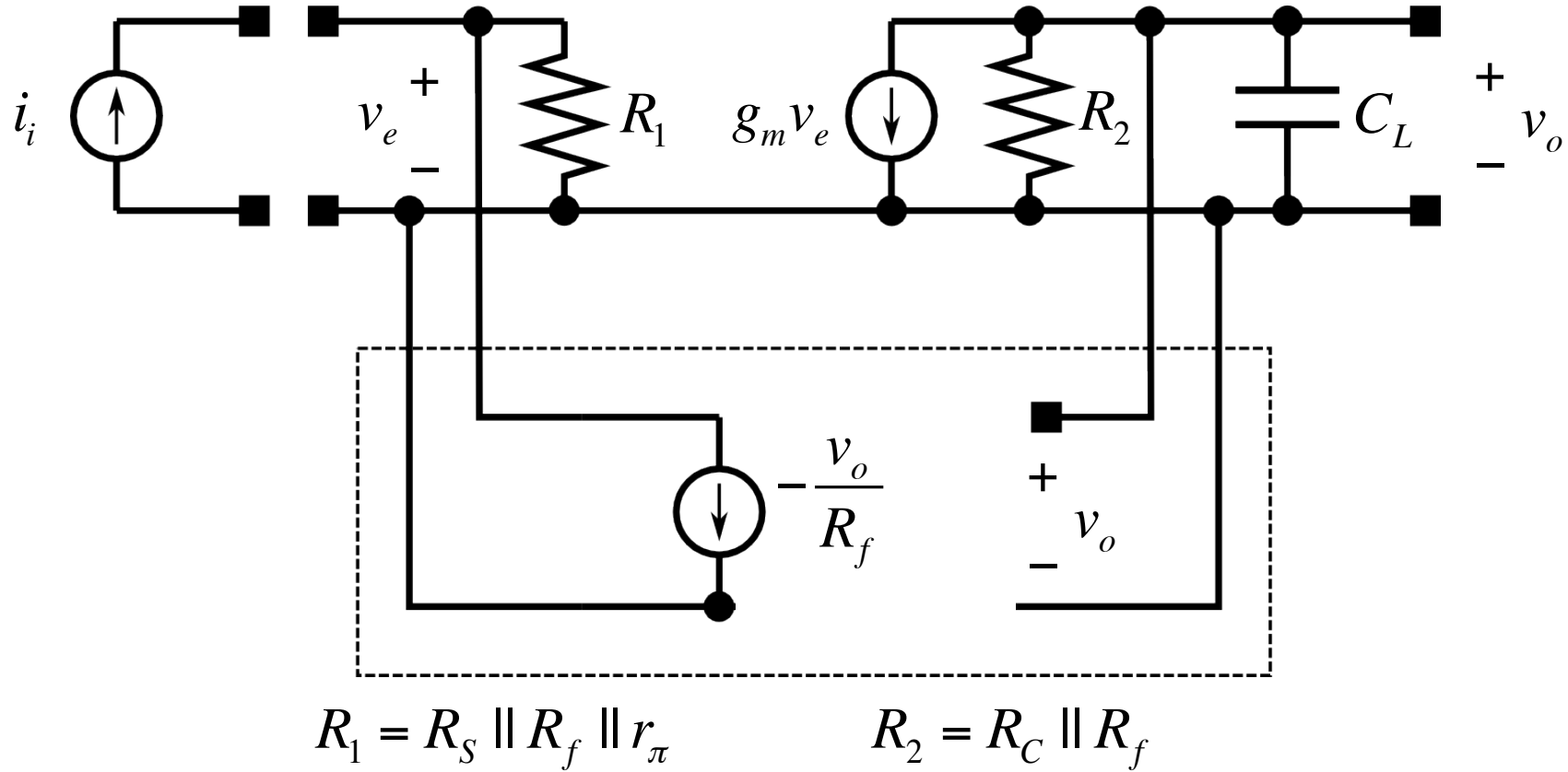

Shunt-Shunt Small Signal Model

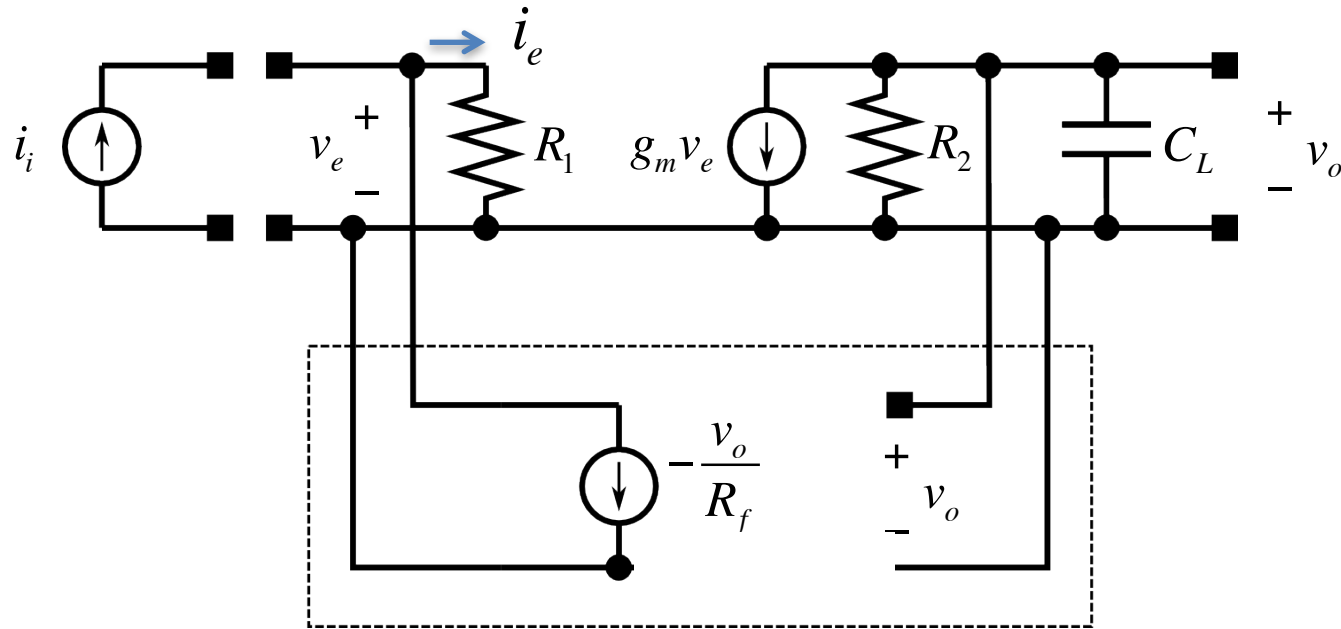

$$\begin{aligned} \frac{v_o}{i_e} &= -\frac{g_m R_1 R_2}{1 + s C_L R_2} \\ &= -\frac{g_m R_1 R_2}{1 + j \frac{\omega}{\omega_p}} \end{aligned}$$

$$f = -\frac{1}{R_f}$$

$$T = \frac{g_m}{R_f} \cdot \frac{R_1 R_2}{1 + s C_L R_2} = \frac{T_0}{1 + j \frac{\omega}{\omega_p}}$$

$$\omega_p = \frac{1}{C_L R_2}$$




Closed Loop Gain

$$\begin{aligned}\frac{v_o}{i_i} &= \frac{1}{f} \cdot \frac{T}{1+T} = -R_f \left[\frac{\frac{g_m R_1 R_2}{R_f} \left(\frac{1}{1+sC_L R_2} \right)}{1 + \frac{g_m R_1 R_2}{R_f} \left(\frac{1}{1+sC_L R_2} \right)} \right] = -R_f \left[\frac{\frac{g_m R_1 R_2}{R_f}}{1 + sC_L R_2 + \frac{g_m R_1 R_2}{R_f}} \right] \\ &= -R_f \frac{\frac{g_m R_1 R_2}{R_f}}{1 + \frac{g_m R_1 R_2}{R_f}} \left[\frac{1}{1 + s \frac{C_L R_2}{1 + \frac{g_m R_1 R_2}{R_f}}} \right] = -R_f \frac{T_0}{1+T_0} \left[\frac{1}{1 + j \frac{\omega}{(1+T_0)\omega_p}} \right]\end{aligned}$$



Closed Loop Magnitude Response

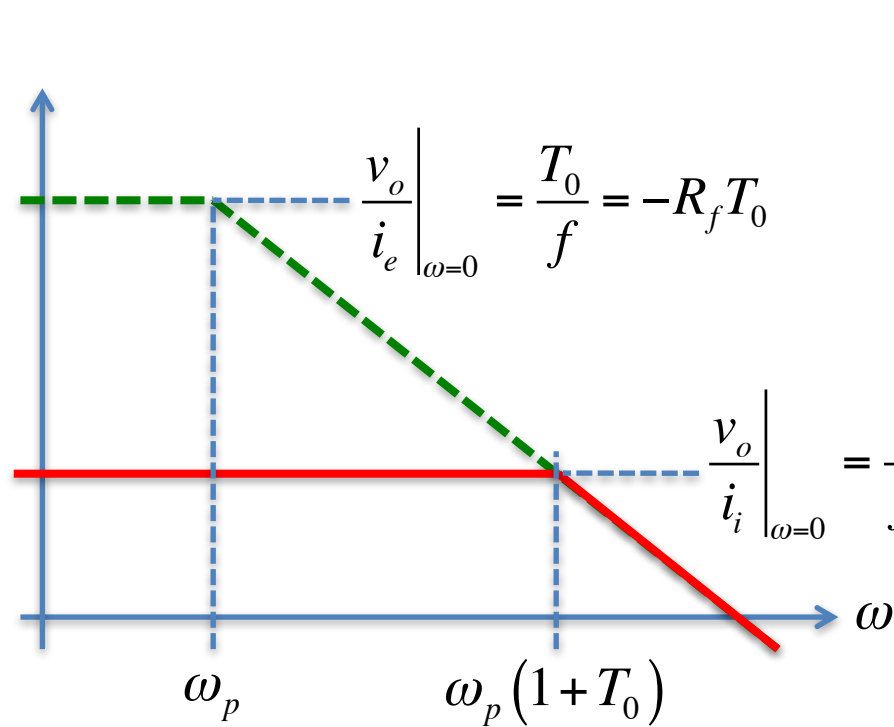


Is this circuit stable?

$$\frac{v_o}{i_i} = -R_f \cdot \frac{T_0}{1+T_0} \left[\frac{1}{1 + j \frac{\omega}{(1+T_0)\omega_p}} \right]$$

$$\frac{v_o}{v_i} = -\frac{R_f}{R_s} \cdot \frac{T_0}{1+T_0} \left[\frac{1}{1 + j \frac{\omega}{(1+T_0)\omega_p}} \right]$$



Feedback and Stability

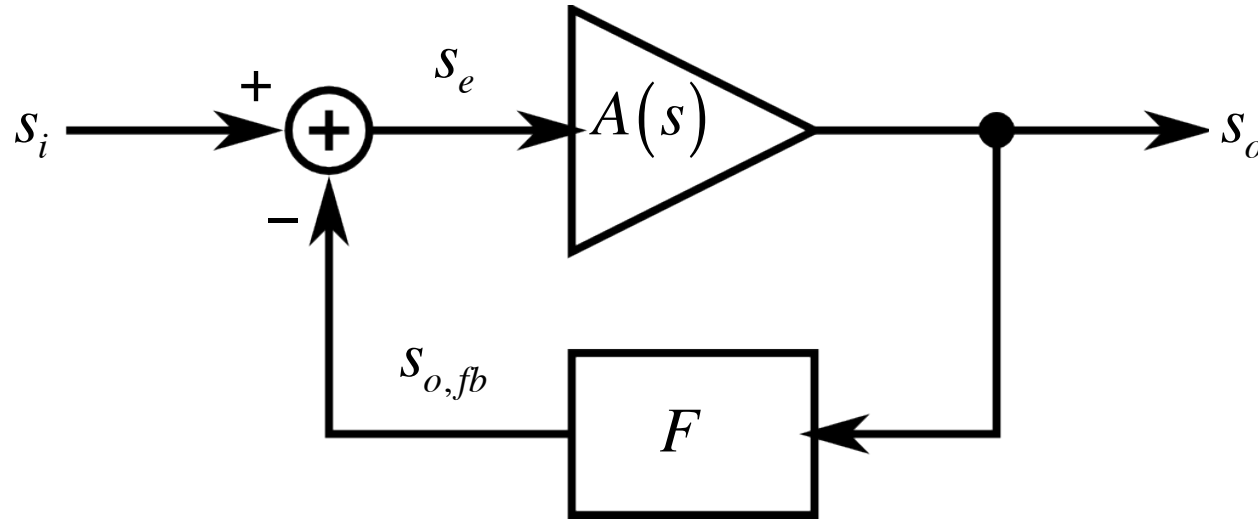


Exponential Stability: For finite input, the output should settle to its final state exponentially




Frequency Response


Right-hand
plane pole:

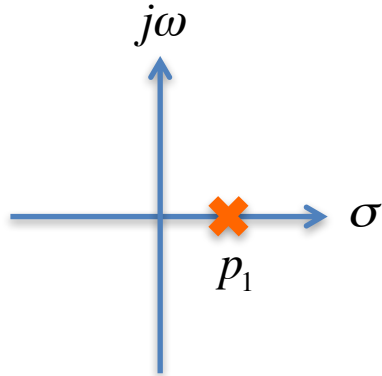


Impulse Response

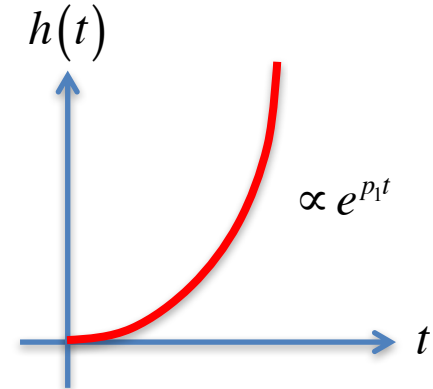


Left-hand
plane pole:

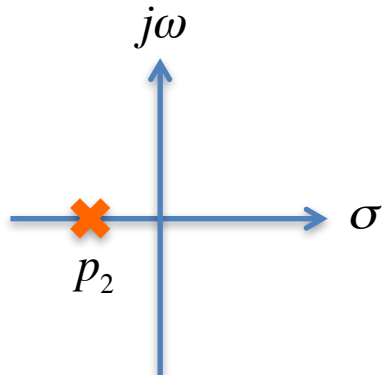

Impulse Response

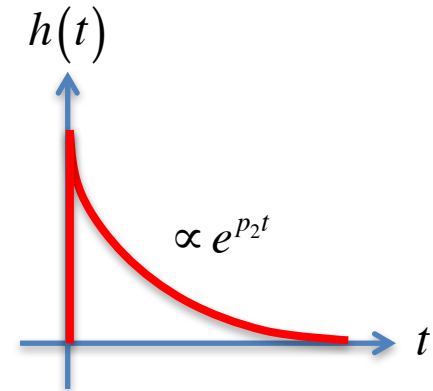

Effect of Frequency Response

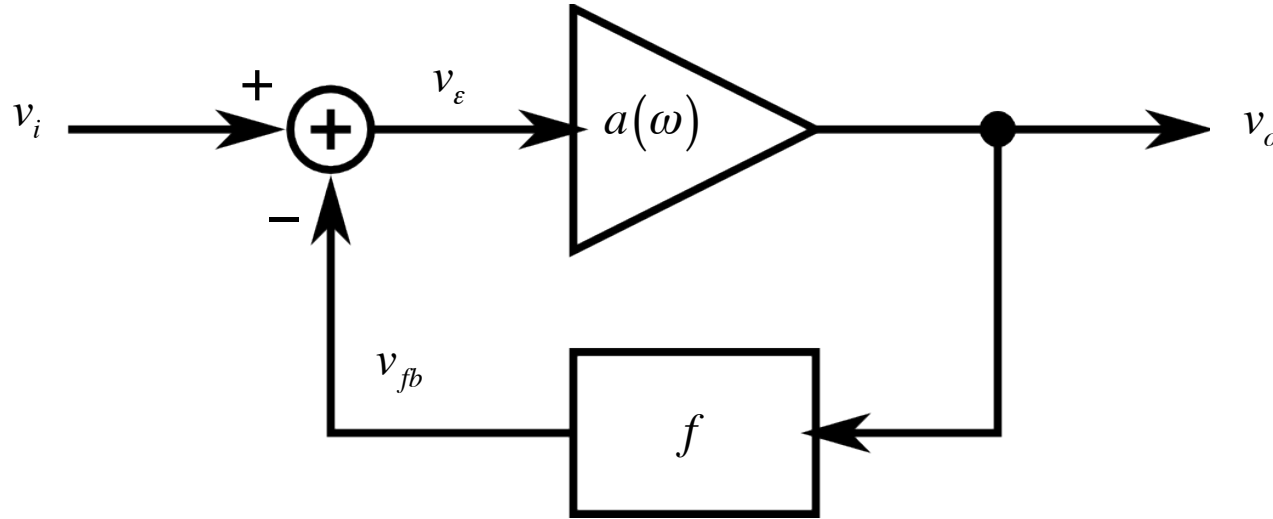

Example:
$$a(\omega) = \frac{a_0}{1 + j \frac{\omega}{\omega_p}}$$



Effect of Frequency Response

Forward gain: $a(\omega) = \frac{a_0}{1 + j\frac{\omega}{\omega_p}}$


Note: $T_0 = a_0 f$

Closed-loop gain: $A_{CL}(\omega) = \frac{1}{f} \cdot \frac{T(\omega)}{1 + T(\omega)} = \frac{\frac{a_0}{1 + j\frac{\omega}{\omega_p}}}{1 + \frac{a_0 f}{1 + j\frac{\omega}{\omega_p}}}$

$$\begin{aligned} &= \frac{a_0}{1 + j\frac{\omega}{\omega_p} + a_0 f} = \frac{a_0}{1 + a_0 f} \cdot \frac{1}{1 + j\frac{\omega}{(1 + a_0 f)\omega_p}} \\ &= \frac{1}{f} \cdot \frac{T_0}{1 + T_0} \cdot \frac{1}{1 + j\frac{\omega}{(1 + T_0)\omega_p}} \end{aligned}$$



Effect of Frequency Response

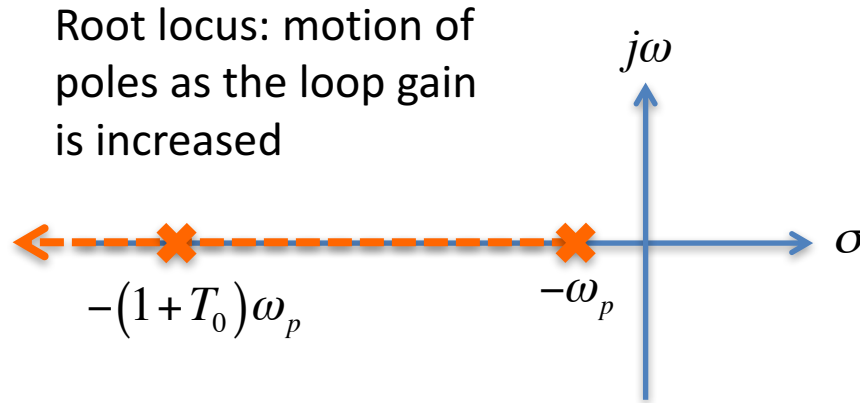

$$a(\omega) = \frac{a_0}{1 + j \frac{\omega}{\omega_p}}$$


$$T(\omega) = a(\omega) \cdot f$$

$$T_0 = a_0 f$$

$$A_{CL}(\omega) = \frac{1}{f} \cdot \frac{T_0}{1+T_0} \cdot \frac{1}{1 + j \frac{\omega}{(1+T_0)\omega_p}}$$



Effect of Frequency Response

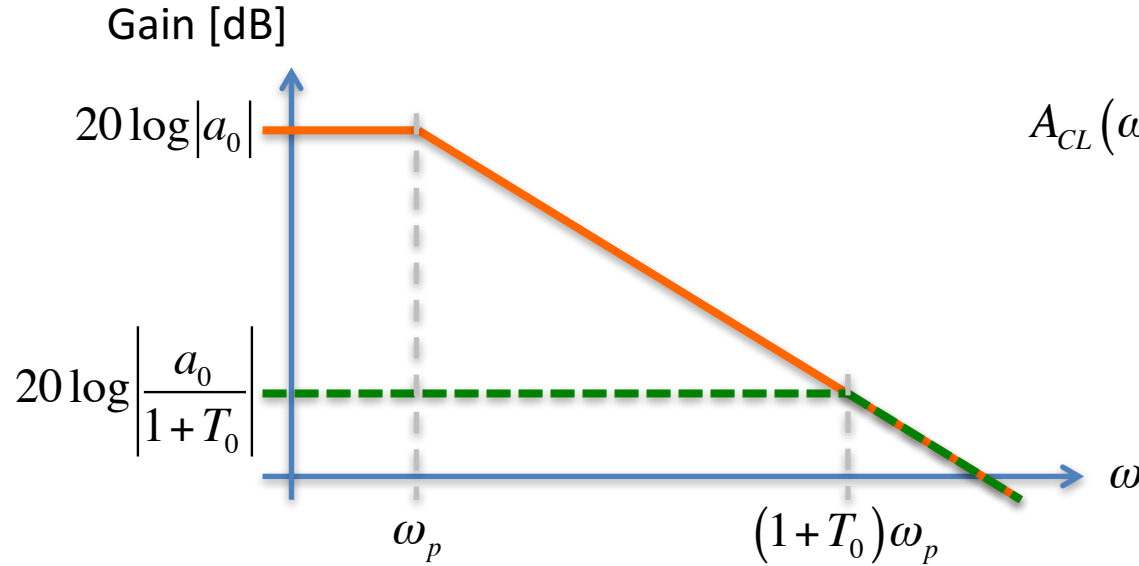

$$A_{CL}(\omega) = \frac{1}{f} \cdot \frac{T_0}{1+T_0} \cdot \frac{1}{1 + j \frac{\omega}{(1+T_0)\omega_p}}$$

$$a(\omega) = \frac{a_0}{1 + j \frac{\omega}{\omega_p}}$$

$$T(\omega) = a(\omega) \cdot f$$

$$T_0 = a_0 f$$

Feedback reduces gain by $(1+T_0)$ and increases the bandwidth by $(1+T_0)$




Effect of Frequency Response

$$a(\omega) = \frac{a_0}{1 + j \frac{\omega}{\omega_p}}$$

$$T_0 = a_0 f$$

$$A_{CL}(\omega) = \frac{1}{f} \cdot \frac{T_0}{1 + T_0} \cdot \frac{1}{1 + j \frac{\omega}{(1 + T_0)\omega_p}}$$

Gain [dB]

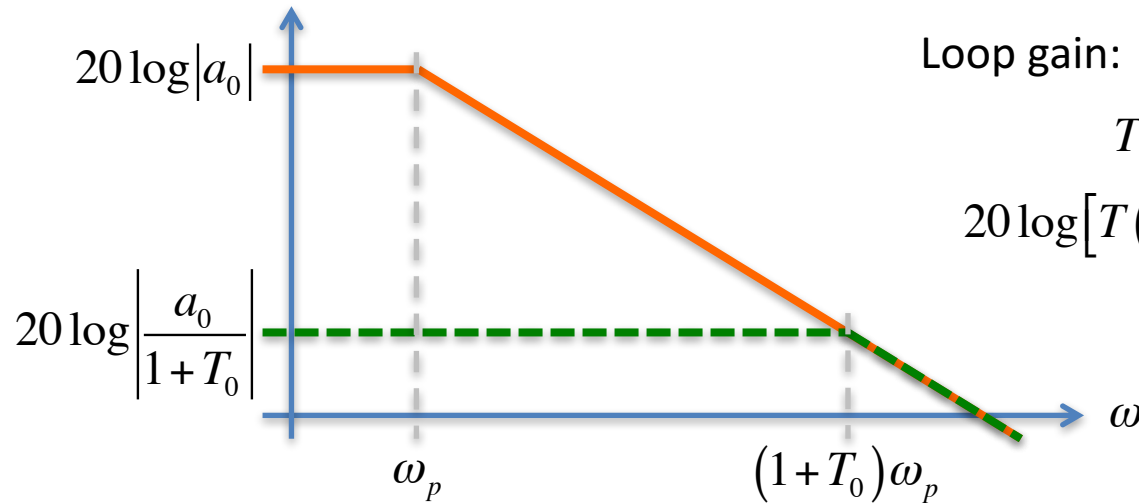

Loop gain:

$$T(\omega) = a(\omega) \cdot f$$

$$20 \log[T(\omega)] = 20 \log[a(\omega) \cdot f]$$


$$= 20 \log[a(\omega)] + 20 \log[f]$$

$$= 20 \log[a(\omega)] - 20 \log\left[\frac{1}{f}\right]$$

Note: $\frac{a_0}{1+T_0} = \frac{1}{f} \frac{T_0}{1+T_0} \approx \frac{1}{f}$



Effect of Frequency Response

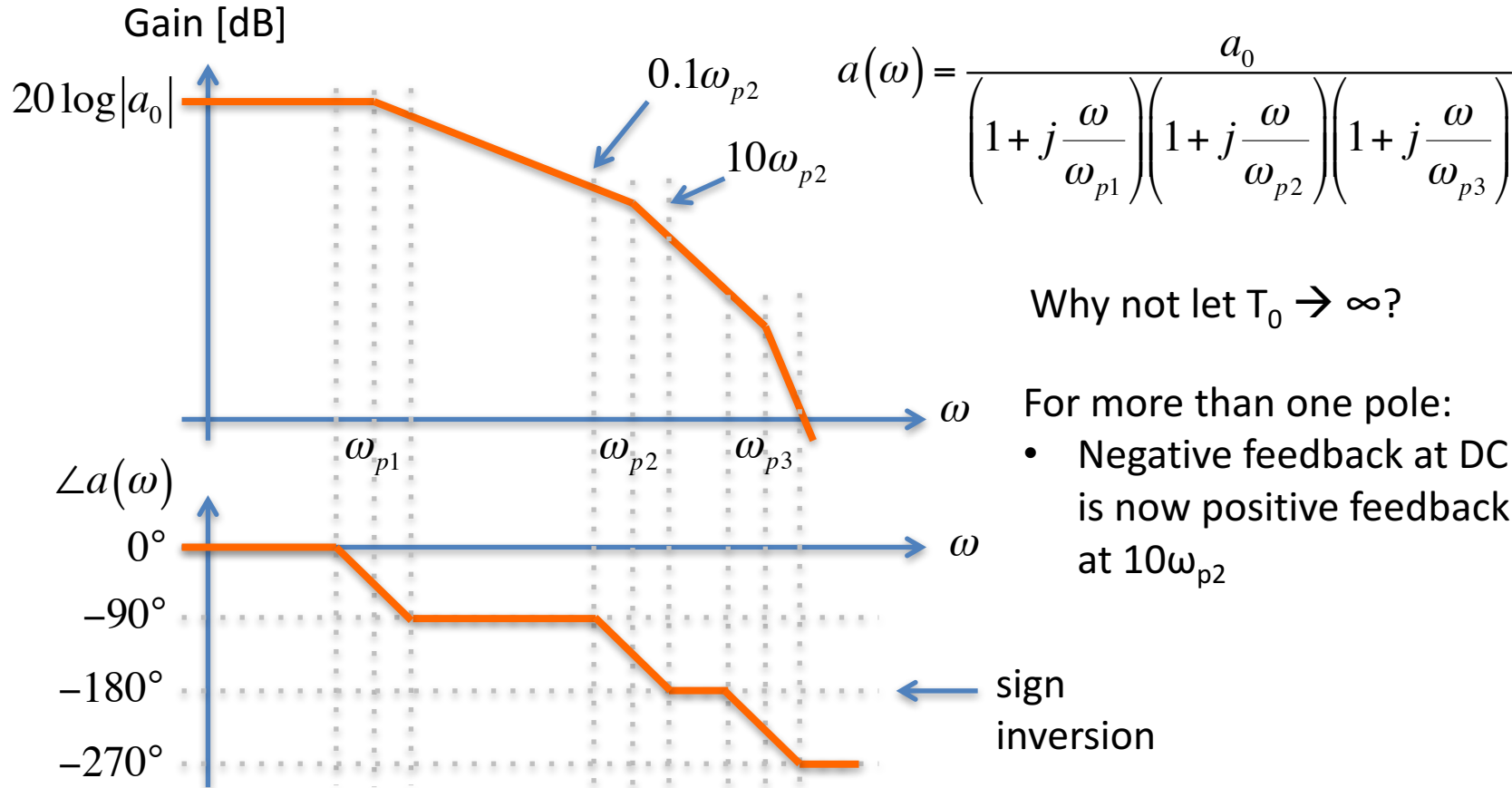


Why not let $T_0 \rightarrow \infty$?

For more than one pole:

- Negative feedback at DC is now positive feedback at $10\omega_{p2}$

Stability

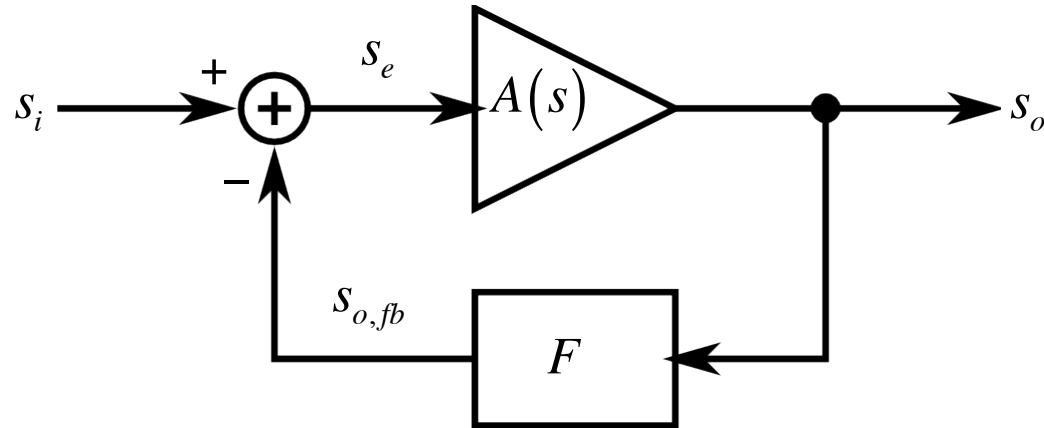

The loop must attenuate all transients when the input has settled.

$$\begin{cases} \angle T < 180^\circ \\ \angle T \geq 180^\circ \Rightarrow |T| < 1 \end{cases}$$



Positive Feedback

Forward gain: $a(\omega) = \frac{a_0}{1 + j\frac{\omega}{\omega_p}}$

Note: $T_0 = a_0 f$


Positive feedback: $A_{CL}(\omega) = \frac{1}{f} \cdot \frac{T(\omega)}{1 - T(\omega)} = \frac{\frac{a_0}{1 + j\frac{\omega}{\omega_p}}}{1 - \frac{a_0 f}{1 + j\frac{\omega}{\omega_p}}}$

$$= \frac{a_0}{1 + j\frac{\omega}{\omega_p} - a_0 f} = \frac{a_0}{1 - a_0 f} \cdot \frac{1}{1 + j\frac{\omega}{(1 - a_0 f)\omega_p}}$$
$$= \frac{1}{f} \cdot \frac{T_0}{1 - T_0} \cdot \frac{1}{1 + j\frac{\omega}{(1 - T_0)\omega_p}}$$



Effect of Frequency Response

Positive feedback:

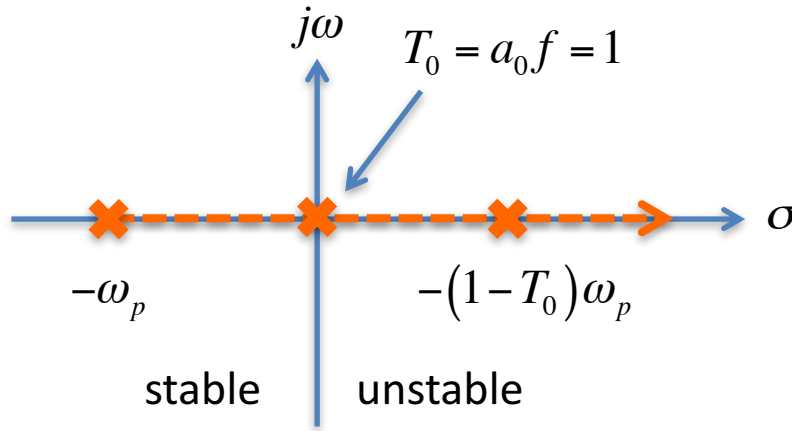

$$a(\omega) = \frac{a_0}{1 + j \frac{\omega}{\omega_p}}$$

$$T(\omega) = a(\omega) \cdot f$$

$$T_0 = a_0 f$$

$$A_{CL}(\omega) = \frac{1}{f} \cdot \frac{T_0}{1 - T_0} \cdot \frac{1}{1 + j \frac{\omega}{(1 - T_0)\omega_p}}$$

Unstable when
 $1 - T_0 < 0$



Effect of Frequency Response

Multi-pole forward gain transfer function: $a(\omega) = \frac{a_0}{\left(1 + j\frac{\omega}{\omega_{p1}}\right)\left(1 + j\frac{\omega}{\omega_{p2}}\right)\dots\left(1 + j\frac{\omega}{\omega_{pn}}\right)}$

Closed loop gain: $A_{CL}(\omega) = \frac{1}{f} \cdot \frac{T(\omega)}{1 + T(\omega)}$

Nyquist Criteria (simple version):

- The circuit is unstable if $|T(j\omega)| > 1$ at the frequency where the phase of $T(j\omega) = -180^\circ$

$$\angle T(j\omega) = \tan^{-1} \left(\frac{\text{Im}\{T(j\omega)\}}{\text{Re}\{T(j\omega)\}} \right)$$




Feedback and Stability

- Metrics
 - Phase margin
 - Gain margin
- Dependent on the loop gain $T(s)$
 - Forward amplifier second (non-dominant) pole
 - Feedback factor
- Worst-case feedback factor?




Effect of Frequency Response

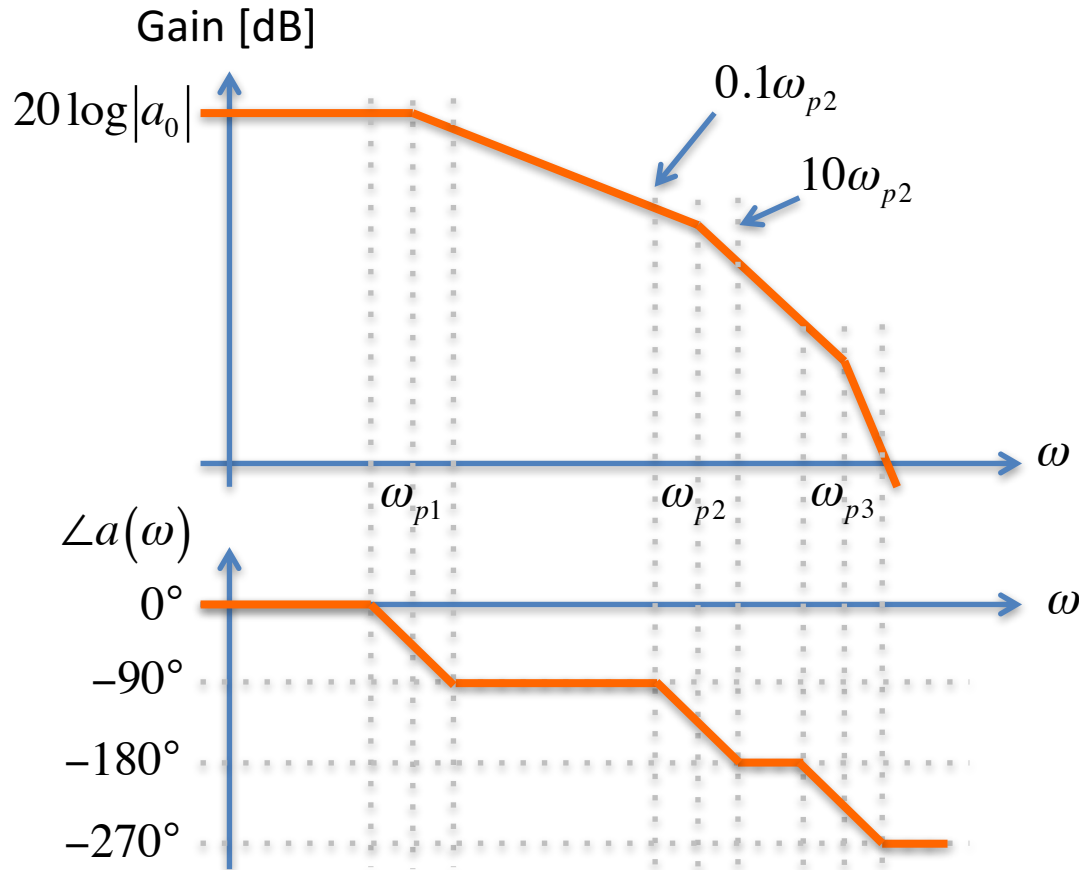

Worst-case feedback factor?




Phase Margin

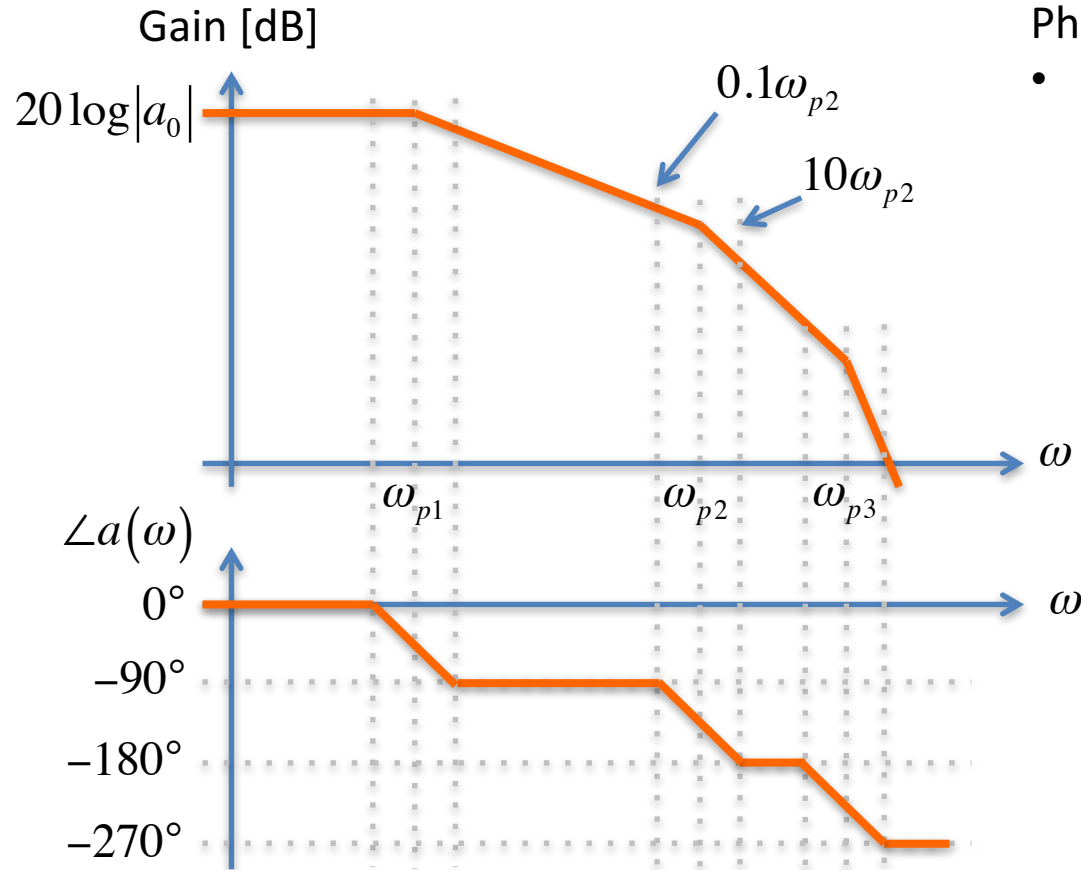


Phase Margin:

- The difference between the actual phase shift and -180° when $|T(j\omega)| = 1$


Phase and Gain Margins

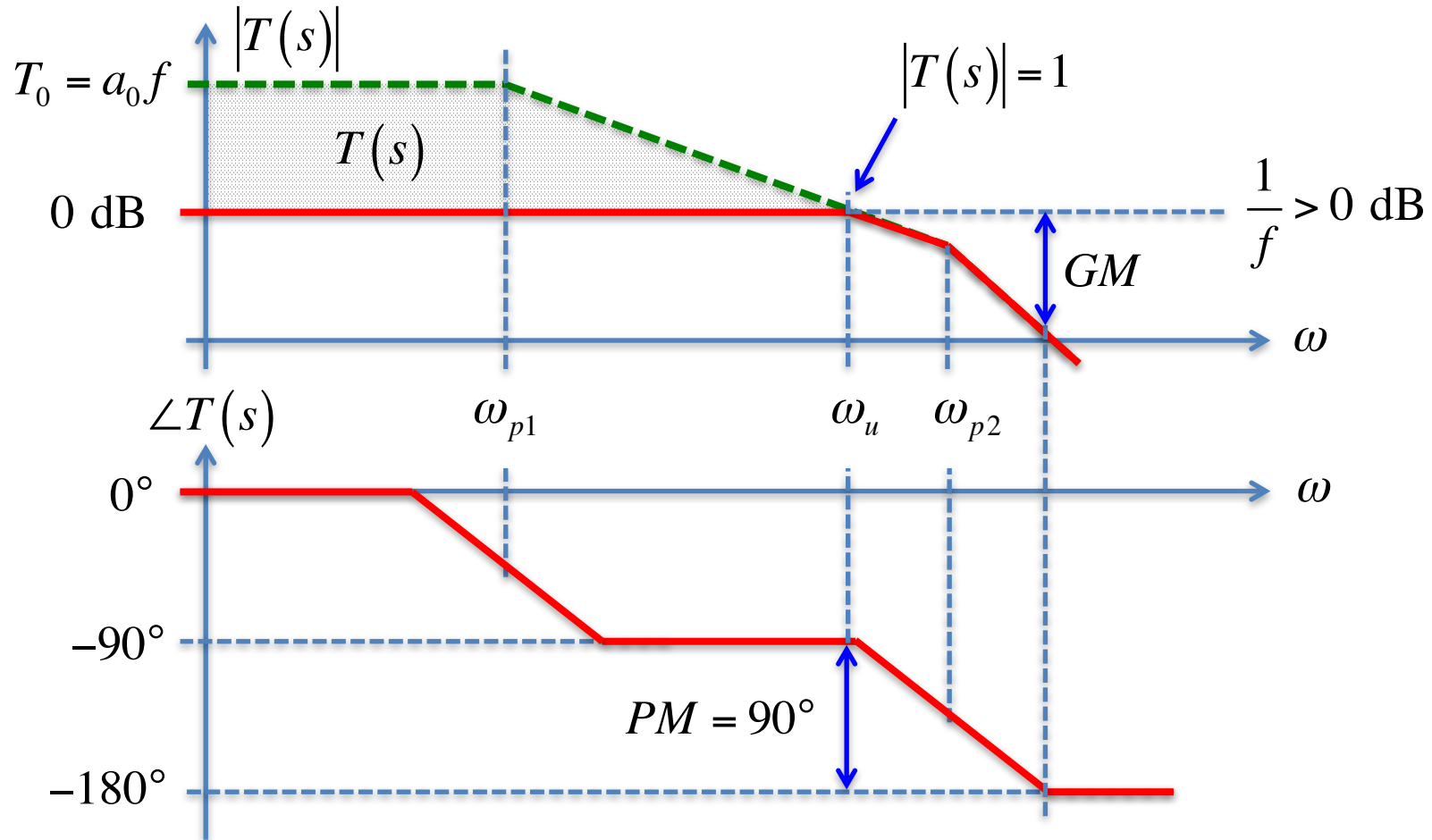


Phase and Gain Margins

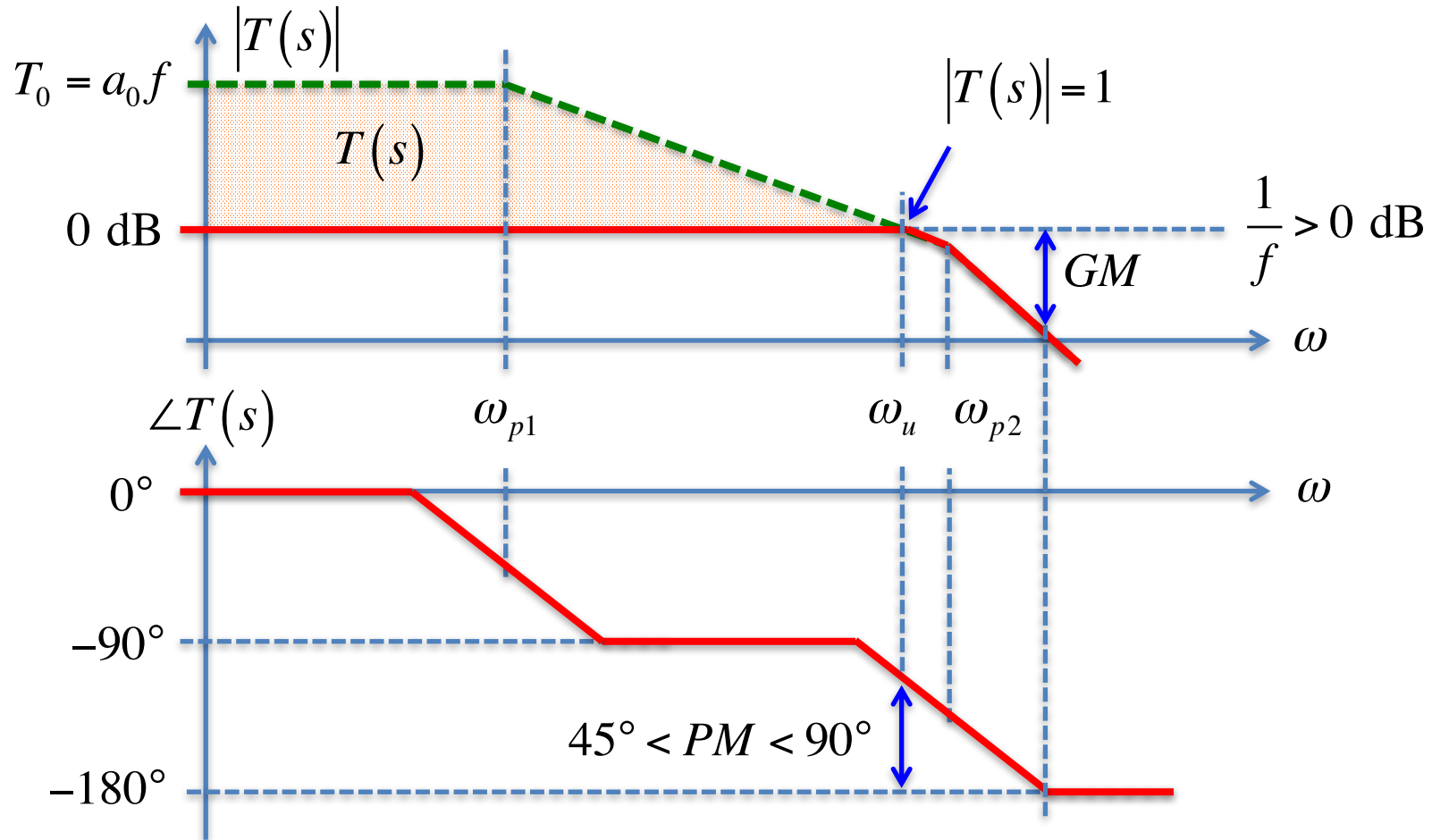

Phase and Gain Margins

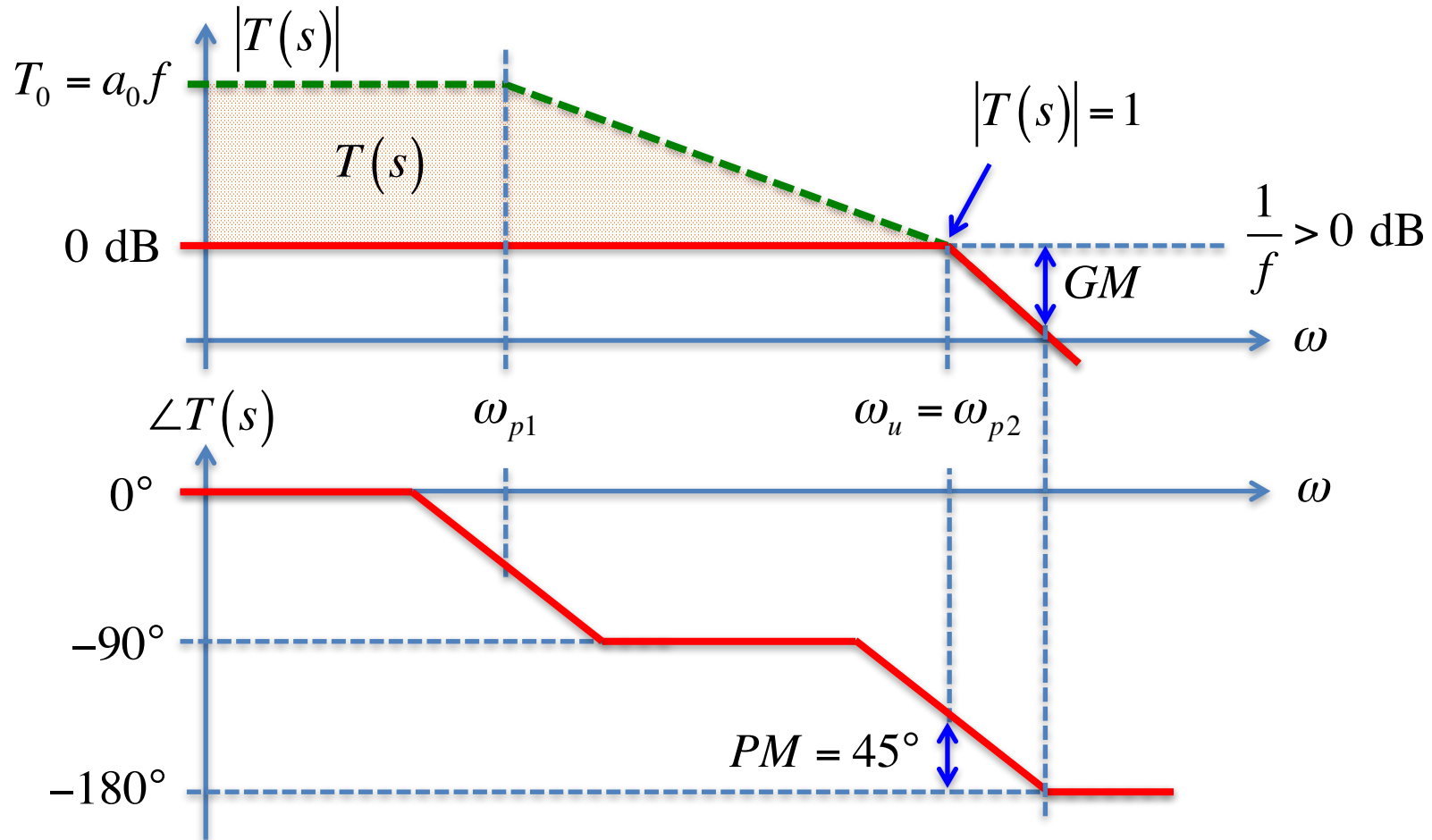

Phase and Gain Margins

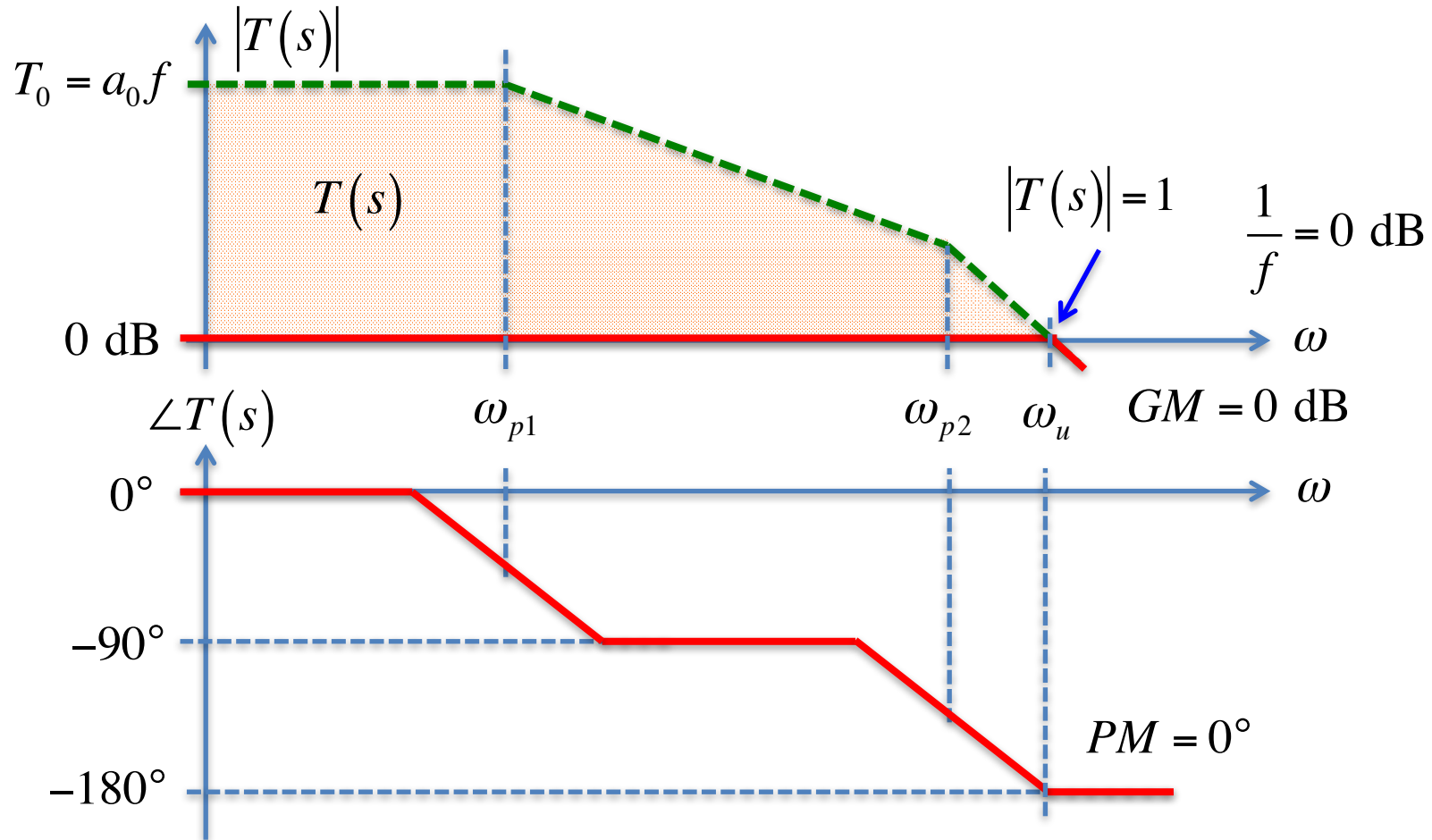

Next Meeting

- Feedback Amplifiers

