




EEE 51: Second Semester 2017 - 2018

Lecture 4

Single-Stage Amplifiers

Today

- Single-Stage Amplifiers

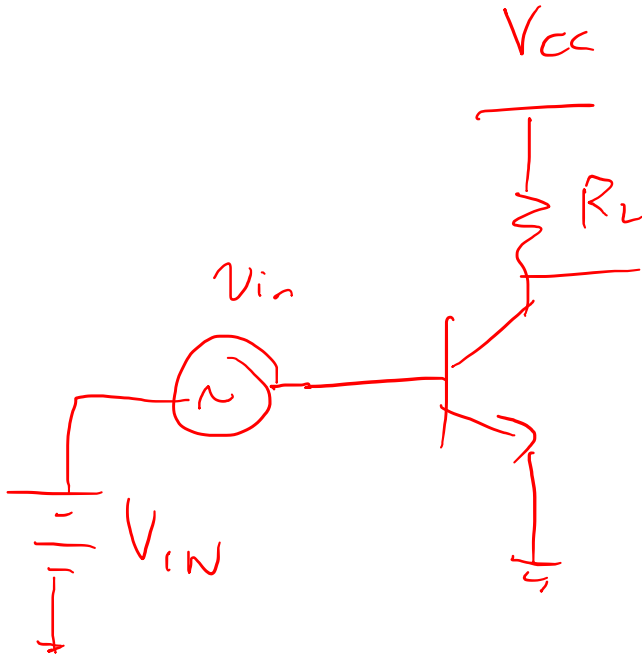


- requires 2 DC sources



A More Practical Common-Emitter Bias Strategy

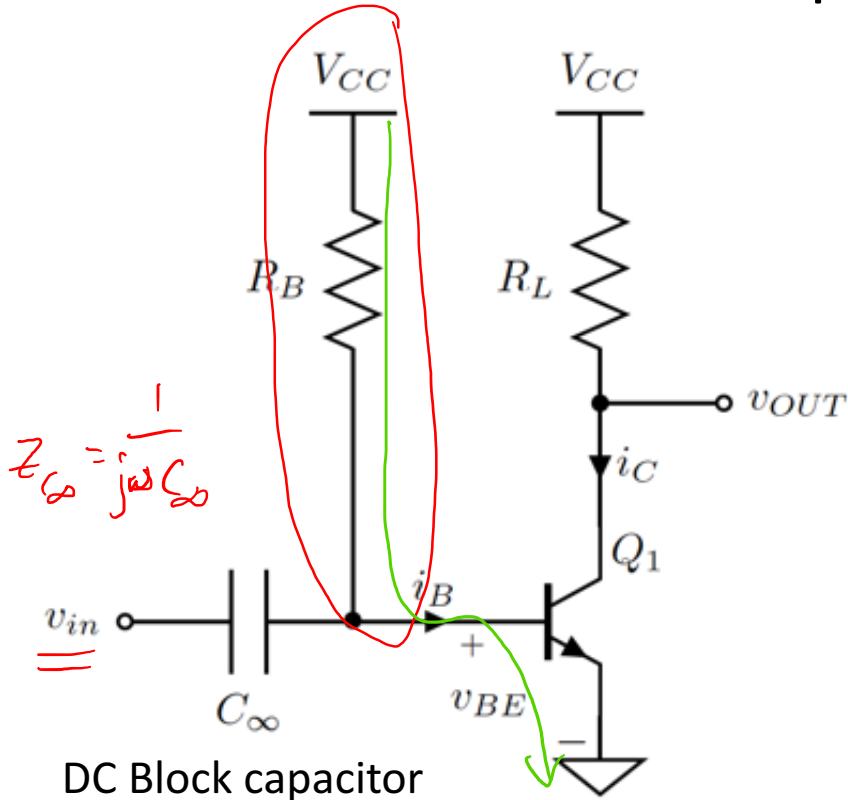- The Fixed-Bias CE Amplifier → only 1 DC source



KVL at the input loop:

$$V_{CC} - I_{B,Q} R_B - V_{BE,Q} = 0$$

$$V_{CC} - \frac{I_{C,Q}}{\beta} R_B - V_T \ln\left(\frac{I_{C,Q}}{I_S}\right) = 0$$

Handwritten notes for KVL:

- $I_C = I_S e^{V_{BE}/V_T}$
- $V_{BE} = V_T \ln\left(\frac{I_C}{I_S}\right)$

Non-linear! How do we solve this?

- Graphical
- Numerical / iterative
 - put those EEE 11/13 skills to good use ☺



Iterative Solution


$$V_{CC} = 5V$$

$$\beta = 100$$

$$R_B = 500k\Omega$$

$$V_T = 26mV$$

$$I_S = 0.2fA$$

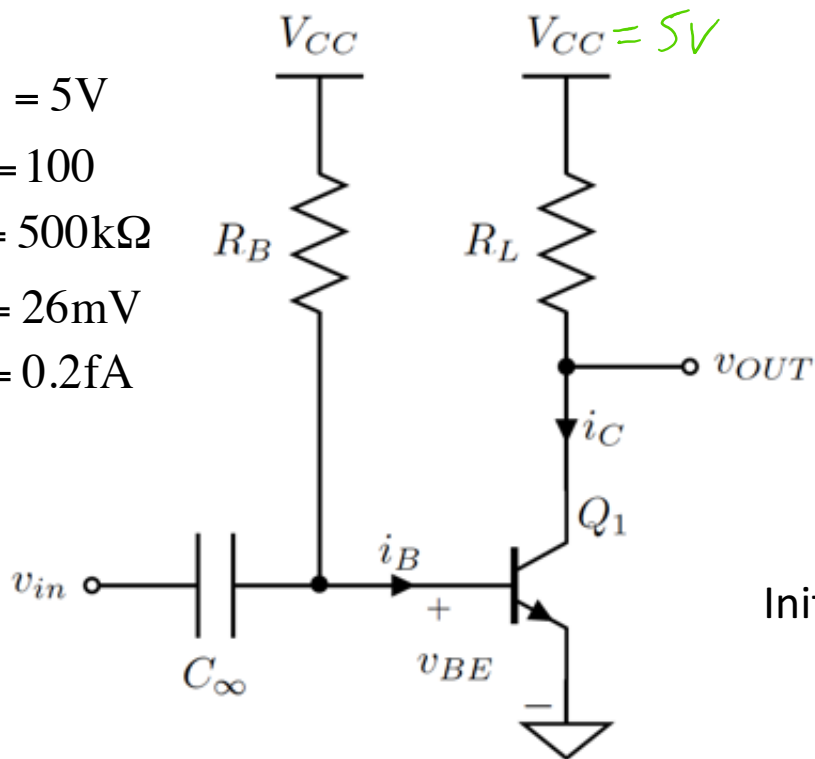

$$V_{CC} - \frac{I_{C,Q}^A}{\beta} R_B - V_T \ln\left(\frac{I_{C,Q}^B}{I_S}\right) = 0$$

Rewrite:

$$I_{C,Q}^A = \frac{\beta}{R_B} \left[V_{CC} - V_T \ln\left(\frac{I_{C,Q}^B}{I_S}\right) \right]$$


Initial guess

$I_{C,Q}^B$	$I_{C,Q}^A$
1mA	0.8479mA
0.8479mA	0.8488mA
0.8488mA	0.8488mA

$$I_{C,Q} = 848.8\mu A$$



Recall: Basic Common-Emitter Amplifier

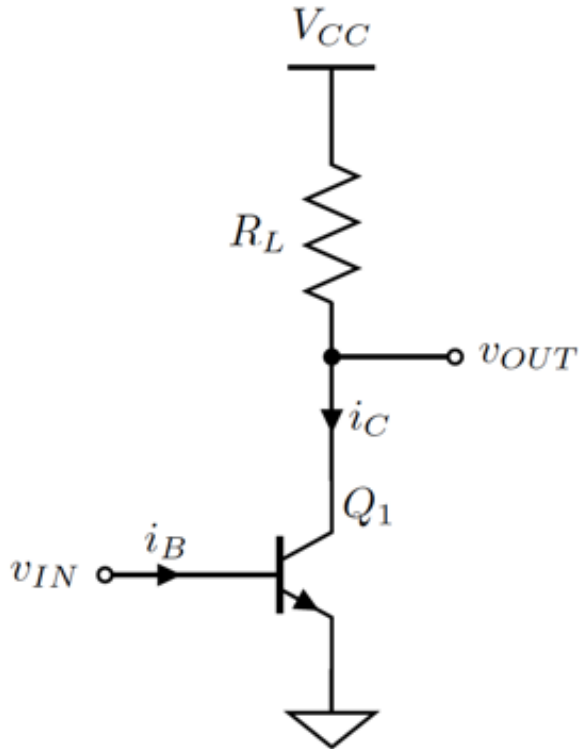

	V_{IN} [mV]	$I_{C,Q}$ [mA]	V_{OUT} [V]	A_v [$\frac{V}{V}$]
Point A	672.5	1	4.5	-21.7
Point B	709.5	5	2.5	-108.7
Point C	718.9	7.5	1.25	-163.0


For a wide range of currents,

$$V_{BE} \approx 0.7V$$

What if we use this approximation?



Fixed-Bias Common-Emitter Amplifier Bias

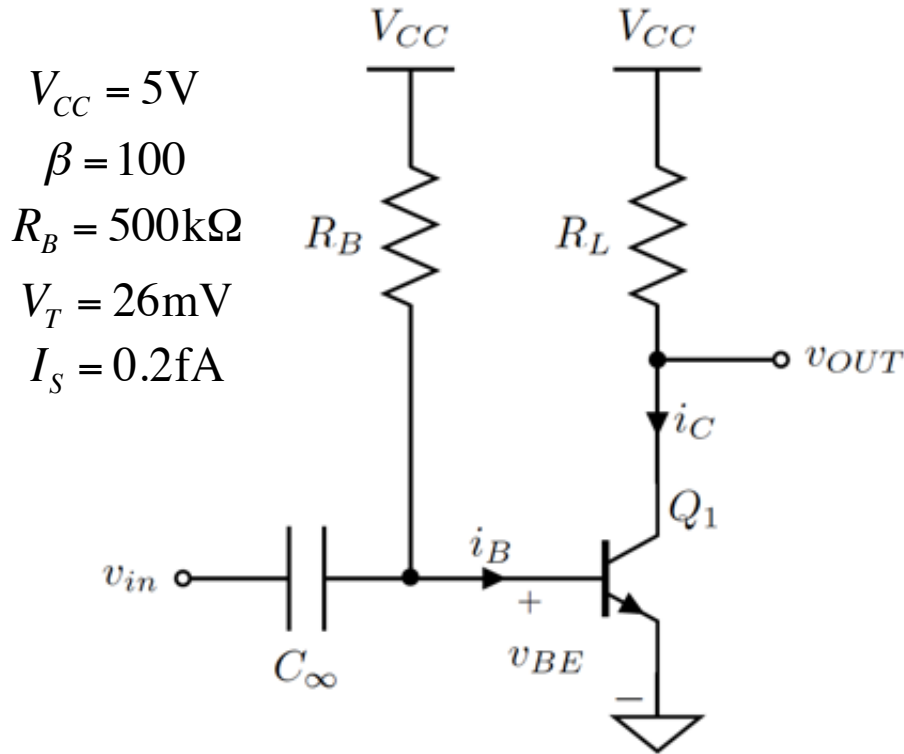

$$V_{CC} - \frac{I_{C,Q}}{\beta} R_B - V_T \ln\left(\frac{I_{C,Q}}{I_S}\right) = 0$$

$\leftarrow V_{BE}$

$$V_{CC} - \frac{I_{C,Q}}{\beta} R_B - \underline{0.7V} = 0$$

Thus,

$$I_{C,Q} = \beta \cdot \frac{V_{CC} - 0.7V}{R_B}$$

$$= 860\mu A$$


Iterative solution:

$$I_{C,Q} = 848.8\mu A \quad (\text{error less than } 2\%)$$


Is this approximation good enough? \rightarrow It depends on the application!



Small Signal Model

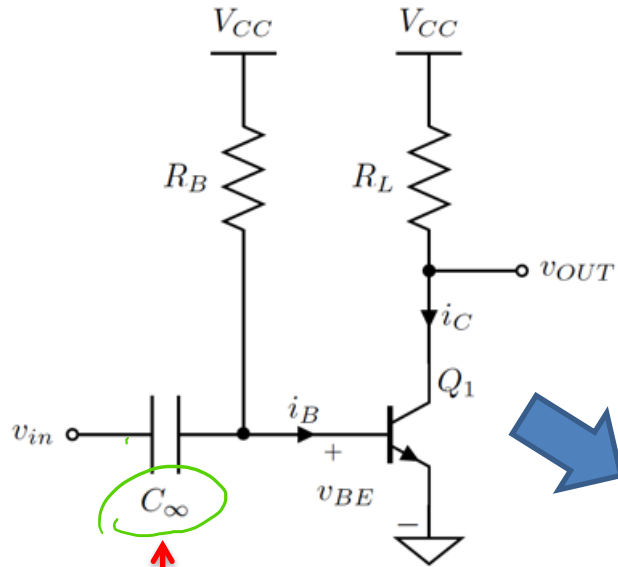

Open: at DC
Short: everywhere else

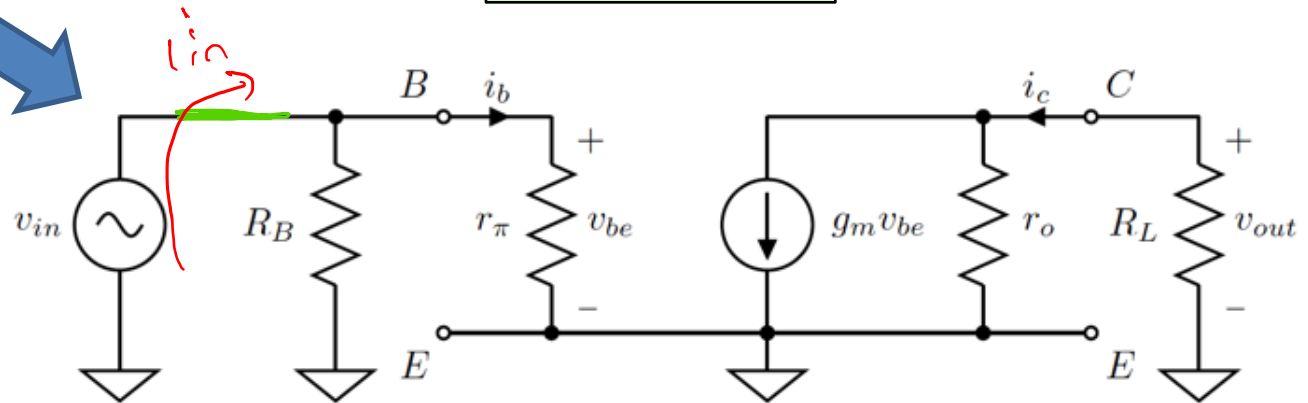

$$\begin{aligned}
 G_m &= g_m \\
 R_i &= r_\pi \parallel R_B \\
 R_o &= r_o \parallel R_L \\
 A_v &= -G_m R_o \\
 &= -g_m (r_o \parallel R_L)
 \end{aligned}$$


Input resistance changes

Common-Emitter → refers to the small signal model



Fixed-Bias Limitations

- β -variations

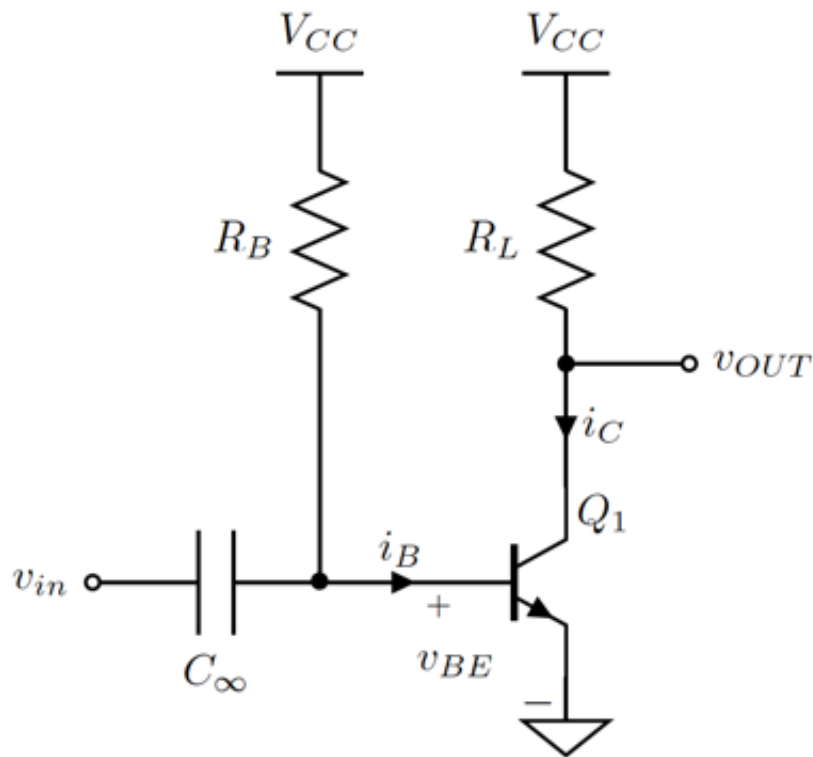

- Due to manufacturing imperfections

$$\beta = \beta_{\text{nominal}} \pm 50\%$$

- β doubles for every 80°C rise in temp

$$V_{CC} - I_B R_B - V_{BE} = 0$$


$$\text{Recall: } I_{C,Q} = \beta \cdot \frac{V_{CC} - 0.7\text{V}}{R_B}$$

$I_{C,Q}$ can vary by a lot \rightarrow due to β variations!

Can we do better than this?



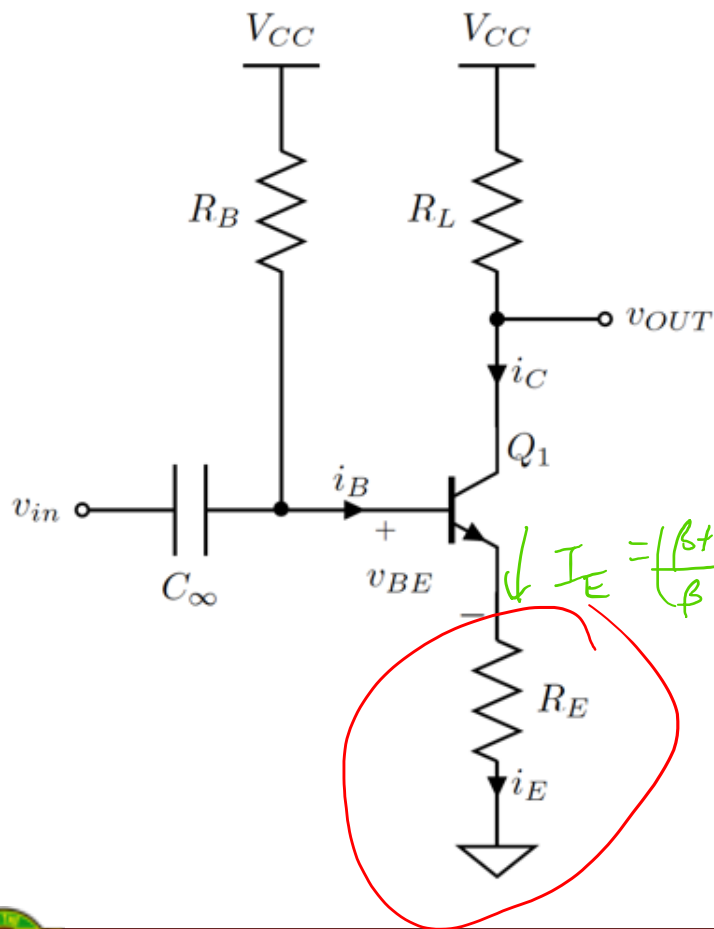Emitter-Degenerated Common-Emitter Amplifier



KVL at the input loop:

$$V_{CC} - I_{B,Q} R_B - V_{BE,Q} - I_{E,Q} R_E = 0$$

$$V_{CC} - \frac{I_{C,Q}}{\beta} R_B - 0.7V - I_{C,Q} \left(1 + \frac{1}{\beta}\right) R_E = 0$$

Solving for the collector current:

$$I_{C,Q} = \beta \frac{V_{CC} - 0.7V}{R_B + (\beta + 1) R_E}$$

Is this bias scheme better?

For $\beta \rightarrow \infty$:

$$I_{C,Q} \approx \frac{V_{CC} - 0.7V}{R_E}$$

Independent of β



Formalizing Parameter Effects

Define Sensitivity of X to Y as $S_Y^X = \frac{\partial X}{\partial Y} \Rightarrow \Delta X = S_Y^X \cdot \Delta Y = \frac{\partial X}{\partial Y} \cdot \Delta Y$

Fixed-Bias

$$\rightarrow I_{C,Q} = \beta \cdot \frac{V_{CC} - 0.7V}{R_B}$$

$$S_\beta^{I_{C,Q}} = \frac{\partial I_{C,Q}}{\partial \beta} = \frac{\partial}{\partial \beta} \left(\beta \cdot \frac{V_{CC} - 0.7V}{R_B} \right) \\ = \frac{V_{CC} - 0.7V}{R_B}$$

Constant sensitivity

Decreasing sensitivity
as β increases

Emitter-Degeneration

$$I_{C,Q} = \beta \frac{V_{CC} - 0.7V}{R_B + (\beta + 1)R_E}$$


$$S_\beta^{I_{C,Q}} = \frac{\partial I_{C,Q}}{\partial \beta} = \frac{\partial}{\partial \beta} \left(\beta \frac{V_{CC} - 0.7V}{R_B + (\beta + 1)R_E} \right) \\ = \frac{V_{CC} - 0.7V}{R_B} \cdot \frac{1 + \frac{R_E}{R_B}}{\left(1 + (\beta + 1) \frac{R_E}{R_B} \right)^2}$$

< 1




Common Emitter

BASIC

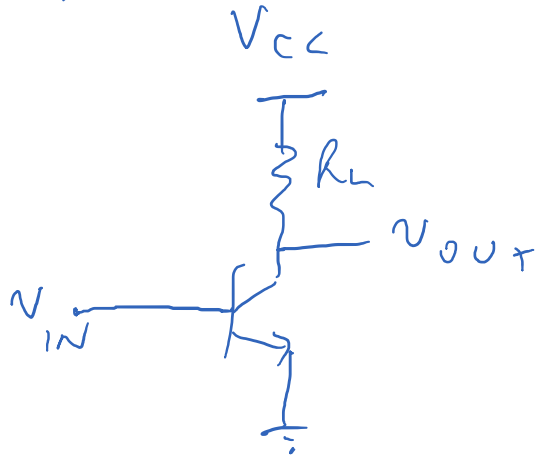

✗ uses 2 DC sources
- impractical


FIXED - BIAS

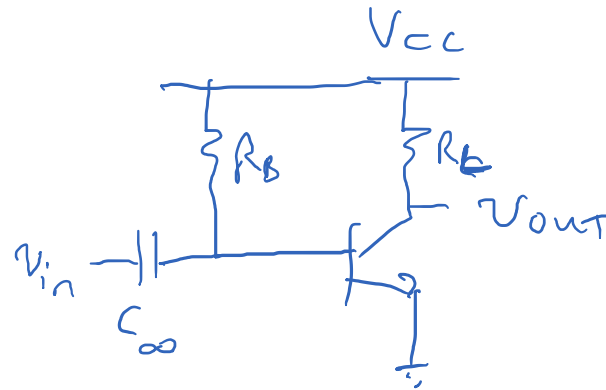

✓ uses only 1 DC source

✗ sensitive to β variations
→ unstable DC operating point


EMITTER - DEGENERATED

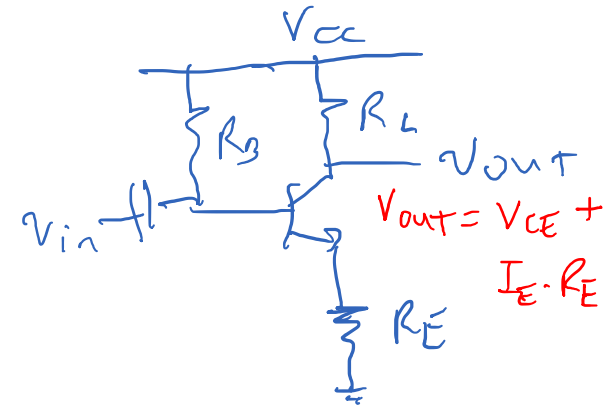


✓ 1 DC source
✓ less sensitive to β variations
✗ lower output swing



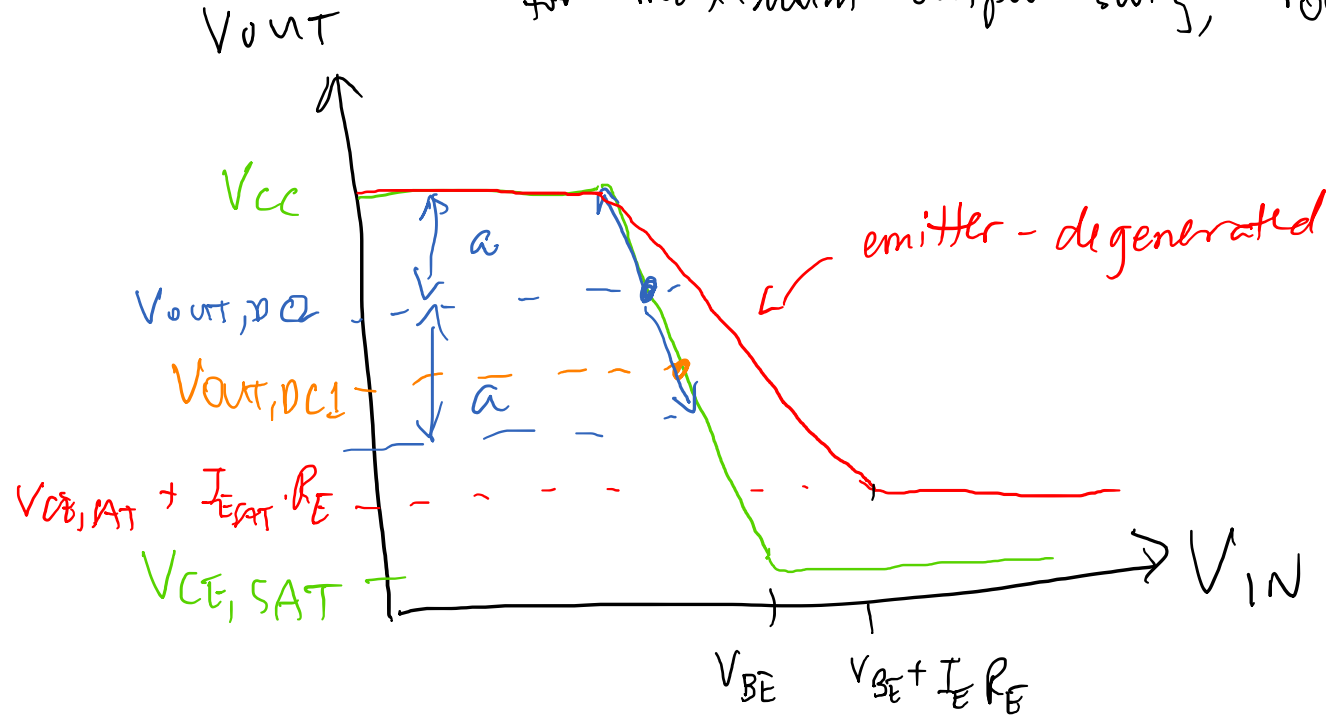for maximum output swing, $V_{out,DC1} = \frac{V_{CC} + V_{CE,SAT}}{2}$



DC Effects of R_E

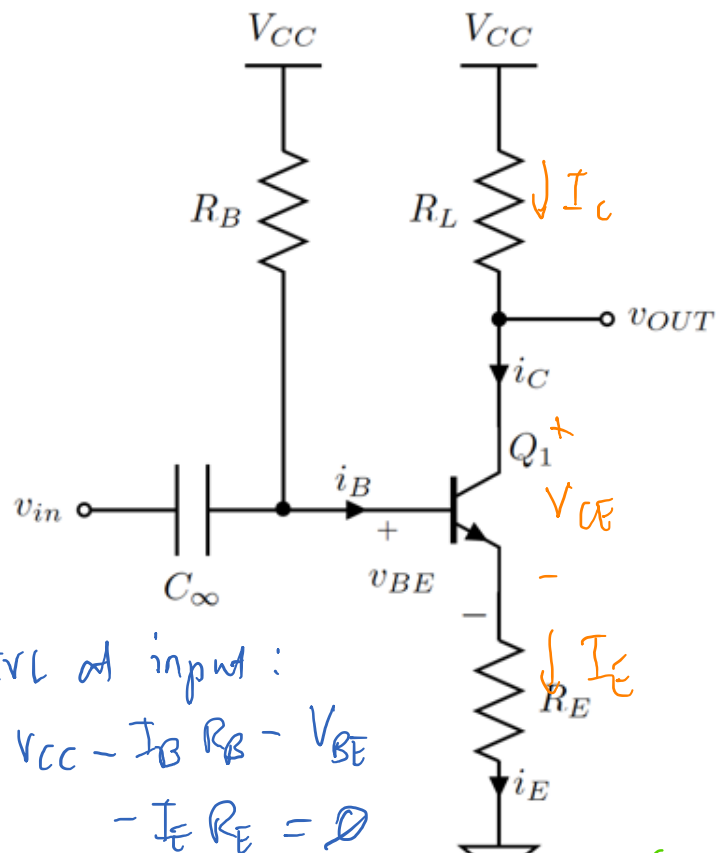

KVL at input:

$$V_{CC} - I_B R_B - V_{BE} - I_E R_E = 0$$

$$V_{CC} - \frac{I_C}{\beta} R_B - V_T \ln\left(\frac{I_C}{I_S}\right) - \left(1 + \frac{1}{\beta}\right) I_C R_E = 0$$

Output KVL:

$$I_E = I_C + I_B = I_C + \frac{I_C}{\beta}$$

$$V_{CC} - I_{C,Q} R_L - V_{CE,Q} - I_{E,Q} R_E = 0$$

$$V_{CC} - I_{C,Q} R_L - V_{CE,Q} - I_{C,Q} \left(1 + \frac{1}{\beta}\right) R_E = 0$$

To keep Q_1 in the forward-active region:

$$\rightarrow V_{CE,Q} > V_{CE,sat}$$

$$\text{Thus, } V_{CE,sat} < V_{CC} - I_{C,Q} R_L - I_{C,Q} \left(1 + \frac{1}{\beta}\right) R_E$$


$$R_E < \frac{V_{CC} - I_{C,Q} R_L - V_{CE,sat}}{I_{C,Q} \left(1 + \frac{1}{\beta}\right)}$$

$$V_{OUT} = ?$$

$$V_{CE} + I_E \cdot R_E$$



Small Signal Equivalent Circuit

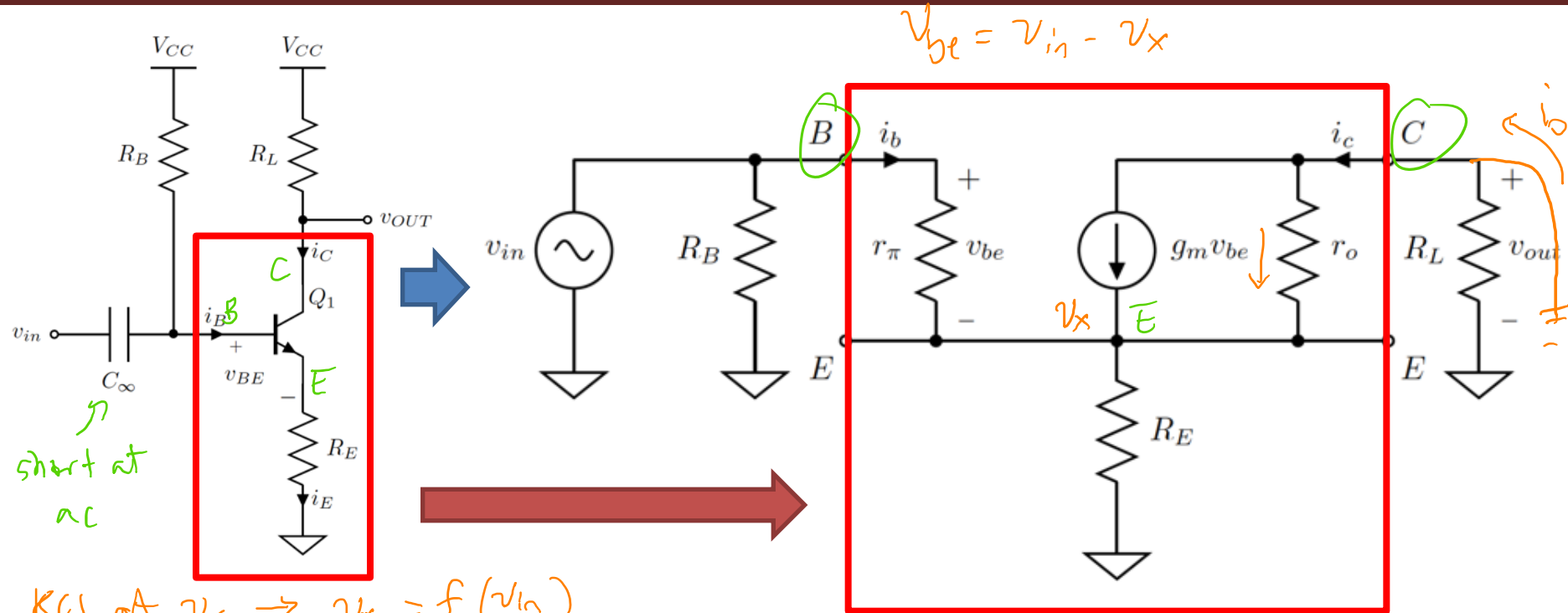


Let's look at the degenerated transistor first
 \rightarrow Derive the 2-port equivalent circuit



The Emitter-Degenerated Transistor (1)

- Calculating the transconductance

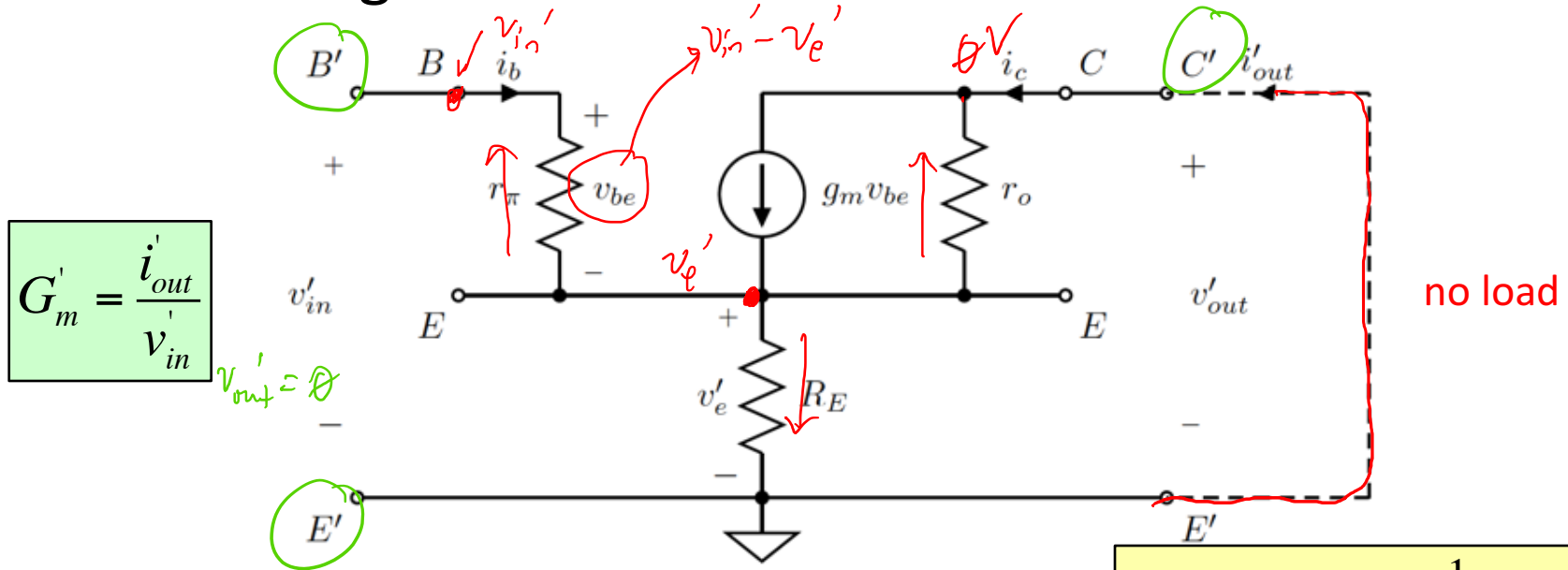

KCL at the emitter node:

$$\frac{v_e' - v_{in}'}{r_\pi} + \frac{v_e'}{R_E} + \frac{v_e'}{r_o} - g_m(v_{in}' - v_e') = 0$$



$$v_e' = v_{in}' \cdot \frac{g_m + \frac{1}{r_\pi}}{g_m + \frac{1}{r_\pi} + \frac{1}{r_o} + \frac{1}{R_E}}$$





The Emitter-Degenerated Transistor (2)

KCL at the collector:


$$i'_{out} = g_m (v'_{in} - v'_e) - \frac{v'_e}{r_o}$$

Recall:
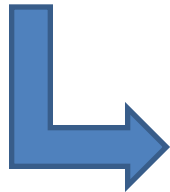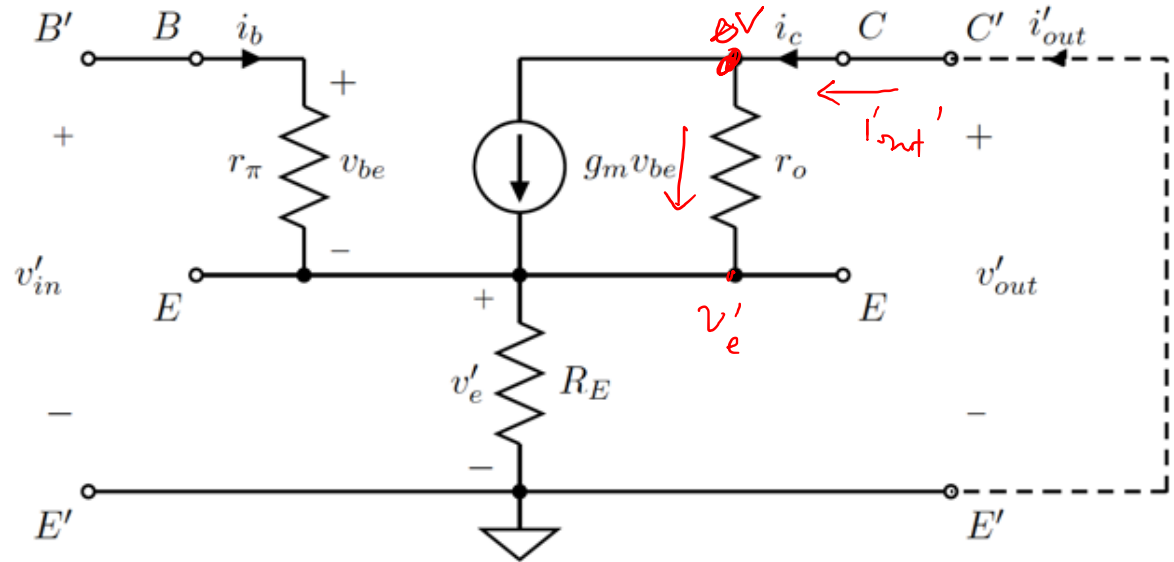
$$v'_e = v'_{in} \cdot \frac{g_m + \frac{1}{r_\pi}}{g_m + \frac{1}{r_\pi} + \frac{1}{r_o} + \frac{1}{R_E}}$$


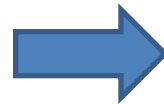
$$i'_{out} = v'_{in} \cdot g_m \cdot \frac{\frac{1}{R_E} - \frac{1}{g_m r_o r_\pi}}{g_m + \frac{1}{r_\pi} + \frac{1}{r_o} + \frac{1}{R_E}}$$



$$G'_m = \frac{i'_{out}}{v'_{in}} = g_m \cdot \frac{\frac{1}{R_E} - \frac{1}{g_m r_o r_\pi}}{g_m + \frac{1}{r_\pi} + \frac{1}{r_o} + \frac{1}{R_E}}$$




The Emitter-Degenerated Transistor (3)

Assume:

$$g_m r_o \gg 1$$

$$g_m r_\pi = \beta \gg 1$$

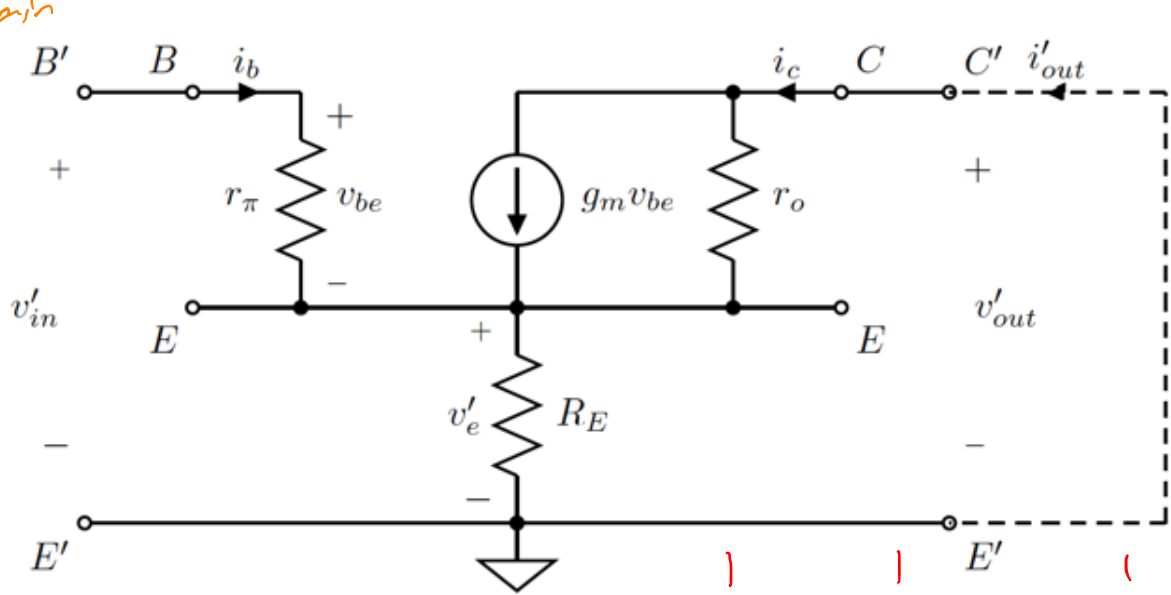
$$\left. \begin{array}{l} r_o \gg R_E \\ r_\pi \gg R_E \end{array} \right\}$$



$$r_\pi = \frac{\beta}{g_m}$$

$$G'_m = \frac{i'_{out}}{v'_{in}} = g_m \cdot \frac{\frac{1}{R_E} - \frac{1}{g_m r_o r_\pi}}{g_m + \frac{1}{r_\pi} + \frac{1}{r_o} + \frac{1}{R_E}} \approx \frac{g_m}{1 + g_m R_E} < g_m$$
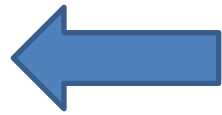
$$\frac{1}{R_E} - \frac{1}{\beta \cdot r_o} \approx \frac{1}{R_E}$$




The transconductance is degenerated by R_E

$$\approx g_m + \frac{1}{R_E} \approx \frac{g_m R_E + 1}{R_E}$$



The Emitter-Degenerated Transistor (4)

- Calculating the output resistance

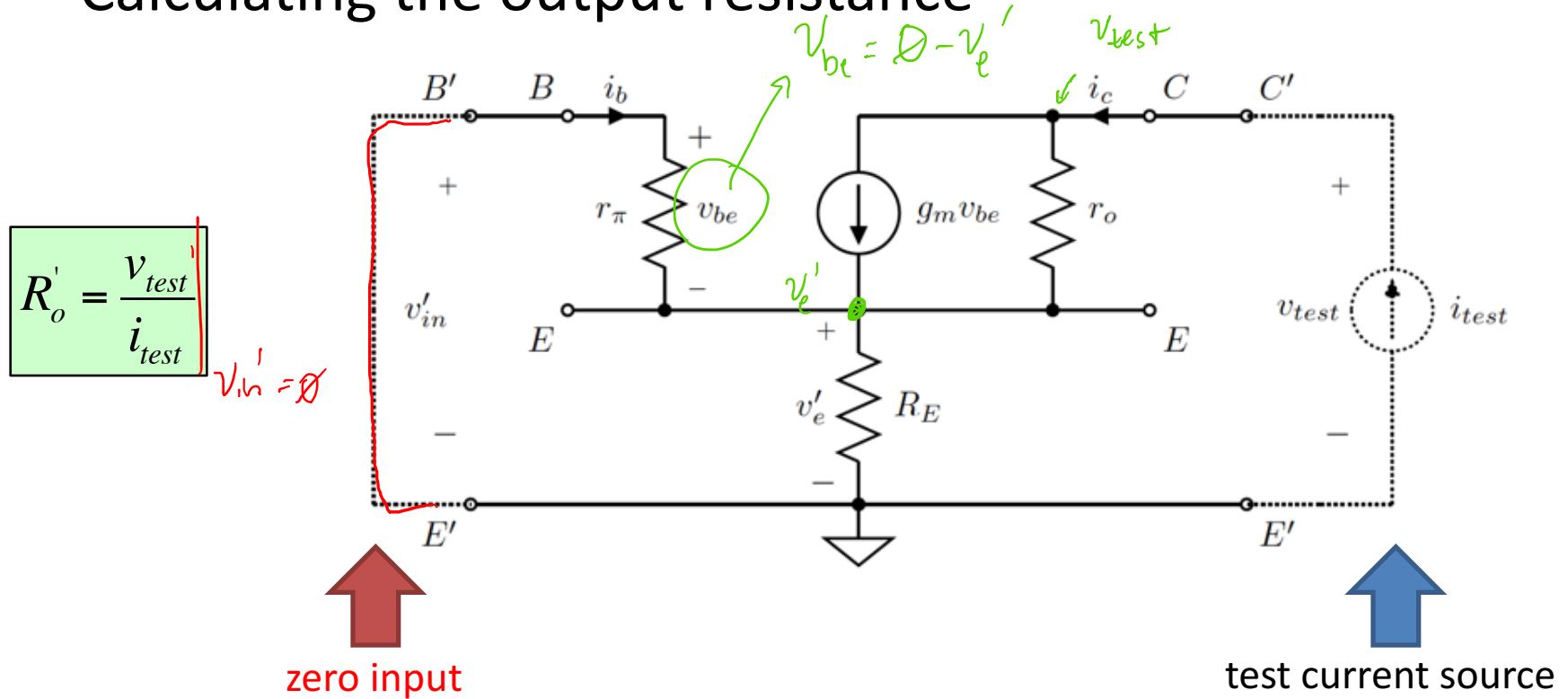

The Emitter-Degenerated Transistor (5)

By inspection:

$$v'_e = i_{test} \cdot (r_\pi \parallel R_E) = -v_{be}$$




Current through r_o :


$$\begin{aligned} i_{r_o} &= i_{test} - g_m v_{be} = i_{test} + g_m v'_e \\ &= i_{test} \cdot (1 + g_m (r_\pi \parallel R_E)) \end{aligned}$$

Solving for v_{test} :
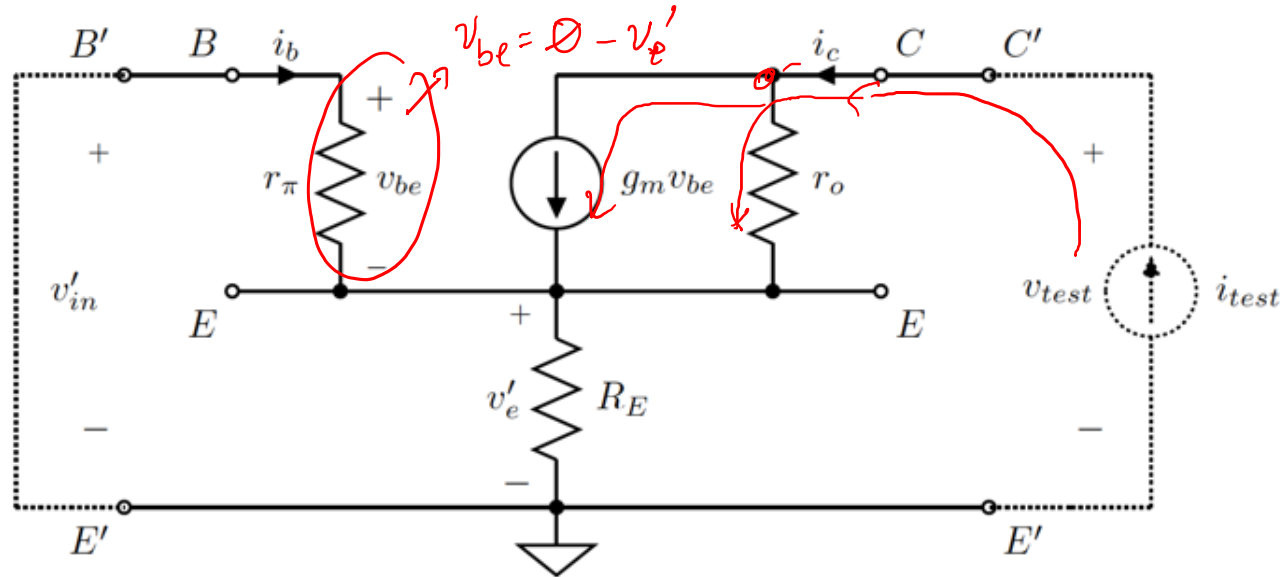
$$v_{test} = i_{r_o} r_o + v'_e = i_{test} \cdot [r_o + g_m r_o (r_\pi \parallel R_E) + (r_\pi \parallel R_E)]$$



The Emitter-Degenerated Transistor (6)

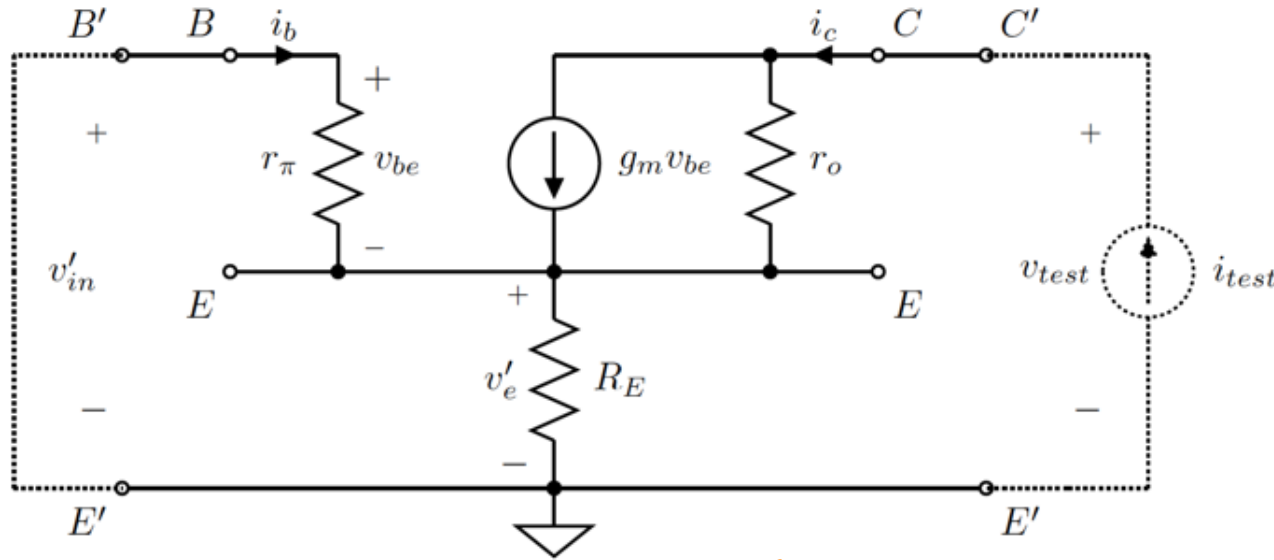

Assume:

$$g_m r_o \gg 1$$

$$g_m r_\pi = \beta \gg 1$$

$$r_o \gg R_E$$

$$r_\pi \gg R_E$$

Recall:

$$v_{test} = i_{test} \cdot \left[r_o + g_m r_o (r_\pi \parallel R_E) + (r_\pi \parallel R_E) \right]$$

$$= i_{test} \left[r_o + g_m r_o R_E + R_E \right]$$

Solving for R'_o :


$$R'_o = \frac{v_{test}}{i_{test}} = \left[r_o + g_m r_o (r_\pi \parallel R_E) + (r_\pi \parallel R_E) \right]$$

$$\approx r_o + g_m r_o R_E \approx r_o (1 + g_m R_E) \gg r_o$$




The Emitter-Degenerated Transistor (7)

- Calculating the input resistance

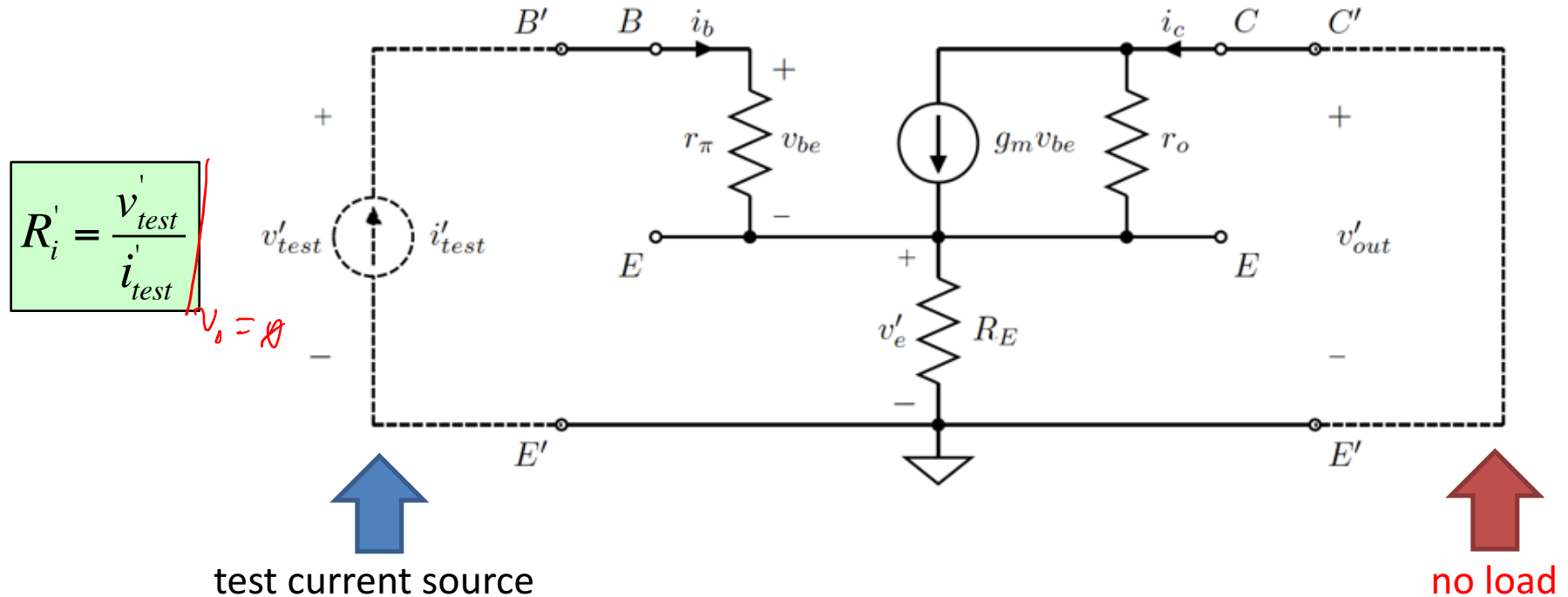

The Emitter-Degenerated Transistor (8)

$$v_{be} = i'_{test} \cdot r_{\pi}$$

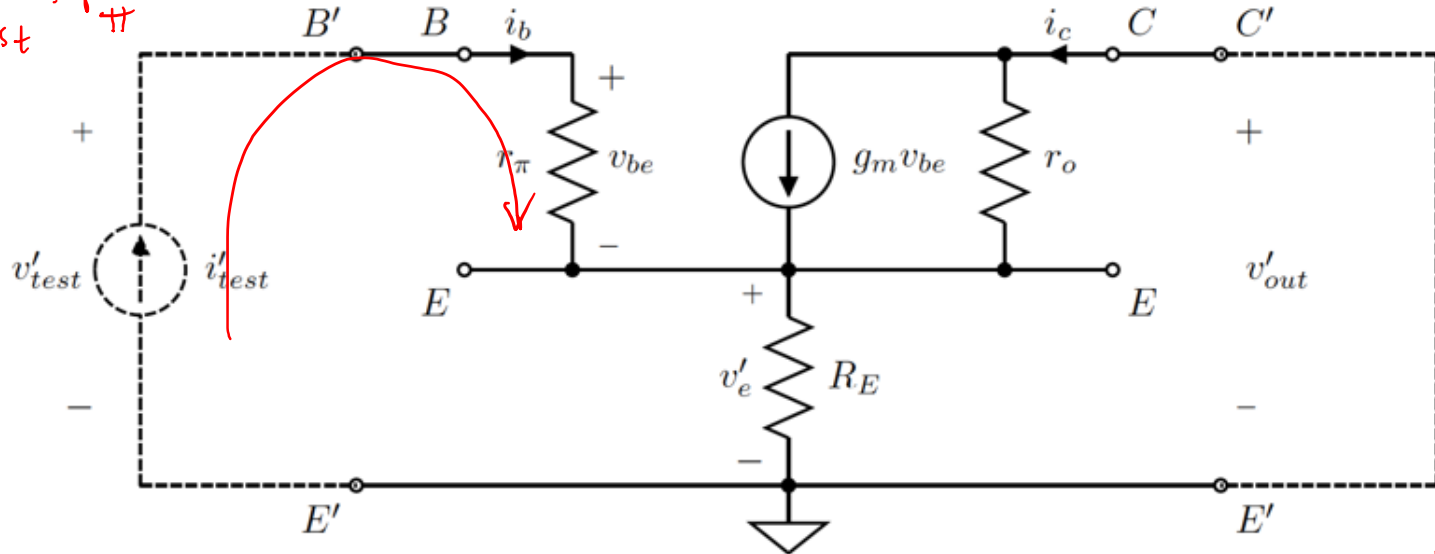

By inspection:

$$\begin{aligned} v'_e &= (i'_{test} + g_m v_{be}) \cdot (r_o \parallel R_E) \\ &= i'_{test} (1 + g_m r_{\pi}) \cdot (r_o \parallel R_E) \end{aligned}$$



$$\begin{aligned} v'_{test} &= v_{be} + v'_e = i'_{test} r_{\pi} + i'_{test} (1 + g_m r_{\pi}) \cdot (r_o \parallel R_E) \\ &= i'_{test} \cdot [r_{\pi} + g_m r_{\pi} (r_o \parallel R_E) + (r_o \parallel R_E)] \end{aligned}$$



The Emitter-Degenerated Transistor (9)


Assume:

$$g_m r_o \gg 1$$

$$g_m r_\pi = \beta \gg 1$$

$$r_o \gg R_E$$

$$r_\pi \gg R_E$$

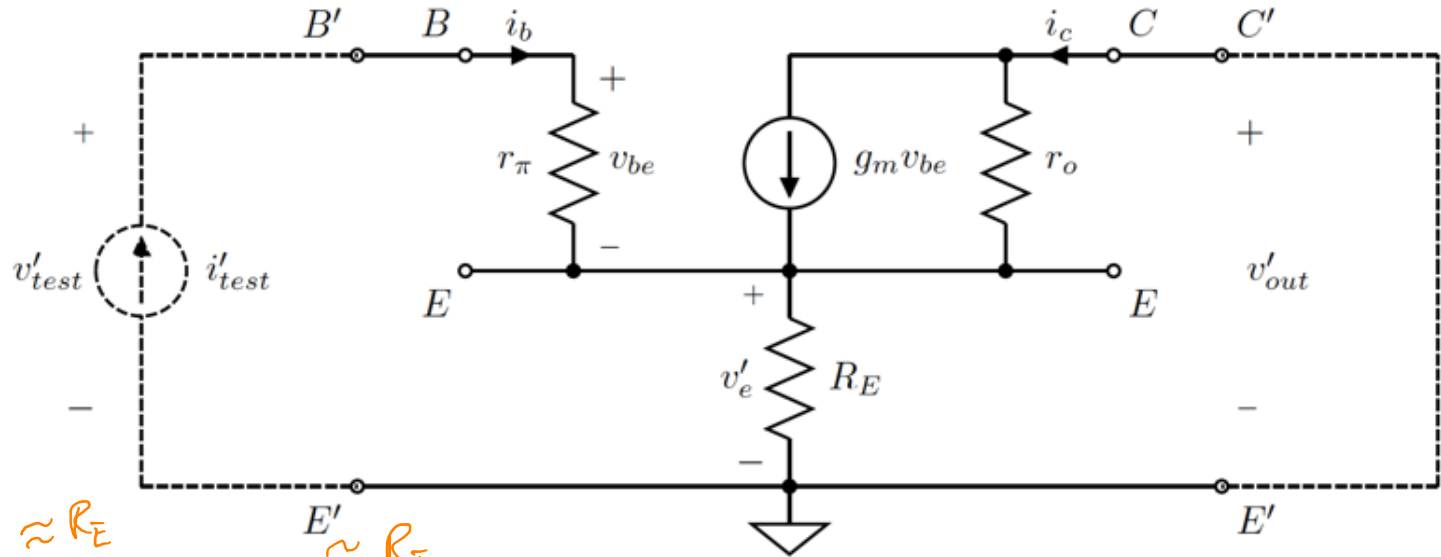

Recall:

$$v'_{test} = i'_{test} \cdot [r_\pi + g_m r_\pi (r_o \parallel R_E) + (r_o \parallel R_E)]$$

$$= i'_{test} [r_\pi + g_m r_\pi R_E + R_E]$$

$\approx r_\pi$


Solving for R'_i :

$$R'_i = \frac{v'_{test}}{i'_{test}} = [r_\pi + g_m r_\pi (r_o \parallel R_E) + (r_o \parallel R_E)]$$


$$\approx r_\pi \cdot (1 + g_m R_E) > r_\pi$$



The Emitter-Degenerated Transistor (10)

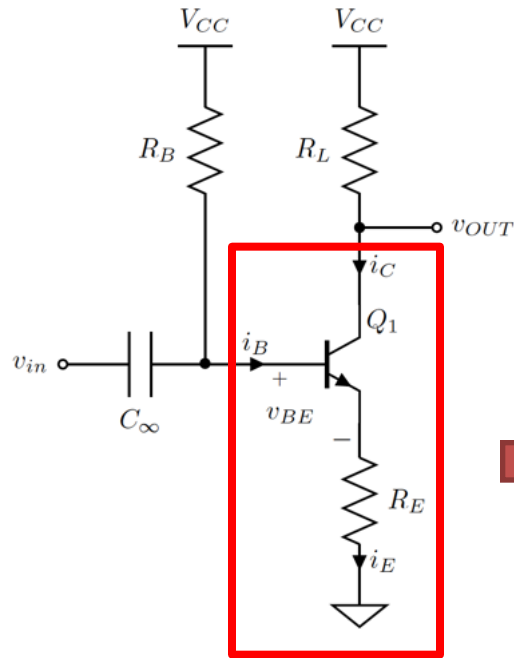

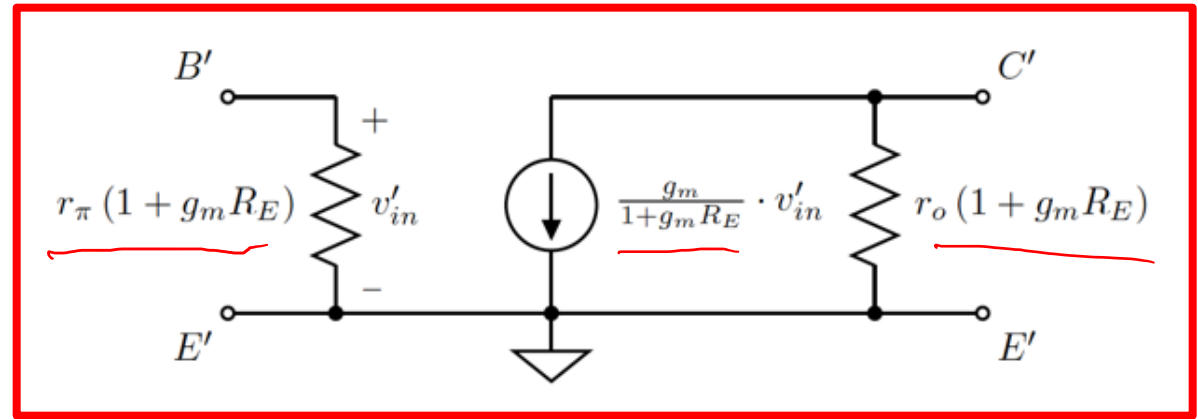Degenerated transistor small signal equivalent




Transconductance \rightarrow reduced (degenerated) by $(1 + g_m R_E)$
Resistances \rightarrow increased by $(1 + g_m R_E)$

Is this good or bad?



Emitter-Degenerated Common-Emitter Amplifier

Overall analysis is now easy!

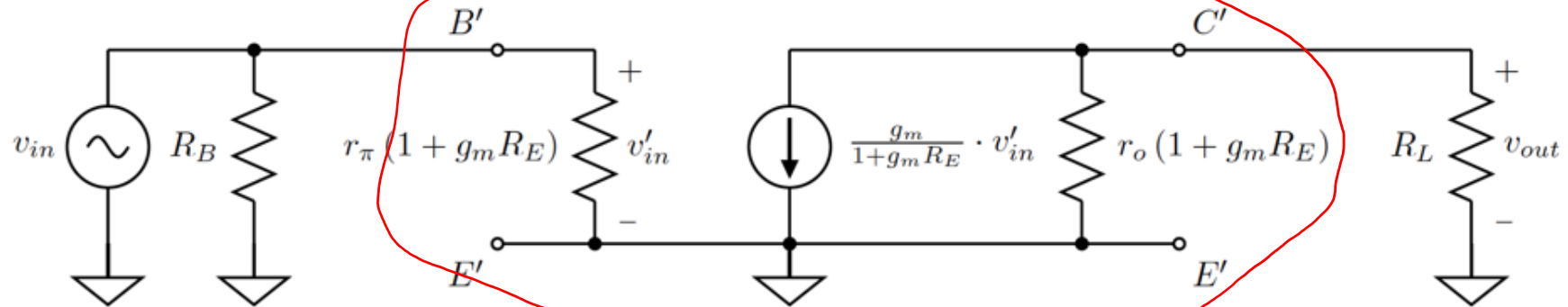

By inspection:

Assume:

$$\left. \begin{array}{l} r_o \gg R_L \\ r_\pi \gg R_B \end{array} \right\}$$

fixed bias:

$$\begin{aligned} A_v &= -g_m (r_o \parallel R_L) \\ &\approx -g_m R_L \end{aligned}$$

$$R_i = r_\pi \cdot (1 + g_m R_E) \parallel R_B \approx R_B$$


$$G_m = \frac{g_m}{1 + g_m R_E}$$

$$R_o = r_o (1 + g_m R_E) \parallel R_L \approx R_L$$

Voltage gain:
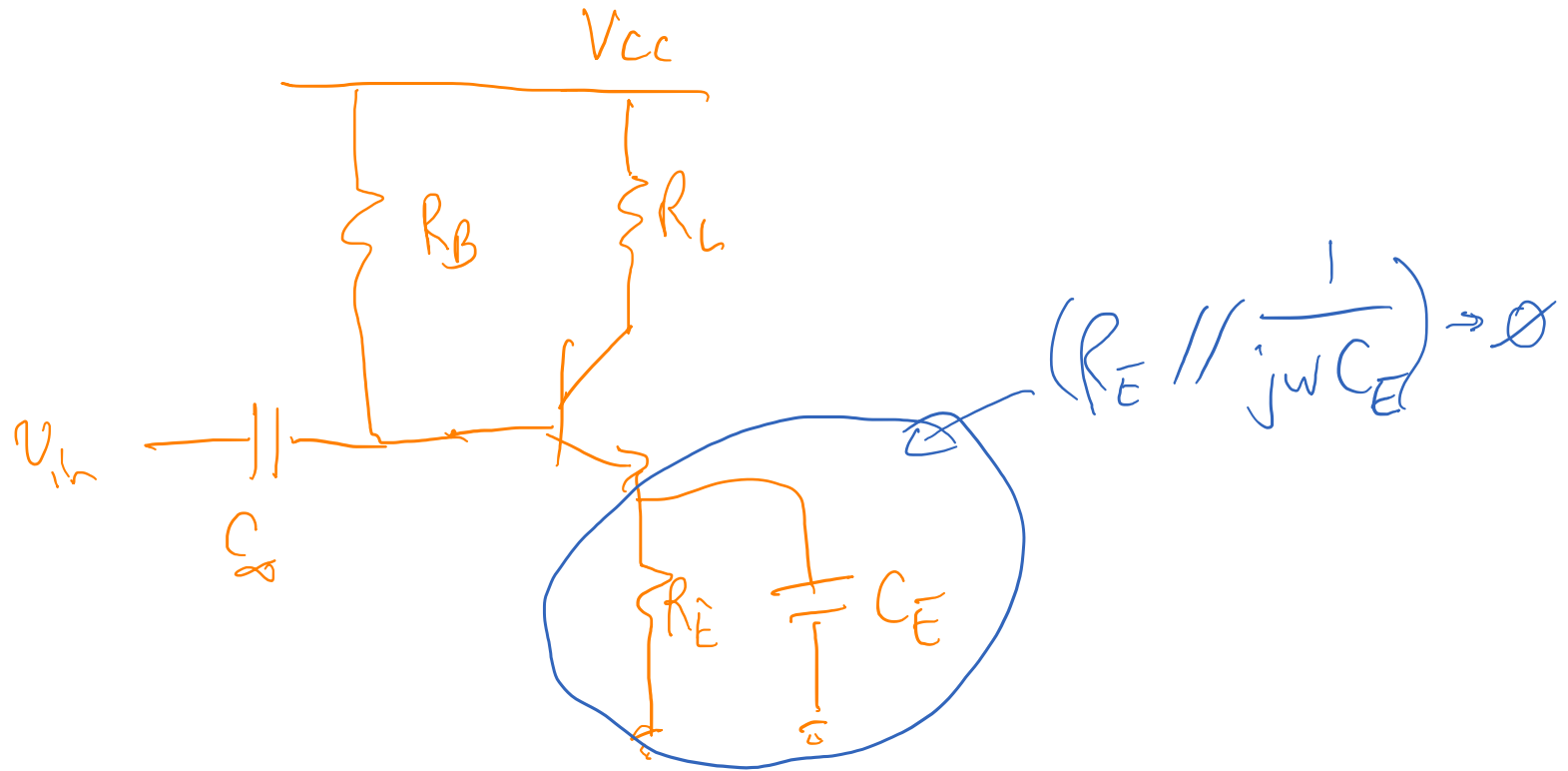
$$A_v = -G_m R_o = -\frac{g_m R_L}{1 + g_m R_E}$$





Next Meeting

- Single-Stage Amplifiers
 - Common-Source Amplifier
 - Common-Base / Common-Gate Amplifier
 - Common-Collector / Common-Drain Amplifier

