


Name:

Solutions

Student No.:

Part III:

(19 points) The differential amplifier below, with $V_{CC} = 5\text{ V}$, $R_E = 50\ \Omega$, and $R_L = 800\text{ k}\Omega$, has the following quiescent state: $I_{C3} = 1\text{ mA}$, $I_{C1} = I_{C2} = 500\ \mu\text{A}$, $V_{GS1} = V_{GS2} = 1.5\text{ V}$, and $V_x = 0.5\text{ V}$. All the BJTs have $|V_{CE,sat}| = 0.2\text{ V}$, with $r_{o,Q1} = r_{o,Q2} = 200\text{ k}\Omega$, and $r_{o,Q3} = 100\text{ k}\Omega$. The MOSFETs are identical, with $V_{TH} = 1\text{ V}$, and $\lambda = 0$. The bias voltage V_{B1} is a constant, while an external circuit (not shown) automatically adjusts V_{B2} to maintain $V_o^+ = V_o^- = 2.5\text{ V}$. Assume $V_T = \frac{kT}{q} = 26\text{ mV}$.

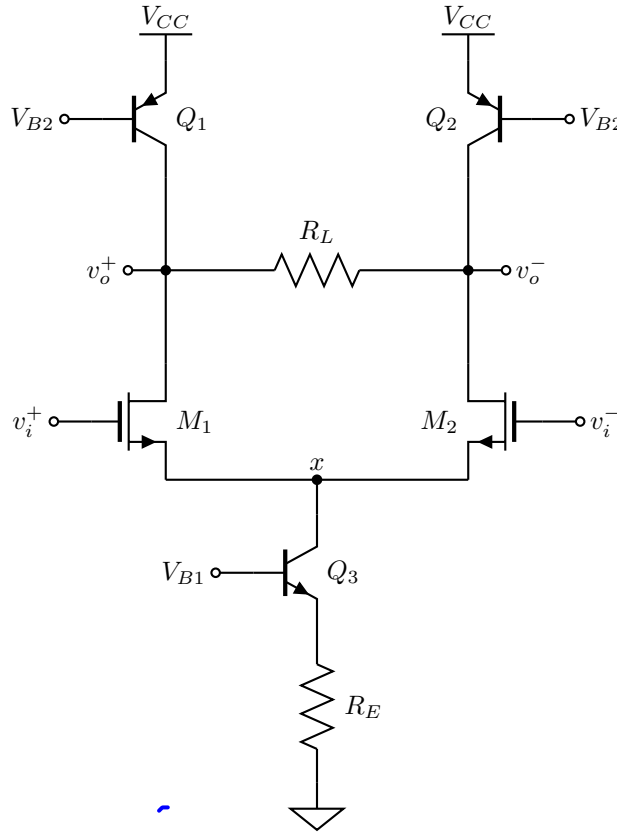

1. Determine the minimum input common mode voltage, $V_{IC,min}$. (3 points)

$$\begin{aligned}
 V_{IC,min} &= V_{GS1} + V_{CE,sat,Q1} + V_{RE} = V_{x,min} \\
 &= 1.5\text{ V} + 0.2\text{ V} + (1\text{ mA} \cdot 50\ \Omega) \\
 &= 1.5\text{ V} + 0.2\text{ V} + 50\text{ mV} \\
 &= 1.75\text{ V}
 \end{aligned}$$

 $V_{IC,min} =$

1.75 V

2. Determine the maximum input common mode voltage, $V_{IC,max}$. (2 points)

$$V_{DS1,min} = V_0^+ - V_{X,max} \text{ but } V_{X,max} = V_{ic,max} - V_{GS1}$$

$$V_{DSat} = V_0^+ - V_{ic,max} + V_{GS1}$$

$$V_{GS1} - V_{TH} = V_0^+ - V_{ic,max} + V_{GS1}$$

$$V_{IC,max} = 3.5V$$


$$\therefore V_{ic,max} = V_0^+ + V_{TH} = 2.5V + 1V = 3.5V$$

3. What is the maximum symmetric differential output voltage swing? (4 points)

If $V_0^+ = V_0^- = 2.5V$, the max. swing of V_0^+ is $V_{DD} - V_{DS,sat} = 5V - 0.2V = 4.8V$.

The min. swing is set by $V_{0,min} - V_X > V_{DSat}$.
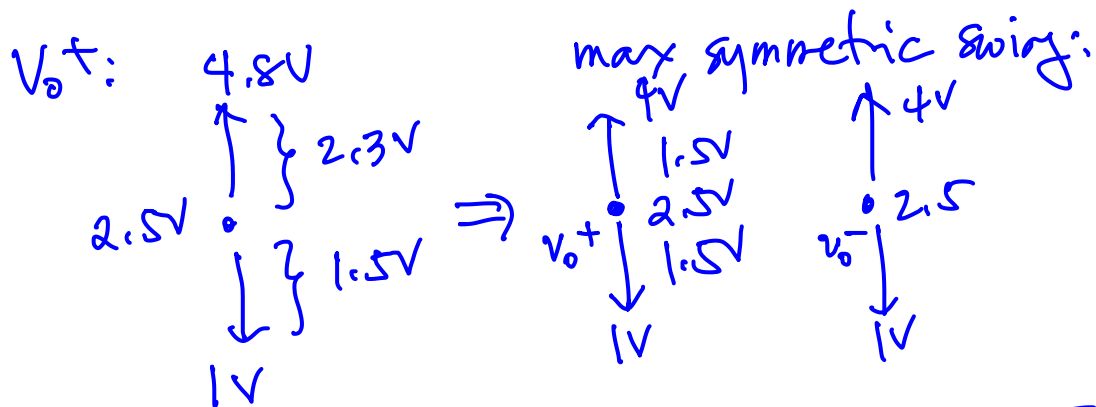
$$\begin{aligned} \therefore V_{0,min} &= V_{DSat} + V_X = V_{GS1} - V_{TH} + V_X \\ &= 1.5V - 1V + 0.5V \\ &= 1V \end{aligned}$$



$$V_{od} = V_0^+ - V_0^-$$

$$\begin{aligned} V_{od,max} &= V_{0,max}^+ - V_{0,min}^- \\ &= 4V - 1V = 3V \end{aligned}$$


$$\begin{aligned} V_{od,min} &= V_{0,min}^+ - V_{0,max}^- \\ &= 1V - 4V = -3V \end{aligned}$$

$$V_{od,swing,max} = 6V$$

4. Determine the maximum differential input voltage swing such that there is no clipping at the output. (5 points)

To get the input swing, we need the diff. voltage gain.

Diff. half circuit:

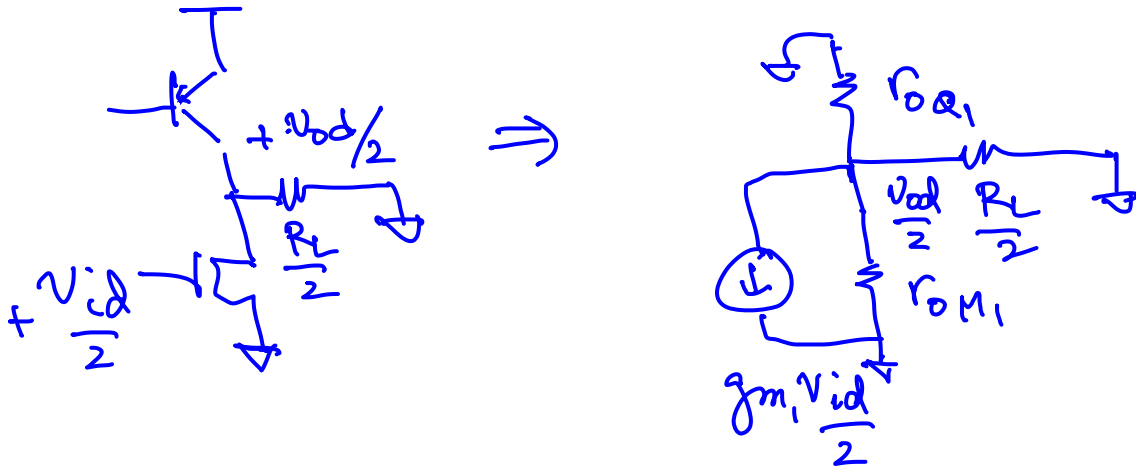


$$\begin{aligned}
 A_{dm} = \frac{v_{od}}{v_{id}} &= -g_{m_{n_1}} (r_{oQ_1} \parallel r_{oM_1} \parallel \frac{R_L}{2}) \\
 &= -\frac{2I_{D_{M_1}}}{V_{GS_1} - V_{TH}} (r_{oQ_1} \parallel r_{oM_1} \parallel \frac{R_L}{2}) \\
 &= -\frac{(2)500 \mu A}{1.5V - 1V} (200k\Omega \parallel \infty \parallel 400k\Omega) \\
 &= -133.3(2) = -266.6
 \end{aligned}$$

$$\therefore v_{id,swing} = \frac{v_{od,swing}}{|A_{dm}|} = \frac{6}{266.6} = 22.5 \text{ mV}$$

$$v_{id,swing,max} = 22.5 \text{ mV}$$

5. Determine the common-mode rejection ratio (CMRR) of the amplifier. (5 points)

CM Half circuit:

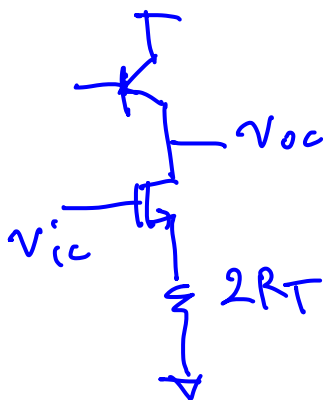


R_T :

$$R_T = r_{o3}(1 + g_{m3}R_E)$$

$$= 100k \left(1 + \frac{1mA}{26mV} \cdot 50\Omega\right)$$

$$= 292k\Omega$$

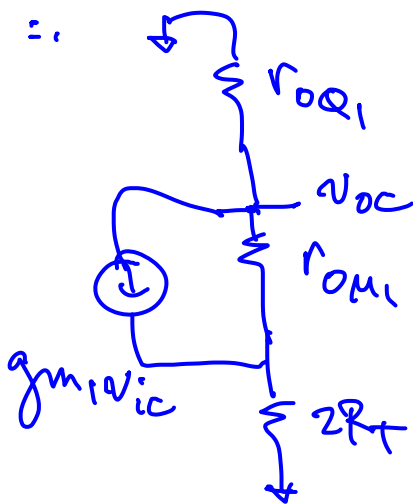

$$A_{cm} = \frac{-g_{m1}}{1 + g_{m1}(2R_T)} \cdot r_{o1}$$

$$= \frac{-2(500\mu A) \cdot (200k\Omega)}{1.5V - 1V}$$

$$= \frac{-400}{1 + \frac{2(500\mu A) \cdot 2 \cdot 292k\Omega}{1.5V - 1V}}$$

$$= \frac{-400}{1 + 1168} = -0.171$$

$$\therefore CMRR = \left| \frac{A_{dm}}{A_{cm}} \right| = \frac{266.6}{0.171} = 1559$$

$$\approx 1560$$

CMRR =

1560