

EEE 51 Assignment 9

2nd Semester SY 2018-2019

Due: 5pm Tuesday, May 7, 2019 (Rm. 220)

Instructions: Write legibly. Show all solutions and state all assumptions. Write your full name, student number, and section at the upper-right corner of each page. Start each problem on a new sheet of paper. Box or encircle your final answer.

Answer sheets should be color coded according to your lecture section. The color scheme is as follows:

THQ – yellow
THU – white
WFX – pink

1. Positive-Negative.

You are to implement an amplifier with feedback. Given in Figure 1 are two possible designs.

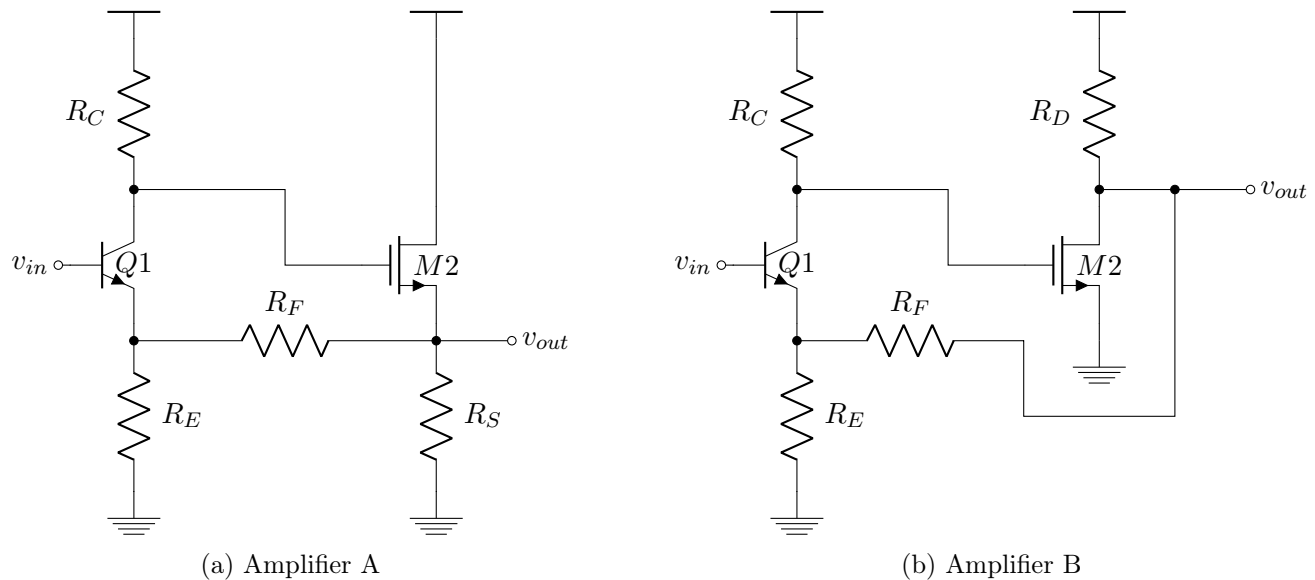


Figure 1: Feedback Amplifiers.

- Both of the designs use the same type of feedback. Identify the type of feedback being used. (1 pt)
- Which of the two designs is valid (employs negative feedback and will not blow-up)? Be careful since your answers in the next item will be dependent here. Committing a mistake in this item will automatically void the answers for the next item. (2 pts)
- Using your answer in (b), use the parameters β , g_{mx} , and r_π ; and the resistors R_C , R_D , R_E , R_F , and R_S to express your answers. Assume that $r_o \rightarrow \infty$ for both transistors. For parallel resistors, just use $(R_1 || R_2 || \dots || R_n)$ notation instead. Do not expand the expressions.
 - Feedback gain $f = \frac{v_{fb}}{v_o}$. (1 pt)
 - Open-loop gain (with feedback loading) $a_v = \frac{v_{out}}{v_{in}}$. (1 pt)
 - Closed-loop gain $A_V = \frac{v_{out}}{v_{in}}$. (1 pt)
 - Closed-loop input resistance $R_{IN} = \frac{v_{in}}{i_{in}}$. (2 pts)
 - Closed-loop output resistance $R_{OUT} = \frac{v_{out}}{i_{out}}$. (2 pts)

- Sbeve

2. Feed me, feed me, feed me back!

The parameters for all transistors are the following: $V_{be,on} = 0.7V$, β and V_A approaches infinity. $v_{in,DC} = 0.9V$, $v_{out,DC} = 2.5V$, $V_{DD} = 5V$. All transistors operate in the forward active region at $T = 300\text{ K}$.

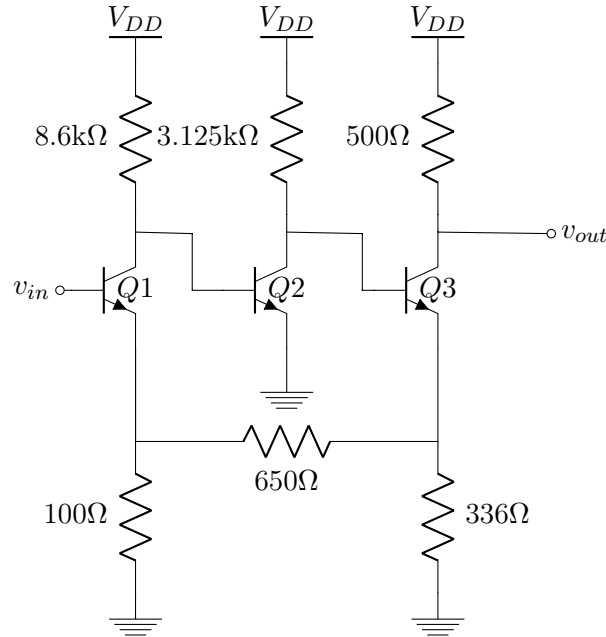


Figure 2: BJT Circuit

- Solve for the collector currents, I_{C1} , I_{C2} , I_{C3} , and small signal g_{m1} , g_{m2} , g_{m3} for transistors Q1, Q2, and Q3 (3 pts)
- Identify the feedback configuration (1 pt)
- Draw the two-port network of the feedback circuit then solve for the feedback parameters $R_{i,fb}$, $R_{o,fb}$, and feedback factor F (4 pts)
- Solve for the loaded open-loop "gain" (depends on your answer in (b)) (2 pts)
- Solve for the closed-loop voltage gain, $\frac{v_{out}}{v_{in}}$ of the whole circuit (3 pts)
- Suppose the open-loop "gain" increased by 10%, by how much is the approximate increase, in percentage, of the closed-loop voltage gain? (2 pts)

3. Give Me Some More Feedback

For the amplifier feedback circuits in Figure 3, assume $k_n = 13.42mA/V^2$, $k_p = 3.83mA/V^2$, $\lambda_{n1} = \lambda_{p3} = 0$, $\lambda_{p2} = 0.2V^{-1}$, $\lambda_{n4} = 0.1V^{-1}$, $I_{D1} = I_{D2} = I_{D3} = I_{D4} = 0.5mA$, $R_F = R_{S1} = R_{D2} = 3k\Omega$ and I_{tail} is an ideal current source.

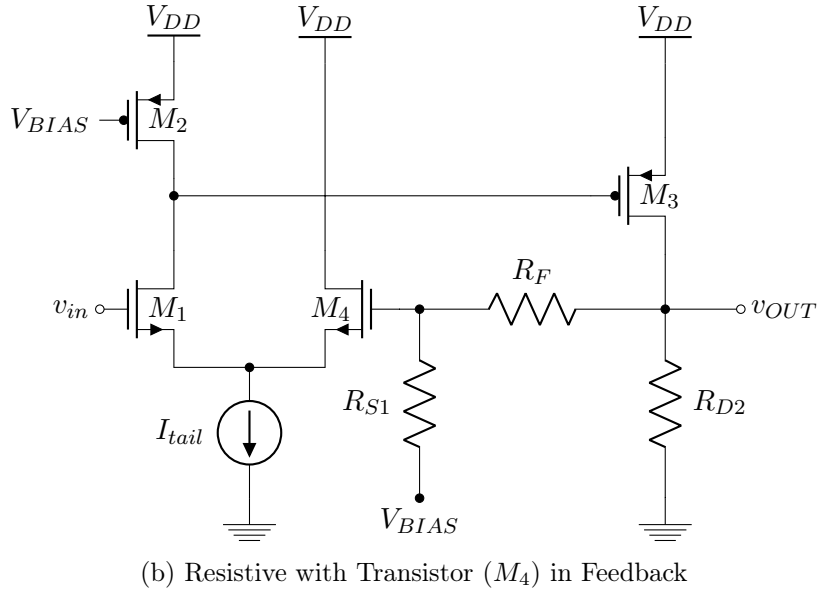
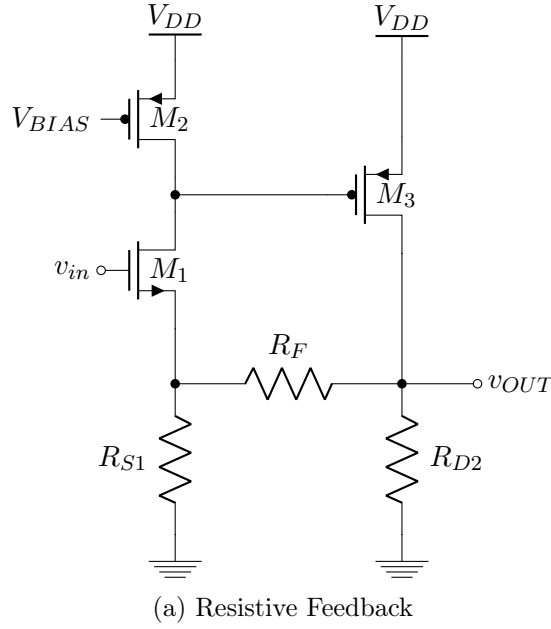


Figure 3: Two-Stage Amplifier with Feedback

For Figure 3a, refer to the following: (**Note:** For parallel resistors, just use $(R_1 || R_2 || \dots || R_n)$ notation instead. Do not expand the expressions for all the items below)

- Identify the feedback configuration and justify why. (1pt)
- Draw the feedback circuit, find the expression for input, output resistance and the feedback factor $(R_{I,fb}, R_{O,fb}, F)$. Using these expressions, transform the feedback circuit to a unilateral two-port equivalent model. (2.5pts)
- Draw the whole small-signal equivalent model circuit (Amplifier+Feedback) (Only include small signal parameters that are finite). Use the obtained feedback unilateral two-port model in (b). Label the

forward path and the **ideal** feedback path. (Hint: Ideal feedback path is where no resistances are in the path. Think this through: How to remove the resistances in the feedback path to make it ideal?) (2pts)

- (d) Derive the expression and solve for the open-loop gain/forward gain $A_{v,ol}$ using the small signal model in (c). (1.5pts)
- (e) Find the expression and solve for the loop gain T . (0.5pt)
- (f) Find the expression and solve for the closed-loop gain $A_{v,cl}$. (0.5pt)
- (g) Find the expression and solve for the output resistance of the feedback amplifier $R_{O,cl}$. (1pt)

For Figure 3b, M_4 is inserted in the feedback loop. Refer to the following:

- (h) Is the feedback configuration changed? Why or Why not? (1pt)
- (i) Repeat (b) to (g) for the second circuit. Transform M_4 to its equivalent small-signal model when drawing the feedback circuit. (8pts)
- (j) Compare the obtained closed-loop gain and output resistance of the two feedback circuits and explain the differences if there is any. What is the use of adding M_4 in the feedback loop? (2pts)

TOTAL: 45 points.