

# EEE 51 Assignment 3

2nd Semester SY 2018-2019

Due: 5pm Tuesday, February 19, 2019 (Rm. 220)

*Instructions:* Write legibly. Show all solutions and state all assumptions. Write your full name, student number, and section at the upper-right corner of each page. Start each problem on a new sheet of paper. Box or encircle your final answer.

Answer sheets should be color coded according to your lecture section. The color scheme is as follows:

**THQ** – yellow  
**THU** – white  
**WFX** – pink

## 1. Single Stage Amplifier with Diode connected Load

Given that  $V_{DD} = 5V$ ,  $k_n = 6mA/V^2$ ,  $k_p = 0.5mA/V^2$ ,  $V_{thn} = 0.7V$ ,  $V_{thp} = -0.5V$ ,  $\lambda_n = 0.1V^{-1}$ ,  $\lambda_p = 0.05V^{-1}$ , and both FETs in saturation, answer the questions below.


 


Figure 1: Amplifier with diode connected load


- What is the amplifier configuration? (1 pt.)
- Solve for  $I_{DS}$  and  $V_{BIAS}$  given that  $V_{OUT} = 2.5V$  (2 pts.)
- Solve for the small signal parameters then draw the small-signal equivalent circuit. Properly label all components and their values as well as terminal names. DO NOT assume that  $|\lambda V_{DS}| \ll 1$  for both transistors in this part (use partial differentiation to get the small signal parameters). (3 pts.)
- Get the expression for  $R_o$  then solve for its value. (2 pts.)
- Get the expression for  $G_m$  then solve for its value. (1 pt.)
- Solve for the value of the small signal voltage gain,  $\frac{v_{out}}{v_{in}}$  (1 pt.)
 
## 2. Single Stage Amplifier with Current Source Load

For Figure 2, Assume that  $Q1$  and  $Q2$  are biased to operate in Forward Active Region @  $T = 300K$  but only  $Q1$  has an early voltage that approaches infinity ( $V_{A_{Q1}} \rightarrow \infty$ ).



 (a) Single Stage Amplifier with Load Resistor  $R_L$



(b) Single Stage Amplifier with  $Q2$

Figure 2

- (a) Refer to Figure 2a for the items below.
- Give the type of amplifier configuration for Figure 2a. (1 pt.)
  - Draw the *simplified* small signal equivalent circuit and label all transistors terminals, small signal parameters and external resistors. (2 pts.)
  - Derive the *simplified* expression for voltage gain  $A_{v1} = \frac{v_{out}}{v_{in}}$  in terms of small signal parameters,  $R_E$  and  $R_L$ . You can assume that  $(r_\pi \gg \frac{1}{g_m})$  so that  $(r_\pi || \frac{1}{g_m}) \approx \frac{1}{g_m}$ . (2 pts.)
- (b) Suppose that  $I_{DC}$  was replaced by  $Q2$  which is shown in Figure 2b, refer to this figure for the items below.
- Is the amplifier configuration type changed when  $R_L$  was replaced with  $Q2$ ? Why or Why not? (Limit your answer into two sentences). (1 pt.)
  - Draw the *simplified* small signal equivalent circuit and label all transistors terminals, small signal parameters and external resistors. (3 pts.)
  - Derive the *simplified* expression for voltage gain  $A_{v2} = \frac{v_{out}}{v_{in}}$  in terms of small signal parameters and  $R_E$ . You can also assume that  $(r_\pi \gg \frac{1}{g_m})$ . (2 pts.)
- (c) Lets say that the  $\beta$ 's for both transistors ( $Q1$  for both figures and  $Q2$ ) are high enough for the base currents ( $I_{B1}$  and  $I_{B2}$ ) to be negligible with respect to the collector currents  $I_{C1}$  and  $I_{C2}$ . Now, for Figures 2a and 2b and given that  $V_{EE} = 8V$ ,  $V_{OUT} = 3V$ ,  $R_E = 80\Omega$  with a voltage drop of

$V_{RE} = 1.6V$ ,  $Q2$  early voltage  $V_{AQ2} = 100V$ , and still holding the assumption for  $Q1$  early voltage to be  $V_{AQ1} \rightarrow \infty$ , Calculate the following:

- i. Values for the derived  $A_{v1}$  and  $A_{v2}$ . (Limit your answer up to two decimal places) (*3 pts.*)
- ii. The percentage increase/decrease of the two gains above relative to  $A_{v2}$ . What can you conclude about this? (*1 pt.*)

TOTAL: 25 points.