



EEE 51: Second Semester 2017 - 2018

Lecture 10


Differential Circuits

Today

- MOSFET Differential Circuits



The MOSFET Differential Amplifier

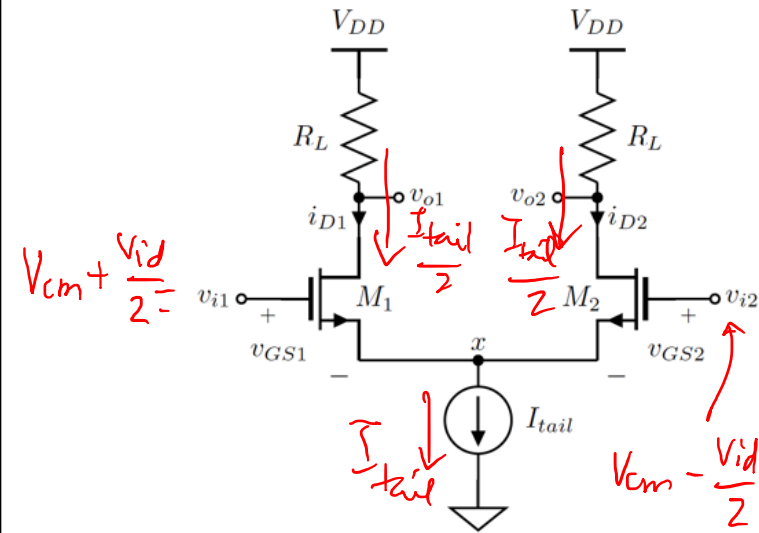

* M_1 & M_2 must be matched

$$- k_1 = k_2, \lambda_1 = \lambda_2, V_{TH1} = V_{TH2}$$

* we want to look at how V_{od} changes with V_{id}

case 1: $V_{id} = 0$ [$V_{i1} = V_{i2}$]

$$I_{D1} = I_{D2} = \frac{I_{tail}}{2}$$


$$V_{O1} = V_{DD} - I_{D1} R_L = V_{DD} - \frac{I_{tail}}{2} R_L$$

$$V_{O2} = V_{DD} - I_{D2} R_L = V_{DD} - \frac{I_{tail}}{2} R_L$$

$$V_{od} = 0$$



The MOSFET Differential Amplifier

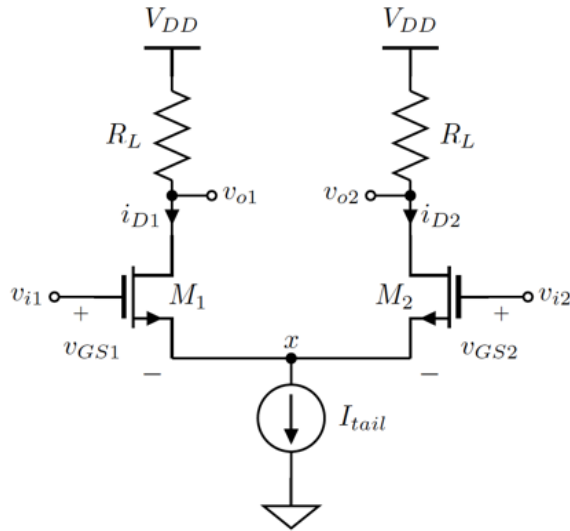

case 2: $V_{id} > 0$ [$V_{i1} > V_{i2}$]

$$I_{D1} > I_{D2} \Rightarrow V_{O1} < V_{O2}$$

$$V_{od} < 0$$

$$\max I_{D1} = I_{tail}$$

$$V_{O1} = V_{DD} - I_{tail} \cdot R_L$$

$$V_{O2} = V_{DD}$$


$$\left. \begin{array}{l} \max I_{D1} = I_{tail} \\ V_{O1} = V_{DD} - I_{tail} \cdot R_L \end{array} \right\} |V_{od, \max}| = (-I_{tail} \cdot R_L)$$

case 3: $V_{id} < 0$ [$V_{i1} < V_{i2}$]

$$I_{D1} < I_{D2} \Rightarrow V_{O1} > V_{O2}$$


$$V_{od} > 0 \quad \max I_{D2} = I_{tail}$$

$$V_{od, \max} = +I_{tail} \cdot R_L$$

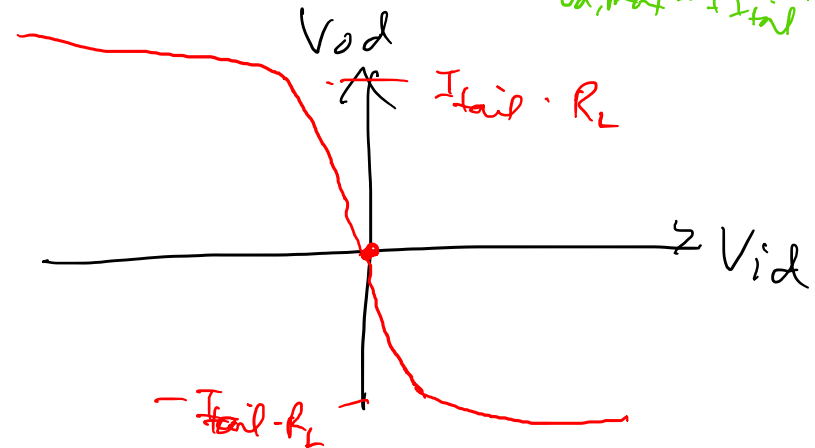

The MOSFET Differential Amplifier (1)

- Source-coupled pair: DC Analysis

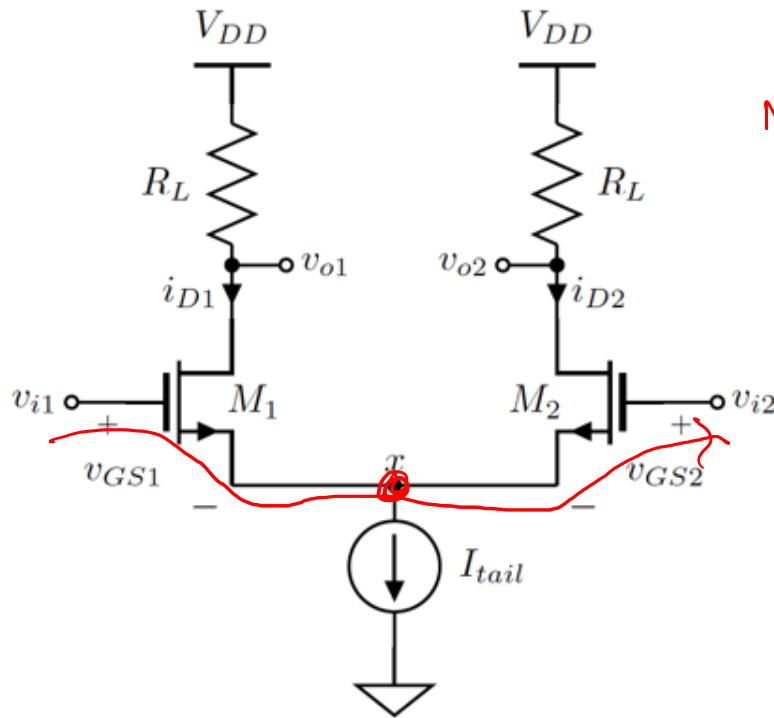

KVL at the input loop: $V_{i1} - V_{GS1} + V_{GS2} - V_{i2} = 0$

MOSFET in sat: $I_D \approx k(V_{GS} - V_{TH})^2$

$$V_{i1} - V_{i2} = V_{GS1} - V_{GS2}$$

$$V_{id} = \left(\cancel{V_{TH}} + \sqrt{\frac{I_{D1}}{k}} \right) - \left(\cancel{V_{TH}} + \sqrt{\frac{I_{D2}}{k}} \right)$$




$$V_{id} = \sqrt{\frac{I_{D1}}{k}} - \sqrt{\frac{I_{D2}}{k}}$$



The MOSFET Differential Amplifier (2)

- Drain currents

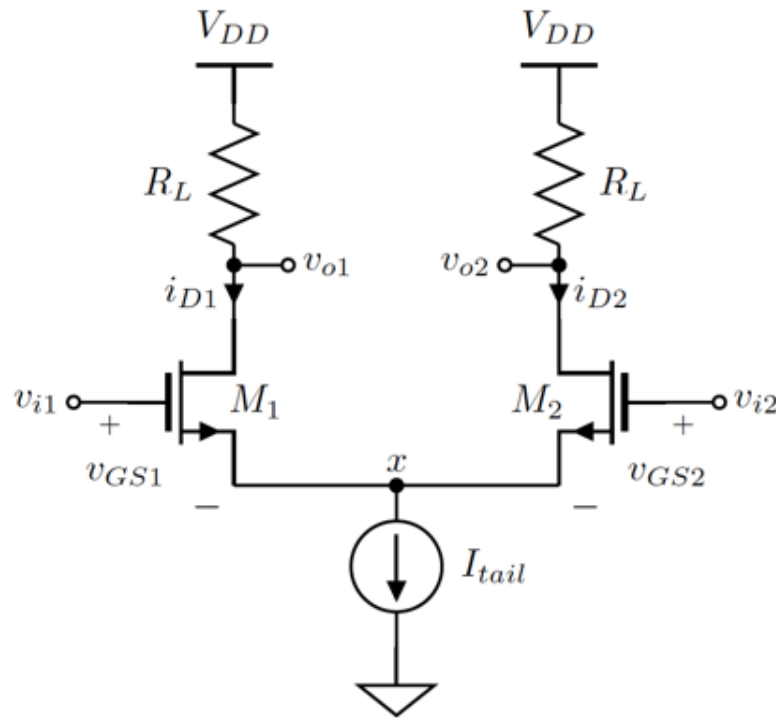

KCL at node x: $I_{tail} = I_{D1} + I_{D2}$ ← $I_{D1} = I_{tail} - I_{D2}$

Recall: $V_{id} = \sqrt{\frac{I_{D1}}{k}} - \sqrt{\frac{I_{D2}}{k}}$



$$I_{D1} = \frac{I_{tail}}{2} + V_{id} \frac{k}{2} \sqrt{\frac{2 \cdot I_{tail}}{k} - V_{id}^2} = \frac{I_{tail}}{2} + \Delta I$$

$$I_{D2} = \frac{I_{tail}}{2} - V_{id} \frac{k}{2} \sqrt{\frac{2 \cdot I_{tail}}{k} - V_{id}^2} = \frac{I_{tail}}{2} - \Delta I$$



$$V_{id} = \sqrt{\frac{I_{o1}}{k}} - \sqrt{\frac{I_{o2}}{k}} \quad (1)$$

$$I_{tail} = I_{o1} + I_{o2} \quad (2)$$

$$(V_{id})^2 = \left(\sqrt{\frac{I_{o1}}{k}} - \sqrt{\frac{I_{tail} - I_{o1}}{k}} \right)^2$$

$$V_{id}^2 = \cancel{\frac{I_{o1}}{k}} - 2 \sqrt{\frac{I_{o1} (I_{tail} - I_{o1})}{k^2}} + \frac{I_{tail} - \cancel{I_{o1}}}{k}$$

$$\left(\sqrt{I_{o1} (I_{tail} - I_{o1})} \right)^2 = \left(\frac{k}{2} \left(\frac{I_{tail}}{k} - V_{id}^2 \right) \right)^2$$

$$I_{o1} (I_{tail} - I_{o1}) = \frac{k^2}{4} \left(\frac{I_{tail}}{k} - V_{id}^2 \right)^2$$



Rearranging the previous equation:

$$I_{D1}^2 - I_{tail} \cdot I_{D1} + \frac{K^2}{4} \left(\frac{I_{tail}}{K} - V_{id}^2 \right)^2 = 0$$


Applying the quadratic formula:

$$I_{D1} = \frac{I_{tail}}{2} \pm \frac{V_{id} \cdot K}{2} \sqrt{\frac{2 I_{tail}}{K} - V_{id}^2}$$



The MOSFET Differential Amplifier (3)

- Drain currents

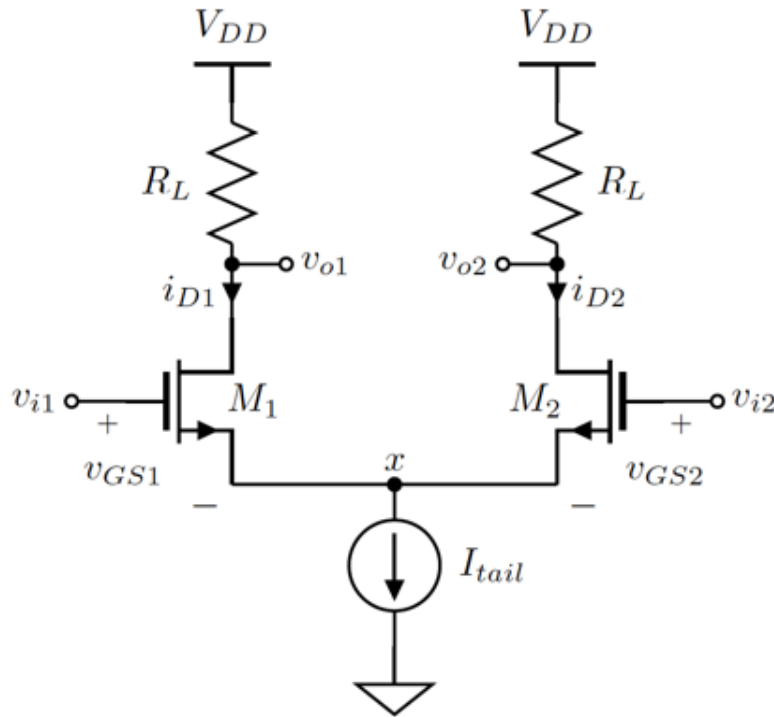

$$I_{D1} = \frac{I_{tail}}{2} + V_{id} \frac{k}{2} \sqrt{\frac{2 \cdot I_{tail}}{k} - V_{id}^2} = \frac{I_{tail}}{2} + \Delta I$$

$$I_{D2} = \frac{I_{tail}}{2} - V_{id} \frac{k}{2} \sqrt{\frac{2 \cdot I_{tail}}{k} - V_{id}^2} = \frac{I_{tail}}{2} - \Delta I$$

Note:

$$\Delta I_{max} = \frac{I_{tail}}{2}$$



$$V_{id,max} = \sqrt{\frac{I_{tail}}{k}}$$



$I_{D1,max} = I_{tail}$
 $= \frac{I_{tail}}{2}$

Beyond this, all the tail current flows in one branch



The MOSFET Differential Amplifier (4)

- The source-couple pair

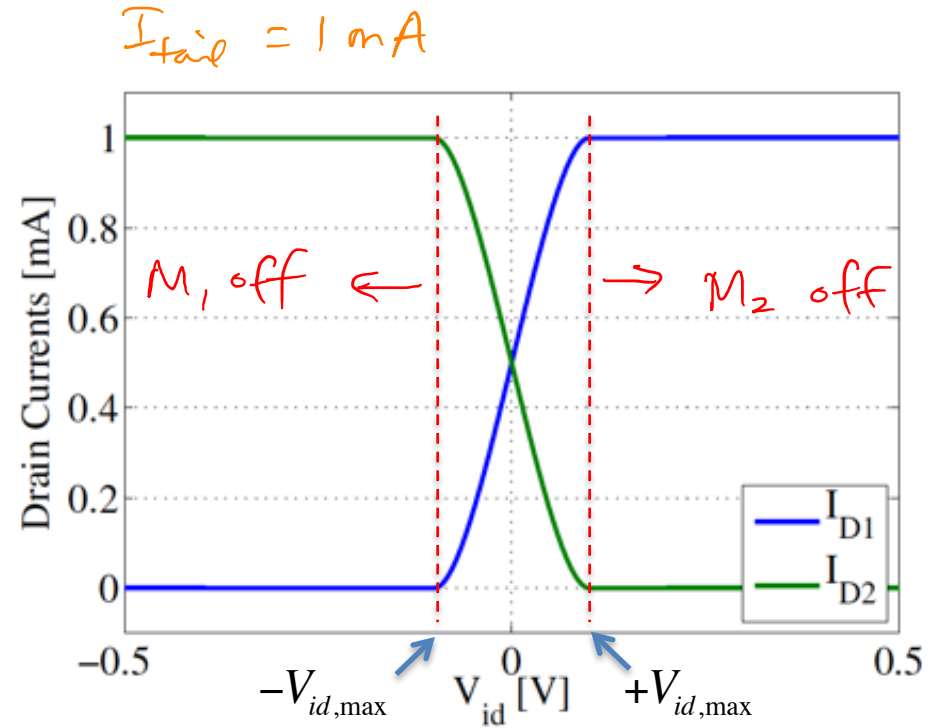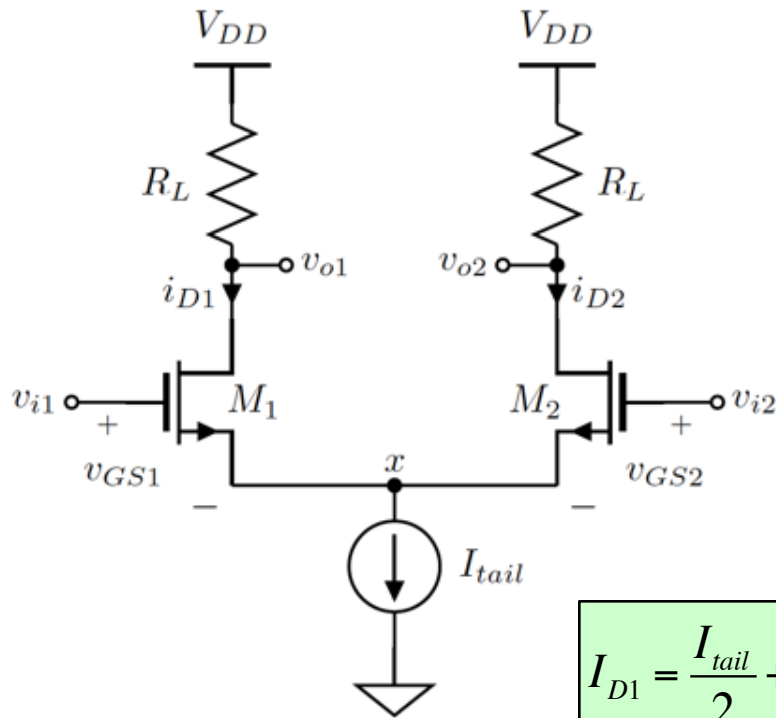


$$I_{D1} = \frac{I_{tail}}{2} + V_{id} \frac{k}{2} \sqrt{\frac{2 \cdot I_{tail}}{k} - V_{id}^2}$$

$$I_{D2} = \frac{I_{tail}}{2} - V_{id} \frac{k}{2} \sqrt{\frac{2 \cdot I_{tail}}{k} - V_{id}^2}$$



The MOSFET Differential Amplifier (5)

- Output voltage

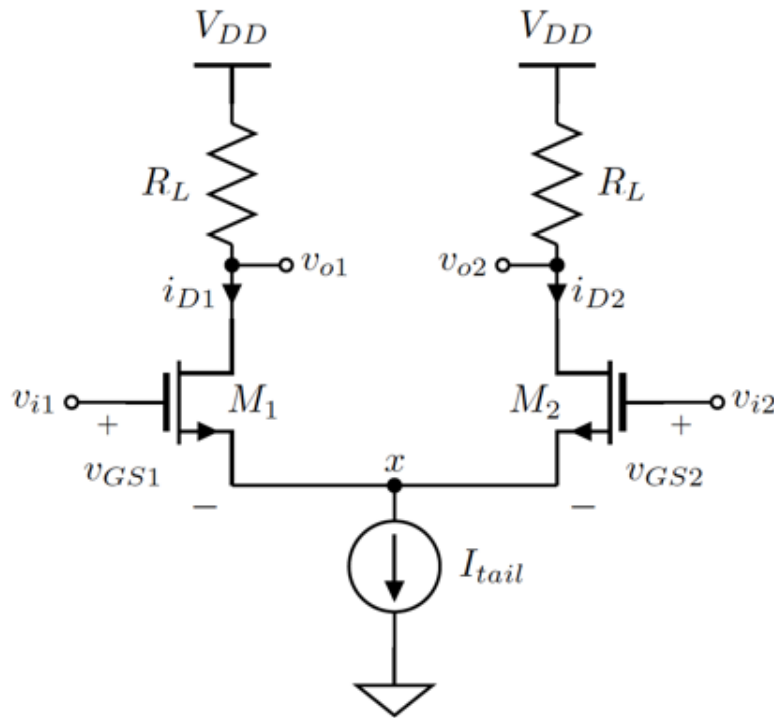

KVL at the output loop:

$$V_{o1} = V_{DD} - I_{D1} \cdot R_L$$

$$V_{o2} = V_{DD} - I_{D2} R_L$$

$$V_{od} = V_{o1} - V_{o2} = R_L (I_{D2} - I_{D1})$$

$$I_{D2} = \frac{I_{tail}}{2} - V_{id} \frac{k}{2} \sqrt{\frac{2 \cdot I_{tail}}{k} - V_{id}^2}$$

$$I_{D1} = \frac{I_{tail}}{2} + V_{id} \frac{k}{2} \sqrt{\frac{2 \cdot I_{tail}}{k} - V_{id}^2}$$





$$V_{od} = -R_L \cdot V_{id} \cdot k \sqrt{\frac{2 \cdot I_{tail}}{k} - V_{id}^2}$$



The MOSFET Differential Amplifier (6)

- Transfer characteristic

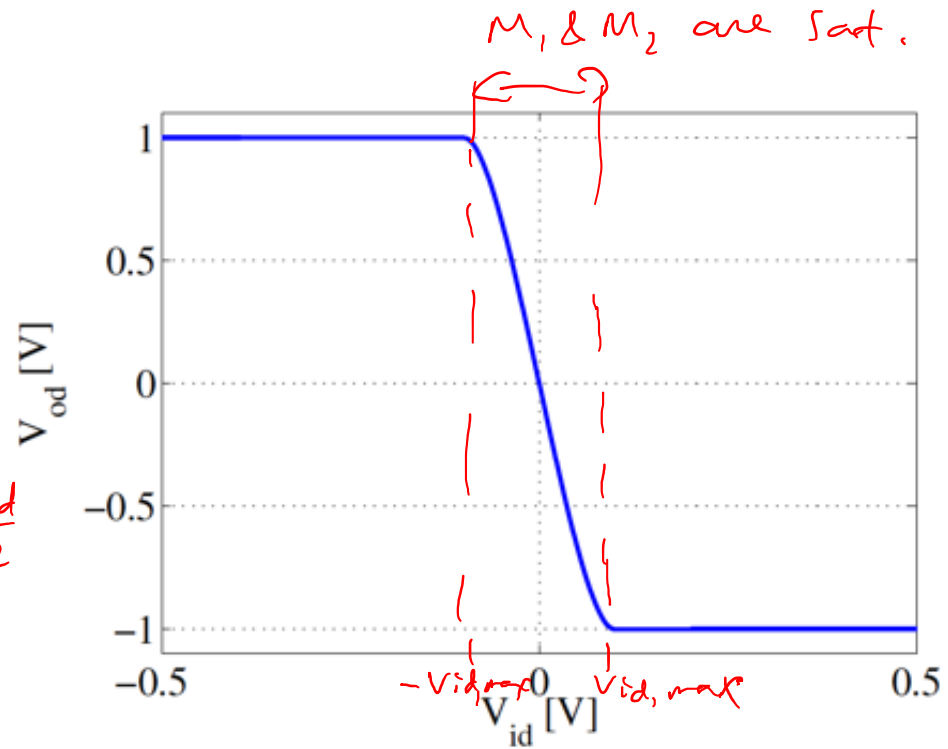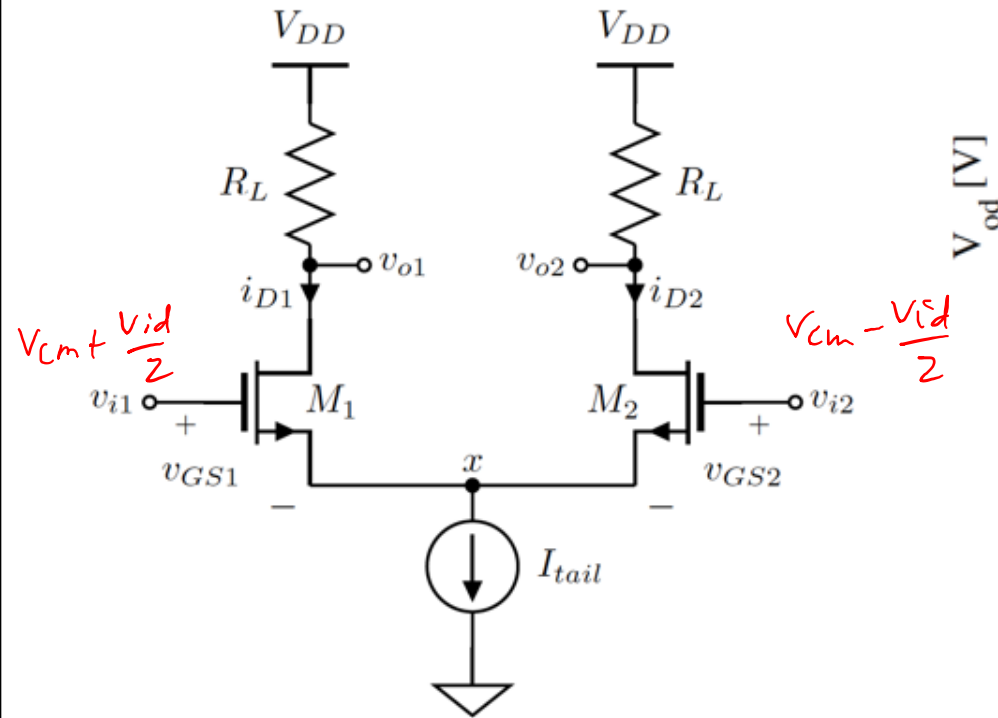


$$V_{od} = -R_L \cdot V_{id} \cdot k \sqrt{\frac{2 \cdot I_{tail}}{k} - V_{id}^2}$$



Common-Mode Input Range (1)

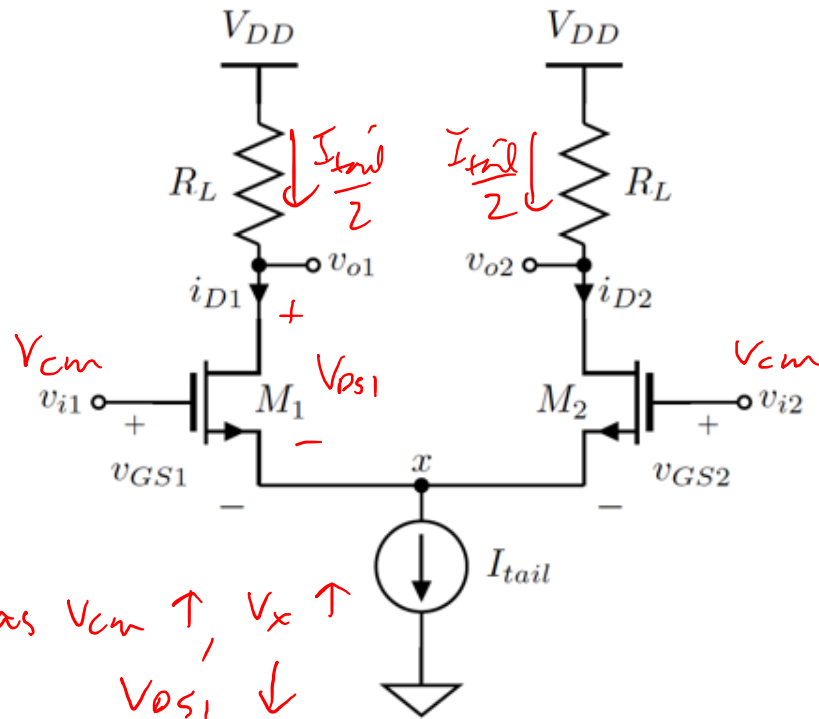- MOSFET operating region? *to keep M_1 sat, $V_{DS1} > V_{GS1} - V_{TH}$*



Assume zero differential input

$$v_{i1} = v_{i2} = V_{cm}$$

$$\text{KVL: } V_{DS1} = V_{DD} - I_{D1} R_L - V_X > V_{GS1} - V_{TH}$$

$$\text{Note: } V_X = V_{I1} - V_{GS1} \quad \frac{I_{tail}}{2}$$

V_X is controlled by the input common-mode (DC input)!

$$V_{DS1} = V_{DD} - I_{D1} R_L - V_{I1} + V_{GS1}$$



Common-Mode Input Range (2)

- MOSFET operating region?


For zero differential input: $v_{ic} = V_{I1} = V_{I2} = V_{cm}$

$$I_{D1} = I_{D2} = \frac{I_{tail}}{2}$$

For a range of common-mode inputs!


$$V_{DS1} = V_{DD} - \frac{I_{tail}R_L}{2} - V_{cm} + V_{GS1}$$
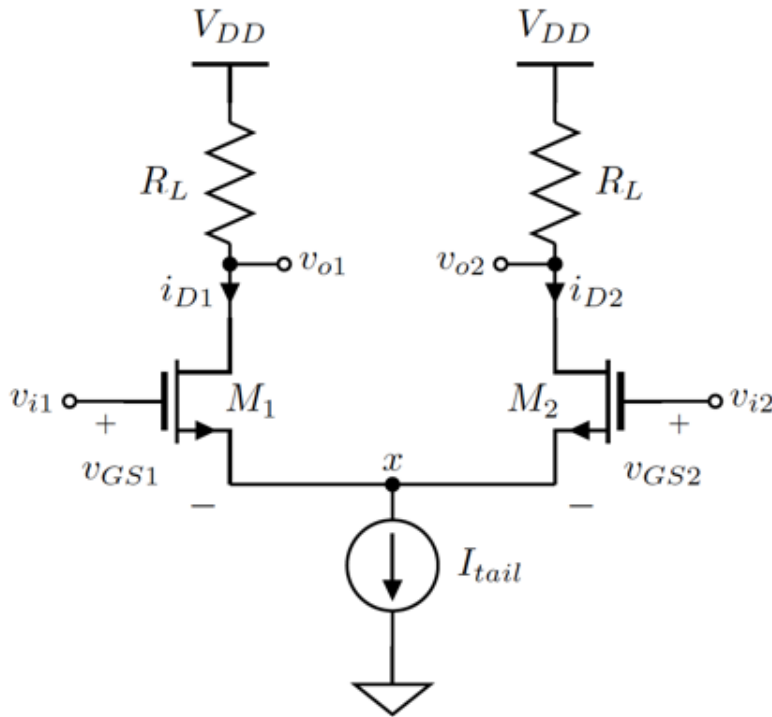
$$V_{DS1} = V_{DD} - \frac{I_{tail}R_L}{2} - V_{cm} + V_{GS1} > V_{GS1} - V_{TH}$$



Common-Mode Input Range (3)

- MOSFET operating region?

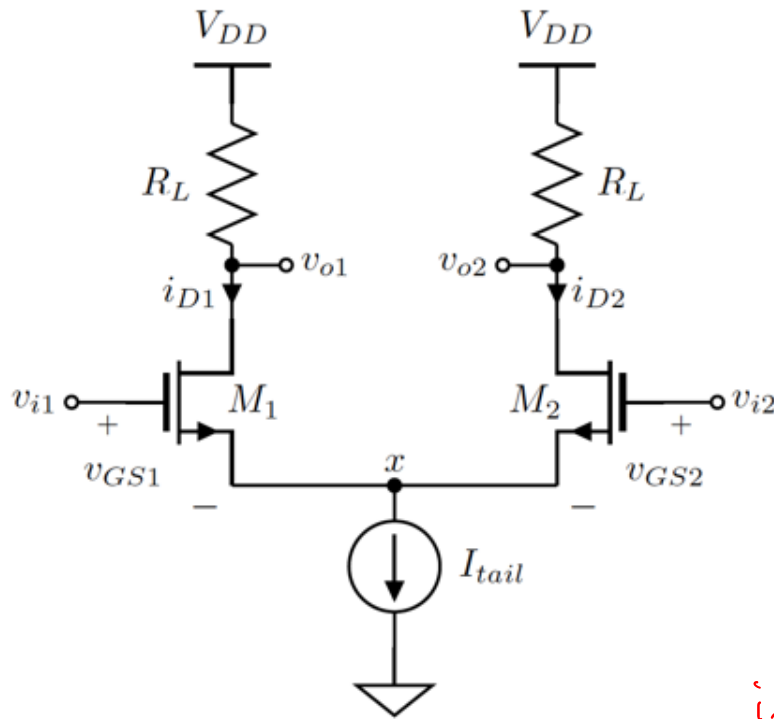

$$V_{DS1} = V_{DD} - \frac{I_{tail}R_L}{2} - V_{cm} + V_{GS1} > V_{GS1} - V_{TH}$$



$$V_{DD} - \frac{I_{tail}R_L}{2} - V_{cm} > -V_{TH}$$

$$V_{cm} < V_{DD} - \frac{I_{tail}R_L}{2} + V_{TH}$$

Maximum common-mode input voltage:


$$V_{cm,max} = V_{DD} - \frac{I_{tail}R_L}{2} + V_{TH}$$

if $V_{cm} > V_{cm,max}$, M_1 & M_2 goes to linear region.



Common-Mode Input Range (4)

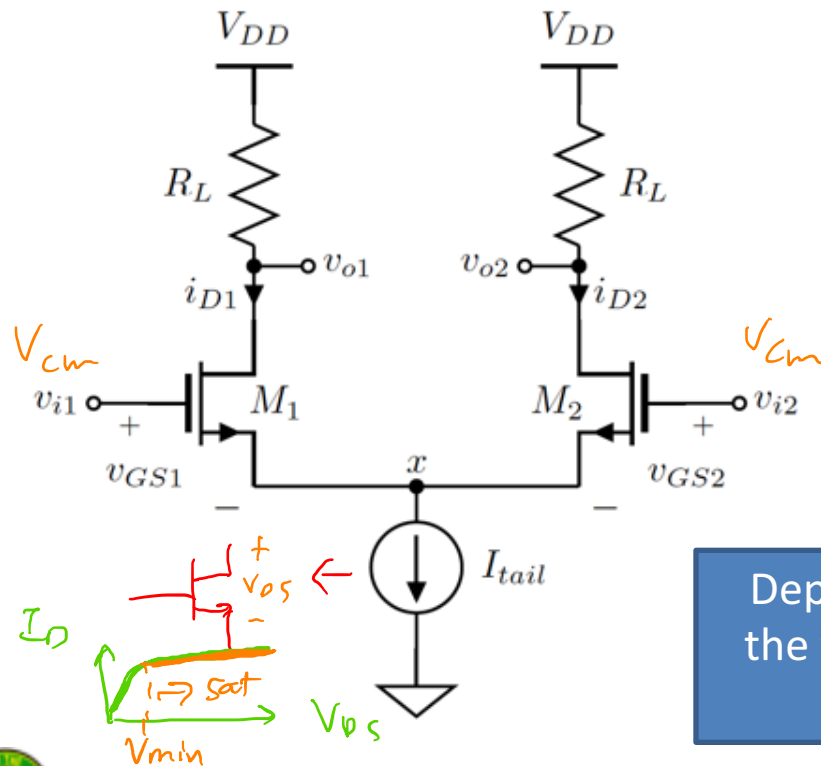- MOSFET operating region? If the tail current is not ideal $\rightarrow V_{\min}$



$$V_X = V_{I1} - V_{GS1}$$

$$V_{cm} = V_{I1} - V_{TH} - \sqrt{\frac{I_{D1}}{k}} = V_{cm} - V_{TH} - \sqrt{\frac{I_{tail}}{2 \cdot k}} > V_{\min}$$

$$V_{cm} > V_{\min} + V_{TH} + \sqrt{\frac{I_{tail}}{2 \cdot k}}$$

Minimum common-mode input voltage:

Dependent on
the tail current
source


$$V_{cm,\min} = V_{\min} + V_{TH} + \sqrt{\frac{I_{tail}}{2 \cdot k}}$$

if $V_{cm} < V_{cm,\min}$, no tail current source



Common-Mode Input Range (5)

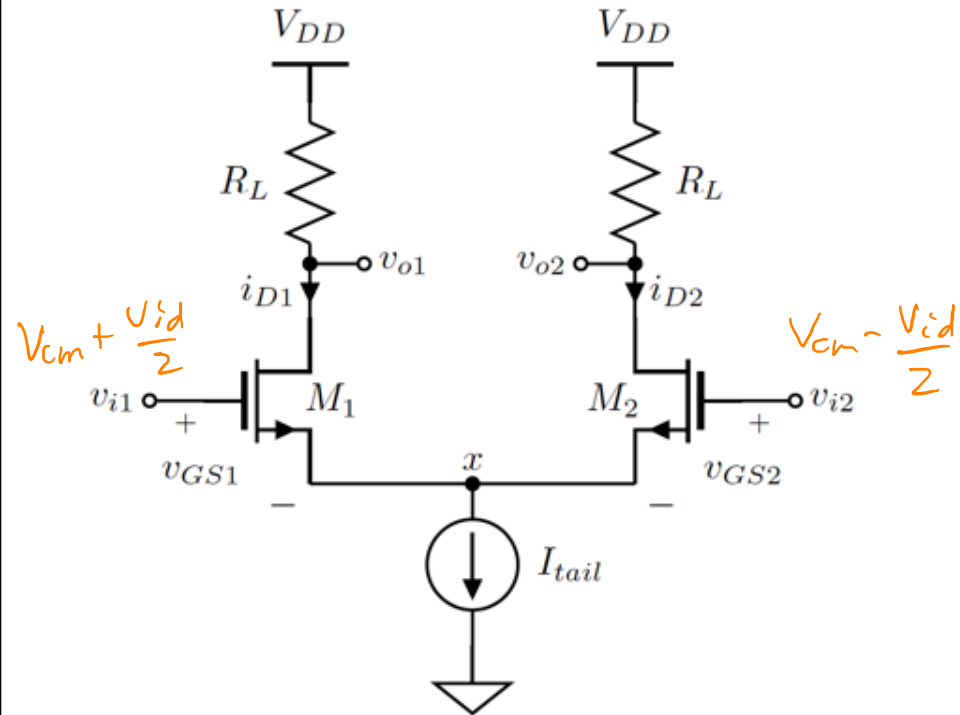- MOSFET operating region: also set by the input common-mode



$$V_{cm,max} = V_{DD} - \frac{I_{tail}R_L}{2} + V_{TH}$$

Common-mode input range

$$V_{cm,min} = V_{min} + V_{TH} + \sqrt{\frac{I_{tail}}{2 \cdot k}}$$



Next Meeting

- Differential Circuit Small Signal Analysis
- Compound Amplifiers

